

---

---

# **Cross Regulation Mechanisms** in Multiple-Output Forward and Flyback Converters

Bob Erickson and Dragan Maksimovic  
Colorado Power Electronics Center (CoPEC)  
University of Colorado, Boulder 80309-0425  
<http://ece-www.colorado.edu/~pwrelect>

# Cross Regulation Mechanisms

## in Multiple-Output Forward and Flyback Converters

---

Design of transformer in development of a multiple-output supply:

- Typically requires substantial engineering effort
- Can represent the largest risk to success of the project
- There is a need for increased understanding of the mechanisms that govern behavior of multiple-output converters

An old problem that has never been adequately addressed in the literature

- Ideal transformers are typically assumed
- Only conduction losses are modeled
- Reduced-order magnetics models do not predict observed waveforms
- Problem is considered intractable

# Objectives of this seminar

---

Explain the magnetics-associated mechanisms that govern cross-regulation in forward and flyback converters, including

- peak detection
- discontinuous conduction mode
- effects of voltage-clamp snubbers

Describe magnetics models suitable for cross-regulation analysis

Approximate analytical expressions and computer simulation


Predict small-signal dynamics

Include laboratory measurement methods and experimental examples


# Modeling Multiple-Output Converters

Cross regulation, CCM/DCM boundaries, dynamics

*Flyback converter*

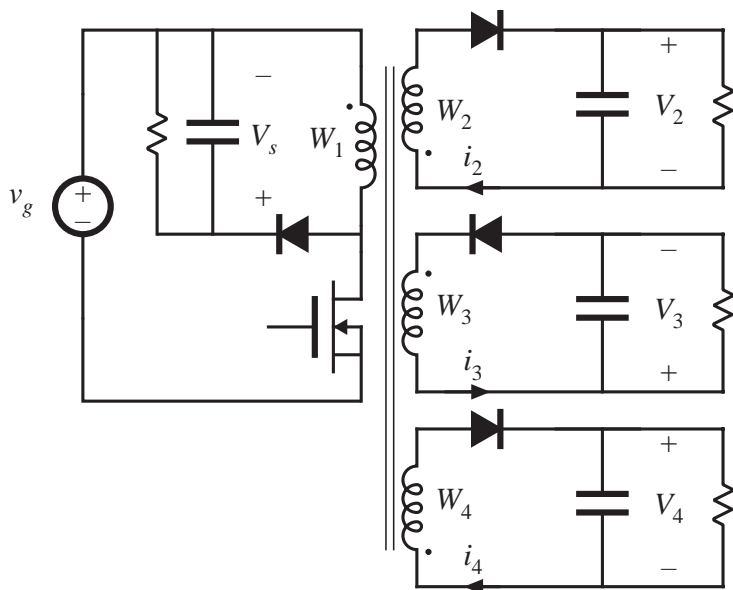

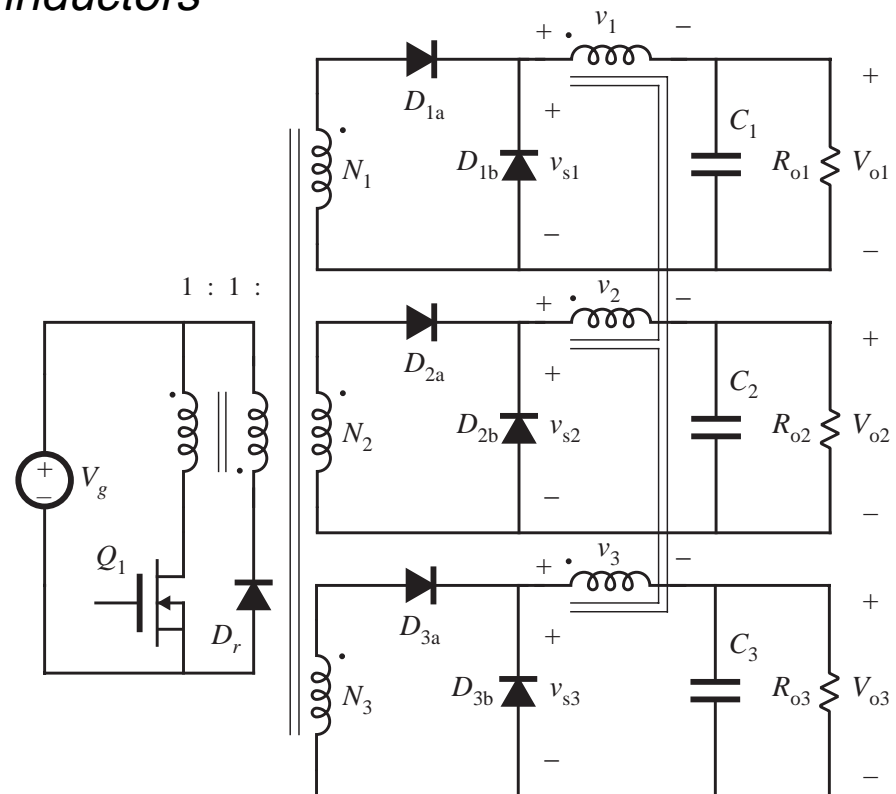*Forward converter with coupled inductors*



# Some ways to view multiple-output converters

---

## With ideal transformer

- Does not predict effect of leakage inductances on cross regulation
- Does not predict change of operating mode
- Does not predict observed converter transfer functions
- Predicts that isolated converters behave as their non-isolated parent converter topologies

## With actual transformer and its leakage inductances

- Analysis previously viewed as intractable, with no hope of gaining physical insight into cross-regulation mechanisms (not so!)
- Waveforms of isolated converters can differ significantly from their non-isolated parent topologies —new phenomena that are not observed in non-isolated versions
- Some outputs may operate in continuous conduction mode (CCM) while others operate in discontinuous conduction mode (DCM)
- To correctly predict dynamics and conduction losses: must account for leakage inductances

# Cross regulation mechanisms

---

## Conduction loss

- Diode forward-voltage drops
- Resistances of windings

## Modeling conduction loss

- Existing averaged modeling methods only partially apply

## Effect of magnetics

- Leakage inductances control shapes of winding current waveforms, especially slopes of winding currents
- Leakage inductances have a first-order effect on cross regulation, as well as dynamics, operating mode, and conduction losses

# What we would like to know and what kinds of answers to expect

We would like to express the output voltages as functions of the output currents


*For example:* three-output converter

CCM matrix equation, 3x3

$$\begin{bmatrix} V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} R_{22} & R_{23} & R_{24} \\ R_{23} & R_{33} & R_{34} \\ R_{42} & R_{42} & R_{44} \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \\ I_4 \end{bmatrix} + \begin{bmatrix} V_{o2} \\ V_{o3} \\ V_{o4} \end{bmatrix}$$

Many outputs  $\Rightarrow$  many equations

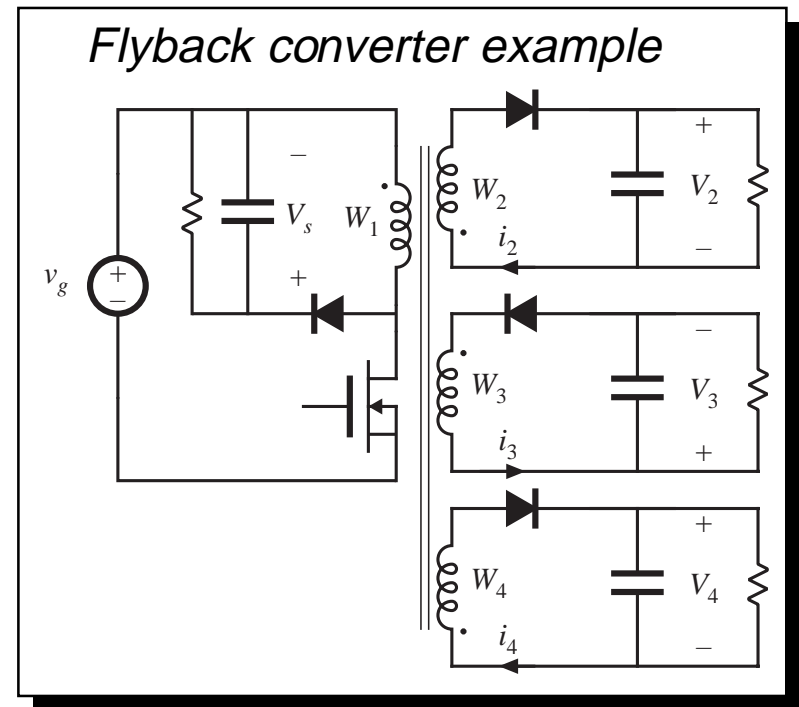Similar comments for CCM/DCM mode boundaries



# What we would like to know and what kinds of answers to expect, p. 2

---

1. A correct transformer model
  - That is well-suited to analysis of the cross-regulation problem
  - Whose parameters can be directly measured
  - That correctly predicts observed waveforms
2. Equations
  - Of output voltage regulation
  - Of mode boundaries
  - Might be best evaluated by computer when there are many auxiliary outputs
3. Insight
  - Describe fundamental operation of transformer-isolated multiple-output converters
  - Explain the physical mechanisms that lead to poor cross-regulation



# Outline of Discussion

---

1. Transformer Modeling—in context of cross regulation
  - Discussion of transformer models
  - The extended cantilever model
  - The  $n$ -port model
2. Cross Regulation in Flyback Converters
  - Qualitative behavior
  - Analytical results
  - Laboratory example
  - Discussion of strategies for improvement of cross regulation
  - Dynamic response
3. Cross Regulation in Forward Converters
  - Coupled-inductor approaches, and their qualitative behavior
  - Analytical results
  - Laboratory example
  - Discussion of strategies for improvement of cross regulation
  - Dynamic response

# 1. Multiple-Winding Transformer Modeling in the context of the cross regulation problem

---

Multiple-output converters are more than simple extensions of parent single-output nonisolated converters:

- Imperfect coupling between windings leads to problems in cross regulation, small-signal dynamics, and multiple operating modes, which have not been fully explored in the literature
- These phenomena are governed primarily by the transformer leakage inductance parameters

Need a suitable multiple-winding transformer model

- that predicts observed waveforms
- that yields insight into converter cross regulation, CCM/DCM boundaries, and dynamics
- that explains how converter performance depends on winding geometry
- that is useful in computer simulation

# Approaches to Multiple-Winding Transformer Modeling

---

## Inductance matrix

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} L_{11} & L_{12} & L_{13} & L_{14} \\ L_{12} & L_{22} & L_{23} & L_{24} \\ L_{13} & L_{23} & L_{33} & L_{34} \\ L_{14} & L_{24} & L_{34} & L_{44} \end{bmatrix} \frac{d}{dt} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}$$

- General
- Reduces the circuit to matrix equations
- Numerically ill-conditioned in tightly-coupled case
- Complete model of four-winding transformer contains ten parameters

# Equivalent-Circuit Approaches to Multiple-Winding Transformer Modeling

---

## **Reduced-order equivalent circuit**

- Physically based
- Not general—Does not predict observed waveforms of flyback converter
- Difficult to apply to some geometries (for ex., toroidal)

## **Full-order equivalent circuits**

- Allow circuit-oriented analysis of converter
- General

Flyback example


# Physical-Based Reduced-Order Model

## 4 winding transformer example


Four-winding transformer example

Physical modeling approach:  
equivalent circuit contains series-  
connected leakage inductances

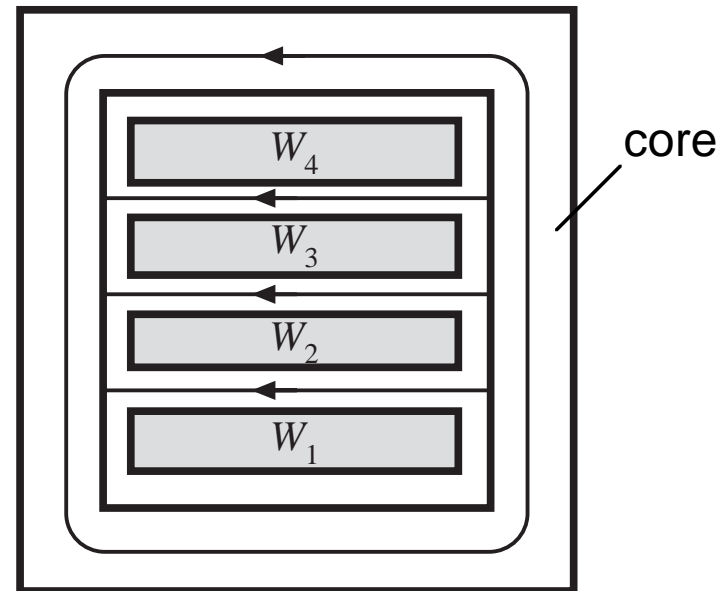
Reduced-order approximation  
based on winding geometry



Equivalent circuit proposed in [12]:

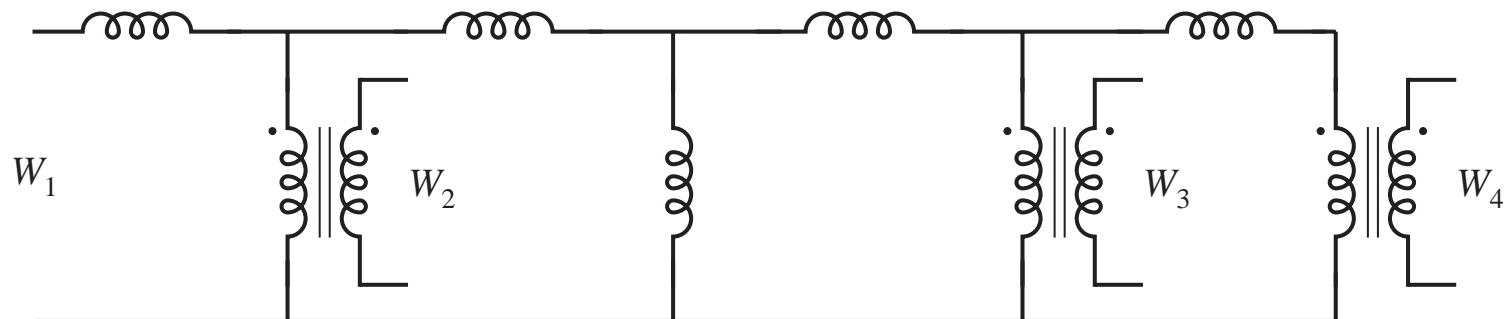
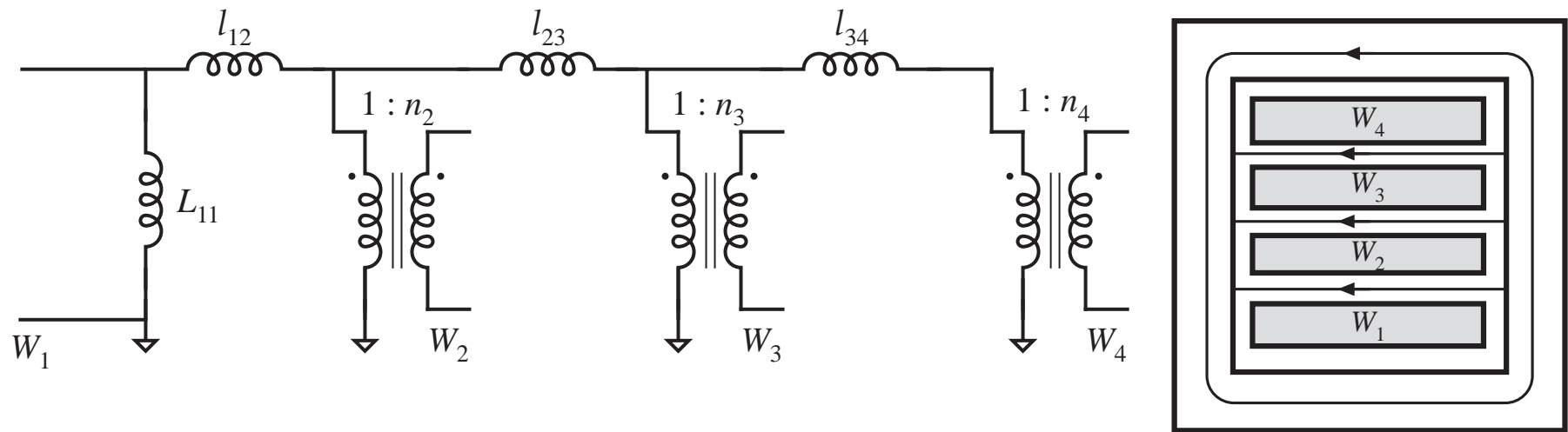
# An Electrically-Equivalent Form of the reduced-order model




- Contains seven independent parameters
- Inductance matrix of four-winding transformer contains ten independent parameters
- Is this model sufficient?

# A Thought Experiment

using the 4-winding reduced-order model

---

---

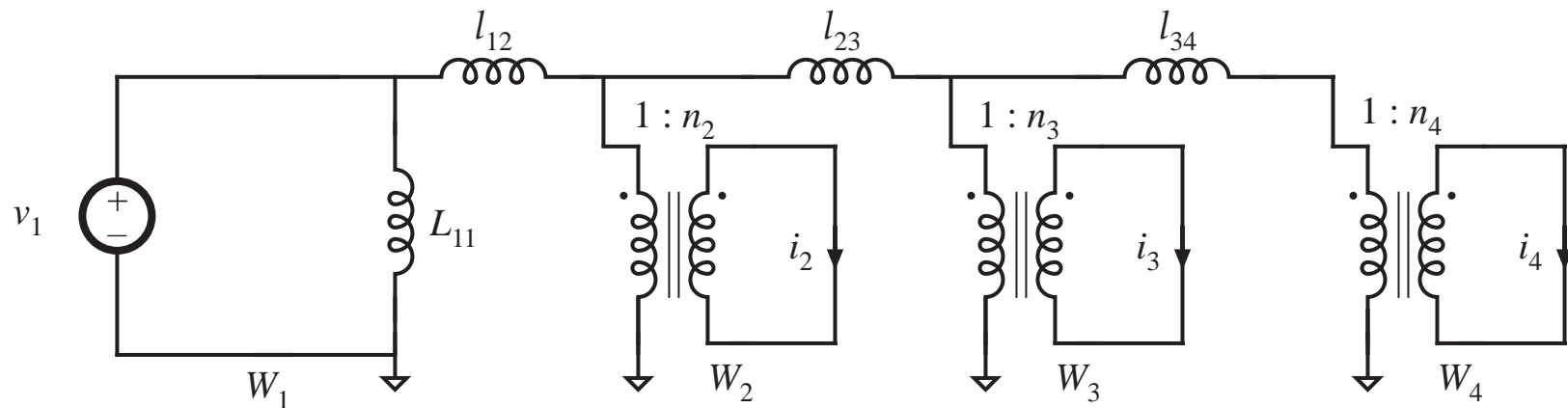

Apply a voltage to winding 1, short windings 2, 3, and 4. Measure short-circuit currents in each winding.


Model predicts that  $i_3$  and  $i_4$  are zero.

# A Full-Order Model

## Extended Cantilever Model

---


---

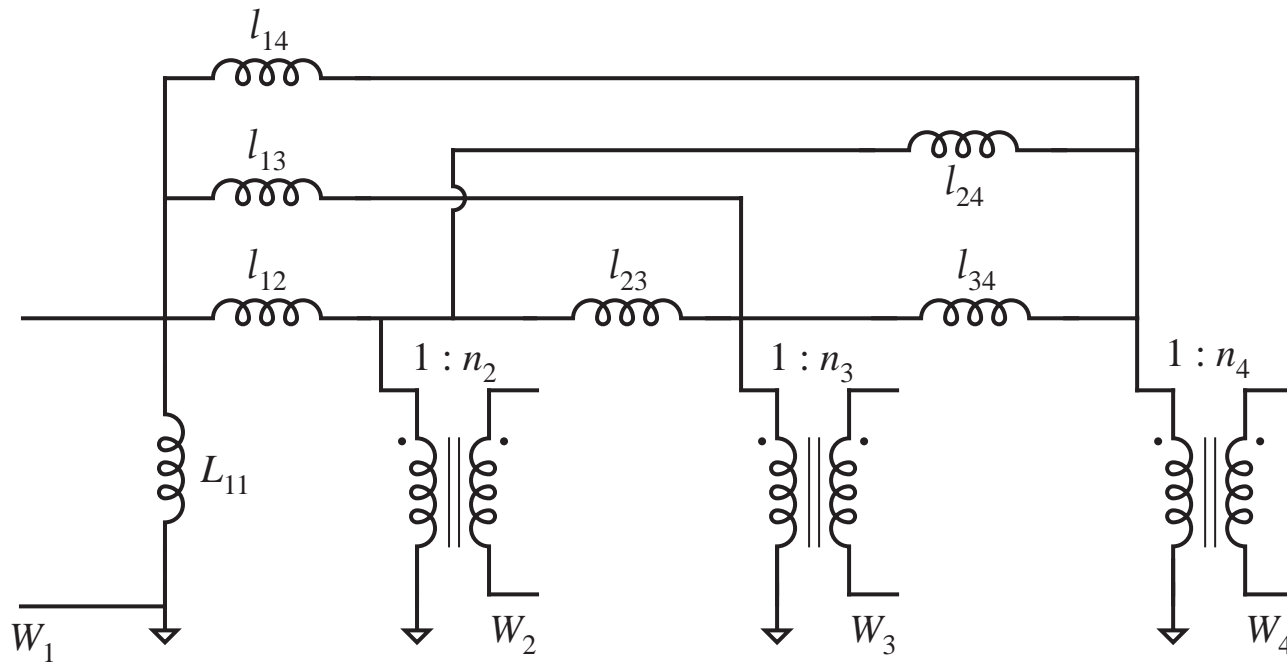

Include “leakage inductances” between each winding



# Thought Experiment—Revisited

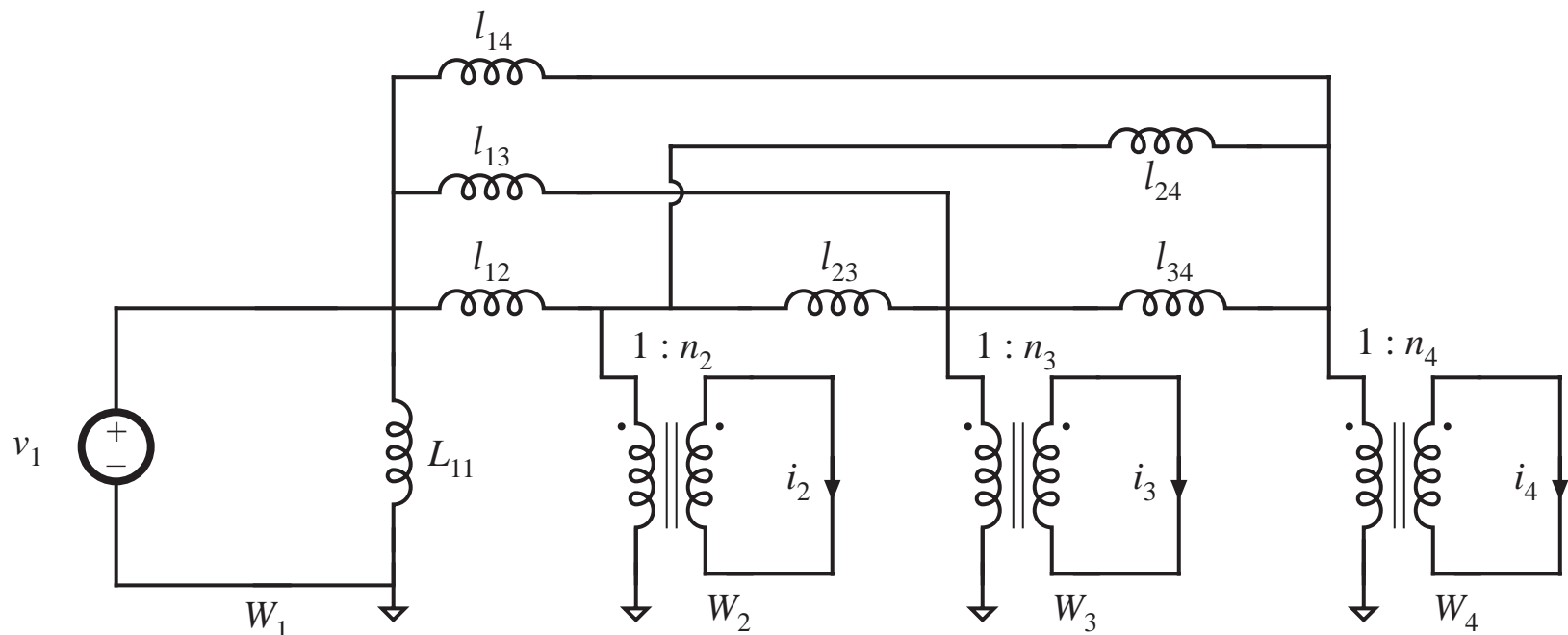

Again apply a voltage to winding 1, short windings 2, 3, and 4. Measure short-circuit currents in each winding.


Model predicts nonzero  $i_3$  and  $i_4$ .

# Discussion

---

- It is always possible to connect a transformer such that a reduced-order model does not predict the actual waveforms
- Are such connections actually encountered in multiple-output converters?

# Flyback converter circuit

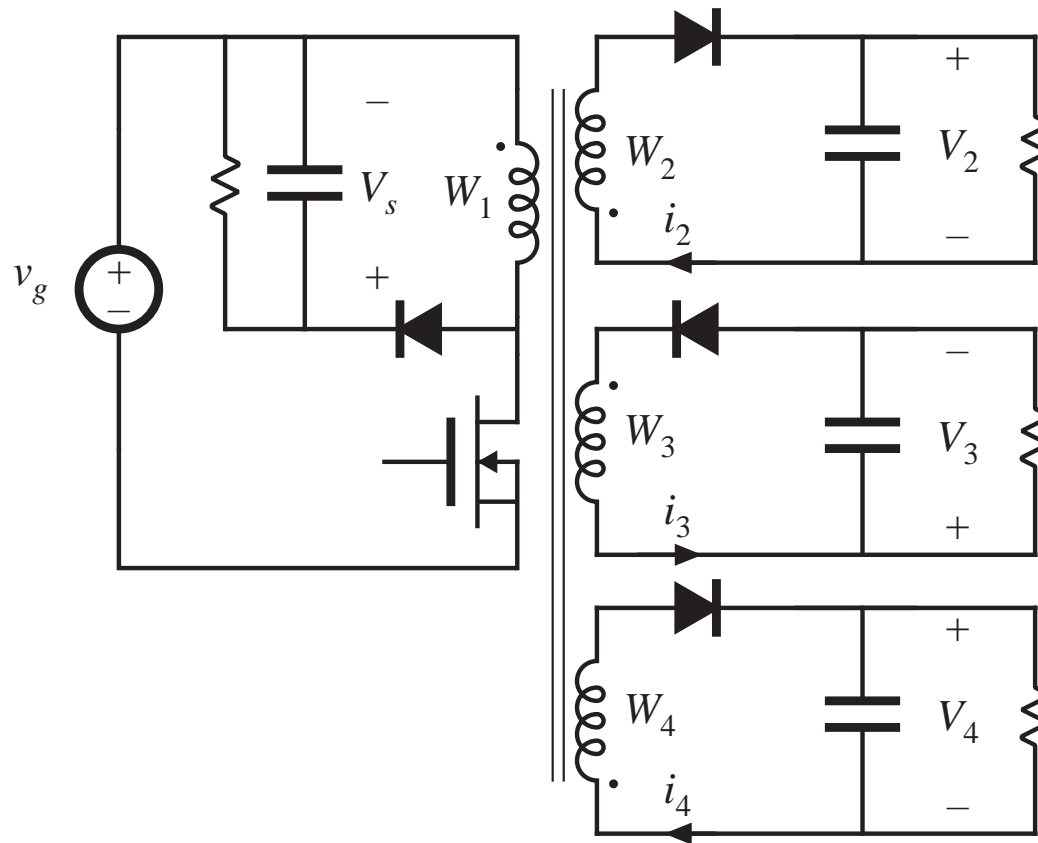


Three outputs

Primary-side voltage-clamp snubber

Cross-regulation is strongly influenced by *commutation interval*, when transistor turns off and magnetizing current shifts to secondary windings
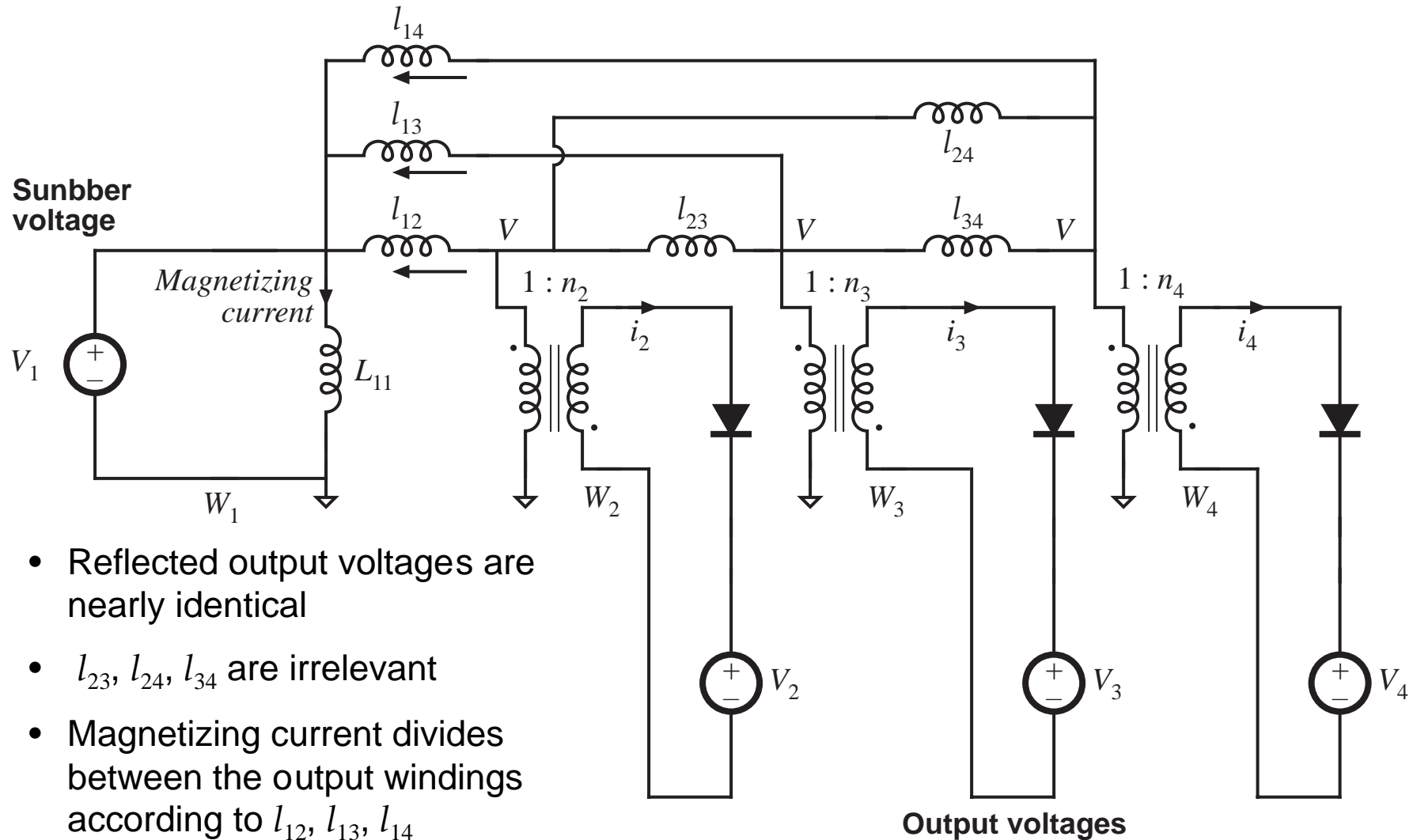
# Commutation Interval


Flyback converter example—similar to thought experiment



- Reflected output voltages are nearly identical
- $l_{23}$ ,  $l_{24}$ ,  $l_{34}$  are irrelevant
- Magnetizing current divides between the output windings according to  $l_{12}$ ,  $l_{13}$ ,  $l_{14}$
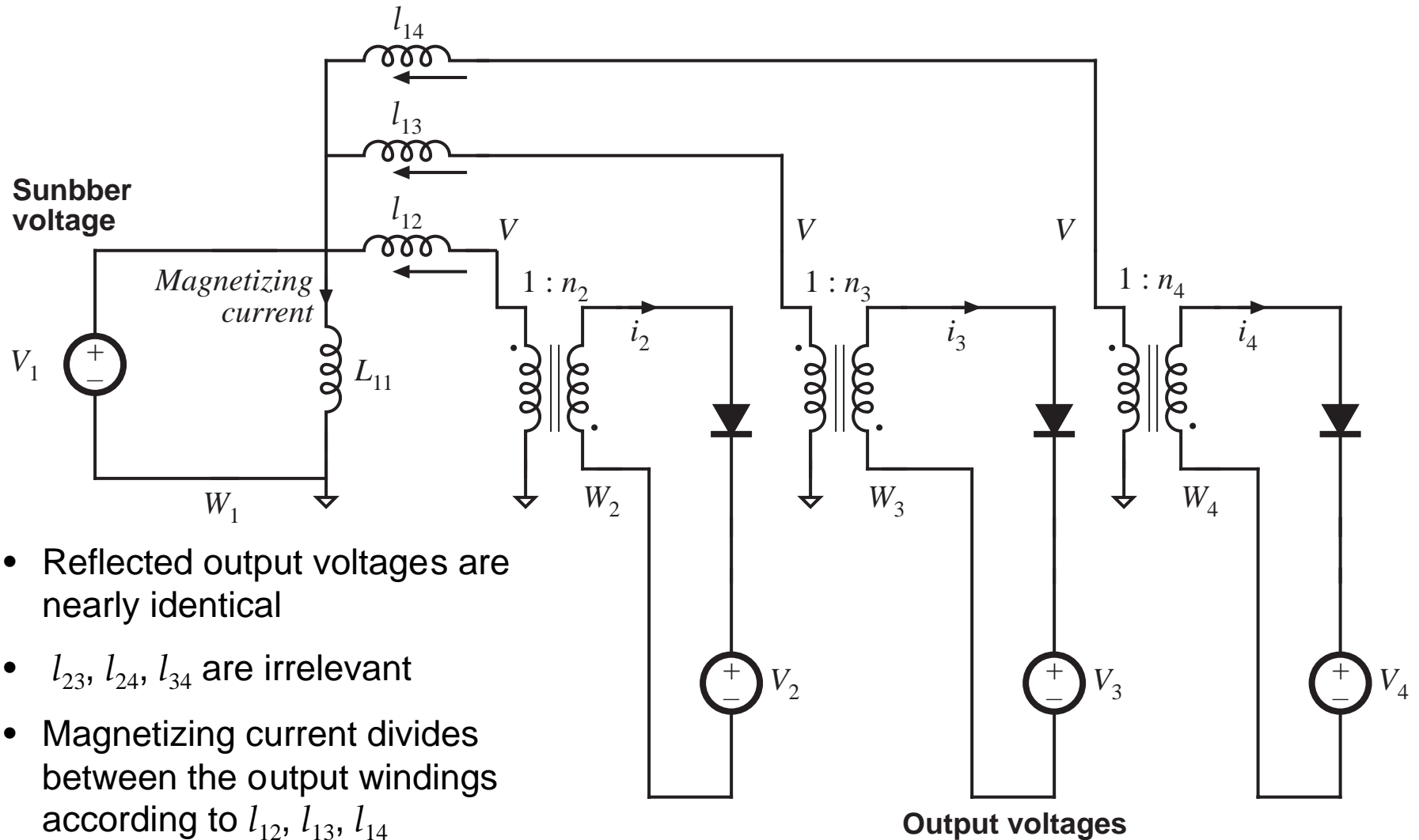
# Commutation Interval

Flyback converter example—similar to thought experiment



- Reflected output voltages are nearly identical
- $l_{23}$ ,  $l_{24}$ ,  $l_{34}$  are irrelevant
- Magnetizing current divides between the output windings according to  $l_{12}$ ,  $l_{13}$ ,  $l_{14}$

# Conclusion: Reduced-Order Modeling


---

- Approximate reduced-order model derived via physical approach does not correctly predict behavior of multiple-output flyback converter
- Approximations must not be based solely on winding geometry
- Application and circuit behavior must be considered before attempting to reduce the order of the model
- Need a suitable full-order model


# Transformer Equivalent Circuit Models

Two-winding transformer models


T

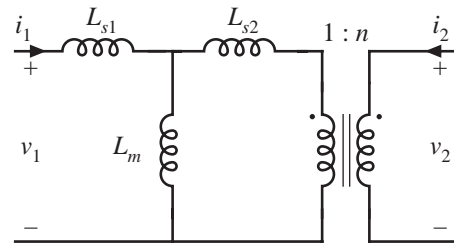


Pi

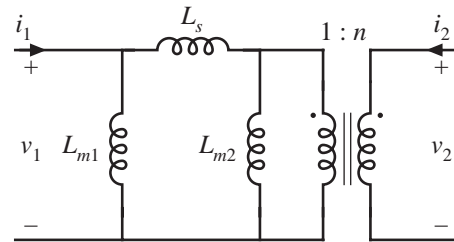

Cantilever

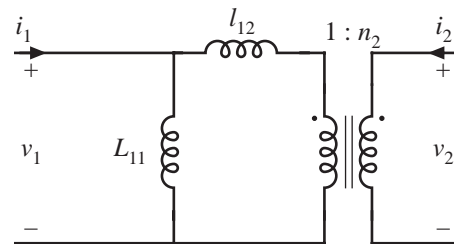


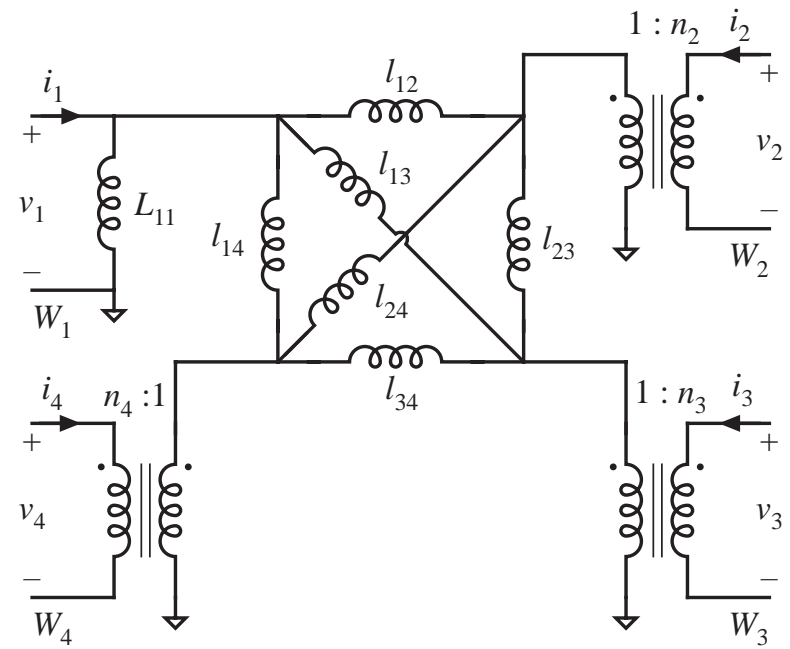Extension of cantilever model to four-winding case




# $N$ -winding transformer models used here


$n$ -winding transformer

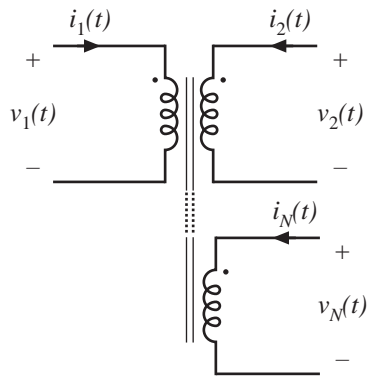

Extended cantilever model

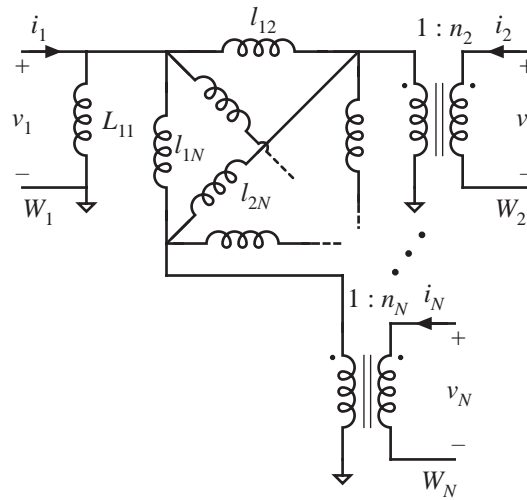

$n$ -port model

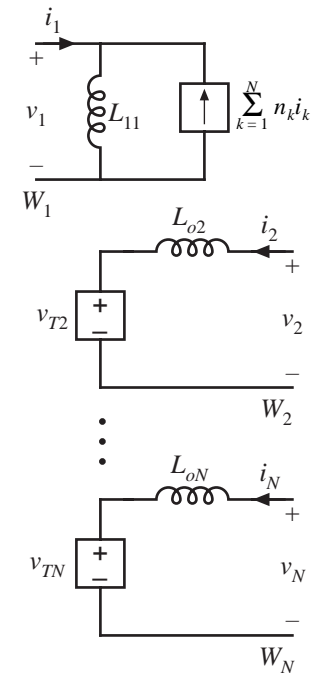



# Relationship between inductance matrix and extended cantilever model

The inductance matrix:

$$\mathbf{v} = s\mathbf{L}\mathbf{i}$$

$$\mathbf{L} = \{L_{jk}\} \quad \text{inductance matrix}$$

$$\mathbf{B} = \mathbf{L}^{-1} = \{b_{jk}\} \quad \text{inverse inductance matrix}$$


For an  $N$ -winding transformer, contains  $N(N + 1)/2$  independent parameters

Extended cantilever model also contains  $N(N + 1)/2$  independent parameters, related to the inductance matrix as follows:

$$L_{11} = L_{11}$$


$$n_j = \frac{L_{1j}}{L_{11}}$$

$$l_{jk} = -\frac{1}{n_j n_k b_{jk}}$$

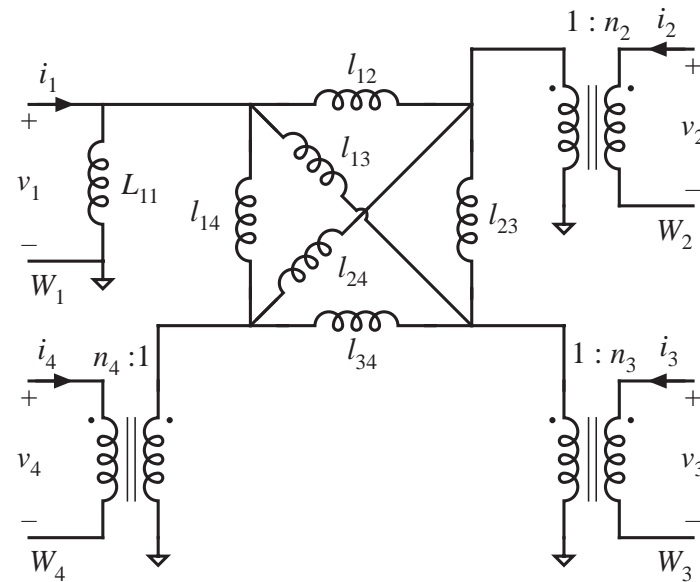
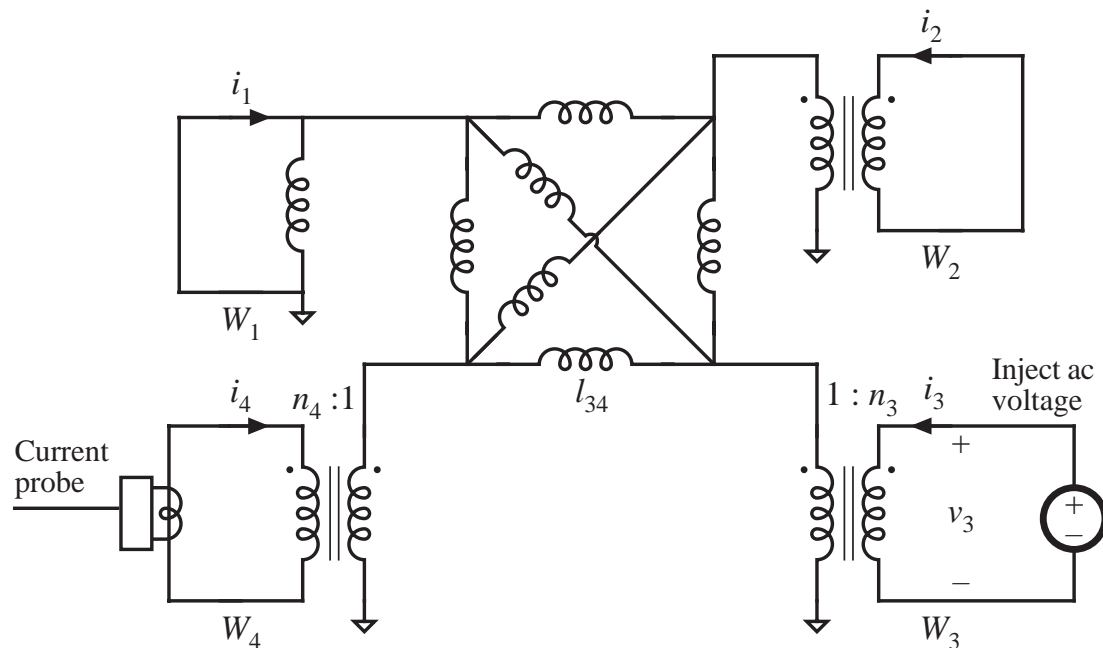
# Measurement of Leakage Inductance Parameters

To measure leakage inductance parameter  $l_{34}$



- Measurement frequency must be sufficiently high, so that leakage reactance  $\gg$  winding resistance

- Inject ac voltage at winding 3
- Short all other windings
- Measure current in winding 4


- $l_{34}$  is given by

$$l_{jk} = \frac{v_j(s)}{sn_j n_k i_k(s)}$$

- Must carefully observe polarities, since  $l_{jk}$  can be negative

# Measurement of Effective Turns Ratios

To measure effective turns ratio  $n_3$

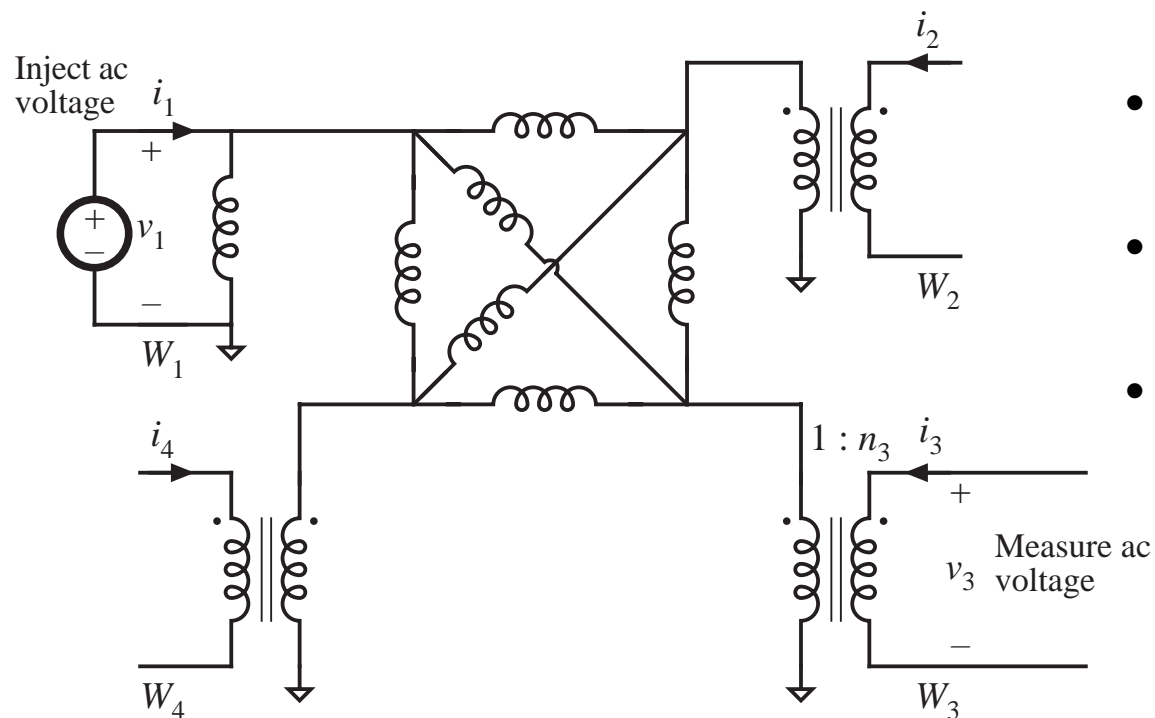

- Inject ac voltage at winding 1
- Open-circuit all other windings
- Measure voltage in winding 3
- $n_3$  is given by

$$n_k = \frac{v_k}{v_1}$$


# The $N$ -Port Transformer Model

- Useful in deriving expressions for current ripples and zero-ripple condition, and for computer simulation
- Primary winding is represented by its current-controlled Norton equivalent
- Each secondary is modeled by a voltage-controlled Thevenin equivalent
- Secondary winding output inductance:

$$L_{ok} = n_k^2 \left( l_{1k} \parallel l_{2k} \parallel \dots \parallel l_{(k-1)k} \parallel l_{(k+1)k} \parallel \dots \parallel l_{Nk} \right)$$

- Secondary winding controlled voltage source:
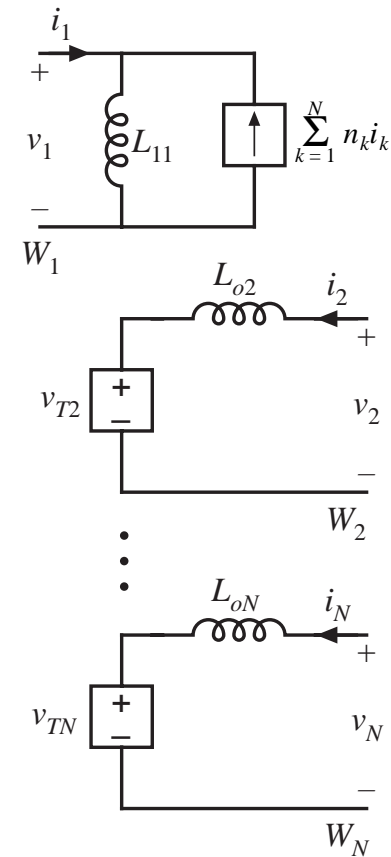
$$v_{Tk} = \frac{L_{ok}}{n_k l_{1k}} v_1 + \frac{L_{ok}}{n_k n_2 l_{2k}} v_2 + \dots + \frac{L_{ok}}{n_k n_{k-1} l_{(k-1)k}} v_{k-1} \\ + \frac{L_{ok}}{n_k n_{k+1} l_{(k+1)k}} v_{k+1} + \dots + \frac{L_{ok}}{n_k n_N l_{Nk}} v_N$$



# Flyback Transformer Example


Experimental example:

Three-output flyback converter

Application specifications:


- Input: 30 V (winding  $W_1$ )
- Output: +12 V (winding  $W_2$ )
- Output: -12 V (winding  $W_3$ )
- Output: +3.3 V (winding  $W_4$ )

Winding and core geometry

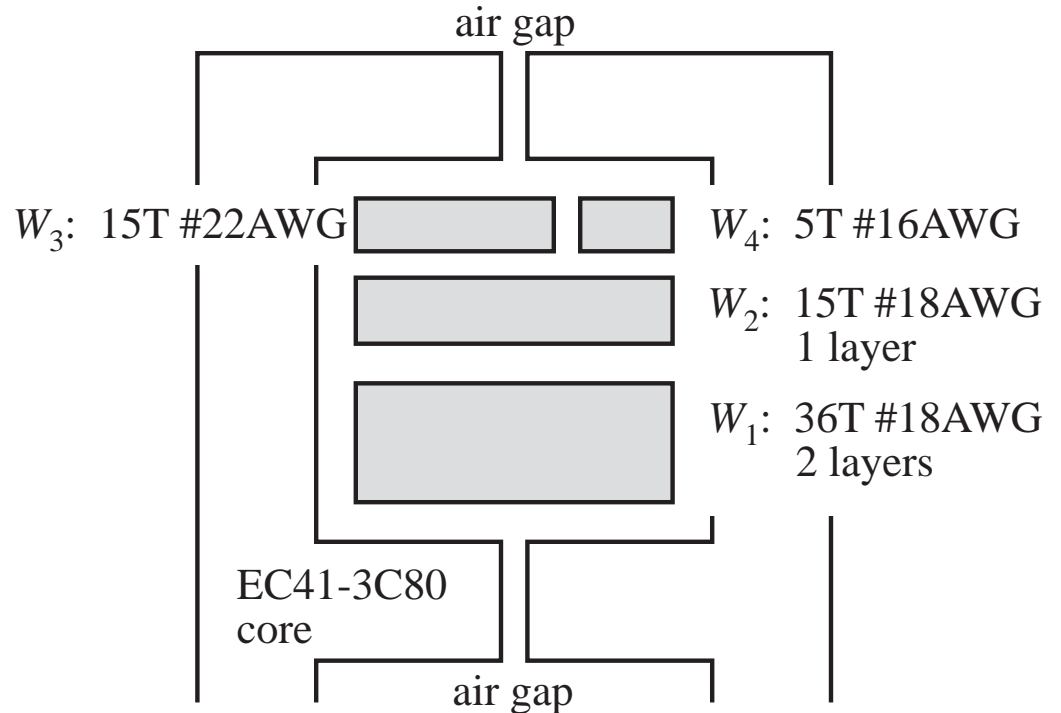
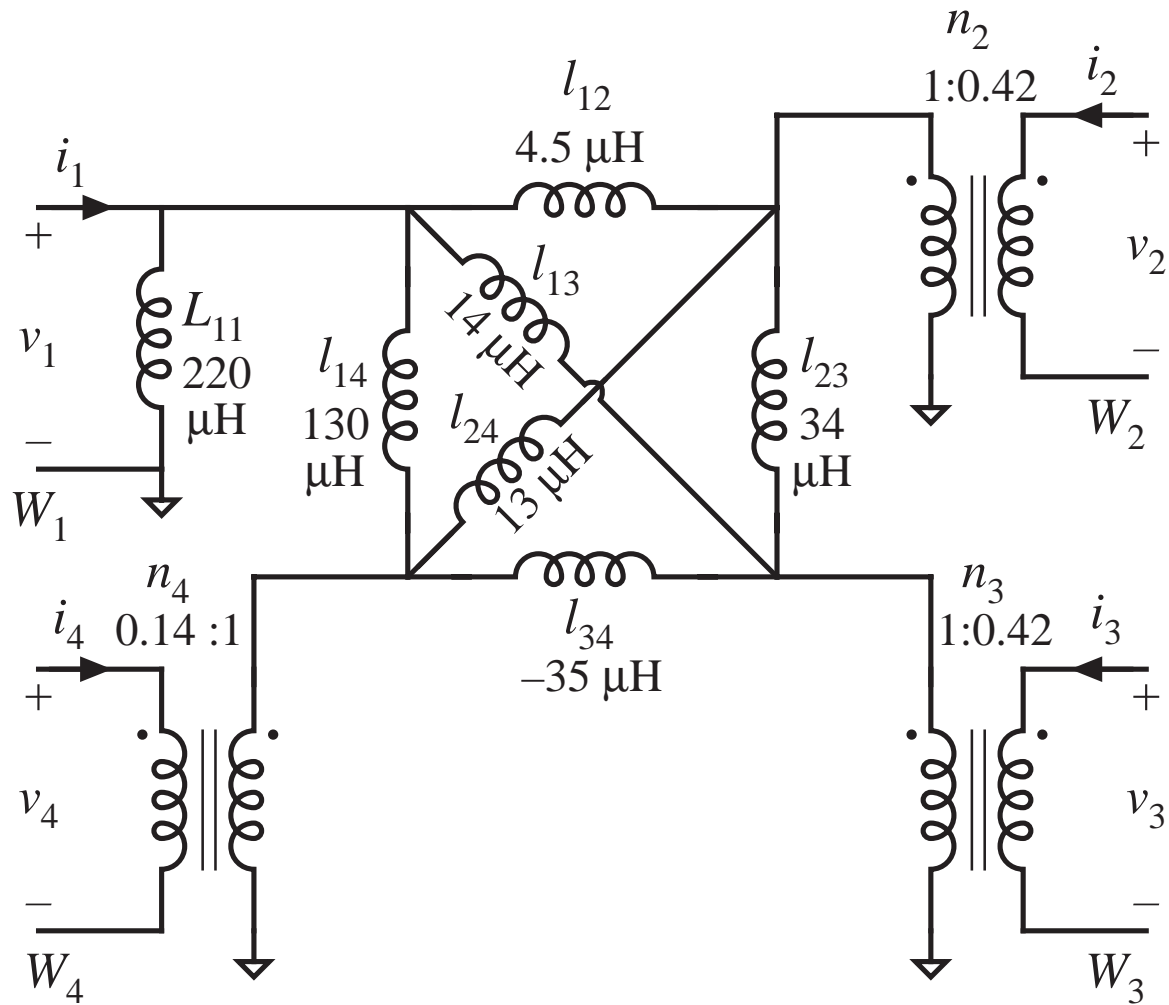
# Measured Model

Flyback transformer extended cantilever model




# Negative $l_{34}$

Directions of induced winding currents, when winding  $W_3$  is driven and windings  $W_1$ ,  $W_2$ , and  $W_4$  are shorted

Negative  $l_{34}$  indicates reversal of polarity of induced current  $i_4$

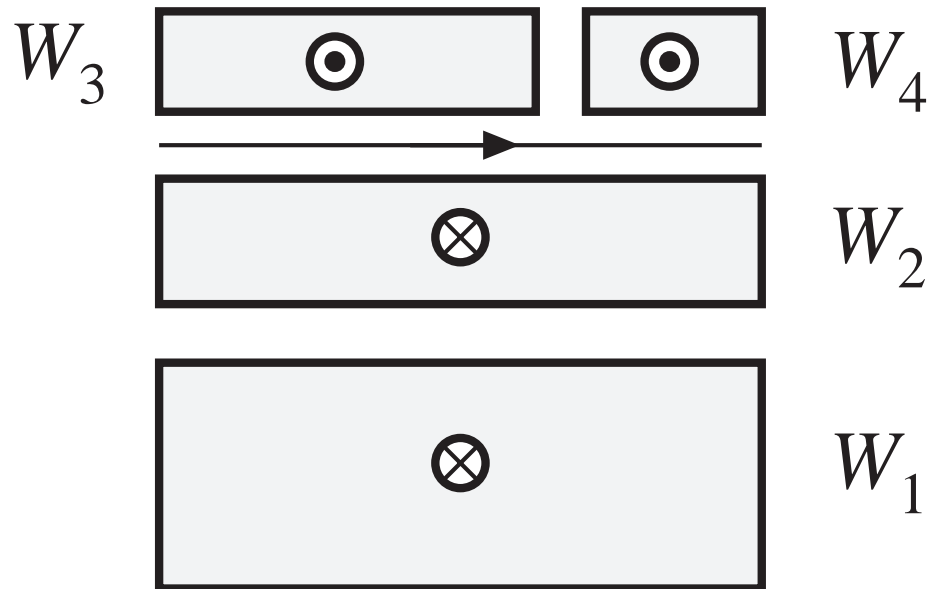Side-by-side winding geometry leads to negative leakage parameter



# Measured $n$ -port parameter model

## Flyback transformer example

$N$ -port parameters are computed from extended cantilever model parameters as follows:


*Winding output impedance*

$$L_{ok} = n_k^2 \left( l_{1k} || l_{2k} || \dots || l_{(k-1)k} || l_{(k+1)k} || \dots || l_{Nk} \right)$$

*Voltage-controlled voltage source*

$$v_{Tk} = \frac{L_{ok}}{n_k l_{1k}} v_1 + \frac{L_{ok}}{n_k n_2 l_{2k}} v_2 + \dots + \frac{L_{ok}}{n_k n_{k-1} l_{(k-1)k}} v_{k-1} \\ + \frac{L_{ok}}{n_k n_{k+1} l_{(k+1)k}} v_{k+1} + \dots + \frac{L_{ok}}{n_k n_N l_{Nk}} v_N$$

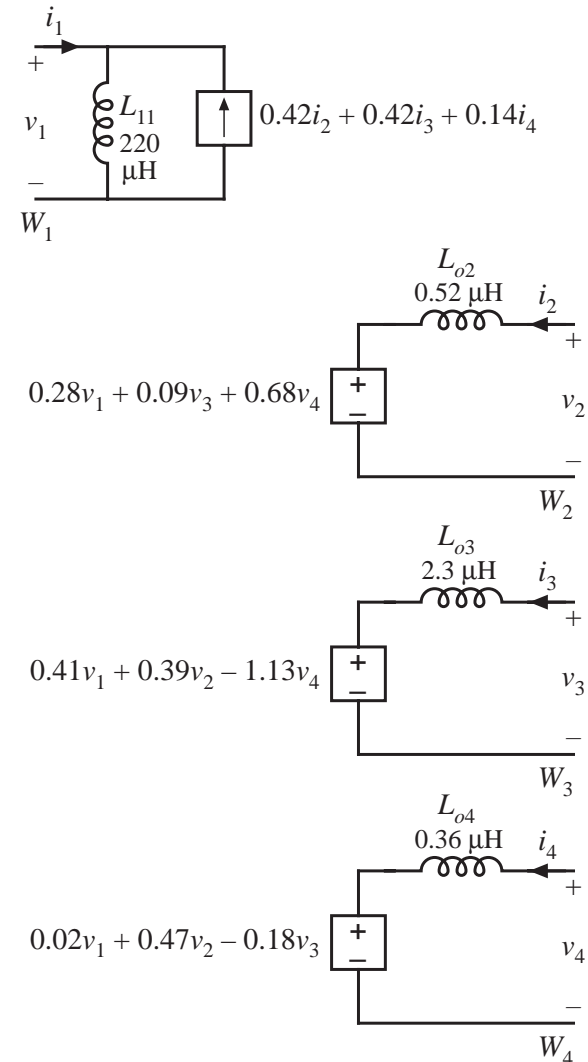Alternatively, these parameters could be directly measured





# Summary—Part 1


---

- Extended cantilever model, and  $N$ -port model, correctly predict observed waveforms of multiple-output converters
- These models are full-order: the number of independent parameters is the same as in the inductance matrix, and the parameters are directly related to the entries of the inverse inductance matrix
- Each model parameter can be directly measured, and the model can be checked using several other measurements
- Reduced-order models generally do not predict the observed phenomena of multiple-output converters


**Next:** the mechanisms of cross-regulation in flyback converters can be explained using the extended cantilever model
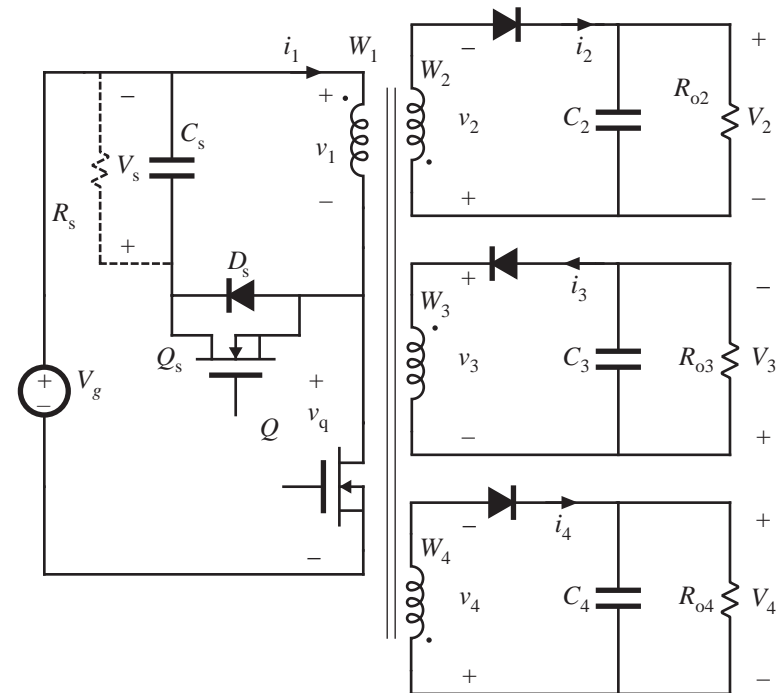
## 2. Cross-Regulation in Flyback Converters

- Widespread applications, usually at low to medium power levels
- Multiple-output flyback transformer design is usually based on practical experience, trial and error
- Operation, steady-state and dynamic properties are strongly affected by transformer leakage inductances
- Modeling is considered intractable (especially if the number of outputs exceeds two)
- Very few analytical results or models are available to aid the designer
- Poor cross-regulation is often observed in practice



# Flyback Converter Circuit

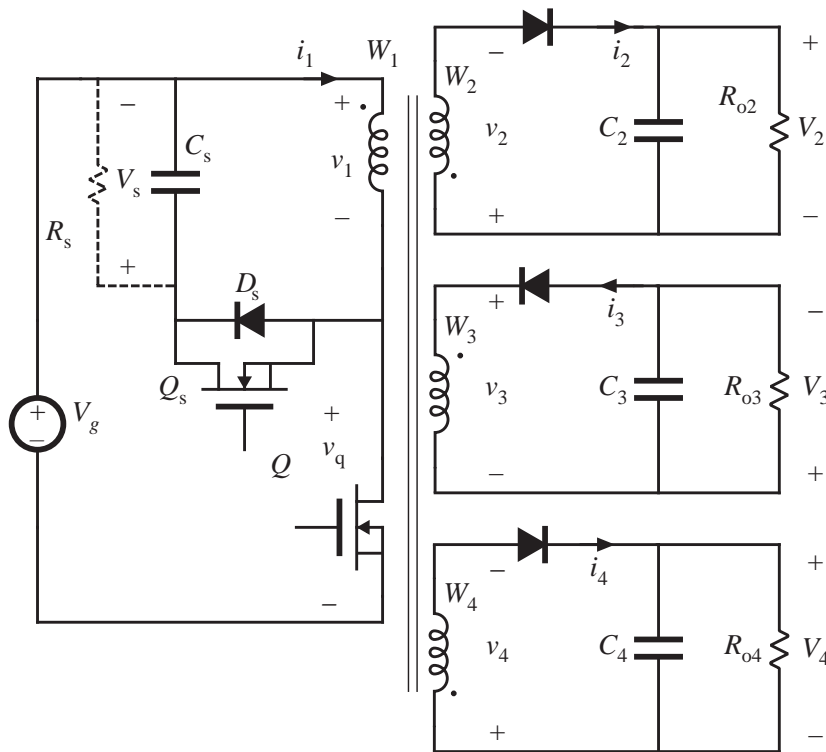

Example: three outputs

Two snubber configurations:

- Passive voltage-clamp snubber:  $D_s, C_s, R_s$
- Active-clamp snubber:  $Q_s/D_s, C_s$

Cross-regulation affected by:


- Conduction losses
- Transformer leakage inductances

# Objectives

---

- Explain qualitative behavior using the extended cantilever magnetics model for the transformer
- Derive general steady-state analytical model capable of predicting static cross-regulation for any number of outputs and arbitrarily complex magnetics configuration
- Compare model predictions with experimental results
- Discuss model implications and strategies for improvement of static cross regulation
- Point to dynamic response considerations
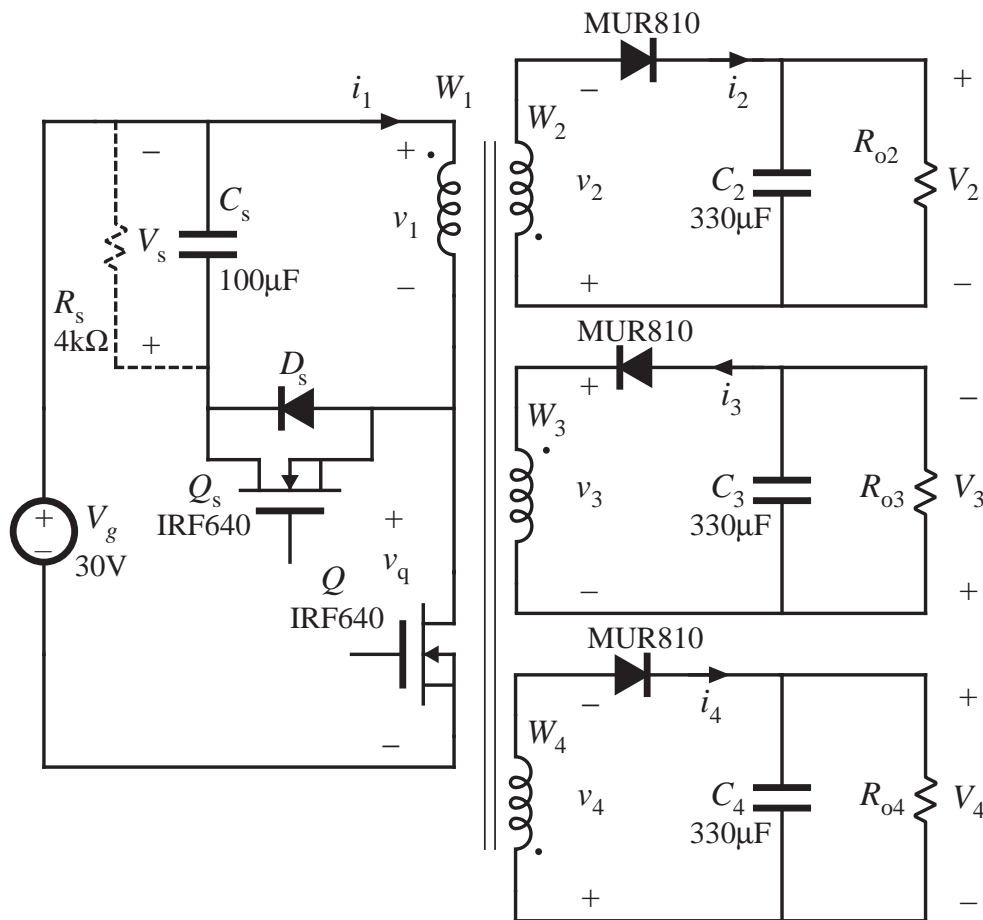
# Experimental 3-Output Flyback Converter



Application specifications:

Input: 30 V (winding  $W_1$ )

Output: +12 V (winding  $W_2$ )

Output: -12 V (winding  $W_3$ )

Output: +3.3 V (winding  $W_4$ )

# Flyback Transformer Example


Experimental example:

Three-output flyback converter

Application specifications:



- Input: 30 V (winding  $W_1$ )
- Output: +12 V (winding  $W_2$ )
- Output: -12 V (winding  $W_3$ )
- Output: +3.3 V (winding  $W_4$ )

Winding and core geometry

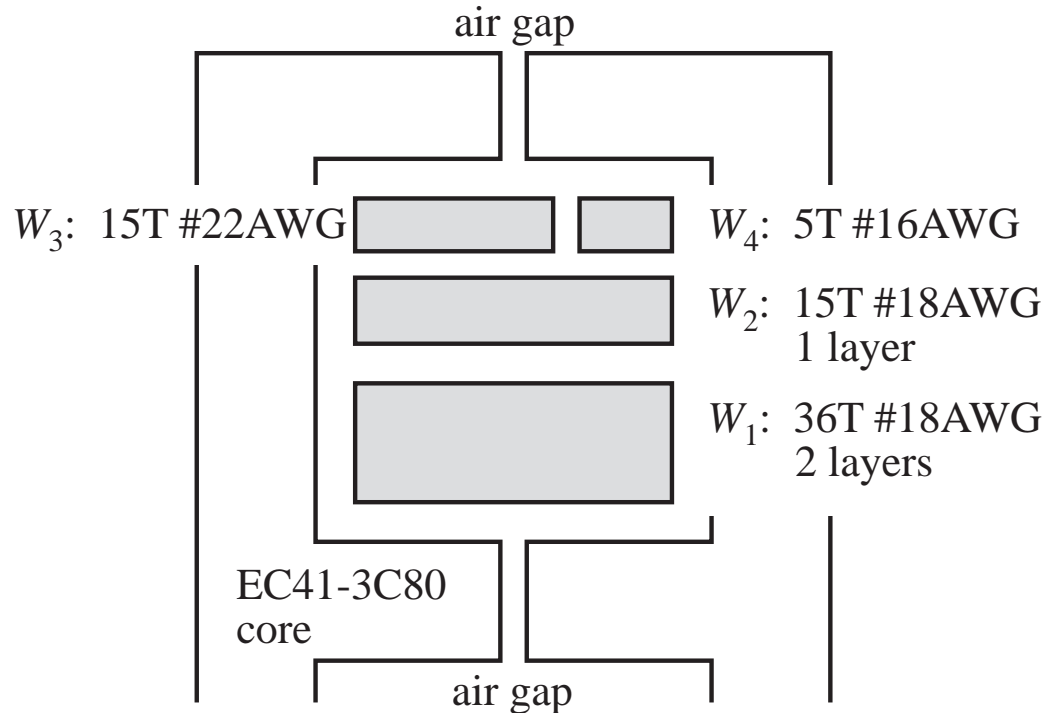

# Measured Model
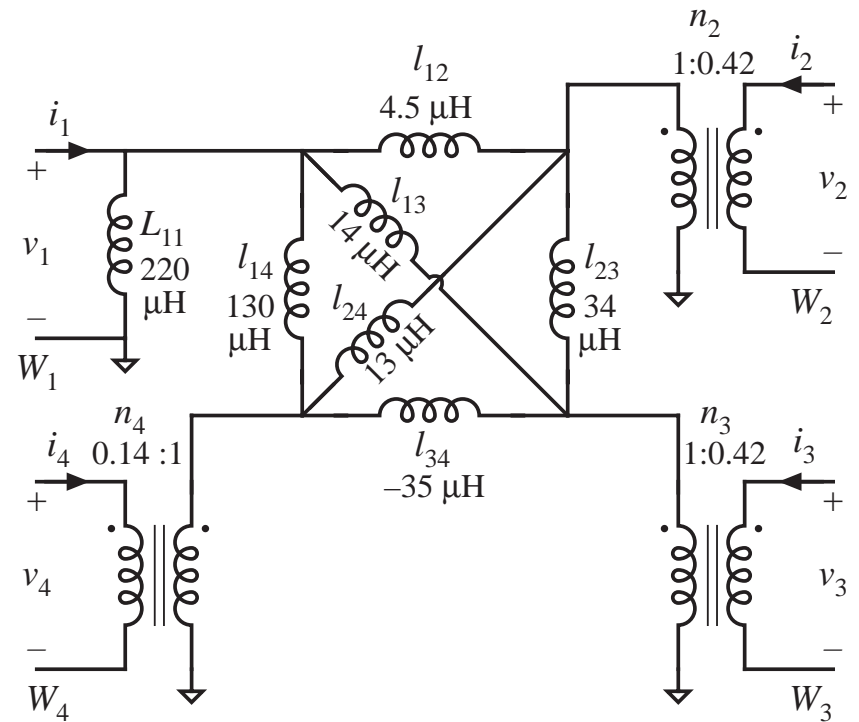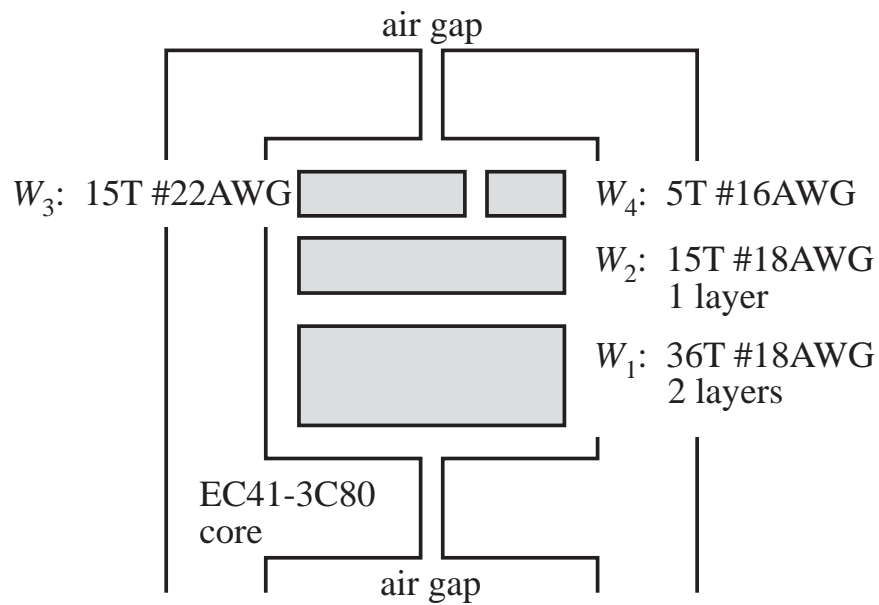
## Flyback transformer extended cantilever model




# Negative $l_{34}$

Directions of induced winding currents, when winding  $W_3$  is driven and windings  $W_1$ ,  $W_2$ , and  $W_4$  are shorted

Negative  $l_{34}$  indicates reversal of polarity of induced current  $i_4$

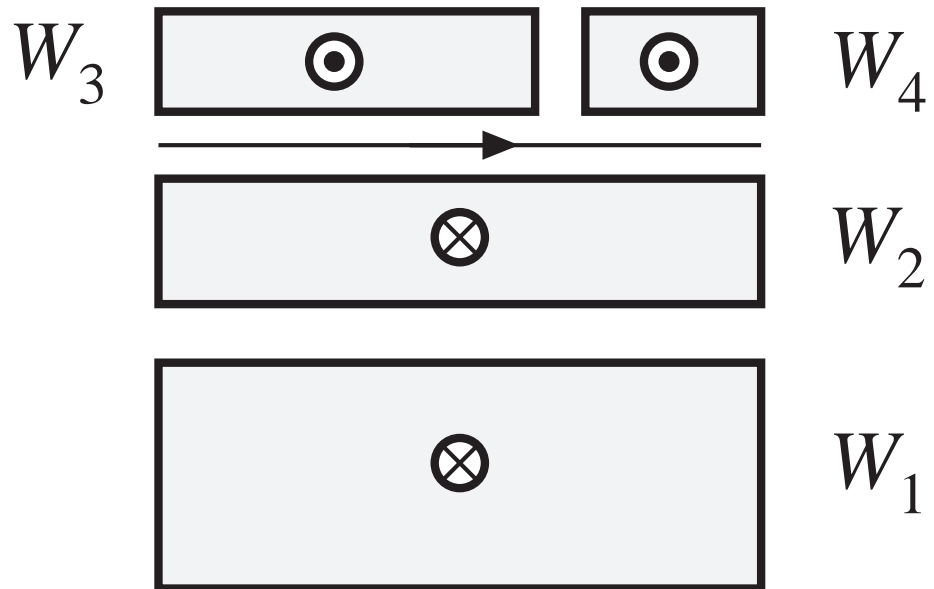
Side-by-side winding geometry leads to negative leakage parameter





# Qualitative Behavior


## Case 1: Passive Voltage-Clamp Snubber

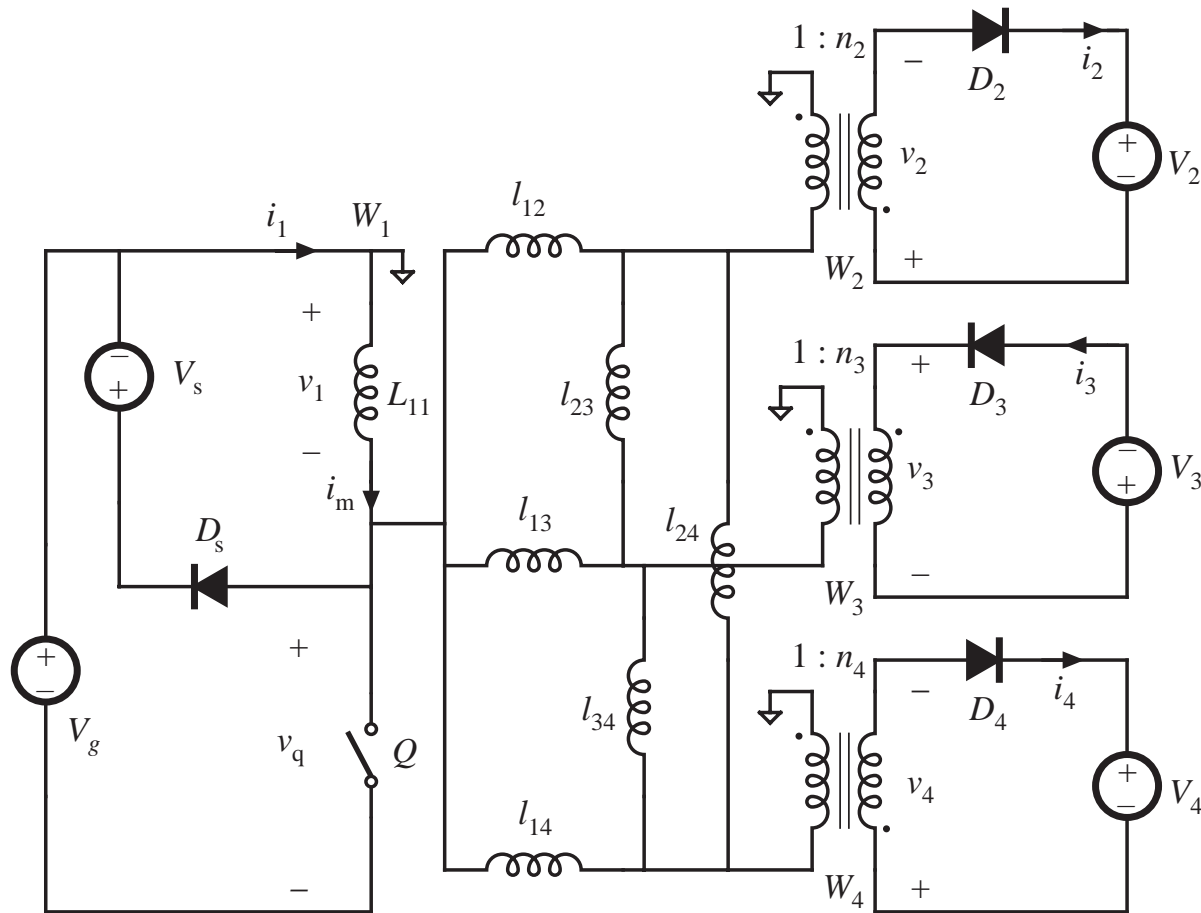

Analysis:

- Use the extended cantilever model for the transformer
- Neglect losses (other than snubber losses due to leakage inductances)
- Neglect capacitor voltage ripples
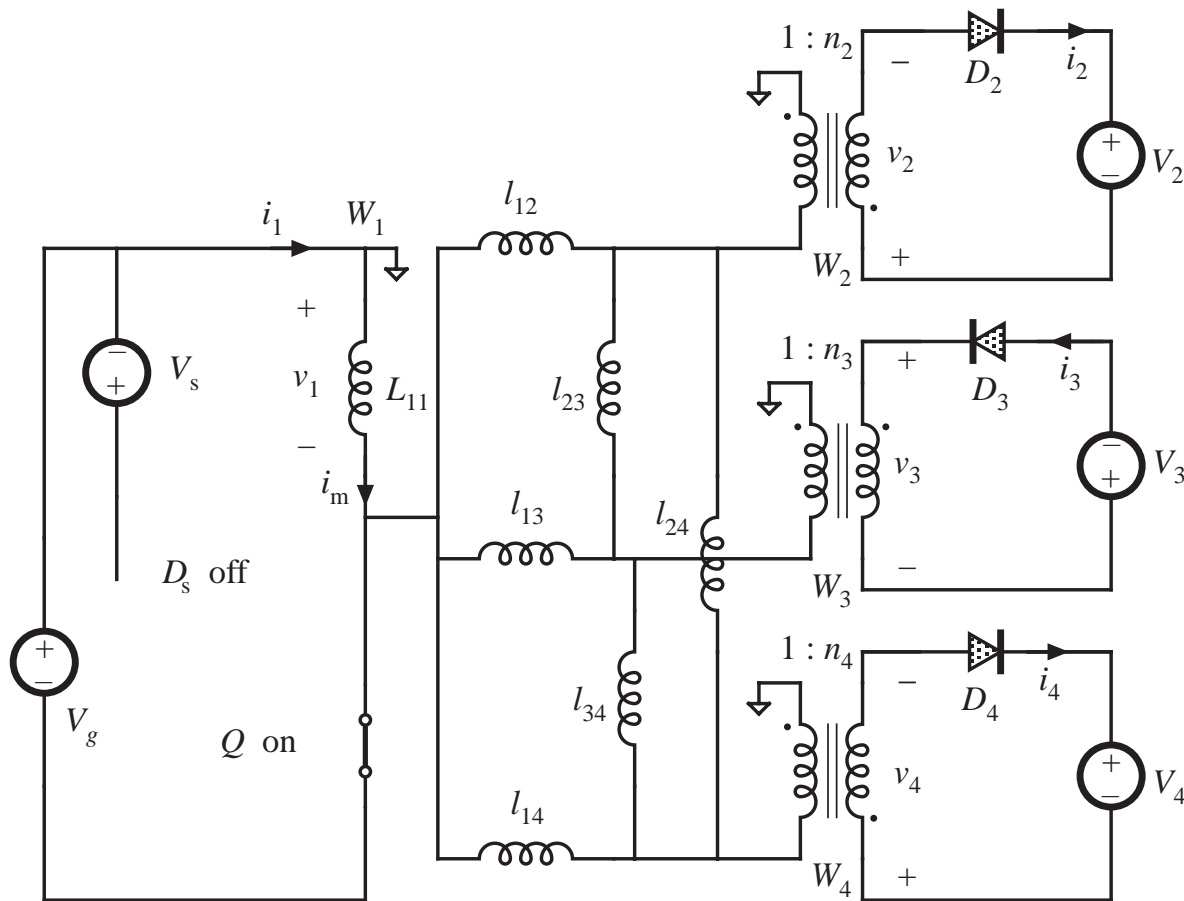
# Start at the Time When the Main Switch is Turned ON: (1) Diode Turn-Off Interval $t_d$




Currents through the leakage inductances decrease to zero after the main switch  $Q$  turns on

Secondary diodes turn off

Diode turn-off times are not equal

## (2) Main switch conduction interval

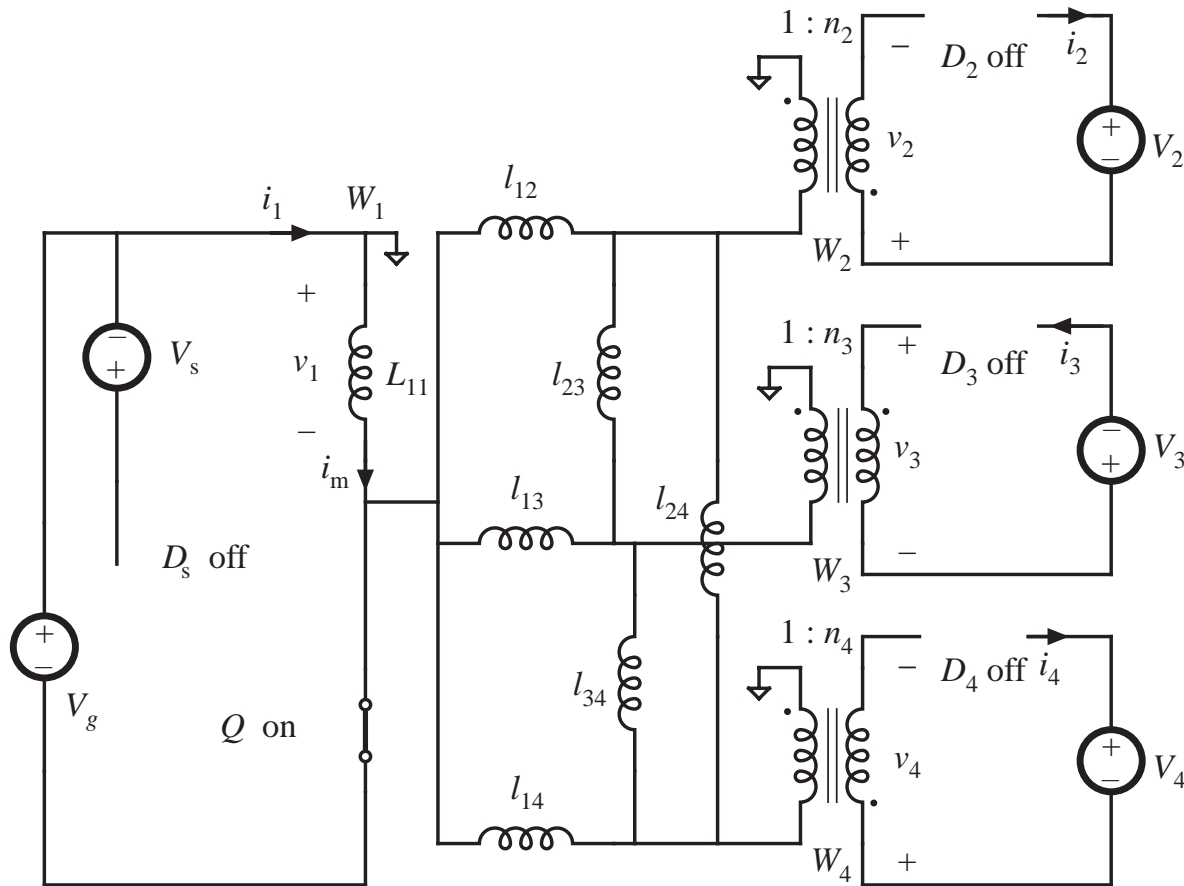


The main switch  $Q$  is on, all diodes are off

The magnetizing current increases

All leakage inductor currents are zero

### (3) Commutation interval $t_c$

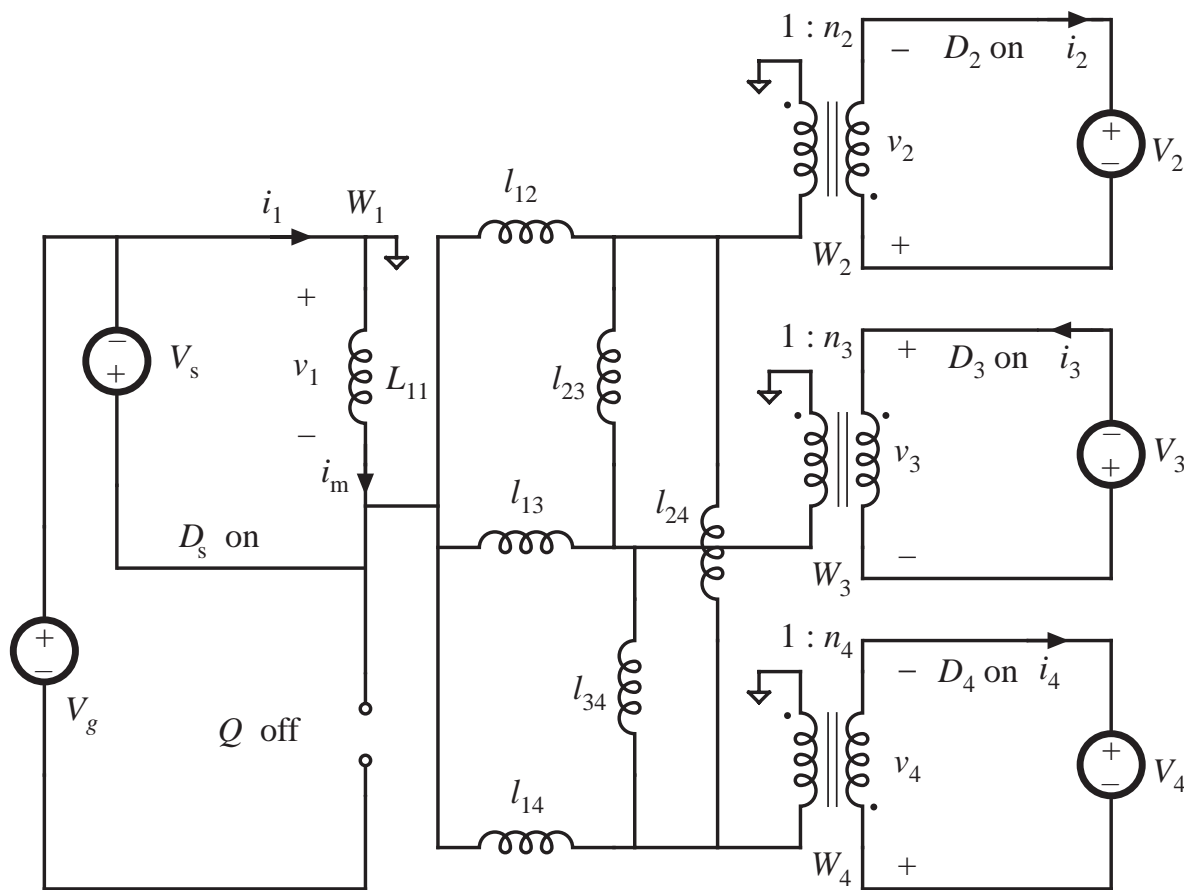


The main switch  $Q$  turns off, the snubber diode  $D_s$  turns on

The secondary diodes turn on, and the secondary winding current start increasing

The interval ends when the reflected secondary currents add to  $i_m$

The magnetizing current divides between the windings according to  $l_{12}$ ,  $l_{13}$ ,  $l_{14}$

## (4) Diode conduction interval

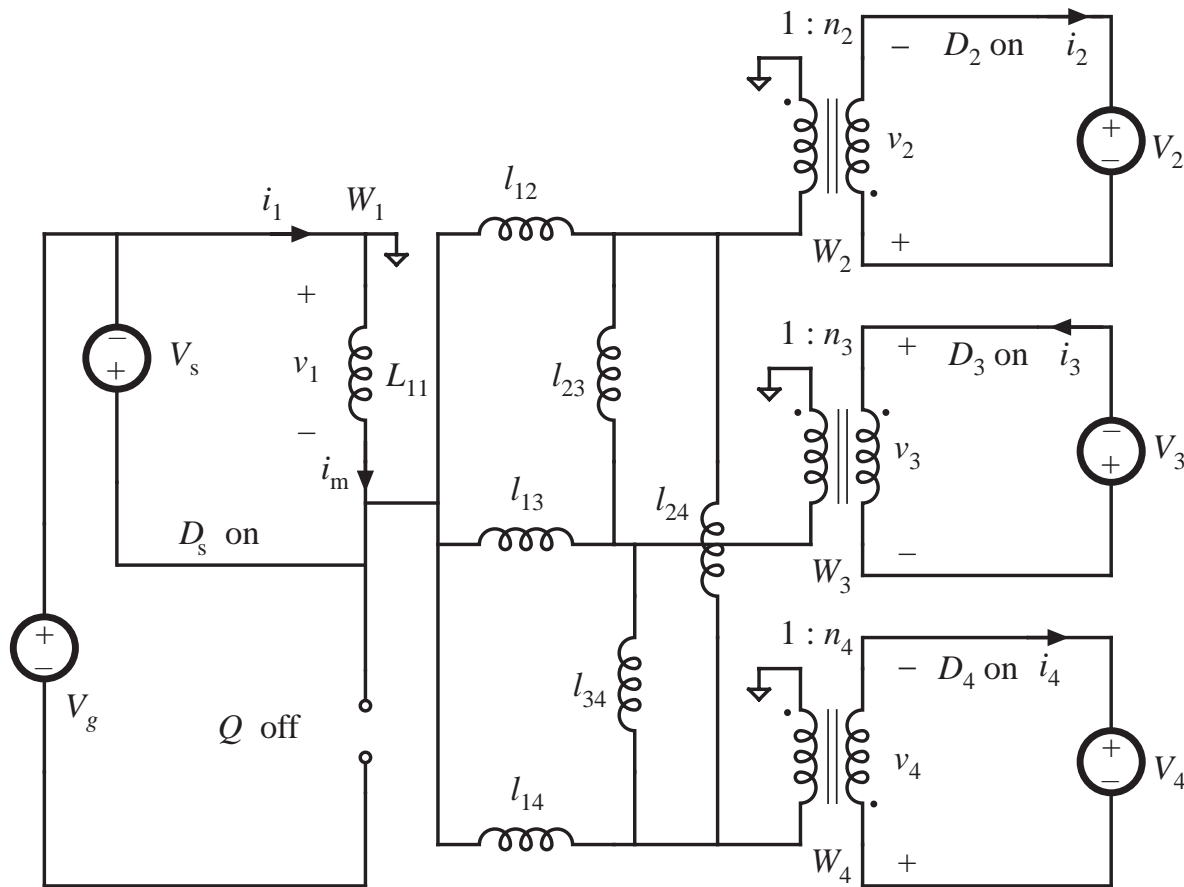


The main switch  $Q$  is off, the snubber diode  $D_s$  is off


The secondary diodes are on, and the secondary winding currents *increase or decrease* at the rates that depend on the initial values and the loads

# Qualitative Behavior


## Case 1: Passive Voltage-Clamp Snubber

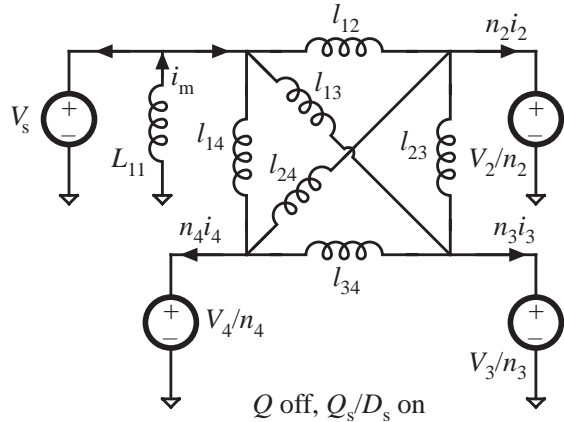

Commutation interval

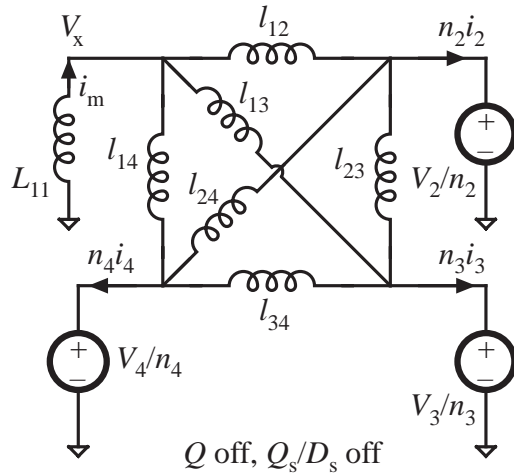


Diode conduction interval

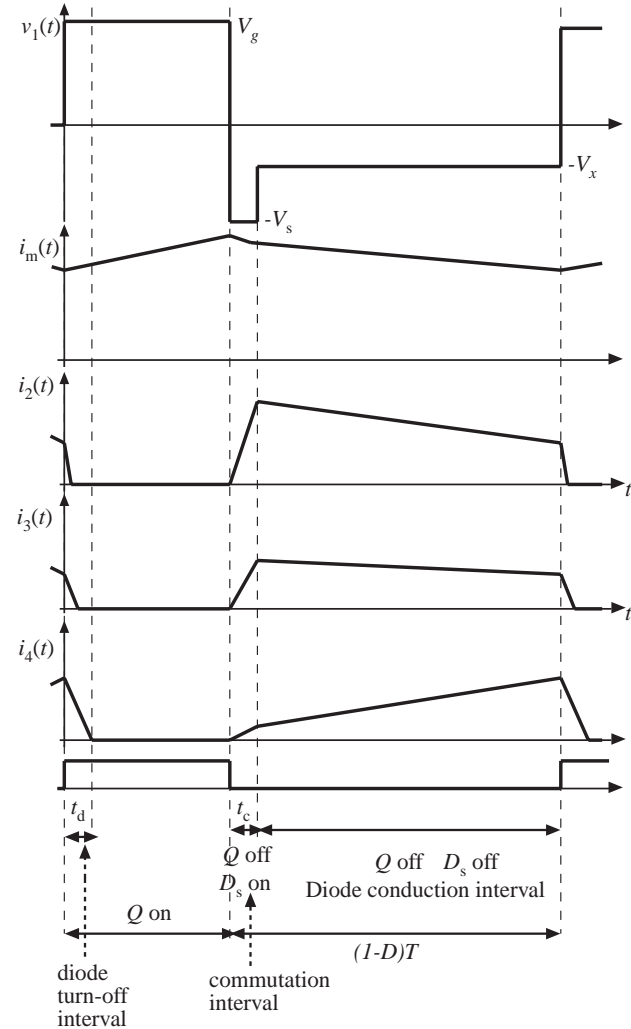


# Measured and predicted waveforms

## Flyback converter example with passive snubber

### Measured waveforms

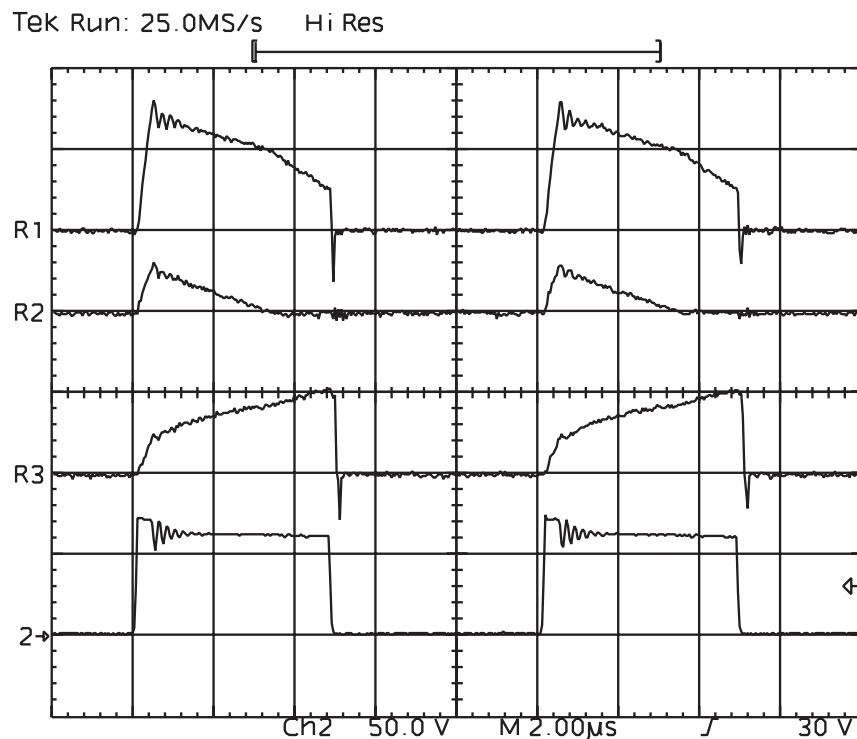

### Simulated waveforms using extended cantilever model

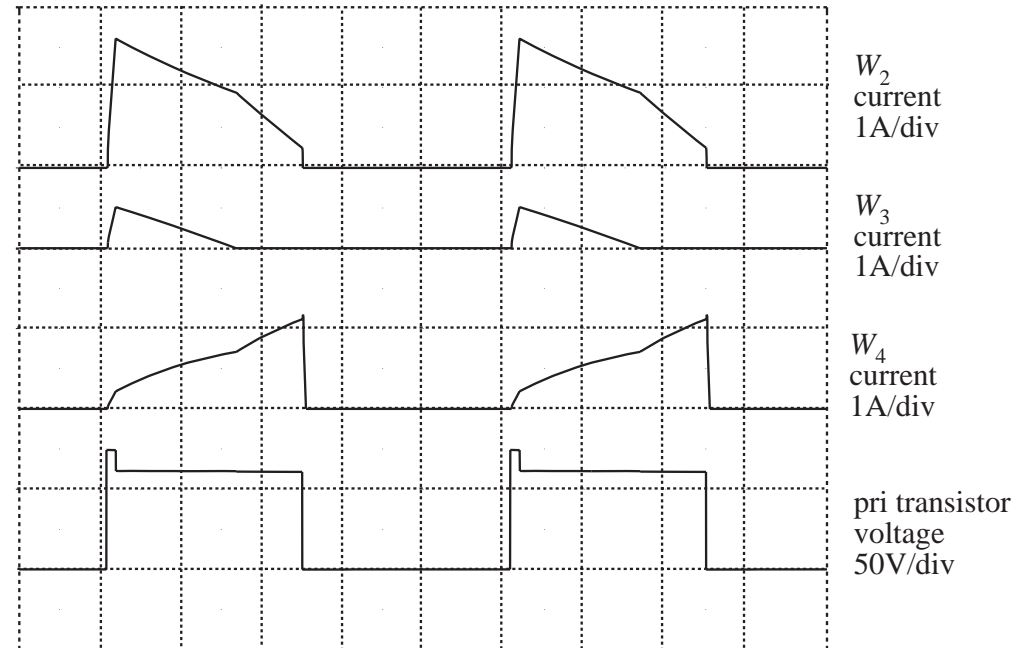



Winding 2: CCM with negative ripple

Winding 4: CCM with positive ripple

Winding 3: DCM

# Secondary current waveforms

## Commutation interval

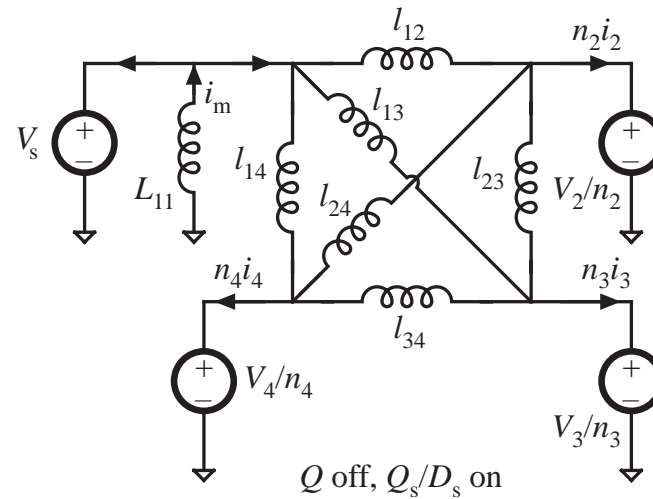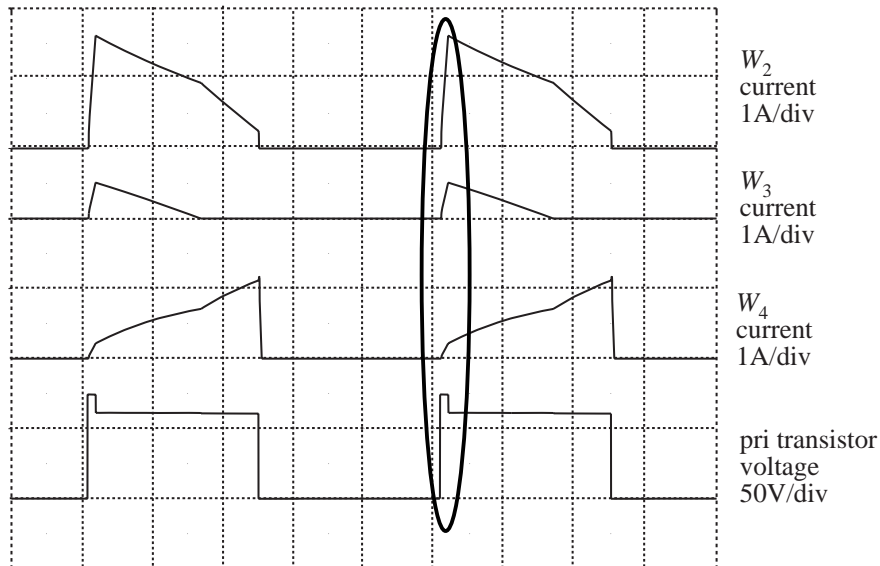


Circuit model referred to the primary side

- Magnetizing current commutes from primary winding to secondary windings
- Reflected output winding voltages are nearly equal
- Essentially zero voltage is applied across  $l_{23}$ ,  $l_{23}$ , and  $l_{23}$
- Large voltage is applied across  $l_{12}$ ,  $l_{13}$ , and  $l_{14}$
- Magnetizing current divides between secondary windings according to relative values of  $l_{12}$ ,  $l_{13}$ , and  $l_{14}$



# Commutation interval analysis

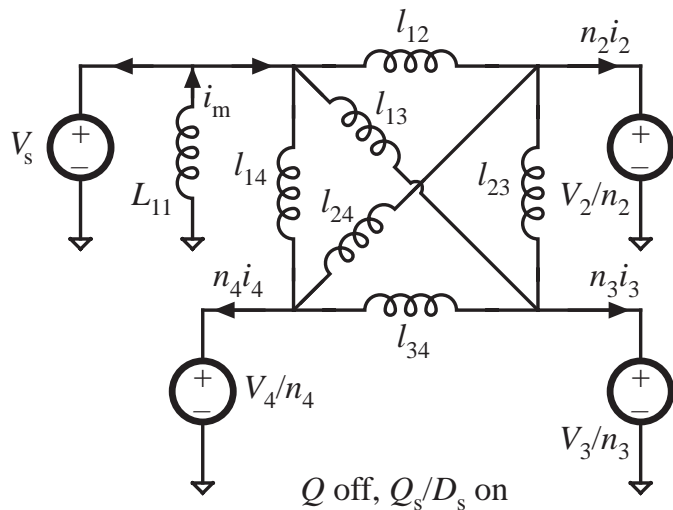

The magnetizing current divides according to relative values of  $l_{12}$ ,  $l_{13}$ , and  $l_{14}$ , not directly related to the loads:

Secondary winding current (W2 example):

$$n_2 \frac{di_2}{dt} = \frac{V_s - V_2/n_2}{l_{12}} + \frac{V_3/n_3 - V_2/n_2}{l_{23}} + \frac{V_4/n_4 - V_2/n_2}{l_{24}}$$

Reflected output voltages are nearly equal:

$$n_2 \frac{di_2}{dt} \approx \frac{V_s - V_2/n_2}{l_{12}}$$

At the end of the commutation interval the reflected secondary currents add up to the magnetizing current:




$$n_2i_2 + n_3i_3 + n_4i_4 = i_m$$

$$n_k i_k = \frac{L_{o1}}{l_{1k}} i_m$$

$$L_{o1} = l_{12} || l_{13} || l_{14}$$



# Secondary Current Waveforms

## Case 1: Passive Voltage-Clamp Snubber

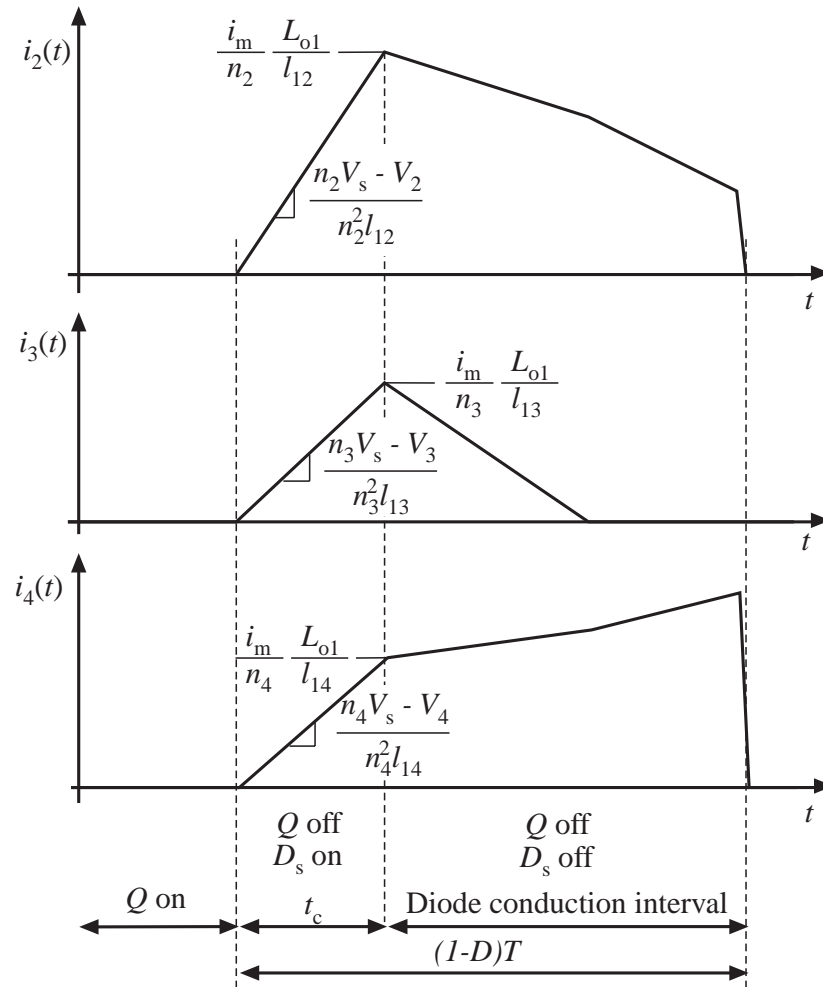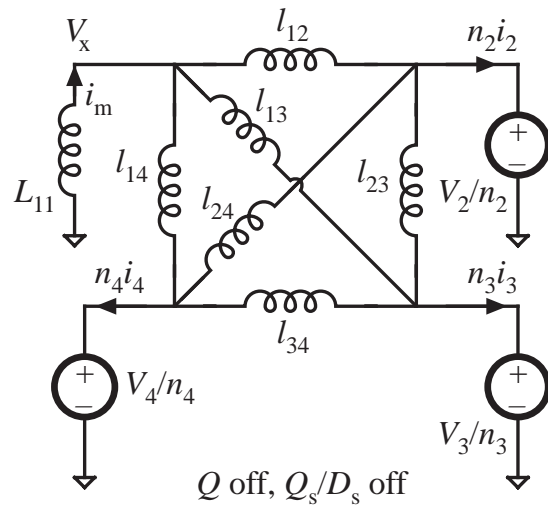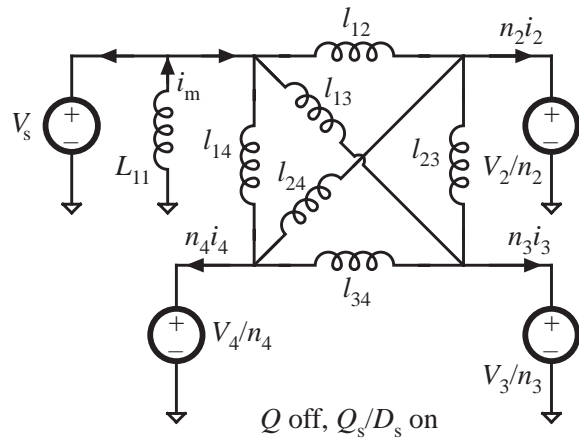

# Secondary current waveforms

## Diode conduction interval

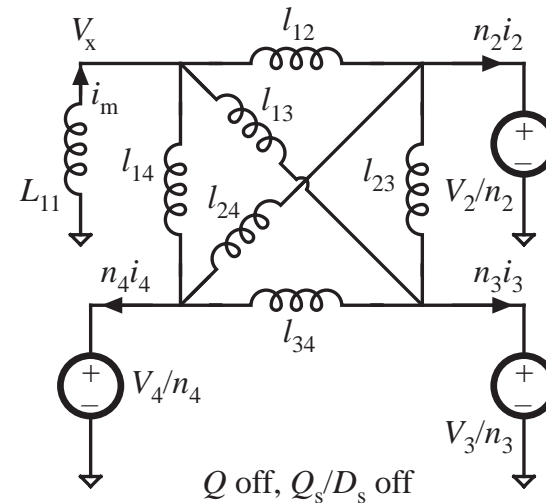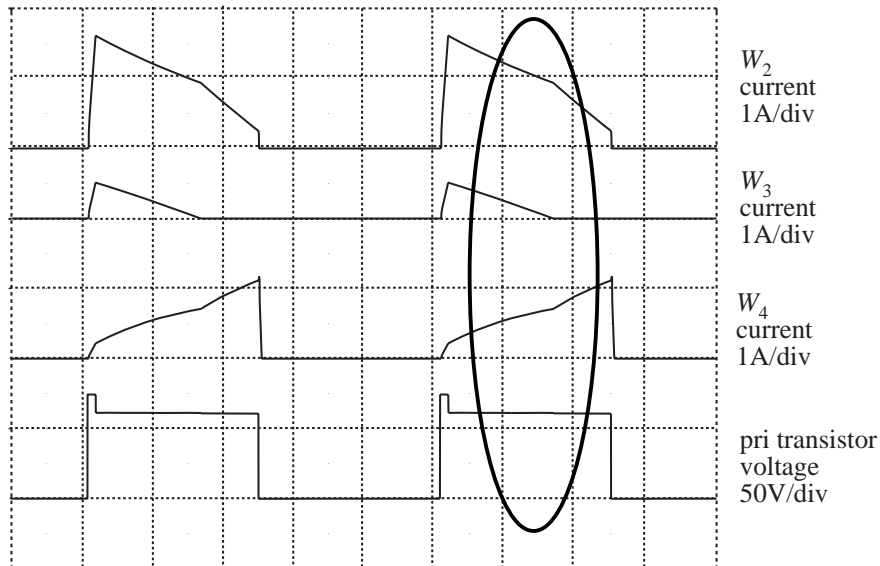

Circuit model referred to the primary side

- The sum of the reflected secondary currents equals the magnetizing current
- Current slopes can be positive or negative, depending on the initial values and the loads
- Increased output voltage reduces slope of winding current waveform, leading to reduced average output current
- Decreased output voltage increases slope of winding current waveform, leading to increased average output current

# Diode conduction interval analysis

Secondary winding current (W2 example):

$$n_2 \frac{di_2}{dt} = \frac{V_x - V_2/n_2}{l_{12}} + \frac{V_3/n_3 - V_2/n_2}{l_{23}} + \frac{V_4/n_4 - V_2/n_2}{l_{24}}$$


$$n_2 \frac{di_2}{dt} = -\frac{V_2/n_2 - V_x}{L_{o2}} + \frac{V_3/n_3 - V_x}{l_{23}} - \frac{V_4/n_4 - V_x}{l_{24}}$$

Winding Thevenin output inductances (ref. to primary):

$$L_{o2} = l_{12} || l_{23} || l_{24}$$

$$L_{o3} = l_{13} || l_{23} || l_{34}$$

$$L_{o4} = l_{14} || l_{24} || l_{34}$$

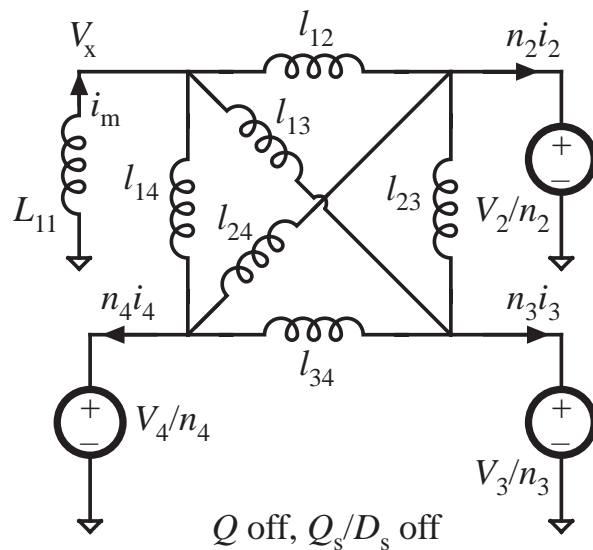

All secondary winding currents:

$$\frac{d\mathbf{i}'}{dt} = \mathbf{B}_1 (\mathbf{V}' - \mathbf{u}V_x)$$

$$\mathbf{B}_1 = \begin{bmatrix} -\frac{1}{L_{o2}} & \frac{1}{l_{23}} & \frac{1}{l_{24}} \\ \frac{1}{l_{23}} & -\frac{1}{L_{o3}} & \frac{1}{l_{34}} \\ \frac{1}{l_{24}} & \frac{1}{l_{34}} & -\frac{1}{L_{o4}} \end{bmatrix}, \quad \mathbf{u} = \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix}$$

# General Steady-State Solution

Case 1: Passive voltage-clamp snubber, all outputs in CCM

---

Averaging of the secondary winding currents gives:

$$\mathbf{B}_1(\mathbf{V}' - \mathbf{u}V_x) = \frac{2f_s}{(1-D)^2}\mathbf{B}_2\mathbf{I}' - \mathbf{b}_2\frac{L_{o1}}{L_{11}}V_x,$$
$$\mathbf{B}_2 = \begin{bmatrix} 1 - \frac{L_{o1}}{l_{12}} & -\frac{L_{o1}}{l_{12}} & -\frac{L_{o1}}{l_{12}} \\ -\frac{L_{o1}}{l_{13}} & 1 - \frac{L_{o1}}{l_{13}} & -\frac{L_{o1}}{l_{13}} \\ -\frac{L_{o1}}{l_{14}} & -\frac{L_{o1}}{l_{14}} & 1 - \frac{L_{o1}}{l_{14}} \end{bmatrix}, \quad \mathbf{b}_2 = \begin{bmatrix} \frac{1}{l_{12}} \\ \frac{1}{l_{13}} \\ \frac{1}{l_{14}} \end{bmatrix}$$

where  $V_x$  is found from the volt-second balance on  $L_{11}$ :

$$V_x \approx V_g \frac{D}{1-D} - \frac{f_s L_{o1}}{(1-D)^2} (\mathbf{u}^T \mathbf{I}')$$

# Thevenin Output Resistance Matrix

Passive voltage-clamp snubber, all outputs in CCM

---

---

Referred to the primary side:


$$\mathbf{R}' = -\frac{2f_s}{(1-D)^2} \left( \mathbf{B}_1^{-1} \mathbf{B}_2 - \frac{L_{o1}}{2} \mathbf{u} \mathbf{u}^T \right)$$

Referred to the secondaries:  $\Delta \mathbf{V} = -\mathbf{R} \Delta \mathbf{I}$

$$\mathbf{R} = \mathbf{N} \mathbf{R}' \mathbf{N}$$

$$\mathbf{N} = \begin{bmatrix} n_2 & 0 & 0 \\ 0 & n_3 & 0 \\ 0 & 0 & n_4 \end{bmatrix}$$
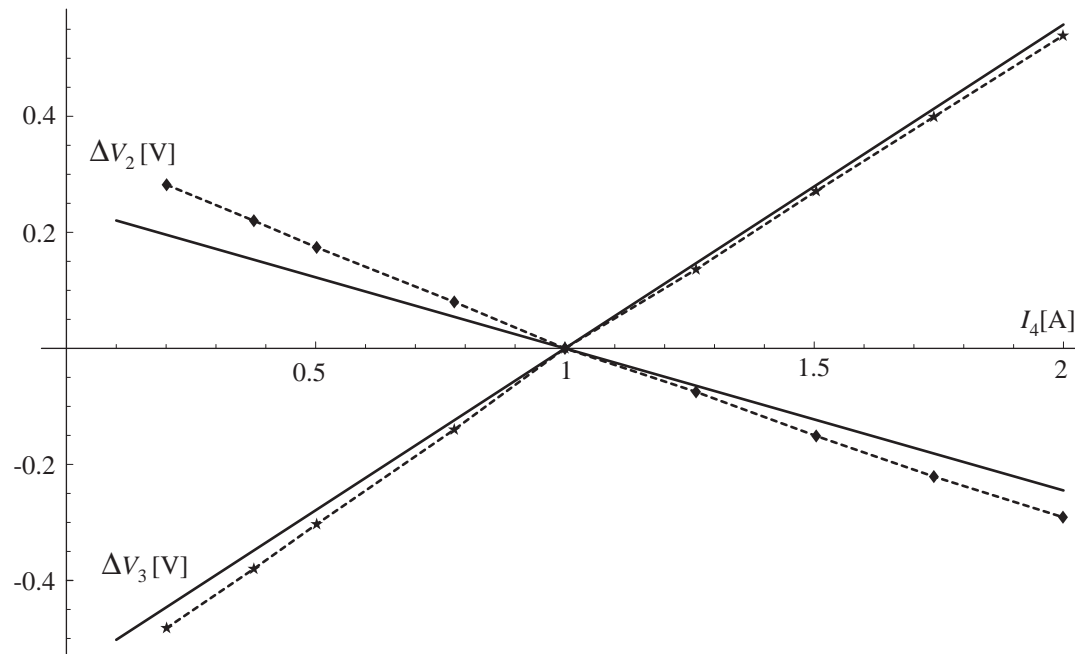
# Predicted and measured cross-regulation (with passive voltage-clamp snubber)



Operating conditions:  $D=0.52$ ,  $I_2=I_3=0.4\text{A}$ ,  $I_4=0.1\text{A}$  to  $2.0\text{A}$

Changing load on the main output has opposite effects on the two auxiliary outputs !

# Predicted and measured output resistance matrix

---

Operating point:  $D=0.52$ ,  $I_2=I_3=0.4\text{A}$ ,  $I_4=1\text{A}$

Predicted:

$$\begin{bmatrix} \Delta V_2 \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix} = - \begin{bmatrix} 0.42 & -0.32 & 0.24 \\ -0.32 & 2.15 & -0.56 \\ 0.24 & -0.56 & 0.54 \end{bmatrix} \begin{bmatrix} \Delta I_2 \\ \Delta I_3 \\ \Delta I_4 \end{bmatrix}$$

Measured variations in the output voltages corresponding to load changes:

$$\begin{bmatrix} \Delta V_2 \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix} = - \begin{bmatrix} 1.22 & -0.2 & 0.24 \\ -0.35 & 3.2 & -0.52 \\ 0.26 & -0.56 & 0.90 \end{bmatrix} \begin{bmatrix} \Delta I_2 \\ \Delta I_3 \\ \Delta I_4 \end{bmatrix}$$



# Experimental verification of the model

---

- Waveforms obtained by simulation match experimentally observed waveforms: the extended cantilever magnetics model can be used to predict complex operation of multiple-output flyback converters
- The extended cantilever model allows easy qualitative explanation of the converter operation, as well as derivation of a general steady-state cross-regulation model
- Good agreement between predictions of the steady-state cross-regulation model and measured results
- Off-diagonal terms (“mutual resistances”) in the Thevenin output resistance matrix are determined mainly by the transformer leakage inductances. Prediction of these terms is very good
- Diagonal terms (“self resistances”) in the Thevenin output resistance matrix are affected by conduction losses. Hence the measured values are greater than predicted by the model.

# Discontinuous conduction modes

---

$$n_2 i_2 + n_3 i_3 + n_4 i_4 = i_m$$


$$n_k i_k = \frac{L_{o1}}{l_{1k}} i_m$$

$$L_{o1} = l_{12} || l_{13} || l_{14}$$


- Initial secondary winding currents at the end of the commutation interval are proportional to the magnetizing current, i.e. to the *total* load, not to the load on the individual output
- The magnetizing current is divided according to the relative values of  $l_{12}$ ,  $l_{13}$ , and  $l_{14}$ , *not* according to individual loads
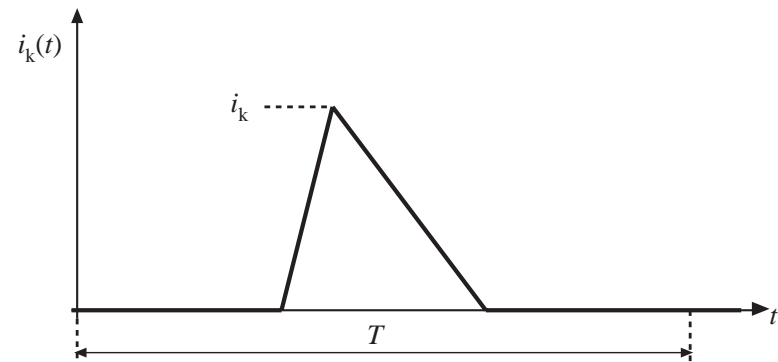
# Discontinuous conduction modes

- A lightly loaded output well coupled to the primary ( $l_{12}$  small)
- Starts with large initial value  $i_k$
- Large negative slope in the diode conduction interval  $\Rightarrow$  DCM with much increased output voltage



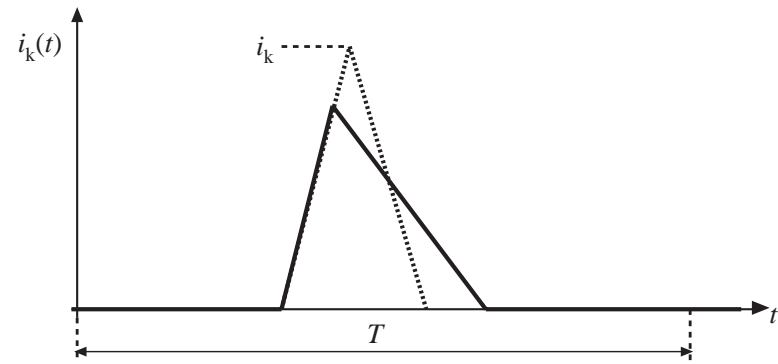- Increasing load on another output increases  $i_k$  further
- Deeper DCM, even larger output voltage
- Very poor cross-regulation (often referred to as “peak detection”)



# CCM boundaries

---

- General result for operation of all outputs in CCM:

$$\begin{bmatrix} 2\frac{l_{12}}{L_{o1}} - 1 & -1 & -1 \\ -1 & 2\frac{l_{13}}{L_{o1}} - 1 & -1 \\ -1 & -1 & 2\frac{l_{14}}{L_{o1}} - 1 \end{bmatrix} \begin{bmatrix} n_2 I_2 \\ n_3 I_3 \\ n_4 I_4 \end{bmatrix} > \frac{(1-D)^2 V_x}{2f_s L_{11}} \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix}$$

- The winding best coupled to the primary is most likely to operate in DCM
- Increasing load on one winding eventually drives all other outputs into DCM
- Improper relative primary-to-secondary couplings and the resulting DCM modes are the major cause of poor cross-regulation
- General rule: the winding with the widest load range should be best coupled to the primary

# CCM boundaries: experimental example

---

- Experimental example:

$$\begin{bmatrix} 0.73 & -0.42 & -0.14 \\ -0.42 & 3.0 & -0.14 \\ -0.42 & -0.42 & 10.9 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \\ I_4 \end{bmatrix} > \begin{bmatrix} 0.17\text{A} \\ 0.17\text{A} \\ 0.17\text{A} \end{bmatrix}$$

- Predicted CCM conditions:

$$I_2 > 0.23\text{A} + 0.58I_3 + 0.19I_4$$


$$I_3 > 0.06\text{A} + 0.14I_2 + 0.05I_4$$

$$I_4 > 0.016\text{A} + 0.045I_2 + 0.045I_3$$

- Good agreement with experiment

# Qualitative Behavior


## Case 2: Active-Clamp Snubber

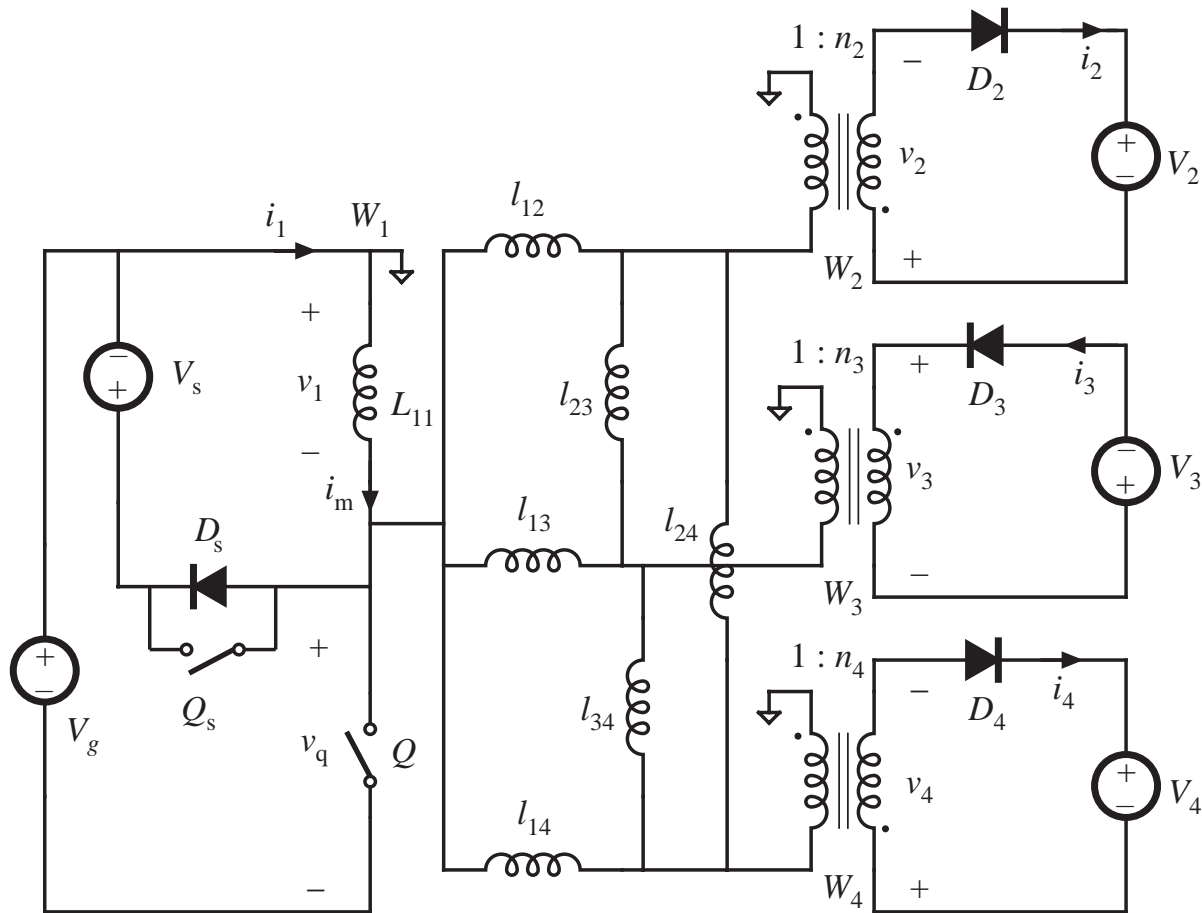

Analysis:

- Use the extended cantilever model for the transformer
- Neglect losses (other than losses due to leakage inductances)
- Neglect capacitor voltage ripples

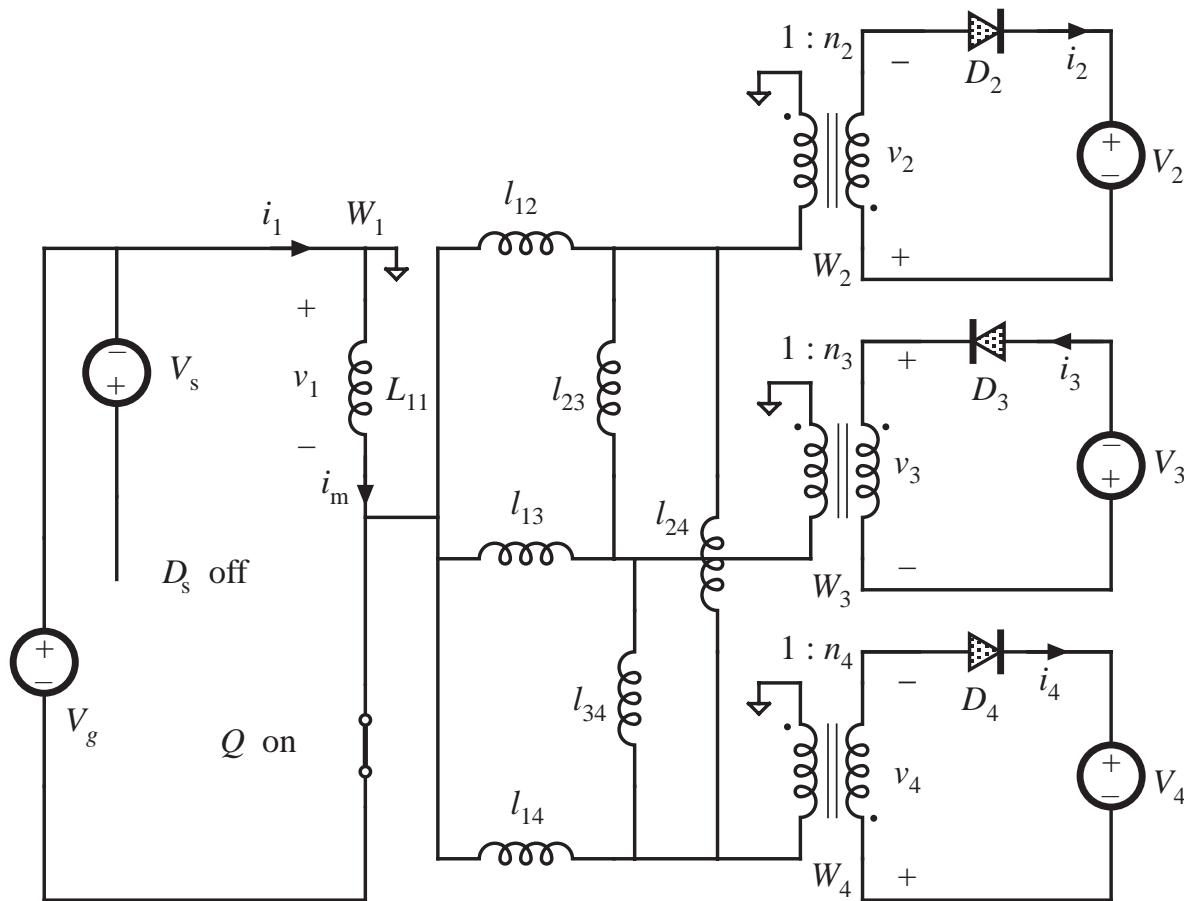
# Diode turn-off interval $t_d$ (same as in Case 1)



Currents through leakage inductances decrease to zero after the main switch  $Q$  turns on; secondary diodes turn off

Diode turn-off times are not equal
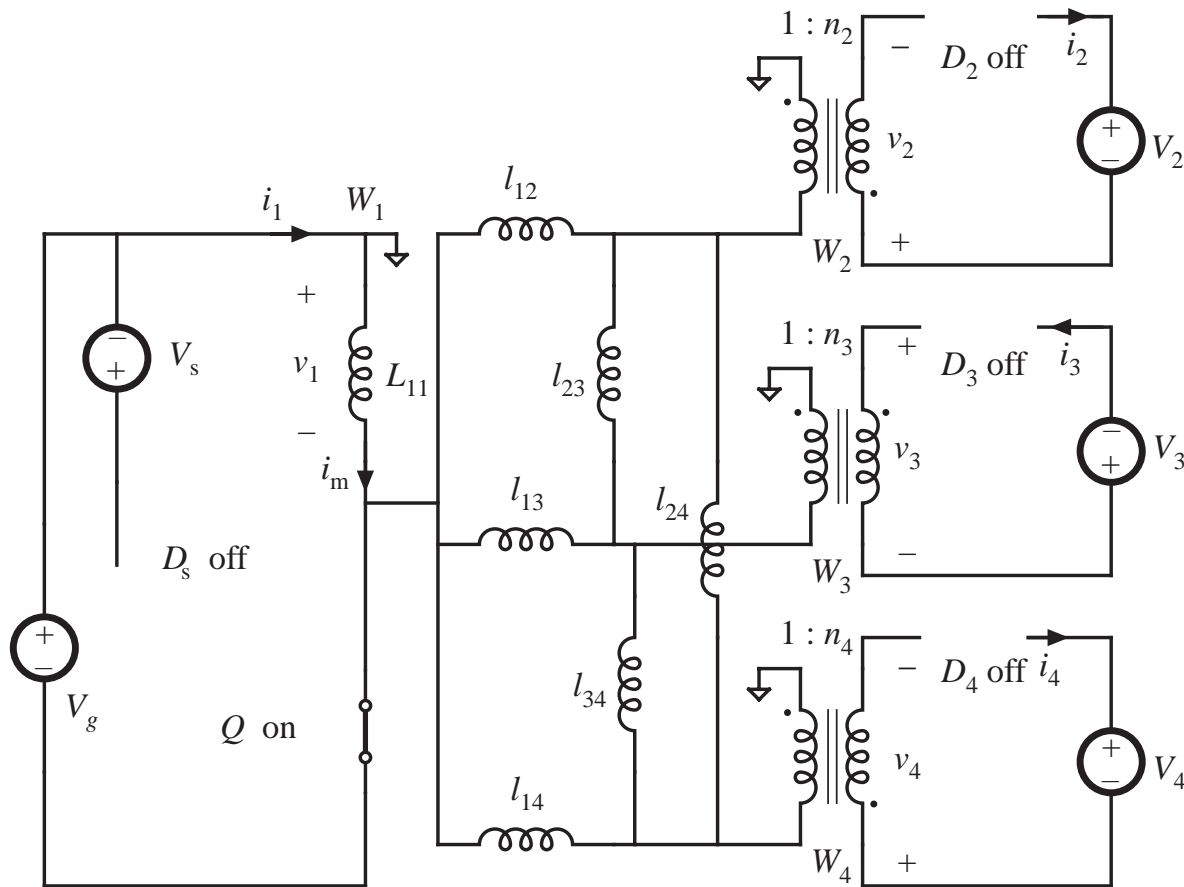
# Main switch conduction interval (same as in Case 1)




The main switch  $Q$  is on, all diodes are off

The magnetizing current increases

All leakage inductor currents are zero


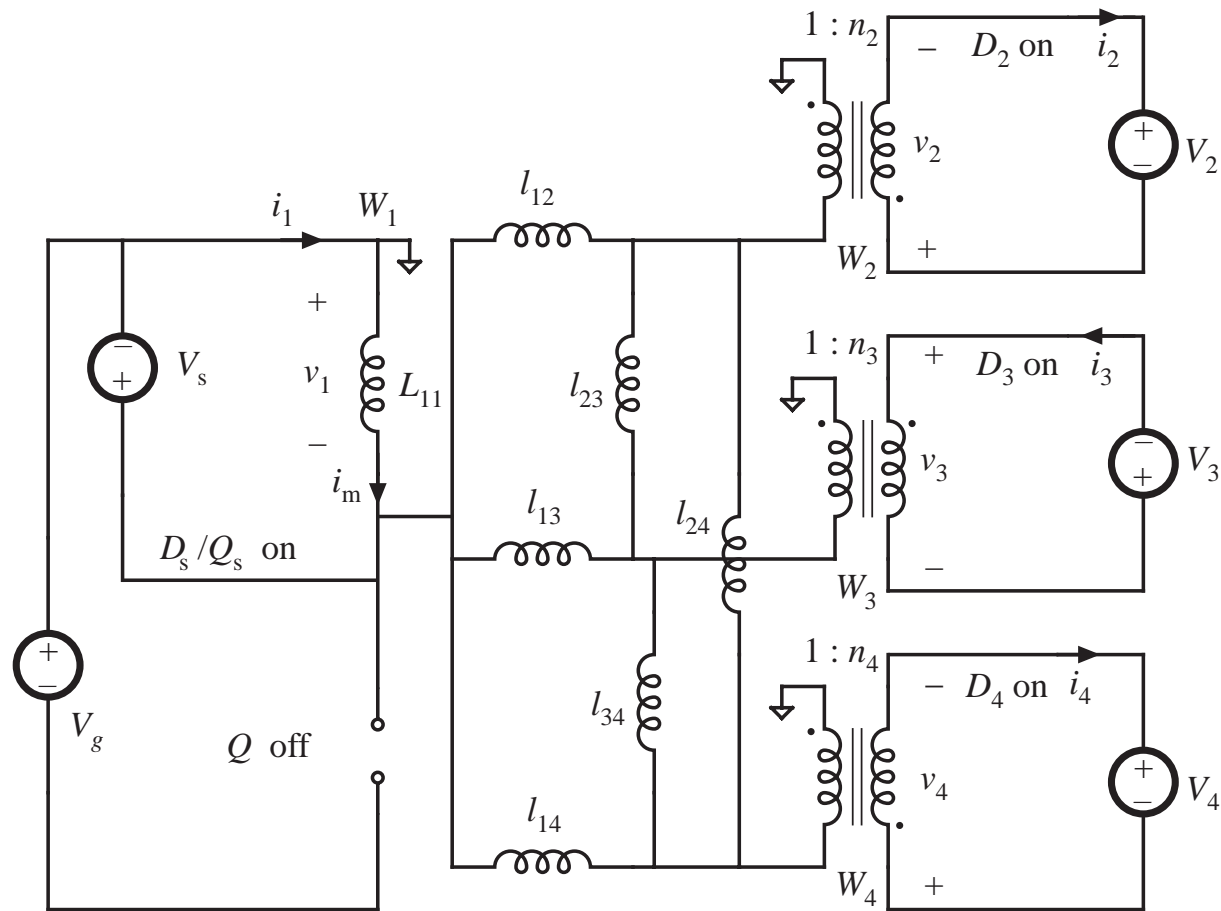
# Commutation & diode conduction interval merge into one




The main switch  $Q$  turns off, the snubber diode  $D_s$  turns on;  $Q_s$  is turned on

The secondary diodes turn on, and the secondary winding currents start *increasing* at the rates that depend on the leakage inductances and loads

All outputs operate in CCM always


# Qualitative Behavior

## Case 2: Active-Clamp Snubber

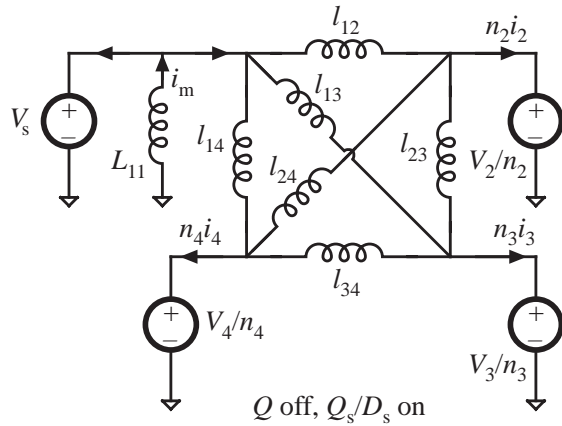

Diode conduction interval

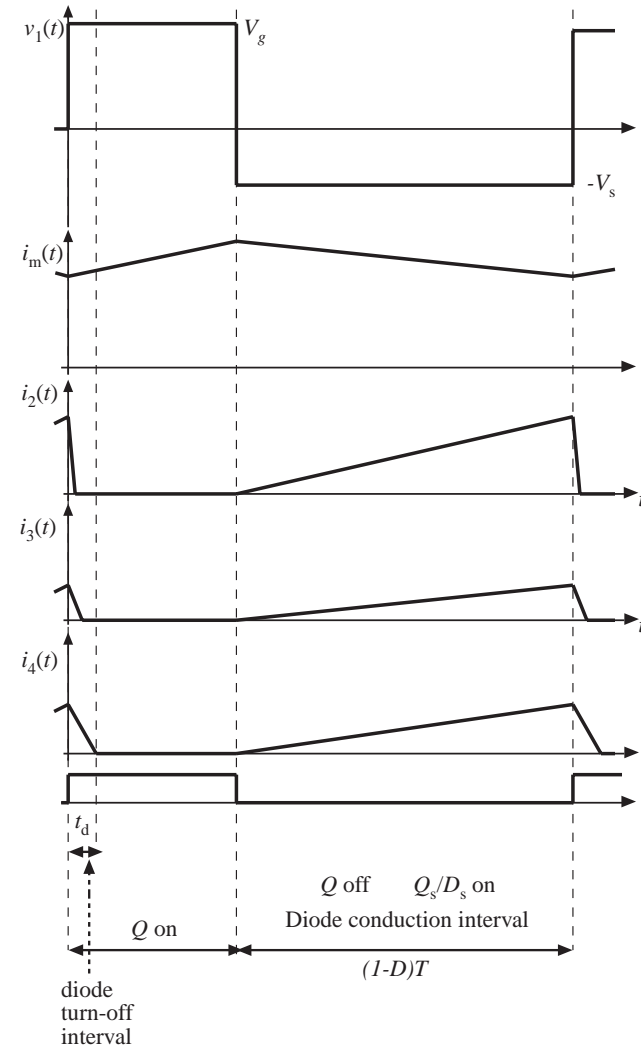
- All secondary winding currents have positive slope
- There is only one operating mode: CCM
- Current slopes can be calculated as in the passive snubber case




# Measured and predicted waveforms

## Flyback converter example: Active-Clamp Snubber

### Measured waveforms

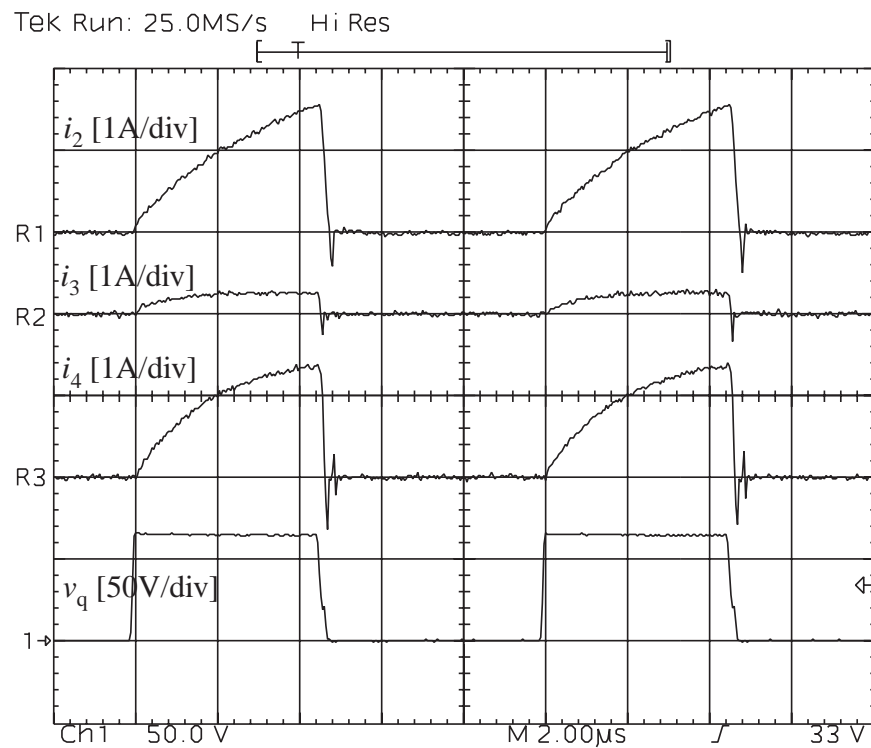

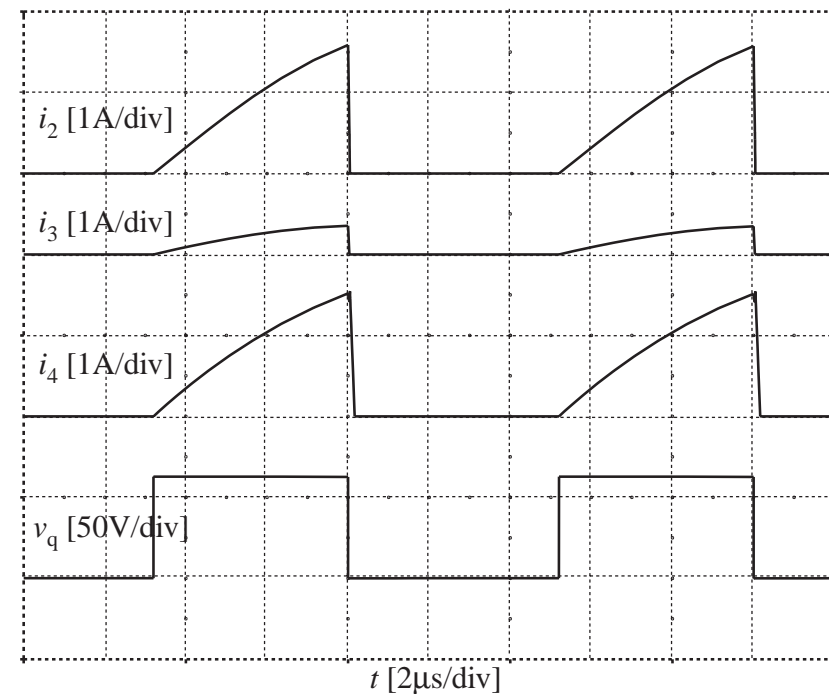
### Simulated waveforms using extended cantilever model



Simulation model included resistive conduction losses


# Secondary Current Waveforms

## Case 2: Active-Clamp Snubber

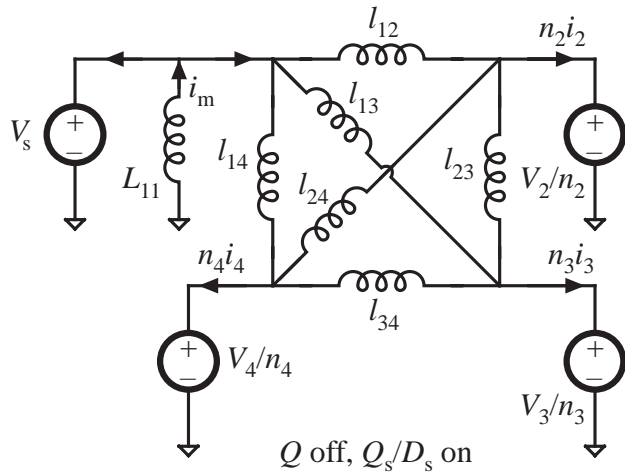

Secondary currents increase at the rates determined by the leakage inductances and the loads

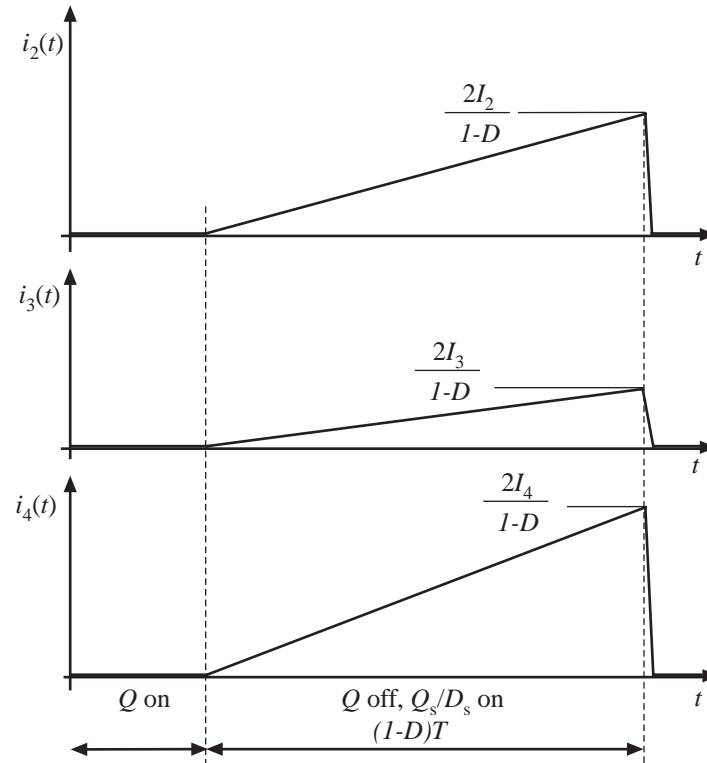Current slopes can be calculated as in the passive snubber case



# General Steady-State Solution (Active-clamp snubber)

---

Averaging of the secondary winding currents gives:

$$\mathbf{B}_1(\mathbf{V}' - \mathbf{u}V_s) = \frac{2f_s}{(1-D)^2}\mathbf{I}'$$

where  $V_s$  is found from the volt-second balance on  $L_{11}$ :

$$V_s = \frac{D}{1-D}V_g$$

# Thevenin Output Resistance Matrix (Active-clamp snubber)

---

Referred to the primary side:

$$\mathbf{R}' = -\frac{2f_s}{(1-D)^2} \mathbf{B}_1^{-1}$$

Referred to the secondaries:  $\Delta \mathbf{V} = -\mathbf{R} \Delta \mathbf{I}$

$$\mathbf{R} = \mathbf{N} \mathbf{R}' \mathbf{N}$$

$$\mathbf{N} = \begin{bmatrix} n_2 & 0 & 0 \\ 0 & n_3 & 0 \\ 0 & 0 & n_4 \end{bmatrix}$$

# Predicted and measured output resistance matrix

---

Operating point:  $D=0.52$ ,  $I_2=I_3=0.4\text{A}$ ,  $I_4=1\text{A}$

Predicted:

$$\begin{bmatrix} \Delta V_2 \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix} = - \begin{bmatrix} 0.67 & -0.07 & 0.33 \\ -0.07 & 2.40 & -0.48 \\ 0.33 & -0.48 & 0.56 \end{bmatrix} \begin{bmatrix} \Delta I_2 \\ \Delta I_3 \\ \Delta I_4 \end{bmatrix}$$

Measured variations in the output voltages corresponding to load changes:

$$\begin{bmatrix} \Delta V_2 \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix} = - \begin{bmatrix} 1.5 & -0.3 & 0.25 \\ -0.16 & 3.3 & -0.64 \\ 0.25 & -0.7 & 0.90 \end{bmatrix} \begin{bmatrix} \Delta I_2 \\ \Delta I_3 \\ \Delta I_4 \end{bmatrix}$$

Compare to the passive-snubber case: resistance values can be significantly different

# Discussion

---

- Cross-regulation (open loop) is in general better if the terms in the Thevenin equivalent output resistance matrix are smaller
- Output resistances are directly proportional to the leakage inductances between the secondaries. Therefore, tighter coupling between the secondaries improves cross-regulation
- On lightly loaded outputs, tight primary-to-secondary coupling may lead to DCM operation and significantly worse cross regulation
- Relative values of primary-to-secondary leakage inductances are important for good cross regulation: the output with the widest load range should have the best coupling to the primary
- Perfect closed-loop cross-regulation can be obtained even if leakage inductances are not small: attempt to match rows of the resistance matrix  $\mathbf{R}'$  referred to the primary side




# Closed-loop cross-regulation

---

- Open-loop cross-regulation model:  $\Delta V = -\mathbf{R}\Delta I$
- Closed-loop operation:
  - Increasing load on the regulated output increases duty ratio  $D$  to compensate for the load-induced drop
  - All other output voltages increase with  $D$
  - If an auxiliary output has the same open-loop dependence on load currents, i.e., the same rows of the resistance matrix  $\mathbf{R}'$  referred to the primary side, then this auxiliary output will have perfect cross-regulation
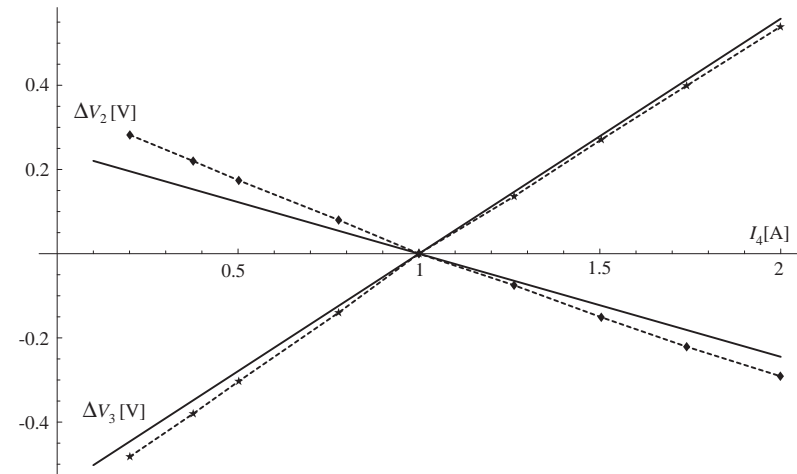
# Experimental example


$$\mathbf{R}' = \begin{bmatrix} 3.8 & -0.4 & 5.5 \\ -0.4 & 13.6 & -8.1 \\ 5.5 & -8.1 & 28.7 \end{bmatrix} \Omega$$



- Winding W4 (the last row) is closed-loop regulated
- Winding W2 has better match of the resistance terms with W4 than winding W3
- Winding W3 has the resistance terms of opposite sign !
- Expect better closed-loop cross-regulation on the W2 output (as long as the outputs operate in CCM)

# Experimental Closed-loop Cross-regulation

---

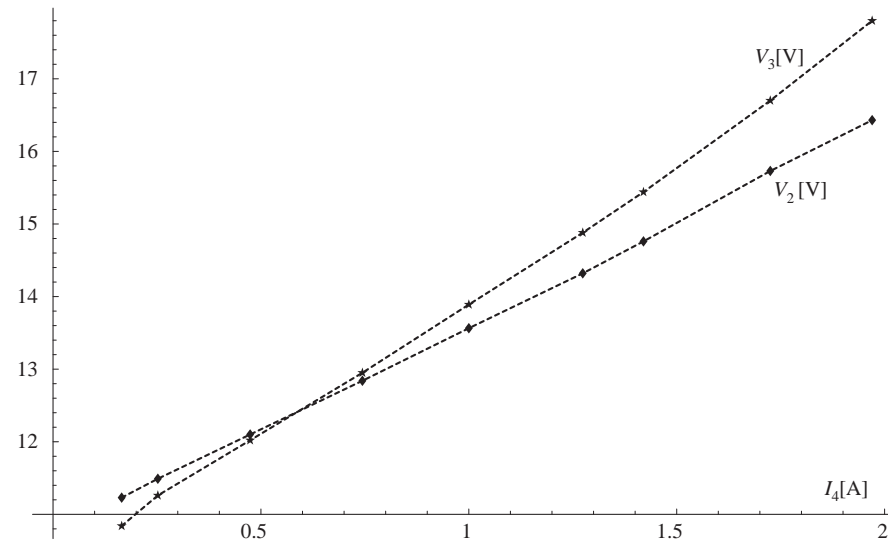

Possible improvements:

- Avoid opposite-sign terms (which in this example came from the negative leakage of the side-by-side winding W3 next to W4)
- Improve matching of resistance terms by better primary-to-regulated output coupling
- Avoid DCM operation by relating primary-to-secondary couplings to loads

# Prediction of small-signal dynamics

---

The extended cantilever model can also be used to predict the converter control-to-output transfer function


- Depends on operating modes of auxiliary windings
- Significant changes observed when auxiliary winding changes from DCM to CCM

Computer modeling method is described in reference [18]

- Small-signal frequency response is generated by *Mathematica*, based on converter impulse responses generated by PSPICE or PETS
- Approach automatically accounts for changes in operating mode
- Transformer was simulated using  $N$ -port model
- Simulations converged quickly and easily, even though system contained eight states

# Measured $N$ -port parameter model

## Flyback transformer example

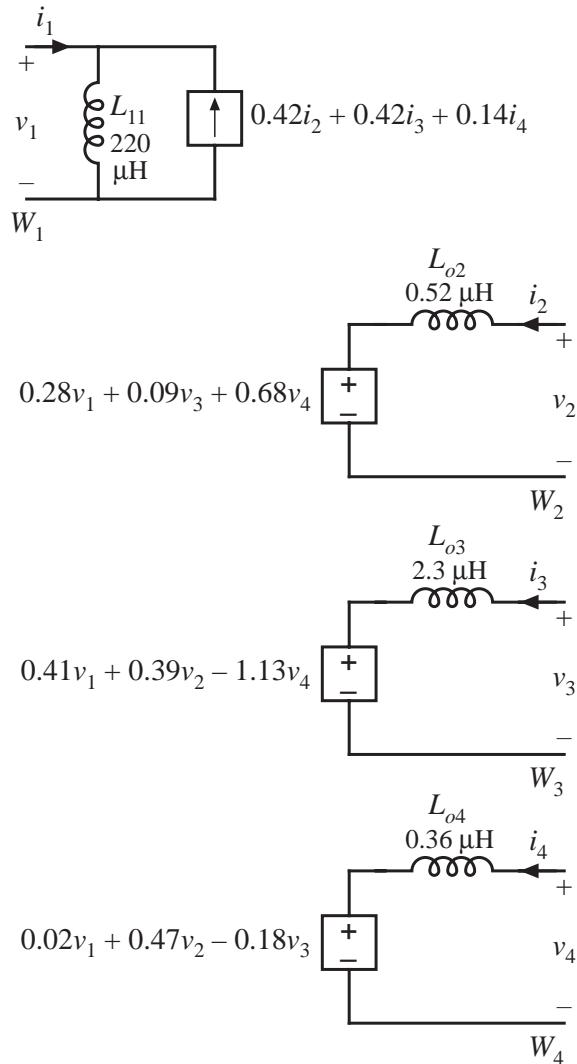

The  $n$ -port model is well-suited for simulation in PSpice or PETS

The number of inductances is equal to the number of states in a multiple-winding transformer


# Measured and predicted transfer functions

## Flyback converter example



Small-signal CCM duty-cycle to  $W_4$  output transfer functions

- (a) with  $W_2$  and  $W_3$  outputs operating in DCM
- (b) with  $W_2$  and  $W_3$  outputs operating in CCM

### Measurements

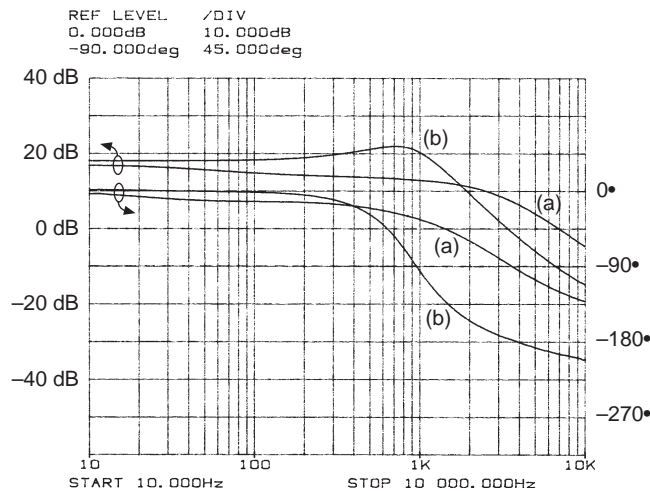

### Predictions of model

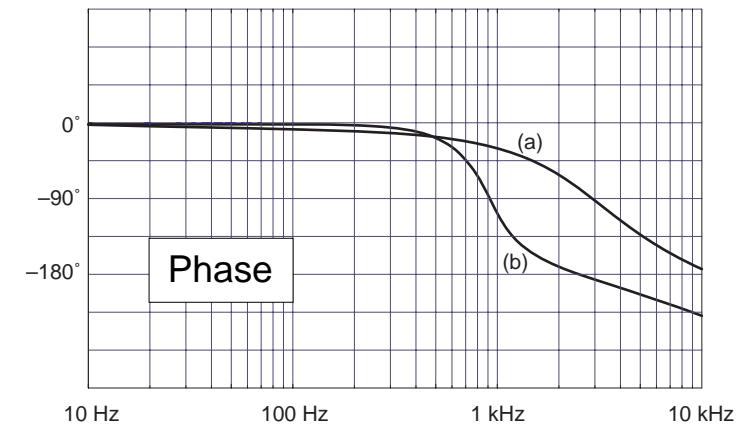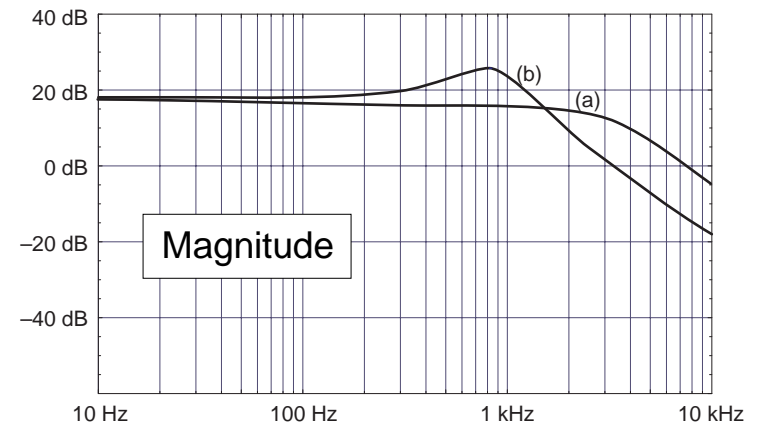


# Summary - Part 2

---

- Two flyback converter cases considered: (1) passive voltage-clamp snubber and (2) active-clamp snubber
- Multiple-output flyback converter has complex operation strongly affected by the transformer leakage inductances
- Extended cantilever model offers easy qualitative explanation of all details of operation
- General analytical models derived to predict static cross-regulation in converters with arbitrary number of outputs
- Cross-regulation mechanisms: DCM operation and output resistances due to leakage inductances are now well understood
- The models can be used to evaluate and compare magnetics designs, and to test various approaches to improve cross-regulation
- The extended cantilever model can also be used to correctly predict the converter control-to-output transfer function, and to investigate frequency-responses at various load conditions
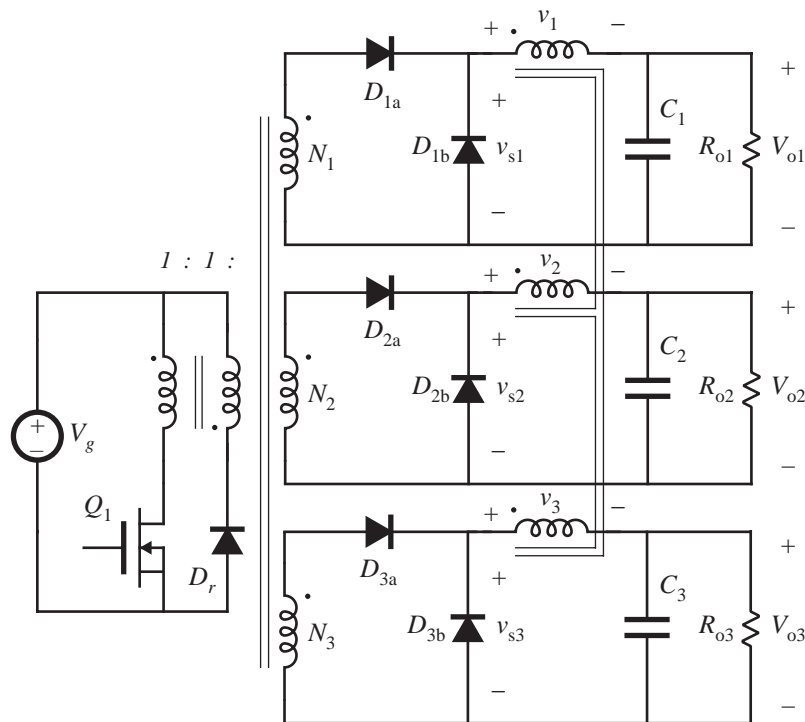
### 3. Cross Regulation in Forward Converters with Coupled Inductors



- Conduction losses
  - diodes
  - windings
  - esr
- Unequal diode conduction times due to the transformer leakage inductances
- Discontinuous conduction modes




# Objectives

---


- Explain effects of inductor coupling on cross-regulation using the extended cantilever magnetics model
- Find general solution for the discontinuous-mode boundaries and steady-state conversion ratio
- Discuss approaches to coupled-inductor design:
  - Near-ideal coupling
  - Moderate coupling
  - “Zero-ripple” approach
- Compare predictions with experimental results
- Point to dynamic response considerations
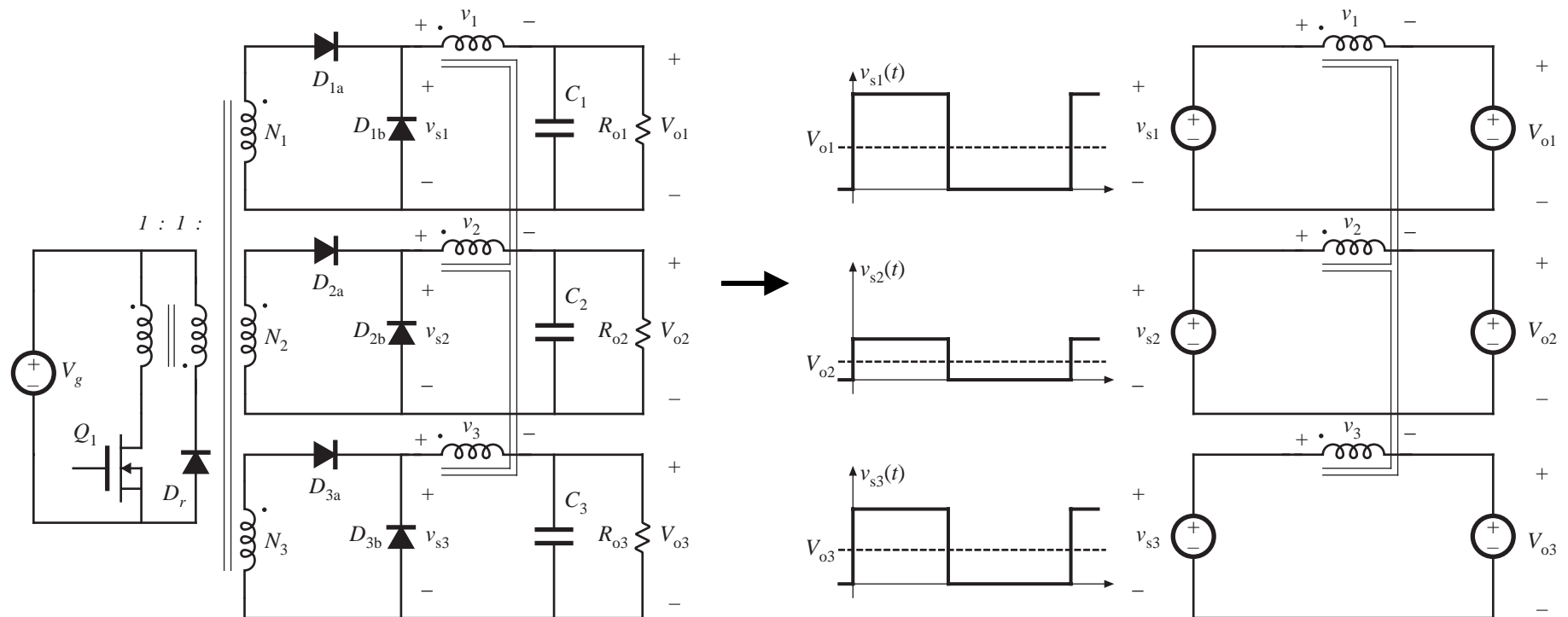
# DCM Analysis Using the Extended Cantilever Model




Step 1: Voltage waveforms across coupled-inductor windings  
(assume all outputs operate in continuous conduction mode)
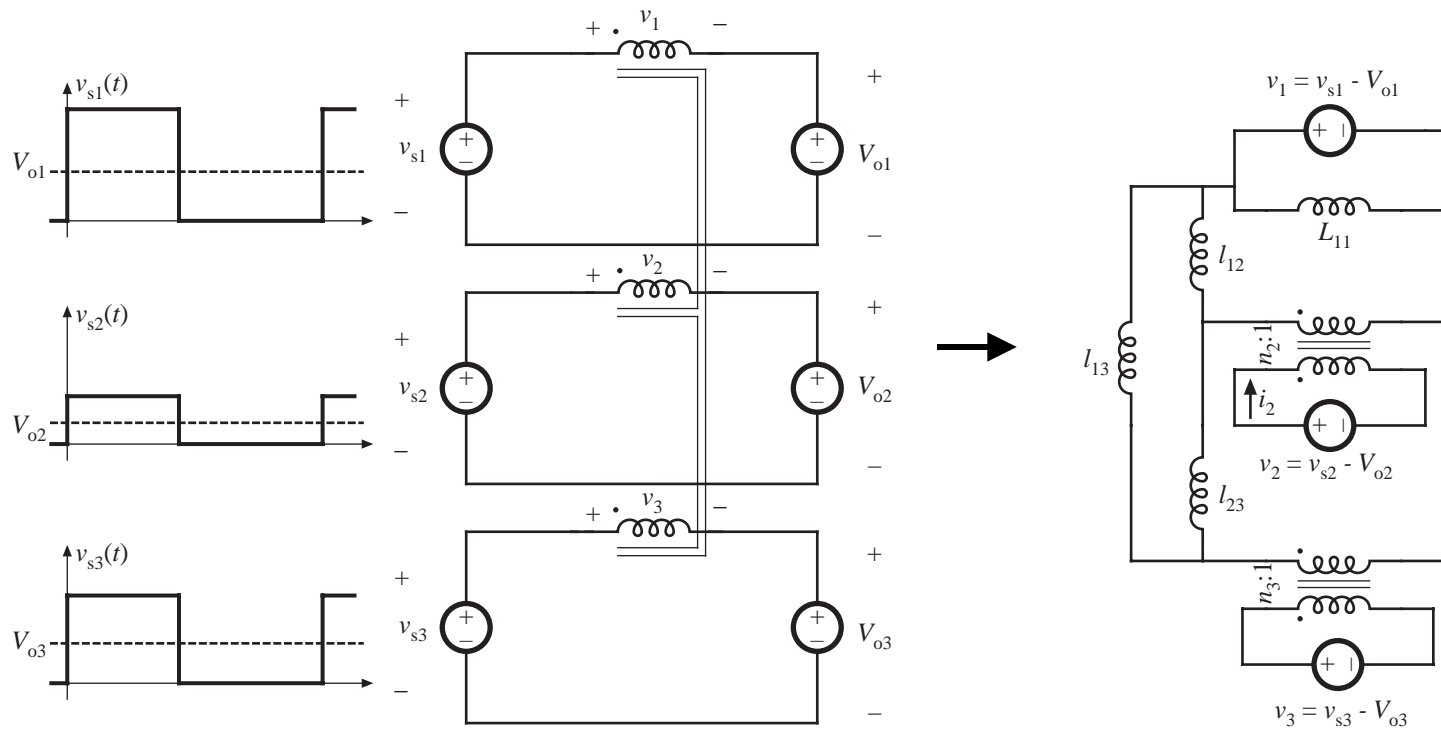
# DCM Analysis Using the Extended Cantilever Model




Step 2: Use the extended cantilever model for the coupled inductor
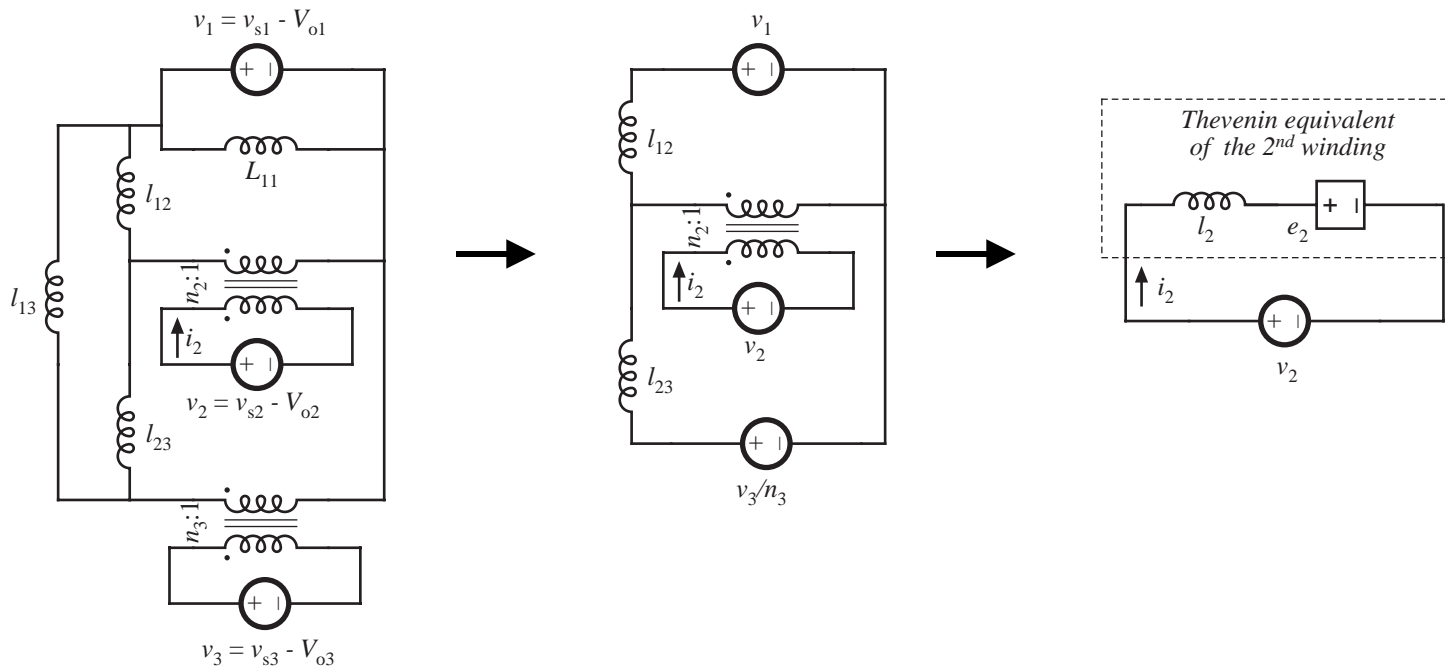
# DCM Analysis Using the Extended Cantilever Model




Step 3: Find Thevenin equivalent for one of the windings
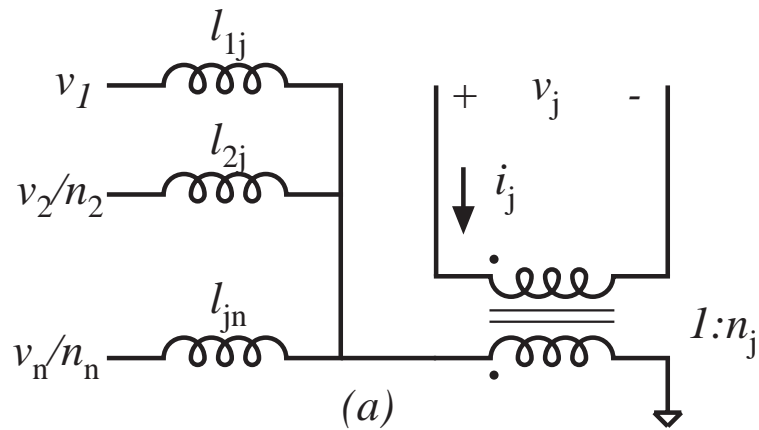
# Thevenin Equivalent for the $j^{\text{th}}$ Winding





$$e_j = \sum_{\substack{k=1, \dots, n \\ k \neq j}} a_{jk} v_k$$
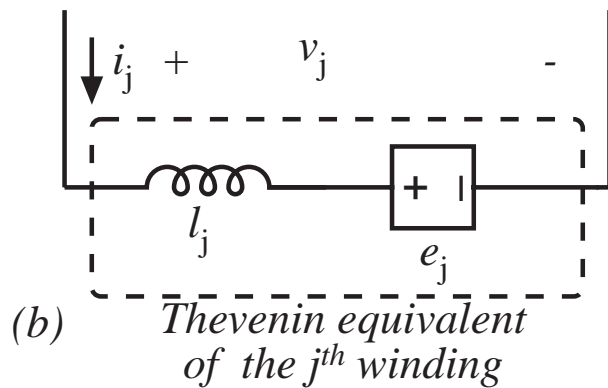
$$a_{jk} = \frac{1}{n_j n_k} \frac{l_j}{l_{jk}}$$



$$\frac{1}{l_j} = \frac{1}{n_j^2} \sum_{\substack{k=1, \dots, n \\ k \neq j}} \frac{1}{l_{jk}}$$
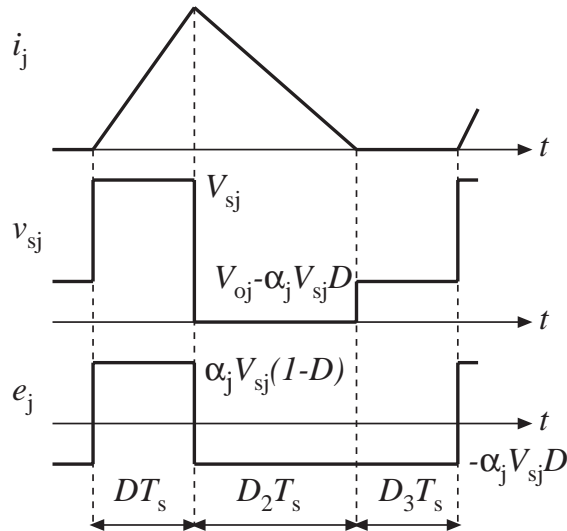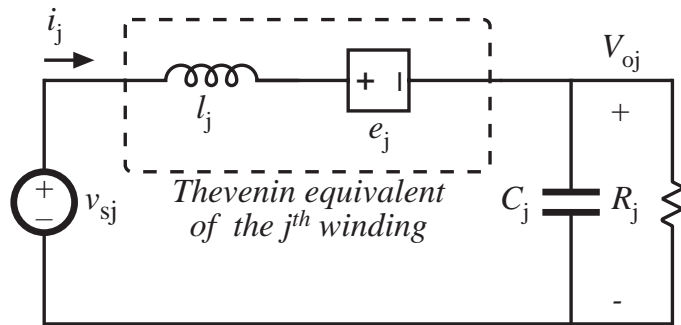
# CCM Condition for the $j^{\text{th}}$ Winding



$$\frac{v_1}{N_1} = \frac{v_2}{N_2} = \dots = \frac{v_n}{N_n}$$

$$e_j = \alpha_j v_j, \quad \alpha_j = \sum_{\substack{k=1, \dots, n \\ k \neq j}} a_{jk} \frac{N_j}{N_k}$$

$$l_j \frac{di_j}{dt} = \begin{cases} (V_{sj} - V_{oj})(1 - \alpha_j), & 0 \leq t \leq DT_s \\ -V_{oj}(1 - \alpha_j), & DT_s < t \leq T_s \end{cases}$$

$$\Delta i_j = \frac{V_{oj} |1 - \alpha_j|}{2l_j f_s} (1 - D)$$

$$k_j \geq (1 - D), \quad k_j = \frac{2l_j f_s}{R_j} \frac{1}{|1 - \alpha_j|} = \frac{K_j}{|1 - \alpha_j|}$$

# DC Conversion Ratio

---

---

- In CCM:


$$\frac{V_{oj}}{V_{sj}} = D$$

- Output  $j$  in DCM, other outputs in CCM:

$$\frac{V_{oj}}{V_{sj}} = \frac{2(1 - (1 - D)\alpha_j)}{1 - \frac{k_j \alpha_j}{D} + \left(1 + \frac{k_j \alpha_j}{D}\right) \sqrt{1 + \frac{4k_j(1 - \alpha_j)}{(D + k_j \alpha_j)^2}}}$$

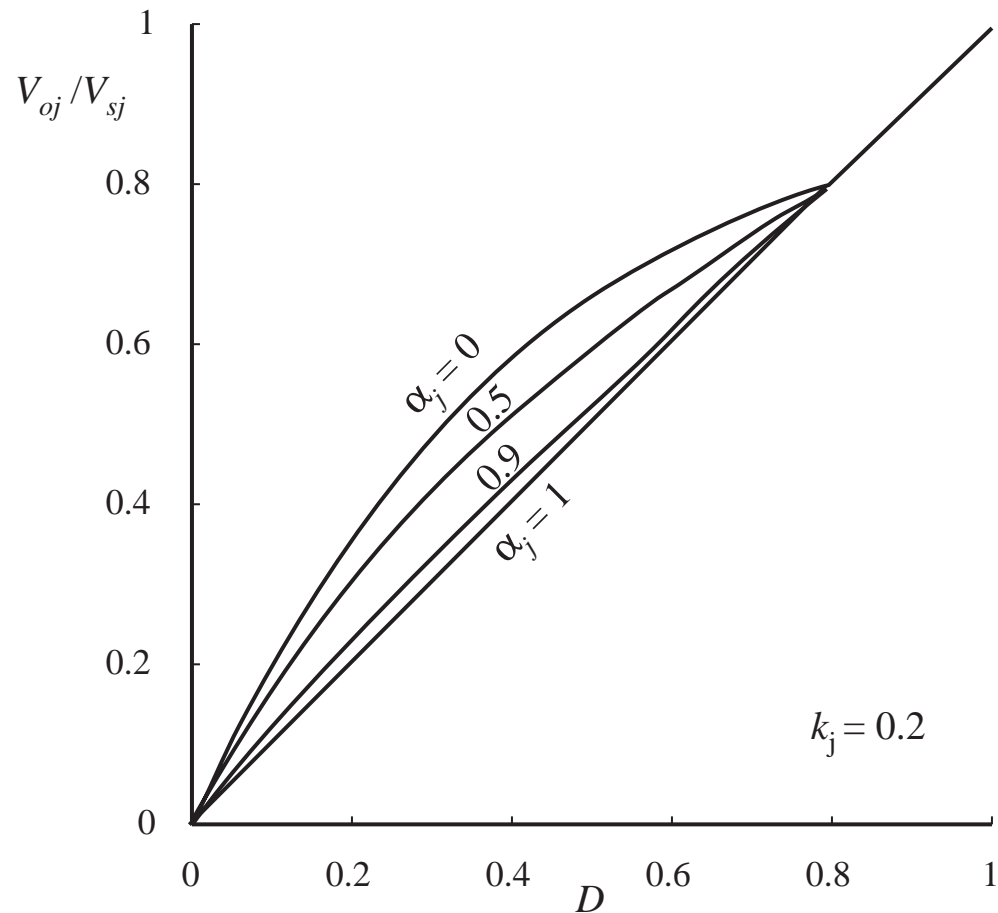
# DC Conversion Ratio

- $\alpha_j = 0$ :  
No coupling
- $\alpha_j = 1$ :  
“Zero-ripple” approach,  
CCM at any load
- Smaller  $l_j$ :  
DCM operation more likely;  
Worse cross-regulation in  
DCM





# Experimental Example

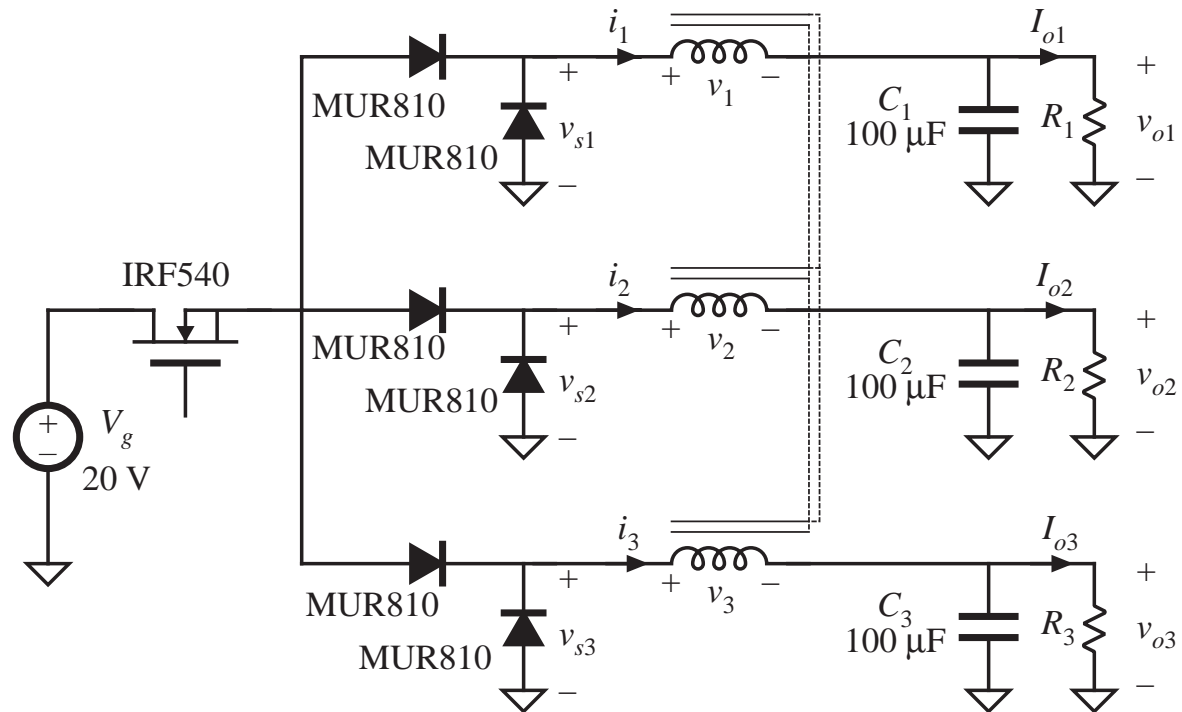


3-output converter,  $V_{o1}$  is the main regulated output at 5.1V

# Coupled-Inductor Design Examples

---

---

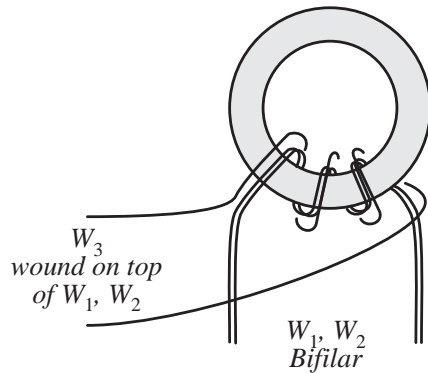


## Design #1:

W1 turns: 24

W2 turns: 24, tightly coupled to W1

W3 turns: 24, moderately coupled to W1

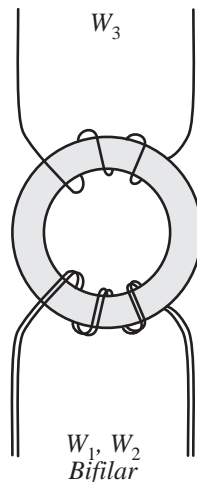

## Design #2:

W1 turns: 24

W2 turns: 24, tightly coupled to W1

W3 turns: 28, poorly coupled to W1, # of turns selected for “zero-ripple”

Magnetics Inc. 58254 powdered iron core

# Model parameters

---

## Design #1:

$$n_2=1.004, n_3=0.919, l_{12}=0.36\mu\text{H}, l_{13}=21.3\mu\text{H}, l_{23}=16.4\mu\text{H}$$

$$l_2=0.36\mu\text{H}, \alpha_2=1.006 \text{ (W2 tightly coupled to W1)}$$

$$l_3=7.81\mu\text{H}, \alpha_3=0.919 \text{ (W3 moderately coupled to W1)}$$


## Design #2

$$n_2=0.997, n_3=0.994, l_{12}=0.36\mu\text{H}, l_{13}=21.3\mu\text{H}, l_{23}=16.4\mu\text{H}$$

$$l_2=0.38\mu\text{H}, \alpha_2=0.99 \text{ (W2 tightly coupled to W1)}$$

$$l_3=44.3\mu\text{H}, \alpha_3=0.994 \text{ ("zero-ripple" approach in W3-to-W1 coupling)}$$
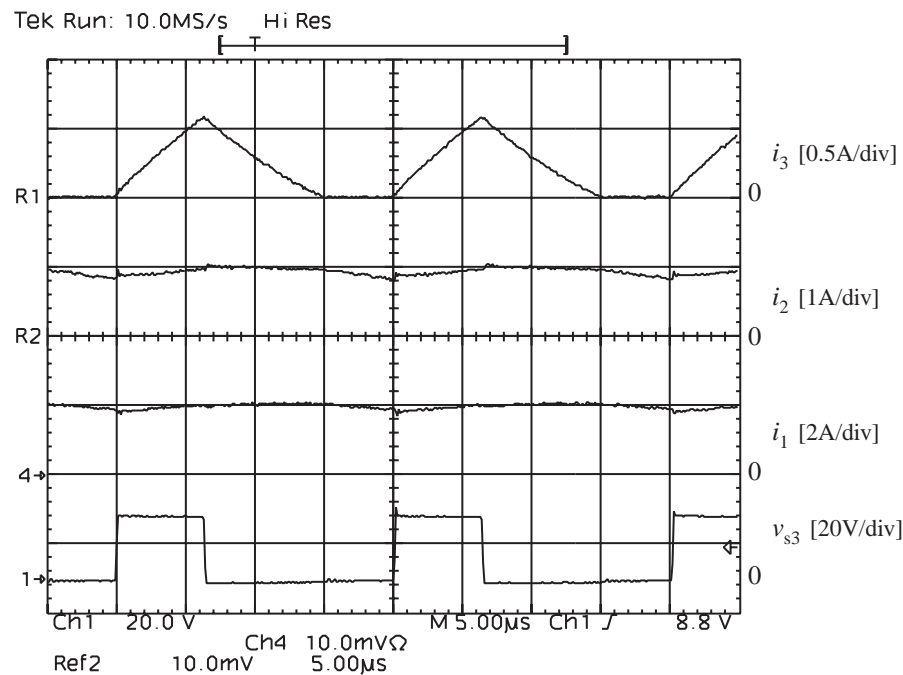
# Near-Ideal Coupling vs. Moderate Coupling Coupled-Inductor Design #1




W3 lightly loaded, operates in  
DCM

$$V_{o1}=5.1\text{V}, I_{o1}=2\text{A}, V_{o2}=5.3\text{V}, I_{o2}=0.97\text{A}, V_{o3}=5.6\text{V}, I_{o3}=0.2\text{A}, V_g=20\text{V}, f_s=100\text{kHz}$$
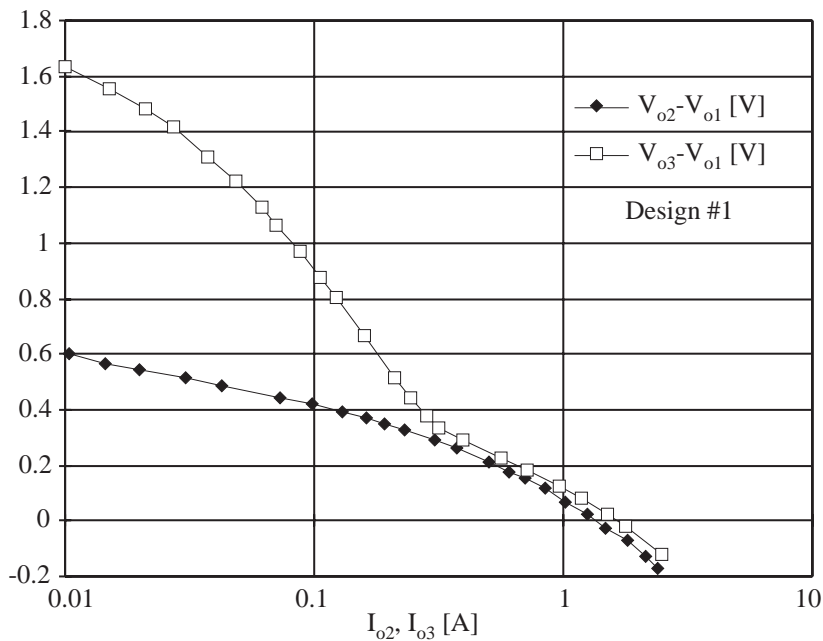
# Near-Ideal Coupling vs. Moderate Coupling Coupled-Inductor Design #1


Measured closed-loop cross-regulation,  $V_{o1}$  regulated at 5.1V,  $I_{o1}=2A$



Worse cross-regulation on the moderately-coupled W3 because of DCM operation

# Near-Ideal Coupling vs. Zero-Ripple Approach

## Coupled-Inductor Design #2

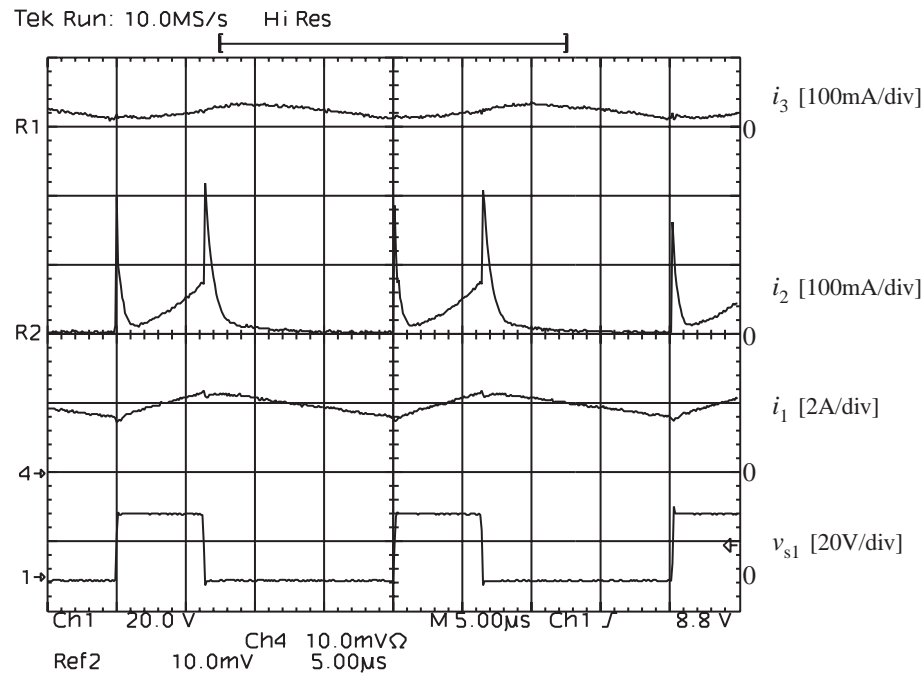


Current spikes and DCM operation on the tightly coupled W2 output

CCM operation and small current ripple on the W3 output

$$V_{o1}=5.1\text{V}, I_{o1}=2\text{A}, V_{o2}=5.7\text{V}, I_{o2}=0.2\text{A}, V_{o3}=5.7\text{V}, I_{o3}=0.2\text{A}$$
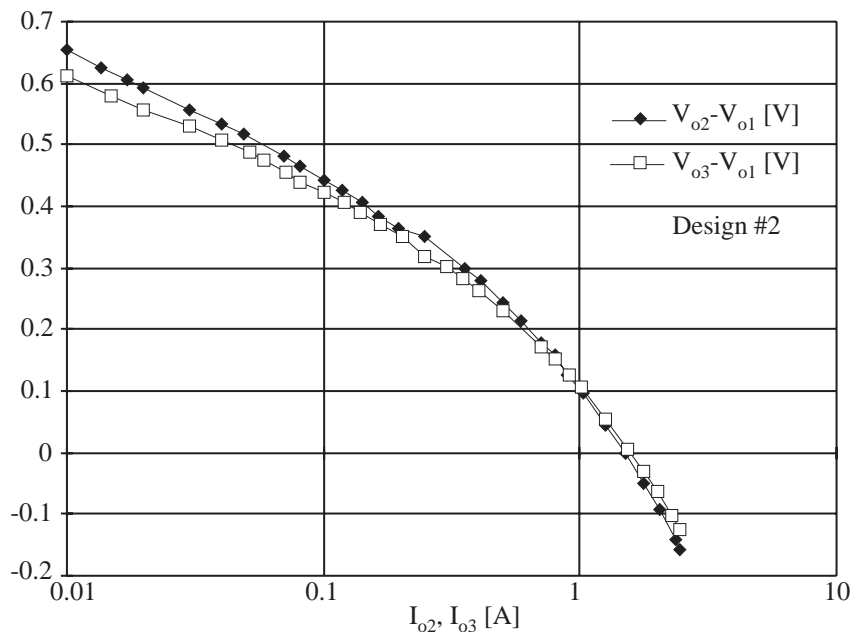
# Near-Ideal Coupling vs. Zero-Ripple Approach Coupled-Inductor Design #2



Measured closed-loop cross-regulation,  
 $V_{o1}$  regulated at 5.1V,  $I_{o1}=2A$


The tightly-coupled output operates in DCM and has large current spikes

Tight coupling may not be easy to achieve with larger number of outputs

The “zero-ripple” approach gives slightly better cross-regulation than tight coupling, and can in practice be achieved easily for any number of outputs

In the “zero-ripple” approach, one output operates with non-zero ripple determined by  $L_{11}$
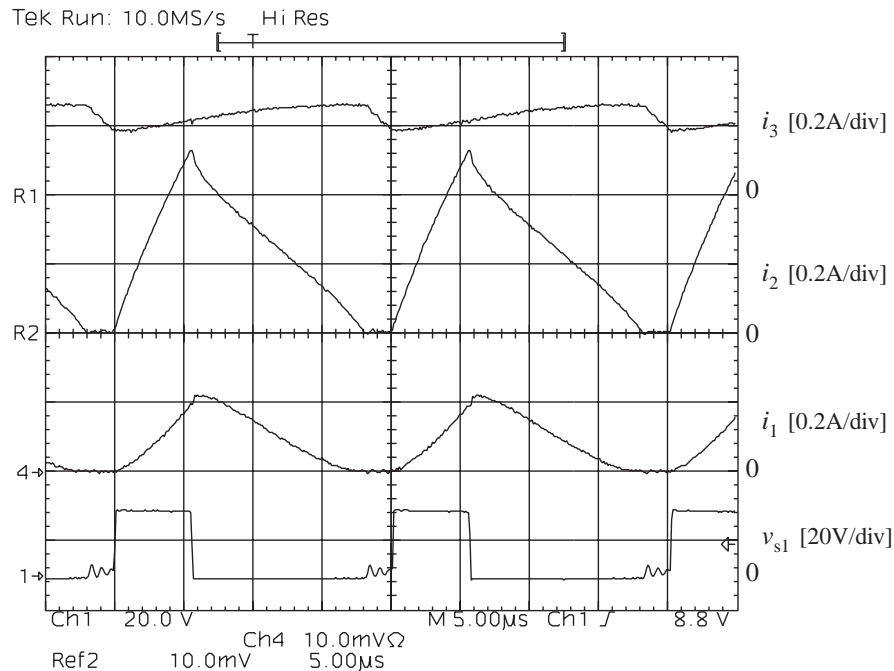
# Zero-Ripple Approach: DCM on Other Outputs



W1 and W2 in DCM, so:


Voltage waveforms across W1 and W3 are no longer proportional

Cross-regulation between the regulated W1 output and the W3 output is affected because of relatively poor coupling between W1 and W3

W3 current has increased ripple


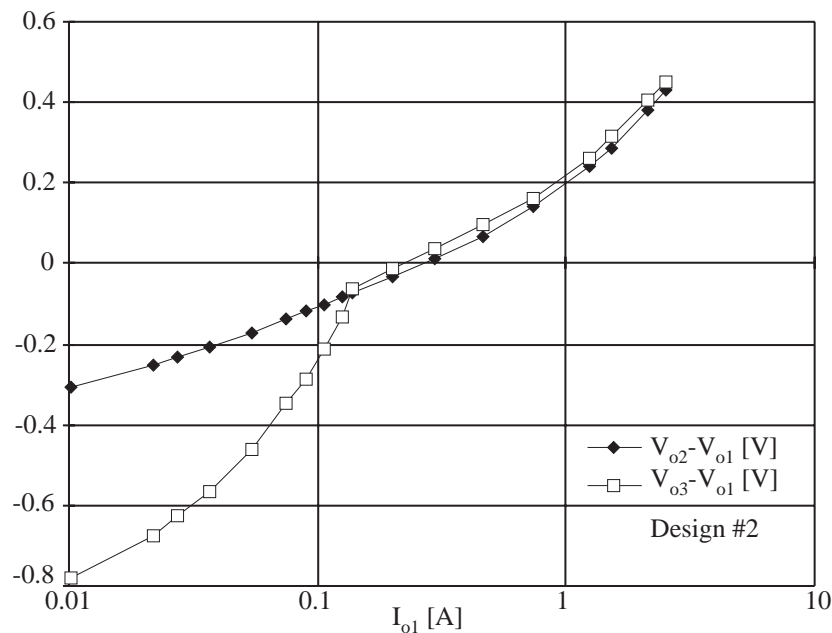
# Zero-Ripple Approach: DCM on Other Outputs



Since W3 is poorly coupled to W1, DCM on W1 causes poor cross-regulation on W3

“Zero-ripple” approach works best if the non-zero-ripple output always operates in CCM

Possible approach:

Use a heavily loaded output as the non-zero-ripple output

Adjust the number of turns on the other windings to scale effective turns ratios and achieve the “zero-ripple” condition of equal induced and applied voltages to the winding

# Coupled-Inductor Design Approaches

---


- Near-ideal coupling: (very small  $l_j$ ,  $\alpha_j \approx 1$ )
  - Good cross-regulation even in DCM
  - Exact matching of turns ratios is necessary
  - Significant current spikes, larger ripples
  - May be difficult to achieve in practice
- Moderate coupling (moderate  $l_j$ ,  $\alpha_j \neq 1$ )
  - Degraded cross-regulation in DCM
- “Zero-ripple” approach (moderate to large  $l_j$ ,  $\alpha_j \approx 1$ )
  - Effective turns ratios match the ratios of imposed voltages
  - Effective turns ratios differ from the turns ratios of physical windings
  - CCM operation down to almost zero load
  - Very small ripples
  - Best static cross-regulation if non-zero-ripple output always operates in CCM

# Frequency-Response Considerations

---


- Experimental 5-output forward converter with current-mode programming used in the feedback loop
- Coupled-inductor had moderately coupled auxiliary windings with physical turns ratios matching the physical turns ratios on the transformer secondaries
- Load variations on the auxiliary outputs produced very large changes in the experimental control-to-output response and cross-over frequency of the feedback loop
- Observed behavior can be explained once discontinuous conduction modes on the auxiliary outputs are taken into account

# 2-output Circuit Model

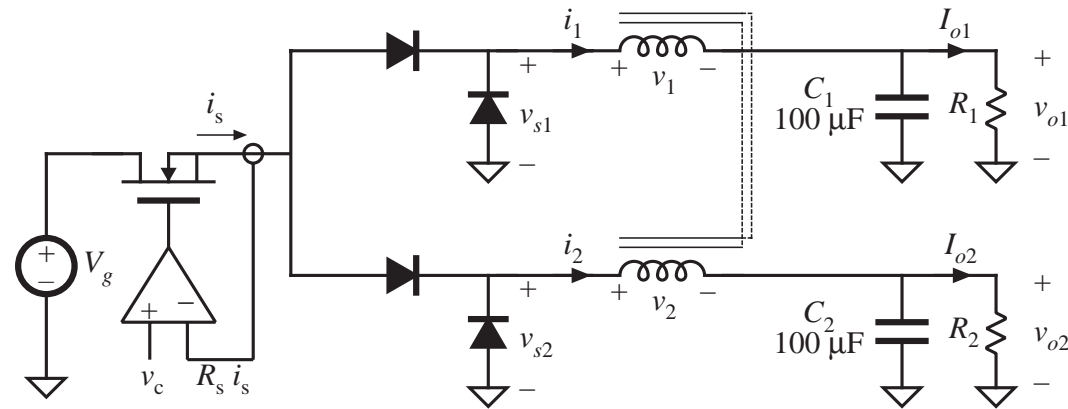

- $V_{o1}$  is the main regulated output
- Coupled-inductor design is using windings W1, W3 of the design #1 with W3 moderately coupled to W1
- Control-to-output frequency response was found using the method of reference [18]
- Load on the auxiliary output changed to move from CCM to DCM

# Control-to-output responses

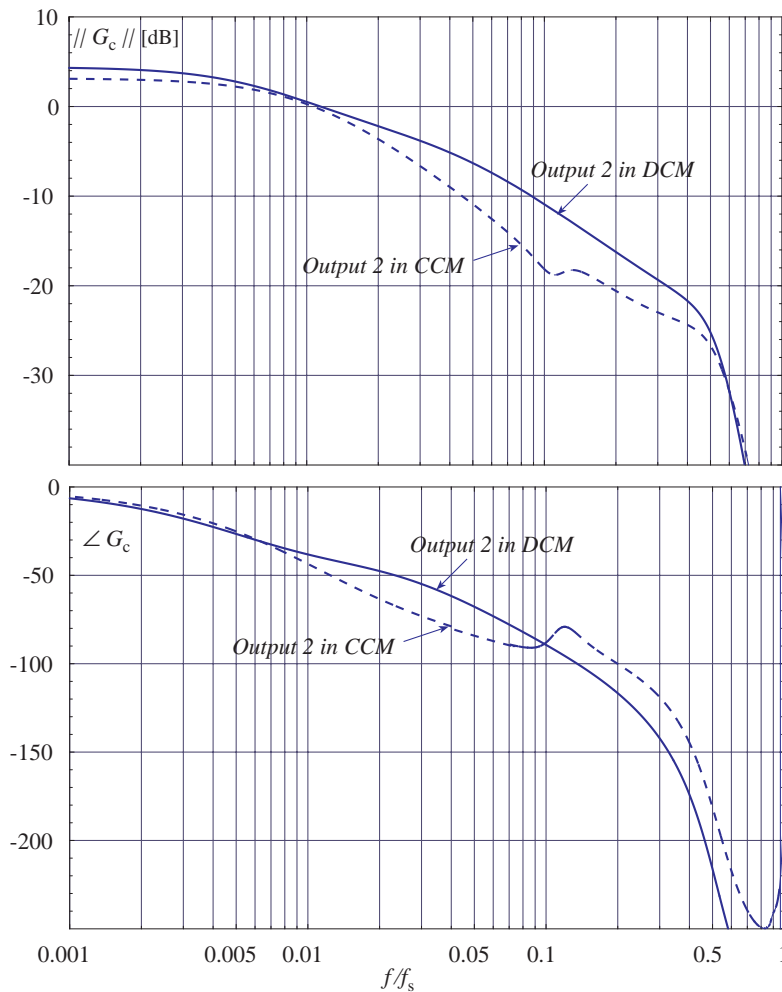


The model correctly predicts a significant change in the magnitude and phase responses

A factor of two change in the cross-over frequency  $f_c$  would result if  $f_c$  is between 5% and 20% of the switching frequency
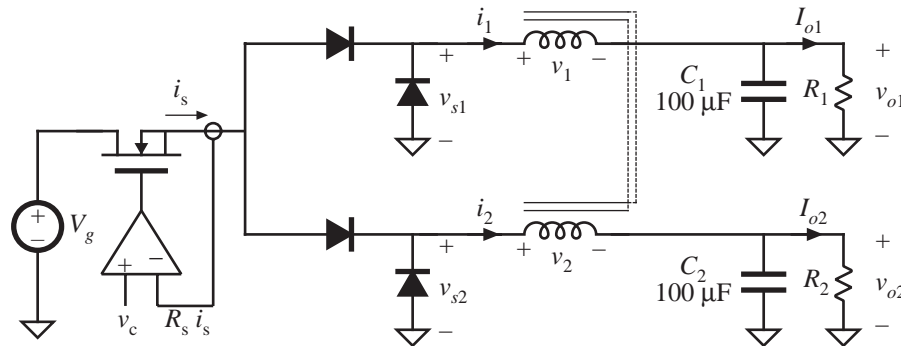
# Explanation

- Simple model for current-mode programming predicts a single-pole response with pole frequency inversely proportional to the output filter capacitance
- When the auxiliary output operates in CCM, the effective filter capacitance referred to the main output is  $C_1 + C_2$
- When the auxiliary output operates in DCM, the effective filter capacitance referred to the main output reduces to  $C_1$ ;  $C_2$  is “disconnected” from the main feedback loop because the auxiliary output operates in DCM



# Summary - Part 3

---

- Extended cantilever model used to explain operation of the coupled-inductor in a multiple-output forward-type converter
- General analytical solution found for DCM/CCM boundaries, and for conversion ratio when one of the outputs operates in DCM
- Three coupled-inductor design approaches evaluated and compared:
  - near-ideal coupling
  - moderate coupling
  - “zero-ripple” approach
- Effects of possible DCM operation in the auxiliary outputs on the main control loop were pointed out and explained