

Power Electronics Notes - D. Perreault

$$V_{\text{eq}} = \sum_{n=0}^{\infty} B_n \cos(n\omega t + \phi_n) e_n(\omega)$$

$$\text{If } H(\omega) = \frac{V_o(\omega)}{V_x(\omega)} \Rightarrow V_o = \sum_n |H(n\omega)| \cos(n\omega t + \phi_n + \angle H(n\omega))$$

Main point: we can replace difficult to handle part of circuit with an equivalent voltage source, then use linear circuit theory to analyze from there.

Summary of Analysis Techniques


- Method of assumed states
- Periodic Steady State
- Equivalent Source Replacement



Introduction To Rectifier Circuits

Reading: KSV Chapter 3

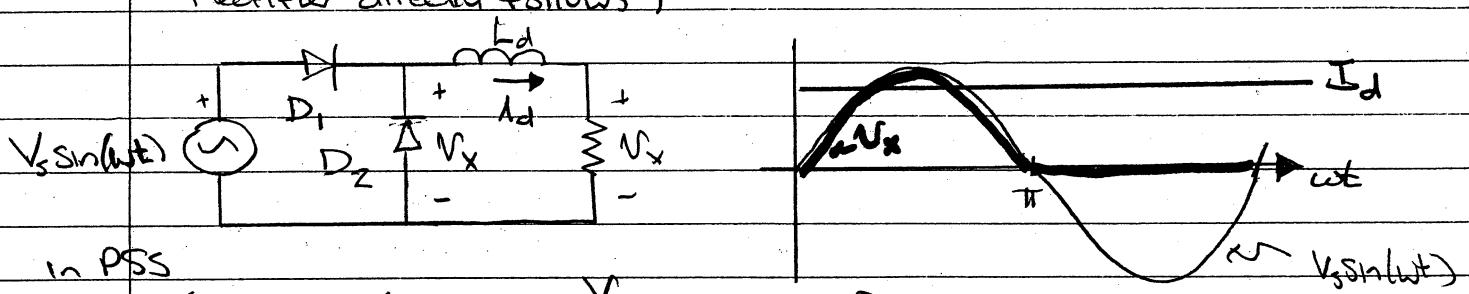Start w/ simple half-wave rectifier (full-bridge rectifier directly follows)



in PSS

$$\langle V_o \rangle = \langle V_x \rangle = \frac{V_s}{\pi}$$

$$\text{If } L_d \text{ big} \rightarrow I_d \approx I_o = \frac{V_s}{\pi R}$$

If $L_d/R \gg \frac{2\pi}{\omega} \Rightarrow$ we can approximate load ckt as a constant current


Power Electronics Notes - D. Perreault

* Load Regulation

Now Consider adding some ac-side inductance L_c
 (reactance $X_c \triangleq \omega L_c$)

→ Common situation. Transformer leakage or line inductance, machine winding inductance, etc.

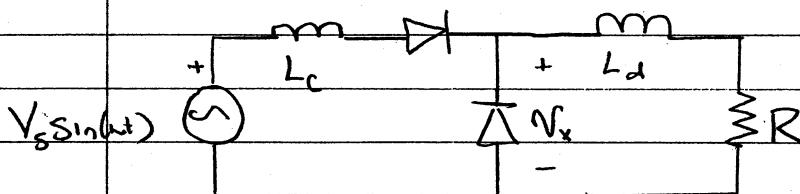
$\rightarrow L_c$ is typ. $\ll L_d$ (filter inductance) as it is a parasitic element.



Assume $L_d \sim \infty$ (so ripple current is small)

We can approximate load as a "special" current source

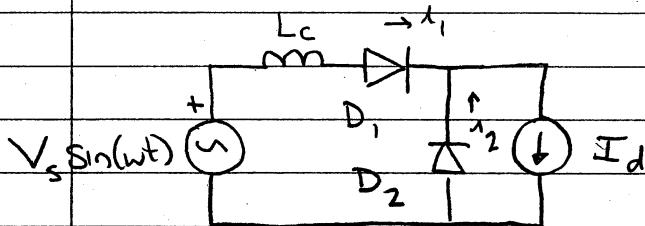\rightarrow "special" since $\langle V_L \rangle = 0$ in P.S.S. ; $I_d = \langle V_a / R \rangle$




Assume we start with D_2 conducting, D_1 off ($V_{sink} < 0$)
 What happens when $V_{sink}(t)$ crosses zero?

\rightarrow D, off no longer valid

→ but just after turn on 1, still = 0

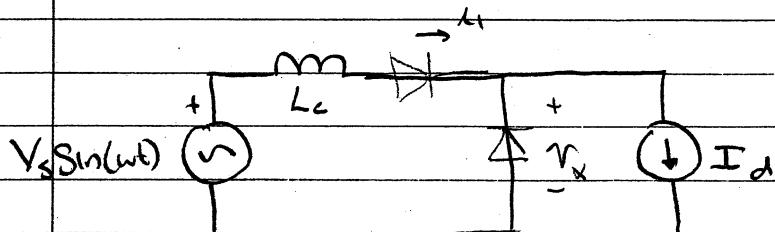$\therefore D_1, D_2$ both on during a commutation period
where current switches from D_2 to D_1



D_2 will stay on as long as $\lambda_2 > 0$ ($\lambda_1 < I_d$)

(8)


Power Electronics Notes - D. Perreault

Analyze: $\frac{dI_1}{dt} = \frac{1}{L_c} V_s \sin(\omega t)$

$$I_1(t) = \int_0^{\omega t} \frac{V_s}{\omega L_c} \sin(\omega t) d(\omega t)$$

$$= \frac{V_s}{\omega L_c} \cos(\varphi) \Big|_{\omega t}^0$$
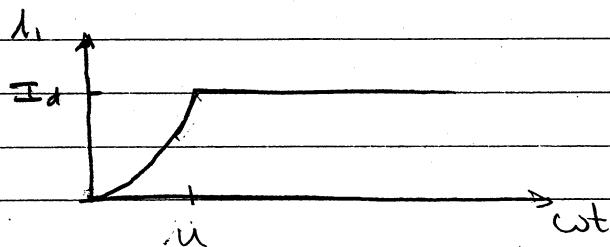
$$= \frac{V_s}{\omega L_c} [1 - \cos(\omega t)]$$






commutation ends at $\omega t = u$ when $I_1 = I_d$

$$I_d = \frac{V_s}{\omega L_c} [1 - \cos u]$$

$$\Rightarrow \boxed{\cos u = 1 - \frac{\omega L_c I_d}{V_s}}$$

★ Commutation period.

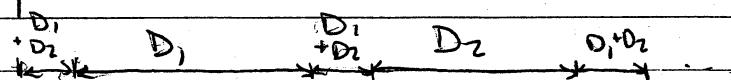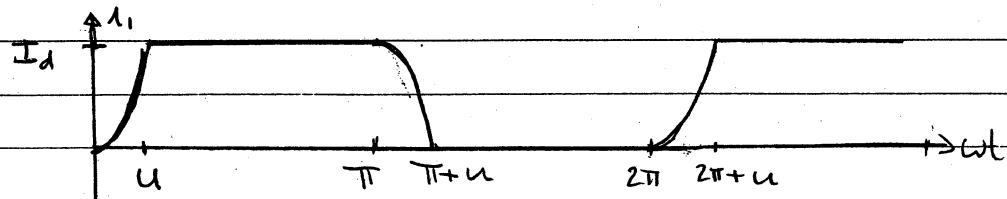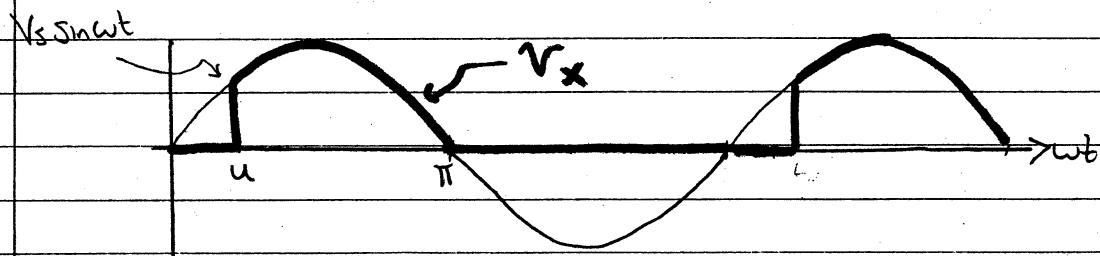

Power Electronics Notes D. Perreault

As compared to the case of no commutating inductance, we lose a piece of output voltage during commutation. We can calculate the average output voltage in P.S.S. from $\langle V_x \rangle$

$$\begin{aligned}\langle V_x \rangle &= \frac{1}{2\pi} \int_u^{\pi} V_s \sin(\varphi) d\varphi \\ &= \frac{V_s}{2\pi} \left[\cos(u) + 1 \right]\end{aligned}$$

from before $\cos u = 1 - \frac{\omega L_c I_d}{V_s} = 1 - \frac{X_c I_d}{V_s}$



$$\boxed{\langle V_x \rangle = \frac{V_s}{\pi} \left[1 - \frac{\omega L_c I_d}{V_s} \right]}$$

So average output voltage drops with

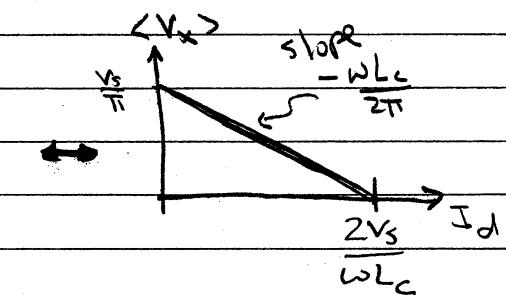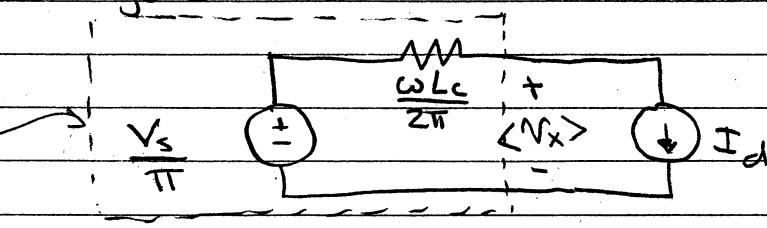1. Increased current
2. Increased frequency
3. decreased source voltage

we get the "Ideal" no L_c case at no load.

We can make a dc-side Thevenin model for such a system as



* This LOAD REGULATION is a major consideration in most rectifier systems.

→ voltage changes w/ load

→ max output power limitation

? All due to nonzero commutation time because of ac-side reactance.

⇒ This effect occurs in most rectifier types (full-wave, multi-phase, thyristor, etc.)