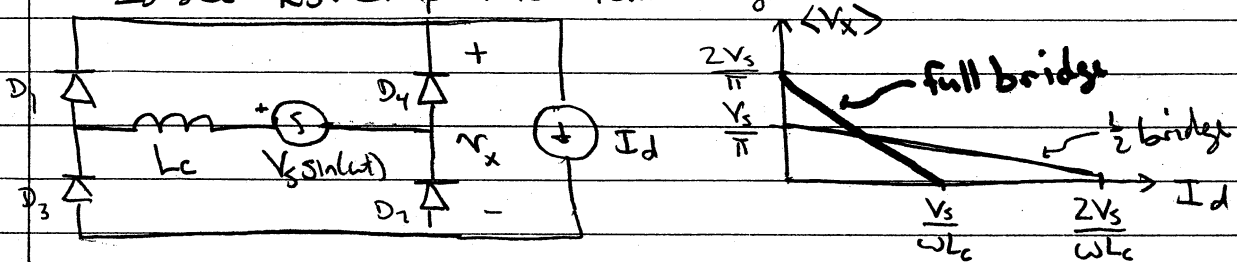


Power Electronics Notes D. Perreault

Full-bridge rectifier has similar problem (similar analysis)
 \Rightarrow see KSV Chap 4 for full bridge



★★

POWER FACTOR + MEASURES OF DISTORTION

\rightarrow Read KS + V ch. 3

look at the AC side.

Definitions + Identities

2 functions x, y orthogonal over $[a, b]$ if

$$\int_a^b x(t)y(t) dt = 0$$

Now $\int_0^{2\pi} \sin(mt) \sin(nt + \phi) dt = 0$ if $n \neq m$

\Rightarrow Sinusoids of different frequencies are orthogonal

$$\int_0^{2\pi} \sin(\omega t) \cos(\omega t) d(\omega t) = 0$$

\Rightarrow sin. + cosine are orthogonal


In general $\frac{1}{2\pi} \int_0^{2\pi} \sin(\omega t) \sin(\omega t + \phi) = \frac{1}{2} \cos \phi$

These definitions will be useful for calculating power, etc.

Power Electronics Notes - D. Perreault

Background

Suppose we plug a resistor into the wall

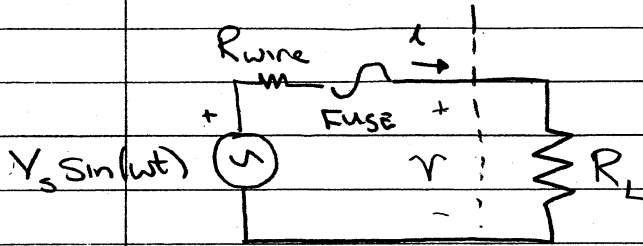

$$P = \langle V i \rangle = V_{rms} I_{rms}$$


$$= I_{rms}^2 R$$

The fuse is rated for a specified RMS current

→ above that, it will blow so that dissipation in R_{wire} does not start a fire

→ 115 V_{ac,rms}, 15 A_{rms} fuse we get ~ 1.7 kW max from wall (neglecting R_{wire})

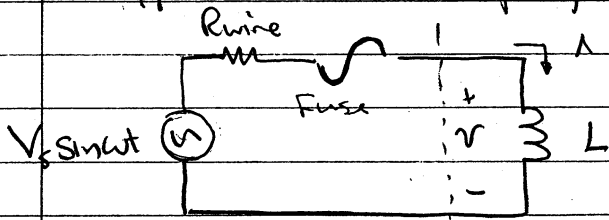Suppose instead we plug an inductor into the wall



neglecting R_{wire} ,

$$i = -\frac{V_s}{\omega L} \cos(\omega t)$$

$$\langle P \rangle = \frac{1}{2\pi} \int V(t) i(t) d(\omega t) = -\frac{V_s^2}{2\pi \omega L} \int \sin(\omega t) \cos(\omega t) d\omega t = 0!$$

(of course!)

mathematically, it is because V, i are orthogonal

while we draw no real power, we still draw current

$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i^2(\omega t) d\omega t} = \frac{1}{\sqrt{2}} \frac{V_s}{\omega L}$$

$$@ 115V, 60Hz, L = 20mH \rightarrow I_{rms} \cong 15A$$

So we still will blow the fuse (to protect the wall wiring) even though we do not draw any real power at the output!
(→ some power dissipated in R_{wire})

⇒ in this case we are not utilizing the source well!

Power Electronics Notes - D. Perreault


- ★ To provide a measure of the utilization of the source we define Power Factor

$$\text{P.F.} \triangleq \frac{\langle P \rangle}{V_{\text{rms}} I_{\text{rms}}}$$

Real Power P
apparent power S

For a resistor $\langle P \rangle = V_{\text{rms}} I_{\text{rms}} \rightarrow \text{P.F.} = 1$ best utilization
for an inductor $\langle P \rangle = 0 \rightarrow \text{P.F.} = 0$ worst utilization

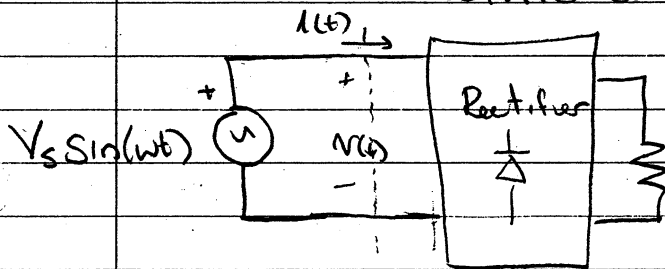Consider a rectifier drawing some current waveform



Note: $I_{\text{RMS}} =$

$$\sqrt{\frac{1}{2}I_1^2 + \frac{1}{2}I_2^2 + \frac{1}{2}I_n^2 + \dots}$$

Express $i(t)$ as a Fourier series

$$i(t) = \sum_{n=0}^{\infty} I_n \sin(n\omega t + \phi_n)$$

sum of weighted shifted sinusoids

$$\langle P \rangle = \frac{1}{2\pi} \int_{2\pi} v(t) i(t) d(\omega t)$$

$$= \frac{1}{2\pi} \int_{2\pi} V_s \sin(\omega t) \sum_n I_n \sin(n\omega t + \phi_n)$$

$$= \sum_{n=0}^{\infty} \frac{1}{2\pi} \int_{2\pi} V_s I_n \sin(\omega t) \sin(n\omega t + \phi_n)$$

by orthogonality all terms except fundamental dropout!

$$\langle P \rangle = \frac{1}{2\pi} \int_{2\pi} V_s I_1 \sin(\omega t) \sin(\omega t + \phi_1)$$

Power Electronics Notes - D. Perreault

$$\langle P \rangle = \frac{1}{2\pi} \int_{2\pi} V_s I_1 \sin(\omega t) \sin(\omega t + \phi_1)$$

$$\langle P \rangle = \frac{V_s I_1}{2} \cos \phi_1 = V_{s,rms} I_{1,rms} \cos(\phi_1)$$

So the only current that contributes to real power is the fundamental component in phase with the voltage

$$P.F. = \frac{V_{rms} I_{1,rms}}{V_{rms} I_{rms}} \cos \phi_1 = \frac{I_{1,rms}}{I_{rms}} \cos(\phi_1)$$

★ we can break down into two factors

$$P.F. = K_d \cdot K_\phi$$

↑ distortion factor
↑ displacement factor

$$P.F. = \left(\frac{I_{1,rms}}{I_{rms}} \right) \cdot \cos(\phi_1)$$

K_d
 K_ϕ

K_d distortion factor (≤ 1) tells us how much the utilization of the source is reduced because of harmonic currents that don't contribute to power

K_ϕ displacement factor (≤ 1) tells us how much utilization is reduced due to phase shift between the voltage + fundamental current.

Power Electronics Notes - D. Perreault

★ Consider another measure of distortion: Total Harmonic Distortion (THD)

$$\text{THD} \triangleq \sqrt{\frac{\sum_{n \neq 1} I_n^2}{I_1^2}}$$

This measures the rms of the harmonics, normalized to the rms of the fundamental (sq. root of the power ratio)

Distortion factor + THD are related:


$$\text{THD} = \sqrt{\frac{\sum_{n \neq 1} I_n^2}{I_1^2}} = \sqrt{\frac{I_{rms}^2 - I_{1,rms}^2}{I_{1,rms}^2}}$$

$$\text{THD}^2 = \frac{I_{rms}^2}{I_{1,rms}^2} - 1$$

$$\frac{I_{rms}^2}{I_{1,rms}^2} = 1 + \text{THD}^2$$

$$K_d = \frac{I_{1,rms}}{I_{rms}} = \sqrt{\frac{1}{1 + (\text{THD})^2}}$$

Example: $V = V_r \sin(\omega t)$

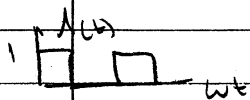


$i(t) = \text{square wave}$

$$\left\{ \begin{array}{l} I_n = \frac{4}{\pi n} \quad n \text{ odd} \\ I_0 = I_{ave} = \frac{1}{2} I_{pk} \end{array} \right.$$

Can find $\rightarrow \text{THD} = 121\%$
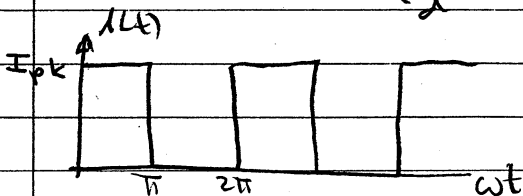
$$K_d = \text{P.F.} = \frac{4/\sqrt{2}}{\sqrt{2}} = \frac{2}{\pi} \approx 0.63$$



Power Electronics Notes - D. Perreault

chap

★ (Passive) Power Factor Compensation KSV 3.4.1

Lets focus on the displacement factor component of power factor. For simplicity, lets assume a linear load (e.g. R-L) so that voltages + currents are sinusoidal.

For sinusoidal V, I P.F. = $\frac{\langle P \rangle}{V_{rms} I_{rms}} = \cos \phi$

ϕ is the power factor angle


- } leading $\phi < 0$ capacitive
- } lagging $\phi > 0$ inductive

Real Power $P = V_{rms} I_{rms} \cos \phi$

★ Define reactive power as

$$Q \triangleq V_{rms} I_{rms} \sin \phi$$

In vector form $\vec{S} = P + jQ$

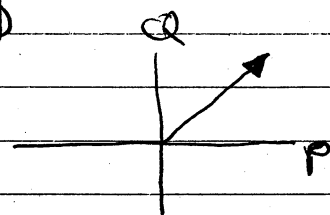


In phasor form $\vec{V}, \vec{I} \rightarrow \vec{S} = \langle V I^* \rangle$

		Units
apparent power	$S = \ \vec{S}\ = V_{rms} I_{rms}$	VA
average power	$\text{Re}\{\vec{S}\} = P = V_{rms} I_{rms} \cos \phi$	W
reactive power	$\text{Im}\{\vec{S}\} = Q = V_{rms} I_{rms} \sin \phi$	VAR

We can use these results to help adjust the displacement factor of a system! (make $Q_{net} \rightarrow 0$)

Power Electronics Notes - D Perreault

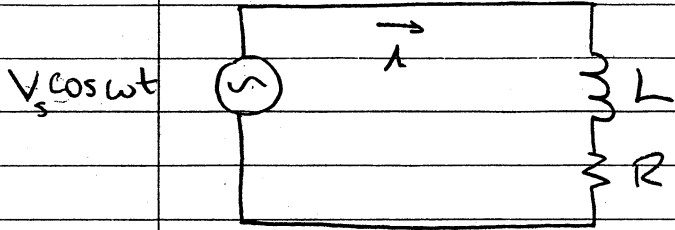Suppose we have an R-L load (e.g. an induction machine)




$$i(t) = \frac{V_s}{\sqrt{\omega^2 L^2 + R^2}} \sin(\omega t - \text{ATAN}\left(\frac{\omega L}{R}\right))$$

voltage-current phase $\phi = \text{ATAN}\left(\frac{\omega L}{R}\right)$


$$\text{P.F.} = \cos\left(\text{ATAN}\left(\frac{\omega L}{R}\right)\right) = \frac{R}{\sqrt{R^2 + \omega L^2}} < 1$$

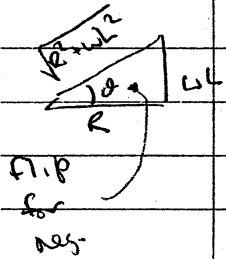Voltage-current phase because $S \triangleq VI^*$



we can add some additional reactive load to balance out + give net unity power factor.
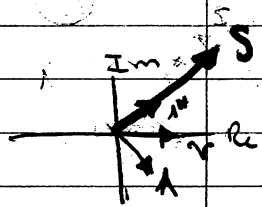
$$S = V_{\text{rms}} I_{\text{rms}} = \frac{1}{2} \frac{V_s^2}{\sqrt{\omega^2 L^2 + R^2}}$$




$$P = S \cos \phi = V_{\text{rms}} I_{\text{rms}} \cos \phi = \frac{V_s^2 R}{2(\omega^2 L^2 + R^2)}$$

$$Q = j S \sin \phi = j V_{\text{rms}} I_{\text{rms}} \sin \phi = \frac{j \omega L V_s^2}{2(\omega^2 L^2 + R^2)}$$

so we have real + Reactive power

Suppose we add a capacitor in parallel

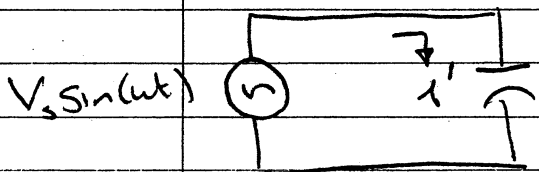

$$Z_c = \frac{1}{j\omega C} = \frac{1}{\omega C} e^{-j\pi/2}$$

$$\frac{1}{Z_c} = \omega C e^{j\pi/2} \quad V_{\text{phase}} - I_{\text{phase}} = -90^\circ$$


$$i' = V_s \omega C \sin(\omega t + \pi/2)$$

$$S' = V_{\text{rms}} i_{\text{rms}} = \frac{1}{2} V_s^2 \omega C \quad P' = 0$$

$$Q' = -j \frac{1}{2} V_s^2 \omega C$$

Power Electronics Notes - D. Perreault

So by placing the Capacitor in parallel

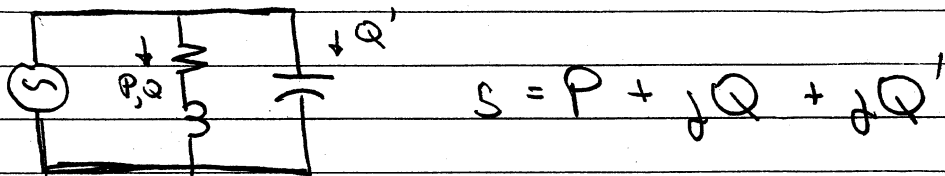

make jQ , jQ' cancel

$$Q + Q' = \pm \frac{\omega L V_s}{2(\omega^2 L^2 + R^2)} - \pm \frac{1}{2} V_s^2 \omega C = 0$$

$$C = \frac{L}{\omega^2 L^2 + R^2}$$

$$\omega = 377 \text{ Rad/sec (60 Hz)}$$

$$R = 1 \Omega$$

$$L = 2.7 \text{ mH}$$

$$\Rightarrow C = 1.32 \text{ mF}$$

If we know our load, we can add reactive elements to compensate so that no displacement factor reduction of line utilization occurs.

Real, Reactive Power Defs. are useful to help us do this.

This does not help with distortion factor.