
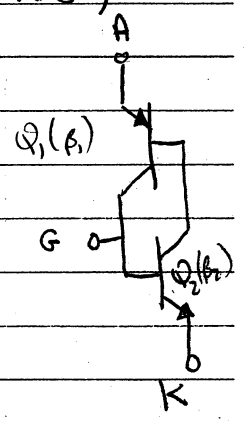


Power Electronics Notes - D. Perreault

★★ Phase - Controlled Converters  
(Read: KSV Ch 5)

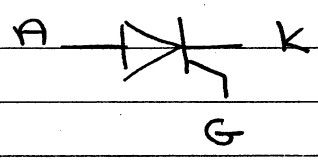Thyristor Devices : SCR (Silicon Controlled Rectifier)




SCR : Acts like a diode where you can select when conduction will start, but not when it stops.

"Transistor"  
View of 4-layer SCR

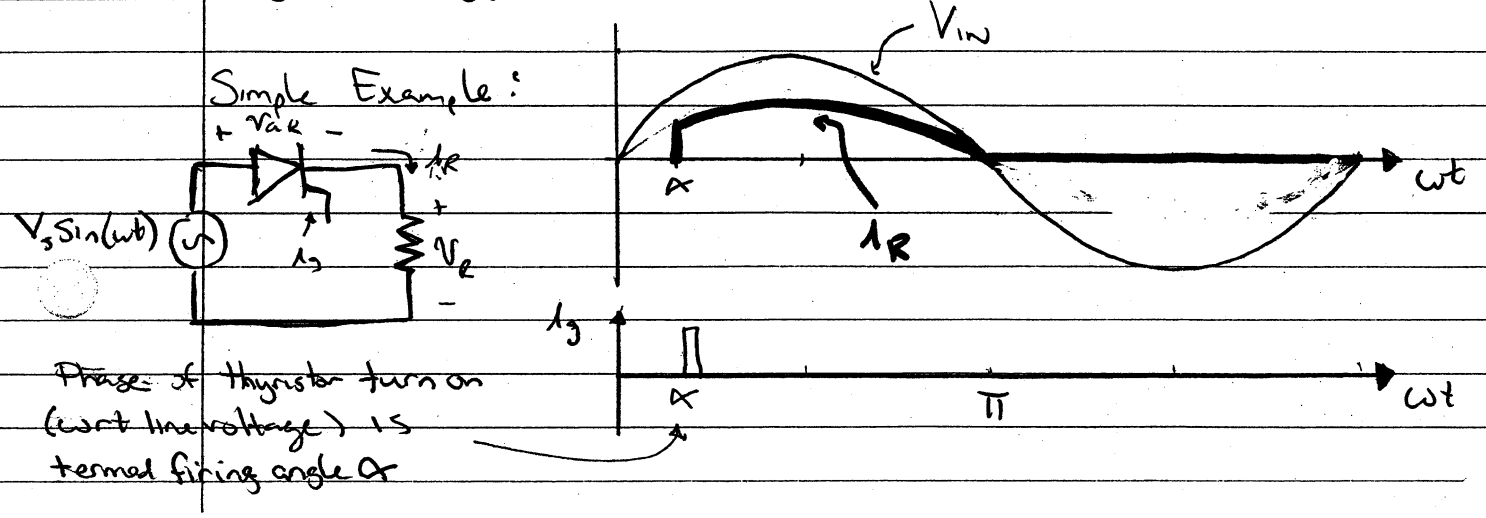- 1. Stays off until a gate pulse is applied while  $V_{AK} > 0$
- 2. Once on, behaves like a diode & does not turn off until  $i \rightarrow 0$
- 3. To stay off (after  $V_{AK} > 0$  again) must have  $i$  stay at 0 for a short time  $t_g$  (10-100  $\mu s$ )


So the device is semi-controlled : we control the turn on point, but only turns off when circuit conditions force it to.



# Power Electronics Notes - D. Perreault

Consider a full-bridge converter (inductive/capacitive load)


Diode Version

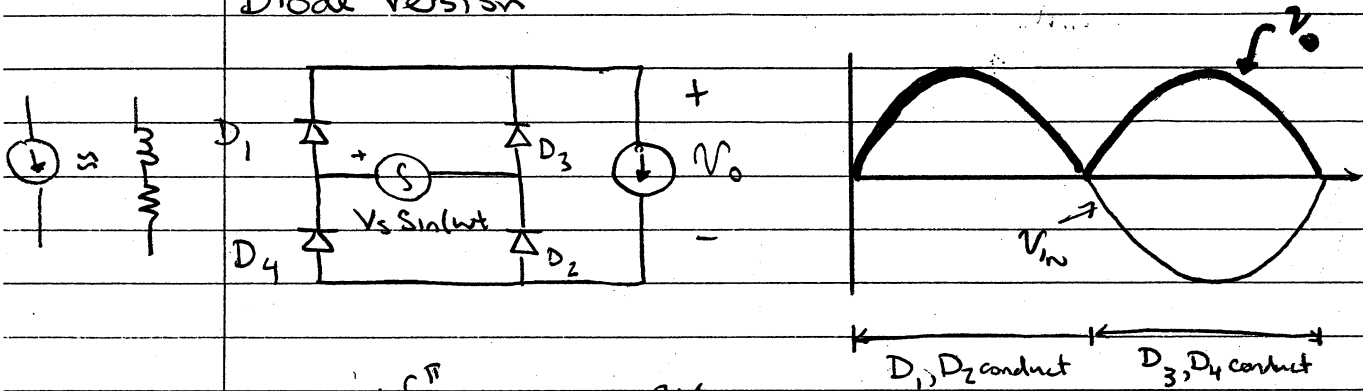

$$\langle V_o \rangle = \frac{1}{\pi} \int_0^{\pi} V_s \sin \phi d\phi = \frac{2V_s}{\pi}$$

Consider Thyristor (Phase-controlled) Version

→ firing angle  $\alpha$


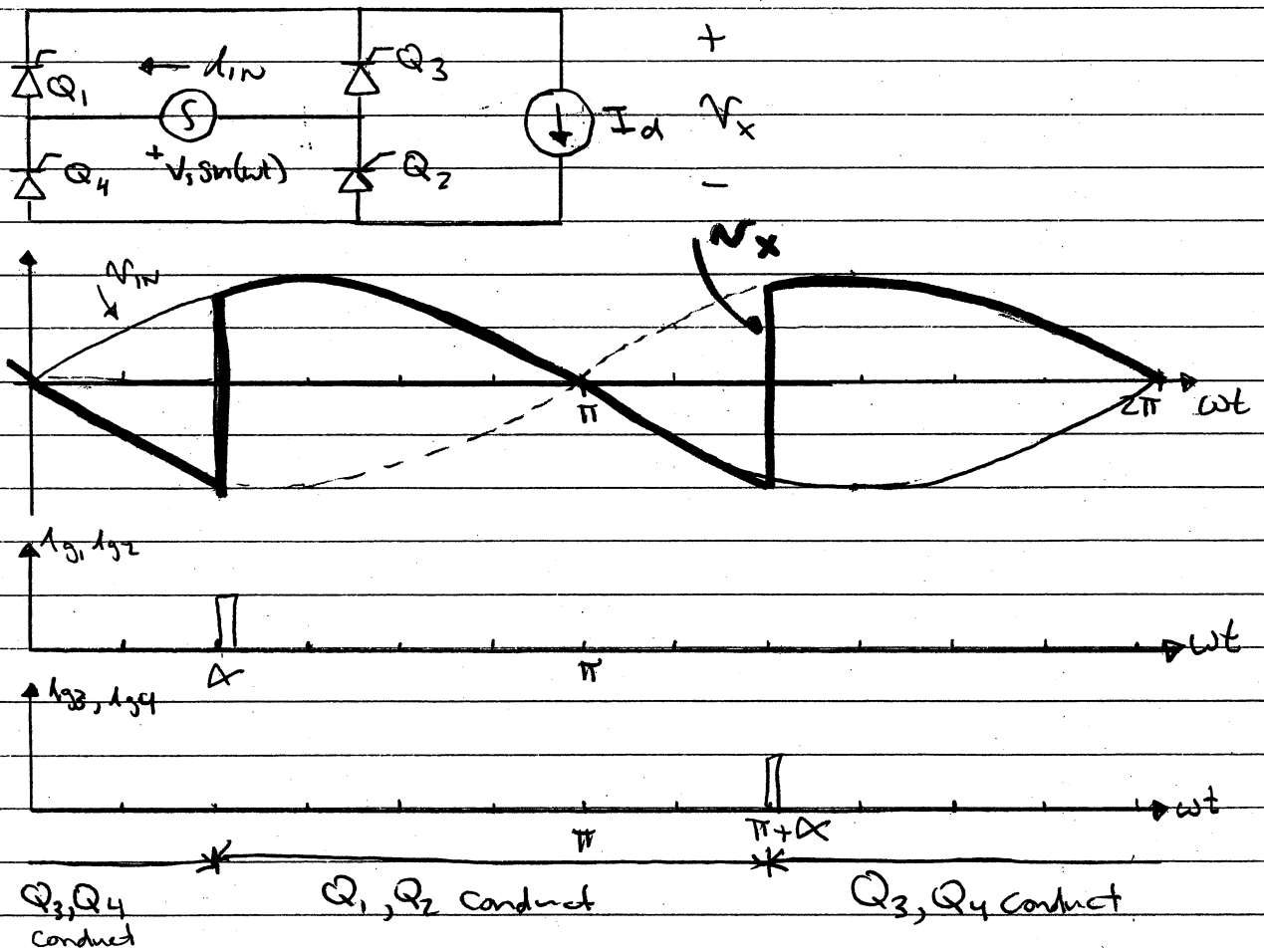


# Power Electronics Notes - D. Perreault

Lets analyze the output voltage  $\langle V_x \rangle$

$$\langle V_x \rangle = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_s \sin(\varphi) d\varphi = \frac{2V_s}{\pi} \cos \alpha$$

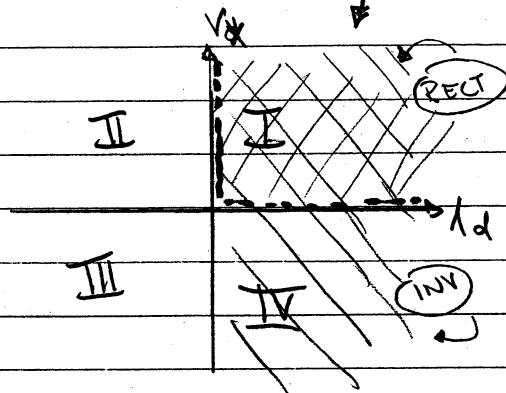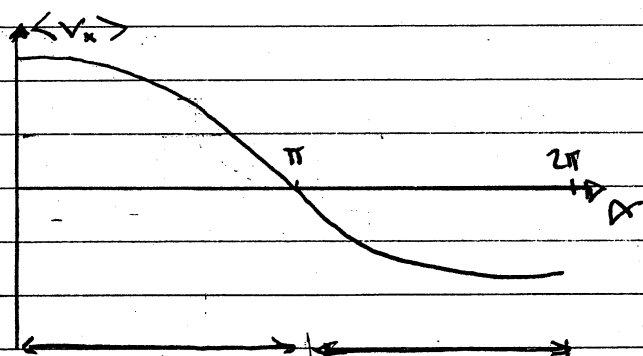$I_d > 0$   
by necessity  
conduction of  
thyristors



Rectification      Inversion


$\langle V_x \rangle > 0$        $\langle V_x \rangle < 0$

Power flows AC  $\rightarrow$  DC      Power flows DC  $\rightarrow$  AC

QUADRANTS OF OPERATION  
IN  $(V, I)$

So with a phase controlled converter, we can regulate the output voltage by varying firing angle  $\alpha$ . We can even cause power flow from dc-side to ac-side as long as  $I_d > 0$  (e.g. pull power out of inductor + put into line.)

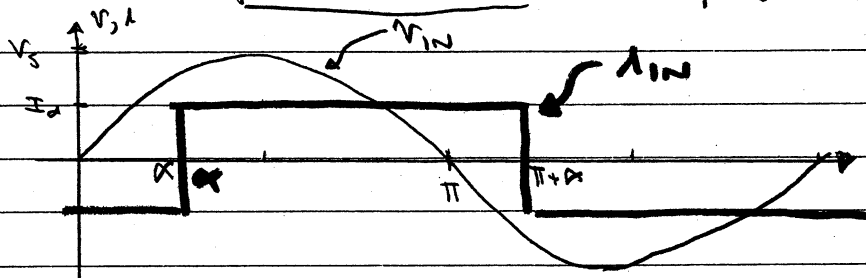Consider the power factor of a phase-controlled converter



$$K_p = K_d K_\theta = \left( \frac{I_{1,rms}}{I_{rms}} \right) \cos(\phi_1) = \frac{4}{\pi\sqrt{2}} \cos \alpha \approx 0.9 \cos \alpha$$

$K_d$                        $K_\theta$

$I_{1,rms}$  for square wave is  $\frac{4}{\pi\sqrt{2}} I_d$

$I_{rms}$  is  $I_d$


phase shift of fundamental of square wave "in phase" w/ square wave

$$\therefore \phi_1 = \alpha$$

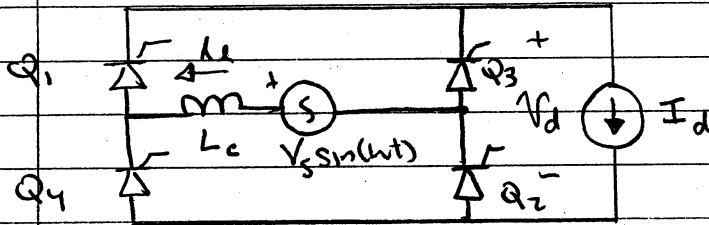
# Power Electronics Notes - D. Perreault

So the power factor of a phase-controlled Converter varies with firing angle  $\alpha$ .

Consider the effects of AC-side reactance



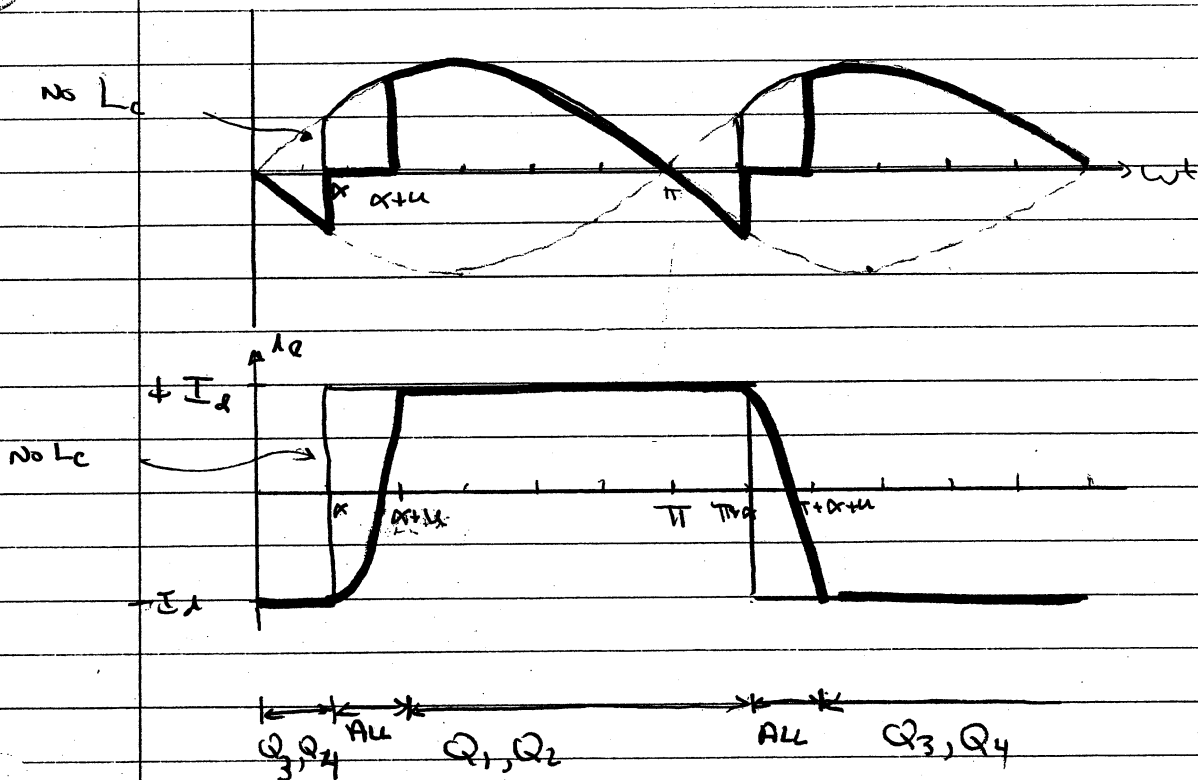Similar to the diode rectifier case, a Commutation period exists during which all devices are on while current in  $L_c$  switches between  $+I_d$  and  $-I_d$  (between  $Q_1/Q_2$  and  $Q_3/Q_4$ )



## POWER ELECTRONICS NOTES - D. PERREAU

A similar analysis to the diode case shows that for the full-bridge thyristor converter

$$\langle V_x \rangle = \frac{2V_s}{\pi} \left[ \cos \alpha - \frac{X_c I_d}{V_s} \right]$$

Note that the need to commutate devices places a limit on how negative the output voltage can be made as a function of  $\frac{X_c I_d}{V_s}$  and  $\alpha$ . This is analyzed in KSV Ch 5.

(Require  $\alpha + \mu < \pi$ )

Summary

