

APPENDIX C

FLYBACK - DISCONTINUOUS INDUCTOR CURRENT - DIRECT DUTY CYCLE CONTROL

Example 1: 12 Volt, 60 Watt Output

$$f_s = 80 \text{ kHz}, \quad T = 12.5 \text{ } \mu\text{sec}$$

$$V_{in} = 12 \text{ to } 24 \text{ V}$$

$$V_o = 12 \text{ V}, \quad I_o = 0.5 \text{ to } 5 \text{ A}$$

$$R_o = 24 \text{ to } 2.4 \text{ Ohms}$$

$$I_{sc} = 6 \text{ A Short Circuit Limit}$$

Discontinuous Current Mode Boundary
Duty Cycle Limit at I_{sc} , min V_{in} :

$$D_{max} = 1/(1+V_{in}/V_o) = 0.5$$

$$\text{Max. } t_d = (1-D)T = 6.25 \text{ } \mu\text{sec}$$


$$\text{Max. } I_p = 2I_{sc}/(1-D) = 2 \times 6/0.5 = 24 \text{ A}$$

$$L = (V_o + V_f)t_d/I_p = 13 \times 6.25/24 = 3.4 \text{ } \mu\text{H}$$

ESR Max for 0.1 V_{pp} Ripple at $I_o = 5\text{A}$:

$$R_c = 0.1/20\text{A} = 5 \text{ m}\Omega \text{ max (1 m}\Omega \text{ min).}$$

$$C = 20,000 \text{ } \mu\text{F}$$

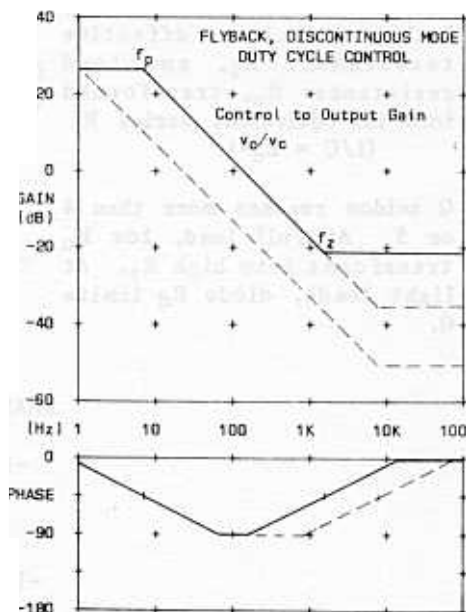

Basic Equations — Duty Cycle Control:

$$D = V_c/V_s:$$

DC Relationships:

$$(1) \quad V_o = V_{in} D \left(\frac{R_o}{2Lf} \right)^{\frac{1}{2}} = V_{in} \frac{V_c}{V_s} \left(\frac{R_o}{2Lf} \right)^{\frac{1}{2}} \quad (1a) \quad V_c = \frac{V_o V_s}{V_{in}} \left(\frac{2Lf}{R_o} \right)^{\frac{1}{2}}$$

Control to Output Gain:

$$(2) \quad \frac{v_o}{v_c} = \frac{V_{in}}{V_s} \left(\frac{R_o}{2Lf} \right)^{\frac{1}{2}} H_e(s). \quad H_e(s) = \frac{1+s/\omega_z}{1+s/\omega_p}, \quad \omega_p = \frac{2}{R_o C}, \quad \omega_z = \frac{1}{R_c C}$$

Line to Output Gain:

$$(3) \quad \frac{v_o}{v_{in}} = \frac{V_c}{V_s} \left(\frac{R_o}{2Lf} \right)^{\frac{1}{2}} H_e(s) = \frac{V_o}{V_{in}} H_e(s)$$

Corner Frequencies from Equation (2):

$$f_p = 2/(2\pi R_o C) = 15.92/R_o = 6.63 \text{ Hz at } 2.4 \text{ } \Omega, \quad .663 \text{ at } 24 \text{ } \Omega$$

$$f_z = 1/(2\pi R_c C) = 7.95/R_c = 1590 \text{ Hz at } 5 \text{ m}\Omega, \quad 7950 \text{ Hz at } 1 \text{ m}\Omega$$

Low Frequency Gain from Equation (2) ($V_s = 2.5 \text{ V}$ for UC1524A)

$$v_o/v_c = .542 V_{in} \sqrt{R_o} = 20.2 \text{ (26.7 dB) at } 24 \text{ V, } 2.4 \text{ } \Omega$$

$$= 31.9 \text{ (30.1 dB) at } 12 \text{ V, } 24 \text{ } \Omega$$

V_c must be clamped to 1.25 V to limit Duty Cycle to 0.5 max.

FLYBACK - DISCONTINUOUS INDUCTOR CURRENT - DIRECT DUTY CYCLE CONTROL

Error Amplifier Compensation:

Control I.C.: UC1524A

Crossover frequency (0 dB loop gain):

$$f_c = f_s/4 = 20 \text{ kHz}$$

E/A gain needed at 20 kHz = 21.5 dB

ESR zero, f_z , cancelled by pole f_p at $\max f_z/10$. This increases low frequency gain and adds 45° more phase lag, still leaving a phase margin of 45° :

$$f_p = \max f_z/10 = 795 \text{ Hz}$$

E/A gain required below f_p is:

$$21.5 + 20 \log(20,000/795) = 49.5 \text{ dB}$$

Total control voltage swing, ΔV_c , needed to maintain constant output voltage V_o with worst case line and load variation is (from Eq. 1a):

$$(1a) \quad V_c = \frac{V_o V_s}{V_{in}} \left(\frac{2Lf}{R_o} \right)^{\frac{1}{2}} = \frac{12 \times 2.5 - 3.4 \times 0.8}{V_{in} \sqrt{R_o}} = 0.188 \text{ to } 1.19 \text{ V.} \quad \Delta V_c = 1.0 \text{ V}$$

Output voltage error with actual E/A DC gain of 298 (49.5 dB):

$$\Delta V_o = \Delta V_c / 298 = 3.4 \text{ mV} \quad (120 \text{ mV} = 1\% \text{ regulation})$$

Implementation: Circuit of Appendix A-1 (omit R_p and C_p)

UC1524A has transconductance error amplifier ($g_m = .002$)


With $R_f = 3M\Omega$, max. gain = $g_m R_f = 6000$ (75.6 dB, > 64 dB required, OK)

Gain required below $f_p = 298$ (49.5 dB) = R_f/R_i .

$$R_i = 3M/298 = 10K$$

Pole at 795 Hz:

 
$$C_f = 1/(2\pi f_p R_f) = 67 \text{ pF}$$



FLYBACK - DISCONTINUOUS INDUCTOR CURRENT - VOLTAGE FEEDFORWARD CONTROL

 Example 2: 12 Volt, 60 Watt Output

All power circuit parameters
are the same as Example 1.



Basic Equations — Voltage Feedforward:

$$D = V_c/V_s, \quad V_s = V_{in}/K, \quad K = V_{in}D/\max V_c$$

DC Relationships:

$$(1) \quad V_o = V_{in}D \left(\frac{R_o}{2Lf} \right)^{\frac{1}{2}} = KV_c \left(\frac{R_o}{2Lf} \right)^{\frac{1}{2}} \quad (1a) \quad V_c = \frac{V_o(2Lf)}{K(R_o)}^{\frac{1}{2}}$$

Control to Output Gain:

$$(2) \quad \frac{v_o}{v_c} = K \left(\frac{R_o}{2Lf} \right)^{\frac{1}{2}} H_e(s), \quad H_e(s) = \frac{1+s/\omega_z}{1+s/\omega_p}, \quad \omega_p = \frac{2}{R_o C}, \quad \omega_z = \frac{1}{R_c C}$$

Line to Output Gain:

$$(3) \quad \frac{v_o}{v_{in}} = 0 \quad \text{Inherent good line regulation and audio susceptibility}$$

Corner Frequencies from Equation (2):

$$f_p = 2/(2\pi R_o C) = 15.92/R_o = 6.63 \text{ Hz at } 2.4 \Omega, \quad .663 \text{ at } 24 \Omega$$

$$f_z = 1/(2\pi R_c C) = 7.95/R_c = 1590 \text{ Hz at } 5 \text{ m}\Omega, \quad 7950 \text{ Hz at } 1 \text{ m}\Omega$$

Low Frequency Gain from Equation (2) (max $V_c = 3.5 \text{ V}$ for UC1840)

$$K = V_{in}D/\max V_c = 12 \times 0.5/3.5 = 1.71 \quad (\text{feedforward factor})$$

$$v_o/v_c = 2.52\sqrt{R_o} = 3.91 \text{ (11.8 dB) at } 2.4 \Omega$$

$$= 12.35 \text{ (21.8 dB) at } 24 \Omega \quad V_{in} = 12 \text{ to } 24 \text{ V}$$

FLYBACK - DISCONTINUOUS INDUCTOR CURRENT - VOLTAGE FEEDFORWARD CONTROL

Error Amplifier Compensation:

Control I.C.: UC1840

Crossover frequency (0 dB loop gain)

$$f_c = f_s/4 = 20 \text{ kHz}$$

E/A gain needed at 20 kHz = 35.8 dB

ESR zero, f_z , is cancelled by pole f_p at $\max f_z/10$. This increases low frequency gain and adds 45° more phase lag, still leaving 45° phase margin.

$$f_p = \max f_z/10 = 795 \text{ Hz}$$

E/A gain required below f_p is:

$$35.8 + 20 \log(20,000/795) = 63.8 \text{ dB}$$

Total control voltage swing, ΔV_c , needed to maintain constant output voltage V_o with worst case line and load variation is (from Eq. 1a):

$$(1a) \quad V_c = \frac{V_o}{K} \left(\frac{2Lf}{R_o} \right)^{\frac{1}{2}} = \frac{12 \sqrt{2 \times 3.4 \times 0.08}}{1.71 \sqrt{R_o}} = 1.05 \text{ to } 3.33 \text{ V} \quad \Delta V_c = 2.28 \text{ V}$$

Output voltage error with actual E/A DC gain of 1550 (63.8 dB):

$$\Delta V_o = \Delta V_c / 1550 = 1.5 \text{ mV} \quad (120 \text{ mV} = 1\% \text{ regulation})$$

Implementation: Circuit of Appendix A-1 (omit R_p and C_p)

Voltage feedforward factor, K , in UC1840 is set by an independent ramp generator whose slope varies directly with V_{in} . A minimum ramp charging current of $36 \mu\text{A}$ is chosen (near the bottom end of the optimum range).

$$R_r = \min V_{in} / \min I_r = 12 / 36 \mu\text{A} = 330\text{K}$$

$$dv/dt = I_r / C_r = V_{in} / R_r C_r = \max v_c / t_{on} \quad R_r C_r = V_{in} t_{on} / \max V_c = K / f$$


$$C_r = K / f R_r = 1.71 / (80\text{K} \times 330\text{K}) = 65 \text{ pF}$$

UC1840 has voltage mode amplifier with 65 dB gain, > 63.8 dB required, OK.

$R_f = 3 \text{ M}$, chosen somewhat arbitrarily because of high gain required.

Gain required below $f_p = 1550$ (64 dB) = R_f / R_i . $R_i = 3\text{M} / 1550 = 2\text{K}$.

 
Pole at $f_p = 795 \text{ Hz}$: $C_f = 1 / (2\pi f_p R_f) = 67 \text{ pF}$



FLYBACK - DISCONTINUOUS INDUCTOR CURRENT - CURRENT MODE CONTROL

 Example 3: 12 Volt, 60 Watt Output

All power circuit parameters are the same as Example 1.



Basic Equations — Current Mode Control:

$$I_p = KV_C, \quad K = \max I_p / \max V_C$$

DC Relationships:

$$(1) \quad V_O = V_{in} D \left(\frac{R_O}{2Lf} \right)^{\frac{1}{2}} = KV_C \sqrt{R_O L f / 2} \quad (1a) \quad V_C = \frac{V_O \sqrt{2}}{K \sqrt{L f R_O}}$$

Control to Output Gain:

$$(2) \quad \frac{V_O}{V_C} = K \sqrt{R_O L f / 2} H_e(s), \quad H_e(s) = \frac{1+s/\omega_z}{1+s/\omega_p}, \quad \omega_p = \frac{2}{R_O C}, \quad \omega_z = \frac{1}{\tau}$$

Line to Output Gain:

$$(3) \quad \frac{V_O}{V_{in}} = 0 \quad \text{Inherent good line regulation and audio susceptibility.}$$

Corner Frequencies from Equation (2):

$$f_p = 2 / (2\pi R_O C) = 15.92 / R_O = 6.63 \text{ Hz at } 2.4 \Omega, \quad .663 \text{ at } 24 \Omega$$

$$f_z = 1 / (2\pi R_C C) = 7.95 / R_C = 1590 \text{ Hz at } 5 \text{ m}\Omega, \quad 7950 \text{ Hz at } 1 \text{ m}\Omega$$

Low Frequency Gain from Equation (2) (V_C clamped to 2.4 V for 24 A I_{SC})

$$K = \max I_p / \max V_C = 24 / 2.4 = 10$$

$$v_o / v_c = 3.7 \sqrt{R_O} = 5.73 \text{ (15.2 dB) at } 2.4 \Omega$$

$$= 18.1 \text{ (25.2 dB) at } 24 \Omega$$

$$V_{in} = 12 \text{ to } 24 \text{ V}$$

FLYBACK - DISCONTINUOUS INDUCTOR CURRENT - CURRENT MODE CONTROL

Error Amplifier Compensation:

Control I.C.: UC1846

Crossover frequency (0 dB loop gain)

$$f_c = f_s/4 = 20 \text{ kHz}$$

E/A gain needed at 20 kHz = 32 dB

ESR zero, f_z , is cancelled by pole f_p at $\max f_z/10$. This decade offset increases low frequency gain and adds 45° more phase lag, still leaving 45° phase margin.

$$f_p = \max f_z/10 = 795 \text{ Hz}$$

E/A gain required at and below f_p is:

$$32 + 20 \log(20,000/795) = 60 \text{ dB}$$

Total control voltage swing, ΔV_c , needed to maintain constant output voltage V_o with worst case line and load variation is (from Eq. 1a):

$$(1a) \quad V_c = \frac{V_o - \sqrt{2}}{K - LfR_o} = \frac{12 - \sqrt{2}}{10 - 3.4 \times 0.08 R_o} = 3.25 / -R_o = 0.664 \text{ to } 2.1 \text{ V.} \quad \Delta V_c = 1.44 \text{ V}$$

Output voltage error with actual E/A DC gain of 1000 (60 dB):

$$\Delta V_o = \Delta V_c / 1000 = 1.44 \text{ mV} \quad (120 \text{ mV} = 1\% \text{ regulation})$$

Implementation: Circuit of Appendix A-1 (omit R_p and C_p)

Current control factor ($K = 10$) is set with the UC1846 by the fixed gain (3X) of the current amplifier and the current sampling resistor, R_s :


$$K = I_p / V_c = 10 = 1 / (3R_s). \quad R_s = 1 / (30) = .033 \Omega$$

UC1846 error amplifier gain limit > 80 dB with $R_f > 30K$, > 60 dB required, OK.

$R_f = 3 \text{ M}$, chosen somewhat arbitrarily because of high gain required.

Gain required below $f_p = 1000$ (60 dB) = R_f / R_i . $R_i = 3M / 1000 = 3K$.

 Pole at $f_p = 795 \text{ Hz}$: $C_f = 1 / (2\pi f_p R_f) = 67 \text{ pF}$



BUCK - CONTINUOUS INDUCTOR CURRENT - DIRECT DUTY CYCLE CONTROL

Example 4: 12 Volt, 240 Watt Output

$$f_s = 40 \text{ kHz}, \quad T = 25 \text{ } \mu\text{sec}$$

$$V_{in} = 30 \text{ to } 60 \text{ V}$$

$$V_o = 12 \text{ V}, \quad I_o = 2 \text{ to } 20 \text{ A}$$

$$R_o = 6 \text{ to } 0.6 \text{ Ohms}$$

$$I_{sc} = 24 \text{ A Short Circuit Limit}$$

Continuous Current Mode Boundary:

$$\text{Min. } I_o = 2 \text{ A}$$

$$\text{Max. } \Delta I_L = 2(\text{min} I_o) = 4 \text{ A}$$

$$D = V_o/V_{in} = 0.2 \text{ to } 0.4$$


$$t_{off} = 0.8 \times 25 = 20 \text{ } \mu\text{s max}$$

$$L = V_o t_{off} / \Delta I_L = 12 \times 20 / 4 = 60 \text{ } \mu\text{H}$$

ESR Max for 0.1 V_{pp} Ripple at $\Delta I_L = 4 \text{ A}$:

$$R_c = 25 \text{ m}\Omega \text{ max (5 m}\Omega \text{ min)}$$

$$C = 4000 \text{ } \mu\text{F}$$

 

Basic Equations — Duty Cycle Control:

$$D = V_c/V_s:$$

DC Relationships:

$$(1) \quad V_o = V_{in} D = V_{in} \frac{V_c}{V_s} \quad (1a) \quad V_c = \frac{V_o V_s}{V_{in}}$$

Control to Output Gain:

$$(2) \quad \frac{v_o}{v_c} = \frac{V_{in}}{V_s} H_e(s). \quad H_e(s) = \frac{1 + s/\omega_z}{1 + (s/\omega_o)/Q + (s/\omega_o)^2}, \quad \omega_o = \frac{1}{\sqrt{LC}}, \quad \omega_z = \frac{1}{R_c C}$$

Line to Output Gain:

$$(3) \quad \frac{v_o}{v_{in}} = \frac{V_c}{V_s} H_e(s) = \frac{V_o}{V_{in}} H_e(s) \quad Q = \frac{R_o}{\omega_o L}$$

Corner Frequencies from Equation (2):

$$f_o = 1/(2\pi\sqrt{LC}) = 325 \text{ Hz}$$

$$f_z = 1/(2\pi R_c C) = 39.8/R_c = 1590 \text{ Hz at } 25 \text{ m}\Omega, \quad 7950 \text{ Hz at } 5 \text{ m}\Omega$$

UC1524A ramp is 2.5 V at 80 kHz. One output is not used which limits duty cycle to 50% max. at 40kHz. V_s projects to 5 V over the full 40 kHz cycle.

Low Frequency Gain from Equation (2):

$$\begin{aligned} v_o/v_c = V_{in}/5 &= 12 \text{ (21.6 dB) at } 60 \text{ V} \\ &= 6 \text{ (15.6 dB) at } 30 \text{ V} \end{aligned}$$

BUCK - CONTINUOUS INDUCTOR CURRENT - DIRECT DUTY CYCLE CONTROL

Error Amplifier Compensation:

Control I.C.: UC1524A

Crossover frequency (0 dB loop gain):

$$f_c = f_s/4 = 10 \text{ kHz}$$

E/A gain needed at 10 kHz = 21.5 dB

A pole at low frequency (<1 Hz) provides enough gain at low frequencies to meet regulation requirements.

Two second order filter poles at f_o are compensated by two zeros at $f_z = f_o/2$. This provides additional phase shift at f_o for sudden second order transition.

$$f_z = 325/2 = 162 \text{ Hz}$$

ESR zero, f_z , is canceled by pole f_p at least 5 times above f_o to avoid adding more phase lag at f_o . This happens to coincide with min. ESR zero, f_z .

$$f_p = 1590 \text{ Hz with } 21.5 \text{ dB gain}$$

E/A gain required at f_z is: $21.5 - 20\log(1590/162) = 1.7 \text{ dB}$

Total control voltage swing, ΔV_c , needed to maintain constant output voltage V_o with worst case line and load variation is (from Eq. 1a):

$$(1a) \quad V_c = \frac{V_o V_s}{V_{in}} = \frac{12 \times 5}{V_{in}} = 1 \text{ to } 2 \text{ V.} \quad \Delta V_c = 1 \text{ V}$$

Output voltage error with actual E/A DC gain of 180 (45 dB at 1 Hz):

$$\Delta V_o = \Delta V_c / 180 = 5.5 \text{ mV} \quad (120 \text{ mV} = 1\% \text{ regulation})$$

Implementation: Circuit of Appendix A-2 (omit R_p , C_p and R_{fp})

UC1524A has transconductance error amplifier ($g_m = .002$). Min. load resistance (min R_{fz}) is 30K. R_{iz} is approx. $1 \times R_{fz}$ (gain is 1.7 dB at f_z).

Set $R_{iz} = 50\text{K}$



Zero 2 at 162 Hz: $C_i = 1/(\omega_z R_{iz}) = 1/2\pi \times 162 \times 50\text{K} = .02 \mu\text{F}$

Pole 2 at 1590 Hz: $R_{ip} = R_{iz}/(R_{iz}\omega_p^2 C_i - 1) = 50\text{K}/(50\text{K} \times 2\pi \times 1590 \times .02) = 5.6\text{K}$

  1.7 dB (1.22) gain at 162 Hz: $R_{fz} = 1.22(R_{ip} + R_{iz}) = 68\text{K}$

Zero 1 at 162 Hz: $C_f = 1/(\omega_z R_{fz}) = 1/(2\pi \times 162 \times 68\text{K}) = .0144 \mu\text{F}$


Pole 1 at 0 Hz: Omitting R_{fp} (open), $\omega_{p1} = 0$. Actual pole occurs at 80 dB gain limit of UC1524A error amplifier at a frequency well below 1 Hz.



BUCK - CONTINUOUS INDUCTOR CURRENT - VOLTAGE FEEDFORWARD CONTROL

 Example 5: 12 Volt, 240 Watt Output

All power circuit parameters are the same as Example 4.



Basic Equations — Voltage Feedforward

$$D = V_c/V_s, \quad V_s = V_{in}/K, \quad K = V_{in}D/\max V_c$$

DC Relationships:

$$(1) \quad V_o = V_{in}D = KV_c \qquad (1a) \quad V_c = \frac{V_o}{K}$$

Control to Output Gain:

$$(2) \quad \frac{v_o}{v_c} = K H_e(s). \quad H_e(s) = \frac{1 + s/\omega_o}{1 + (s/\omega_o)/Q + (s/\omega_o)^2}, \quad \omega_o = \frac{1}{\sqrt{LC}}, \quad \omega_z = \frac{1}{R_c C}$$

Line to Output Gain:

$$(3) \quad \frac{v_o}{v_{in}} = 0 \quad \text{Inherent good line regulation} \qquad Q = \frac{R_o}{\omega_o L}$$

Corner Frequencies from Equation (2):

$$f_o = 1/(2\pi\sqrt{LC}) = 325 \text{ Hz}$$

$$f_z = 1/(2\pi R_c C) = 39.8/R_c = 1590 \text{ Hz at } 25 \text{ m}\Omega, \quad 7950 \text{ Hz at } 5 \text{ m}\Omega$$

Low Frequency Gain from Equation (2) ($\max V_c = 3.5 \text{ V}$ for UC1840):

$$K = V_{in}D/\max V_c = 30 \times 0.5/3.5 = 4.29 \quad (\text{feedforward factor})$$

$$v_o/v_c = V_{in}/5 = 4.29 \text{ (12.6 dB) at } 30 \text{ to } 60 \text{ V in.}$$

BUCK - CONTINUOUS INDUCTOR CURRENT - VOLTAGE FEEDFORWARD CONTROL

Error Amplifier Compensation:

Control I.C.: UC1840

Crossover frequency (0 dB loop gain):

$$f_c = f_s/4 = 10 \text{ kHz}$$

E/A gain needed at 10 kHz = 31 dB

A pole at low frequency (<1 Hz) provides enough gain at low frequencies to meet regulation requirements.

Two second order filter poles at f_o are compensated by two zeros at $f_z = f_o/2$. This provides additional phase shift at f_o for sudden second order transition.

$$f_z = 325/2 = 162 \text{ Hz}$$

ESR zero, f_z , is canceled by pole f_p at least 5 times above f_o to avoid adding more phase lag at f_o . This happens to coincide with min. ESR zero, f_z .

$$f_p = 1590 \text{ Hz with } 31 \text{ dB gain}$$

E/A gain required at f_z is: $31 - 20\log(1590/162) = 11.2 \text{ dB}$

Total control voltage swing, ΔV_c , needed to maintain constant output voltage V_o with worst case line and load variation is (from Eq. 1a):

$$(1a) \quad V_c = \frac{V_o}{V} = \frac{12}{4.29} = 2.8 \text{ V constant DC. } \Delta V_c = 0$$

DC Output voltage error is theoretically zero. Loop gain is required only for good dynamic response.

Implementation: Circuit of Appendix A-2 (omit R_p , C_p and R_{fp})

Voltage feedforward factor, K , in UC1840 is set by an independent ramp generator whose slope varies proportional to V_{in} . Minimum ramp charging current of 30 μA is chosen, near the bottom of the optimum range.

$$R_T = \min V_{in}/\min I_T = 30/30\mu\text{A} = 1\text{M}$$

$$dv/dt = I_T/C_T = V_{in}/R_T C_T = \max v_c/t_{on}. \quad R_T C_T = V_{in} t_{on}/\max v_c = K/f$$

$$C_T = K/fR_T = 4.29/(40\text{K} \times 1\text{M}) = 107 \text{ pF}$$

Set $R_{iz} = 50\text{K}$. With gain appx. 4 at 162 Hz (f_z), R_f of 200K is OK to drive.


$$\text{Zero 2 at } 162 \text{ Hz: } C_i = 1/(\omega_{z2} R_{iz}) = 1/2\pi \times 162 \times 50\text{K} = .02 \mu\text{F}$$

$$\text{Pole 2 at } 1590 \text{ Hz: } R_{ip} = R_{iz}/(R_{iz}\omega_{p2} C_i - 1) = 50\text{K}/(50\text{K} \times 2\pi \times 1590 \times .02) = 5.6\text{K}$$

$$11.2 \text{ dB (3.63) gain at } 162 \text{ Hz: } R_{fz} = 3.63(R_{ip} + R_{iz}) = 202\text{K}$$


$$\text{Zero 1 at } 162 \text{ Hz: } C_f = 1/(\omega_{z1} R_{fz}) = 1/(2\pi \times 162 \times 200\text{K}) = .0049 \mu\text{F}$$

 Pole 1 at 0 Hz: Omitting R_{fp} (open), $\omega_{p1} = 0$. Actual pole occurs at 80 dB gain limit of UC1840 error amplifier at a frequency below 1 Hz.



BUCK - CONTINUOUS INDUCTOR CURRENT - CURRENT MODE CONTROL

Example 6: 12 Volt, 240 Watt Output

 

All power circuit parameters are the same as Example 4.

Basic Equations — Current Mode Control:

$$I_L = KV_C, \quad K = \max I_L / \max V_C$$

DC Relationships:

$$(1) \quad V_O = I_L R_O = KV_C R_O \quad (1a) \quad V_C = \frac{V_O}{KR_O}$$

Control to Output Gain:

$$(2) \quad \frac{V_O}{V_C} = KR_O H_e(s), \quad H_e(s) = \frac{1 + s/\omega_z}{1 + s/\omega_p}, \quad \omega_p = \frac{1}{R_O C}, \quad \omega_z = \frac{1}{R_C C}$$

Line to Output Gain:

$$(3) \quad \frac{V_O}{V_{in}} = 0 \quad \text{Inherent good line regulation and audio susceptibility}$$

Corner Frequencies from Equation (2):

$$f_p = 1/(2\pi R_O C) = 66.3 \text{ Hz at } 0.6 \Omega, \quad 6.63 \text{ Hz at } 6 \Omega$$

$$f_z = 1/(2\pi R_C C) = 39.8/R_C = 1590 \text{ Hz at } 25 \text{ m}\Omega, \quad 7950 \text{ Hz at } 5 \text{ m}\Omega$$

Low Frequency Gain from Equation (2) (max V_C clamped to 2.5 V for 25 A I_{SC}):

$$K = \max I_L / \max V_C = 25 / 2.5 = 10$$

$$v_O/v_C = KR_O = 6 \text{ (15.6 dB) at } 0.6 \Omega, \quad 60 \text{ (35.6 dB) at } 6 \Omega$$

BUCK - CONTINUOUS INDUCTOR CURRENT - CURRENT MODE CONTROL

Error Amplifier Compensation:

Control I.C.: UC1846

Crossover frequency (0 dB loop gain):

$$f_c = f_s/4 = 10 \text{ kHz}$$

E/A gain needed at 10 kHz = 12 dB

ESR zero, f_{zC} , is canceled by pole f_p at max $f_z/10$. This decade offset increases low frequency gain and adds 45° more phase lag, still leaving 45° phase margin.

$$f_p = \max f_z/10 = 795 \text{ Hz}$$

E/A gain required at and below f_p is:

$$12 + 20\log(10000/795) = 34 \text{ dB (50)}$$

Total control voltage swing, ΔV_c , needed to maintain constant output voltage V_o with worst case line and load variation is (from Eq. 1a):

$$(1a) \quad V_c = \frac{V_o}{KR_o} = \frac{12}{10R_o} = 0.2 \text{ to } 2 \text{ V.} \quad \Delta V_c = 1.8 \text{ V}$$

Output voltage error with actual E/A gain of 50 (34 dB)

$$\Delta V_o = \Delta V_c/50 = 36 \text{ mV (0.3% regulation)}$$

Implementation: Circuit of Appendix A-1 (omit R_p and C_p)

Current control factor, $K = 10$, in the UC1846 is set by the fixed gain (3X) of the current sense amplifier together with current sampling resistor R_s .

$$K = I_L/V_c = 10 = 1/(3R_s). \quad R_s = 1/30 = .033 \Omega$$


UC1846 error amplifier gain limit is >80 dB with $R_f >30K$. 34 dB needed, OK

Gain required at and below $f_p = 795$ Hz is 50 (34 dB) = R_f/R_i .

$$\text{Let } R_f = 500K, \quad R_i = R_f/50 = 10K$$

1 Pole at $f_p = 795$ Hz. $C_f = 1/(2\pi f_p R_f) = 400$ pF

Slope compensation: Current downslope is $4A/20\mu s$, or $5A$ projected over 25 μs period, equating to $5 \times .033 = .165$ volts p-p at input of current sense amplifier. Compensation ramp should be $.165/2 = .082$ V positive ramp. UC1846 oscillator ramp is 2 V. A 24:1 divider provides .083 V. Put 1K between current sense R_s and current sense amplifier input, and 24K from timing capacitor C_t to current sense ampl. input.

 

FLYBACK - CONTINUOUS INDUCTOR CURRENT - DIRECT DUTY CYCLE CONTROL

Example 7: 12 Volt, 60 Watt Output

$$f_s = 80 \text{ kHz}, \quad T = 12.5 \text{ } \mu\text{sec}$$

$$V_{in} = 12 \text{ to } 24 \text{ V}$$

$$V_o = 12 \text{ V}, \quad I_o = 0.5 \text{ to } 5 \text{ A}$$

$$R_o = 24 \text{ to } 2.4 \text{ Ohms}$$

$$I_{sc} = 6 \text{ A Short Circuit Limit}$$

Continuous Current Mode Boundary:

$$\text{Min. } I_o = 0.5 \text{ A}$$

$$D = V_o / (V_o + V_i) = 0.33 \text{ to } 0.5$$

$$\text{Max. } \Delta I_L = 2(\text{min} I_o) / (1 - D_{\text{min}}) = 1.5 \text{ A}$$

$$t_{\text{off}} = 12.5(1 - D) = 8.33 \text{ } \mu\text{s max}$$

$$L = V_o t_{\text{off}} / \Delta I_L = 12 \times 8.33 / 1.5 = 72 \text{ } \mu\text{H}$$

$$I_{L\text{max}} = \text{max} I_o / (1 - D_{\text{max}}) = 10 \text{ A}$$

ESR Max for 0.1 V_{pp} Ripple at I_L = 10 A:

$$R_c = 10 \text{ m}\Omega \text{ max (2 m}\Omega \text{ min)}, \quad C = 10,000 \text{ } \mu\text{F}$$

Basic Equations -- Duty Cycle Control:

$$D = V_c / V_s:$$

$$\omega_o = \frac{1-D}{\sqrt{LC}}, \quad \omega_z = \frac{1}{R_c C}, \quad Q = \frac{R_o}{\omega_o L}$$

DC Relationships:

$$(1) \quad V_o = V_{in} D / (1 - D) = V_{in} / (V_s / V_c - 1)$$

$$(1a) \quad V_c = V_s \frac{V_o}{V_i + V_o}$$

Control to Output Gain:

$$(2) \quad \frac{V_o}{V_c} = \frac{V_{in}}{V_s} (1 + V_o / V_i)^2 f_1(s) H_e(s), \quad H_e(s) = \frac{1 + s/\omega_z}{1 + (s/\omega_o)/Q + (s/\omega_o)^2}$$

Line to Output Gain:

$$(3) \quad \frac{V_o}{v_{in}} = \frac{V_c}{V_s} H_e(s) = \frac{V_o}{V_{in}} H_e(s) \quad \text{RHP zero: } f_1(s) = 1 - \frac{sL}{R} \frac{V_o(V_o + V_i)}{V_i^2}$$

Corner Frequencies:

$$f_o = (1-D) / (2\pi\sqrt{LC}) = 94 \text{ Hz at } 12 \text{ V}, \quad 125 \text{ Hz at } 24 \text{ V}$$


$$f_z \text{ (ESR)} = 1 / (2\pi R_c C) = 1590 \text{ Hz at } 10 \text{ m}\Omega, \quad 7950 \text{ Hz at } 2 \text{ m}\Omega$$

$$f_z \text{ (RHP)} = 2728 \text{ Hz at } 12 \text{ V and } 2.4 \text{ } \Omega, \quad = 7275 \text{ Hz at } 24 \text{ V and } 2.4 \text{ } \Omega$$

UC1524A ramp V_s = 2.5 V. The two outputs of the UC1524A are paralleled.

Low Frequency Gain from Equation (2):
 
$$v_o / v_c = 19.2 \text{ (25.6 dB) at } 12 \text{ V}, \quad = 21.6 \text{ (26.7 dB) at } 24 \text{ V}$$



FLYBACK - CONTINUOUS INDUCTOR CURRENT - DIRECT DUTY CYCLE CONTROL

Error Amplifier Compensation:

Control I.C.: UC1524A

Crossover frequency (0 dB loop gain):

$f_c = 800$ Hz (best achievable - RHP zero)

E/A gain needed at 800 Hz = 11.6 dB

A pole at low frequency (<1 Hz) provides enough gain at low frequencies to meet regulation requirements.

Two second order filter poles at f_o are compensated by two zeros at $f_z = f_o$.

$$f_z = 94 \text{ Hz}$$

E/A gain required at f_z : -7 dB

Two additional poles cancel the ESR zero and right-half-plane zero. The location of these two poles is adjusted by trail and error. Although above the crossover frequency these poles are necessary or the gain would stay flat or even rise, causing instability at higher frequency.

$$f_p = 2700 \text{ Hz at } 22.2 \text{ dB gain, } \quad f_p = 8000 \text{ Hz also at } 22.2 \text{ dB}$$

Total control voltage swing, ΔV_c , needed to maintain constant output voltage V_o with worst case line and load variation is (from Eq. 1a):

$$(1a) \quad V_c = V_s \frac{V_o}{V_{in} + V_o} = 0.833 \text{ to } 1.25 \text{ V. } \quad \Delta V_c = .417 \text{ V}$$

Output voltage error with actual E/A DC gain of 40 (32 dB at 1 Hz):

$$\Delta V_o = \Delta V_c / 40 = 10 \text{ mV (0.1% regulation)}$$

Implementation: Circuit of Appendix A-2 (omit R_{fp})

UC1524A has transconductance error amplifier ($g_m = .002$). Min. load resistance (min R_{fz}) is 30K. R_{iz} is appx. $2xR_{fz}$ (gain is -7 dB at f_z).

Set $R_{iz} = 100K$

$$\text{Zero 2 at } 94 \text{ Hz: } C_i = 1/(\omega_z 2R_{iz}) = 1/2\pi \cdot 94 \times 100K = .017 \mu F$$


$$\text{Pole 2 at } 2700 \text{ Hz: } R_{ip} = R_{iz}/(R_{iz}\omega_p^2 C_i - 1) = 100K/(100K \times 2\pi \cdot 2700 \times .017 - 1) = 3.6K$$

$$\text{-7 dB (.45) gain at } 94 \text{ Hz: } R_{fz} = .45(R_{ip} + R_{iz}) = 47K$$

$$\text{Zero 1 at } 94 \text{ Hz: } C_f = 1/(\omega_z 1R_{fz}) = 1/(2\pi \cdot 94 \times 47K) = .036 \mu F$$

Pole 1 at 0 Hz: Omitting R_{fp} (open), $\omega_{p1} = 0$. Actual pole occurs at 80 dB gain limit of UC1524A error amplifier at a frequency well below 1 Hz.

 
$$\text{Pole 3 at } 8000 \text{ Hz. } R_p = R_{ip}/10 = 360 \Omega. \quad C_p = 1/(2\pi f_p 3R_p) = .055 \mu F$$



FLYBACK - CONTINUOUS INDUCTOR CURRENT - CURRENT MODE CONTROL

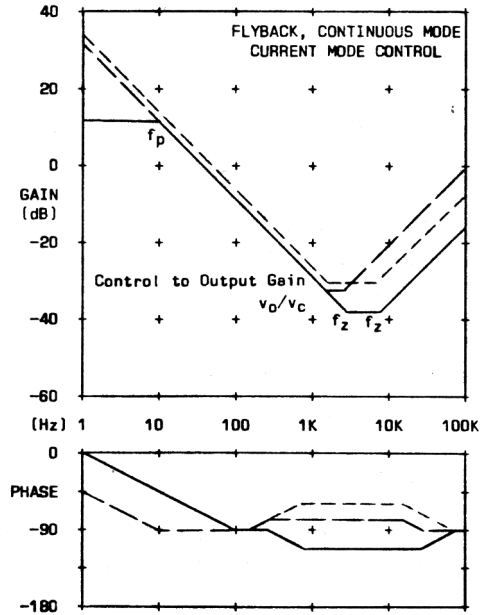Example 8: 12 Volt, 60 Watt Output

All power circuit parameters
are the same as Example 7.



Basic Equations — Duty Cycle Control:

$$I_o = I_L(1-D), \quad I_L = K V_C, \quad K = \max I_L / \max V_C, \quad \omega_z = \frac{1}{R_C C}, \quad \omega_p = \frac{1+D}{R_o C}, \quad D = \frac{V_{in}}{V_o + V_{in}}$$

DC Relationships:

$$(1) \quad V_o = V_{in} D / (1-D) = K V_C R_o \frac{V_{in}}{V_o + V_{in}} \quad (1a) \quad V_C = \frac{V_o(V_o + V_{in})}{K R_o V_{in}}$$

Control to Output Gain:

$$(2) \quad \frac{v_o}{v_c} = K R_o \frac{V_{in}}{(2V_o + V_{in})} f_1(s) H_e(s), \quad H_e(s) = \frac{1 + s/\omega_z}{1 + s/\omega_p}$$

Line to Output Gain:

$$(3) \quad \frac{v_o}{v_{in}} = \frac{V_o^2}{2V_o V_{in} + V_{in}^2} H_e(s) \quad \text{RHP zero: } f_1(s) = 1 - \frac{sL}{R} \frac{V_o(V_o + V_{in})}{V_{in}^2}$$

Corner Frequencies:

$$f_p = (1+D) / (2\pi R_o C) = 0.884 \text{ Hz at } 24 \text{ V, } 24 \Omega, \quad = 9.95 \text{ Hz at } 12 \text{ V, } 2.4 \Omega$$

$$f_z (\text{ESR}) = 1 / (2\pi R_C C) = 1590 \text{ Hz at } 10 \text{ m}\Omega, \quad 7950 \text{ Hz at } 2 \text{ m}\Omega$$

$$f_z (\text{RHP}) = 2728 \text{ Hz at } 12 \text{ V and } 2.4 \Omega, \quad = 7275 \text{ Hz at } 24 \text{ V and } 2.4 \Omega$$

Low Frequency Gain from Equation (2):

$$K = \frac{\max I_L}{\max V_C} = \frac{\max I_o}{(1-D) \max V_C} = \frac{6}{(1-.5)2.5} = 4.8$$

$$v_o/v_c = 57.6 \text{ (35.2 dB) at } 24 \text{ V, } 24 \Omega, \quad = 3.84 \text{ (11.7 dB) at } 12 \text{ V, } 2.4 \Omega$$

FLYBACK - CONTINUOUS INDUCTOR CURRENT - DIRECT DUTY CYCLE CONTROL

Error Amplifier Compensation:

Control I.C.: UC1846

Crossover frequency (0 dB loop gain):

$f_c = 800$ Hz (best achievable - RHPzero)

E/A gain needed at 800 Hz = 26.4 dB

Two poles cancel the ESR zero and right-half-plane zero. The location of these two poles is set by trail and error. Although above the crossover frequency, these poles are necessary or the gain would stay flat or even rise, causing instability at higher frequency.

$f_p = 2700$ Hz at 26.4 dB gain

$f_p = 8000$ Hz at 17.1 dB

The E/A gain is flat (26.4 dB) below the first pole at 2700 Hz.

Total control voltage swing, ΔV_c , needed to maintain constant output voltage V_o with worst case line and load variation is (from Eq. 1a):

$$(1a) \quad V_c = \frac{V_o(V_o+V_{in})}{KR_o V_{in}} = 0.156 \text{ to } 2.08 \text{ V.} \quad \Delta V_c = 1.92 \text{ V}$$

Output voltage error with actual E/A DC gain of 20.1 (26.4 dB below 2700 Hz):

$$\Delta V_o = \Delta V_c / 20.1 = 1.92 / 20.1 = 95 \text{ mV} \quad (1\% \text{ regulation})$$

Implementation: Circuit of Appendix A-1

Current control factor, $K = 4.8$, in the UC1846 is set by the fixed gain (3X) of the current sense amplifier together with current sampling resistor R_s .

$$K = I_L / V_c = 4.8 = 1 / (3R_s). \quad R_s = .069 \Omega$$


UC1846 error amplifier gain limit is >80 dB with $R_f >30K$. 26.4 dB needed, OK

Gain required (26.4 dB) = 20.9 = R_f / R_i . Let $R_f = 500K$, $R_i = 500K / 20.9 = 24K$.

Pole 1 at $f_p = 2700$ Hz. $C_f = 1 / (2\pi f_p R_f) = 120$ pF

Pole 2 at $f_p = 8000$ Hz $R_p = R_i / 10 = 2.4K$. $C_p = 1 / (2\pi f_p R_p) = 8200$ pF

Slope compensation: Current downslope is 1.5A/8.33 μ s, or 2.25A projected over the 12.5 μ s period. This equates to $2.25 \times .069 = .155$ volts p-p at the current sense amplifier input. Compensation ramp should be $.155 / 2 = .0775$ V positive ramp. UC1846 oscillator ramp is 2 V. A 25:1 divider provides .077 V. Put 1K between current sense resistor R_s and current sense amplifier input, and 24K from timing capacitor C_t to current sense amplifier input.

 

BOOST CONFIGURATIONS -- BASIC EQUATIONS

Boost regulator topologies have the same general characteristics as their flyback circuit counterparts. The Bode plots have the same shape, and the same type of compensation is employed. The specific values of gain and pole/zero frequencies are slightly different because of modifying factors in the various basic equations: Accordingly, only the basic equations are given for the boost circuits.

BOOST -- Discontinuous Inductor Current -- Duty Cycle Control:

DC Relationships:

$$(1) \quad V_o = V_{in} \left(\frac{1}{2} + \sqrt{\frac{1}{4} + \frac{D^2}{J}} \right)^{\frac{1}{2}}, \quad D = V_c/V_s, \quad J = 2Lf_s/R_o$$

Control to Output Gain:

$$(2) \quad \frac{v_o}{v_c} = \frac{V_{in}}{V_s \sqrt{J}} \left(\frac{4 - V_{in}/V_o}{4 - V_{in}/V_o - V_{in}^2/V_o^2} \right)^{\frac{1}{2}} H_e(s), \quad H_e(s) = \frac{1+s/\omega_z}{1+s/\omega_p}$$

Line to Output Gain:

$$(3) \quad \frac{v_o}{v_{in}} = \frac{V_o}{V_{in}} H_e(s), \quad \omega_z = \frac{1}{R_c C}, \quad \omega_p = \frac{2+1/\sqrt{1+4D^2/J}}{R_o C}$$

BOOST -- Discontinuous Inductor Current -- Voltage Feedforward:

DC Relationships:

$$V_s = V_{in}/K, \quad K = V_{in}D/\max V_c$$

$$V_o = V_{in} \left(\frac{1}{2} + \sqrt{\frac{1}{4} + \frac{(K^2/J)V_c^2/V_{in}^2}} \right)^{\frac{1}{2}}, \quad D = V_c/V_s = \frac{KV_c}{V_i}, \quad J = 2Lf_s/R_o$$

Control to Output Gain:

$$(2) \quad \frac{v_o}{v_c} = \frac{K}{\sqrt{J}} \left(\frac{4 - V_{in}/V_o}{4 - V_{in}/V_o - V_{in}^2/V_o^2} \right)^{\frac{1}{2}} H_e(s), \quad H_e(s) = \frac{1+s/\omega_z}{1+s/\omega_p}$$

Line to Output Gain:

$$(3) \quad \frac{v_o}{v_{in}} = \frac{V_o}{2V_o - V_{in}} H_e(s), \quad \omega_z = \frac{1}{R_c C}, \quad \omega_p = \frac{2+1/\sqrt{1+4D^2/J}}{R_o C}$$

BOOST -- Discontinuous Inductor Current -- Current Mode Control:

DC Relationships:

$$I_p = KV_c, \quad K = \max I_p/\max V_c$$

$$(1) \quad V_o = V_{in} \left(\frac{1}{2} + \sqrt{\frac{1}{4} + \frac{(K^2/J)V_c^2/V_{in}^2}} \right)^{\frac{1}{2}}, \quad D = V_c/V_s = \frac{KV_c}{V_i}, \quad J = 2Lf_s/R_o$$

Control to Output Gain:

$$(2) \quad \frac{v_o}{v_c} = \frac{K}{\sqrt{J}} \left(\frac{4 - V_{in}/V_o}{4 - V_{in}/V_o - V_{in}^2/V_o^2} \right)^{\frac{1}{2}} H_e(s), \quad H_e(s) = \frac{1+s/\omega_z}{1+s/\omega_p}$$

Line to Output Gain:

$$(3) \quad \frac{v_o}{v_{in}} = \frac{V_o}{2V_o - V_{in}} H_e(s), \quad \omega_z = \frac{1}{R_c C}, \quad \omega_p = \frac{2+1/\sqrt{1+4D^2/J}}{R_o C}$$

BOOST CONFIGURATIONS -- BASIC EQUATIONS

Boost -- Continuous Inductor Current -- Direct Duty Cycle Control:

$$D = V_c/V_s, \quad (1-D) = V_i/V_o, \quad \omega_o = \frac{1-D}{-LC}, \quad \omega_z = \frac{1}{R_c C}, \quad Q = \frac{R_o}{\omega_o L}$$

DC Relationships:

$$(1) \quad V_o = V_{in}/(1-D) = V_{in}/(1-V_c/V_s) \quad (1a) \quad V_c = V_s \frac{V_o - V_{in}}{V_o}$$

Control to Output Gain:

$$(2) \quad \frac{v_o}{v_c} = \frac{V_{in}}{V_s} \frac{V_o^2}{V_{in}^2} f_1(s) H_e(s), \quad H_e(s) = \frac{1 + s/\omega_z}{1 + (s/\omega_o)/Q + (s/\omega_o)^2}$$

Line to Output Gain:

$$(3) \quad \frac{v_o}{v_{in}} = \frac{V_o}{V_{in}} H_e(s) \quad \text{RHP zero: } f_1(s) = 1 - \frac{sL}{R} \frac{V_o^2}{V_i^2}$$

Boost -- Continuous Inductor Current -- Current Mode Control:

$$I_o = I_L(1-D), \quad I_L = KV_c, \quad \omega_p = \frac{2}{R_o C}, \quad \omega_z = \frac{1}{R_c C}, \quad D = \frac{V_o - V_{in}}{V_o}$$

DC Relationships:

$$(1) \quad V_o = -\sqrt{KV_c R_o V_i} \quad (1a) \quad V_c = V_o^2 / (KR_o V_i)$$

Control to Output Gain:

$$(2) \quad \frac{v_o}{v_c} = \frac{KR_o}{2} \frac{V_{in}}{V_o} f_1(s) H_e(s), \quad H_e(s) = \frac{1 + s/\omega_z}{1 + (s/\omega_o)/Q + (s/\omega_o)^2}$$

Line to Output Gain:

$$(3) \quad \frac{v_o}{v_{in}} = \frac{V_o}{2V_{in}} H_e(s) \quad \text{RHP zero: } f_1(s) = 1 - \frac{sL}{R} \frac{V_o^2}{V_i^2}$$

Voltage feedforward control does not perform effectively with continuous mode boost and flyback circuits, and this use is not recommended.