

AN1546

High Voltage, High Side Driver for Electronic Lamp Ballast Applications

Prepared by: Larry Baxter
Power Products Division

INTRODUCTION

As electronic ballasts continue to displace their old core and coil predecessors, we see increased emphasis being placed upon cost reduction, reduced part count, and overall simplification of designs. Motorola's new MPIC2151 Self Oscillating Half-Bridge Driver was developed to simplify electronic ballast designs, using Mos gated output switches in a half-bridge configuration.

The MPIC2151 is just one in a family of monolithic High Voltage Integrated Circuits (HVICs) from Motorola, which offer "single chip" solutions to drive problems which involve interfacing control logic to the high voltage output stage. These HVICs will accept ground referenced input signals and produce high and low side drive outputs, capable of driving either MOSFET or IGBT gates.

The MPIC2151 offers a floating channel high side driver, designed for boot strap operation in applications with a positive rail up to 600 volts. It also contains the low side driver output for the bottom switch in the half-bridge. Other features of the MPIC2151 include the provision for programmable oscillator frequency and under voltage lock out protection.

THEORY OF OPERATION

We will begin by discussing the functional block diagram of the MPIC2151, see Figure 1.

The MPIC2151 is intended to be powered from the rectified A-C line voltage, through a low wattage, high resistance dropping resistor to the V_{CC} pin. This HVIC has an internal zener clamp between V_{CC} (pin 1) and Common (pin 4) which

regulates at a nominal 15.6 volts. This requires typically less than 5 mA of current through the dropping resistor to regulate the voltage to the "on-board" circuitry.

The front end of the MPIC2151 operates much like a conventional CMOS 555 timer and can be configured for either synchronized running or self oscillation, with the addition of external R_T (pin 2) and C_T (pin 3) components. When used in the self oscillating mode, the frequency of operation can be stated by:

$$f_{osc} = \frac{1}{1.4(R_T * C_T)}$$

The MPIC2151 has internal circuitry which provides for a nominal 1.2 μs dead time between the High Output (pin 7) and the Low Output (pin 5). This is intended to minimize the possibility of both power switches being in conduction at the same time. It is also important to note that the R_T (pin 2) and L_O (pin 5) are in phase with each other.

The propagation delays for the outputs H_O and L_O are matched in order to simplify 50% duty cycle operation. This is taken care of by internal design features of the MPIC2151.

Finally, the High output (pin 7) can be used to drive an N-channel MOSFET or an IGBT as the upper switch in a half bridge circuit. This output is not referenced to Common, instead it gets its reference through V_S (pin 6) to the mid-point of the half bridge. The MPIC2151 will operate in rail conditions from 10-600 Vdc.

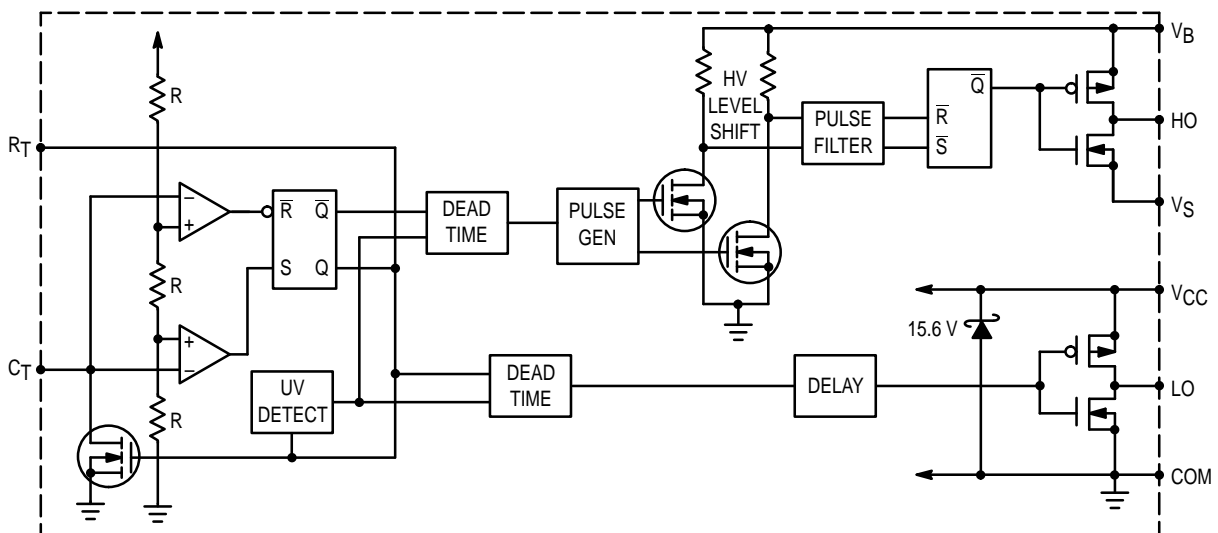


Figure 1.

APPLICATION

One example of a lamp ballast circuit application for the MPIC2151 is the self oscillant, half bridge topology employed in most compact fluorescent lamp products. The half bridge configuration offers the most advantages with lower voltage components for a given line voltage and therefore, lower system cost. Generally speaking, galvanic isolation is not a consideration in this application (1).

The demonstration circuit in Figure 2 is an example of a compact fluorescent lamp, powered from 230 Vac mains. The rectified DC buss voltage will be approximately 320 Vdc and the component values were selected for applications up to 20 watts.

This circuit is greatly simplified by the MPIC2151, as there is no need for the conventional diac start-up circuitry and the space consuming saturable transformer normally used to produce the gate drive. This allows for a more compact, lighter weight ballast. It should be noted that the circuit density can be further increased by the use of surface mounted components.

Lay Out

When designing with the MPIC2151, there are some considerations to be observed in the beginning. This will help to avoid many of the "pit falls" which may require attention after the circuit has been assembled.

First, proper layout of the circuit board is critical. Noise can interfere with the operation of the control circuitry, causing erratic operation or misfiring of the power devices. It is important to minimize stray inductances along the main current loop, as these can cause very fast high voltage spikes to occur.

Second, Use high frequency de-coupling techniques in the power stage to minimize the effects of stray capacitance.

Third, use series gate resistors (see R₃ and R₄) to control the turn off speed (Dv/Dt) of the power devices.

Fourth, the physical location of the bootstrap capacitor must be placed as close to the HVIC V_B and V_S leads as practical. This further helps to keep the stray inductance on the V_S lead to a minimum.

And finally, when looking for noise spikes, probe at the MPIC2151 lead itself. Looking further away may not give an accurate indication of the total effects of the stray inductance (2).

Selecting the Dropping Resistor Value

In the self oscillating mode, the MPIC2151 self starts when the high voltage dropping resistor R₁ charges the I_C supply filter capacitor C₂ to a value above the HVICs internal Under Voltage Lock-Out threshold (V_{CCUV+} = 8.4 volts typical). The output of the half bridge then oscillates at a frequency determined by the timing components R_T and C_T (with a 50% duty cycle).

Selecting the correct value for the dropping resistor is accomplished by taking into account the total current requirements for the HVIC and surrounding components. These include:

1. The current required to regulate V_{CC} through the internal zener clamp from V_{CC} (pin 1) to Common (pin 4).
2. The current required to switch the gates of the power MOSFETs or IGBTs.
3. The quiescent current I_{QCC} of the MPIC2151.
4. The high voltage level shifting currents within the HVIC.
5. The current sourced into the R_T resistor from the chip V_{CC} (3).

Obviously, the largest component of current is that for the zener clamp. Generally speaking, the "rule of thumb" solution for R₁ can be expressed by:

$$R_1 = \frac{(V_{buss} - 15.6 \text{ volts})}{(I_{CC} \times \kappa)}$$

Where: **V_{buss}** = the rectified DC value of the AC line voltage, **15.6 volts** is the nominal internal clamp voltage, **I_{CC}** (from the MPIC2151 data sheet = 5 mA nominal), **κ** = 1.30 to 1.40 multiplier to provide sufficient current for the other circuit elements, over the expected operating temperature range.

$$R_1 = \frac{(320 - 15.6)}{(6.48) \times 10^{-3}} = 47 \text{ k}\Omega$$

In our schematic example, V_{buss} = 320 Vdc, V_{clamp} = 15.6 V, I_{CC} = 5 mA, plus 30% = 1.48 mA, and R₁ = 47 kΩ. Also, it should be noted that C₂ should be sufficiently large that it does not become discharged during normal circuit operation. The value we selected in our example is a 47 μF electrolytic capacitor.

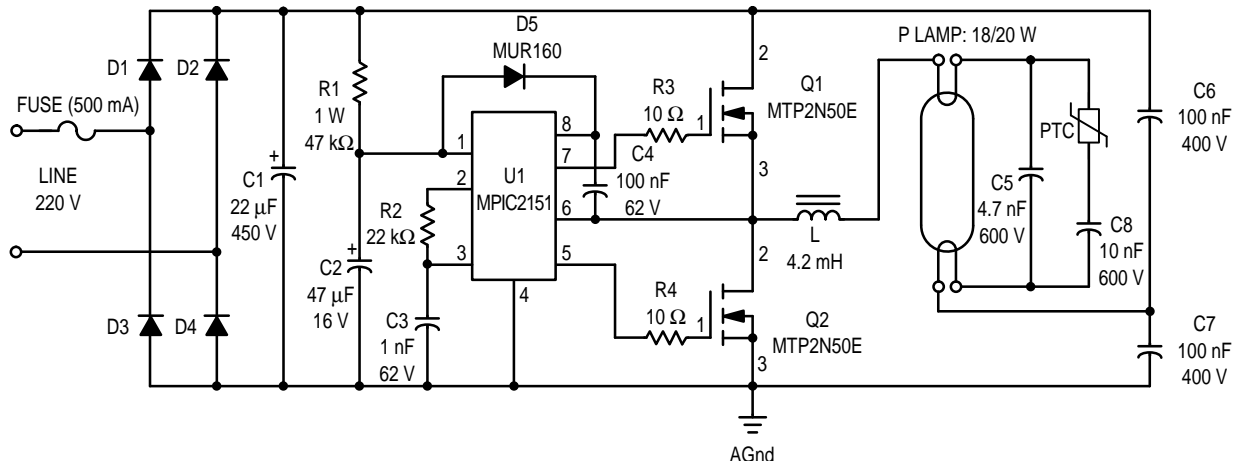


Figure 2.

Once the lamp has struck, aided with the high voltage pulses developed by the starting network (L, C₅, C₈, and the PTC), the lamp operates at the resonant frequency defined by the L-C tank circuit formed mainly by the inductor L and C₆,

C₇ in parallel. Therefore, the values of R₂ (R_T) and C₃ (C_T) are selected to set the output frequency of the MPIC2151 slightly above or below the F₀ of the tank circuit. The output of Q₁ and Q₂ will be a 160 volt RMS square wave at 50% duty cycle.

Recommended Board Layout

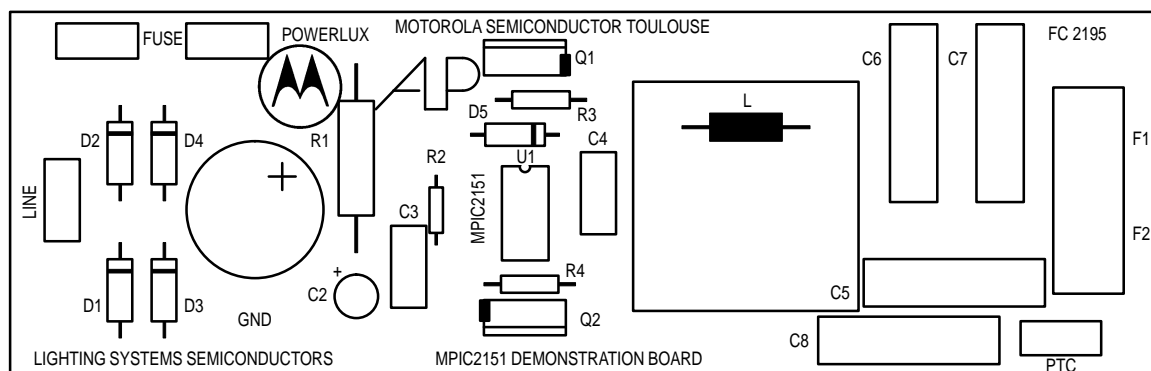


Figure 3. (Top View)

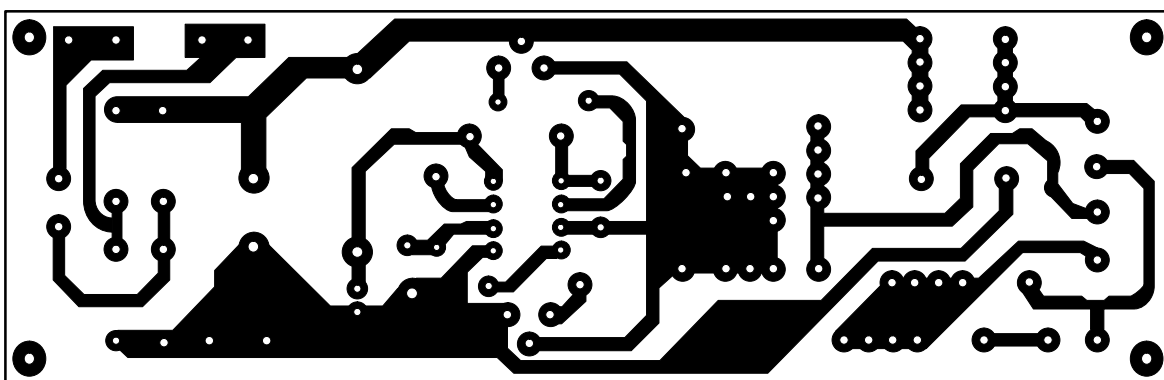


Figure 4. (Bottom View)

Parts List

C ₁	22 μF/450 V/electrolytic	R ₁	47 kΩ
C ₂	47 μF/25 V/electrolytic	R ₂	22 kΩ
C ₃	1 nF/63 V/ceramic	R ₃ , R ₄	10 Ω
C ₄	100 nF/63 V/ceramic	L	4.2 mH
C ₅	4.7 nF/1000 V/polypropylene	Lamp	18–20 W Compact Fluorescent
C ₆ , C ₇	100 nF/400 V	Q ₁ , Q ₂	MTP2N50E
C ₈	10 nF/1000 V		
D ₁ , D ₂ , D ₃ , D ₄	1N4007		
D ₅	MUR160		

Notes: All resistors are ±5%, 0.25 watt unless otherwise noted.


All capacitors are polycarbonate, 63 V, ±10% unless otherwise noted.

ACKNOWLEDGEMENTS

The author wishes to thank Michael Bairanzade and Francois Comes for providing valuable information and insight to the writing of this paper.

REFERENCES

- (1) Bairanzade, Michael "Electronic Lamp Ballast Design" App-Note, Motorola, Inc.
- (2) Wood, Peter N. "Simplified Ballast Designs Using High Voltage Mos Gate Drivers". High Frequency Power Conversion Conf. 1994.
- (3) Houk, Tick "Choosing the Correct Dropping Resistor Value for the IR2151 / IR2152 / IR2155 Control IC's" App-Note, I.R. Corp.

Motorola reserves the right to make changes without further notice to any products herein. Motorola makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Motorola assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters can and do vary in different applications. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. Motorola does not convey any license under its patent rights nor the rights of others. Motorola products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Motorola product could create a situation where personal injury or death may occur. Should Buyer purchase or use Motorola products for any such unintended or unauthorized application, Buyer shall indemnify and hold Motorola and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Motorola was negligent regarding the design or manufacture of the part. Motorola and  are registered trademarks of Motorola, Inc. Motorola, Inc. is an Equal Opportunity/Affirmative Action Employer.

How to reach us:

USA / EUROPE: Motorola Literature Distribution;
P.O. Box 20912; Phoenix, Arizona 85036. 1-800-441-2447

JAPAN: Nippon Motorola Ltd.; Tatsumi-SPD-JLDC, Toshikatsu Otsuki,
6F Seibu-Butsuryu-Center, 3-14-2 Tatsumi Koto-Ku, Tokyo 135, Japan. 03-3521-8315

MFAX: RMFAX0@email.sps.mot.com – TOUCHTONE (602) 244-6609
INTERNET: <http://Design-NET.com>

HONG KONG: Motorola Semiconductors H.K. Ltd.; 8B Tai Ping Industrial Park,
51 Ting Kok Road, Tai Po, N.T., Hong Kong. 852-26629298

