

Mixed-Mode EMI and It's Implications to Filter Design

By
Dan Chen


EMI

-Differential Mode (DM)

-Common Mode (CM)


- *Mixed Mode*

Review of Conventional EMI Theory

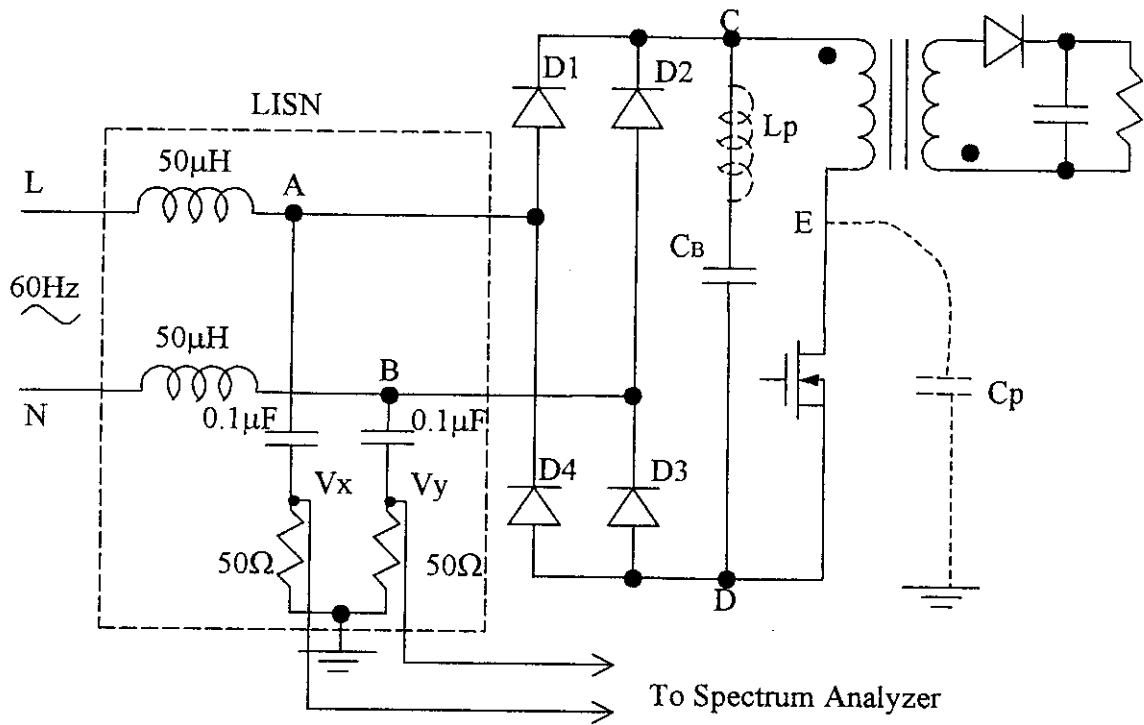


$$\text{CM Noise: } \frac{V_x + V_y}{2}$$




$$\text{DM Noise: } V_x - V_y$$

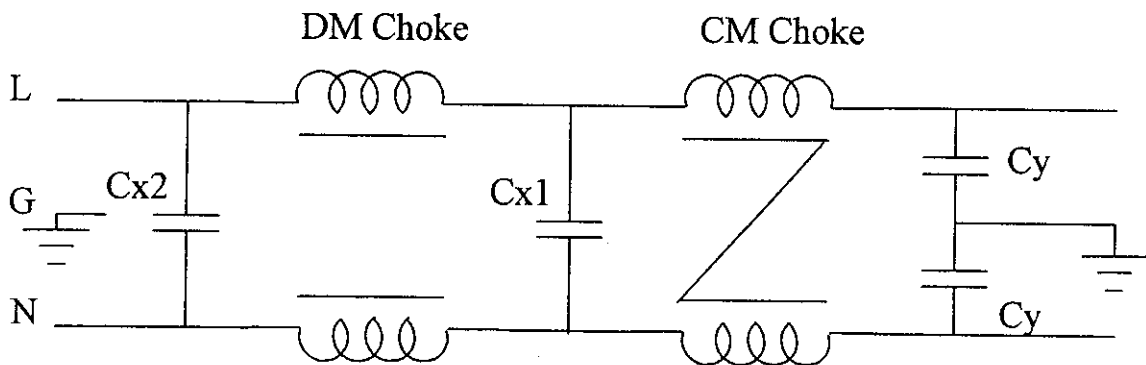

Composite EMI Filter

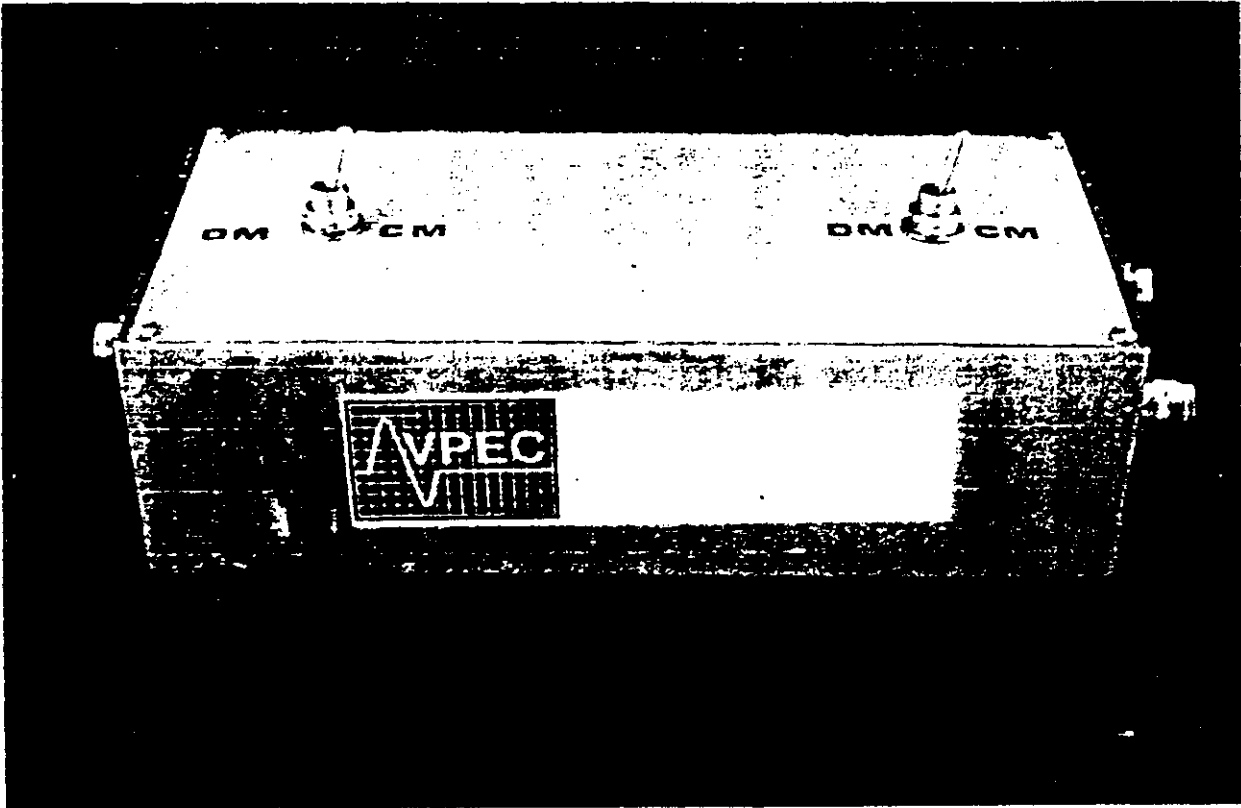

Filter Equivalent Circuits

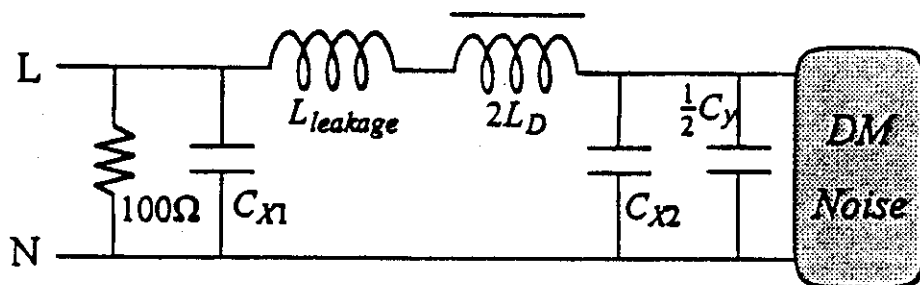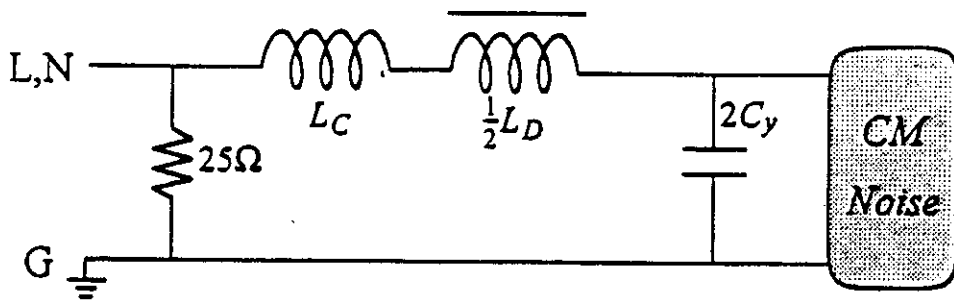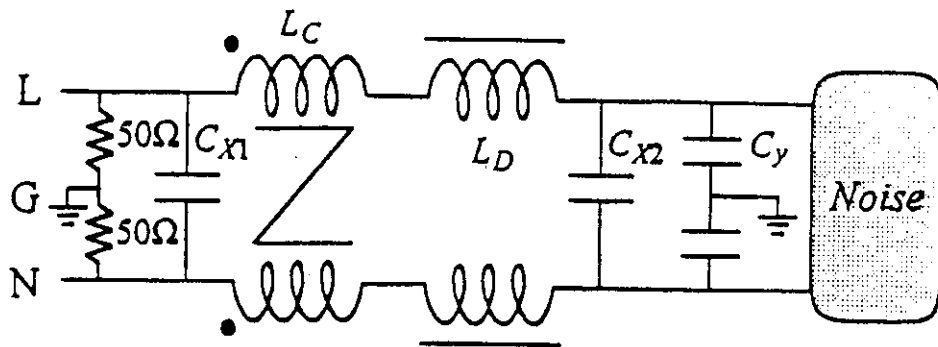

Tests Using a Noise Separator

Test # 2: "Tests Using Noise Separator"

Test # 1: No filter is inserted.

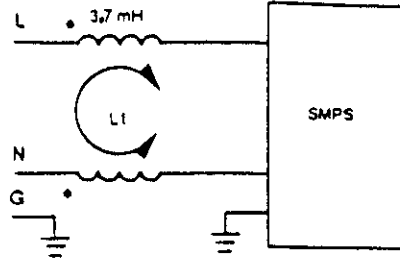


Figure 6(a) Test 2 Diagram

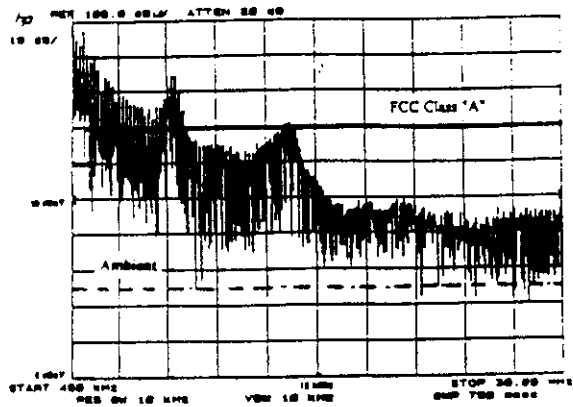


Figure 5(a) Total Noise

Total

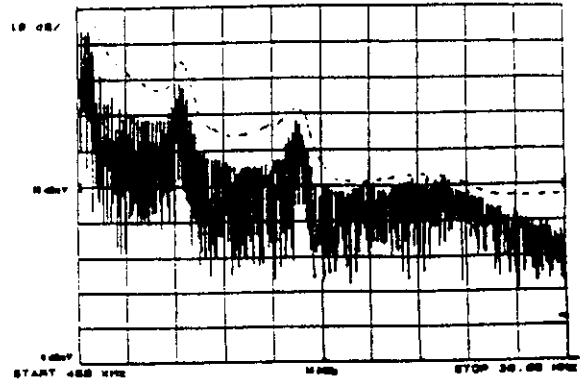


Figure 6(b) Total Noise

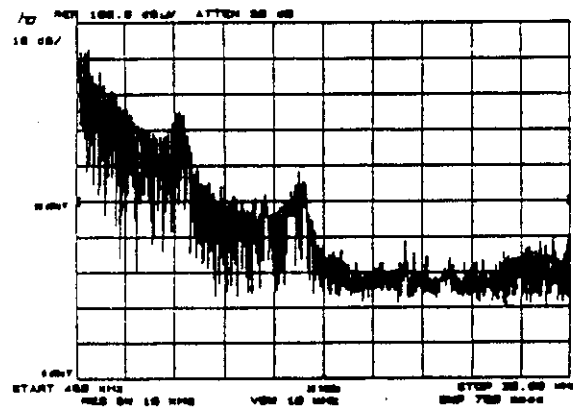


Figure 5(b) DM Noise

DM

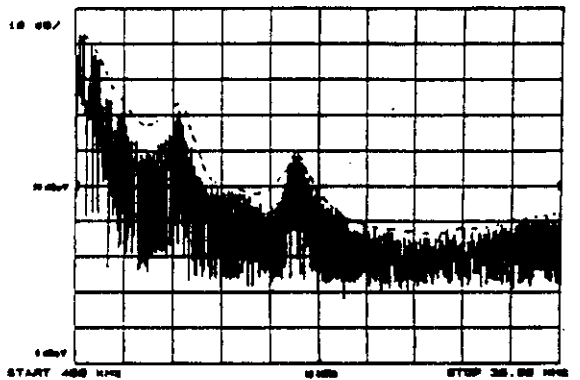


Figure 6(c) DM Noise

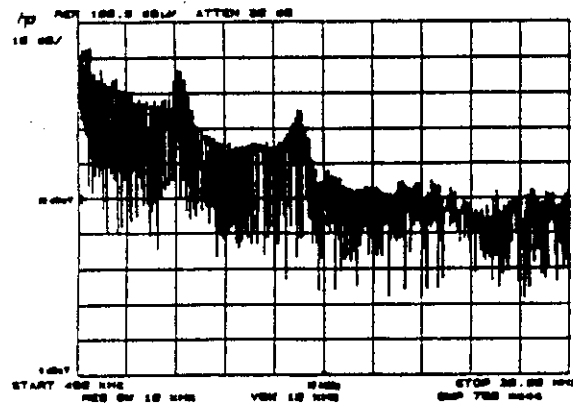


Figure 5(c) CM Noise

CM

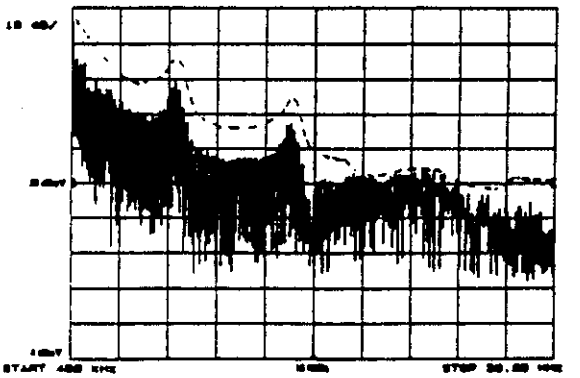


Figure 6(d) CM Noise

Test # 3:

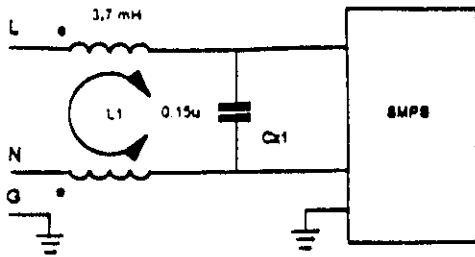


Figure 7(a) Test 3 Diagram

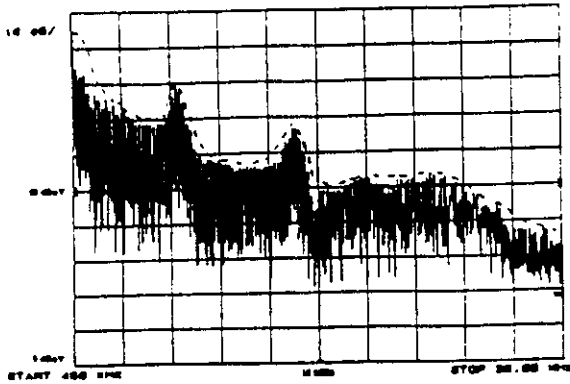


Figure 7(b) Total Noise

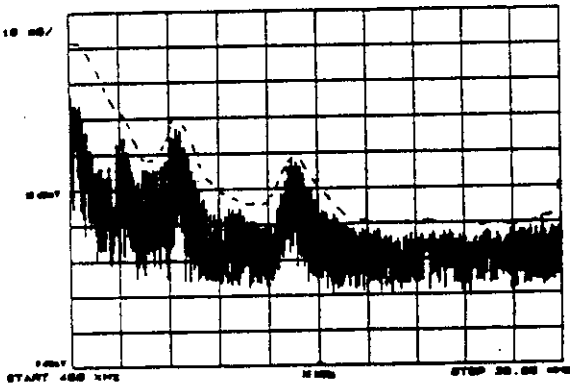


Figure 7(c) DM Noise

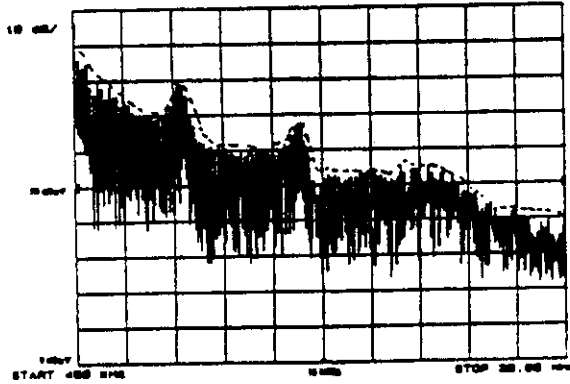


Figure 7(d) CM Noise

Test # 4:

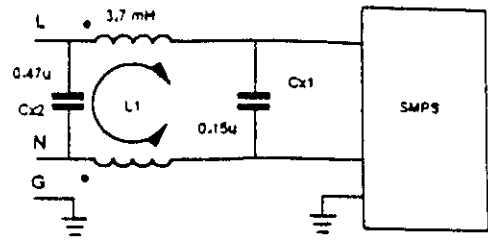


Figure 8(a) Test 4 Diagram

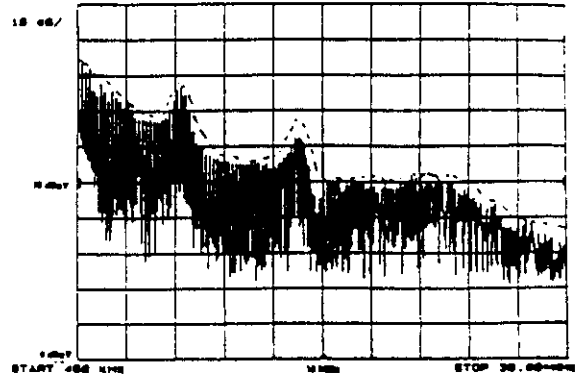


Figure 8(b) Total Noise

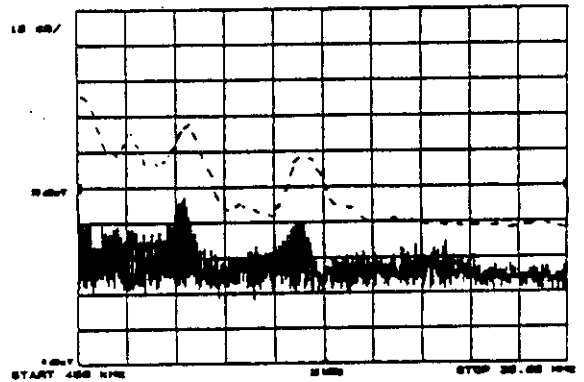


Figure 8(c) DM Noise

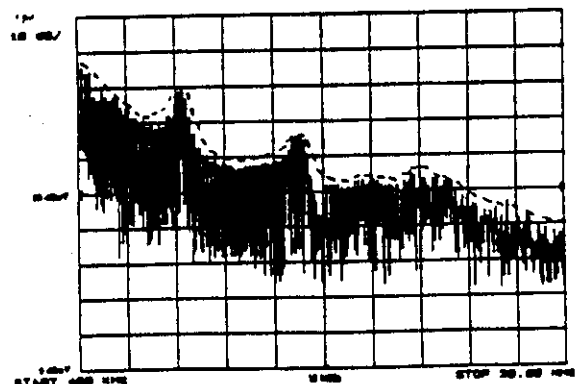


Figure 8(d) CM Noise

Test # 9:

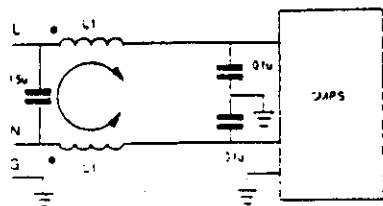


Figure 13(a) Test 9 Diagram

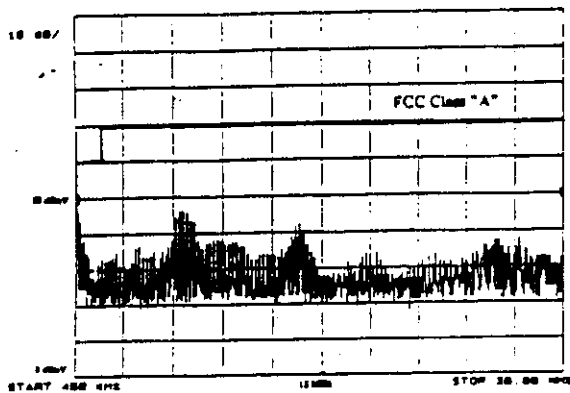


Figure 13(b) Total Noise

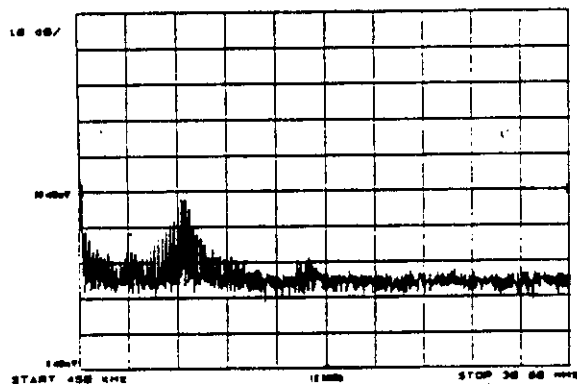


Figure 13(c) DM Noise

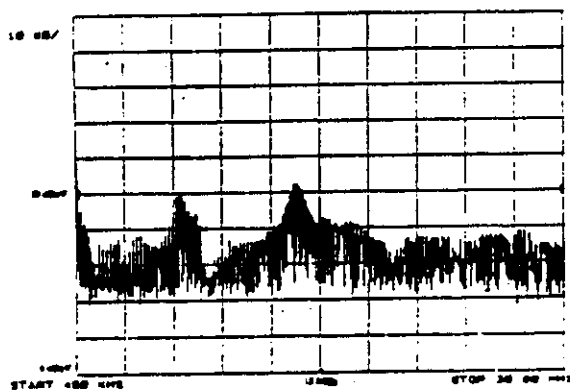


Figure 13(d) CM Noise

Test # 10:

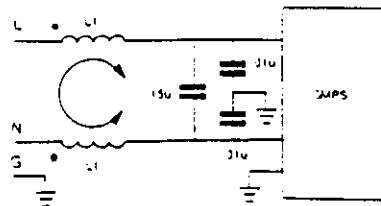


Figure 14(a) Test 10 Diagram

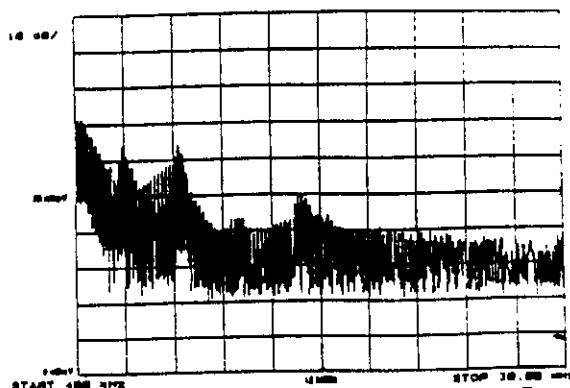


Figure 14(b) Total Noise

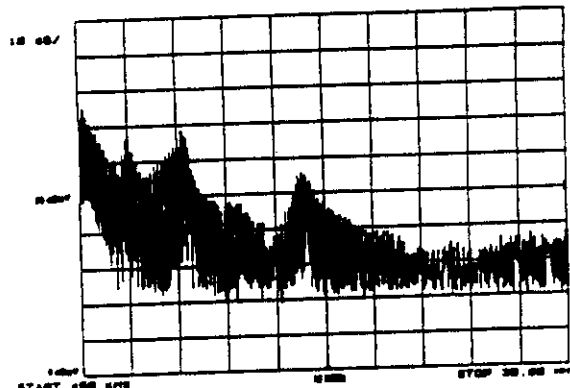


Figure 14(c) DM Noise

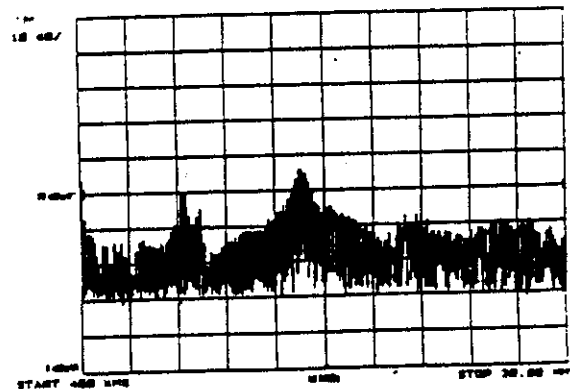



Figure 14(d) CM Noise

7


Mixed-Mode EMI Noise in Offline Converters

- Formerly called Non-Intrinsic Differential-Mode (NIDM) Noise
- Caused by dv/dt coupling through unbalanced noise current path
- Can be effectively attenuated by balancing noise current path (using an X capacitor)
- Tools for investigation:
 - DM/CM Noise Separator
 - Zero-Span Mode of Spectrum Analyzer

Mixed-Mode EMI Noise

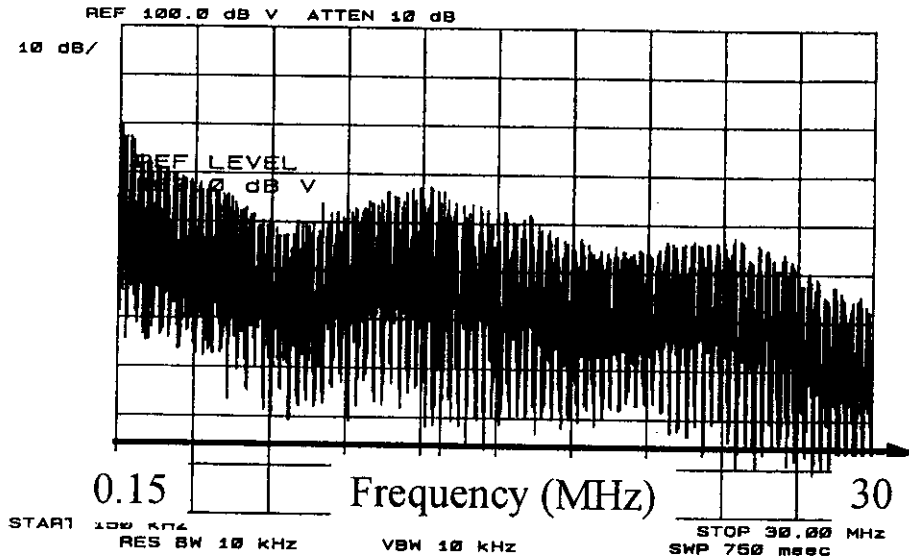


Regular EMI spectrum

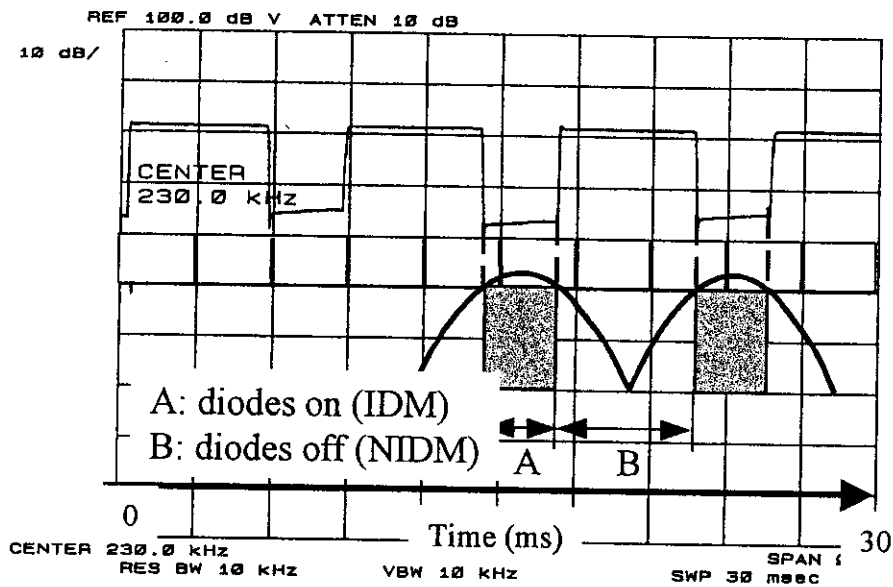


Zero-span mode

Mechanism of Mix-Mode Noise Coupling

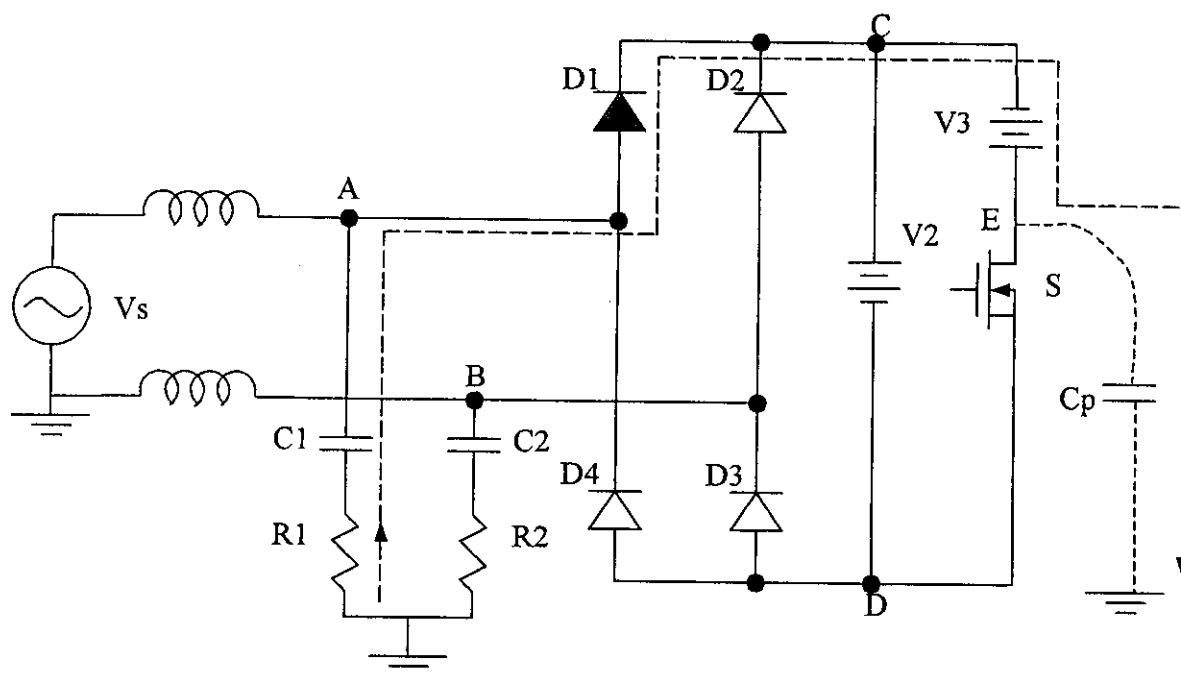


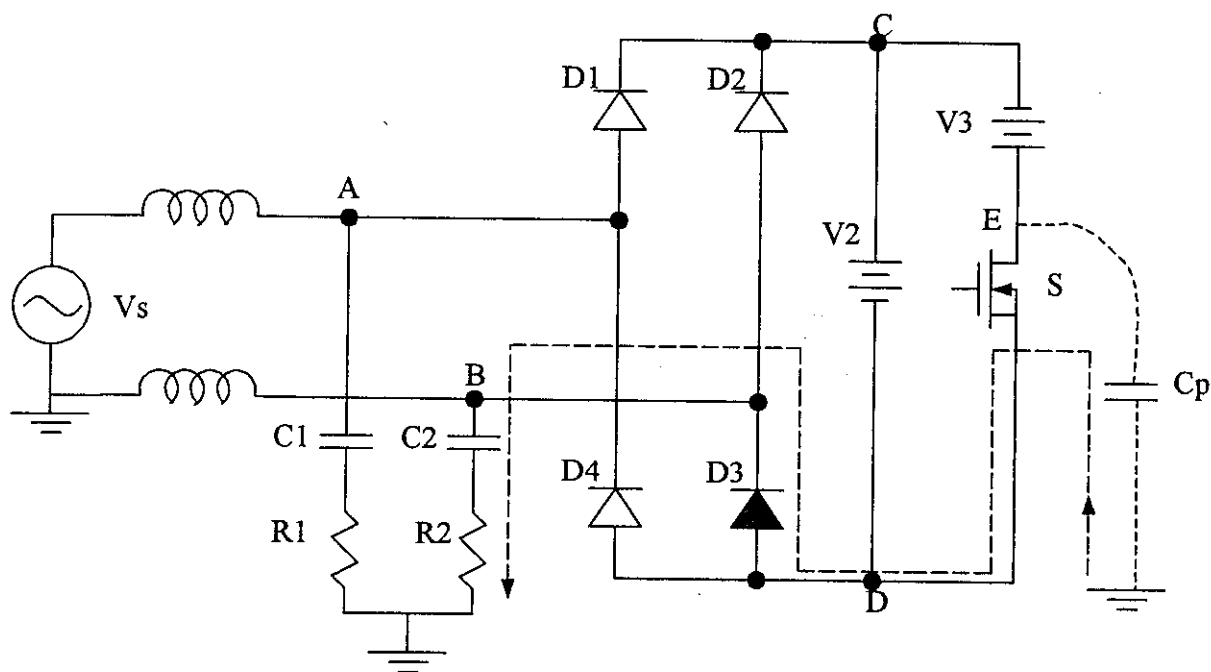Diodes off, MOSFET turned off, C_p charged




Diodes off, MOSFET turned on, C_p discharged

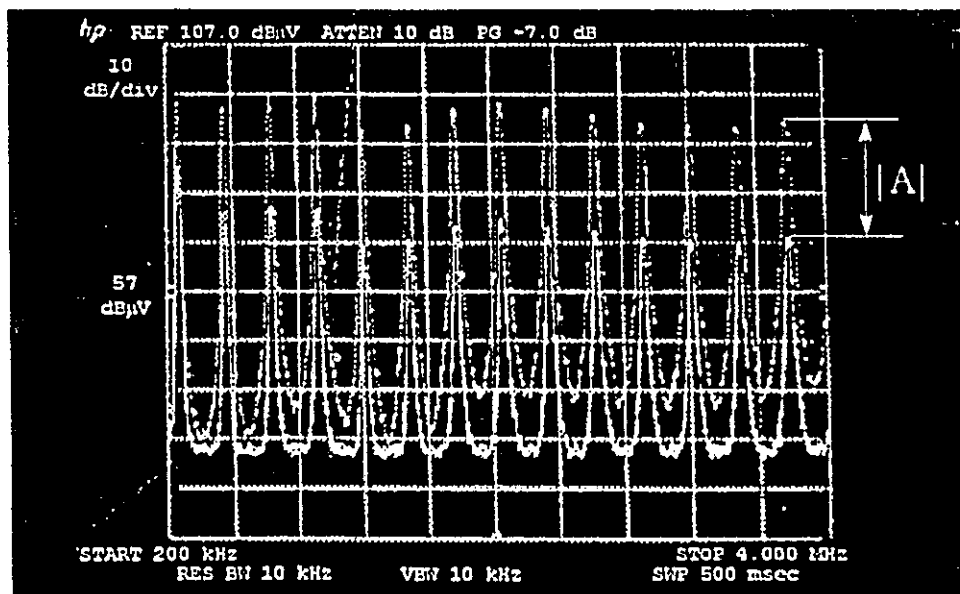
EMI Measurement of an Off-line Power Supply



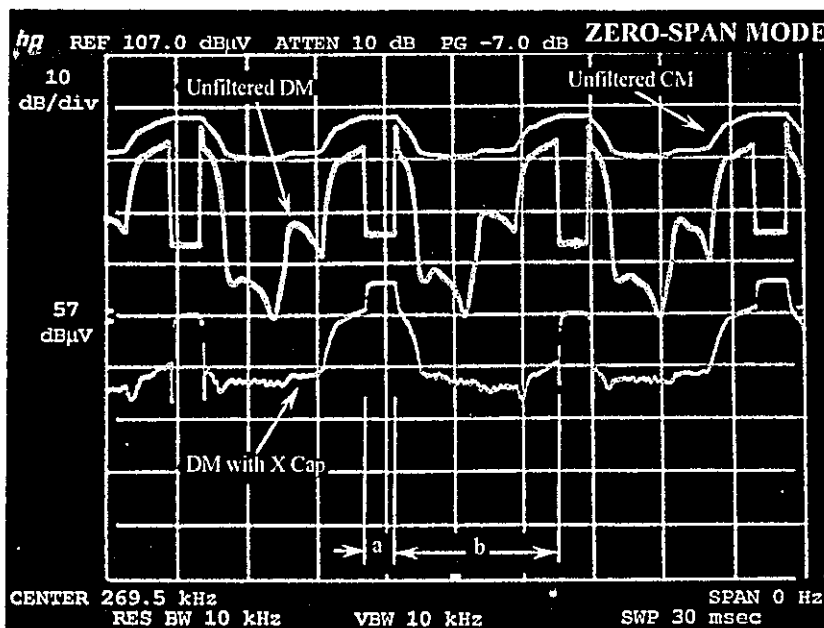- Sweep in the time-domain reserves only maximum values.



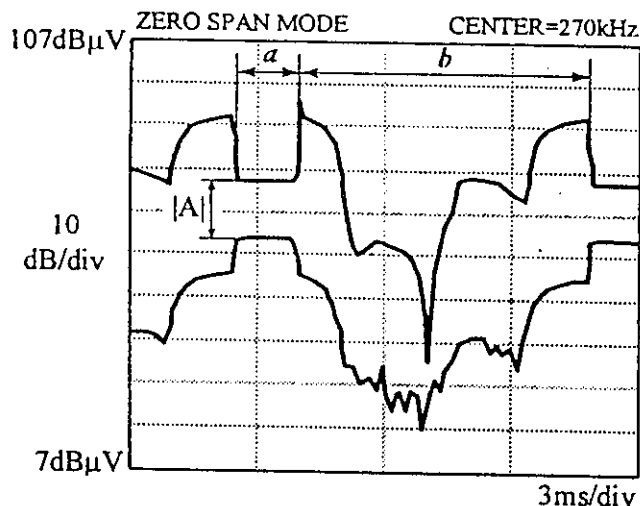EMI Measurement of an off-line Power Supply (Using Zero Span Mode)




- *a*: Diode Bridge ON; *b*: Diode Bridge OFF
- $|A|$ must be measured for every harmonic.

DM



MODULATED CM HARMONIC MAGNITUDE

- a: Rectifier On"
- b: Rectifier "Off"

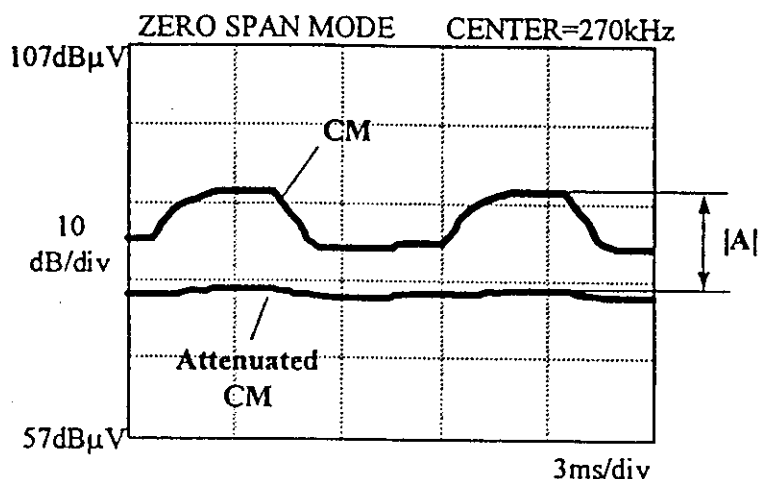




- Harmonic magnitude is modulated by the diode bridge.
- Only peak values are useful.

CM




Implications of Mixed-Mode EMI Noise

Symmetrical Vs. Asymmetrical DM Chokes





Symmetrical Choke

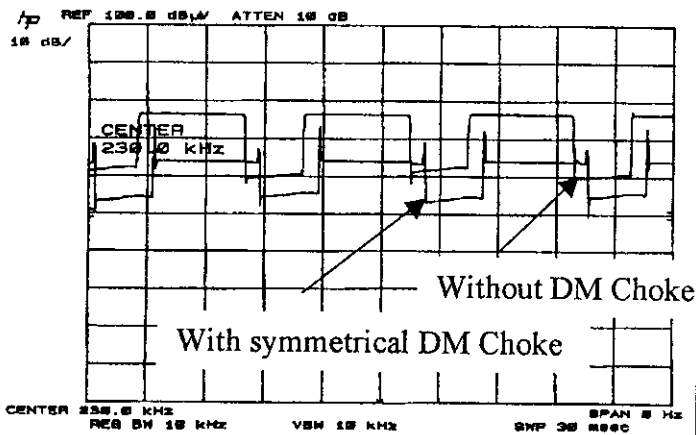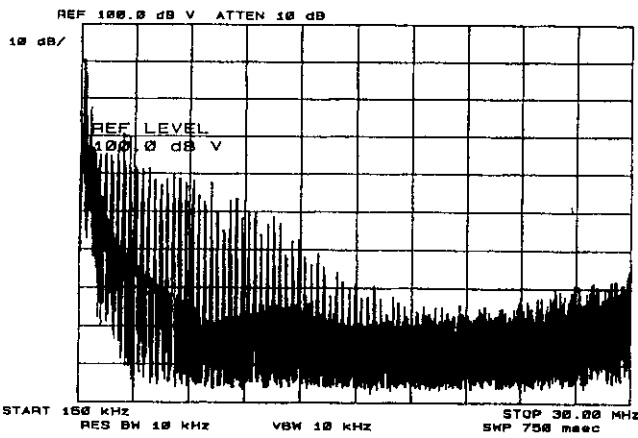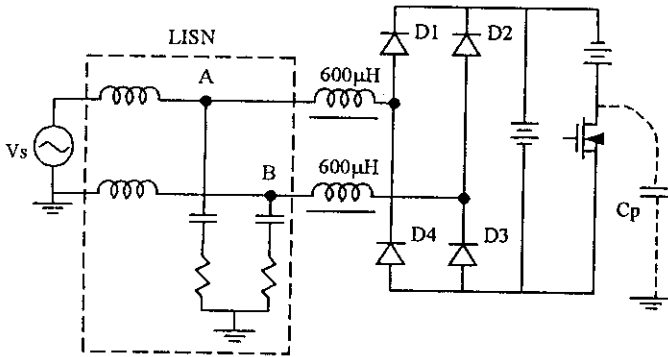



Asymmetrical Choke

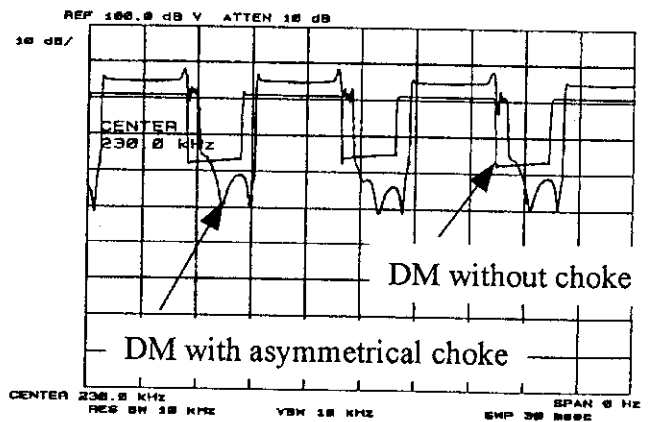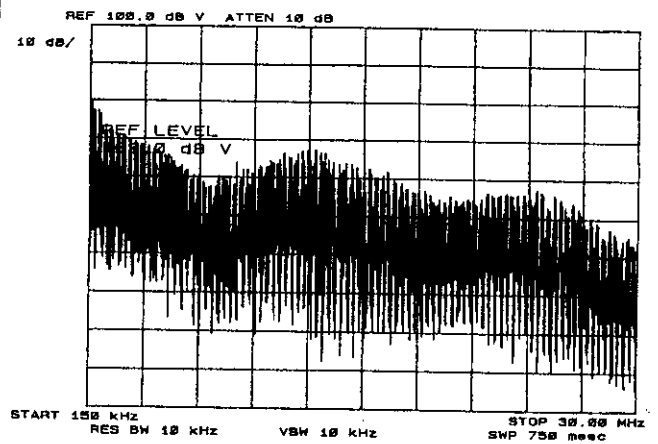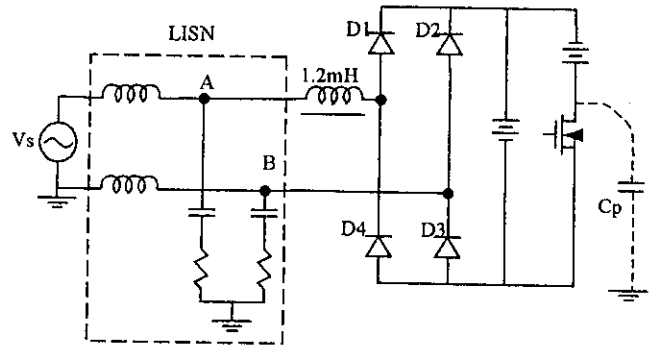

Symmetrical Vs. Asymmetrical DM Chokes

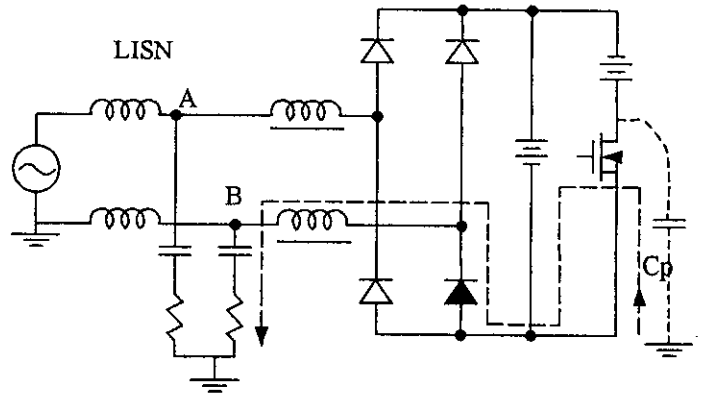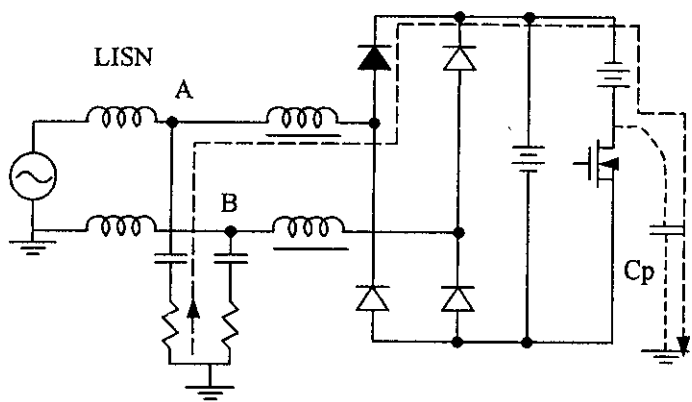
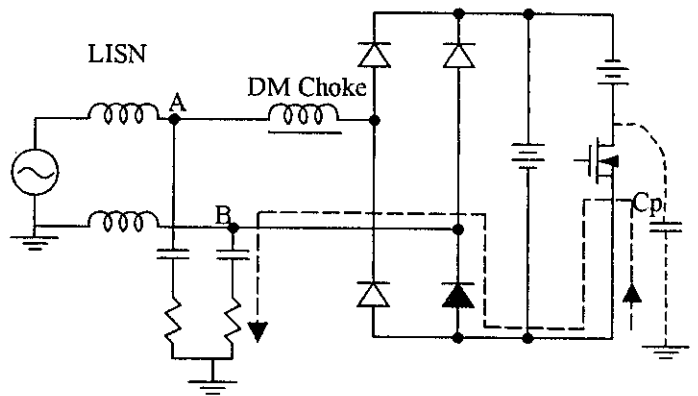
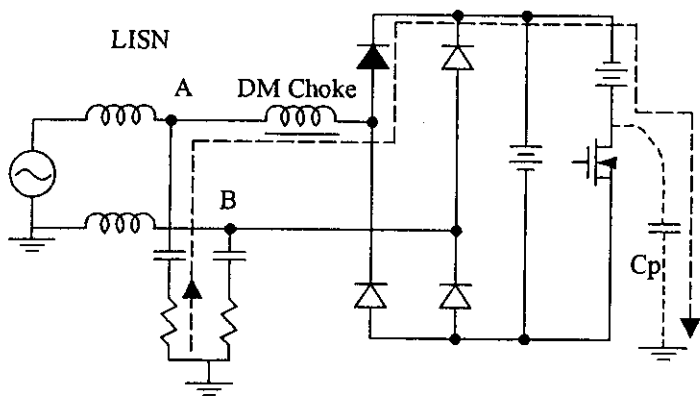


Using X Cap to Balance MM

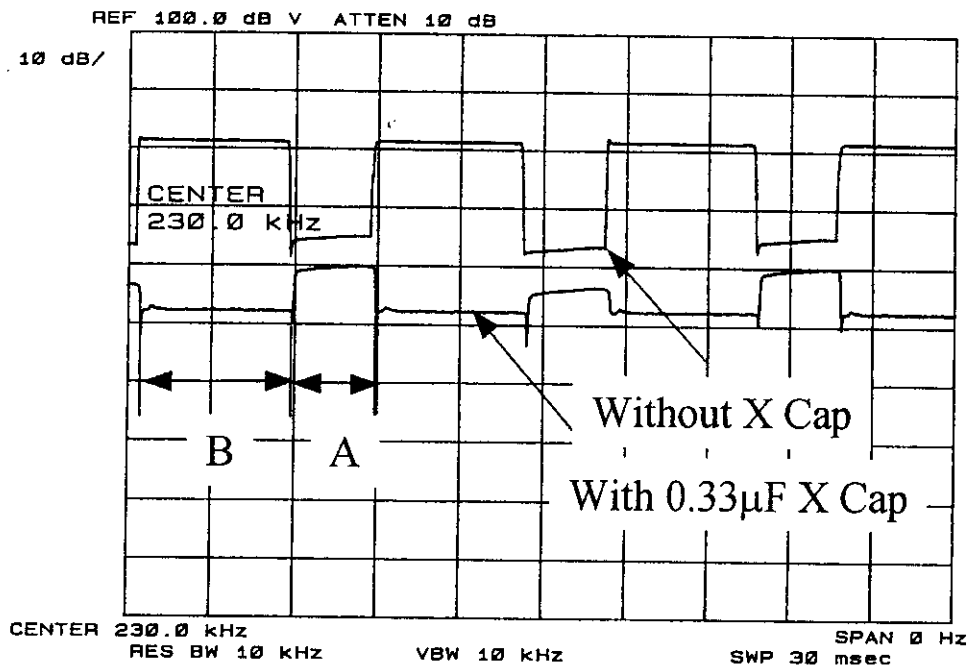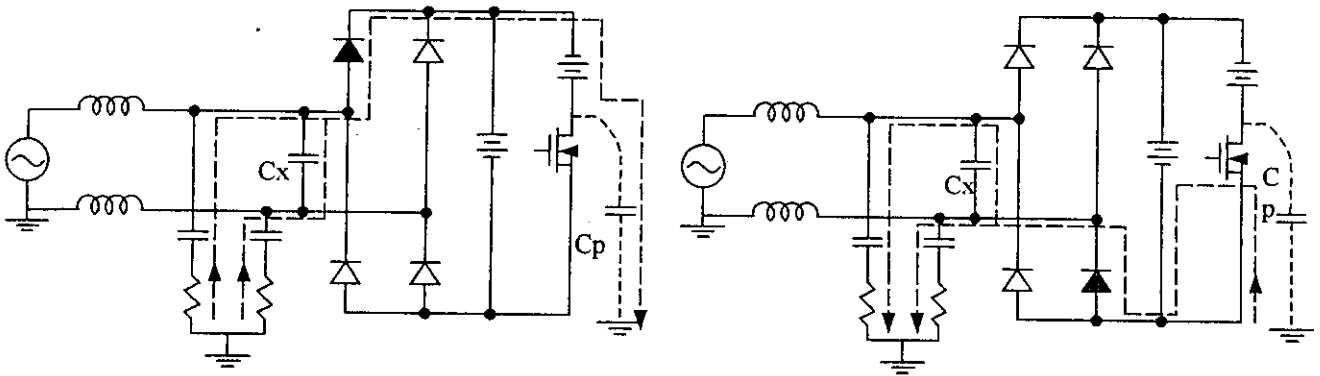





Which Side Should the X Cap Be Placed?

Asymmetrical Choke

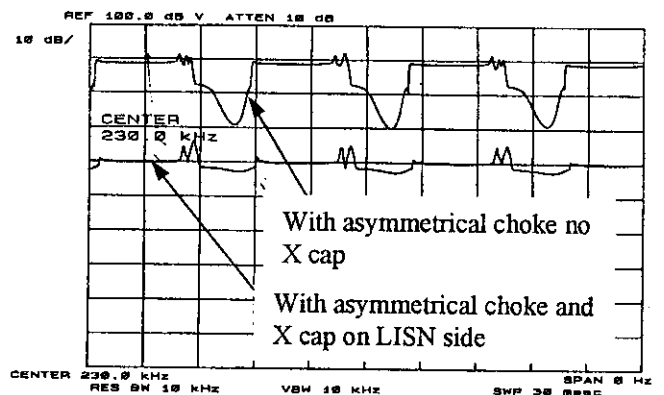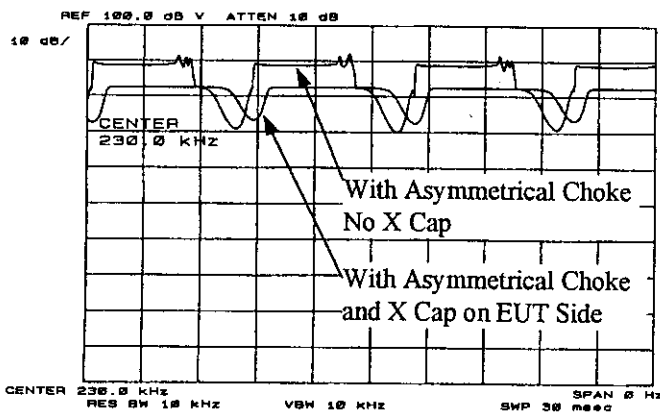
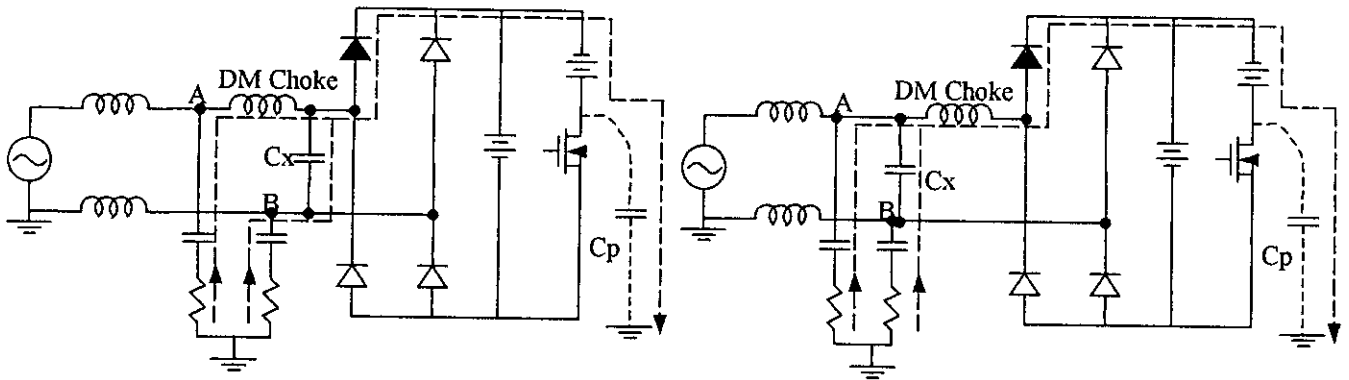


Which Side Should the X Cap Be Placed?


Symmetrical Choke

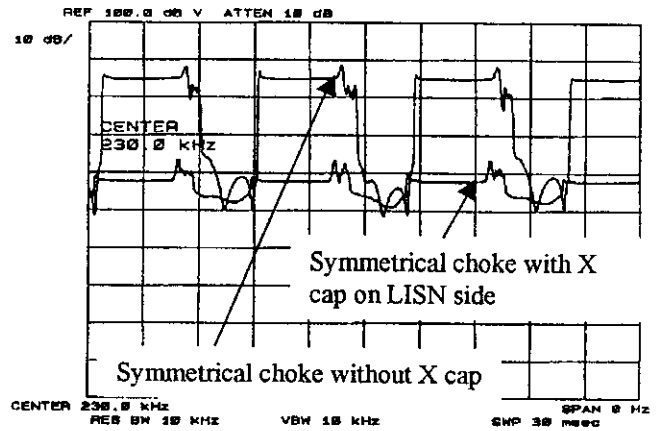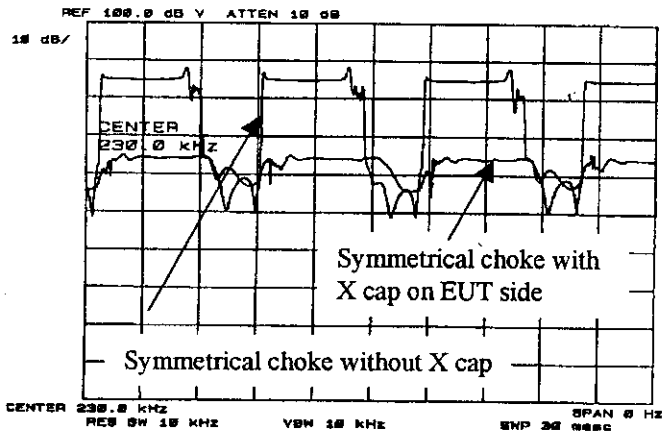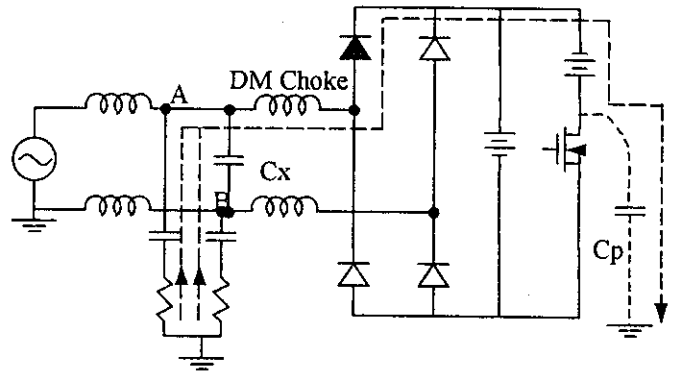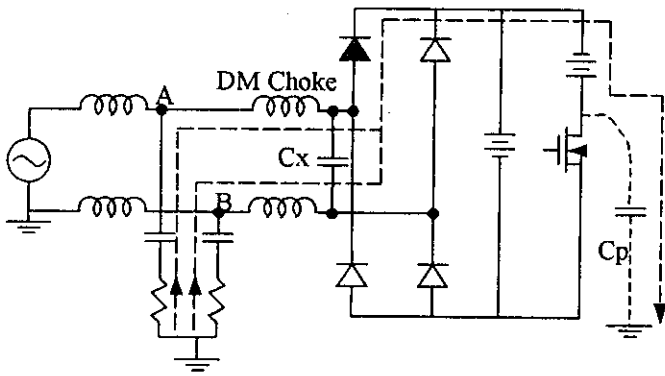


Effect of CM Choke on MM Noise

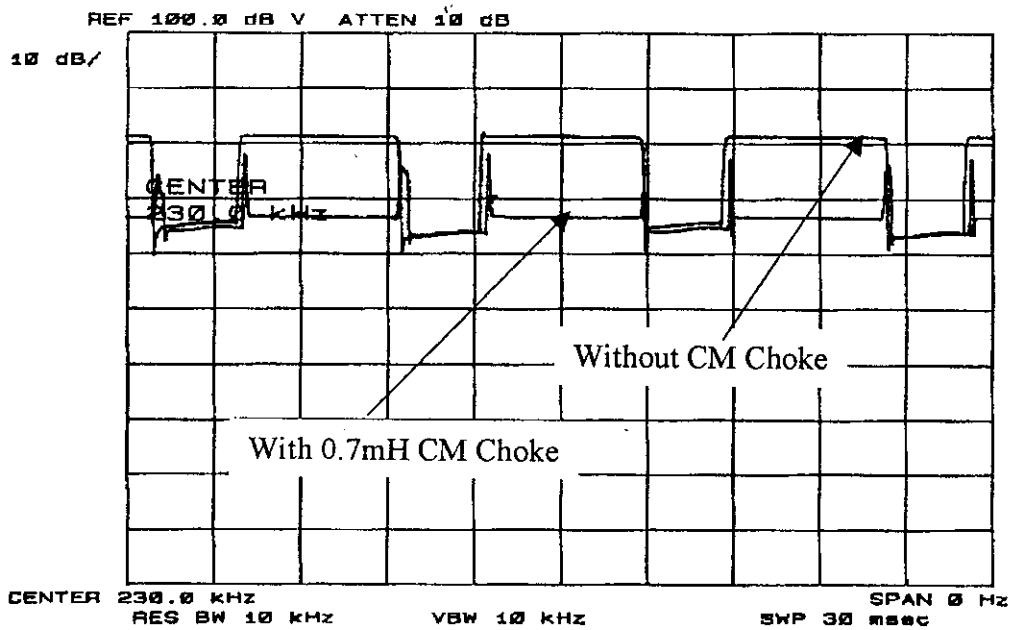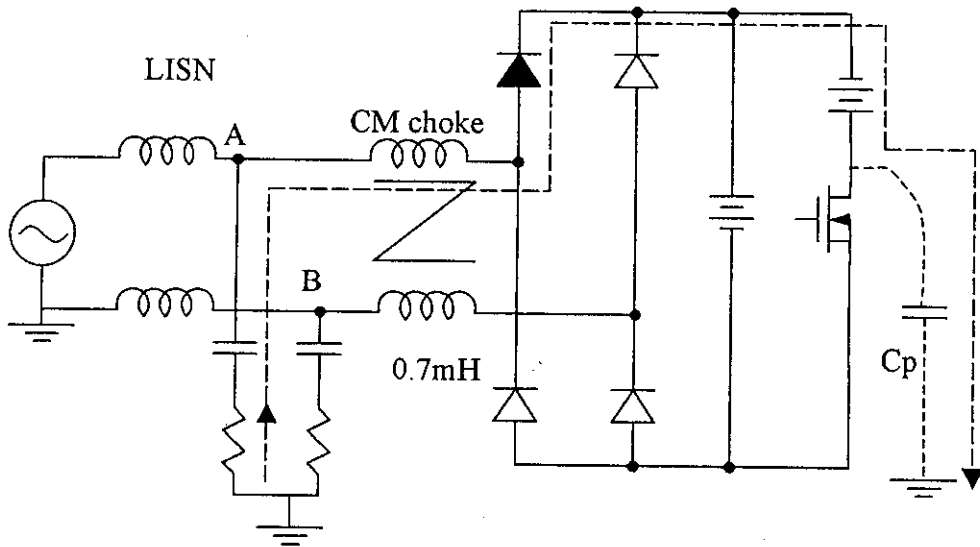

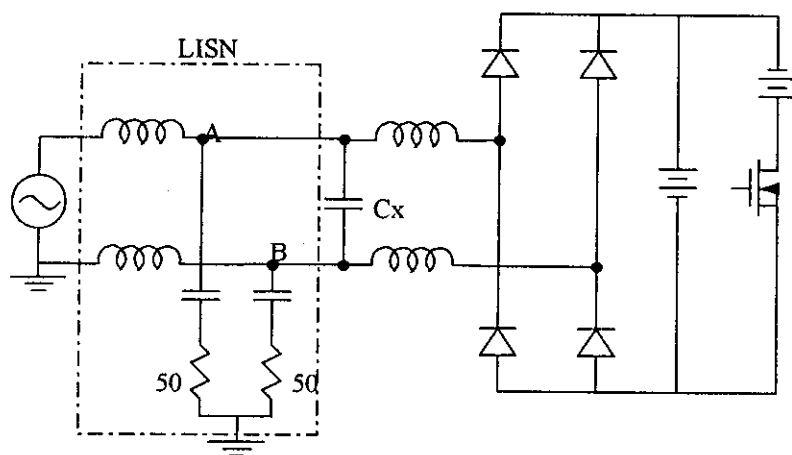
How Much C Is Needed to Balance the Current




$$\frac{1}{2\pi f C_x} \ll 50 \Omega$$

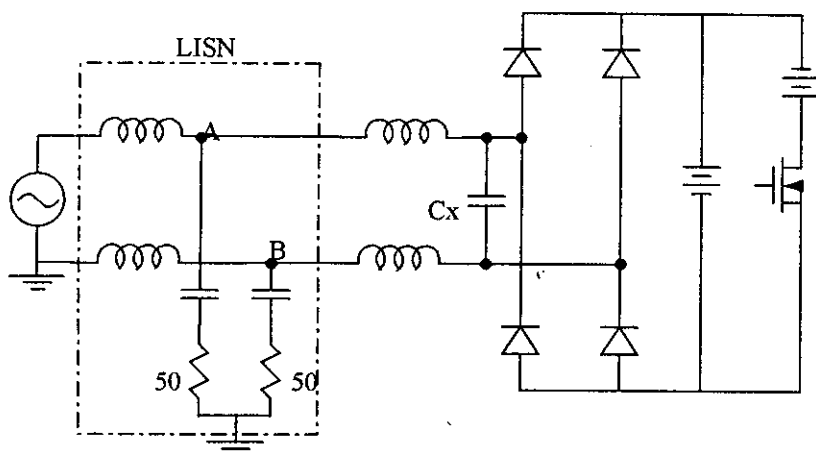

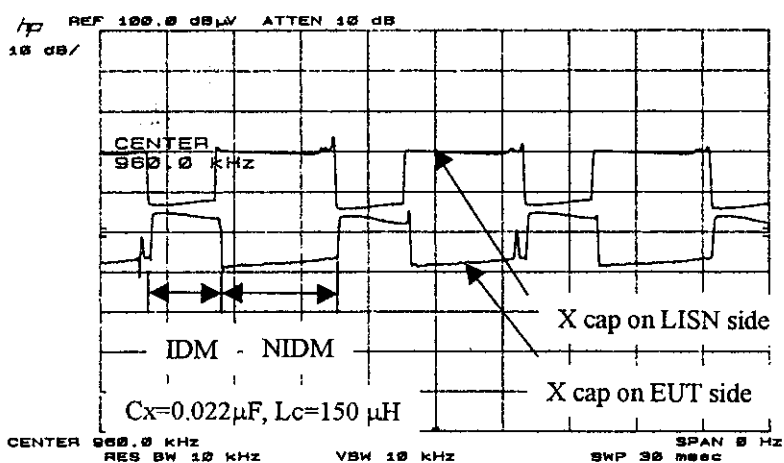
$$\frac{1}{2\pi f C_x} \ll \{50\Omega + j2\pi f(L_{DM} + L_{CM})\}$$




Impedance Effects on Filter Attenuation

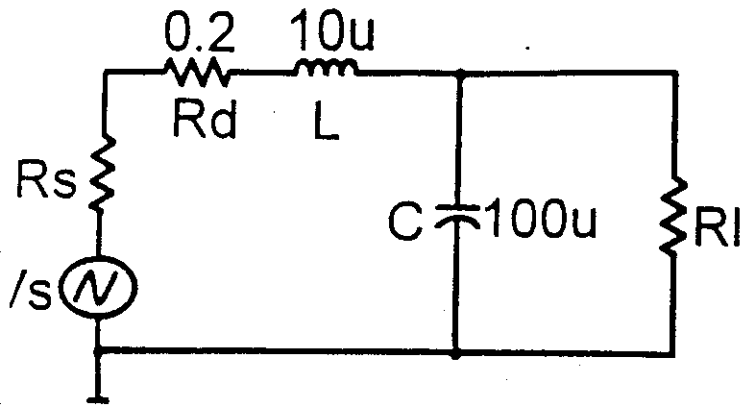


Filter Type A

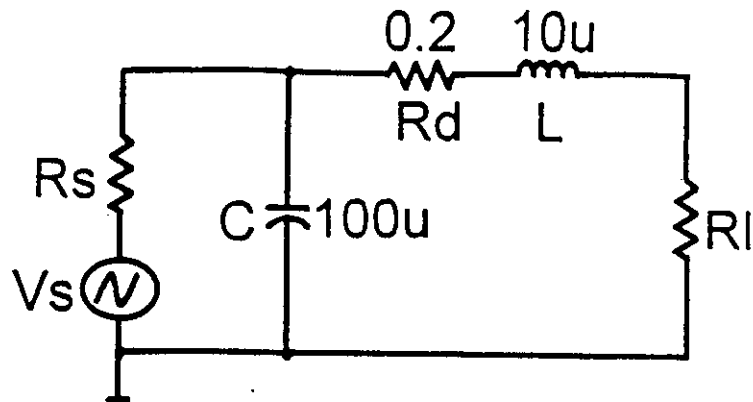


Filter Type B

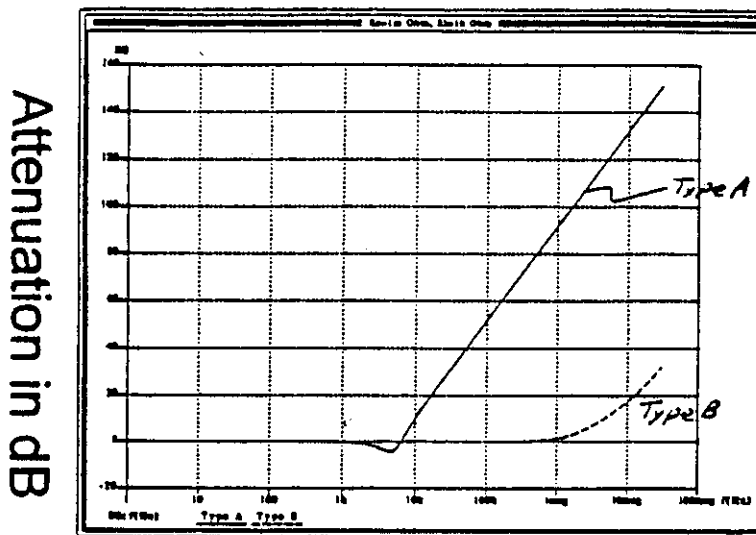

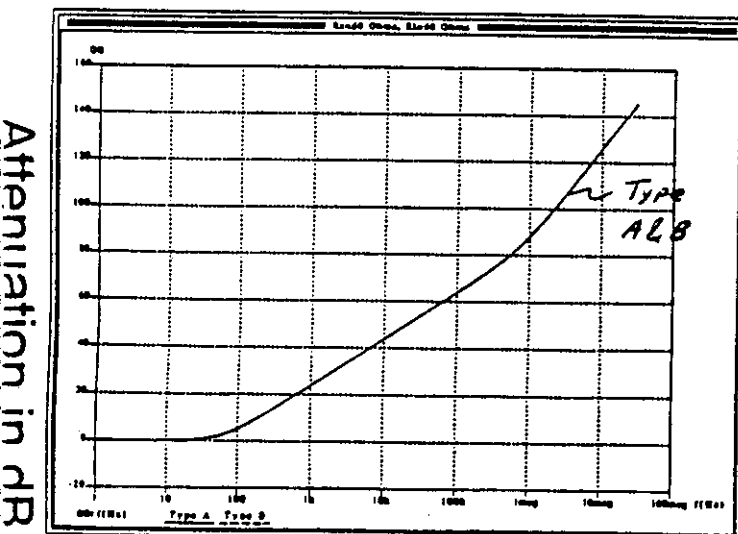Frequency in Hz
 $R_s=1\text{m Ohm}$, $R_l=1\text{K Ohm}$







Frequency in Hz
 $R_s=R_l=50\text{ Ohm}$

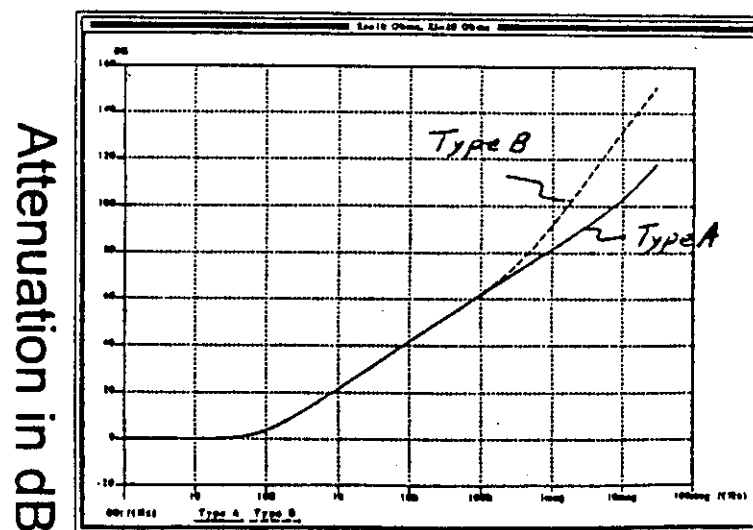





Frequency in Hz
 $R_s=1\text{K Ohm}$, $R_l=20\text{ Ohm}$

20




Effectiveness of a Filter

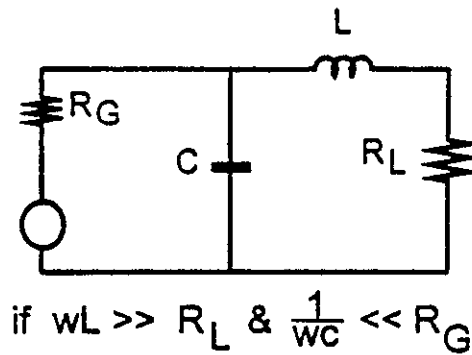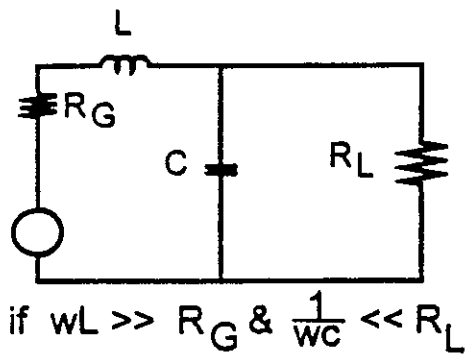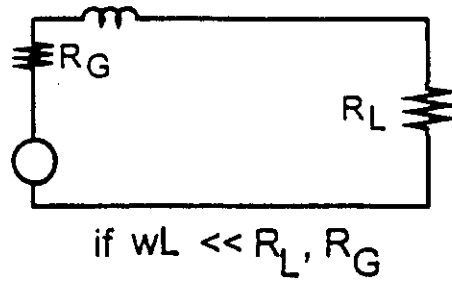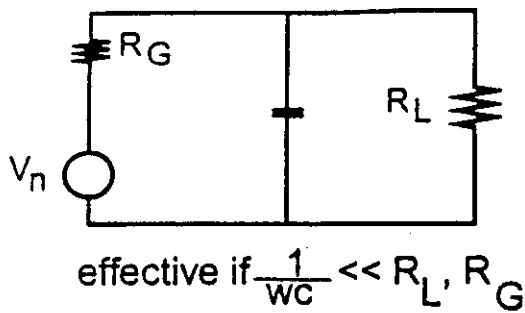

Higher-Order Filters

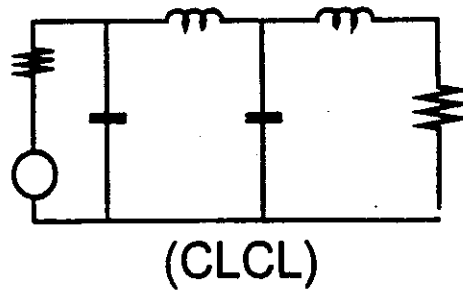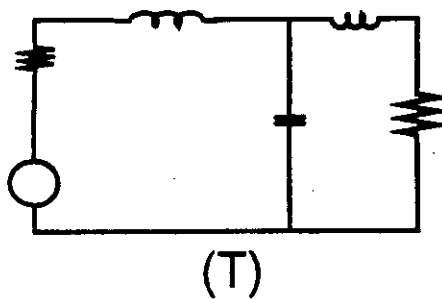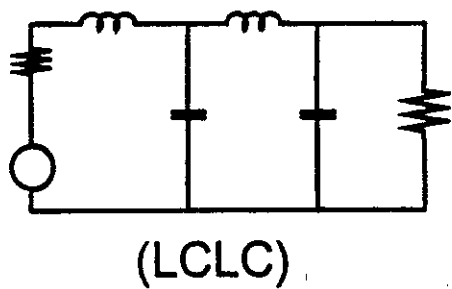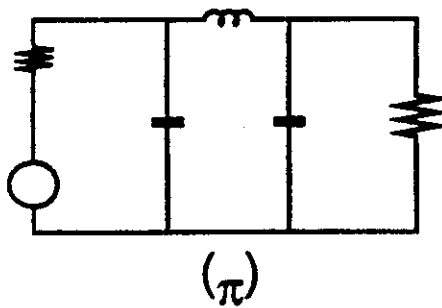

Noise Source Impedance

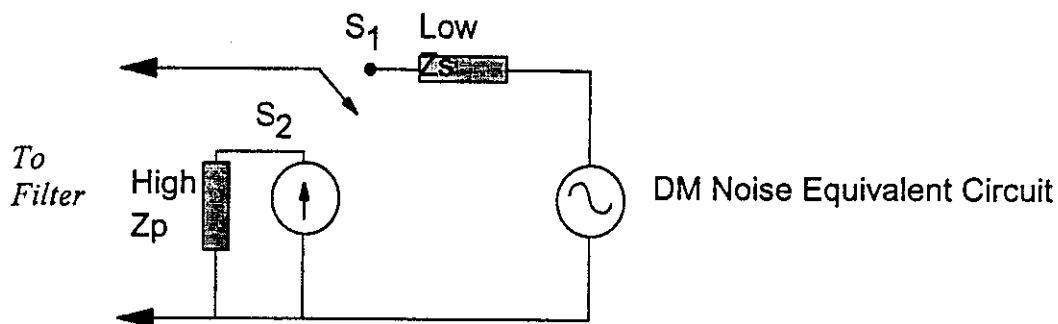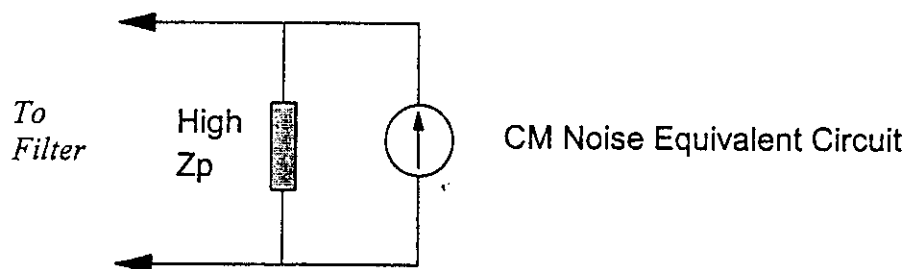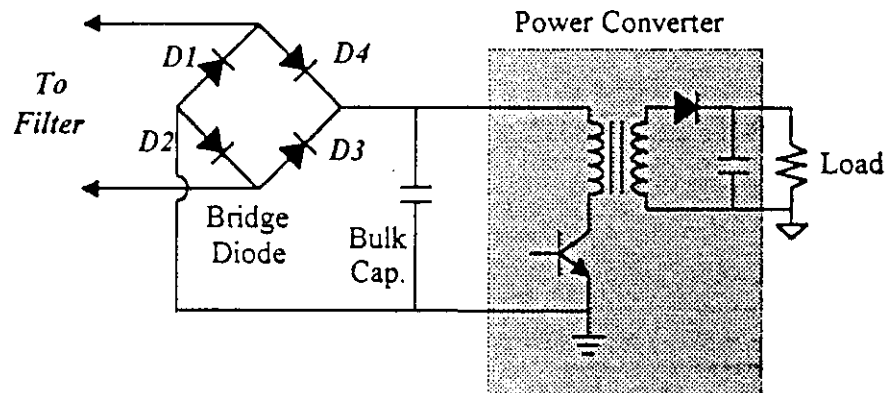


When rectifier diodes "on" \Rightarrow S_1 "on", S_2 "off"

When rectifier diodes "off" \Rightarrow S_1 "off", S_2 "on"

- Practically difficult to measure*


* Ref [2]

Experimental Source Impedance

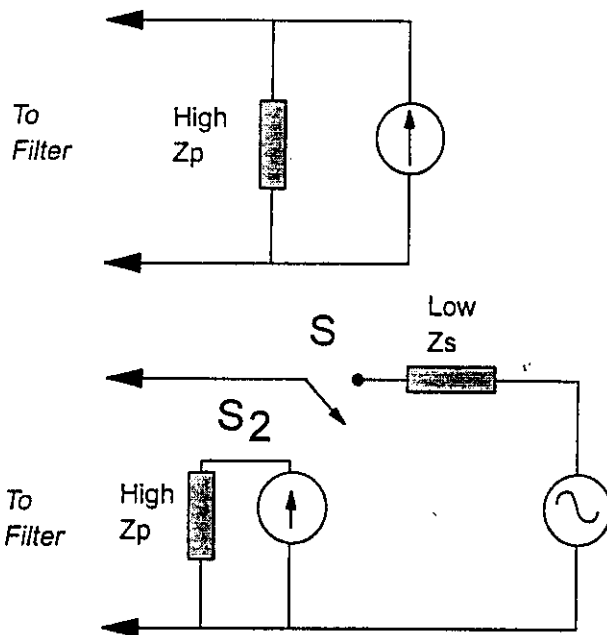


CM:

Z_p :

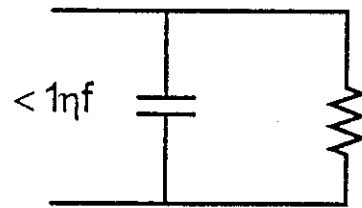


DM:

Z_s :

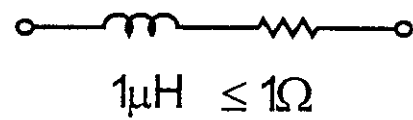




Z_p :

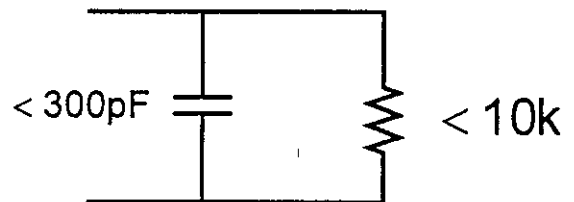



* For Power Supplies 50-500 Watts

*Ref [2], [3]

A Commonly-Used Filter Topology

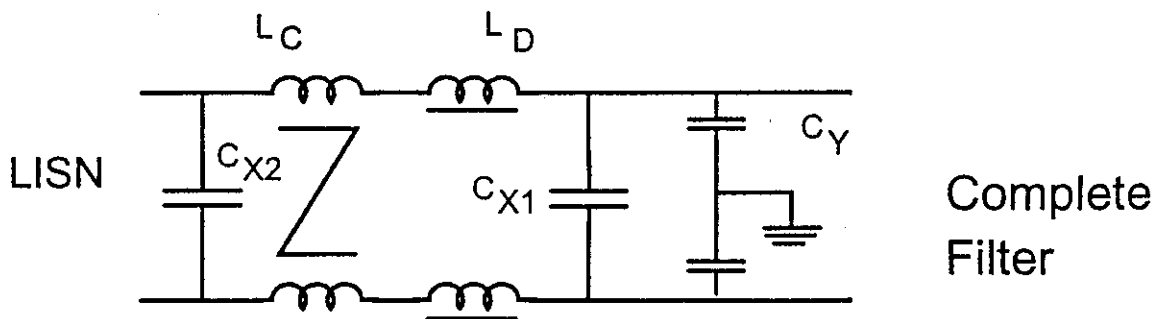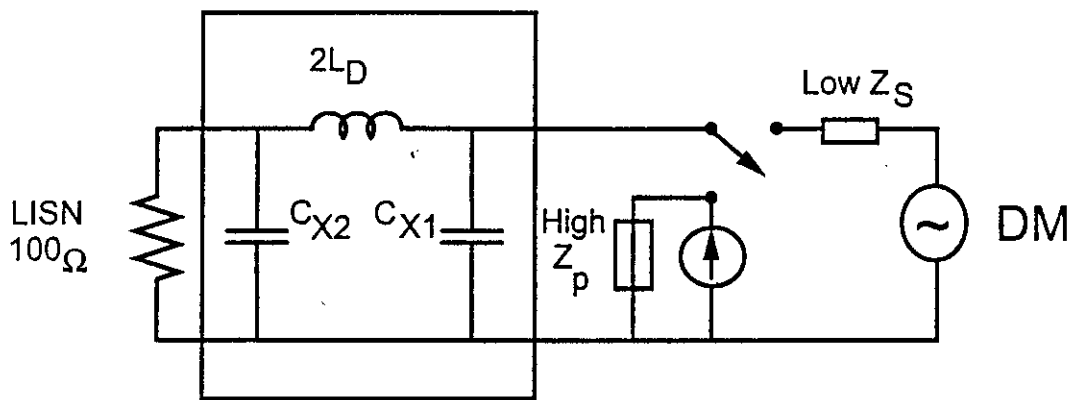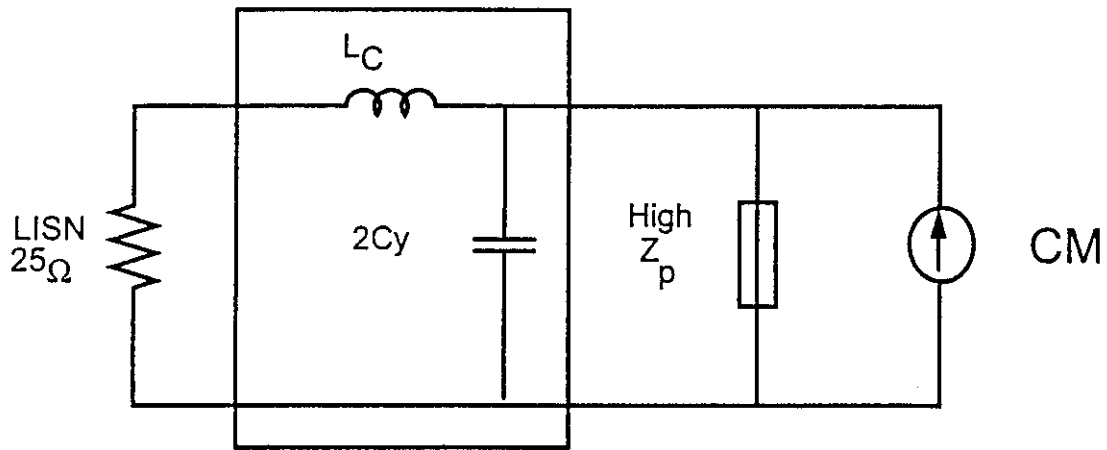

How to Place X Capacitor?

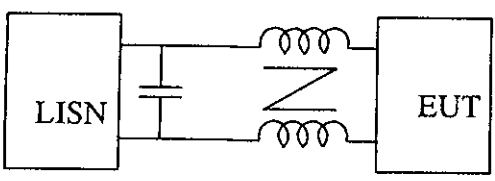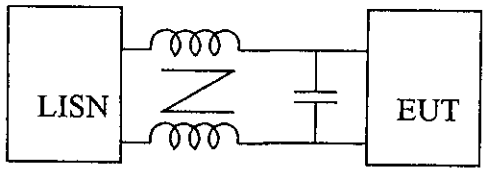	IDM	NIDM
 <p>The diagram shows a LISN block connected to a series combination of an X-capacitor, an L-match network (represented by two inductors and a capacitor), and an EUT block.</p>	More Effective	Less Effective
 <p>The diagram shows a LISN block connected to a series combination of an L-match network (represented by two inductors and a capacitor), an X-capacitor, and an EUT block.</p>	Less Effective	More Effective

Asymmetrical Filter Topology: X Cap is always on LISN side

Symmetrical Filter Topology: When IDM is dominant, X cap should be on LISN side;
When NIDM is dominant, X cap should be on EUT side.