

# Coupled Inductor Improves Cross Regulation in Multiple Output Forward Converters

Scott Deuty, ON Semiconductor Inc., Phoenix, Arizona  
C. S. Mitter, Semtech, Newbury Park, California

**M**ultiple output power converters suffer from cross regulation issues. This problem is present in ATX desktop power supplies where multiple output voltages of 5, 3.3, 12, -12, and -5 Vdc are required. Although all these outputs reference the same ground, cross regulation suffers from the fact that feedback control often references one output via an optocoupler for isolation. When a large load swing occurs on an output other than the sensed output, poor regulation can result. The coupled inductor is employed as a method of feeding back load swing information to the sensed winding to provide better regulation. The method for designing a coupled inductor for an ATX power supply can be applied to any multiple output forward converter.

## Basic Multiple Output Forward Converter

The basic, multiple output, forward converter for today's ATX computer supply is shown in *Figure 1*. Note that only one output, the 5Vdc output is sensed. When using separate inductors for each output, poor regulation results in other outputs. Poor regulation will be greatest in outputs with large load swings, especially the 3.3Vdc output that sees load currents of up to 10A at a slew rate of 30% of rated current at 2.5A/ $\mu$ sec<sup>[2]</sup>. The ATX must maintain a voltage above the minimum allowable 3.14Vdc during load swing situations. With separate

inductors in a standard multiple output design, the feedback would have to transmit from the 3.3Vdc output through the 3.3V inductor, to the 3.3V secondary and couple to the 5V secondary through the 5Vdc inductor and finally the feedback loop in order for the converter to respond. By forcing the information to propagate through the transformer and inductor, the 5Vdc output would not see as much of a voltage reduction nor would it see it as quickly as the 3.3Vdc output would. Therefore it is likely that the 3.3Vdc output would fall out of regulation unless a feedback method is introduced.

The purpose of coupled inductors is to relay current loading information directly through the inductor as shown

in *Figure 1*. The information is again relayed through magnetic coupling but not through the transformer like before, but through the inductor itself. Changes in load current will feedback to the 5V winding much faster and therefore the system will react quicker. Other benefits of the coupled inductor design are:

- One magnetic element for the coupled windings rather than one inductor per winding
- Reduced board space
- Confined areas of EMI generation
- Smaller output capacitors (if ripple currents are effectively steered)
- Reduced cost.

For all the coupled inductor design

**The coupled inductor design procedure involves basic transformer reflection analysis using turns ratios to reflect the loads to the sensed 5Vdc output. The resulting loads are normalized to the 5Vdc output in order to calculate relative parameters, such as desired ripple current and leakage inductance values.**

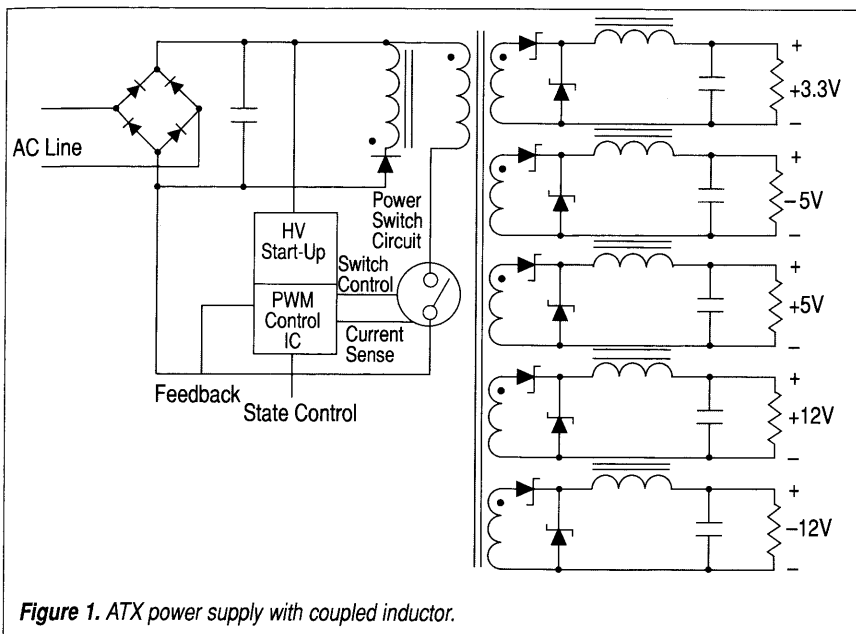


Figure 1. ATX power supply with coupled inductor.

benefits, there are some disadvantages. These include:

- Leakage inductance and its relation to ripple currents
- More difficult winding
- Confining the heat to one element rather than spreading it to several

inductors

- Somewhat difficult design calculations

### Coupled Inductor Design Basics

Before beginning design, it's best

to provide some basic rules. Further information can be found in<sup>[1]</sup>. These are the basic rules of design that must be remembered with coupled inductors:


1. The turns ratio of the inductor must match exactly the turns ratio of the transformer secondaries. This is the ratio between the output windings for the various outputs, not the ratio of the output winding to the primary.
2. It is best to steer the ripple current to the highest voltage winding as this winding usually has the largest allowable variation in output voltage. Therefore, the high voltage winding should have the lowest leakage inductance and be the closest winding to the inductor core.
3. For best results, reflect all of the windings to the feedback winding. With these rules in mind, one should revisit transformer theory prior to beginning the design. For this

## Need More Power *WITHOUT* More Space?

**CALL IXYS!** Our new PLUS247™ HiPerFETs™ offer the industry's LOWEST  $R_{DS(on)}$  in a TO-247 package outline. That's right—compare IXYS' "Best of Class" product specs below with any other manufacturer's TO-247 package outline FETs. We give you lower on-resistance and higher current ratings—more muscle in a small mounting area. From 70V to 1000V, they're the designer's choice for switching power conversion circuits!
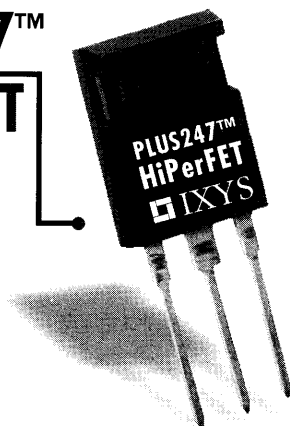
### PLUS247™ HiPerFET

**IXYS Corporation**  
3540 Bassett Street  
Santa Clara, CA 95054  
CALL! (408) 982-0700  
FAX! (408) 496-0670  
IN EUROPE:  
IXYS Semiconductor, GmbH  
CALL! +49.6206.5030  
FAX +49.6206.503.627  
www.ixys.com



PART TYPE	$V_{DS}$	$I_{D25}$	$R_{DS(on)}$ (max)	$t_{rr}$ (max)
IXFX180N07	70V	180A	0.005Ω	250ns
IXFX180N10	100V	180A	0.008Ω	250ns
IXFX120N20	200V	120A	0.017Ω	250ns
IXFX90N30	300V	90A	0.033Ω	250ns
IXFX55N50	500V	55A	0.080Ω	250ns
IXFX44N60	600V	44A	0.130Ω	250ns
IXFX34N80	800V	34A	0.240Ω	250ns
IXFX26N90	900V	26A	0.330Ω	250ns
IXFX24N100	1000V	24A	0.400Ω	250ns

• Also available...TO-264 and SOT-227 versions

**SMALL PACKAGE...BIG POWER...THINK IXYS!**

**IXYS...POWERING THE 21<sup>ST</sup> CENTURY<sup>SM</sup>**

## Coupled Inductors

example we will refer to the feedback or main winding with a subscript of M and the subordinate winding with a subscript of R. Equations reference *Figure 2*.

The basic transformer voltage equation is:

$$\frac{V_M}{N_M} = \frac{V_R}{N_R} \quad (1)$$

From this we can calculate the voltage reflected to main winding M:

$$V_M = \frac{V_R}{N_R} \times N_M \quad (2)$$

Similarly, from the basic transformer current equation:

$$I_M \times N_M = I_R \times N_R \quad (3)$$

We can calculate the current reflected to main winding, M:

$$I_M = \frac{I_R \times N_R}{N_M} \quad (4)$$

These equations will be helpful in calculating voltage and current. How-

ever, to calculate inductors, capacitors, and resistances, use the impedance relationship. Impedance viewed from the main winding M is:


$$Z_M = \frac{V_M}{I_M} \quad (5)$$

By substituting the reflected voltage and current equations developed earlier, the reflected impedance can be found to be:

$$\begin{aligned} Z'_R &= \frac{V_M}{I_M} = \frac{V_R \times N_M}{I_R \times N_R} \quad (6) \\ &= \frac{V_R}{I_R} \times \left( \frac{N_M}{N_R} \right)^2 = Z_R \times \left( \frac{N_M}{N_R} \right)^2 = Z'_R \end{aligned}$$

Often, the exact turns of the transformer are not known until the transformer is designed. However, the actual design can proceed if the turns ratio is substituted where the turns ratio, TR, is:

$$TR = \frac{N_M}{N_R} \quad (7)$$

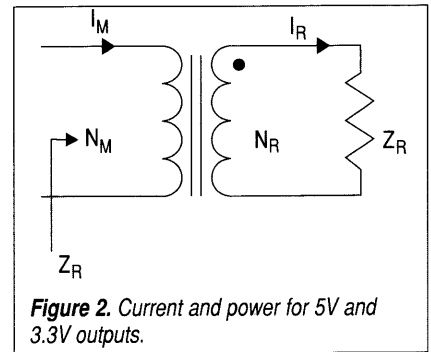

**Figure 2.** Current and power for 5V and 3.3V outputs.


Transformer theory provides the following rules:

1. The voltage reflected to the main winding, M, is the voltage from the reflected winding, R, multiplied by the turns ratio TR. (Voltage is multiplied by TR.)
2. The current reflected to the main winding, M, is the current from the reflected winding, R, divided by the turns ratio, TR. (Current is divided by TR.)
3. The impedance reflected to the main winding, M, is the impedance from the reflected winding,

# INTEGRATED INDUCTIVE COMPONENT
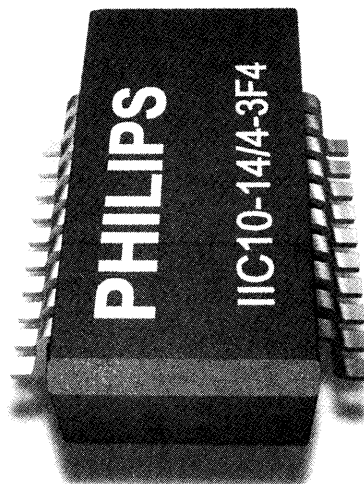
## A New Concept for Inductors, Transformers and Chokes from Philips

Introducing the inductive SMD component that looks like a standard IC outline (SOT). The IIC can be automatically placed and soldered together with other IC's on the board. It is also suitable for reflow soldering. Windings are completed by PCB tracks. A wide range of magnetic functions can be realized with the same product, depending on track layout.



**ELNA**  
FERRITE  
TECHNOLOGIES

### IIC With Partial Airgap

Improves energy storage:

- POWER INDUCTOR
- OUTPUT CHOKE
- EMI-CHOKE WITH BIAS

### IIC Without Partial Airgap

Suitable for:

- POWER TRANSFORMER
- SIGNAL TRANSFORMER
- COMMON-MODE CHOKE

Ask Elna for the IIC technical note "IIC" and the application note "10 Watt DC/DC Converter using IIC." Then let us know which free samples you need for evaluation. Elna stocks the complete range of Philips Magnetic Products.

P.O. Box 395, 234 Tinker Street Woodstock, NY 12498 • (800) 553-2870 • FAX: (914) 679-7010

E-MAIL ferrite@ulster.net INTERNET www.elna-ferrite.com

Variable	Value
Estimated max rectified Input Vinmax=	407
Estimated min rectified input Vinmin=	240
Dmax=	0.51
Np/N5 = TR5p=	22.35
(Vo5+vSchott)*TR5p/Vinmax = DminNew=	0.30
(Vo5+vSchott)*TR5p/Vinnom = DminNom=	0.36
Np/N33 = TR33p=	32.34
Np/N12 = TR12p=	9.83
Np/NN12 = TRN12p=	9.83


**Table 1.** ATX power converter main parameters and turns ratio.

R, multiplied by the turns ratio, TR *squared*. (Impedance is multiplied by TR *squared*.)

These basic equations will assist in the design of the coupled inductor as well as its associated output parameters.

## Coupled Inductor Design Details

Detailed design of the coupled inductor assumes that the transformer turns ratios have already been calculated. Then the duty cycle range is predicted over all input line voltages.

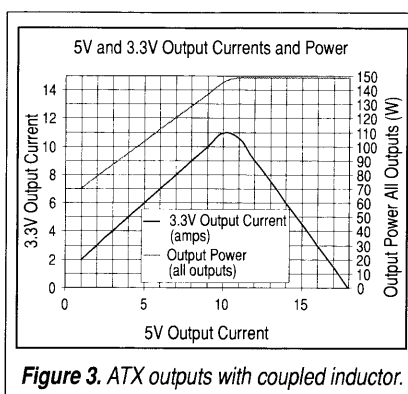

**Figure 3.** ATX outputs with coupled inductor.

Max Current (amps)	Max Current Variable Names	Min Output Current (amps)	Min Current Variable Names	Output Voltage (VDC)	Output Ripple (Vp-p)	Output Range (%)	Minimum Output Voltage (VDC)	Maximum Output Voltage (VDC)
18	I5max	1	I5min	5	0.05	0.05	4.75	5.25
10	I33max	0.3	I33min	3.3	0.05	0.05	3.135	3.465
4.5	I12max	0	I12min	12	0.12	0.05	11.4	12.6
0.3	IN12max	0	IN12min	-12	0.12	0.1	-10.8	-13.2
0.3	IN5max	0	IN5min	-5	0.05	0.1	-4.5	-5.5

**Table 2.** ATX specification for a 140W converter.


Using the computation method described here results in the turns ratio values shown in *Table 1*.

Note that the calculations are from an EXCEL program and therefore are in EXCEL equation format. The specifications used for the 140W converter are shown in *Table 2*.

Also note that the combined power for the 5Vdc and 3.3Vdc outputs cannot exceed 90W as illustrated in *Figure 3*. The core energy calculation uses the maximum value of 90W, however, the windings must be calculated to

# LOOKING FOR INTEGRATED IGBT POWER MODULE SOLUTIONS?

## Converter Brake Inverter IGBT Modules

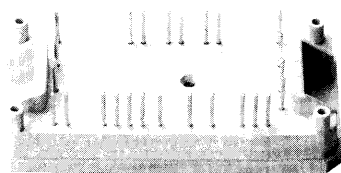

Call IXYS! Our new low-profile, CBI modules combine three popular motor drive building blocks in one easy to use package—3 phase rectifier converter, braking IGBT/Diode, and 3 phase IGBT/Diode inverter. We've even included a thermistor for thermal measurement and protection. They're the reliable and economical approach for motor drive design!

**IXYS Corporation**  
 3540 Bassett Street  
 Santa Clara, CA 95054  
 CALL! (408) 982-0700  
 FAX! (408) 496-0670  
 IN EUROPE:  
 IXYS Semiconductor, GmbH  
 CALL! +49.6206.5030  
 FAX +49.6206.503.627

	PART NUMBER	3~ Rectifier		Brake Chopper		3~ Inverter	
		VRRM (V)	IFAVM (A)	VCES (V)	Ic90 (A)	VCES (V)	Ic90 (A)
600 V	MUBW6-06A6	1200	11	600	7	600	4.5
	MUBW10-06A6	1200	11	600	11	600	8
	MUBW15-06A6	1200	11	600	11	600	10
	MUBW20-06A6	1200	11	600	11	600	13
	MUBW25-06A6	1200	11	600	18	600	16
	MUBW35-06A6	1200	25	600	23	600	25
1200 V	MUBW4-12A6	1600	11	1200	2.5	1200	2.4
	MUBW10-12A6	1600	11	1200	2.5	1200	8
	MUBW15-12A6	1600	25	1200	8	1200	11.5
	MUBW30-12A6	1600	25	1200	9	1200	17

Data Sheets at [www.ixys.com](http://www.ixys.com)

**IXYS...INNOVATIONS FOR THE 21<sup>ST</sup> CENTURY<sup>SM</sup>**

## Coupled Inductors

handle the maximum current each output will see. The information in the table allows us to determine the maximum current a winding will see or determine the amount of current on the 5Vdc output based on the output current on the 3.3Vdc output.

The inductance of L5 is chosen using the EXCEL formula:  
 $L5fin = ((1 - D_{min}) * T * (V_{o5} + v_{Schott})) / (I_{ndPctMaxIo} * I5max)$  (8)

Where the switching frequency,  $f = 100\text{kHz}$  and therefore  $T = 10$  (sec).

Now that the inductance value of the 5Vdc output is known from earlier calculations, inductance values for the other outputs are calculated using the turns ratio impedance principle developed earlier. Figures 4, 5, and 6 show how the windings reflected to the 5V winding. The prime symbol (') on the reflected windings means these windings have been normalized to the 5V winding. In this case, normalized means multiplied by the output turns

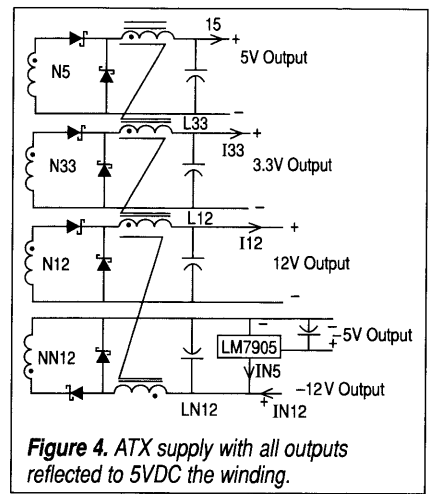



Figure 4. ATX supply with all outputs reflected to 5VDC the winding.

Variable	Inductance Formula Using Transformer Turns Ratios	Inductance ( $\mu\text{H}$ )	Leakage Percentage of Main Inductance (%)	Leakage Inductance (H)	Leakage Inductance ( $\mu\text{H}$ )	Leakage Inductance (Normalized to 5V) (H)	Equation Used in Normalizing Leakage Inductance to 5 VDC Winding
		L		lk	lk	lk'	
L5fin		29.0	20%	5.79E-06	5.790	5.79E-06	
L33fin	$=L5fin * (TR33p/TR5p)^2$	60.6	25%	1.516E-05	15.162	7.238E-06	$lk33' = lk33 / (TR33p/TR5p)^2$
L12fin	$=L5fin * (TR12p/TR5p)^2$	5.6	2%	5.79E-07	0.579	2.991E-06	$lk12' = lk12 / (TR12p/TR5p)^2$
LN12fin	$=L5fin * (TRN12p/TR5p)^2$	5.6	10%	0.000005	5.000	2.583E-05	$lkN12' = lkN12 / (TRN12p/TR5p)^2$

Table 3. Leakage inductance values; actual and reflected (normalized).
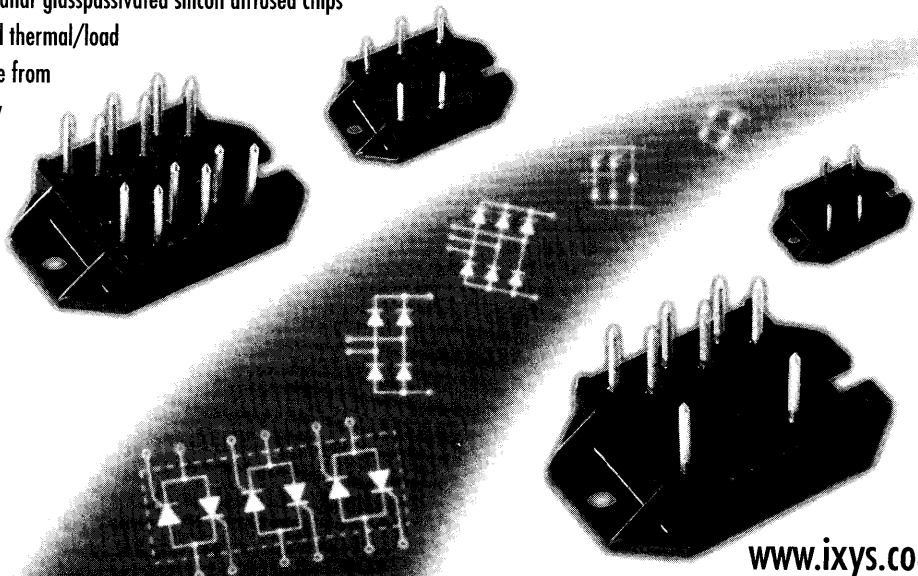
## ECO-PAC™ — a new package for Power Semiconductors

ECO-PAC™ offers the widest choice of diode, thyristor, and FRED circuit configurations in a low profile (9mm high), easy to mount package. This new package design provides isolation voltages of over 3600 VAC RMS, allows optimum heat transfer direct to the heat sink, and is suitable for soldering on to a printed circuit board. IXYS DCB technology and planar glasspassivated silicon diffused chips provide excellent long term reliability and thermal/load cycling capability. ECO-PAC products range from 600 to 1600 V, 20 to 80 A and can easily replace up to 6 discrete devices. Simplify your power circuits today with the ECO-PAC from IXYS.



**IXYS Corporation**

3540 Bassett Street  
 Santa Clara, CA 95054  
 CALL! (408) 982-0700  
 FAX! (408) 496-0670  
 IN EUROPE:  
 IXYS Semiconductor, GmbH  
 CALL! +49.6206.5030  
 FAX! +49.6206.503.627

www.ixys.com

**IXYS... POWERING THE 21<sup>ST</sup> CENTURY<sup>SM</sup>**


CIRCLE 225 or www.1rs.com/912pm-225

## Coupled Inductors


ratios. Note from *Figures 4, 5* and *6* that the  $-5\text{Vdc}$  output goes through a post regulator via the  $-12\text{Vdc}$  output. The  $-5\text{Vdc}$  output current is added to the  $-12\text{Vdc}$  output current for accuracy.

*Table 4* shows the calculated inductance values as well as the EXCEL formulas used to find them. Note that a column of data titled "leakage inductance percentage of main inductance" is shown. These values were used to predict ripple currents in the


final design so that minimum capacitor values could be calculated. The lowest percentage shown is 2% for the highest voltage winding. It was established earlier that the ripple current would be steered to this winding and therefore, it should have the lowest leakage. This provides the magnetics designer with some flexibility in designing the inductor and orienting windings for leakage. The ripple steering inductance will be determined in breadboard experimentation, and this ripple steering induc-

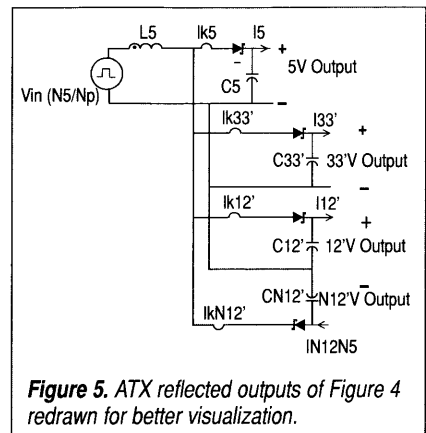

**Figure 5.** ATX reflected outputs of Figure 4 redrawn for better visualization.

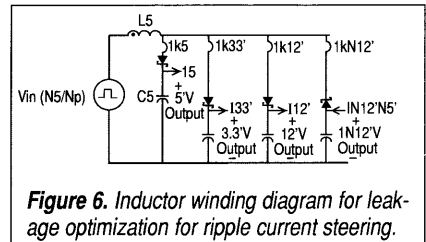

**Figure 6.** Inductor winding diagram for leakage optimization for ripple current steering.

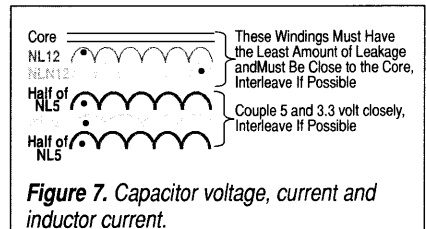

**Figure 7.** Capacitor voltage, current and inductor current.


tance could be a combination of the leakage inductance and an external series inductor. Similarly, the final output capacitance value will be a combination of available values, holdup time specifications, and final filtering of the output.

Based on the inductor calculations, the winding current and therefore wire size can be determined. This information is in *Table 5* (which was given to the magnetics design house).

More information needs to be given to the inductor designer in order to choose the proper core. The currents in all windings are reflected to the 5V winding. The reflected current squared is then multiplied by the inductance value, as shown in the *Table 6*.

Finally, for the purposes of steering the ripple current to the high voltage winding, a winding diagram is presented in *Figure 7*. The 12 VDC (NL12) winding will get most of the

# Ultra-Low ESR Capacitors

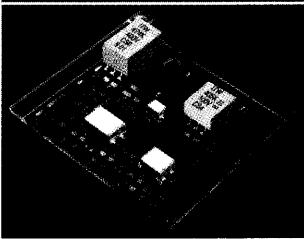

**Chips Are Not Ceramic**

**Now Available in Shell or Epoxy Enclosure**

0.33 $\mu\text{F}$  to 20.0 $\mu\text{F}$ ; 50 to 500 volts

## Multilayer Polymer Film (MLP) Capacitors

- Ultra-Low ESR & ESR
- Self-cleaning - does not fail short
- Stable under AC and DC voltages no capacitance fall-off
- Telecom grade - long life/no aging
- 0.33 $\mu\text{F}$  to 20.0 $\mu\text{F}$ ; 50 to 500 volts
- SMD packages for reflow soldering
- Excellent TCE match on FR4 boards
- Avoids cracking problems

TYPICAL 500Vdc RIPPLE CURRENT

VALUE $\mu\text{F}$	Irms AMPS
1.0	3.6
2.2	5.2
4.0	11.5
10.0	15.3

**TWPaktron**  
FILM CAPACITORS

*An integral part of tomorrow's technology*

P.O. Box 4539; 1205 McConville Rd., Lynchburg, VA 24502

804-239-6941 • FAX: 804-239-4730

<http://www.paktron.com>

Available through these distributors:

- ATLANTIC COMPONENTS (1-800-433-6600) • FUTURE (1-800-388-8731) •
- GOPHER (1-800-592-9519) • KENT (1-800-422-8005) • MALLORY (1-317-273-2424) •

CIRCLE 226 or [www.1rs.com/912pm-226](http://www.1rs.com/912pm-226)

## Coupled Inductors

ripple current and must have the lowest leakage inductance and therefore be located closest to the core. The negative 12Vdc output (NLN12) is located next and finally the high current 5Vdc and 3.3Vdc windings are interleaved for close coupling and better regulation.

### References

1. "Coupled Filter Inductors in Multiple Output Buck Regulators

Provide Dramatic Performance Improvement," author not listed, page M7-1, Unitrode Power Supply Design Seminar SEM 800, Unitrode Semiconductor Products Division, Unitrode Corporation, 7 Continental Boulevard, P.O. Box 399, Merrimack, NH 03054, <http://www.unitrode.com> TEL: 603-424-2410 FAX: 603-424-3460

2. *Intel ATX Power Supply Design Guide*, Version 0.9 Intel Corporation
3. ATX 5Vdc and 3.3Vdc Output




Current – Maximum Values Based On 90W

4. ATX Outputs with Coupled Inductor
5. ATX Supply with all Outputs Reflected to 5VDC the Winding
6. ATX Reflected Outputs of *Figure 4* Redrawn for Better Visualization
7. Inductor Winding Diagram for Leakage Optimization for Ripple Current Steering
8. Capacitor charge balance timing diagram

## The World's Best Kept Secret
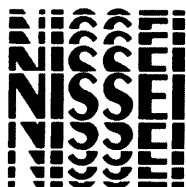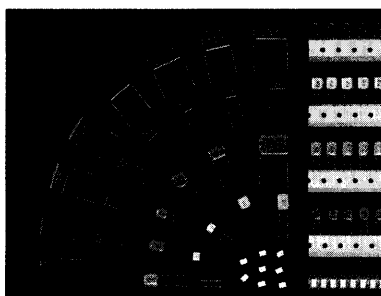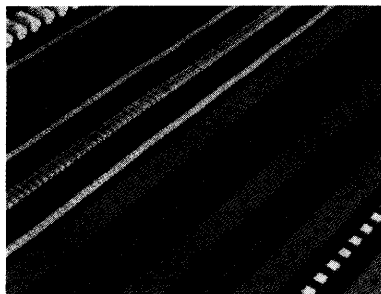
# Your Best Place To Call for any film capacitor needs.

Domestic warehousing and distribution means this international company can deliver anywhere, anytime.



**NISSEI ARCOTRONICS**  
FILM CAPACITORS

7873 S.W. Nimbus Ave., Beaverton, OR 97008  
503-646-1434 • FAX 503-641-9594  
Visit our web site at: [www.nissei-arco.com](http://www.nissei-arco.com)

#### Nissei Arcotronics Distributors:

Arizona Components  
AtCom  
California Capacitors  
E.W. Electronics

Future/FAI Electronics  
NEP Electronics  
Pridmore Electronics

Priebe Electronics  
Schuten Electronics  
U.S. Electronics

### APPENDIX: Capacitor Value Calculation Method

For the capacitor, the charge must be balanced. As shown in *Figure 8*, the shaded areas must be equal in area. The voltage across the capacitance is expressed in terms of this triangular area. The area product of current versus time is equivalent to the integral expression of the equation:

$$\int_{t_1}^{t_2} i_C \times dt = (\text{shaded area}) \quad (9)$$

Where  $i_C$  = Capacitor current

The voltage across the capacitance is:

$$\Delta V_{oc} = \frac{1}{C} \times (\text{area}) \quad (10)$$

The new expression becomes:

$$\Delta V_{oc} = \frac{1}{C} \times \frac{1}{2} \times \frac{1}{2} \Delta i_L \times \frac{1}{2} T_s \quad (11)$$

Where  $D'$  = Duty cycle and  $T_s$  = SMPS Switching Period

Where  $i_L$  = Inductor current

The peak-to-peak inductor current is:

$$\Delta i_L = \frac{V_o}{L} D' \times T_s \quad (12)$$

Time (dt) is:

$$t_2 - t_1 = \frac{1}{2} T_s \quad (13)$$

The final expressions for the ripple voltage due to capacitance is:

$$\Delta V_{oc} = \frac{1}{8} \times \frac{V_o}{LC} \times D' \times T_s^2 \quad (14)$$


The final expressions for the total output ripple voltage is :

# Apex Microtechnology


PWM Amplifiers • Power Amplifiers • DC-DC Converters
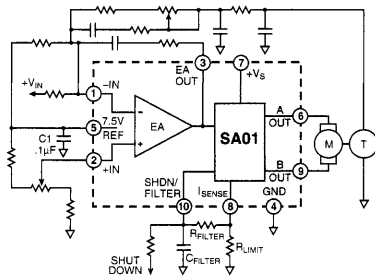
## High-Reliability Hybrid PWM "Switching" Amplifiers

Up To 97% Efficient,  
High Voltage Up To 500V,  
High Current 5A Up To 30A,  
Power Delivery Up To 10K Watts



SA01 Motor Driver with Tach Feedback

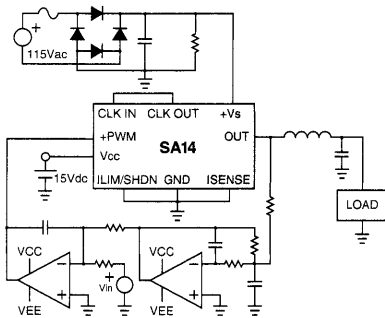

SA14 Transformer-less AC/DC Converter

### Find it Here

[www.apexmicrotech.com/see/pcim](http://www.apexmicrotech.com/see/pcim)

- Parametric Product Search Engine
- Product Data Sheets
- Computer-Aided Power Design Tool
- Sample Circuit Center
- Request Free CD-ROM or Data Book

### Free CD-ROM or Data Book

Call: 1-800-862-1020

E-Mail: [prodlit@apexmicrotech.com](mailto:prodlit@apexmicrotech.com)

Fax: 520-888-3329



5980 N. Shannon Road, Tucson, AZ 85741-5230

[www.apexmicrotech.com/see/pcim](http://www.apexmicrotech.com/see/pcim)

## Coupled Inductors

$$\Delta V_o = i_c \times R_c + \frac{1}{8} \times \frac{V_o}{LC} \times D' \times T_s^2 \quad (15)$$

Where  $R_c$  = Capacitor ESR

By using the leakage calculated for each winding to predict the ripple steered to or from that winding along with the established capacitor equations, the capacitor values can be found. The calculated capacitor values are illustrated in the *Table 6*. The low ripple currents that result from the ripple steering produces low capacitor values and favorable ESR values. Final capacitor values will be much higher and LC filtering on the output will filter some of the ripple voltage that will occur across the ESR of the large capacitors.

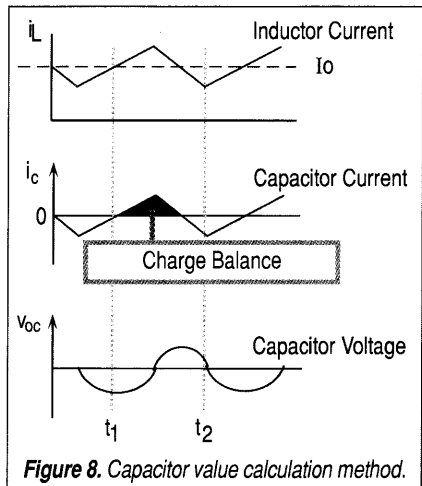


Figure 8. Capacitor value calculation method.

For more information about the products or services covered in this article, please use the reader service inquiry card and... **CIRCLE 351**

E-mail questions and comments to [editor@pcim.com](mailto:editor@pcim.com)

Output Voltage of Converter (VDC)	Winding Label	Max Inductor Current (ADC)	Inductance (µH)	Turns Ratio (winding/5V)	Leakage Inductance (µH)	Comments
5	NL5	18	29.0	1.0	5.8	Leakage Can Be High for Ripple Steering But Coupling to 3.3 volt winding must be close
3.3	NL33	10	60.6	1.4	15.2	Leakage Can Be High for Ripple Steering But Coupling to 5 volt winding must be close
12	NL12	4.5	5.6	0.4	0.6	Need Lowest Leakage for Ripple Steering
-12	NLN12	0.6	5.6	0.4	5.0	Need Second Lowest Leakage for Ripple Steering

Table 4. Inductor values and parameters used to determine inductor windings.

L5	DC Current Reflected to 5V Winding (A)	DC Current In Reflected 5 volt Winding (Amps)	Inductor LI Squared Calculation
2.9E-05	34.71768	$=I5_{max} + I33_{max} \times (TR33p/TR5p) + I12_{max} \times (TR12p/TR5p) + (IN12_{max} + IN5_{max}) \times (TRN12p/TR5p)$	0.0348956

Table 5. Total inductor current reflected to the 5 VDC winding (used to determine core power).

Output Voltage of Converter (VDC)	Normalized Ripple Steered by Leakage Inductance (A p-p)	Actual Ripple Steered by Leakage Inductance (A p-p)	$C_{o(min)}$ (F)	Capacitor Calculation Equations	$C_{o(min)}$ µF	ESR max (ohms)
5	0.404	0.404	1.01E-05	$=iripple5/(8 \times V_o5ripl)$	10.1	0.12
3.3	0.323	0.467	1.17E-05	$=iripple33/(8 \times V_o33ripl)$	11.7	0.11
12	0.781	0.344	3.58E-06	$=iripple12/(8 \times V_o12ripl)$	3.6	0.35
-12	0.090	0.040	4.15E-07	$=irippleN12/(8 \times V_oN12ripl)$	0.4	3.01

Table 6. Calculated capacitor values.