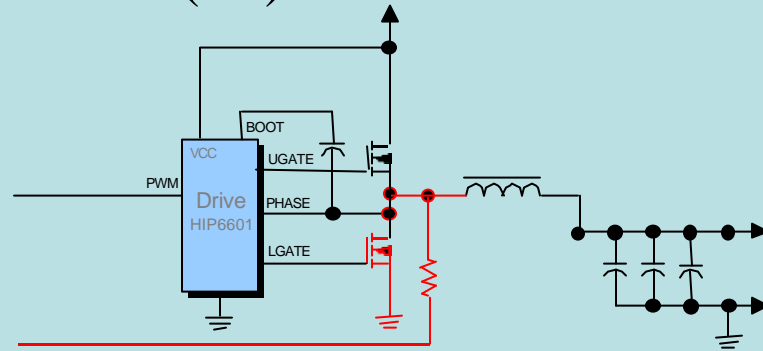



Rds(on) and DCR sense

Rds(on)



- Over 2 Years in Market
- High Reliability and Excellent Stability
- Controllable for Multi-Source FETs
- Friendly Layout and Seamless Copy
- **Need Temperature Compensation**

DCR


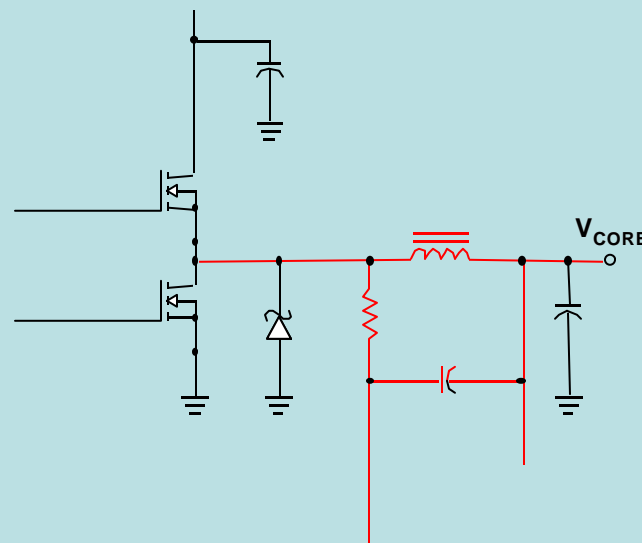


- Sensitive to Layout
- Not Proven in Very High Volume
- Not Easy Model to Model Copy
- RC Filter Produces one Pole
- **RC and L/DCR Mis-matching Issue**
- **Need Temperature Compensation**

Current Sensing Via Intrinsic Elements

- **Inductor DCR**
 - **Initial Accuracy » 10%**
 - Wire Length and Diameter
 - 3σ Design reduces tolerance
 - **Thermal Dependence**
 - Copper Material
 - TCO = 0.00352 - 0.00393

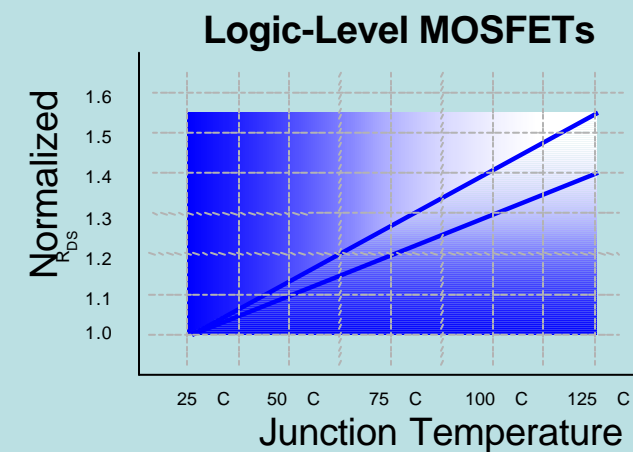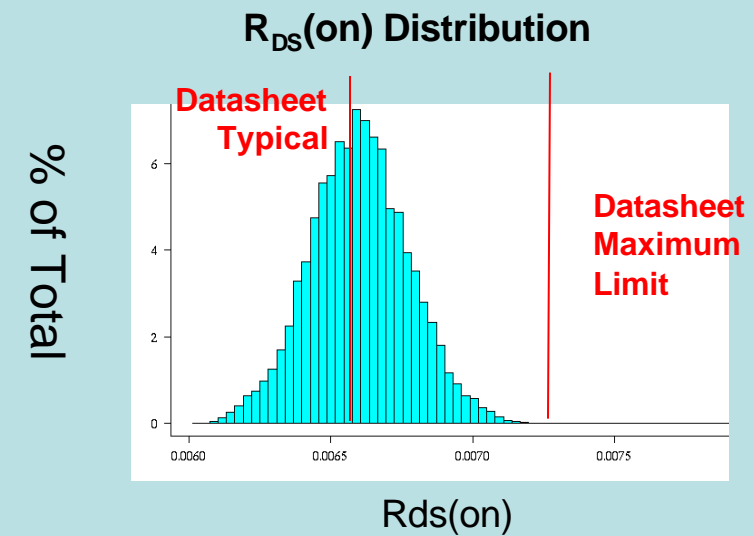- **MOSFET $R_{DS(on)}$**
 - **Initial Accuracy » 10%**
 - 3σ Design reduces tolerance
 - **Thermal Dependence**
 - Silicon, Aluminum, and Copper Materials
 - TCO = 0.0040 - 0.0055
 - **Fewer Components Required**




DCR Sensing Network

A simple R-C network to measure current

Voltage on C is equal to voltage on DCR

ONLY IF TIME CONSTANTS ARE EQUAL

Voltage across C is measured

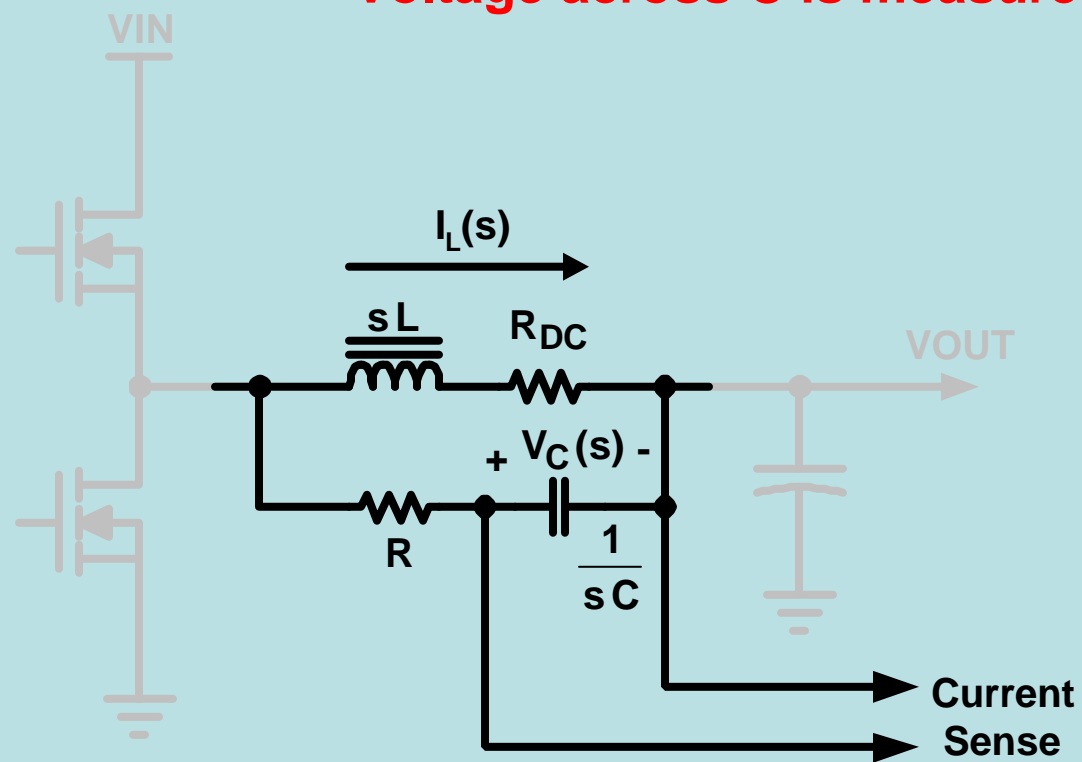

$$V_C(s) = V_L(s) \frac{\frac{1}{sC}}{R + \frac{1}{sC}}$$

$$= I_L(s) R_{DC} \frac{s \frac{L}{R_{DC}} + 1}{sRC + 1}$$

$$V_C(s) = I_L(s) R_{DC} \quad \text{if} \quad \frac{L}{R_{DC}} = RC$$

Accurate DCR Sensing Requires Accurate Time-constant Matching

- **Four elements effect time constant matching**
 - Inductance
 - varies with current
 - varies with tolerance
 - DCR
 - varies with temperature
 - varies with tolerance
 - Measurement Resistor
 - minor tolerance variation
 - Measurement Capacitor
 - tolerance variation
 - temperature variation

Parameter	Variation
Inductor nominal value	±15%
Inductor low-load value	+3%
Inductor full-load value	-3%
Inductor DCR at 25°C	±10%
Inductor DCR temperature	.39%/°C
Time-constant resistor	±1%
Time-constant capacitor initial	±10%
Time-constant capacitor cold	0%
Time-constant capacitor hot	-7%

- Inductor with tight tolerances on L and R_{DC} is expensive
- Analysis indicates about a 20% variation in time-constant mismatch over temperature and load using these values

Tolerance Analysis

Description of parameter	Tol	Sym	Minimum	Nominal	Maximum
Number of phases in multi-phase buck converter		N_F		3	
Minimum inductor temperature		$T_{L,MIN}$		20	
Maximum inductor temperature		$T_{L,MAX}$		120	
Inductor nominal value	15%	L_{NOM}	512E-09	560E-09	608E-09
Inductor low-load value		L_{LL}		543E-09	
Inductor full-load value		L_{FL}		577E-09	
Inductor DCR at 25 °C	10%	R_{DC}	763.23E-06	810.00E-06	8.57E-04
Inductor DCR temperature coefficient		α_L		0.390%	
Inductor DCR cold		$R_{DC,COLD}$		794.205E-06	
Inductor DCR hot		$R_{DC,HOT}$		1.11E-03	
Time-constant resistor	1%	R_t	5.87E+03	5.9E+03	5.93E+03
Time-constant capacitor initial value	10%	C_t	94.2E-09	100E-09	106E-09
Time-constant capacitor to inductor coupling coefficient				60%	
Time-constant capacitor maximum temperature				80	
Time-constant capacitor cold		$C_{t,COLD}$		100E-09	
Time-constant capacitor hot		$C_{t,HOT}$		93.0E-09	


Standard deviations to report 3.5

RSS Results

Time-constant mismatch - cold, low load	8.0%	13.7%	19.5%
Time-constant mismatch - hot, low load	-19.6%	-12.1%	-4.7%
Time-constant mismatch - cold, full load	13.3%	18.8%	24.2%
Time-constant mismatch - hot, full load	-12.6%	-5.6%	1.4%

Rising Transient Edge


Well-Matched Time Constant

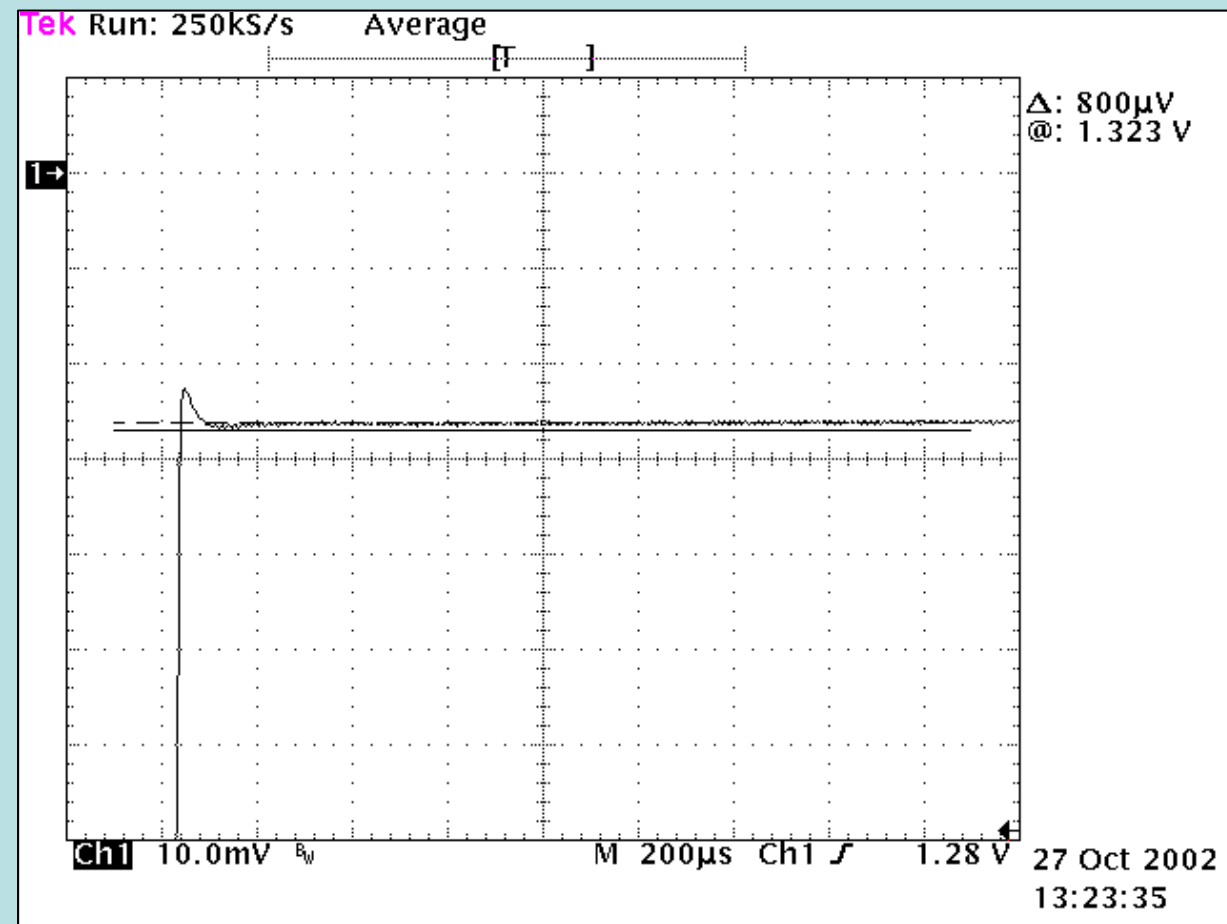

Approximately 1mV of offset related overshoot

Falling Transient Edge


Well-Matched Time Constant

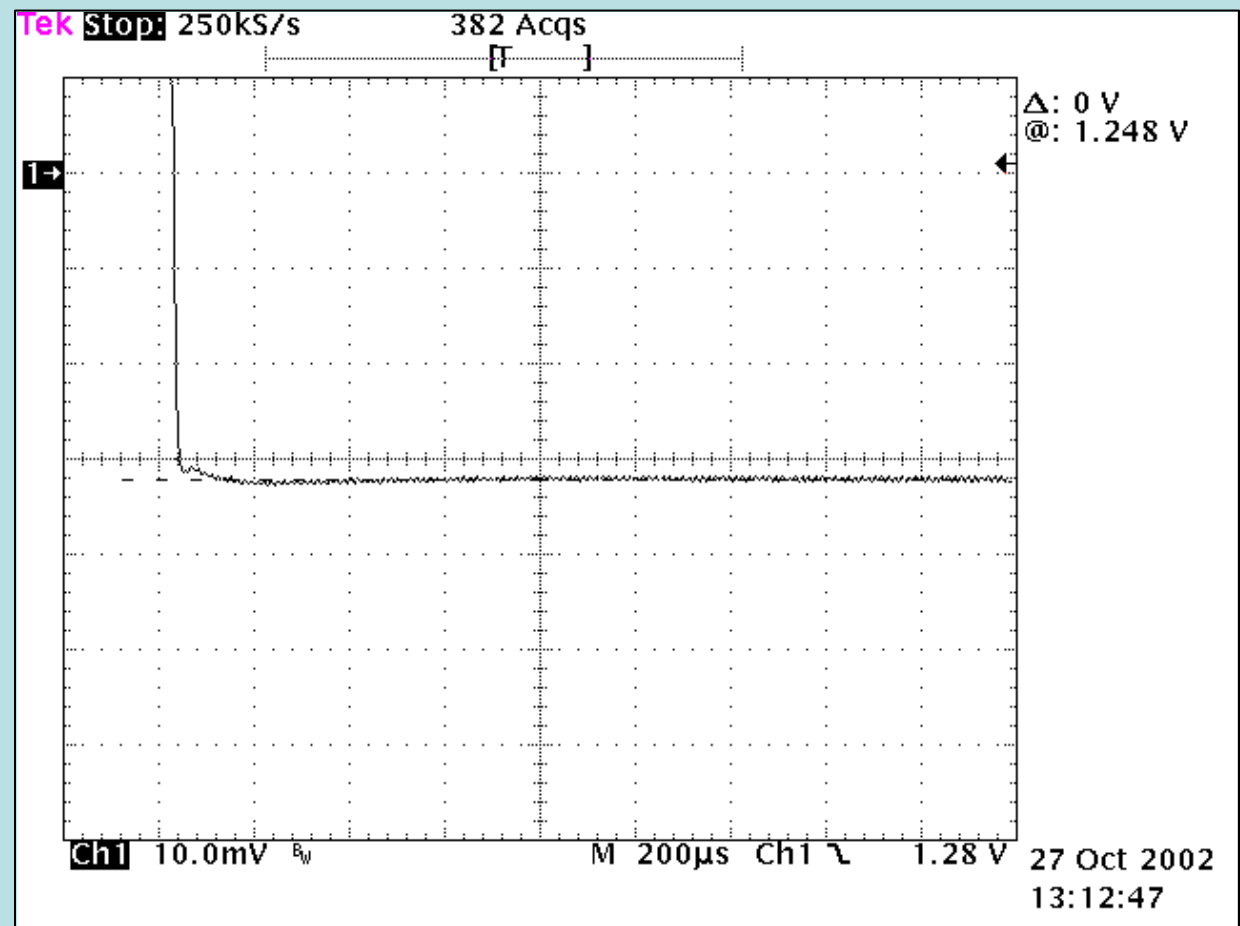

Negligible offset-related undershoot

Rising Transient Edge


+20% mismatch...

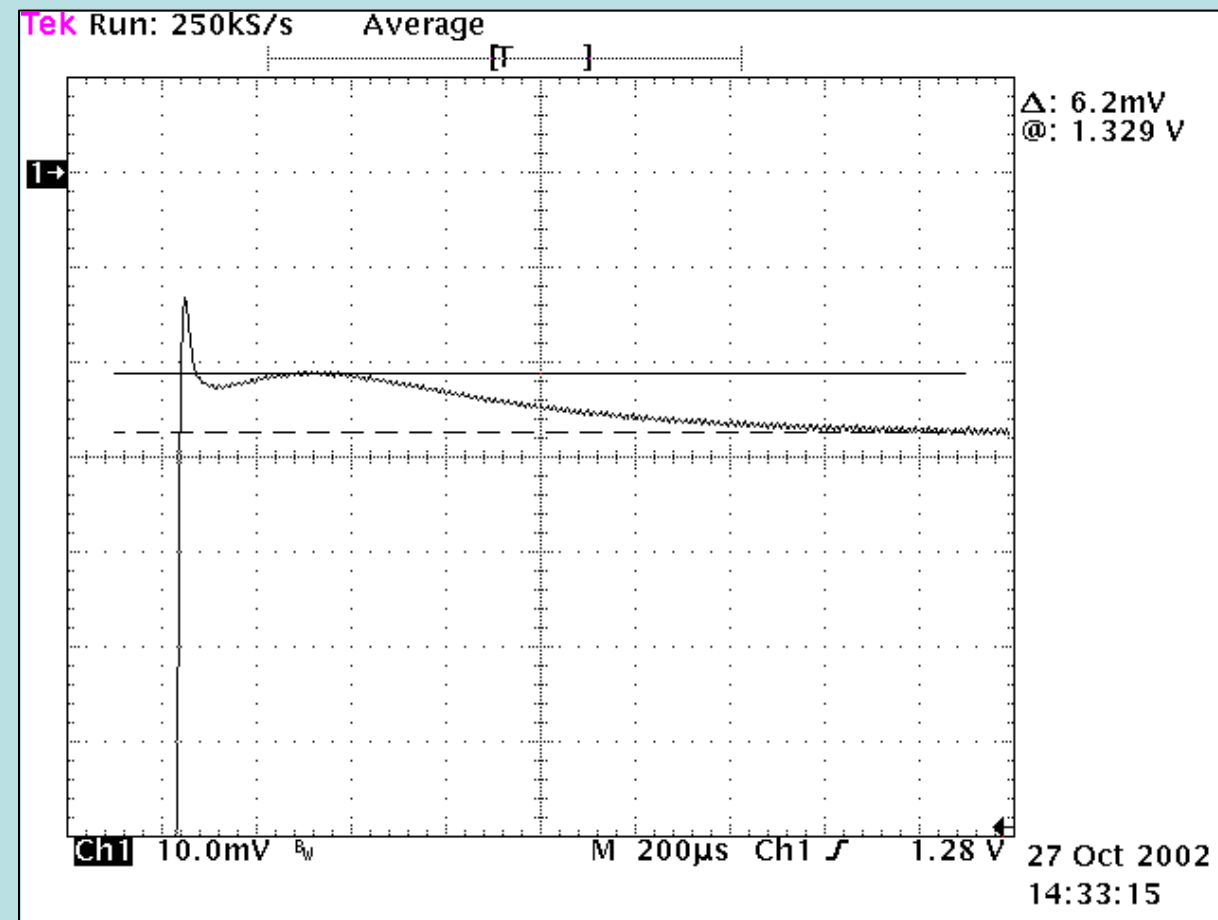

Approximately 6mV of offset-related overshoot

Falling Transient Edge

+20% mismatch...

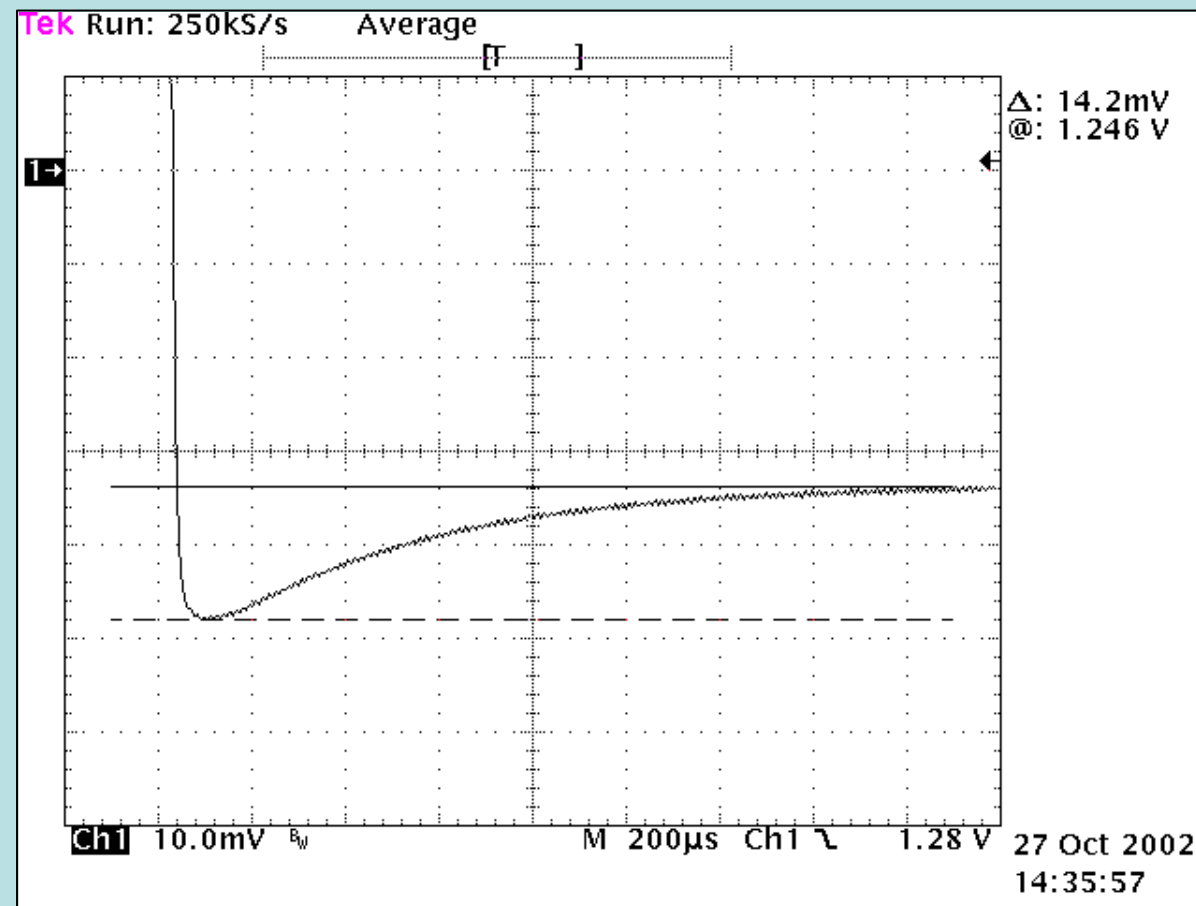

Approximately 14mV of offset-related undershoot

Temperature effect on current sensing


- V_{DROOP} depends on temperature

$$V_{\text{DROOP}}(T) = R_{\text{FB}} I_{\text{SEN}}$$

$$= R_{\text{FB}} \frac{I_{\text{OUT}}}{N} \frac{R_{\text{DS(ON)}}(T)}{R_{\text{ISEN}}}$$

The problem is, we need V_{DROOP} to depend on I_{OUT}

Not on T!

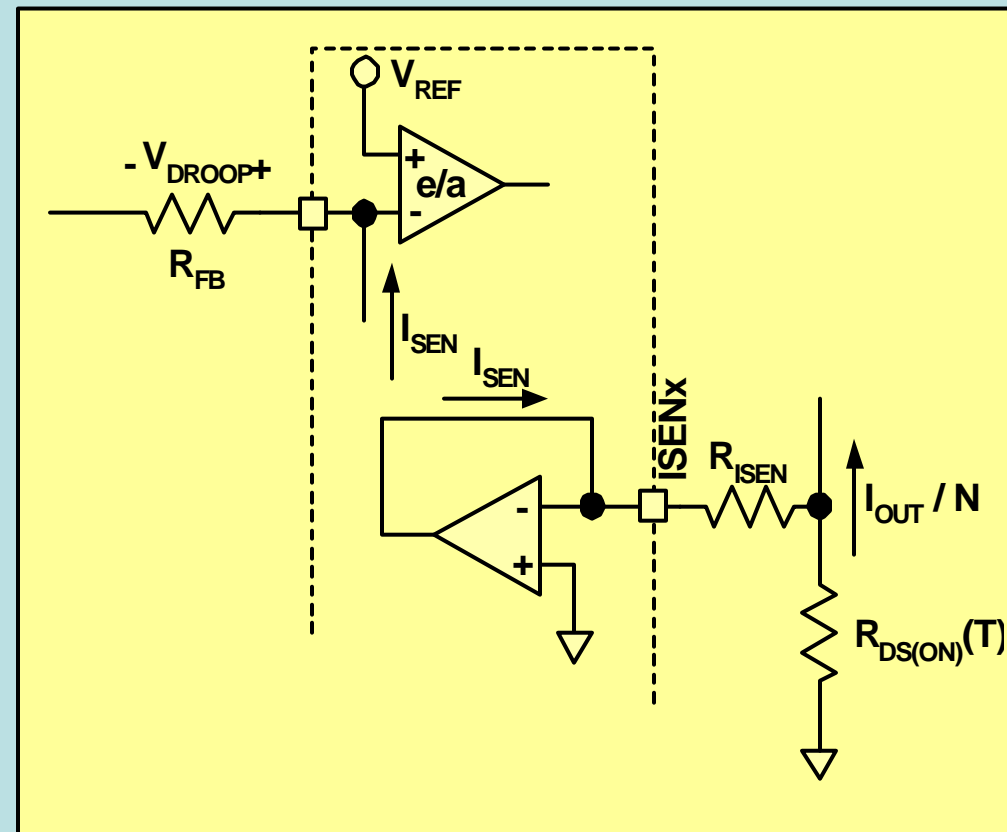

$$V_O + V_{\text{DROOP}} = V_{\text{ID}}$$

$$V_O = V_{\text{ID}} - R_O * I_{\text{OUT}}$$

RDS(ON) Increase With Temperature

$$\mathbf{a} = \frac{\mathbf{DR}}{\mathbf{DT}} = \frac{1.28 - 1.0}{95 - 25} = 0.40 \frac{\%}{^{\circ}\mathbf{C}}$$

- Now we have an easy formula for calculating $R_{DS(ON)}(T)$

$$\mathbf{R}_{DS(ON)}(T) = \mathbf{R}_{DS(ON)}(25) \mathbf{[1 + a (T - 25)]}$$

- Obviously this presents a problem
 - We need accurate current sensing, but...
...we can't pay the dollar cost to keep \mathbf{DT} small.

V_{DROOP} Temperature Dependence

- We want $R_o = \frac{V_{\text{DROOP}}}{I_{\text{OUT}}}$ to be constant
- One way to make sure of that is to give R_{FB} the right kind of temperature dependence


$$R_o = \frac{R_{\text{FB}}(T)}{N} \frac{R_{\text{DS(ON)}}(T)}{R_{\text{ISEN}}}$$

SO...

$$R_{\text{FB}}(T) = \frac{R_o N R_{\text{ISEN}}}{R_{\text{DS(ON)}}(T)}$$



$$= \frac{R_o N R_{\text{ISEN}}}{R_{\text{DS(ON)}}(25) [1 + a(T - 25)]}$$

(simplification)

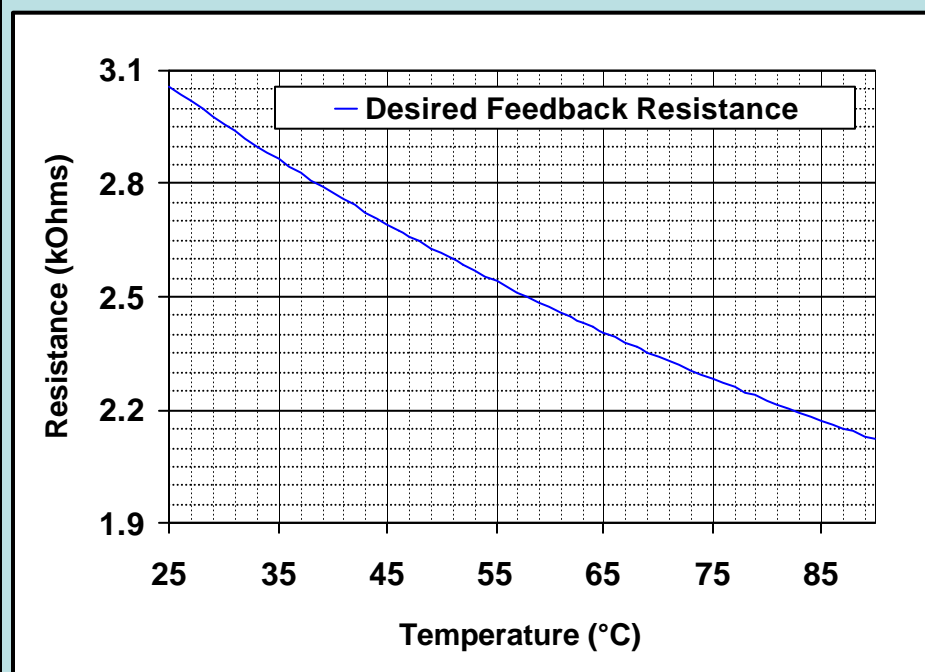

NTC Temperature Compensation

- Replace R_{FB} with this NTC network

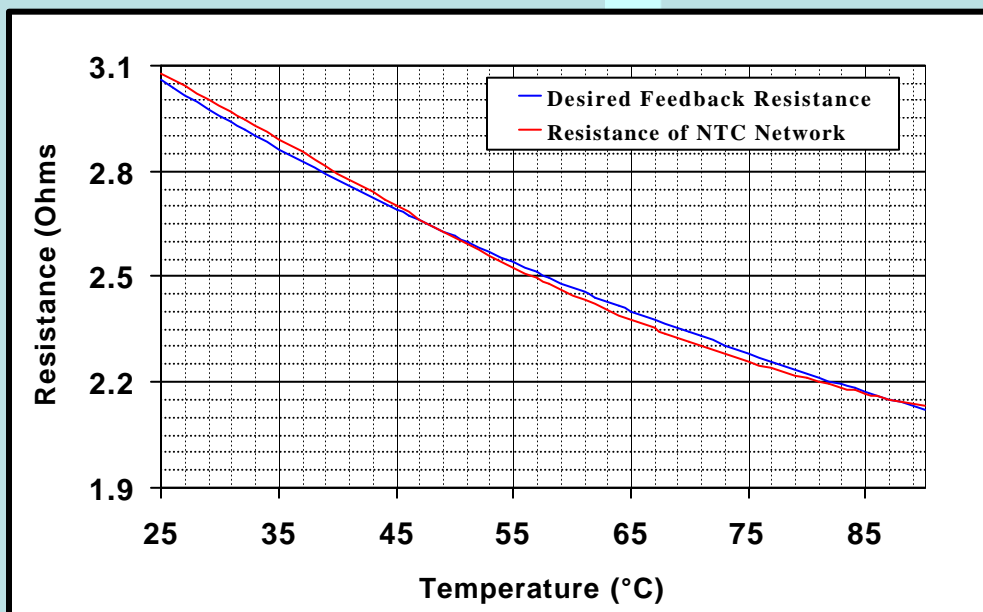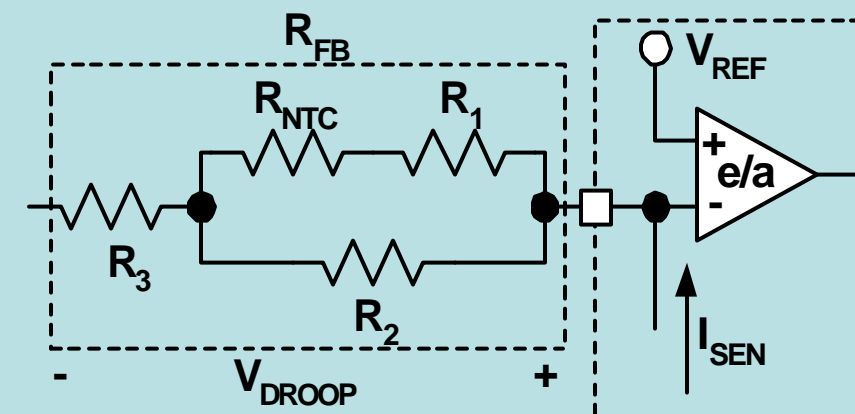

Careful tuning of R_{NTC} , R_1 , R_2 , and R_3 leads to good accuracy

PTC Temperature Compensation

$$R_o = \frac{R_{FB}(T)}{N} \frac{R_{DS(ON)}(T)}{R_{ISEN}}$$

SO...

$$R_{ISEN}(T) = \frac{R_{DS(ON)}(T)R_{FB}}{NR_o}$$

Alternative is to use PTC for R_{ISEN}

PTC Temperature Compensation

Replace R_{SEN} with Positive Temperature Coefficient (PTC) Thermistor

- Use TFPT08052R2KF (Vishay Dale) or Similar
- Stabilizes Current Feedback Signal
 - Close Match of Thermistor and MOSFET Temperature Coefficient
 - Monitors PCB Temperature
- Maintains High Efficiency
- Increases Cost
 - 0805 PTC Thermistor ~\$0.06 each
 - Requires One for Each Power Channel

