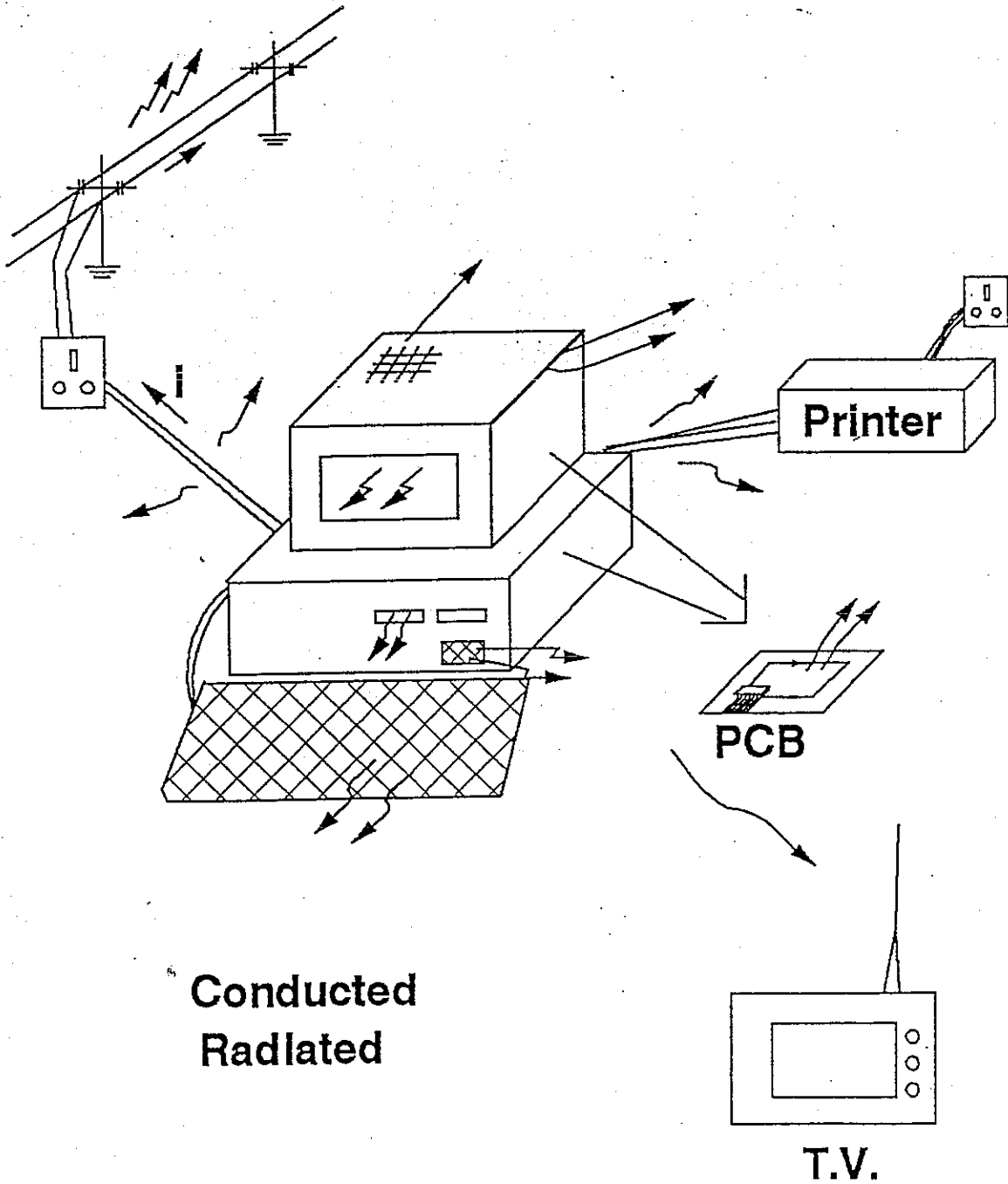


一、簡介


(Introduction)

EMI Problem in PC



EMI , EMC

干 擾 相 容

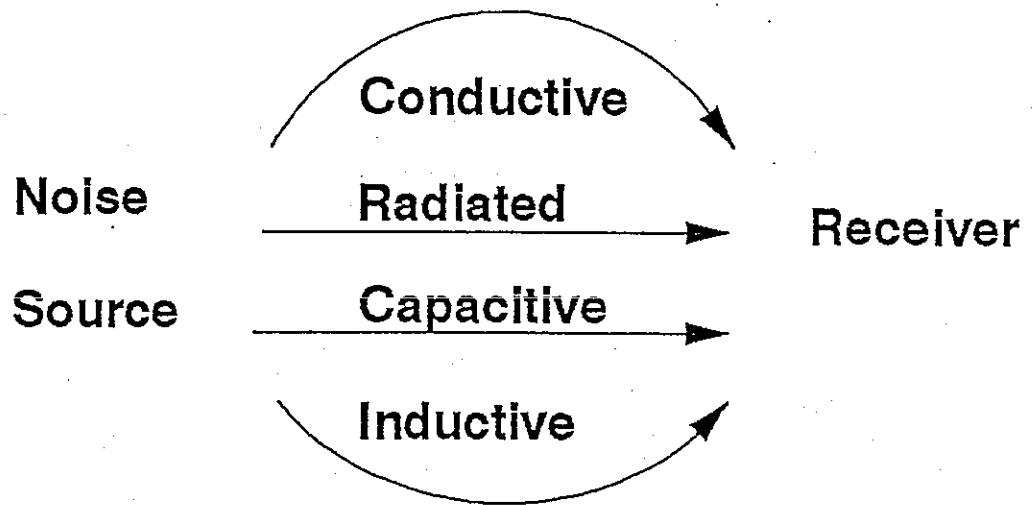

Cure


filtering , shielding , grounding

isolation , seperation , orientation

Purposes of EMI Control

(目的)

Minimize Noise in a Circuit 減少干擾

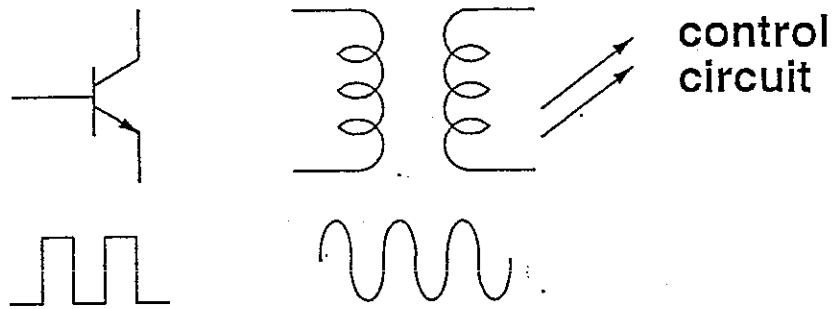

Meet Government Regulation 符合標準

FCC A, B

VDE A, B

MIL SPEC

二、導體耦合之雜訊

(Noise Coupled Through Conductors)

(I * Z coupling)

II — Noise Coupled through Conductors

導線傳導之雜因

Capacitive Coupling

(E field coupling)


Inductive Coupling

(B field coupling)


Common Impedance Coupling

(I * Z coupling)

Capacitive Coupling

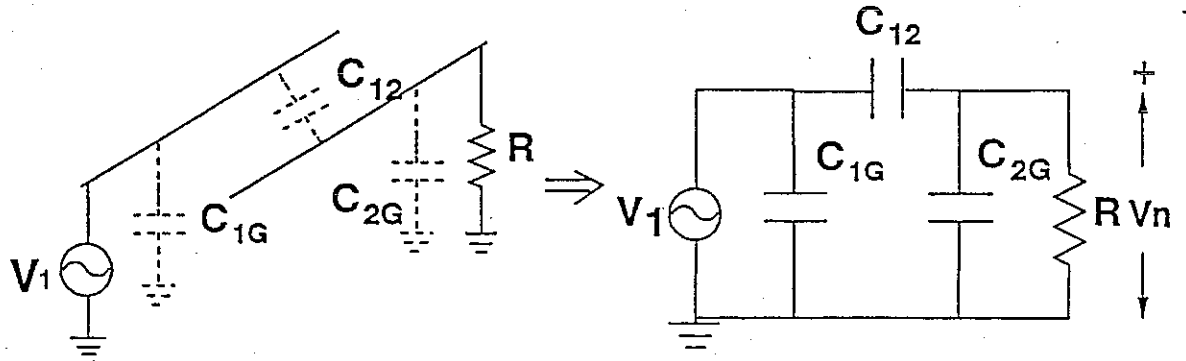


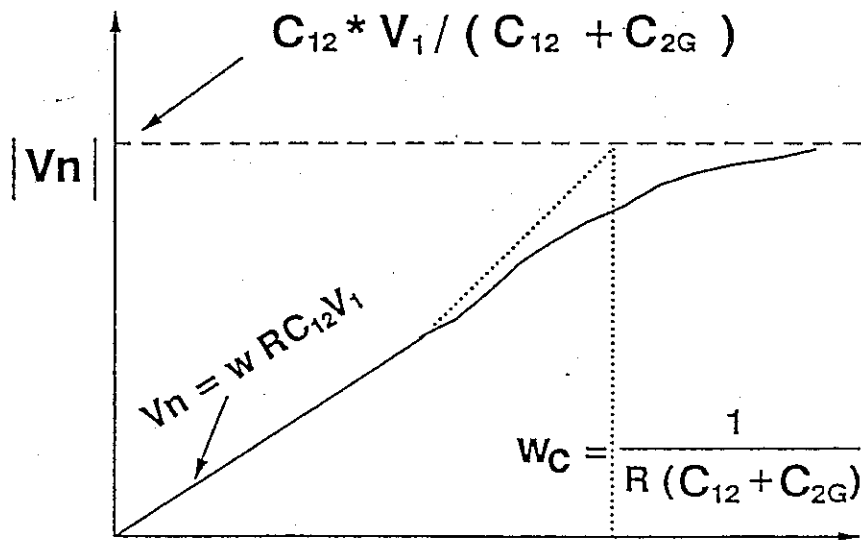
$$V_n = \frac{j\omega [C_{12} / (C_{12} + C_{2G})]}{j\omega + 1/R * (C_{12} + C_{2G})} V_1$$



$V_n \uparrow$ if $C_{12} \uparrow$, $\omega \uparrow$, $R \uparrow$

Effect of a Shield

隱蔽效應

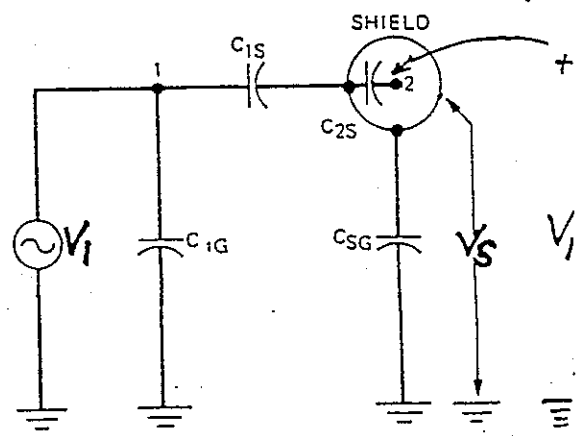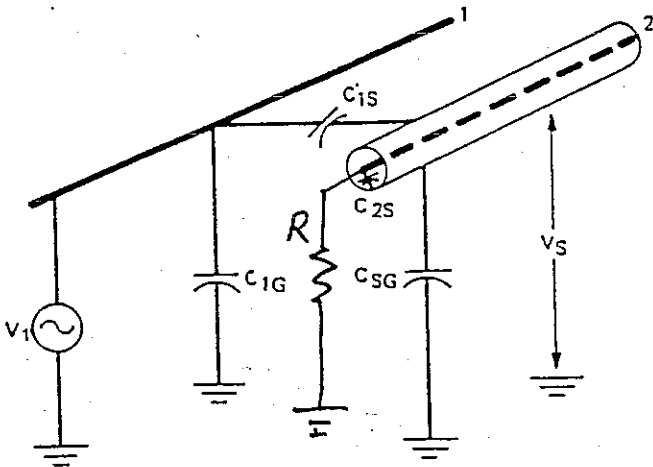

- $$V_s = \frac{C_{1S}}{C_{1S} + C_{GS}} V_1$$
- $V_n = V_s$ if $R \rightarrow \infty$
- If the shield is grounded, $V_n = V_s = 0$
If the shield is connected to a d.c. voltage, $V_n = ?$
- Ground wire must be low impedance to be effective.
(Use wide conductor, soldered well)

- Ungrounded Shield


—— ineffective (無效) shield

- Poor Grounding


—— poor shielding

(不太有效)

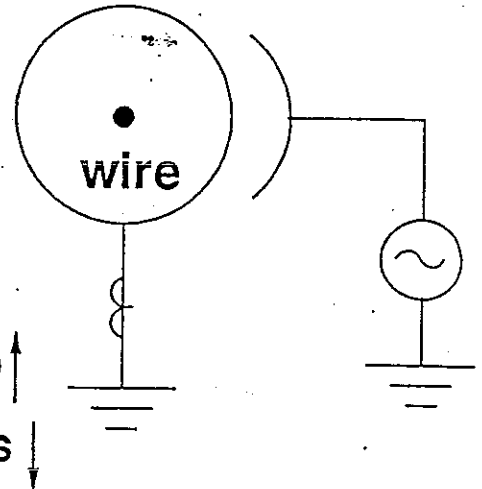- Frequency (of noise) ↑
shielding effectiveness ↓




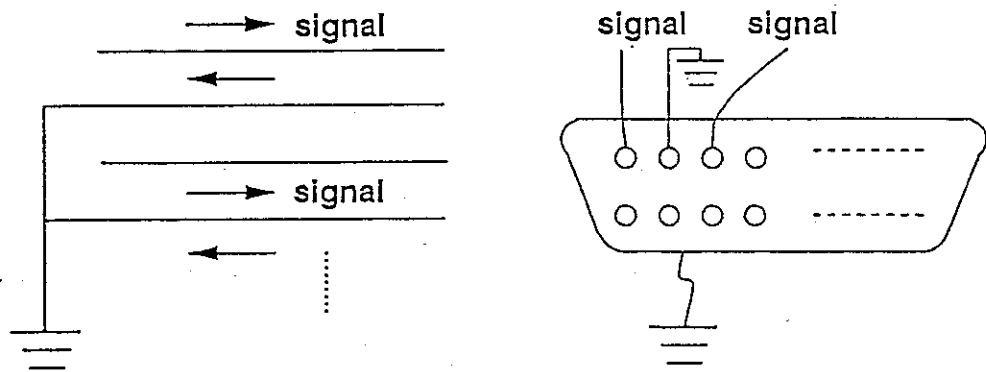Shielding of Ribbon Cables and Connectors



- Grounded wire provides shielding between signal lines
- Separate return avoid common impedance coupling
- $C_{12} \approx 2\text{P.F} / \text{in}$

Transformer Shielding

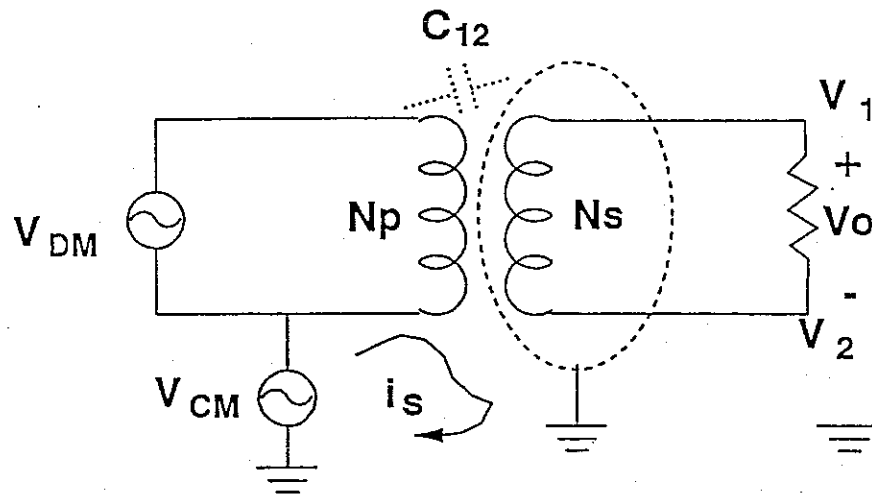


- $V_o = V_{DM} * \frac{N_s}{N_p} + V_{CM} / CMRR$

CMRR (Common Mode Rejection Ratio)
 CMRR \uparrow with shield


- Shield diverts current i to ground
 導向
- Improper shield construction affects magnetic coupling
- Typical Reduction : 100 db at 60 HZ
 20 db at 1 MHZ

Transformer Shield Construction


如何用 shield ?

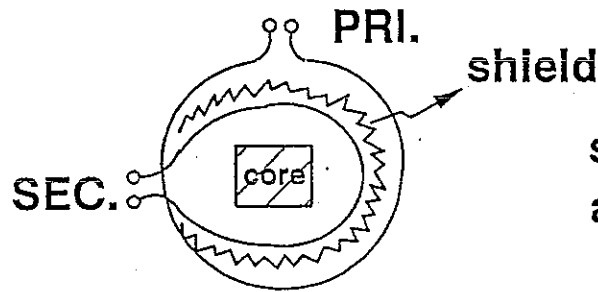


shield must not form a closed loop !!

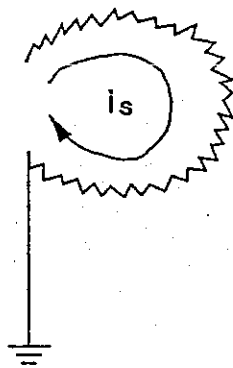

(A)

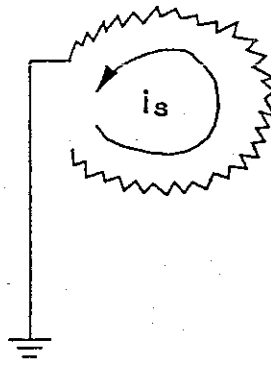


(B)


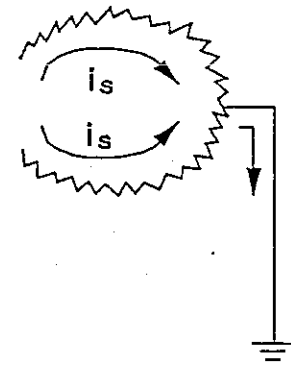


(C)

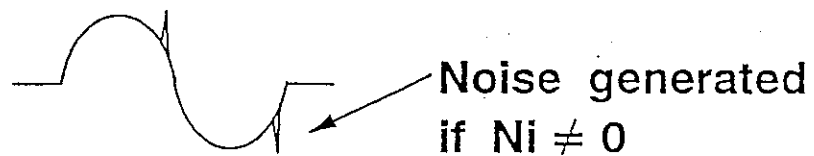Case (C) is best because $\sum N_i = 0$
 \Rightarrow does not affect magnetic coupling




Which Side Shield Tied to ?

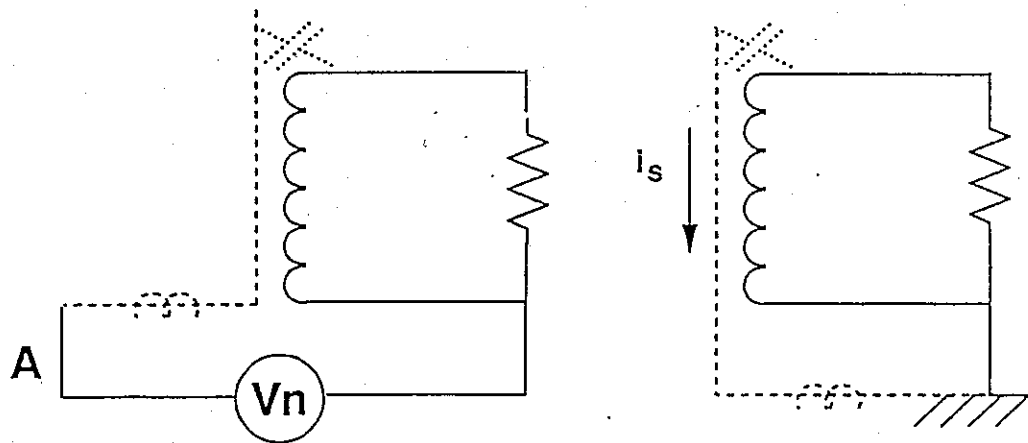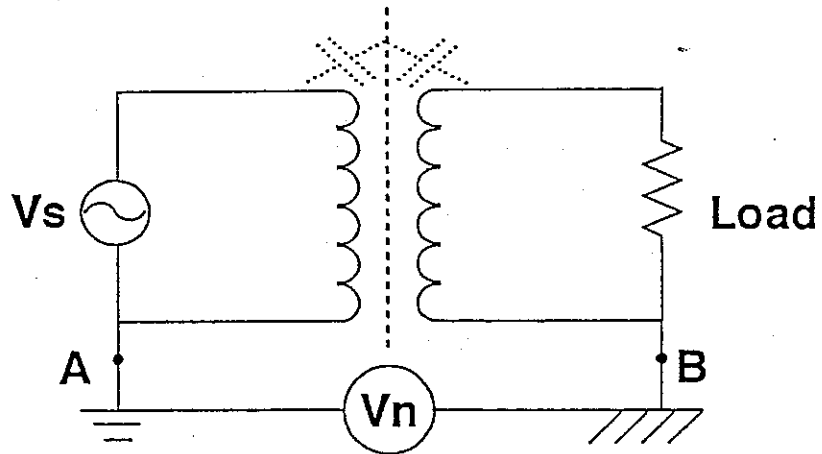

Tie it to the side that you want to protect.

Photo - Coupler

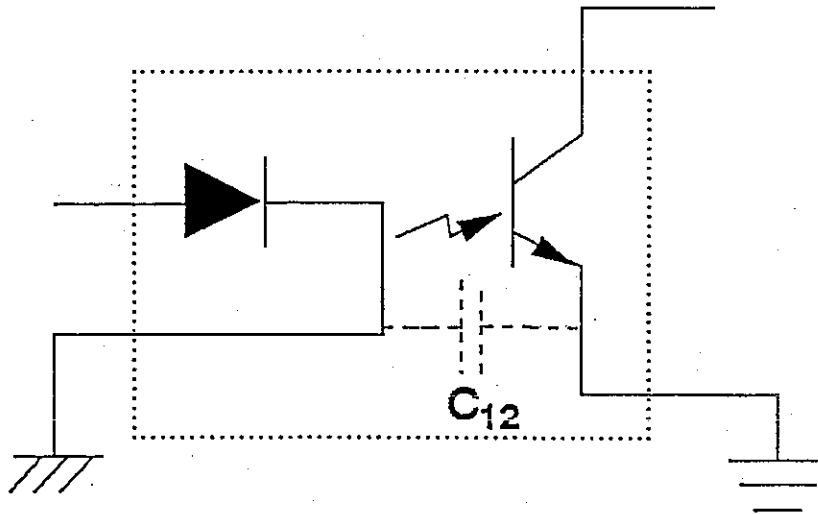


- **Shielded photo-coupler improves noise immunity.**

Reducing Capacitively - Coupled Noise


減少 C - 耦合之雜訊

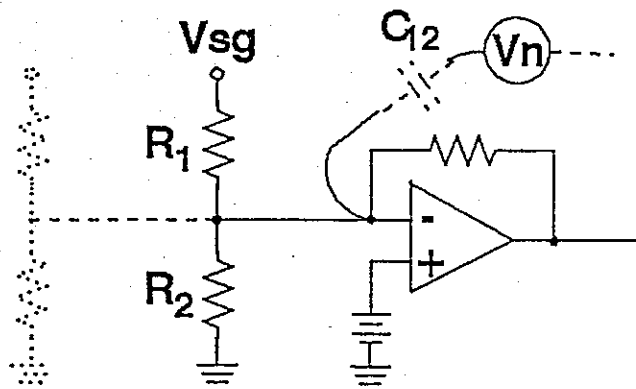- Sensitive line should stay away from high dv/dt line
- Sensitive line should be as low impedance (to ground) as possible
- Sensitive point should stay as close to the amplifier as possible





- Ground unused pins in a I.C. or a connector.

Common Impedance Coupling

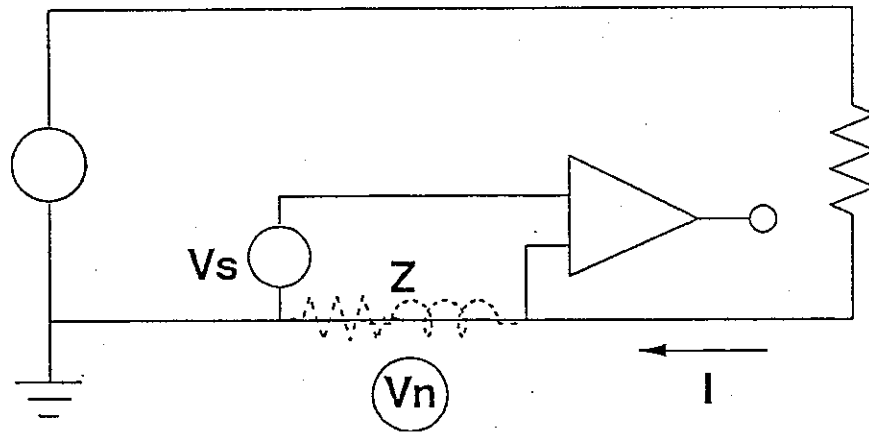


- $I Z$ couples noise into circuit
- $Z = R + j\omega L$; R effect small
 L effect can be large
- $L \approx 20 \text{ nH}$ for 2.5 cm long #20 wire
$$V_n = L \frac{di}{dt} = 20 \text{ nH} * \frac{100\text{mA}}{20\text{ns}} = 100\text{mv}$$

Noise Coupled Through Common Impedance

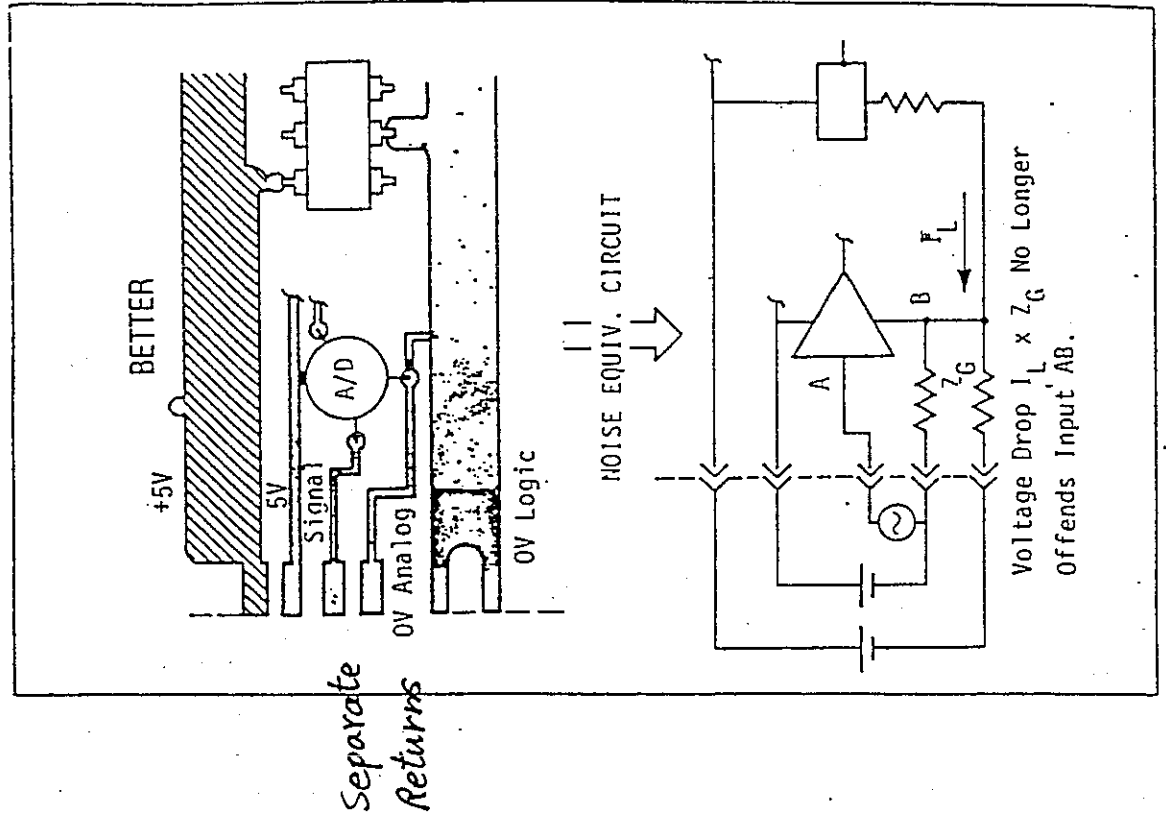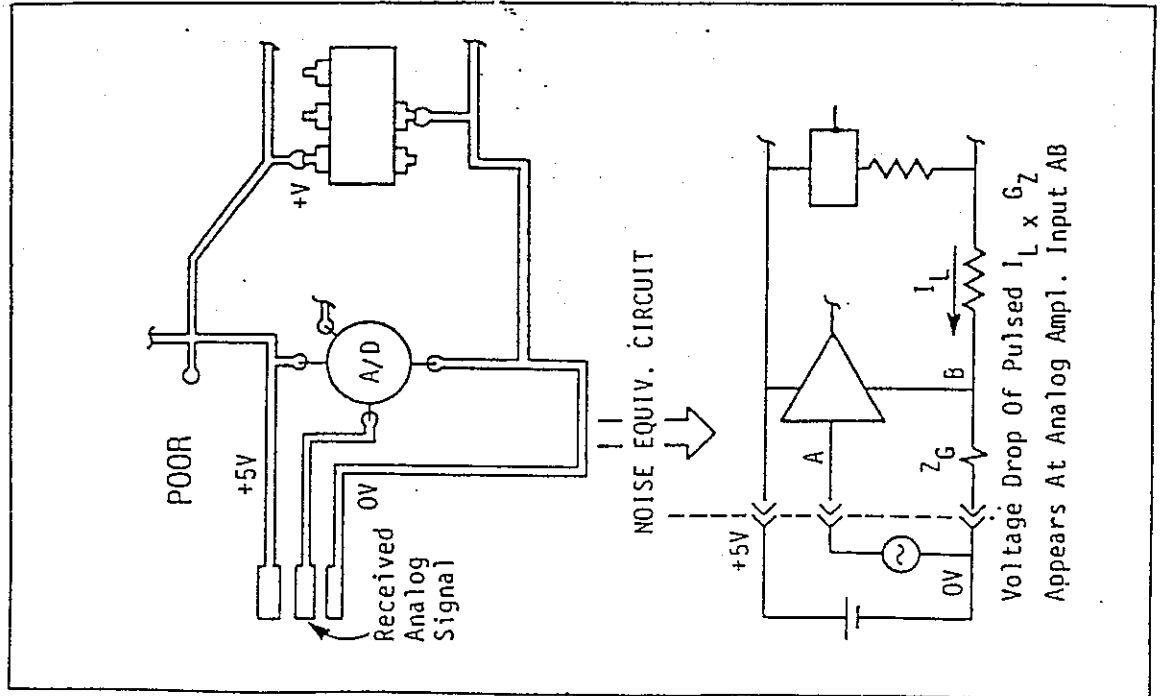

Inductive Coupling

磁性耦合

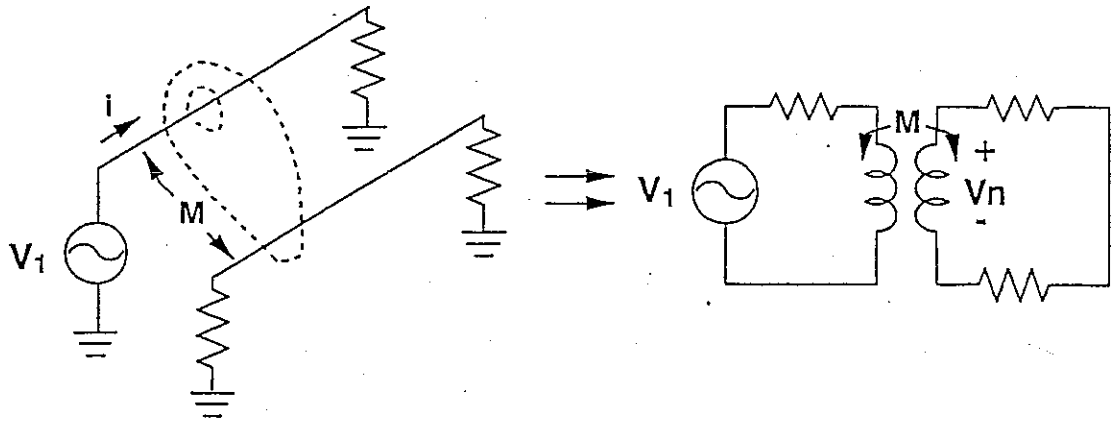

$$V_n = M \frac{di}{dt} = j\omega M i_1$$

M (mutual inductance)

$$= \frac{A \cos \theta \mu}{l_m}$$

A : Area

μ : permeability

l_m : magnetic mean length

θ : angle of two planes

Ground-Plane Impedance
of 1-Oz. Copper Foil (t=.03mm)



Frequency	Impedance mΩ/sq.	Frequency	Impedance mΩ/sq.
100 Hz	0.574	20 MHz	1.61
1 kHz	0.574	30 MHz	2.03
10 kHz	0.574	50 MHz	2.62
100 kHz	0.574	70 MHz	3.09
1 MHz	0.582	100 MHz	3.69
2 MHz	0.604	200 MHz	5.22
3 MHz	0.638	300 MHz	6.39
5 MHz	0.736	500 MHz	8.26
7 MHz	0.855	700 MHz	9.77
10 MHz	1.04	1 GHz	11.6

- Beyond 5 MHz, $Z \propto \sqrt{f}$
due to skin effect
- Inductive effect is slightly evident
above 500 MHz
- Wire : length \gg width
ground plane : length \approx width

Reciprocal Theorem

對等原理 (易收者亦能放)

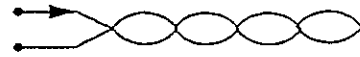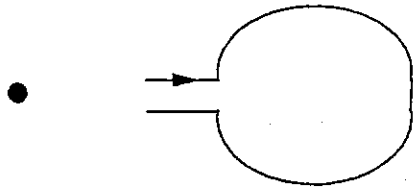
Geometry good for receiving is also good for radiating



Better for radiation control and also less susceptible to radiation

- Case (C) better than (B) better than (A)

Coaxial Cables

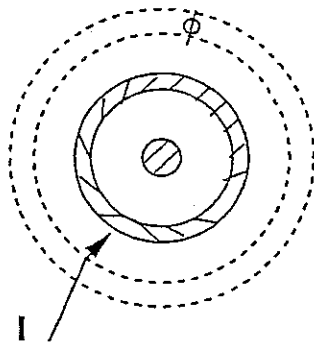

L_s (self inductance)

$$= \phi / I$$


M (mutual inductance)

$$= \frac{\phi_s}{I} \text{ (Generated by } I \text{ that encircles the shield)}$$

- Because of close coupling , $\phi_s = \phi$


$$\therefore \boxed{L_s = M}$$

- Coaxial Cable =

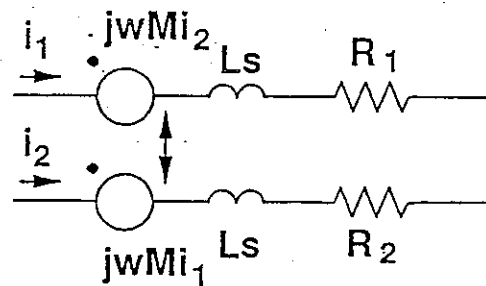

- Twisted wire , M smaller , but still close to L_s

Inductive Decoupling

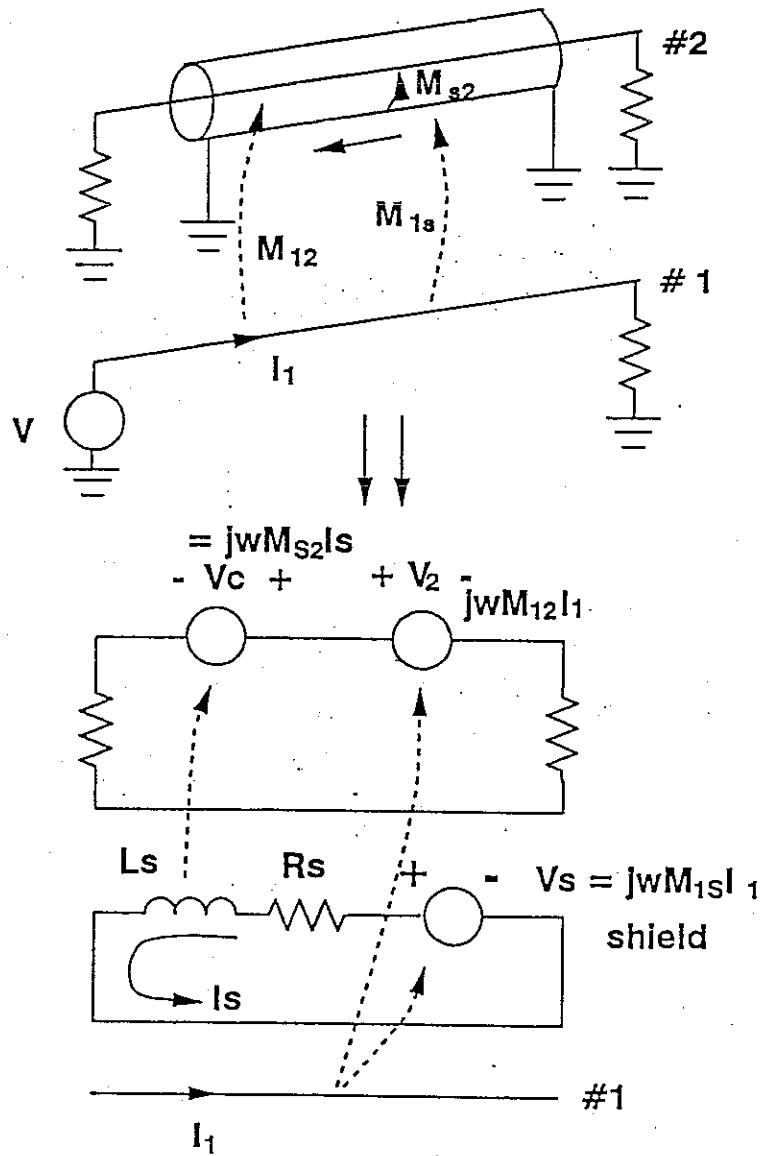

$$V_n \text{ (in \#2 wire)} = V_2 - V_c = j\omega (M_{12} I_1 - M_{s2} I_s)$$


Shielding Effectiveness

$$V_n = j\omega (M_{12} I_1 - M_{s2} I_s)$$

$$= j\omega (M_{12} I_1 - M_{s2} \frac{j\omega M_{1s} I_1}{j\omega L_s + R_s})$$

$$\left(\begin{array}{l} \because M_{1s} \\ = M_{12} \end{array} \right) \Rightarrow = j\omega M_{12} I_1 \left(1 - \frac{j\omega M_{s2}}{j\omega L_s + R_s} \right)$$
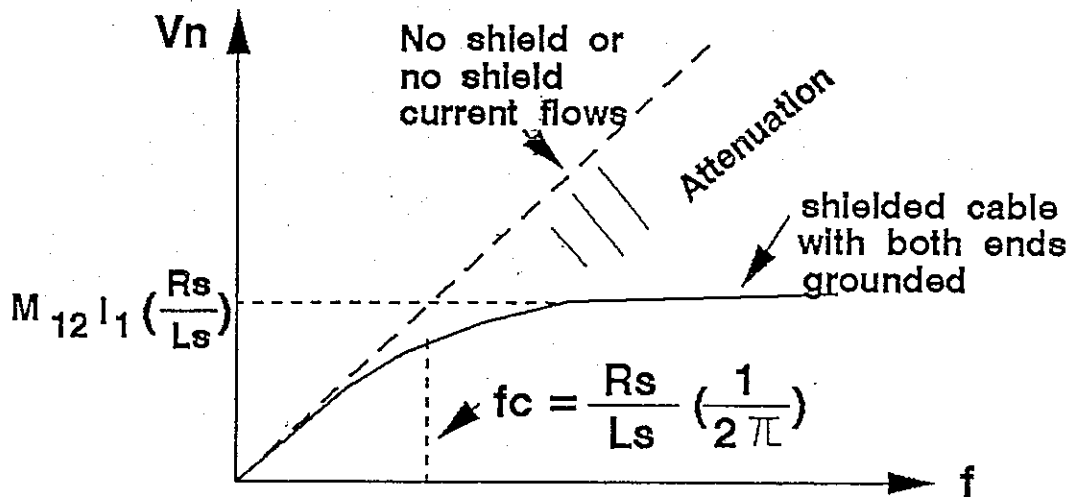
$$\left(\begin{array}{l} \because M_{s2} \\ = L_s \end{array} \right) \Rightarrow = j\omega M_{12} I_1 \left(\frac{R_s / L_s}{j\omega + R_s / L_s} \right)$$



Comments on Shielding Effectiveness



- Shield grounded at one end \implies
no magnetic shielding effect
- Low frequency magnetic field ($f < f_c$)
 $= \frac{R_s}{2\pi L_s}$) is difficult to shield

fc : coaxial cable	RG - 213	0.7 KHZ
	RG' - 59C	1.6 KHZ


Shielded twisted
pair 22 Ga "

7 KHZ


Insertion of C.M. Choke

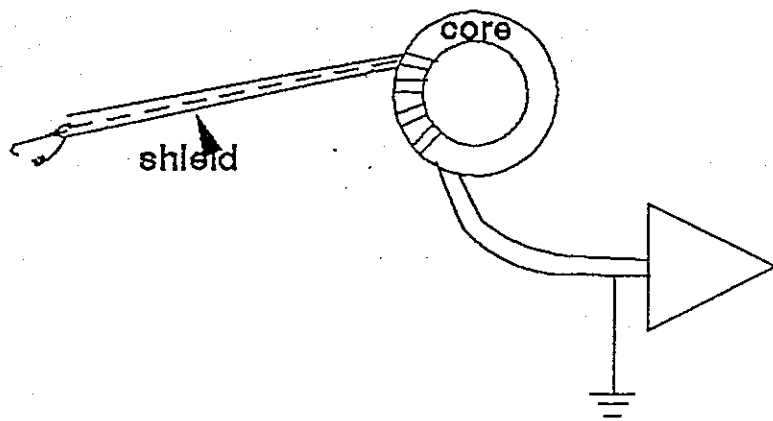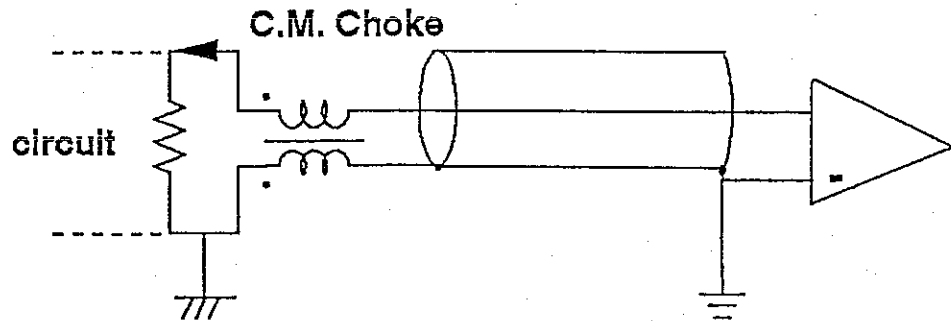

Common -- Mode Chokes

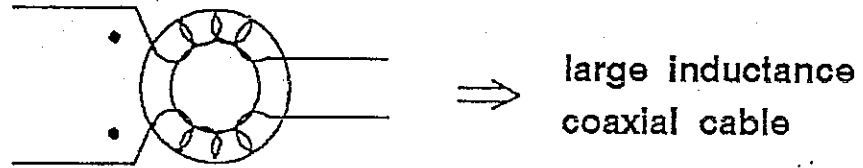


- Differential - Mode signal Unaffected

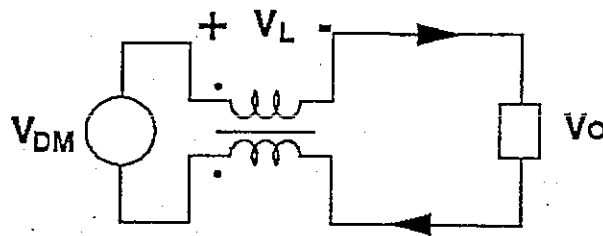

$V_o = V_{DM}$; $V_L = 0$ because $\sum Ni = 0$
 $H = 0 \Rightarrow B = \text{constant} \Rightarrow V_L = 0$





- Increase Loop Impedance

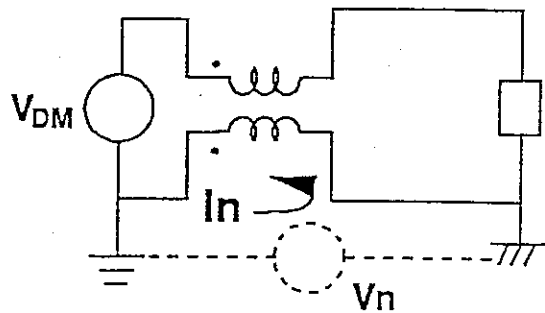

$$I_N = \frac{V_n}{j\omega L_s + R_s}$$


L_s large

Ferrite Beads as Chokes

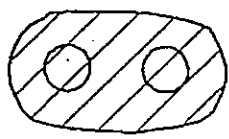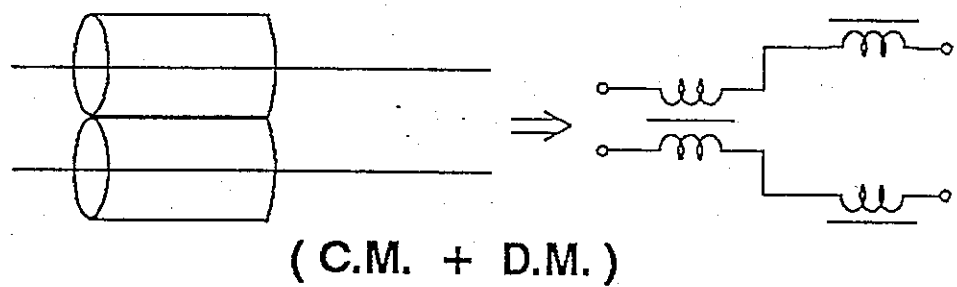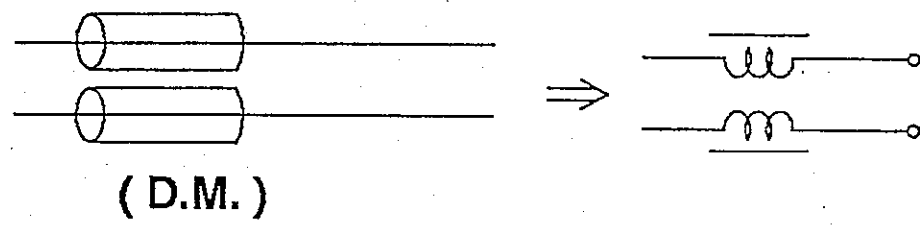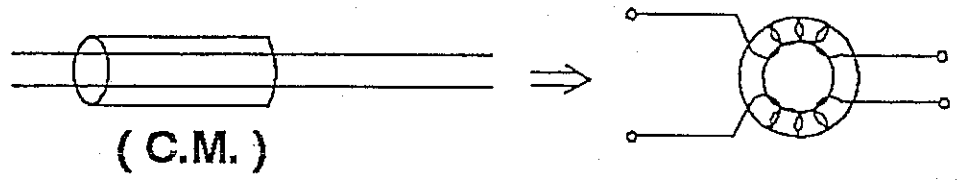


五、傳導性 EMI (Conducted EMI)

Conducted EMI

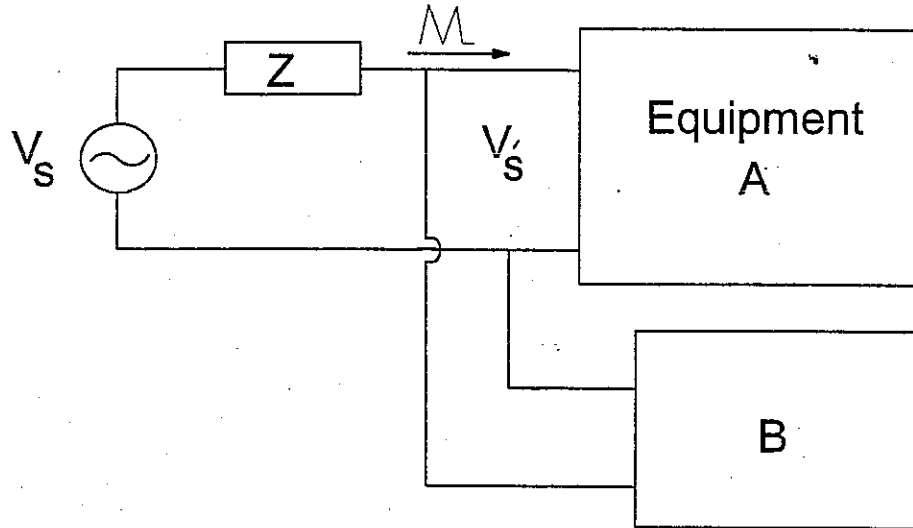


- EMI Depends on Line Impedance Z

Typical Power Line Impedance

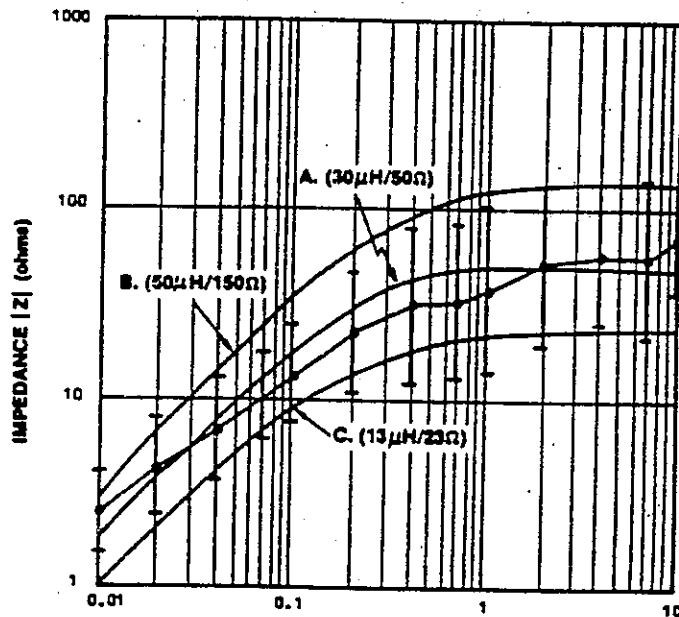


Ref [1]

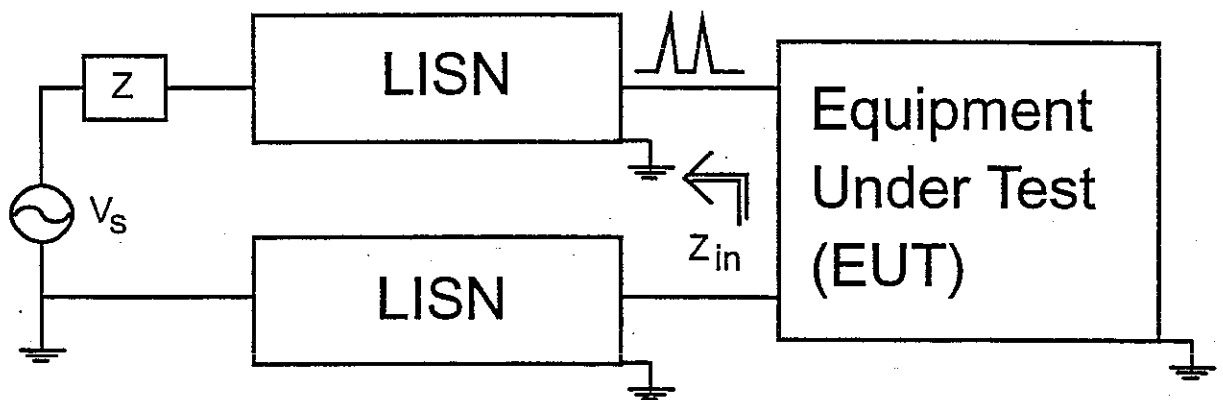Line Impedance Stabilizing Network (LISN)





- A LISN is used to ensure repeatable EMI measurement
- Power frequency signal passes through LISN unaffected.
- For noise frequency, $Z_{in} \approx 50\Omega$

LISN

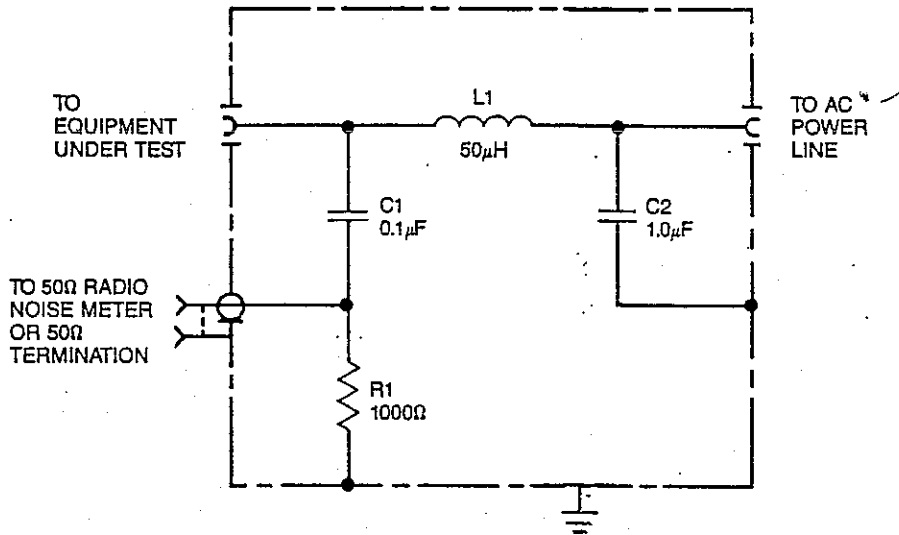


Power
Frequency

Noise (EMI)
Frequency

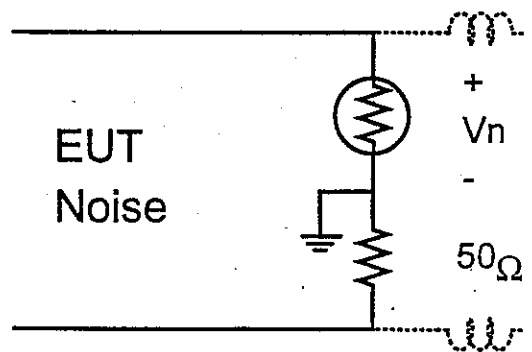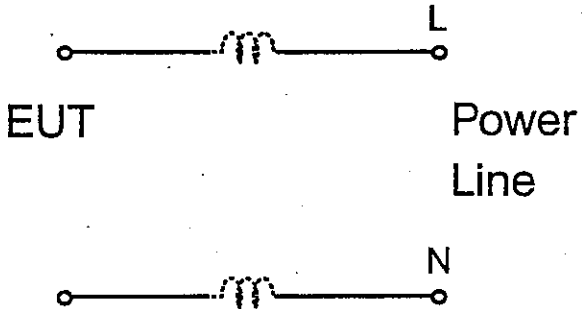


V_n : EMI voltage (conducted)


FCC Conducting Emission Test

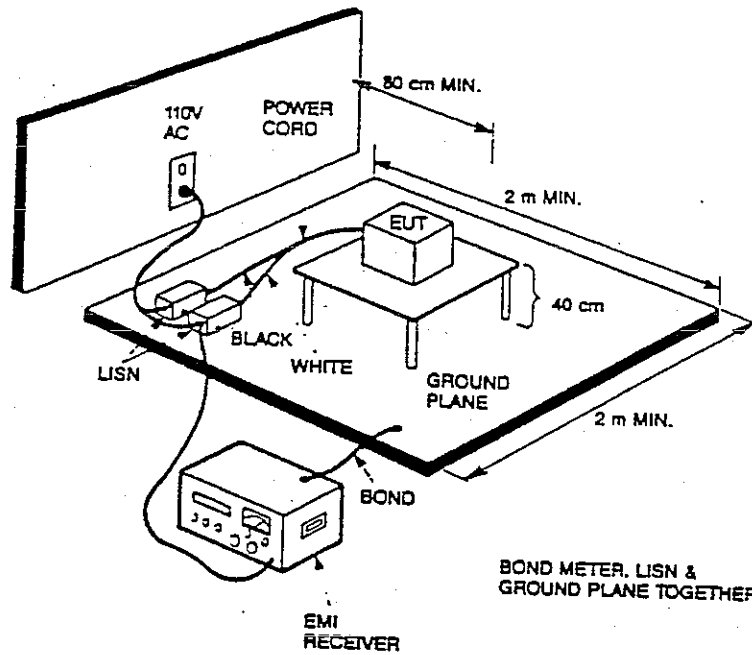


Conduction Emission Limits

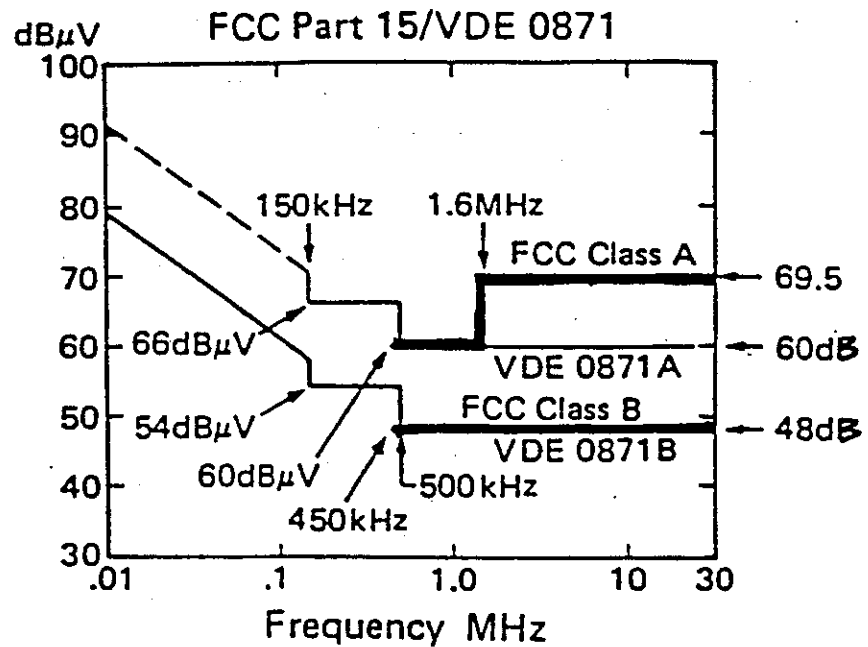

Conducted EMI Measurement

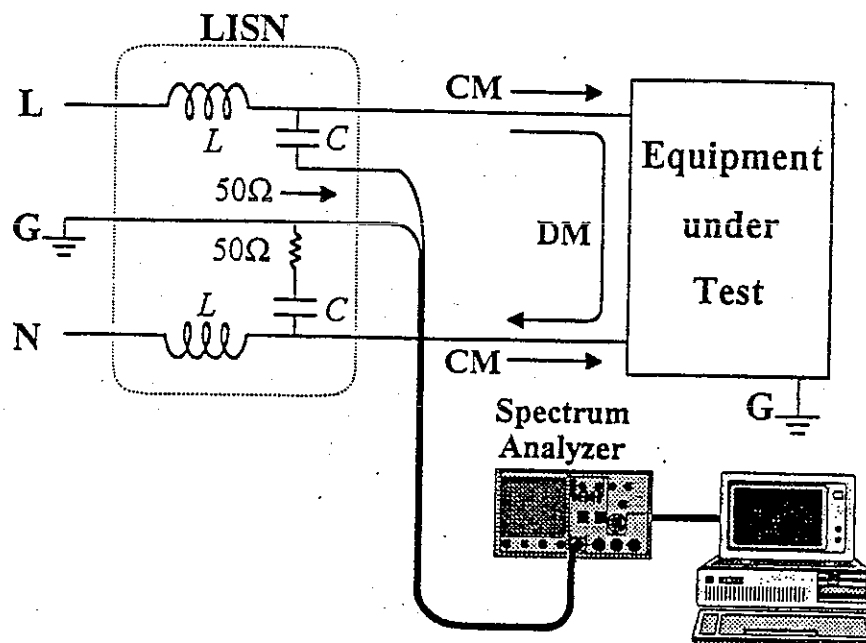

Conducted EMI Test

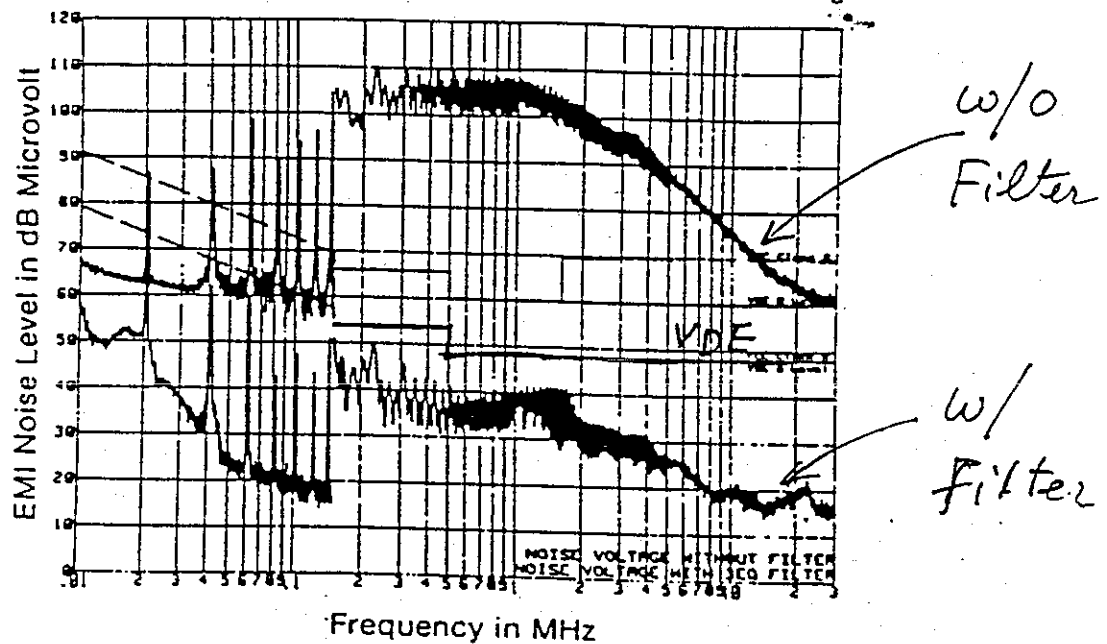


- Measurement bandwidth changes (RBW) at 150 KHz


10K Hz - 150 KHz, RBW = 200 Hz

150 KHz - 30 MHz, RBW = 9 KHz


MIL-STD 461 D-CE102 Limit

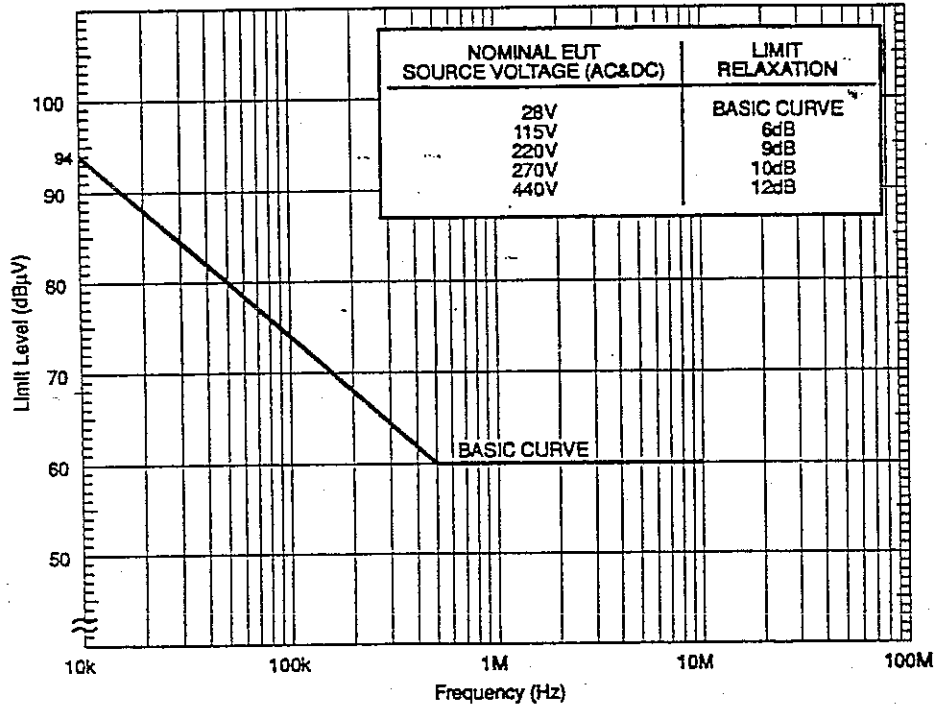

LISN

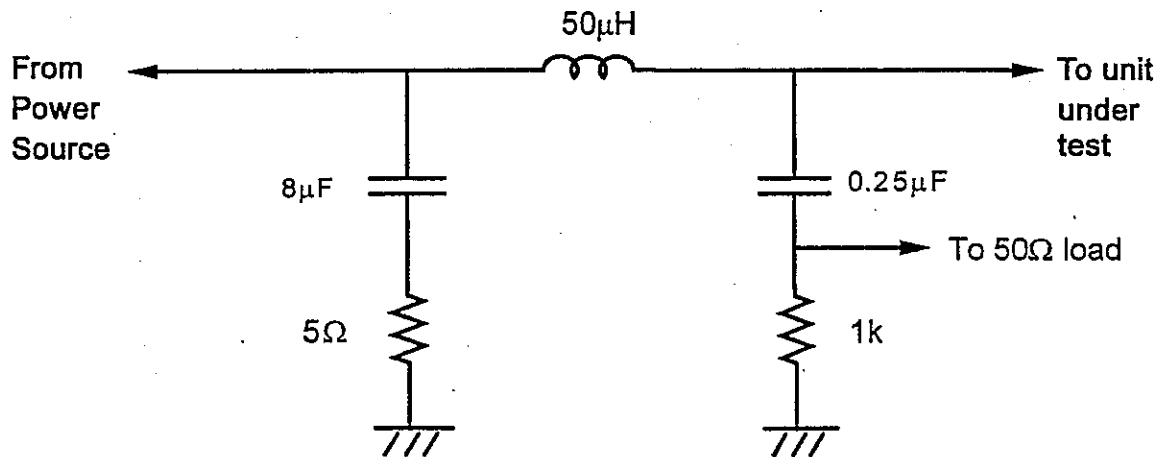



Noise Sources and Coupling Pathes

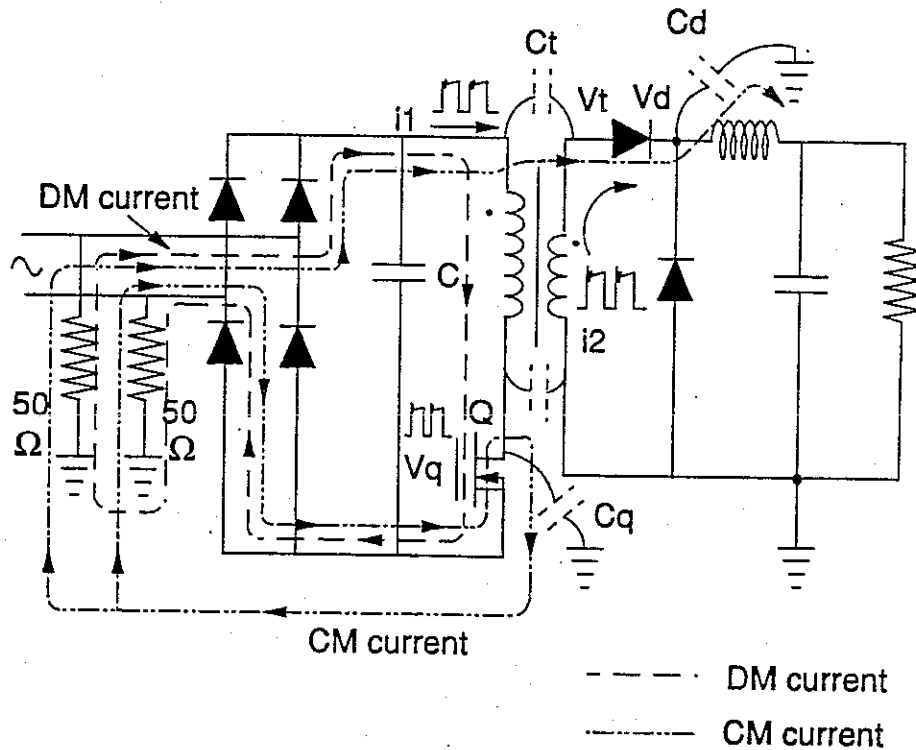


D.M. Noise - Caused by i_1

C.M. Noise - Caused by Parasitic Capacitances

Differential Mode vs. Common Mode

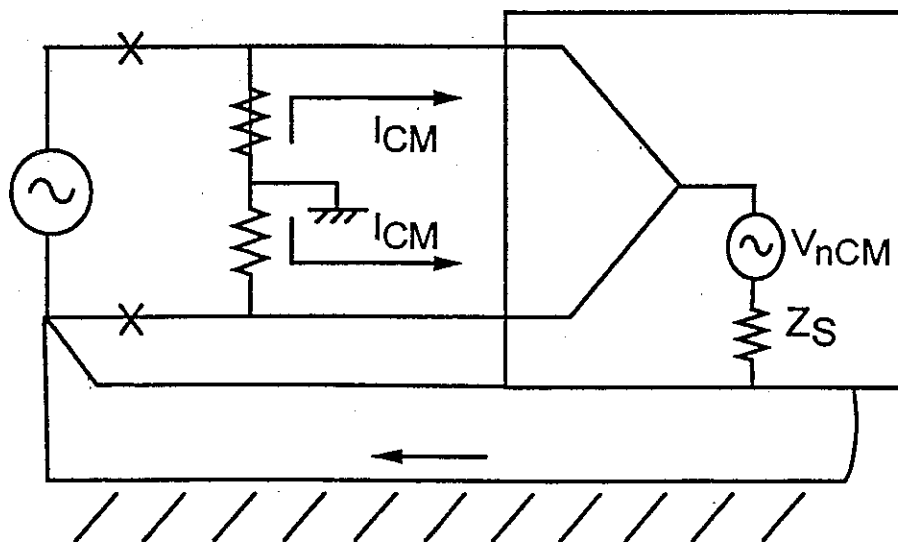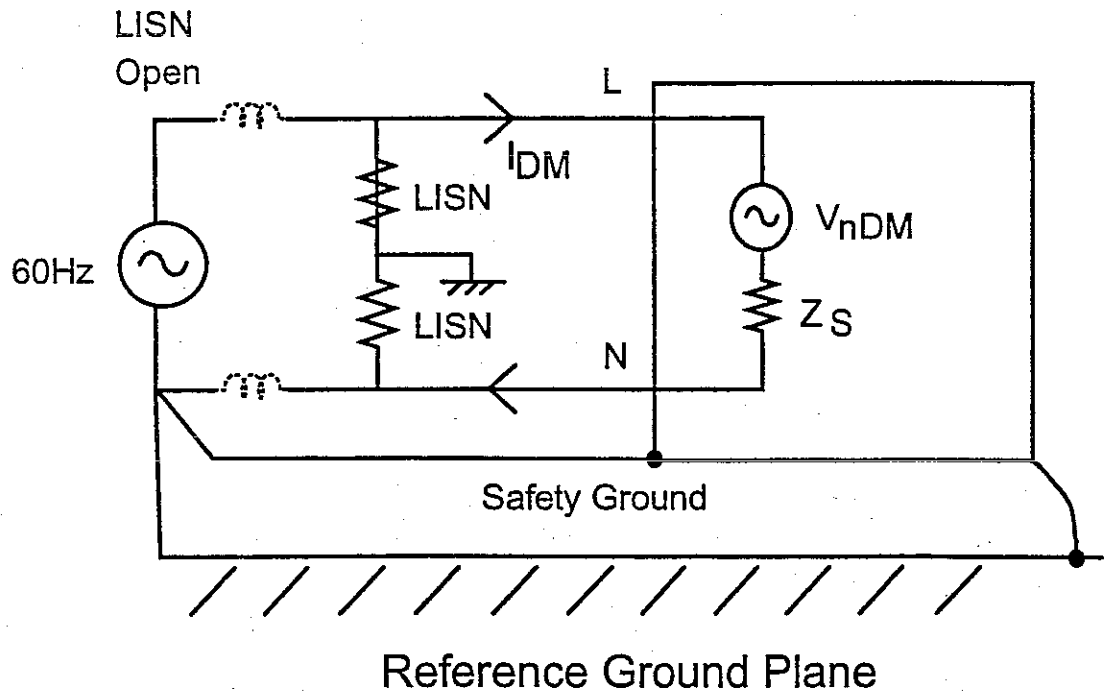

Reducing D.M. EMI

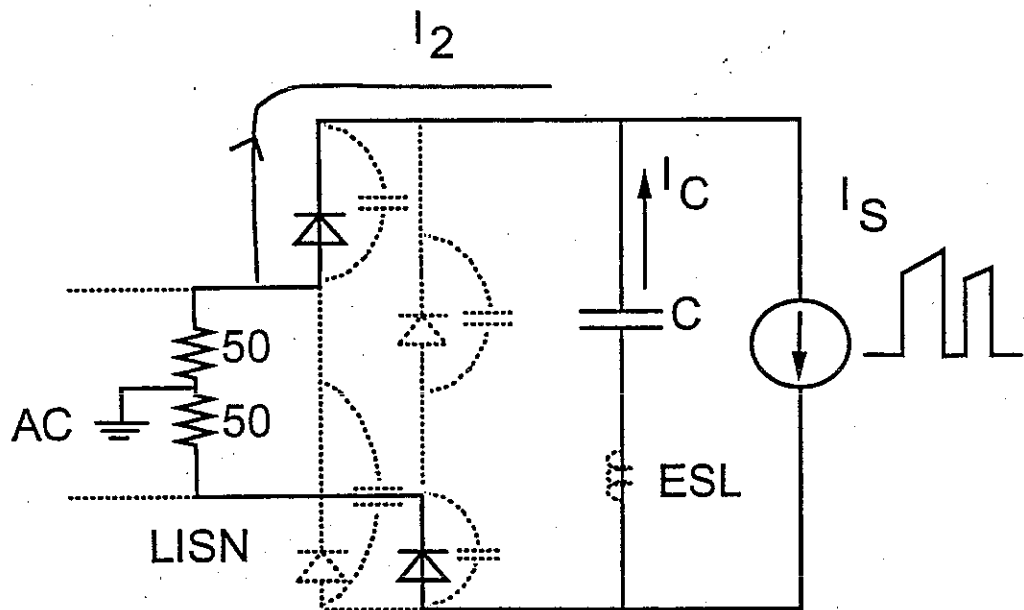


- Is Dependent
- ESL Critical at High Frequency
For $C=20 \text{ uf}$, $ESL = 30 \text{ n.H.}$, $Z_c = 8 \text{ mr}$, $Z_l = 200 \text{ mr}$ at 1 MHz .
- Use small ceramic cap. in parallel with large C, across rectifiers


Reducing CM EMI

Transistor Effects



- Reducing ringing

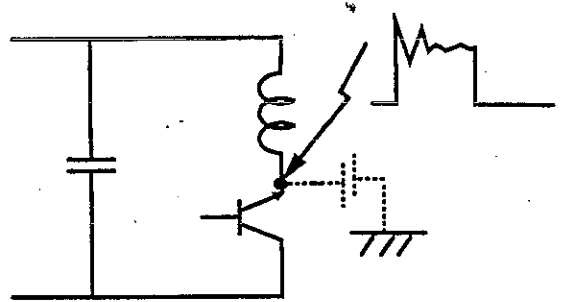

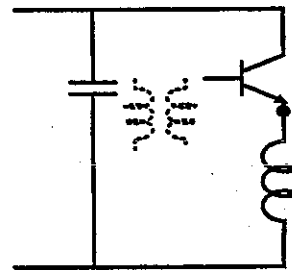
- Tie package (Collector/Drain) to AC ground but this needs an isolated drive



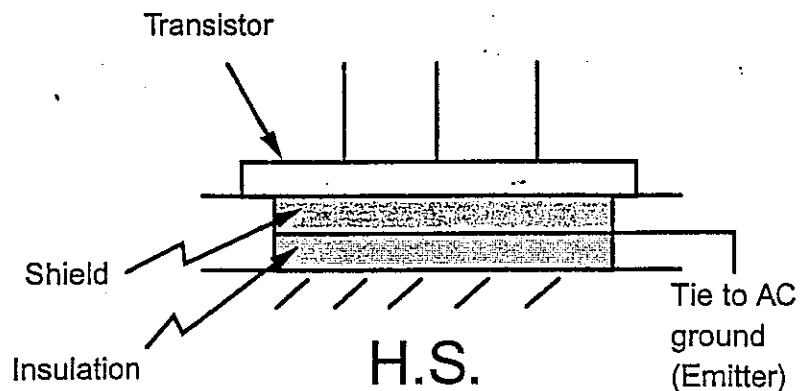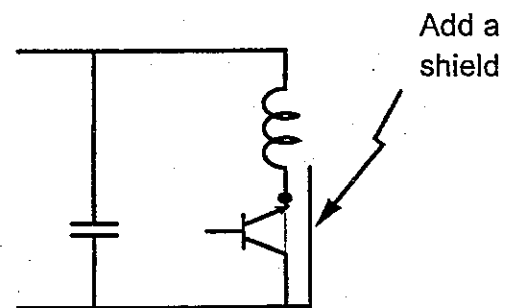- Add a shield and tie the shield to AC ground (Emitter)



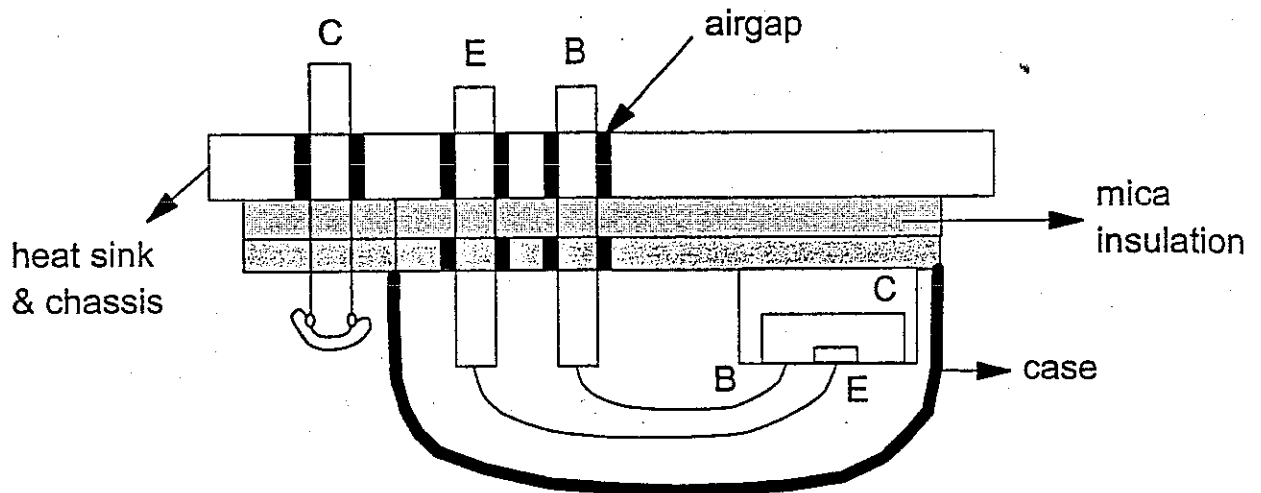Parasitic Capacitances in Transistor Package






$C_{\text{collector - heat sink}}$ >> $C_{\text{emitter - heat sink}}$
 (100 p.f. for TO-3 and mica layer) (< 5 p.f.)

- $C_{\text{parasitic}} \approx 100 \text{ p.f.}$ for TO - 3
 $\approx 80 \text{ p.f.}$ for TO - 5
 $\approx 30 \text{ p.f.}$ for TO - 220
 for normal thickness mica insulation
- For isolate package, $C_{\text{parasitic}}$ depends very much on chip area. For a 600-V, 75-A IGBT, $C \approx 25 \text{ pf}$

Reducing CM EMI


Diode Effects

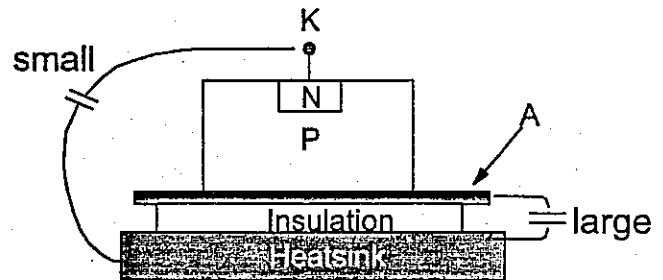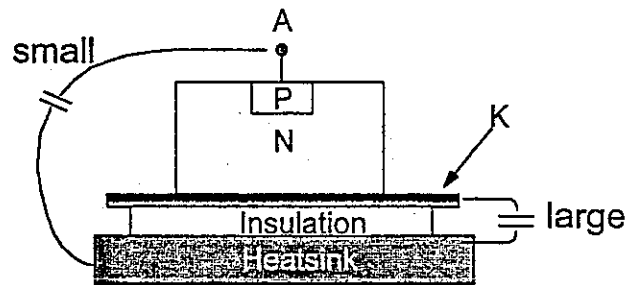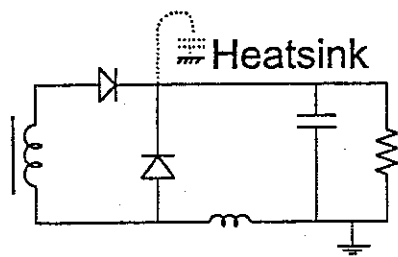



- Tie diode package to AC ground
- Use snubber to reduce ringing
- Use soft diodes

Reducing CM EMI


Transformer Effects

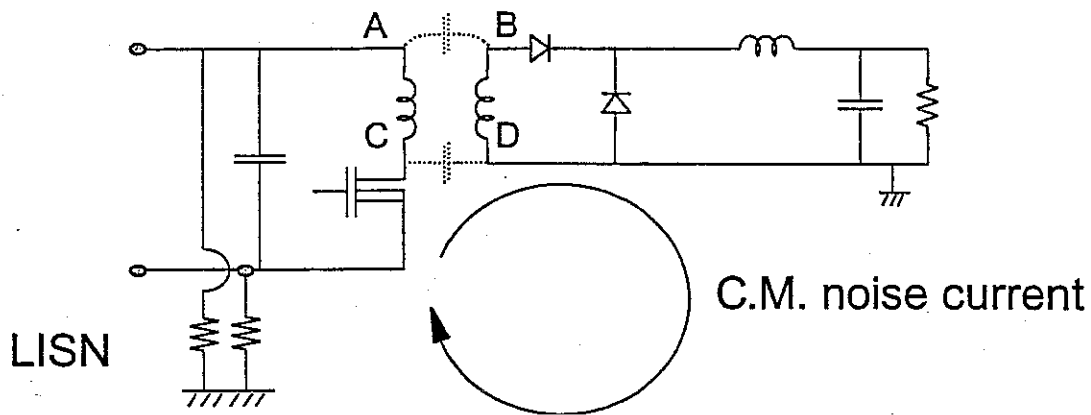

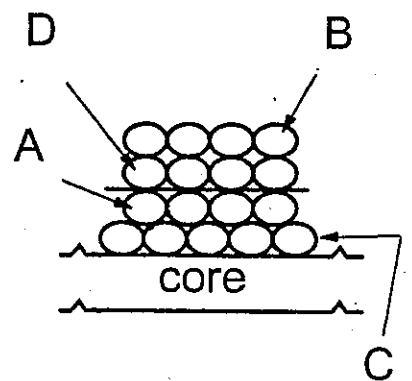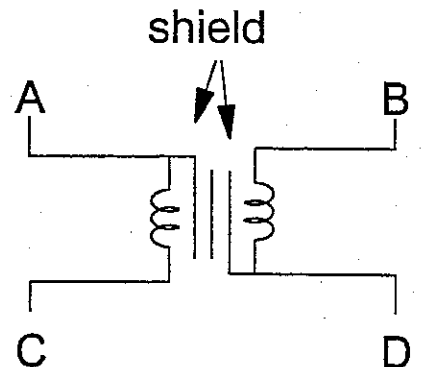
- Use shield (expensive)
- Tie sheilds to AC ground
- If shields are not used, wind the turns such that A and D are close to each other




Transformer Shield Construction

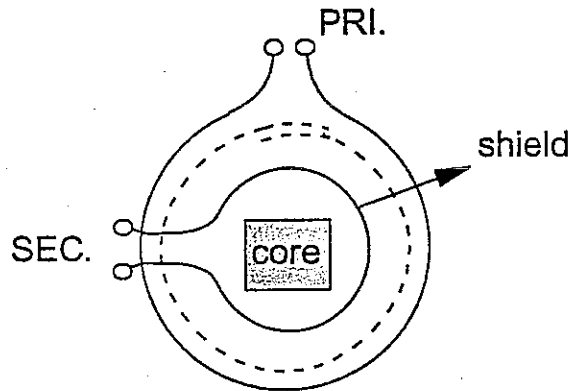


shield must not form a closed loop !!

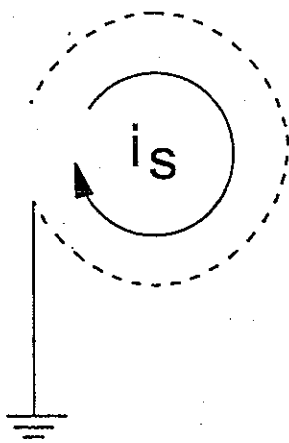

(A)

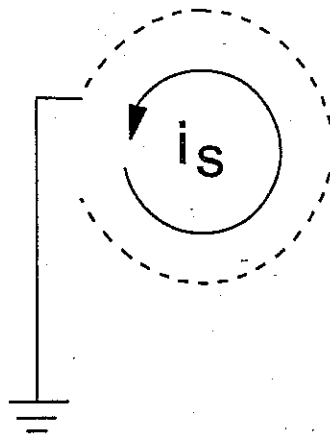

(B)

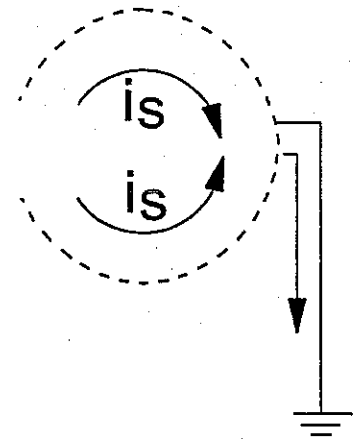


(C)

- Case (c) is best because $\sum Ni = 0$
 \Rightarrow does not affect magnetic coupling
- Keep ground wire impedance small

Inductance of Conductors


$$L = \frac{\Phi}{I}$$

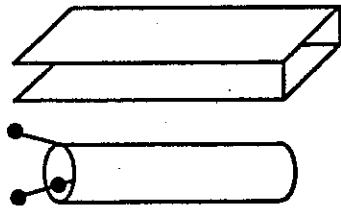


0.01 μ H



0.03 μ H
(20 twists)

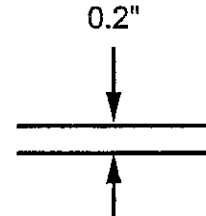


0.15 μ H

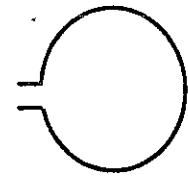

1 μ H
(#22 wire)




* All for 6" long

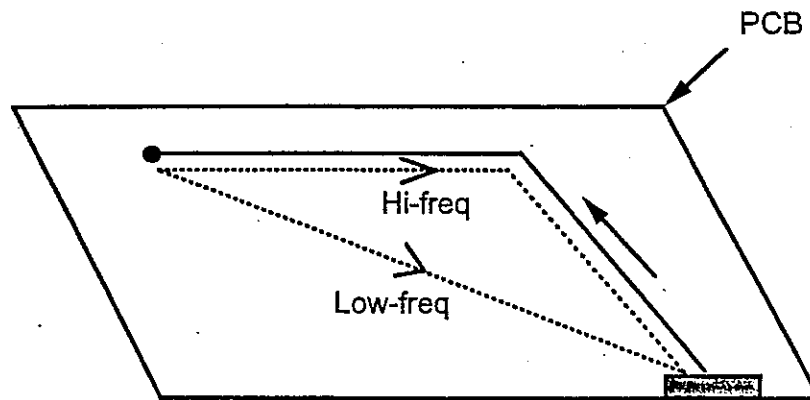High-Frequency Current Path in a Conducting Plane



conducting plane on reverse side



Radiation Coupling

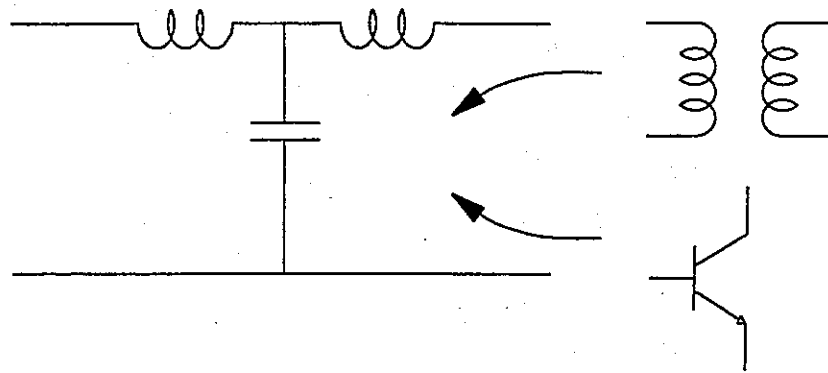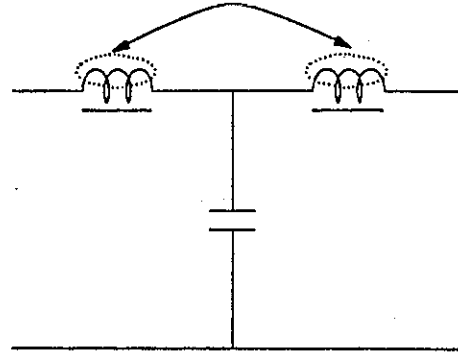
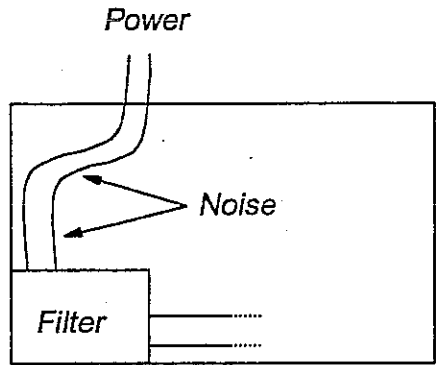


Symptoms: Measured EMI not affected by
changing filter component

Possible Cures: Rearranging layout, shielding
Reducing wire loop

Radiation Coupling to Conducted EMI

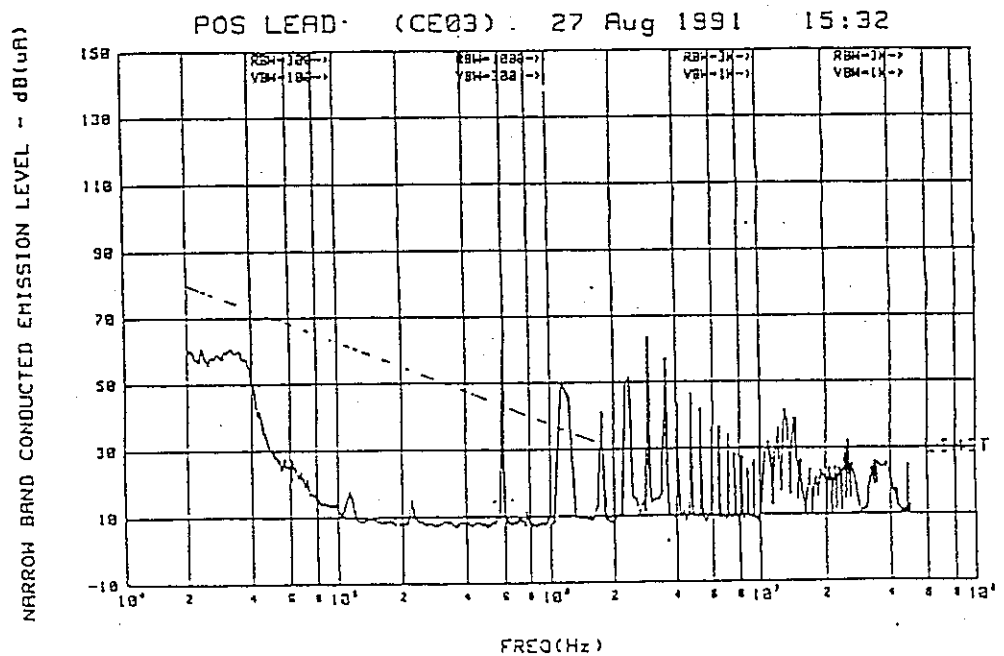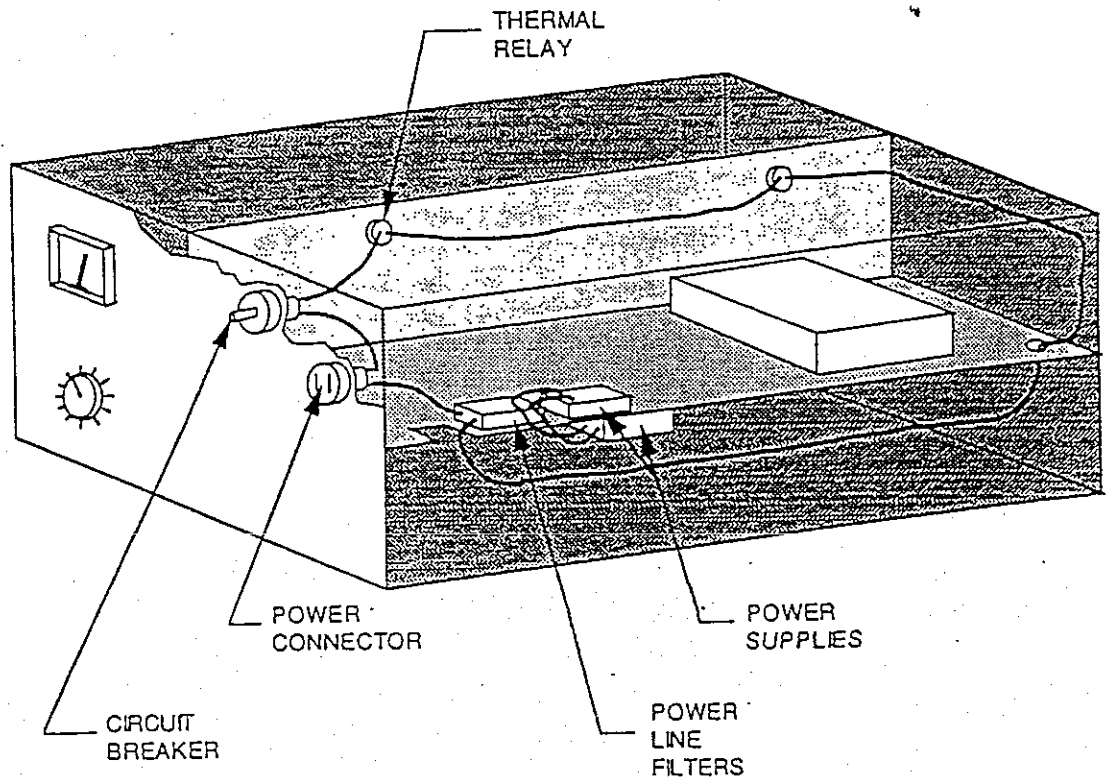


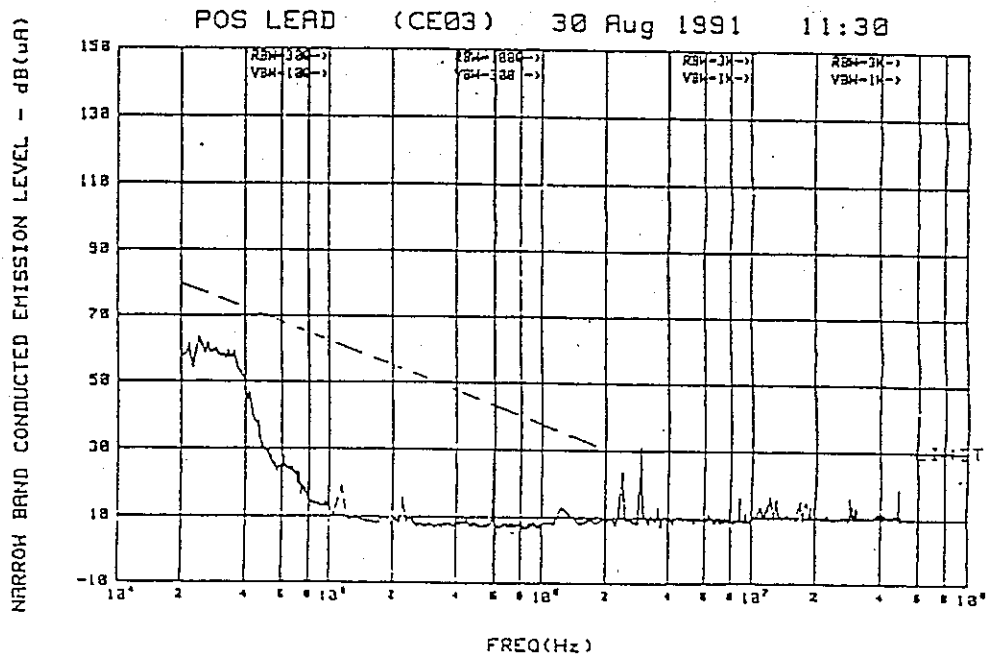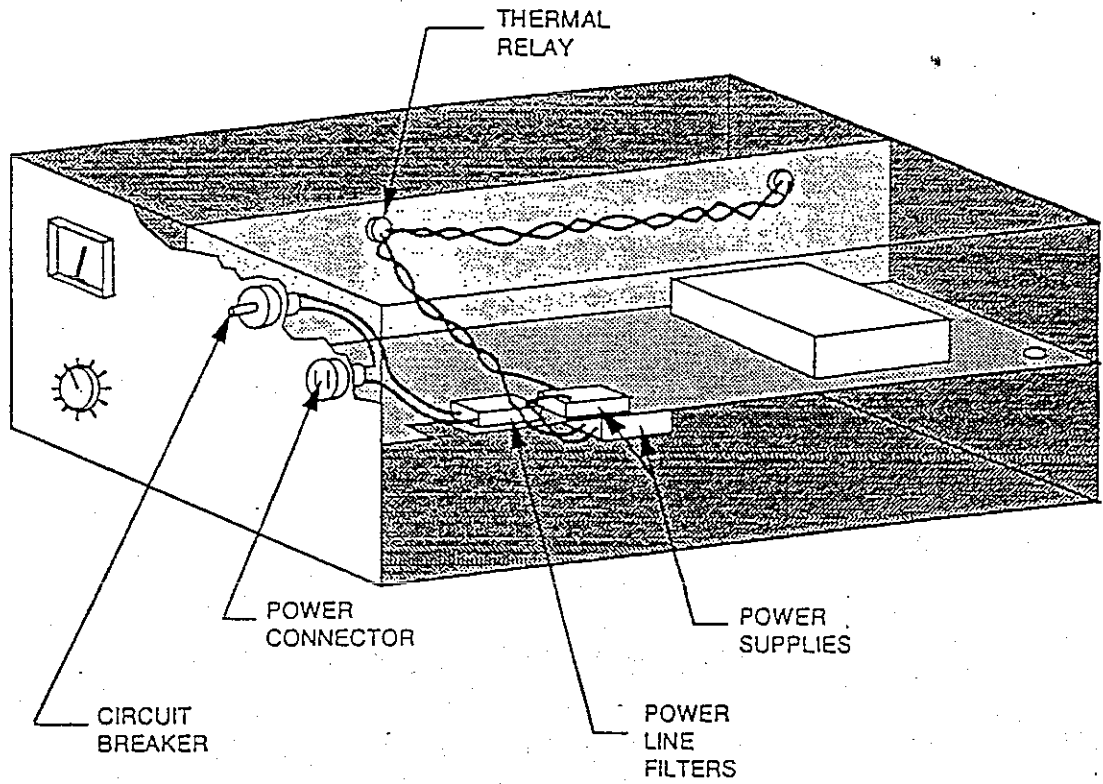

六、EMI 濾波器

(EMI Filters)





Filter Attenuation

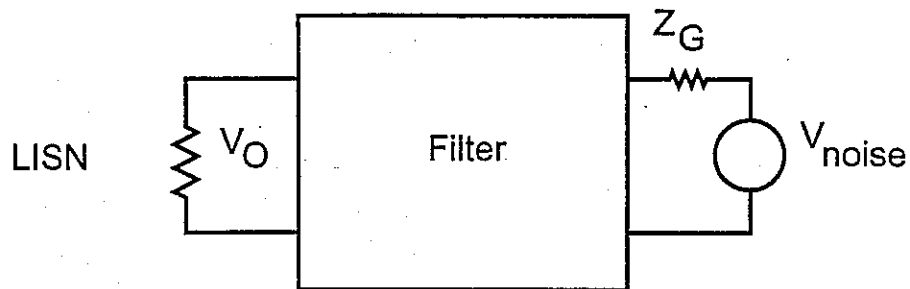





$$Ad_B = 20 \log \frac{(V_O) \text{ w/o filter}}{(V_O) \text{ with filter}}$$

- Ad_B depends not only on the filter used but also on noise-source impedance and LISN impedance.
- $Ad_B \uparrow$ as impedance mismatch \uparrow
- Commercial filter attenuation obtained in a $50\Omega - 50\Omega$ system.


Effectiveness of a Filter

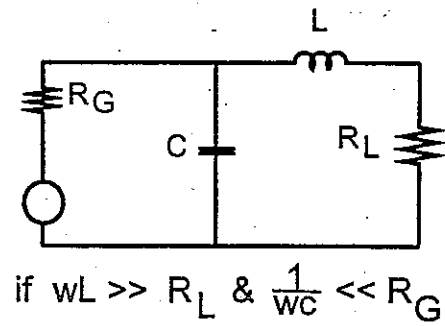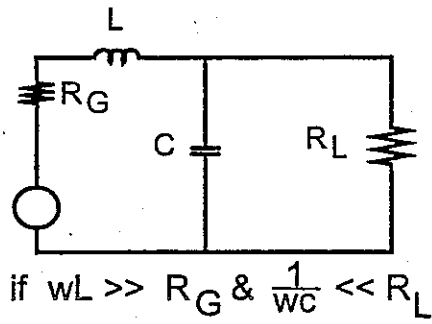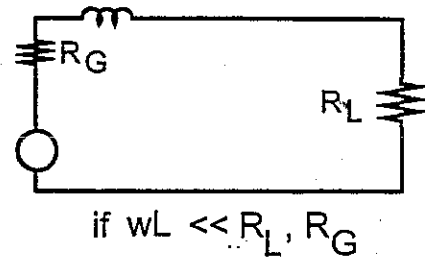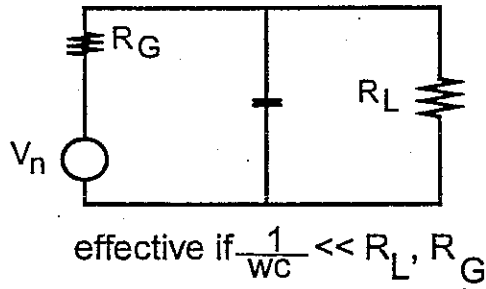


Higher-Order Filters

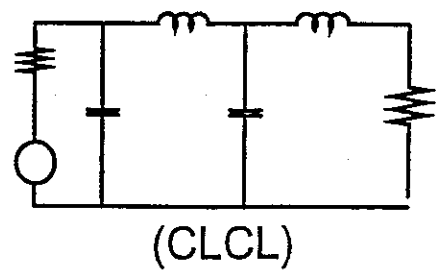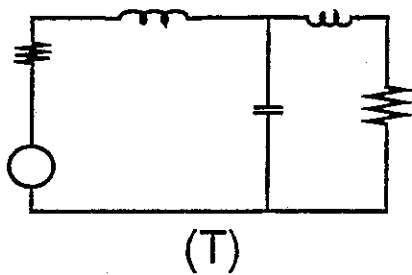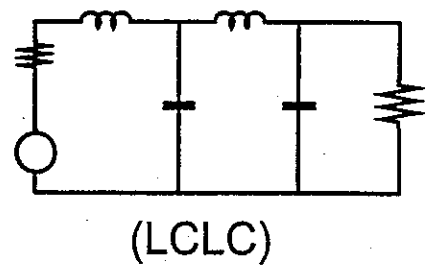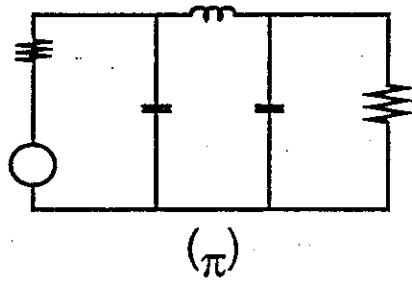


Impedance Effects on Filter Attenuation

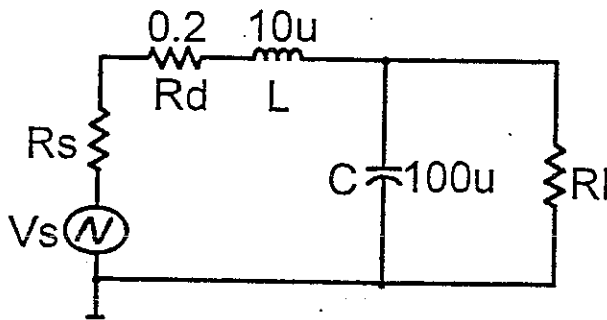


Filter Type A

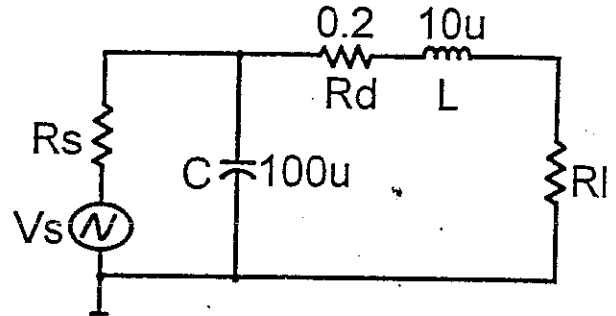


Filter Type B

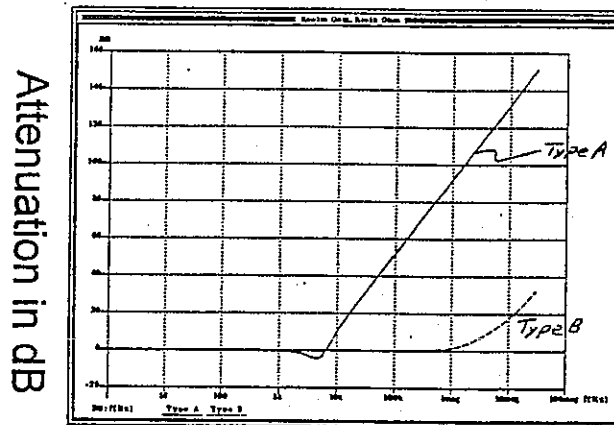

Frequency in Hz
Rs=1m Ohm, RI=1K Ohm



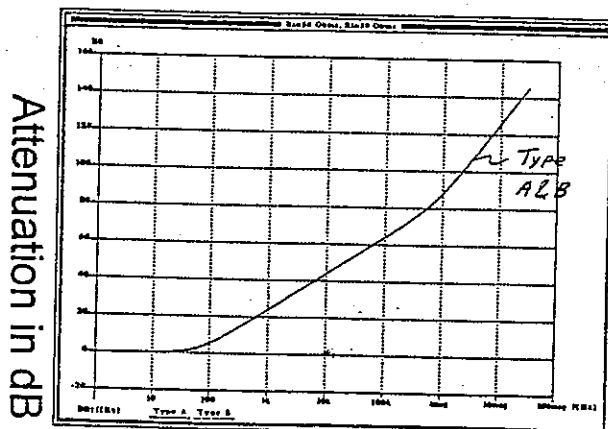


Frequency in Hz
Rs=RI=50 Ohm

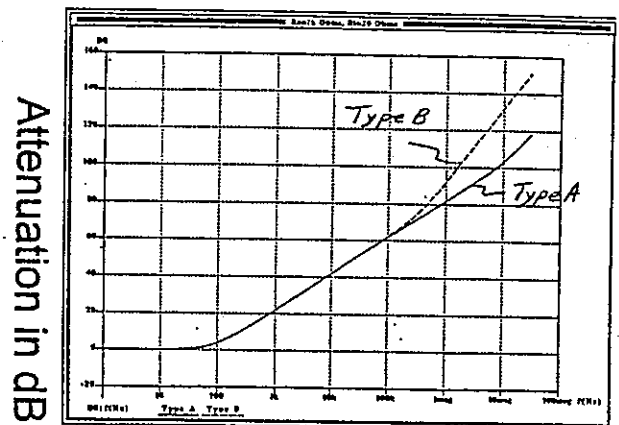

Frequency in Hz
Rs=1K Ohm, RI=20 Ohm

Noise Source Impedance

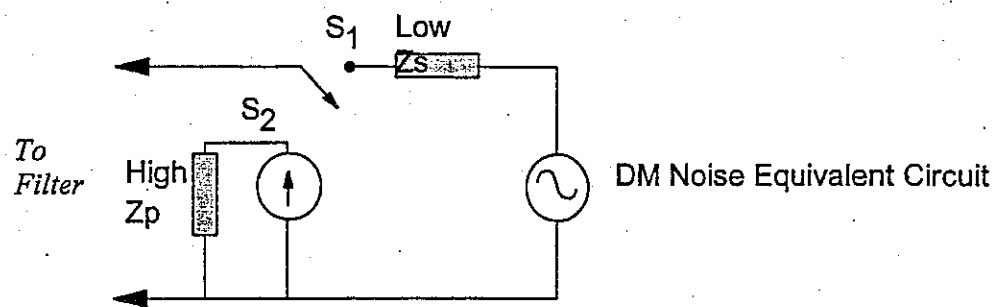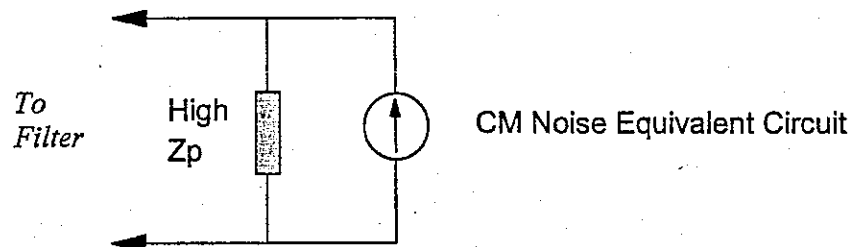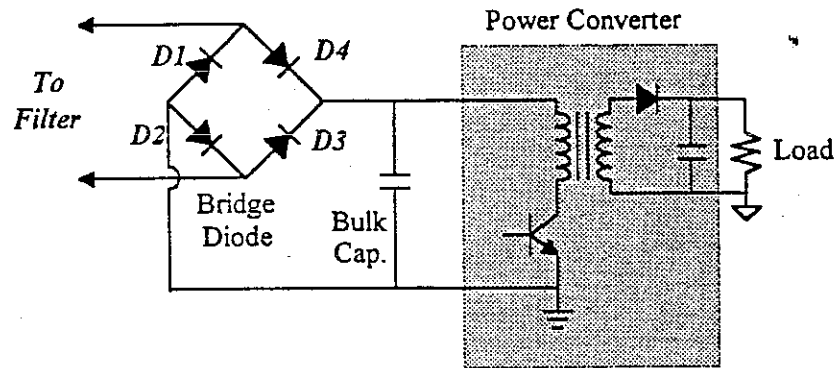


When rectifier diodes "on" \rightarrow S_1 "on", S_2 "off"

When rectifier diodes "off" \Rightarrow S_1 "off", S_2 "on"

- Practically difficult to measure*


* Ref [2]

Experimental Source Impedance

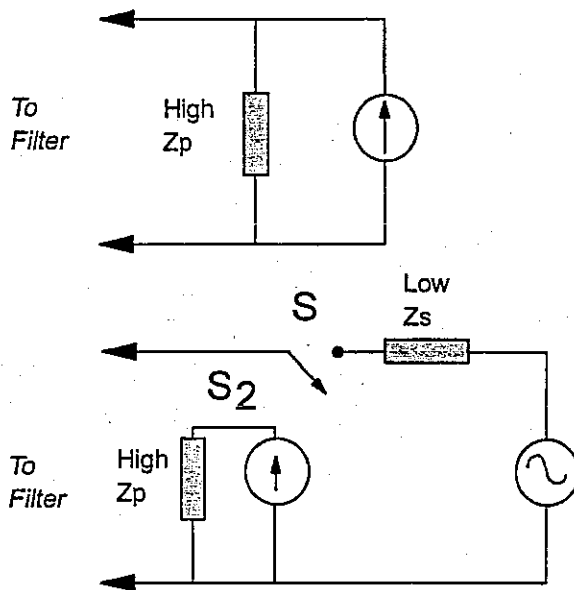


CM:

Z_p :

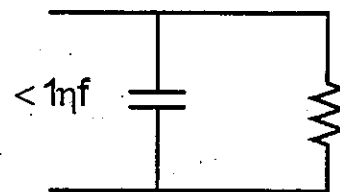


DM:

Z_s :

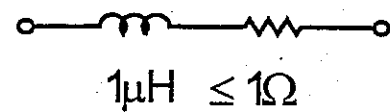




Z_p :

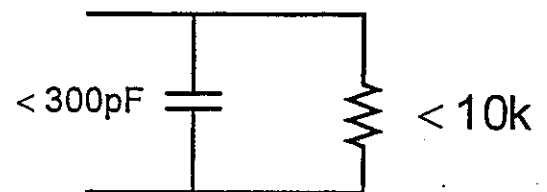




* For Power Supplies 50-500 Watts

*Ref [2], [3]

A Commonly-Used Filter Topology

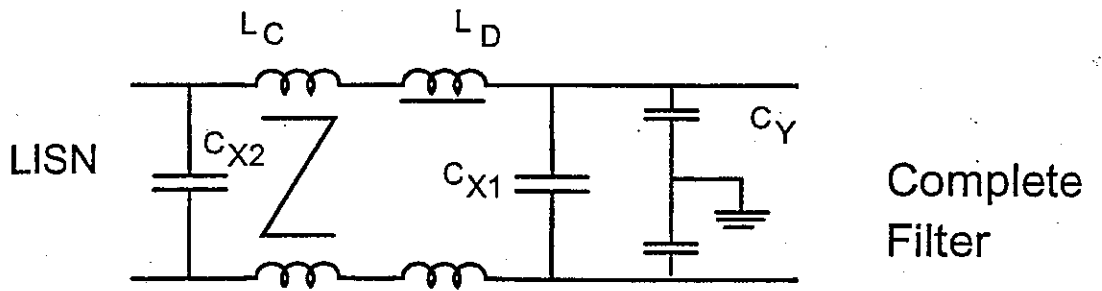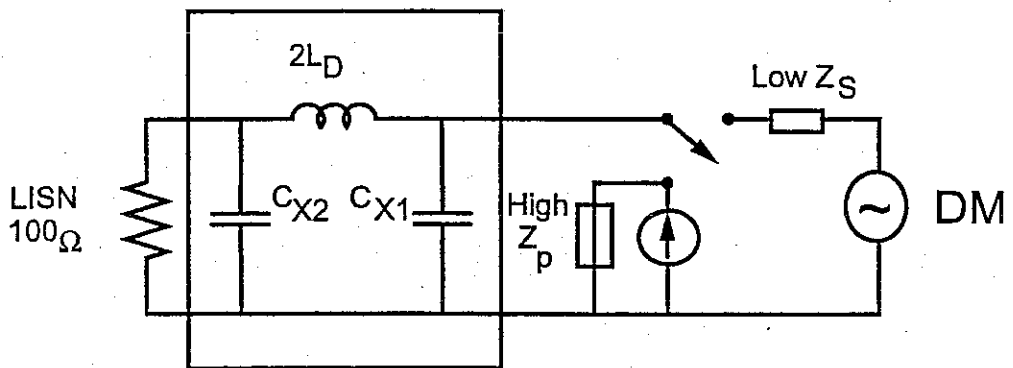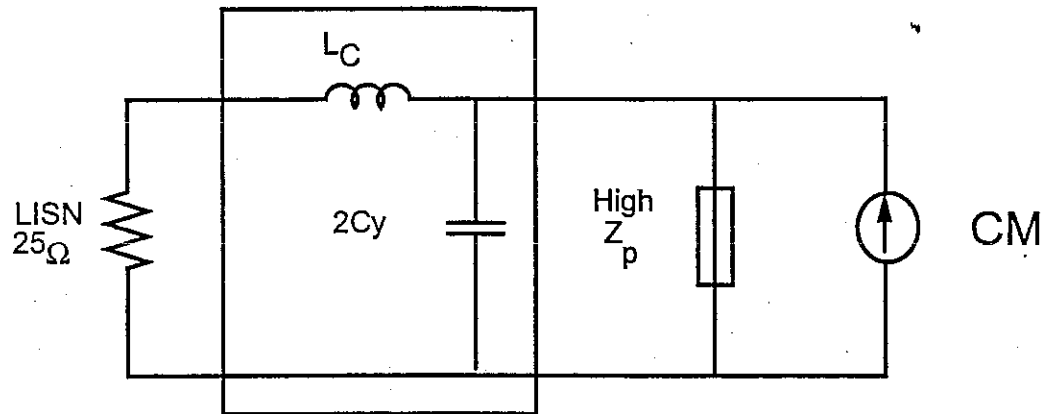


Filter Equivalent Circuits

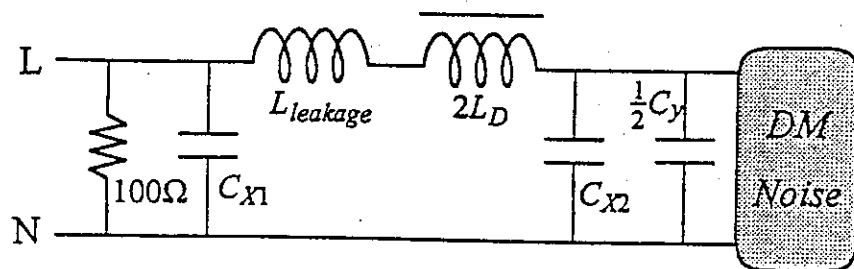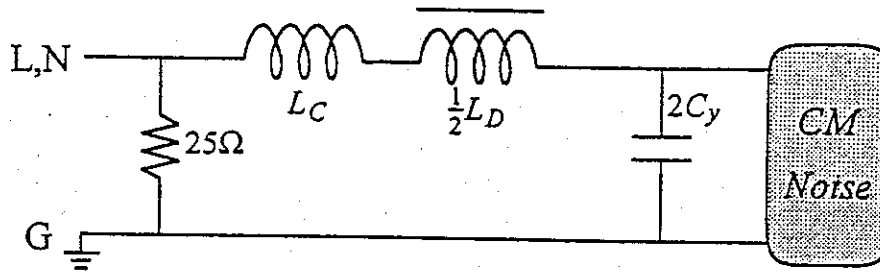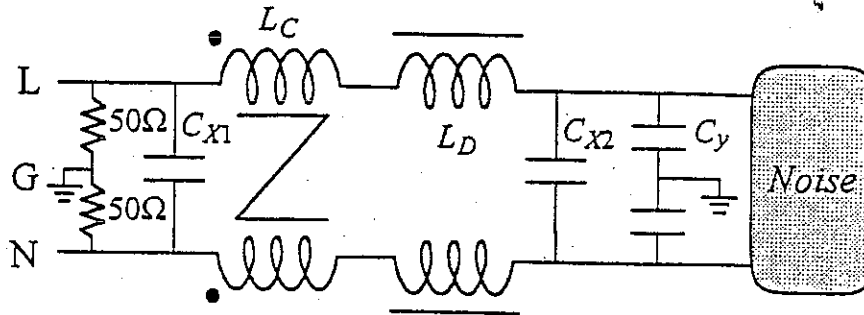

FILTER COMPONENTS

CM Choke (LC)

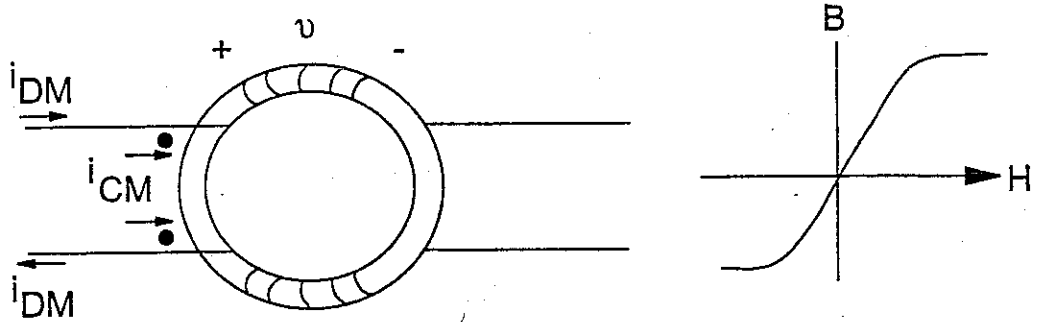


- DM current sees no CM choke

$$\text{Total MMF} = \sum_j N_j i_j = 0 \Rightarrow H = 0$$


$$v = N \frac{d\phi}{dt} = 0$$

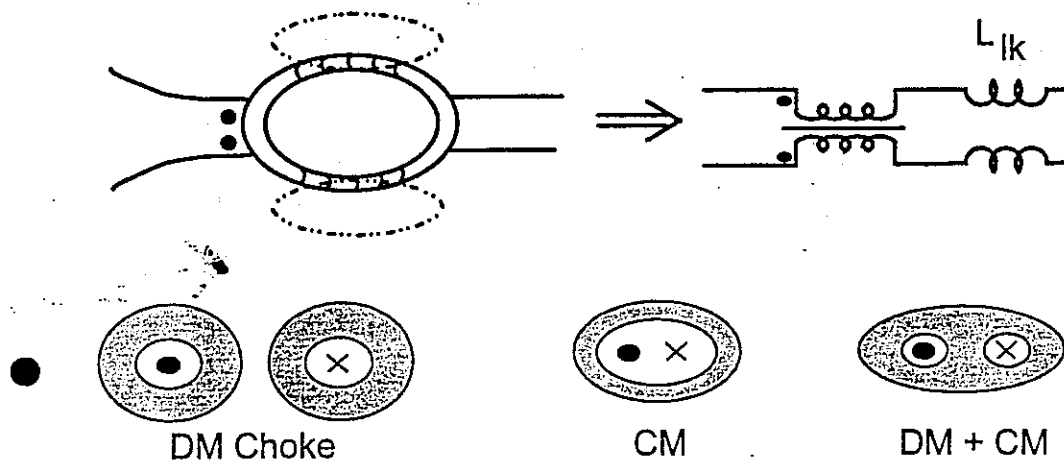- Power (DM) current doesn't saturate the core \Rightarrow Normally, high- μ cores are used
- Leakage inductance becomes DM choke




High-Frequency Effects on Filter Components

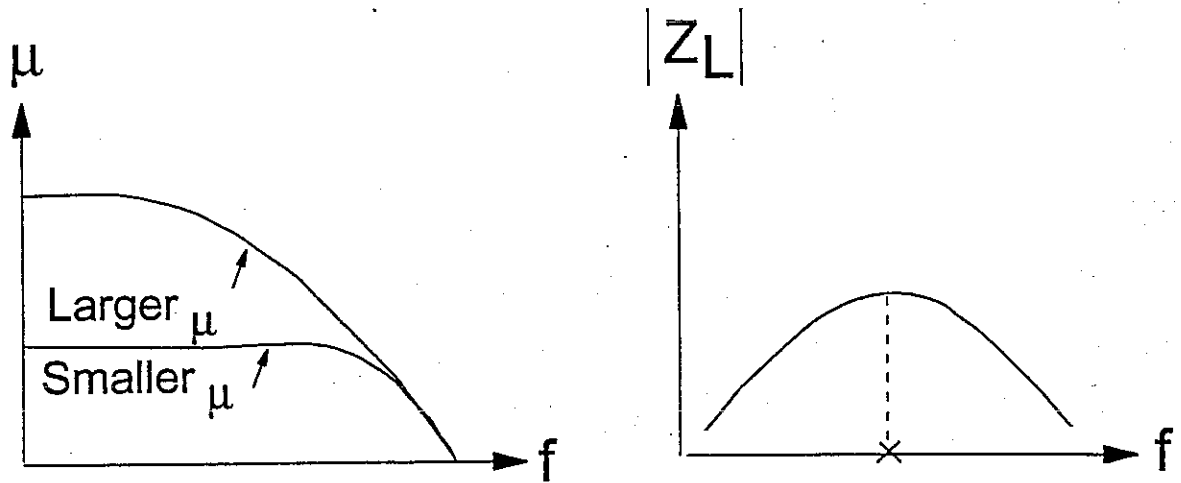- Reduction of inductor impedance due to core permeability reduction and self resonance



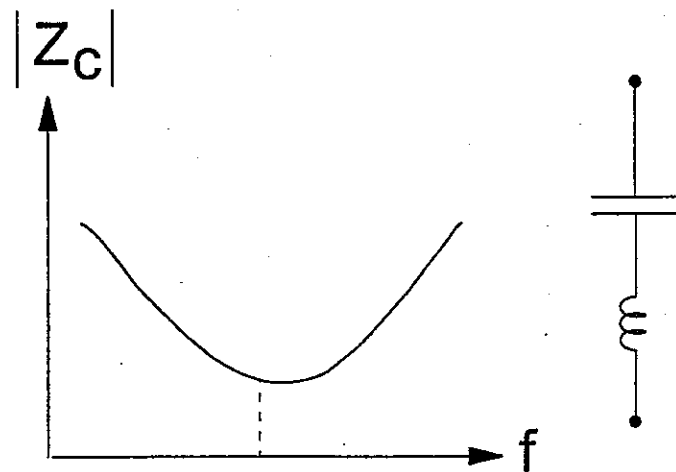- Increase of capacitor impedance due to resonance



七、分離 DM 與 CM 雜訊
(Separation of DM and CM)


Why Separating DM and CM?

- 1. Identify the noise sources.**
- 2. Treat DM and CM individually.**


Conventional Approaches

- 1. Differential Mode Rejection Network (DMRN).**
- 2. Current probe.**
- 3. High Performance Differential Amplifier.**

Using Noise Separator

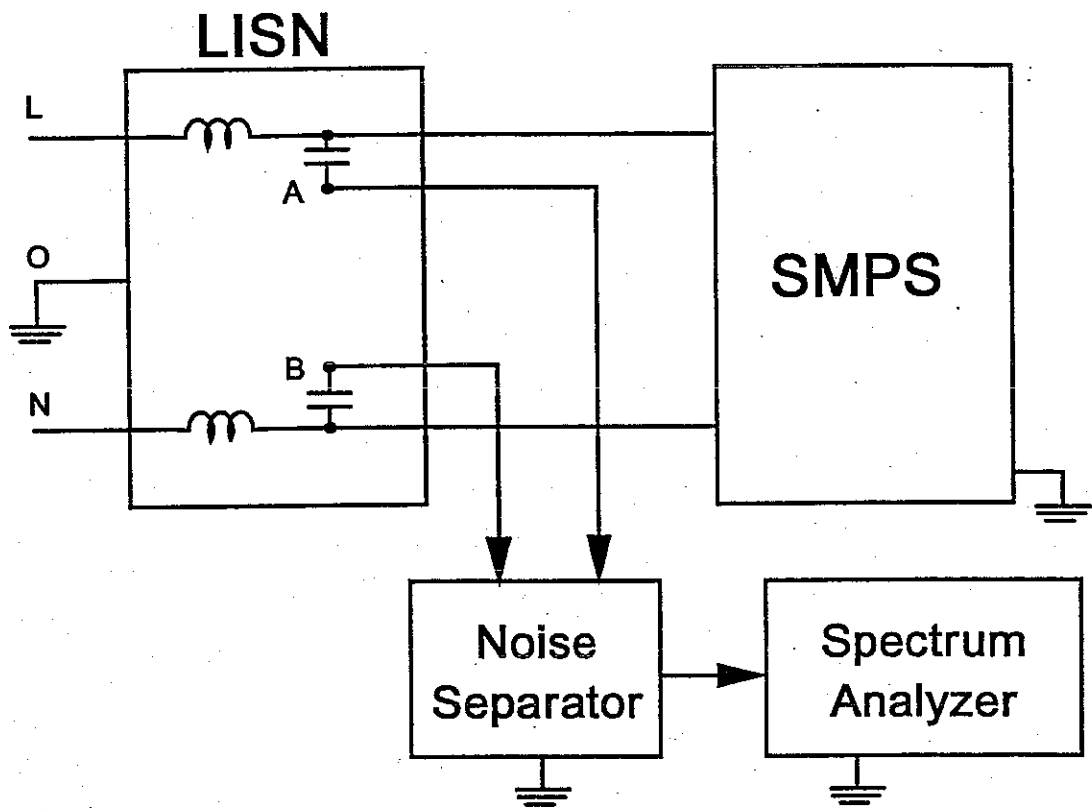


Basic Principle of Noise Separation

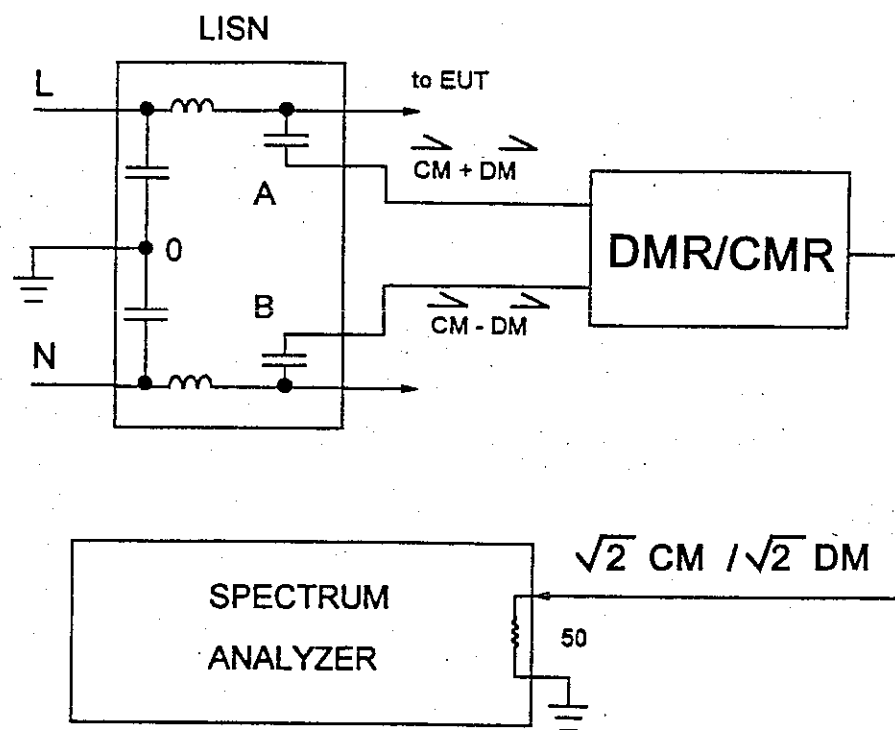



- DMR: 0° power combiner
- CMR: 180° power combiner

Measurement of Rejection of DMR

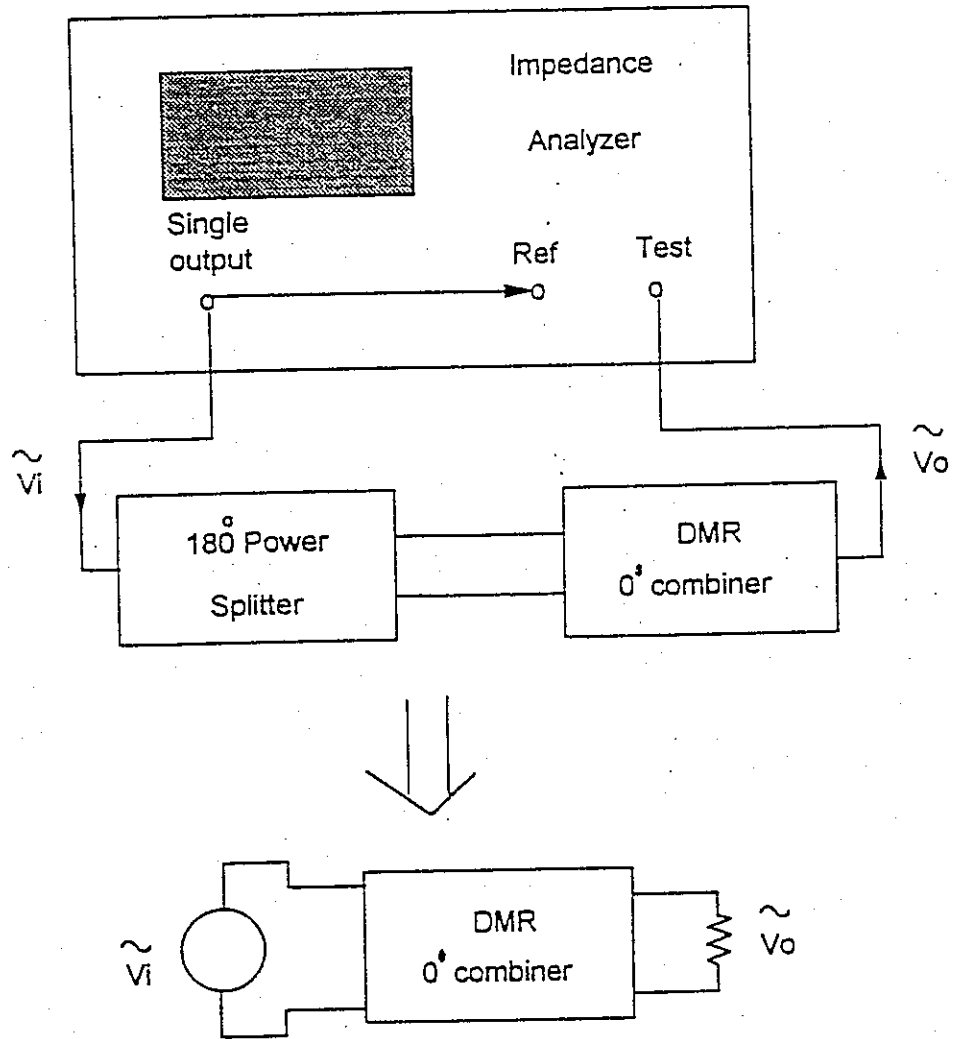


Measurement of Rejection of CMR

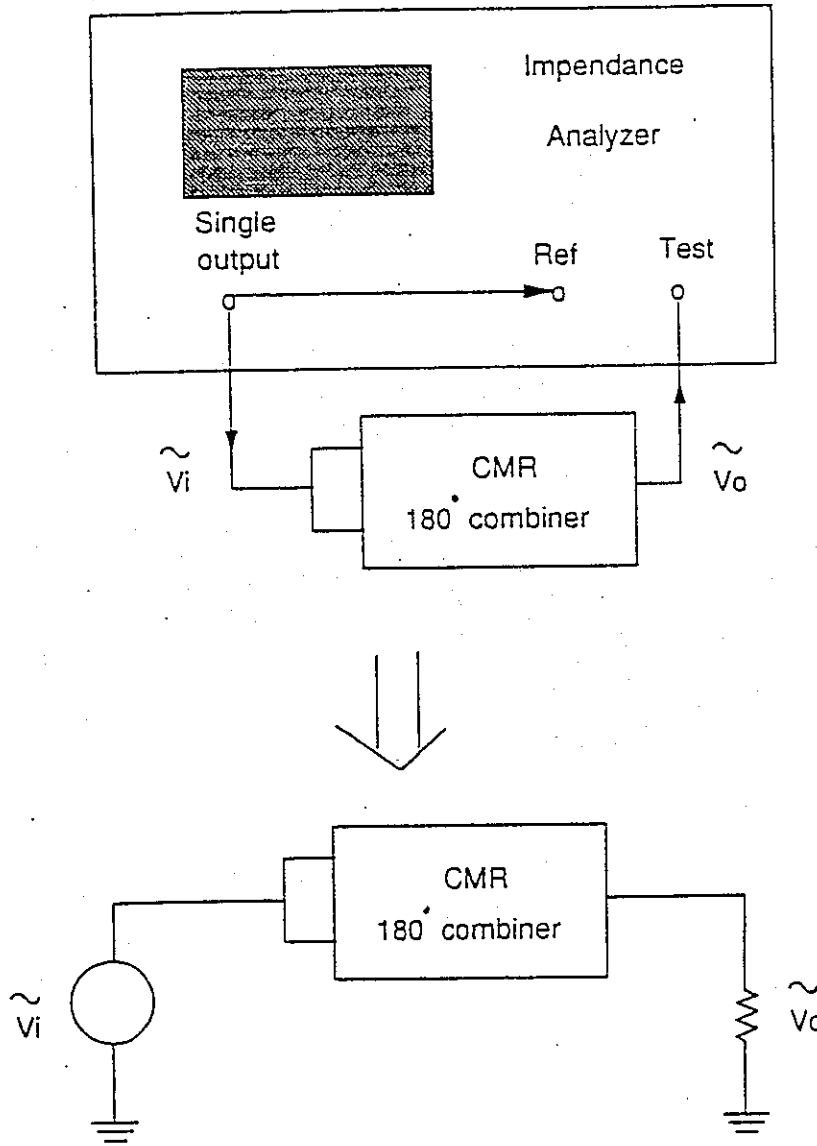

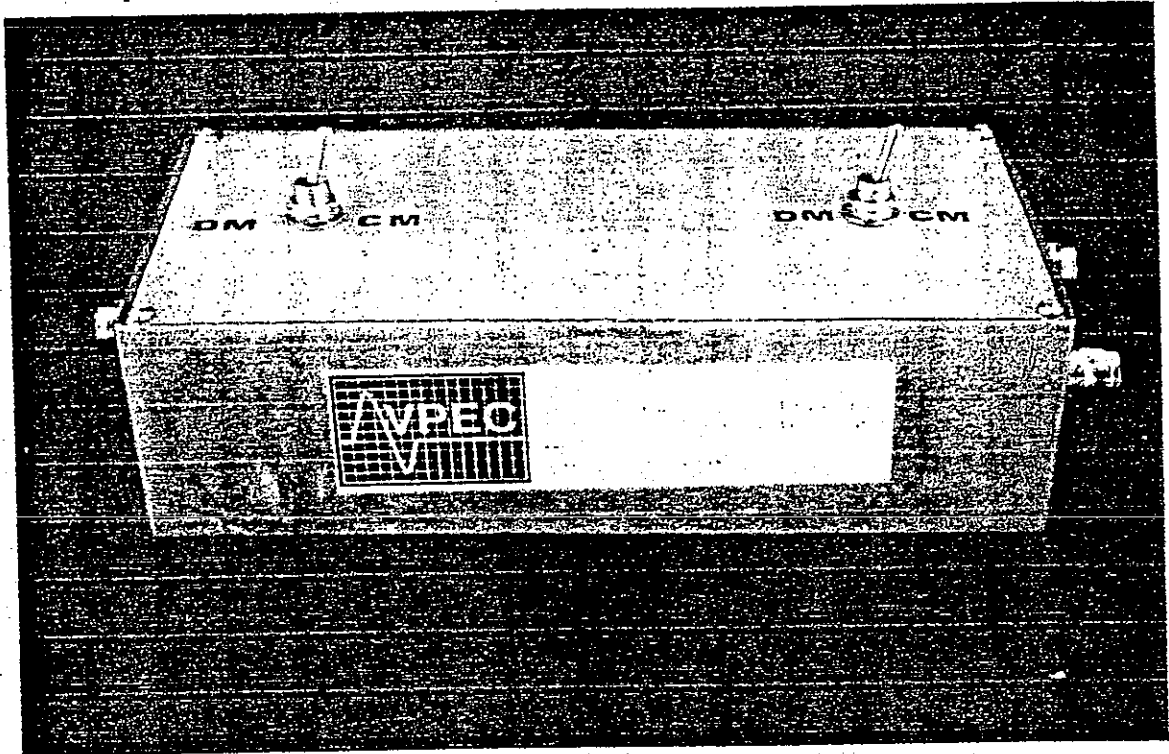

Test Result of CMR Rejection

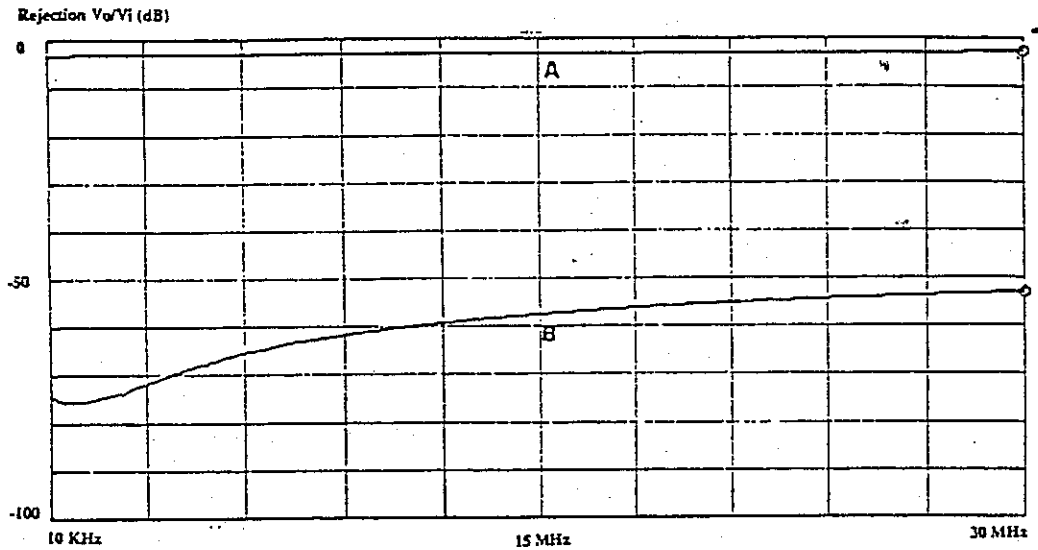

A: V_i

B: V_o

Test Result of DMR Rejection

