

## 八、用分離器診斷傳導性 EMI (Diagnosis Using Separator)

# Tests Using a Noise Separator

Test # 2: "Tests Using Noise Separator"

Test # 1: No filter is inserted.

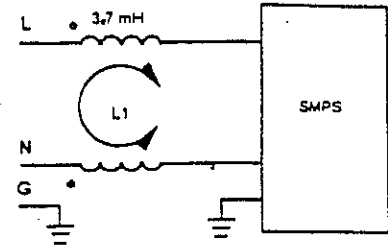


Figure 6(a) Test 2 Diagram

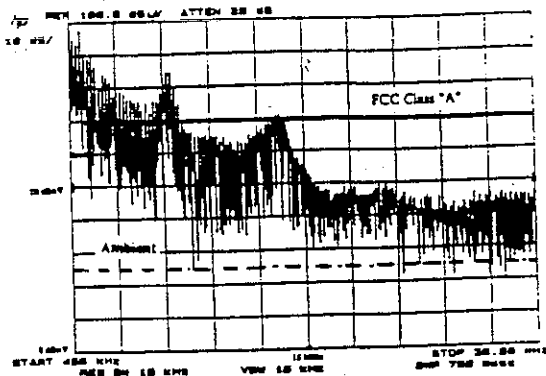


Figure 5(a) Total Noise

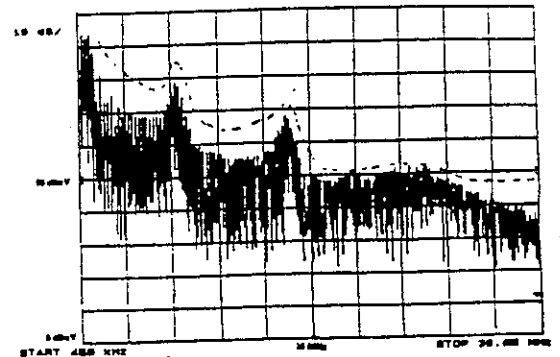


Figure 6(b) Total Noise

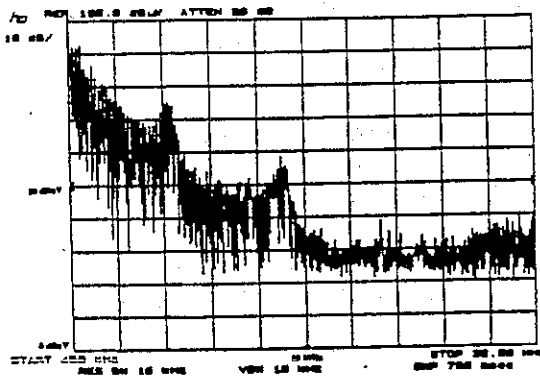


Figure 5(b) DM Noise

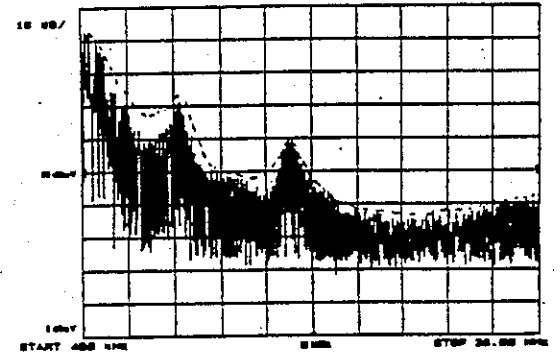


Figure 6(c) DM Noise

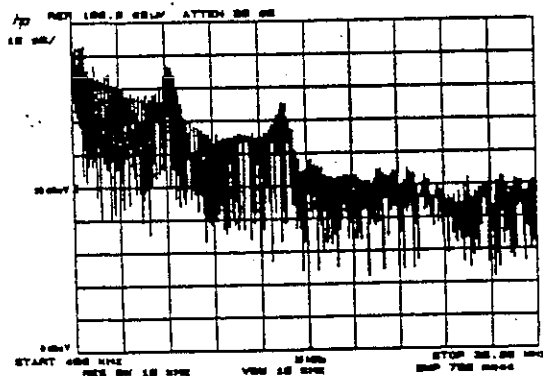


Figure 5(c) CM Noise

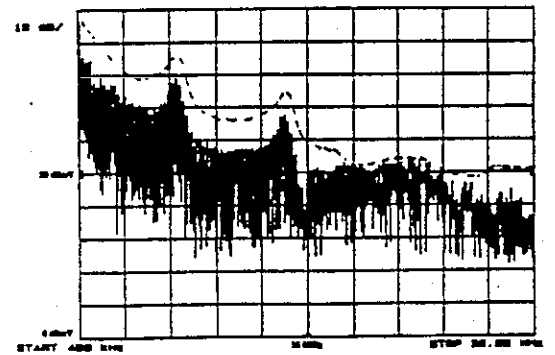


Figure 6(d) CM Noise

Test # 3:

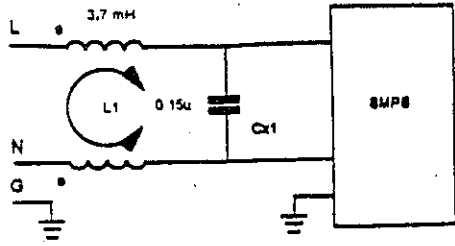


Figure 7(a) Test 3 Diagram

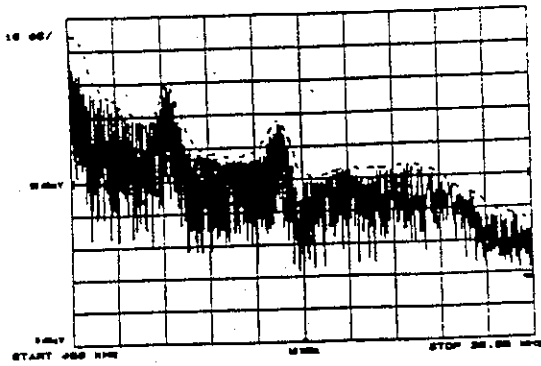


Figure 7(b) Total Noise

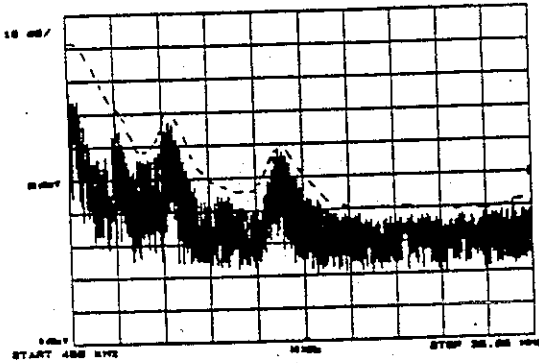


Figure 7(c) DM Noise

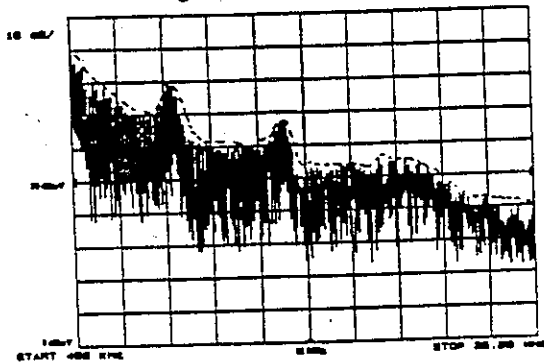


Figure 7(d) CM Noise

Test # 4:

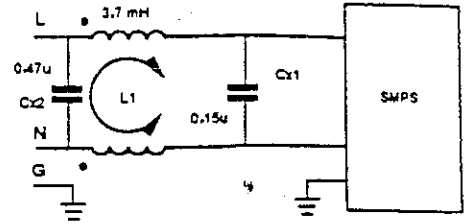


Figure 8(a) Test 4 Diagram

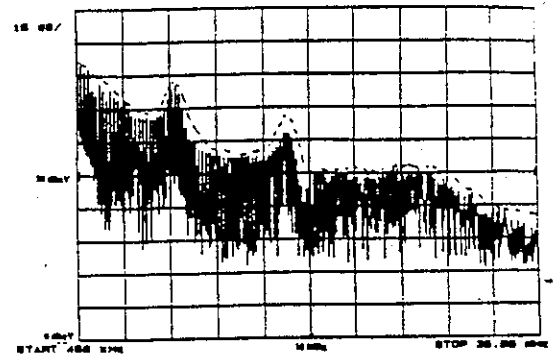


Figure 8(b) Total Noise

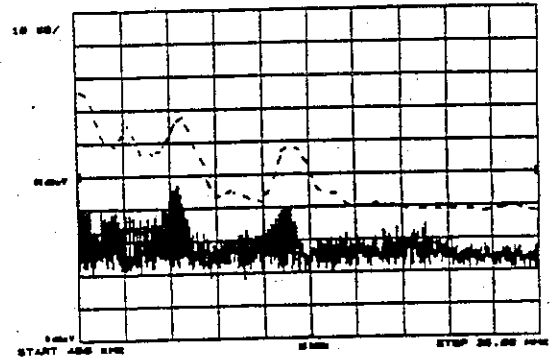


Figure 8(c) DM Noise

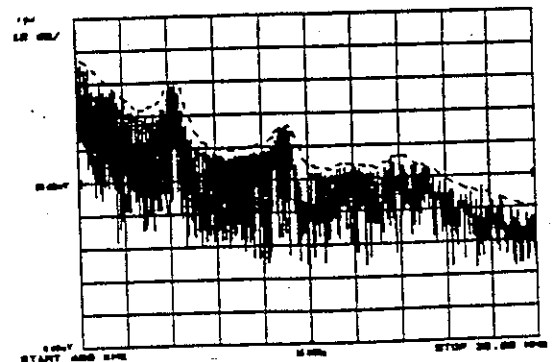


Figure 8(d) CM Noise

Test # 5:

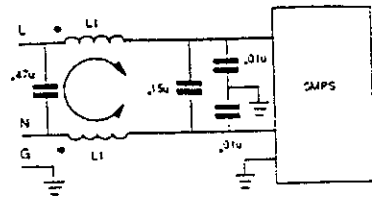


Figure 9(a) Test 5 Diagram

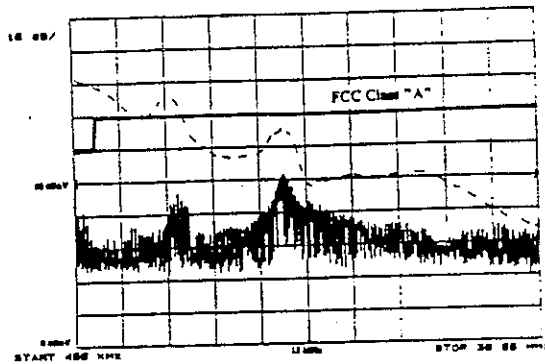


Figure 9(b) Total Noise

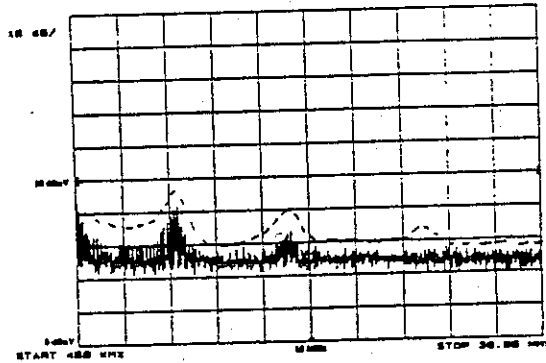


Figure 9(c) DM Noise

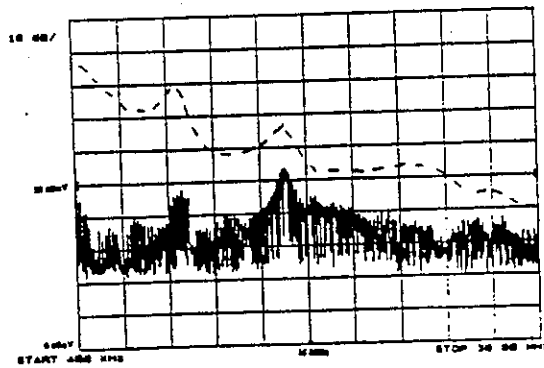


Figure 9(d) CM Noise

Test # 6:

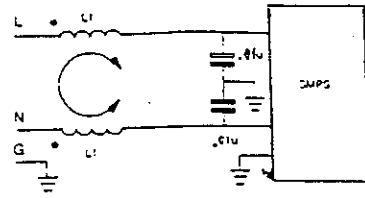


Figure 10(a) Test 6 Diagram

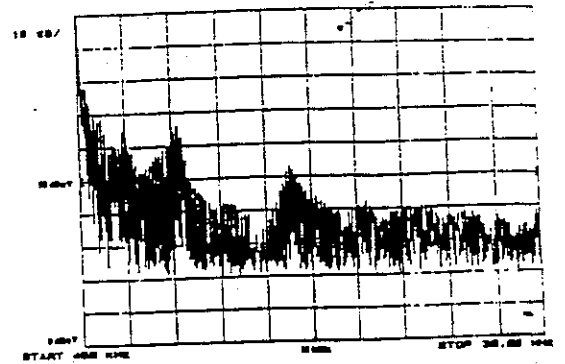


Figure 10(b) Total Noise

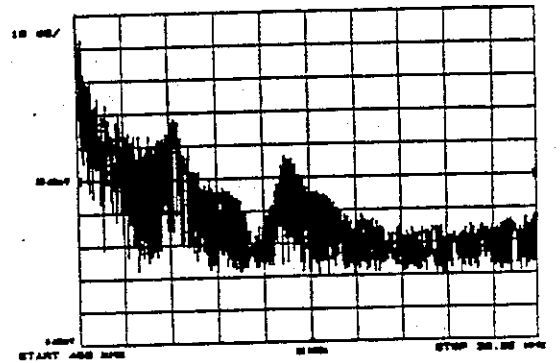


Figure 10(c) DM Noise

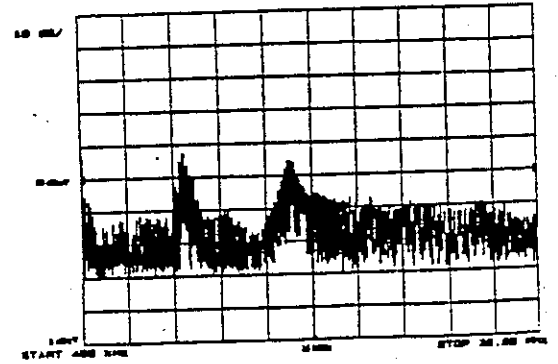


Figure 10(d) CM Noise

Test # 7:

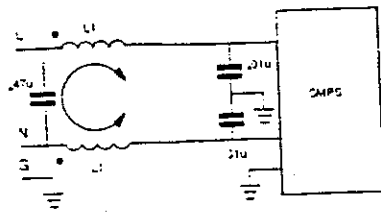


Figure 11(a) Test 7 Diagram

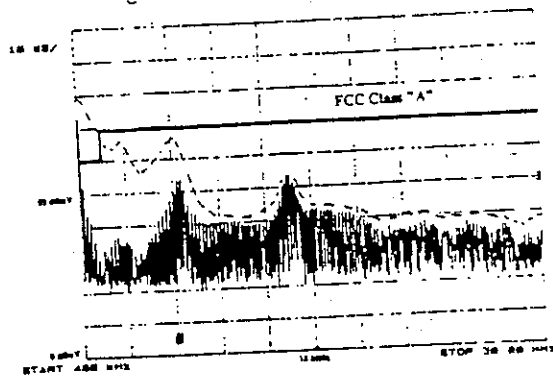


Figure 11(b) Total Noise

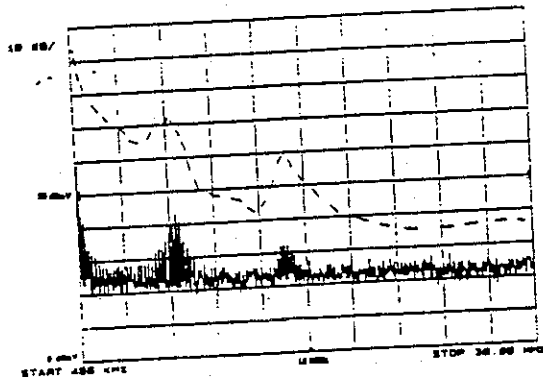


Figure 11(c) DM Noise

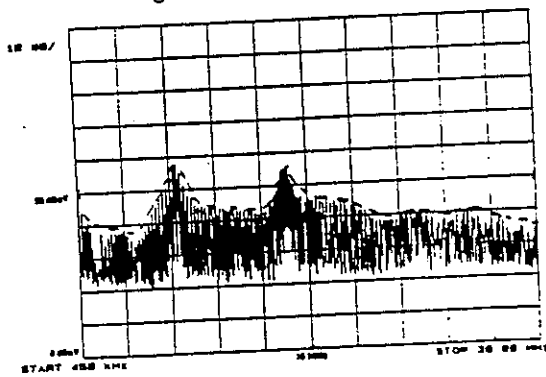


Figure 11(d) CM Noise

Test # 8:

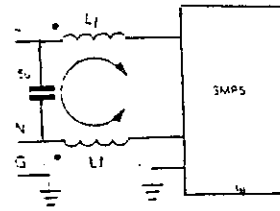


Figure 12(a) Test 8 Diagram

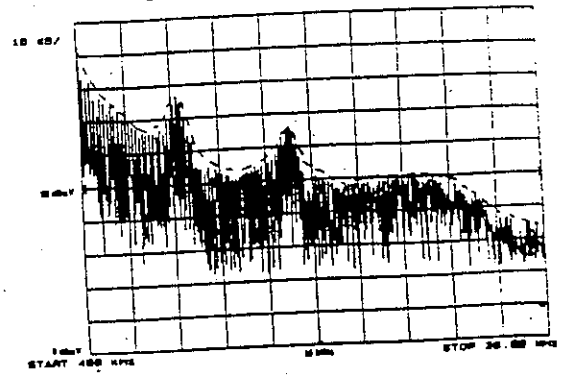


Figure 12(b) Total Noise

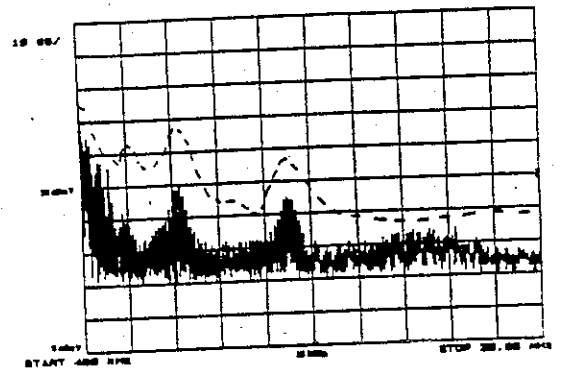


Figure 12(c) DM Noise

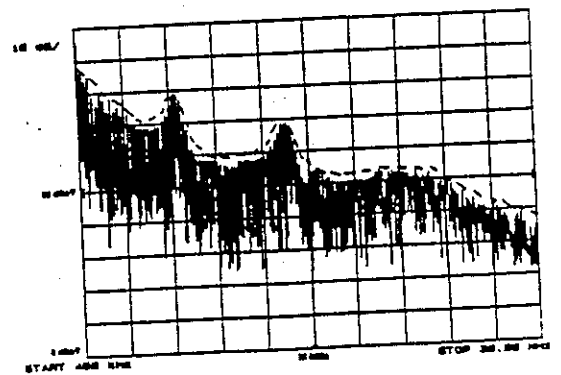


Figure 12(d) CM Noise

Test # 9:

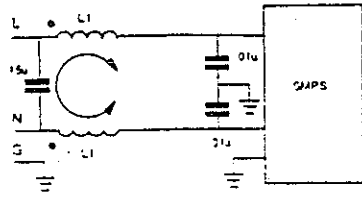


Figure 13(a) Test 9 Diagram

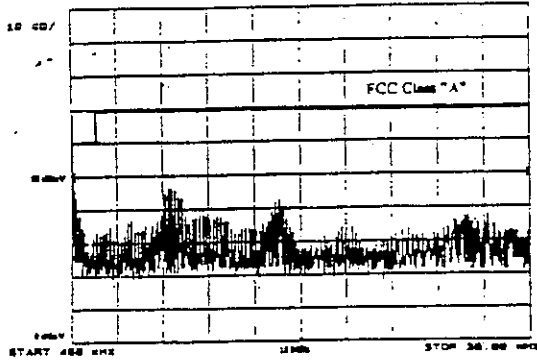


Figure 13(b) Total Noise

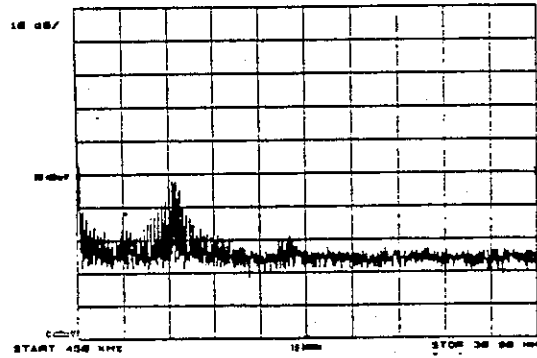


Figure 13(c) DM Noise

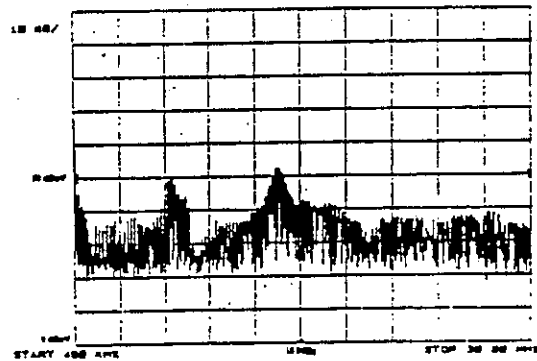


Figure 13(d) CM Noise

Test # 10:

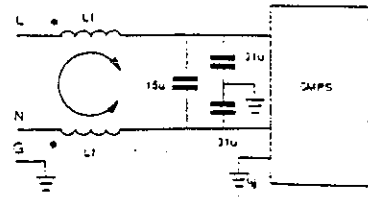


Figure 14(a) Test 10 Diagram

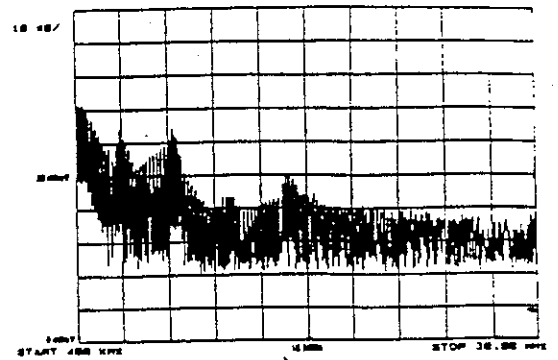


Figure 14(b) Total Noise

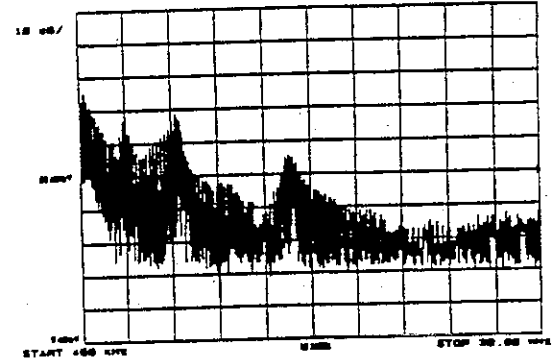


Figure 14(c) DM Noise

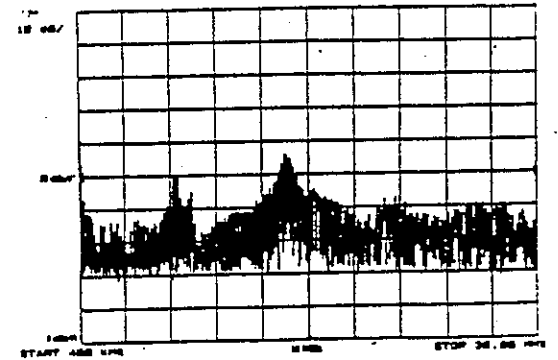


Figure 14(d) CM Noise

## Difficulties of EMI Filter Design

- Base-line (no filter) EMI unknown without measurement
- Noise source impedance unknown
- High-frequency effects difficult to predict


# 九、濾波器設計

## (Filter Design)





# Filter Design Flow Chart

## Block I

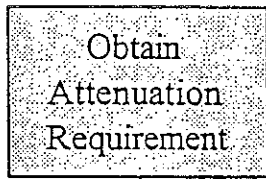


## Block II

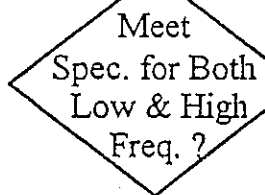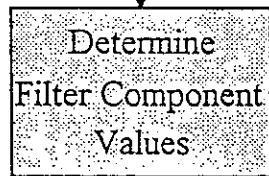


Yes

END

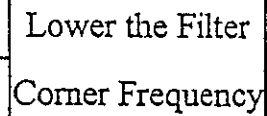


Yes


No

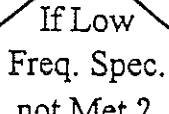


## Block III

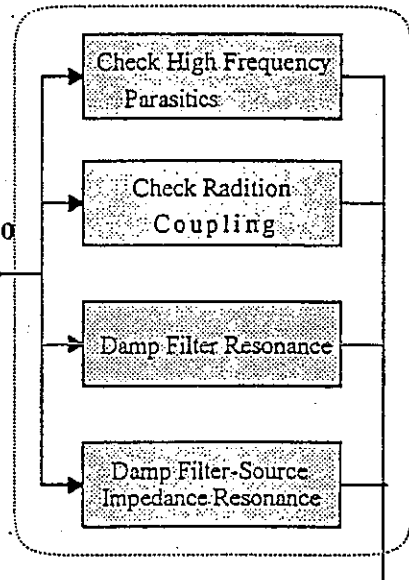


# Filter-Source Impedance Resonance

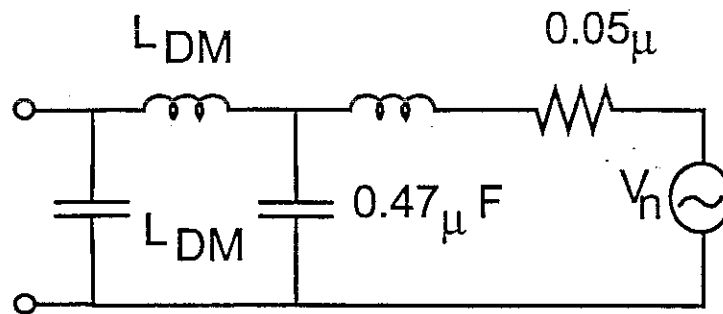



Attenuation

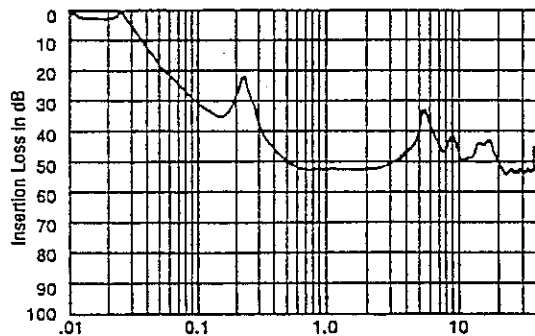

EMI

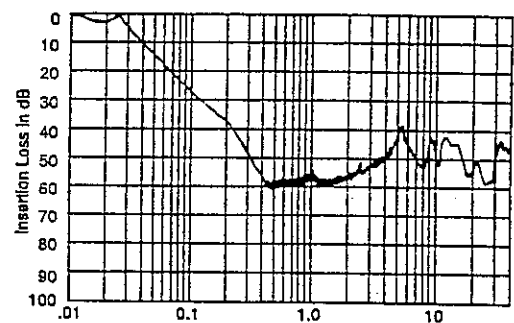

Before damping

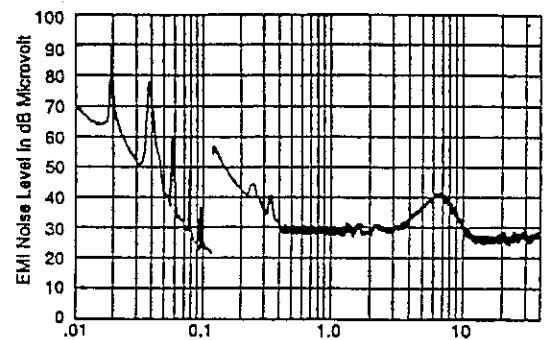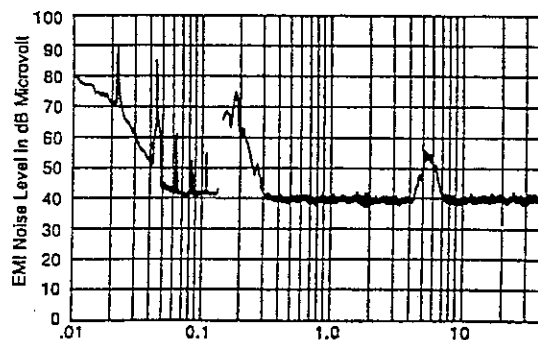

After damping

\*Permission fro Mark Nave, EMC Service

# A Procedure for Determining Filter Component Values

Step 1: Measure base-line (i.e. without filter) common-mode EMI noise ( $V_{CM}$ ) and differential-mode EMI noise ( $V_{DM}$ ) using a Noise Separator.



Step 2: Determine CM attenuation requirement  $V_{req,C}$  and DM attenuation requirement  $V_{req,DM}$

$$(V_{req,CM})_{dB} = (V_{CM})_{dB} - (V_{Limit})_{dB} + 3dB$$

$$(V_{req,DM})_{dB} = (V_{DM})_{dB} - (V_{Limit})_{dB} + 3dB$$

where  $(V_{CM})_{dB}$  and  $(V_{DM})_{dB}$  are obtained from Step 1.
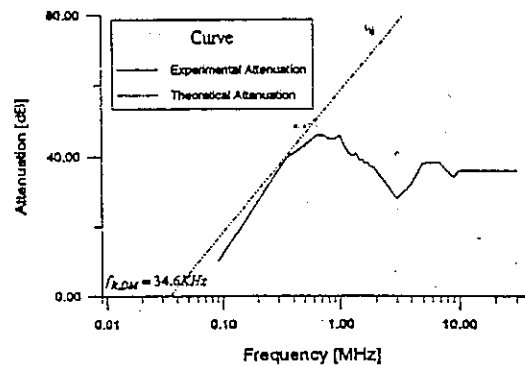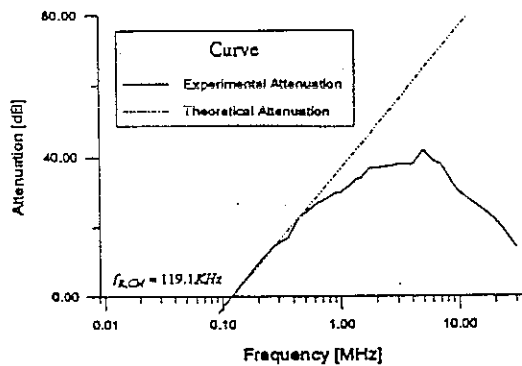
## Step 4: Determine filter corner frequencies.



## Step 4: Determine filter component values.

- (a) CM component  $L_C$  and  $C_Y$   
 $C_Y$  is determined by leakage current requirement

$$L_C = \left( \frac{1}{2\pi \cdot f_{R,CM}} \right)^2 \cdot \frac{1}{2 \cdot C_Y} \quad \dots \text{Eq.(1)}$$

- (b) DM component  $L_D$ ,  $C_{X1}$  and  $C_{X2}$



$$C_{X1} = C_{X2} = C_{DM} = \left( \frac{1}{2\pi \cdot f_{R,DM}} \right)^2 \cdot \frac{1}{L_{DM}} \quad \dots \text{Eq.(2)}$$

Converter - filter interaction should be taken into consideration in choosing  $L_{DM}$  and  $C_D$



# Design Example 1

Example 1: Design an EMI filter for an off-line (90V-260V) flyback converter switching power supply (90kHz, 43w output), to meet a VDE limit. For proper margin, under 6dB limit is used in the design.

## Step 1: Base Line EMI Measurement

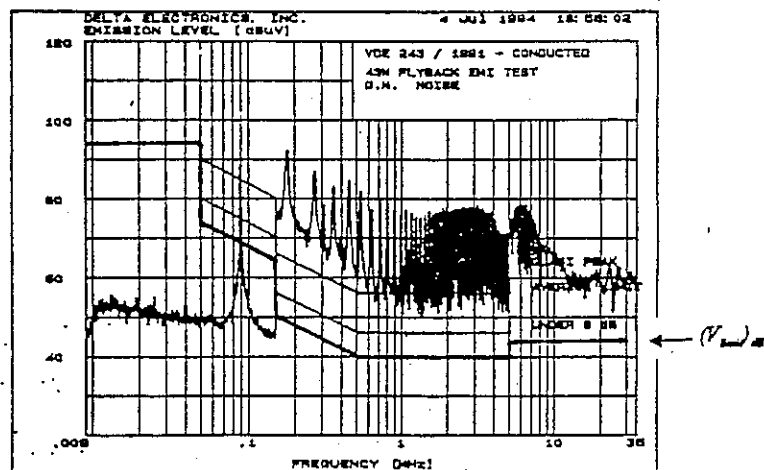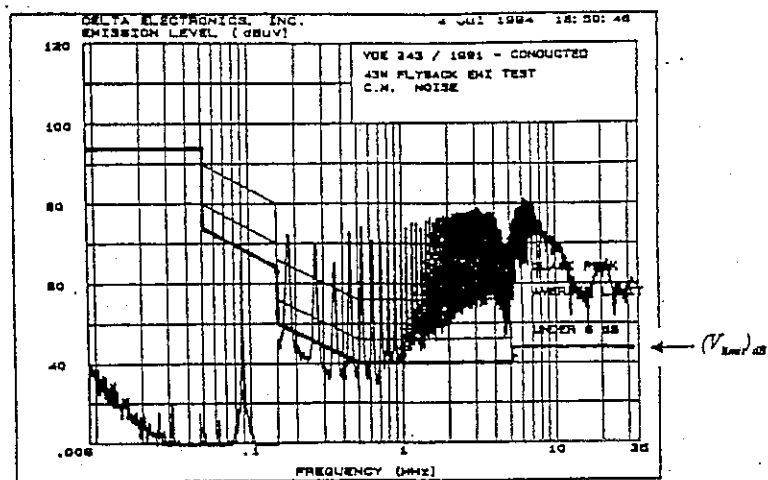
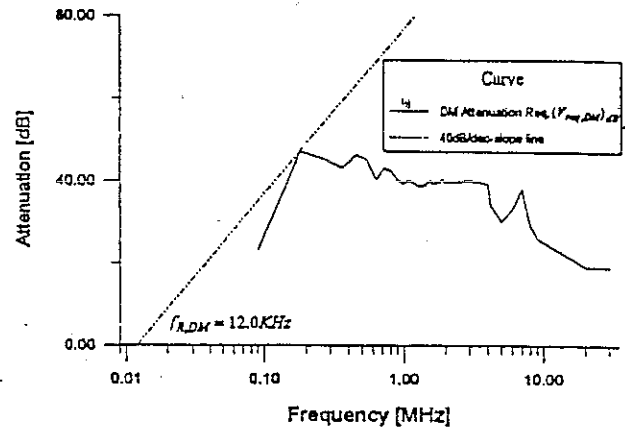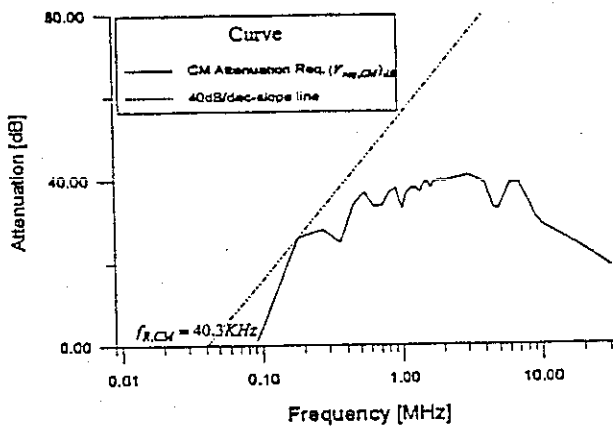
## Step 2: Plot Filter Attenuation Requirement



## Step 3: Determine Corner Frequency

$$f_{R,CM} = 40.3KHz \quad \text{and} \quad f_{R,DM} = 12.0KHz$$

Step 4a: Determine  $C_Y$ , and  $L_C$ . Use  $C_Y = 3300pF$ , calculate  $L_C$  according to Eq.(1),

$$L_C = \left[ \frac{1}{2\pi(40.3 \times 10^3)} \right]^2 \cdot \frac{1}{2 \cdot 3300 \times 10^{-12}} = 2.36mH$$

Select  $L_C = 2.4mH$ , and the leakage inductance  $L_{leakage} = 36\mu H$  can be obtained by measurement.



Step 4(b)

Determine  $C_{X1}$ ,  $C_{X2}$  and  $L_{DM}$ .




Using  $f_{R,DM} = 12.0\text{KHz}$  in Eq.(2), there are infinite sets of solution for  $L_{DM}$  and  $C_{DM}$






Three sets of solutions are listed for discussion in the following:

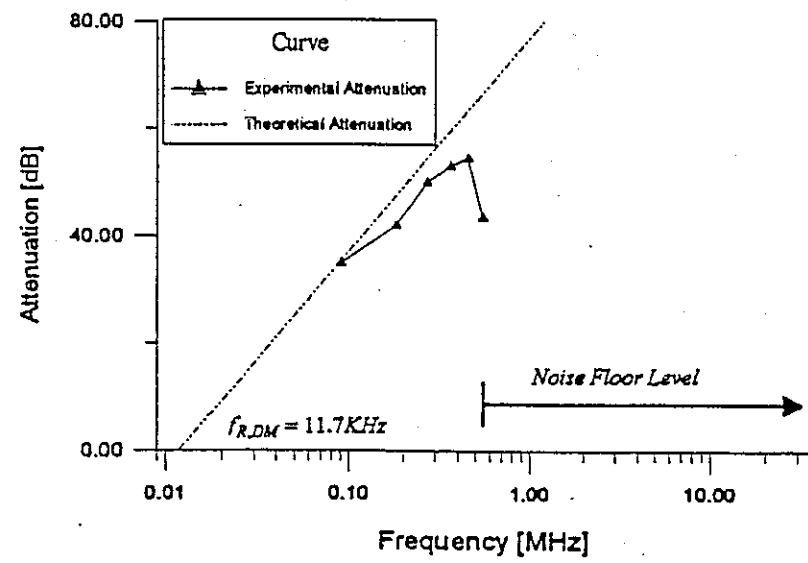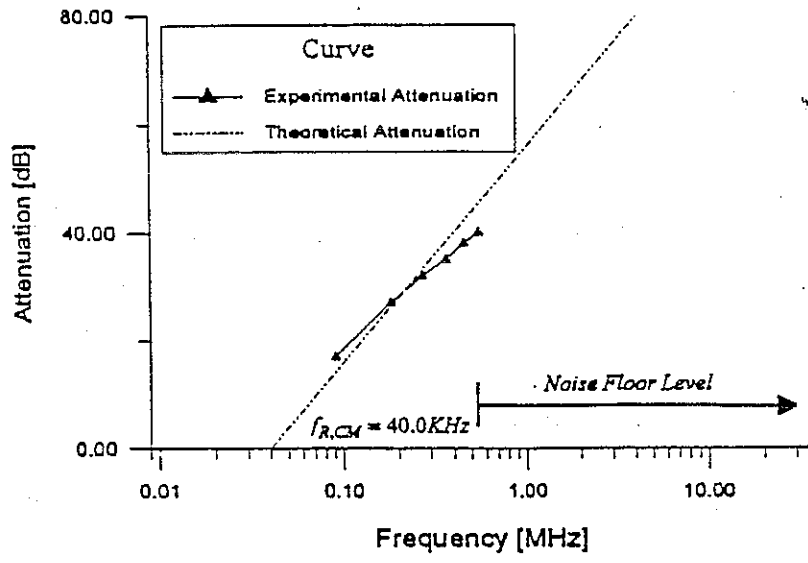- (1) Use the leakage inductance as the DM choke. Since  $L_{DM} = L_{\text{leakage}} = 36\mu\text{H}$ , then  $C_{CM}(= C_{X1} = C_{X2}) = 4.75\mu\text{H}$  which is an impractical value for line-voltage rated filter capacitor. The physical volume of such a capacitor is much to bulky.
- (2) If  $C_{DM}$  are chosen to be  $0.47\mu\text{F}$ , a commonly available filter capacitor value, then  $L_{DM} = 374\mu\text{H}$  and 
$$L_D = \frac{L_{DM} - L_{\text{leakage}}}{2} = 169\mu\text{H}$$
, a practical inductance value. Select  $L_D = 180\mu\text{H}$ .
- (3) If  $C_{DM} = 0.22\mu\text{F}$ , then  $L_{DM} = 800\mu\text{H}$  and  $L_D = 382\mu\text{H}$ , a practical value also. Select  $L_D = 380\mu\text{H}$ .







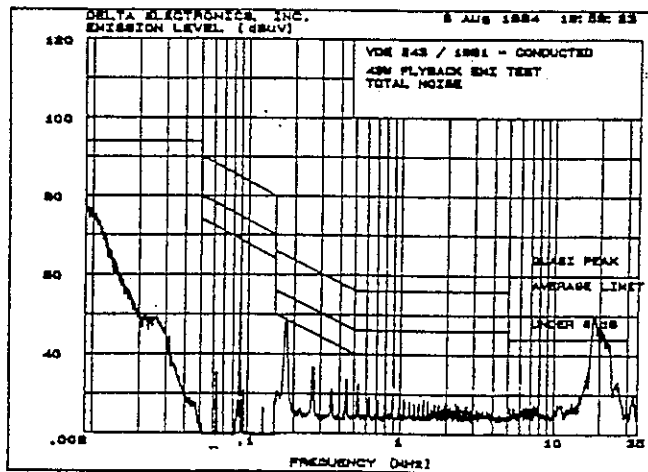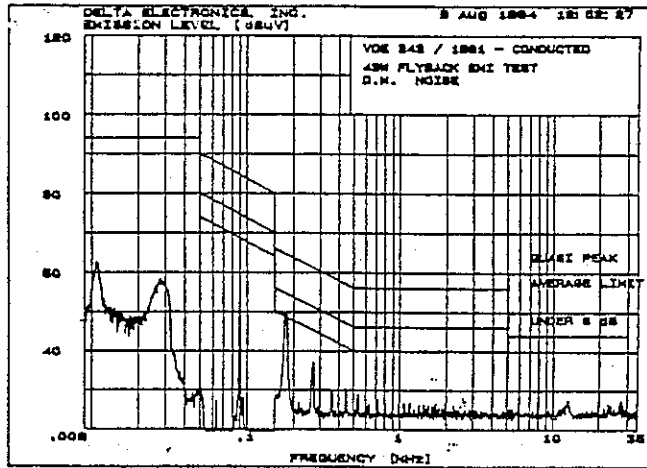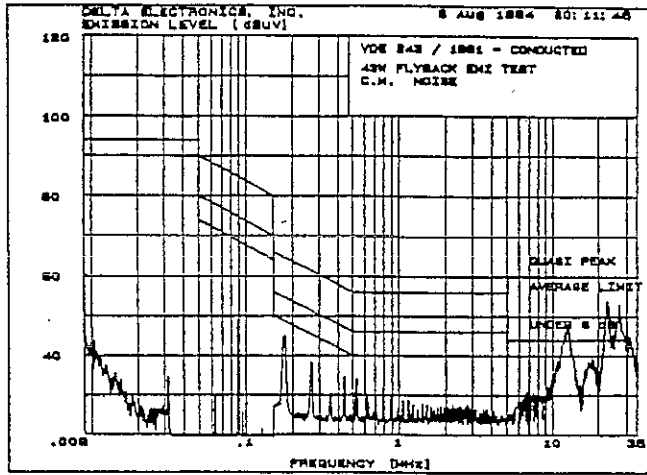


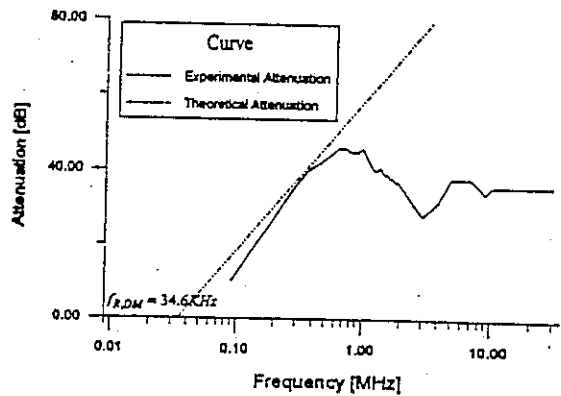
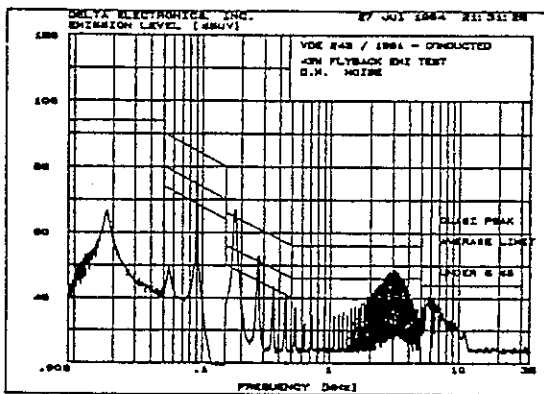
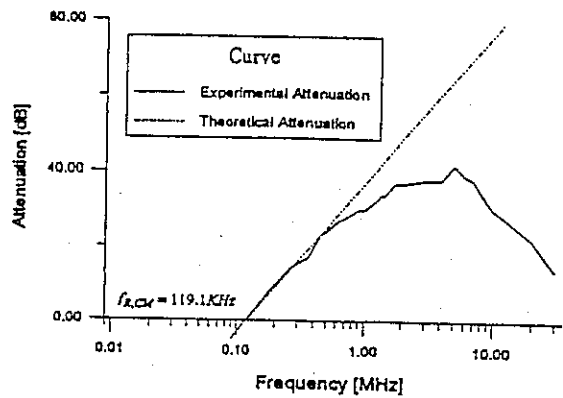
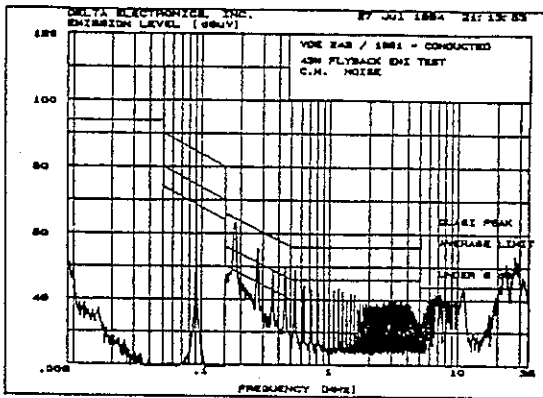
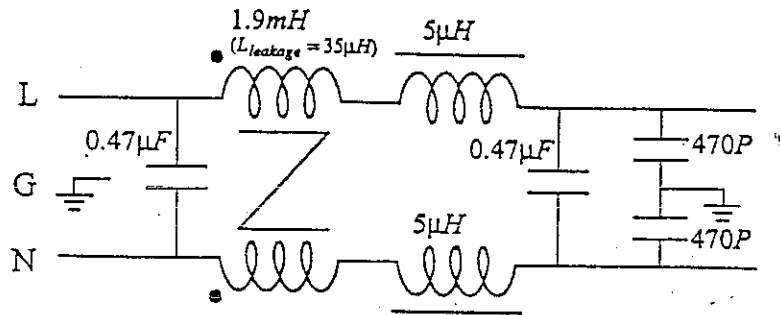

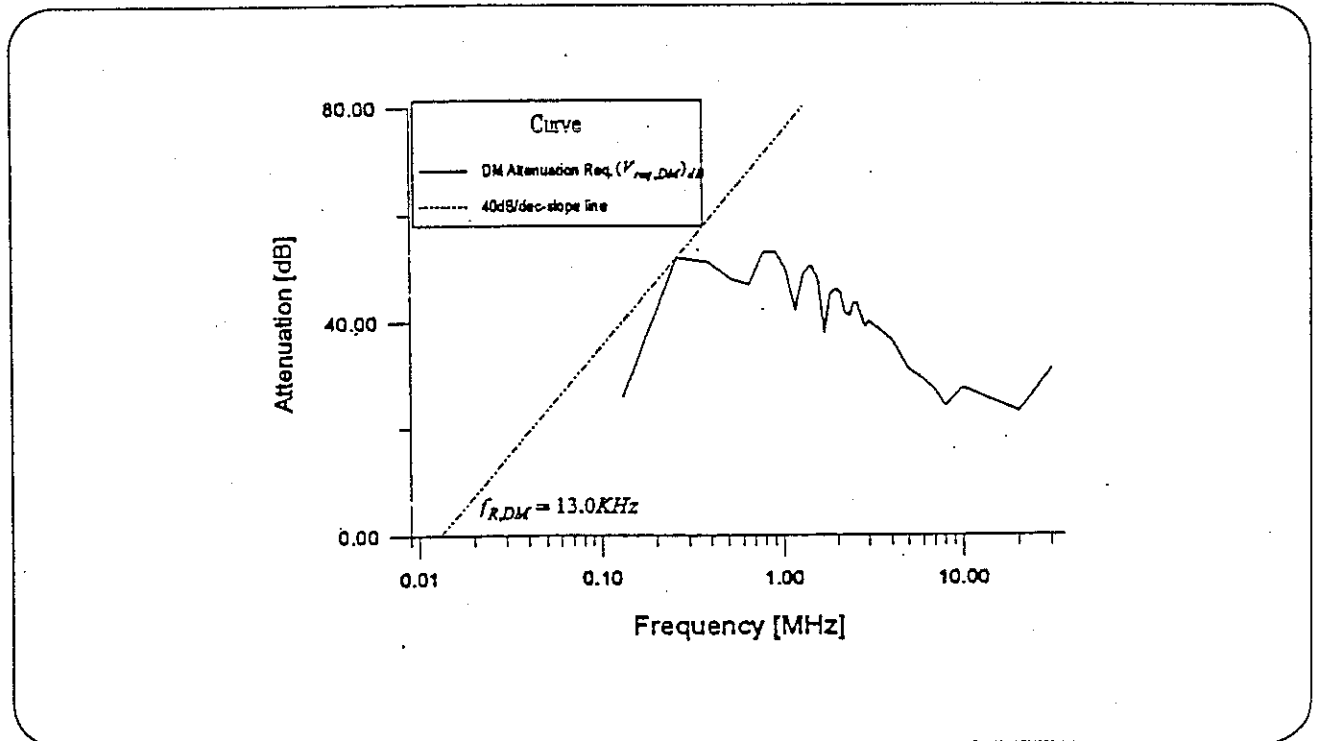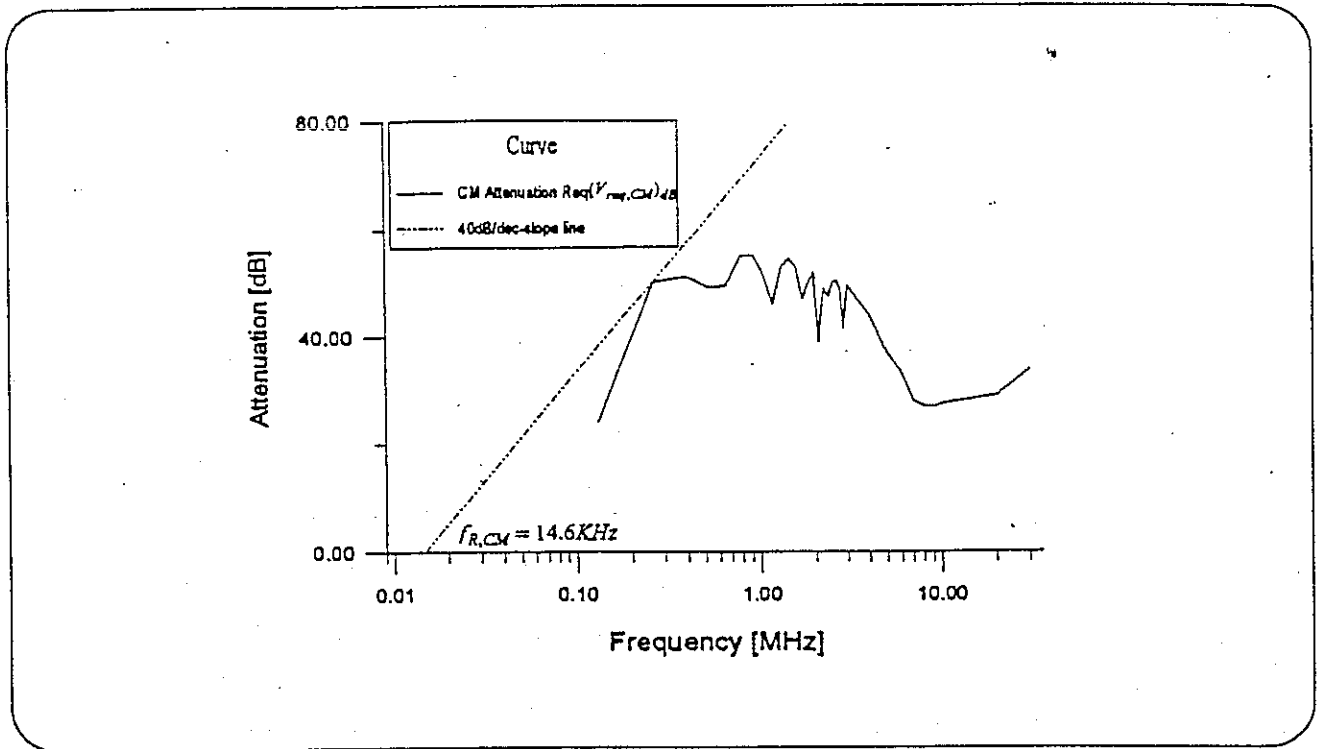
# EXAMPLE 2: 100-W Off-Line Forward Converter Power Supply



# Without Filter

# With Filter

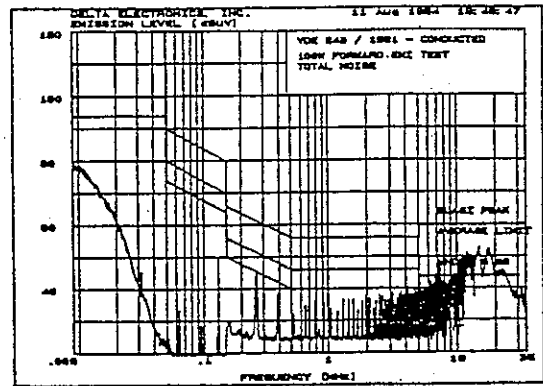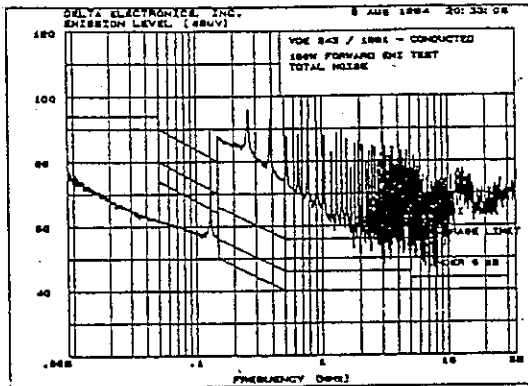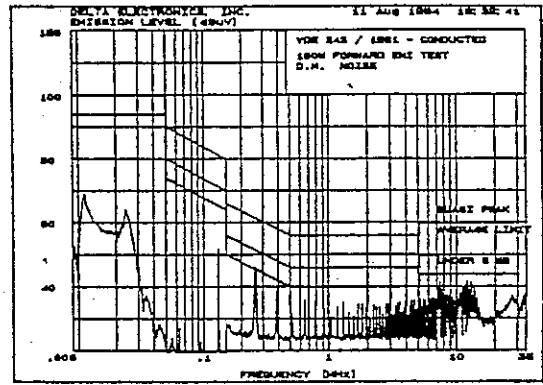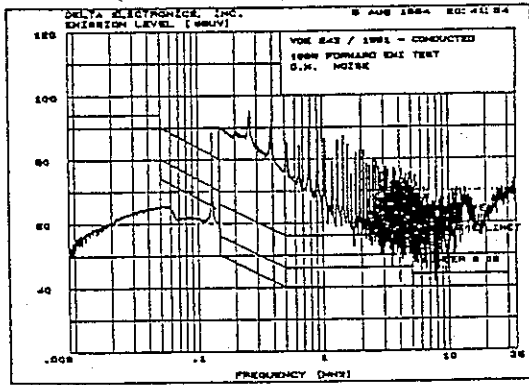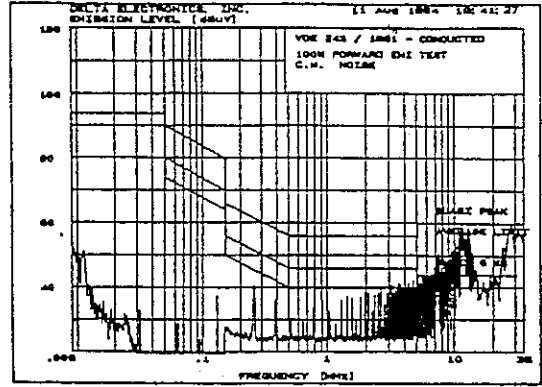
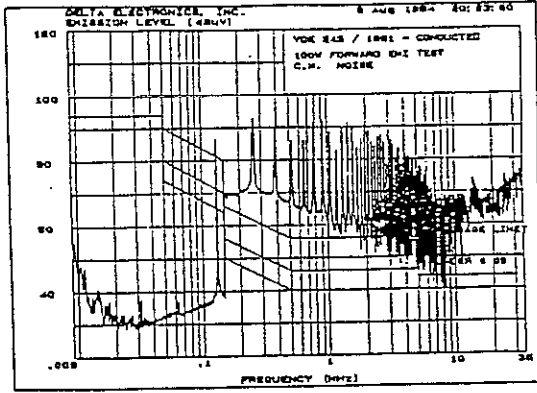


# 十、用調頻方法減少 EMI (EMI Reduction by FM)

# Conducted EMI Reduction by Frequency Modulation

- Suppression
- Decoupling
- Filtering / Shielding
- Frequency Modulation


# Frequency Spectrum of FM Signals

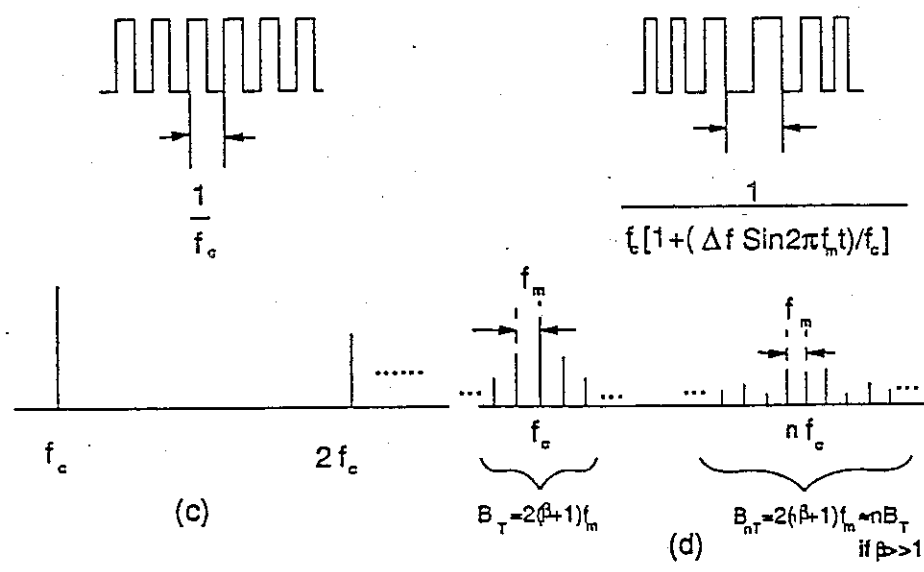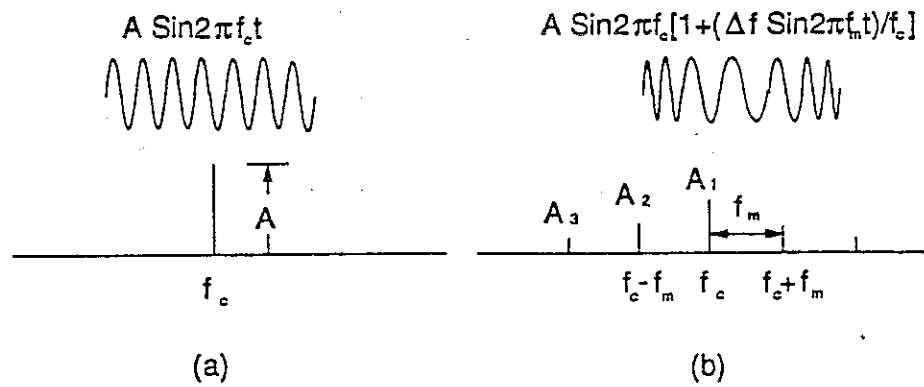

# Effects of $\beta (\underline{\Delta} \Delta f / f_m)$ on FM Spectrum

$$\Delta f: (f_{m \max} - f_{m \min}) / 2$$


$f_m$ : modulating signal

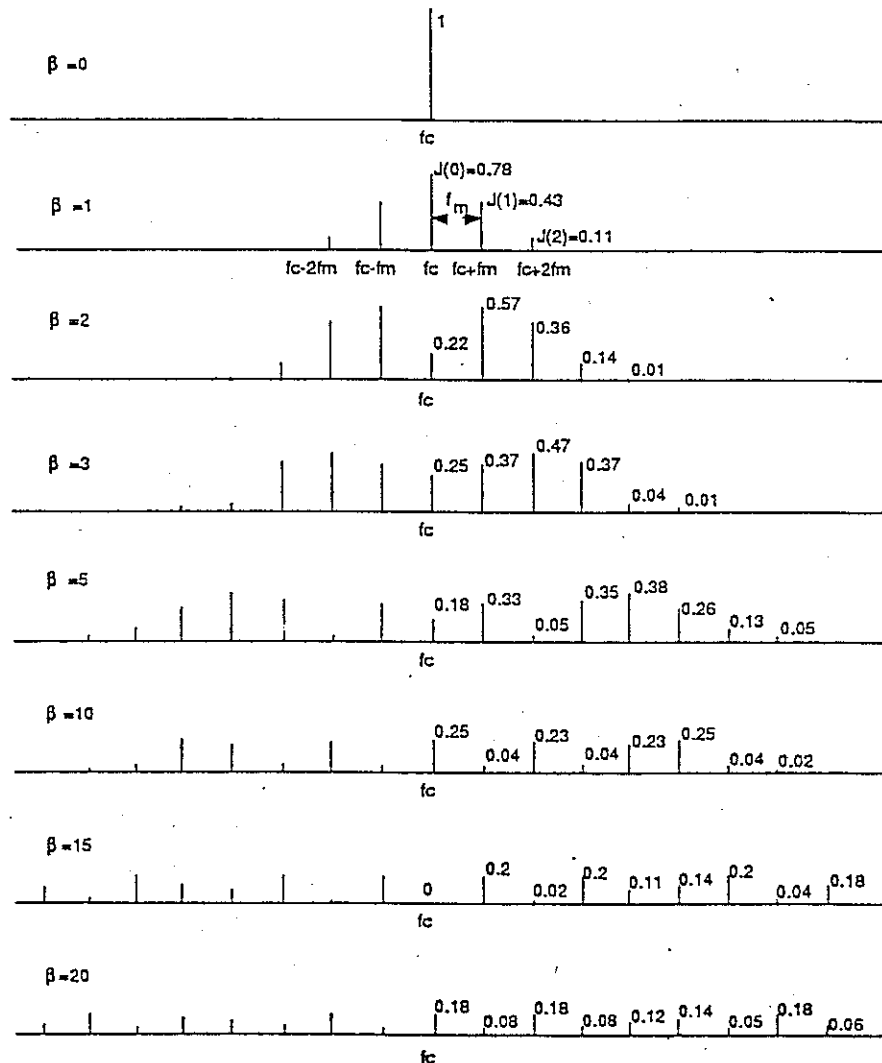


Carlson's Rule:

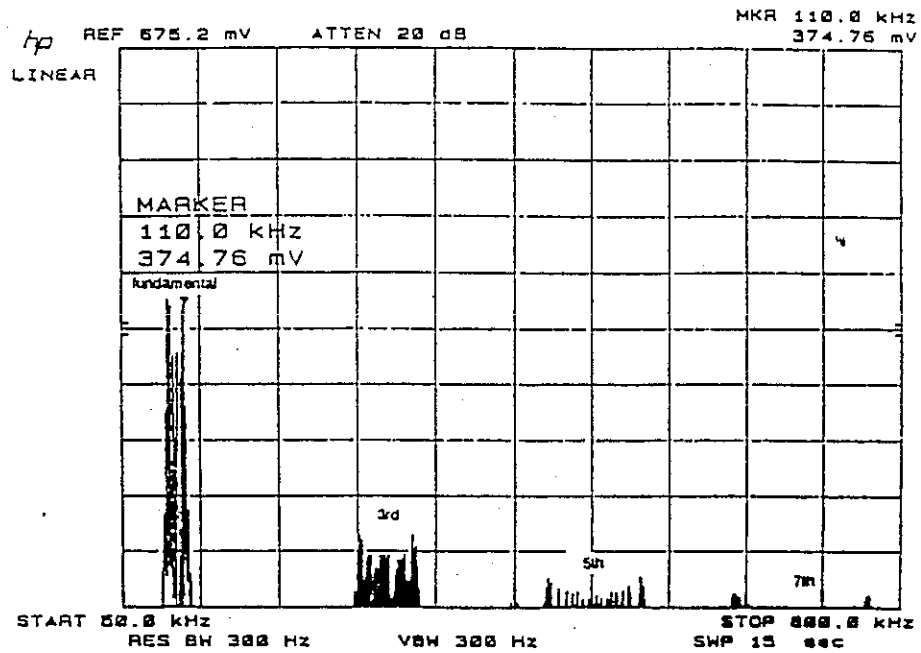1. Total Energy Unchanged
2. 98% of Energy is contained within  $B_T = 2(\beta + 1)f_m$







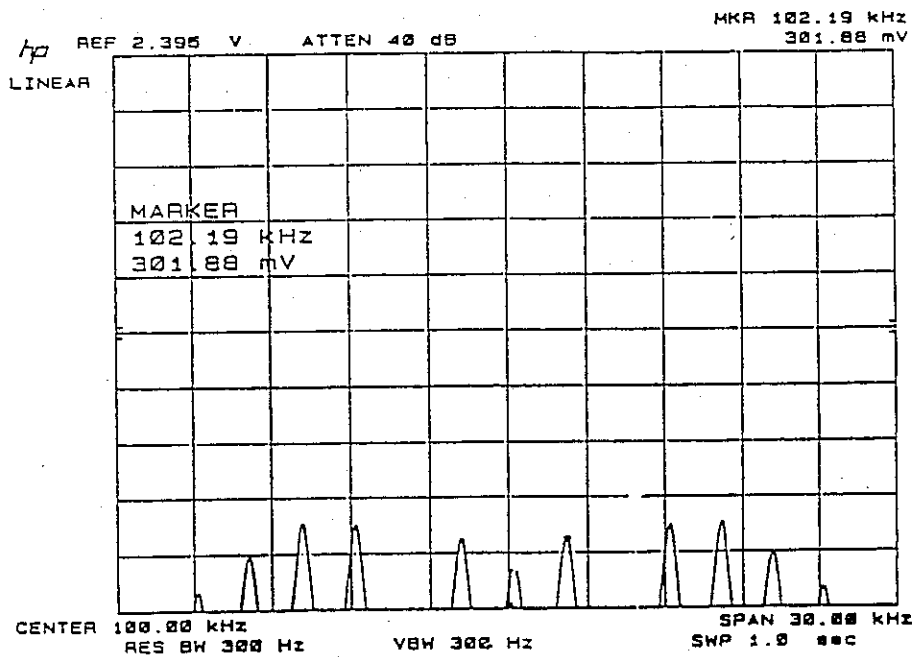$f_c = 100 \text{ kHz}$ ,  $f_m = 2 \text{ kHz}$ ,  $\Delta f = 10 \text{ kHz}$ ,  $\beta = 5$ ,  $\text{RBW} = 10 \text{ kHz}$   
Spectrum Of A Modulated Pulse-Train Signal







$\Delta f = 10 \text{ kHz}$ ,  $f_m = 2 \text{ kHz}$ ,  $\beta = 5$ ,  $\text{RBW} = 300 \text{ Hz}$   
Side-Band Harmonics Of The Fundamental Switching Harmonic

# FM Effect

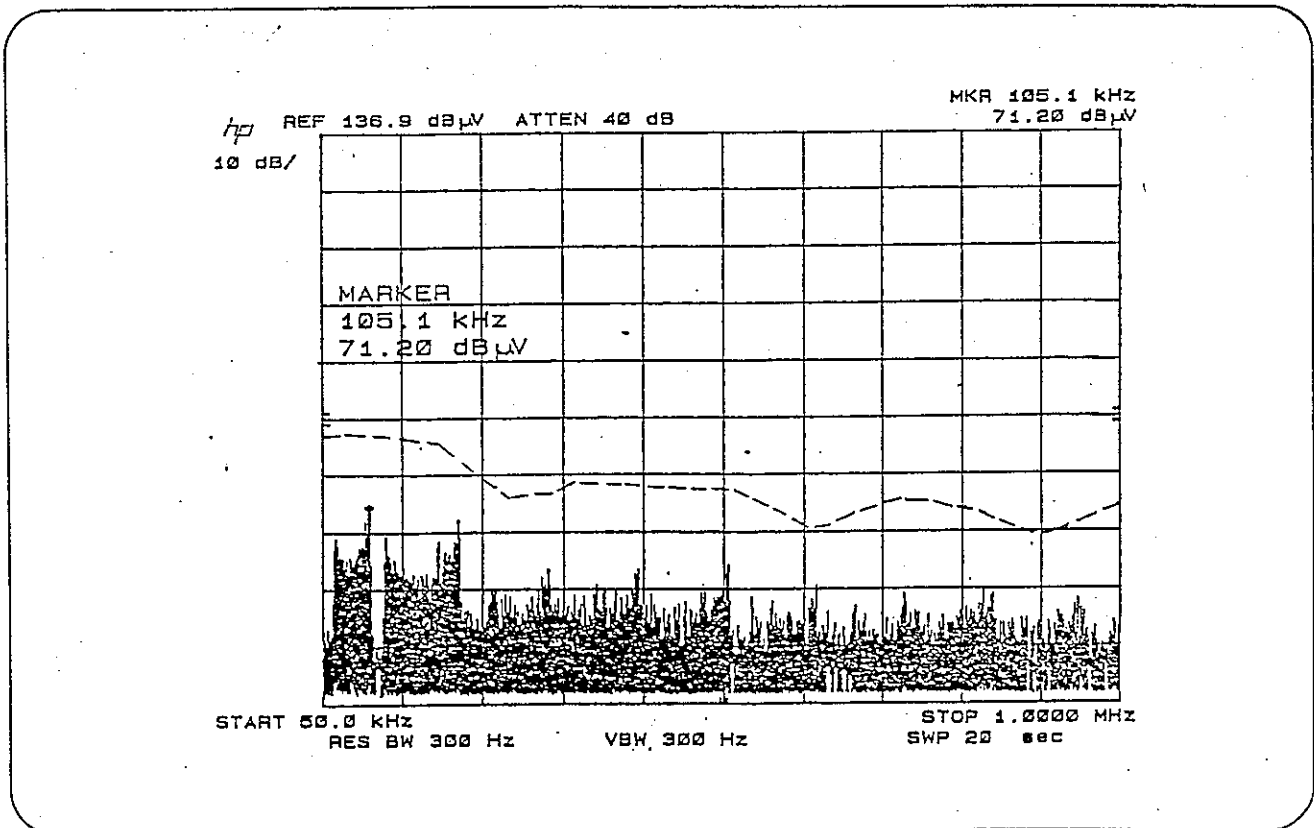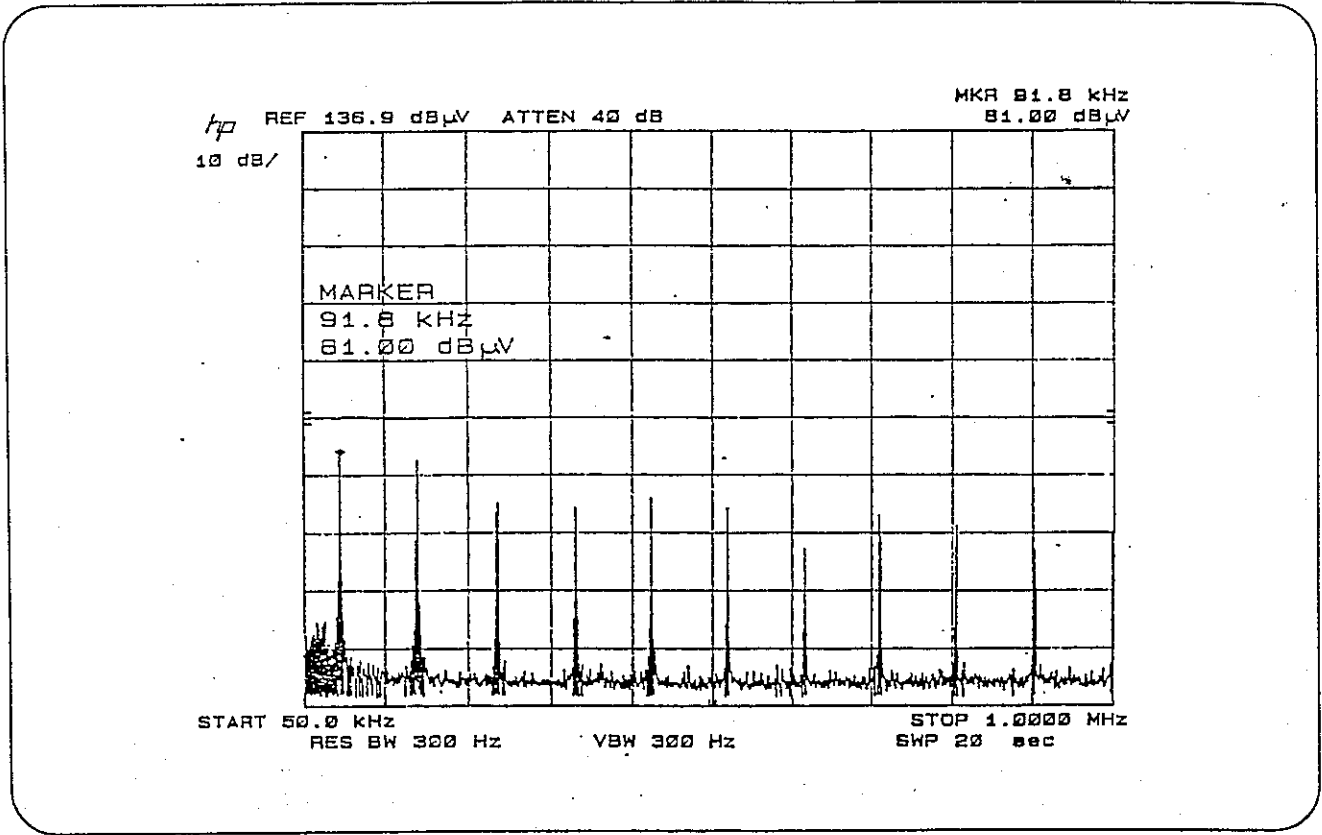
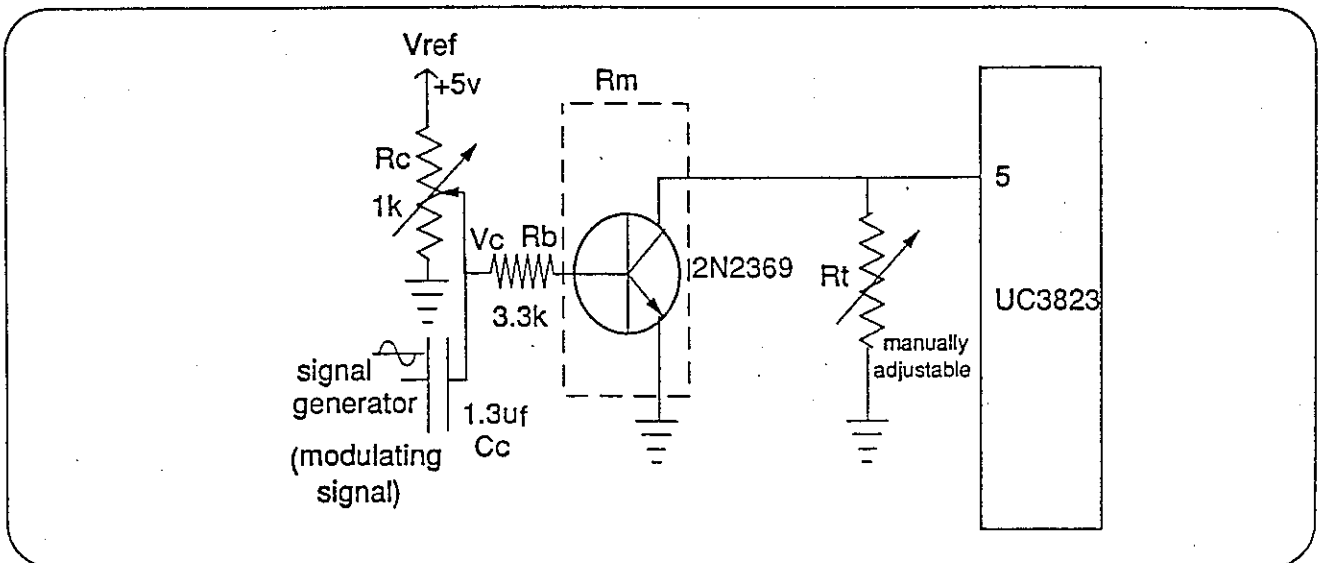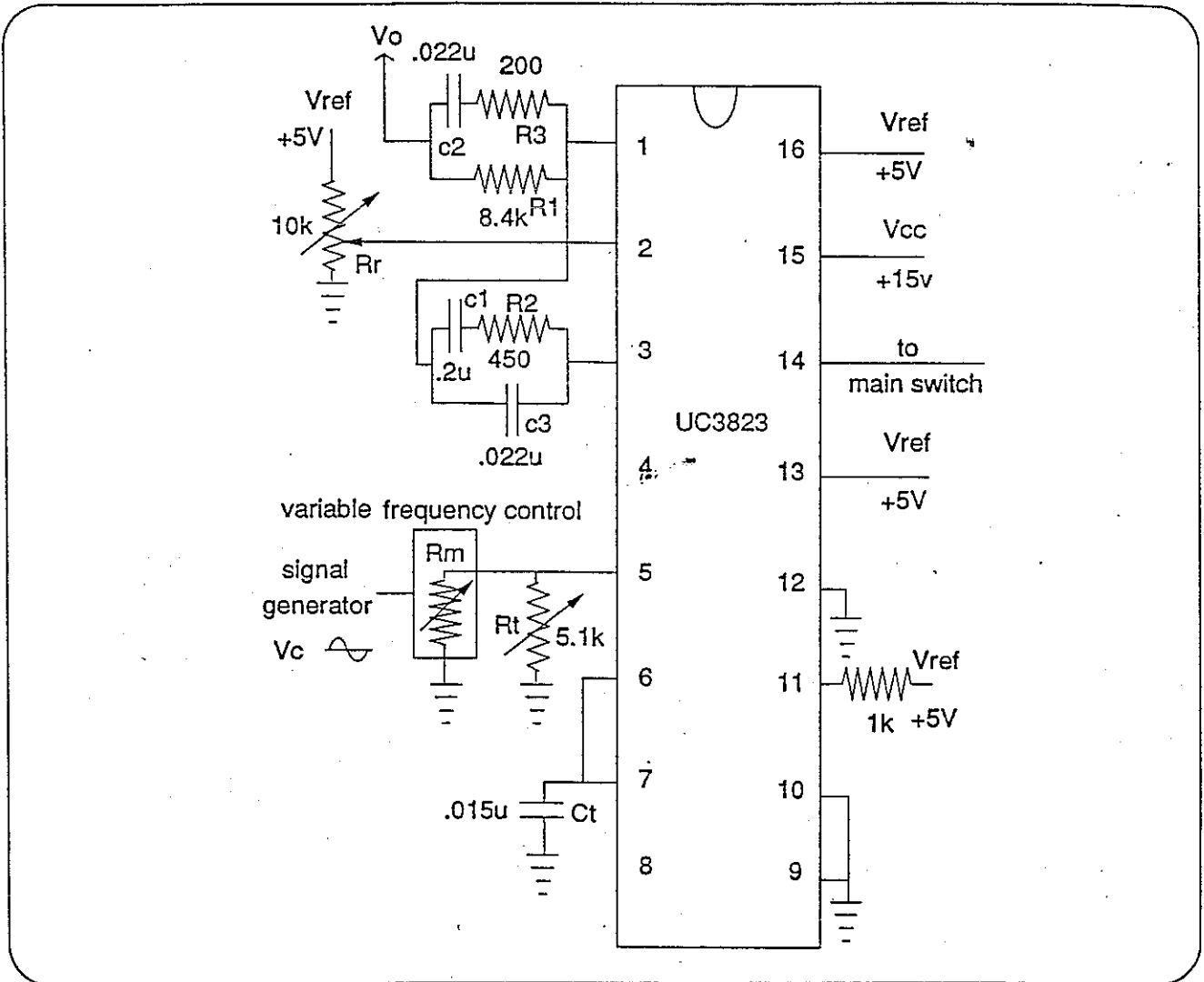
# Circuit Implementing FM in Power Supplies



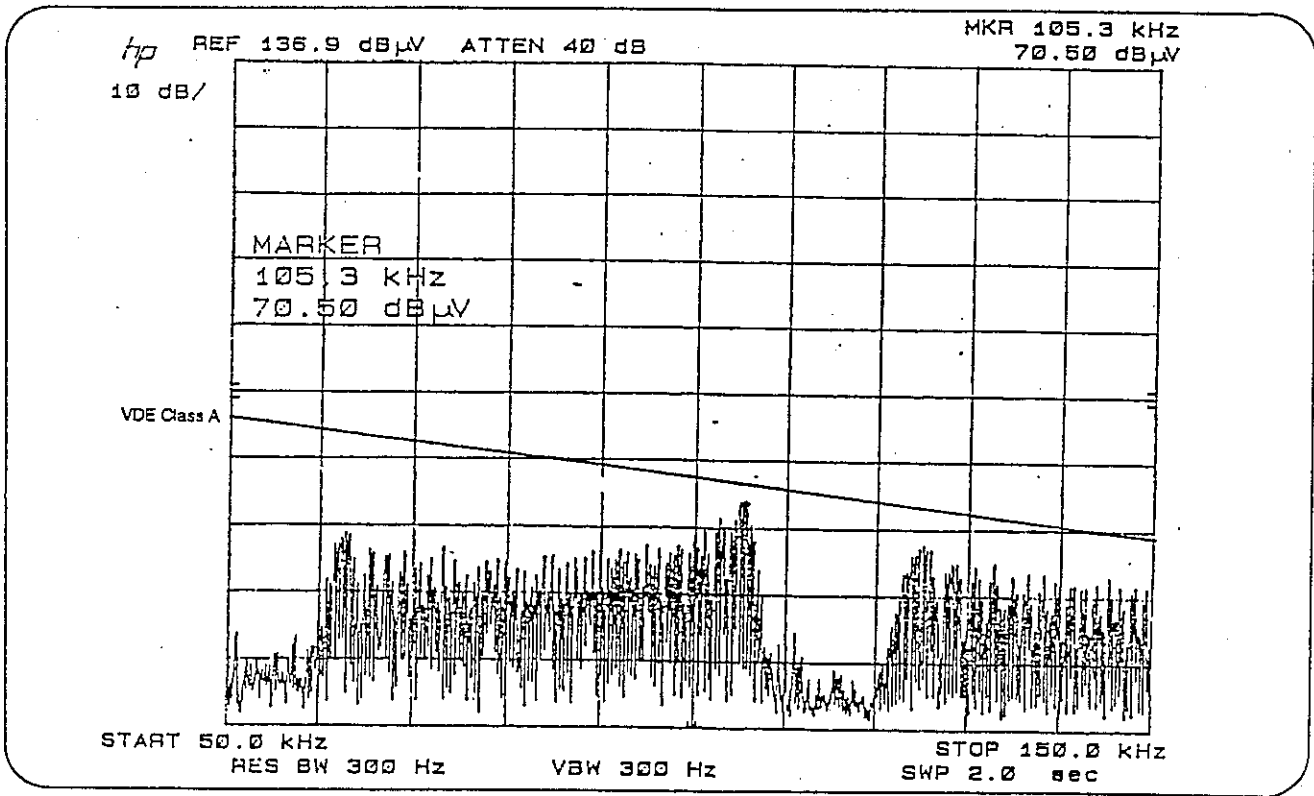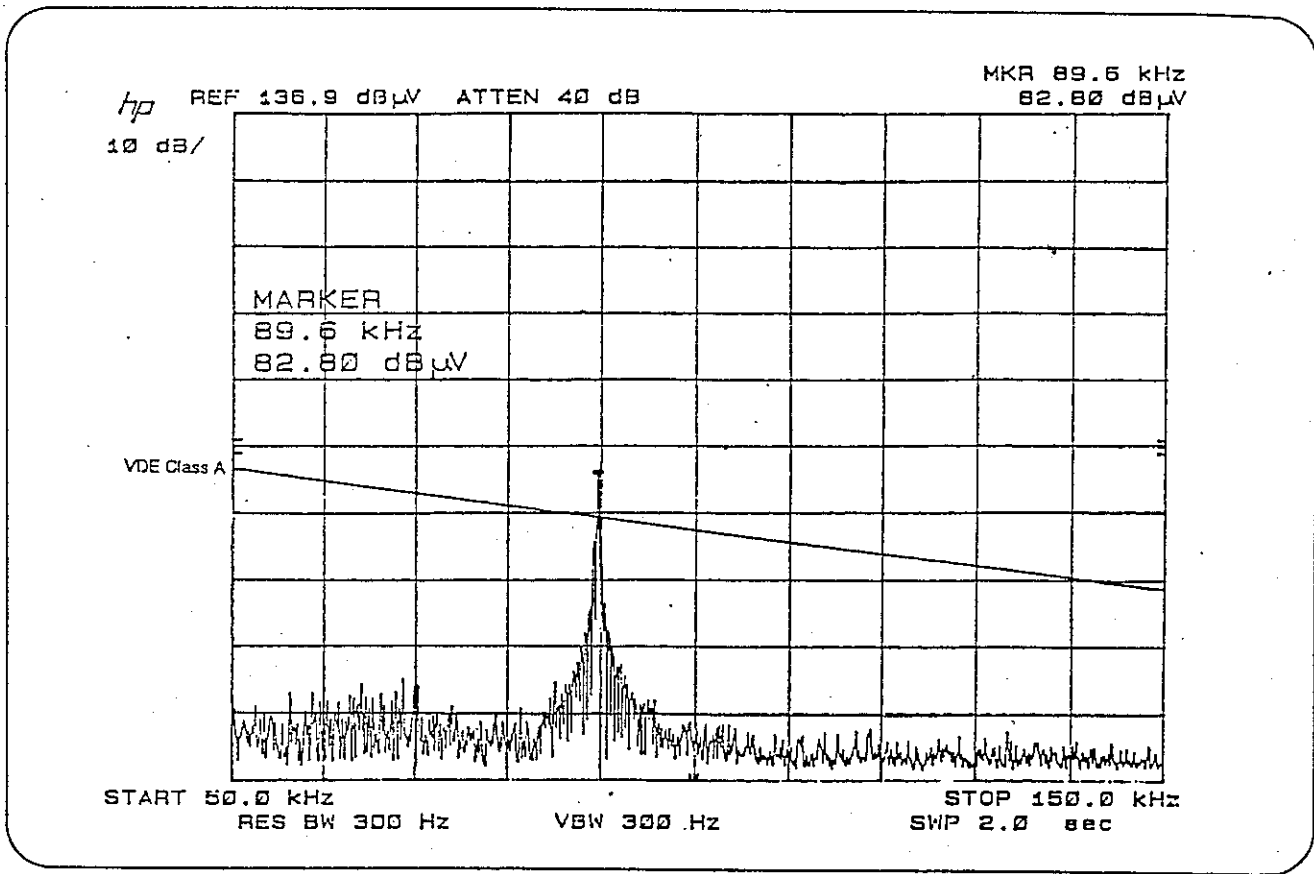

hp


REF 136.9 dB $\mu$ V ATTEN 40 dB

MKR 7.25 MHz  
88.20 dB $\mu$ V

10 dB/

MARKER  
7.25 MHz  
88.20 dB $\mu$ V

VDE Class A

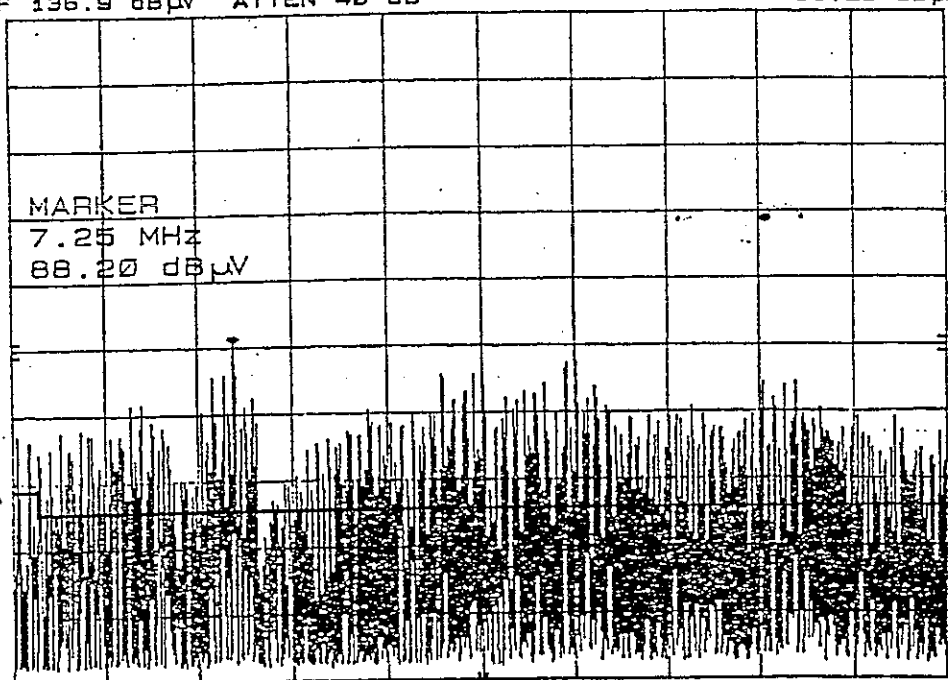

START 150 kHz RES BW 10 kHz VBW 10 kHz STOP 30.00 MHz SWP 750 msec

hp


REF 136.9 dB $\mu$ V ATTEN 40 dB

MKR 6.96 MHz  
81.80 dB $\mu$ V

10 dB/

MARKER  
6.96 MHz  
81.80 dB $\mu$ V

VDE Class A

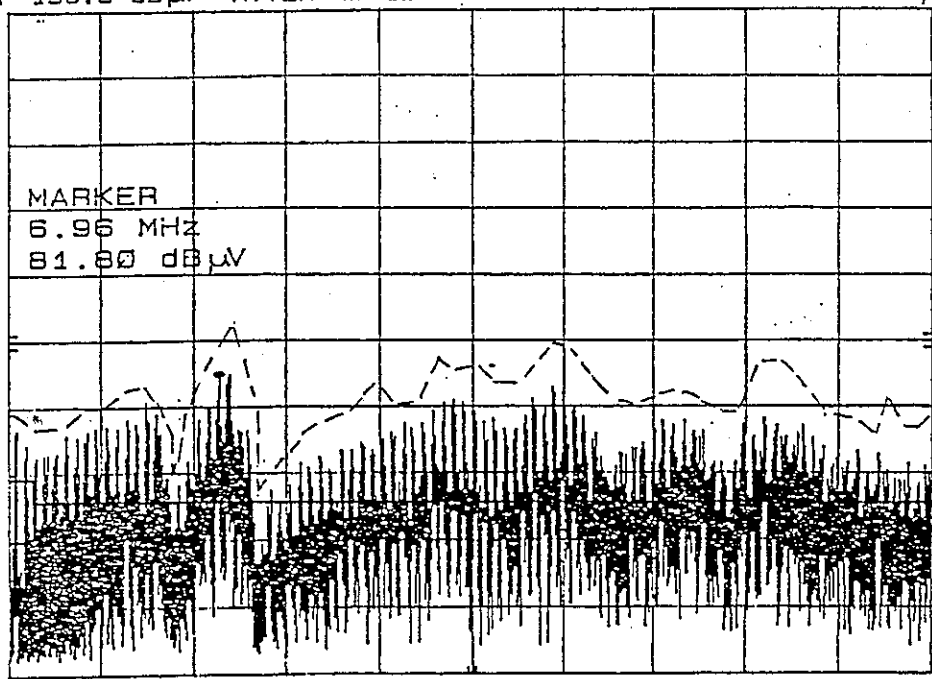

START 150 kHz RES BW 10 kHz VBW 10 kHz STOP 30.00 MHz SWP 750 msec

# Parameters Affecting the Performance

$$\beta = \Delta f / f_m$$

Larger  $\beta$  , better noise shattering

$\Delta f$ : Too small  $\Delta f$  , Small  $\beta$   
Too large  $\Delta f$  , bad for magnetic component selection

$f_m$ : Too large  $f_m$ , small  $\beta$  ; regulation problems  
Too small  $f_m$ , no significant reduction in measured EMI if  $f_m \ll \text{RBW}$

# Conclusions

1. Modulating Parameters ( $\Delta f, f_m, \beta$ ) must be chosen properly to have effective EMI reduction without causing significant side effects.
2. To reduce fundamental harmonic noise:

If  $f_s < 150\text{kHz}$ , use  $f_m \approx 200\text{Hz}$

If  $f_s > 150\text{kHz}$ , use  $f_m \approx 9\text{kHz}$

3. FM is effective in reducing both the DM and the CM noise.


FM not effective in reducing noise generated by ringing.

4. EMI filter must be properly damped to avoid possible amplification of noises at the filter pole frequencies.
5. FM should be effective in reducing radiated EMI, but this has not been verified.
6. Other modulating waveforms can be considered to improve the performance.



# 十一、輻射 EMI 控制 (Radiated EMI)

## IX. Radiated EMI

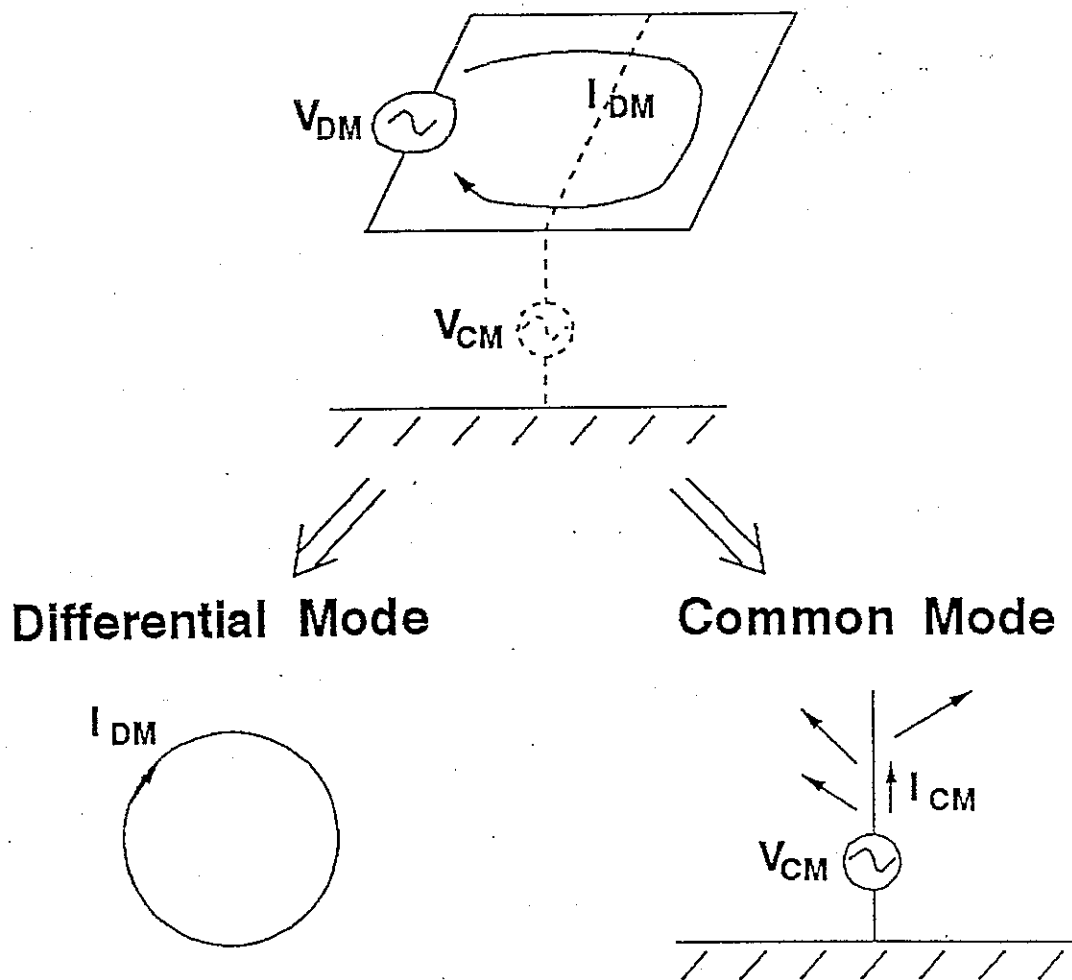

- Requires different treatments
- In general, C.M. noise is harder to control.

**Standard**  
**FCC Vs. Military**

**Radiation  
Test**

**FCC**  
**open field**

**Military**  
**enclosed chamber**

**Conducted  
Test**

**Measure  
Voltage**

**Measure  
Current**

# FCC Radiation Test

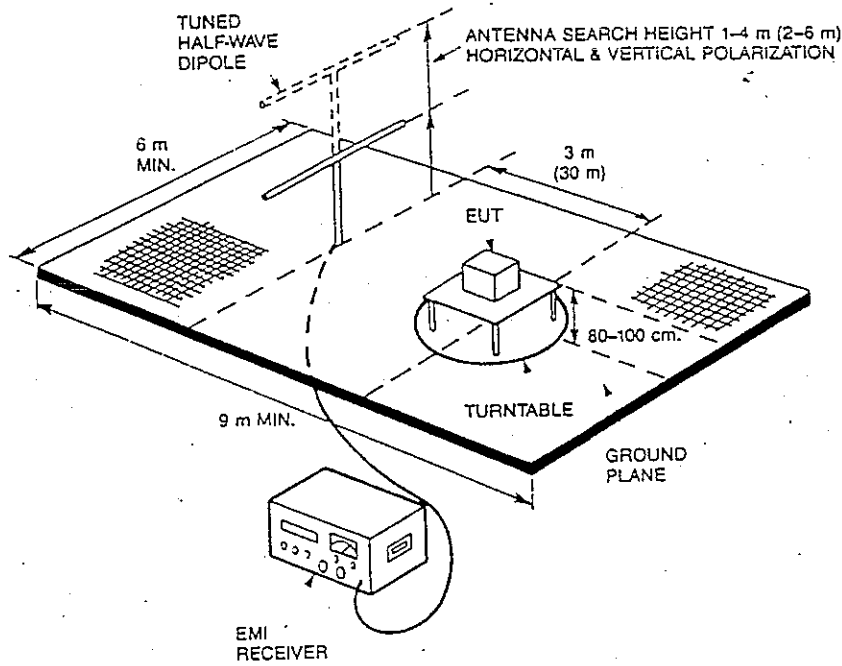


Figure 1-5. Open field test site for FCC radiated emission test. Equipment under test (EUT) is on the turntable.


Table 1-1 FCC Class A Radiated Emission Limits

Frequency (MHz)	Measuring Distance (m)	Field Strength ( $\mu\text{V/m}$ )
30-88	30	30
88-216	30	50
216-1000	30	70

Table 1-2 FCC Class B Radiated Emission Limits

Frequency (MHz)	Measuring Distance (m)	Field Strength ( $\mu\text{V/m}$ )
30-88	3	100
88-216	3	150
216-1000	3	200

## Differential - Mode Radiation

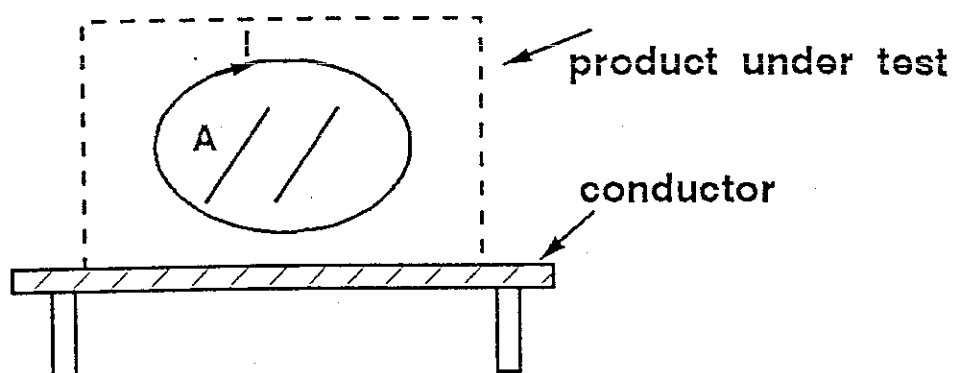

$$\bullet E_{\max} = 263 * 10^{-16} (f^2 A I) * \frac{1}{r} \quad \left\{ \begin{array}{l} E : \text{v} / \text{m} \\ A : \text{m}^2 \\ I : \text{A} \\ r : \text{m} \end{array} \right.$$

- At  $f = 30 \text{ MHz}$ ,  $A = 10 \text{ cm}^2$ ,  $I = 100 \text{ mA}$   
 $r = 3 \text{ m}$ ,  $E_{\max} \cong 800 \text{ uv} / \text{m}$ .

FCC part 15, Class B,  $E = 100 \text{ uv} / \text{m}$


- Equation is accurate for small loop  
 (perimeter  $\ll \lambda / 4$ ).

$E$  varies with location.



## D.M. Radiation from Clock Signal

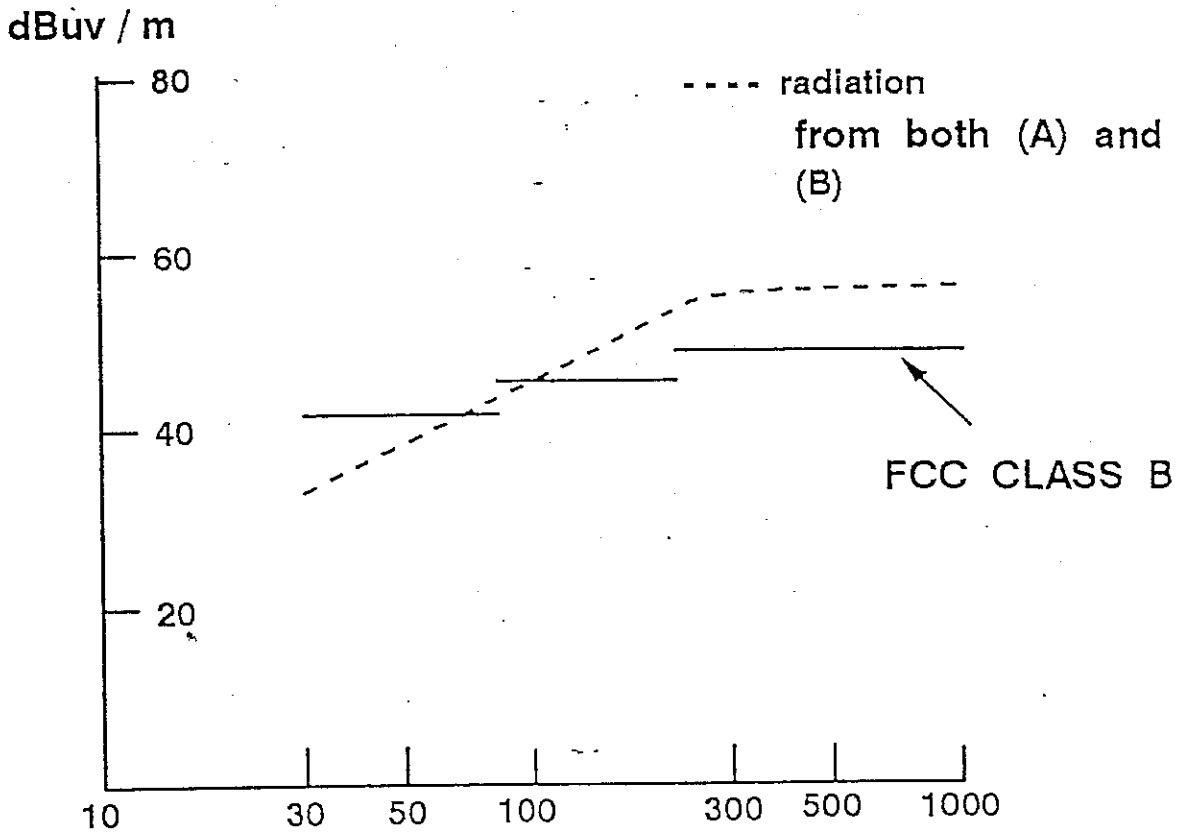(A) 4" - long, 1/2" - wide trace carries 16 MHz  
4 ns rise time, 35 mA clock signal  
(PC-board trace)

or (B) 3' - long, 50 mil adjacent return, 4 ns,  
35 mA (cable)



## D.M. Radiation in Power Supplies

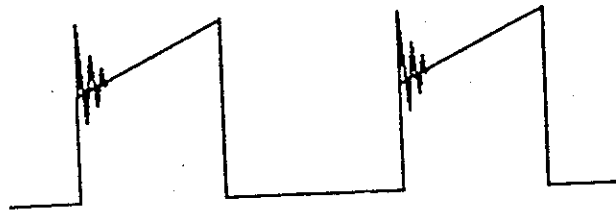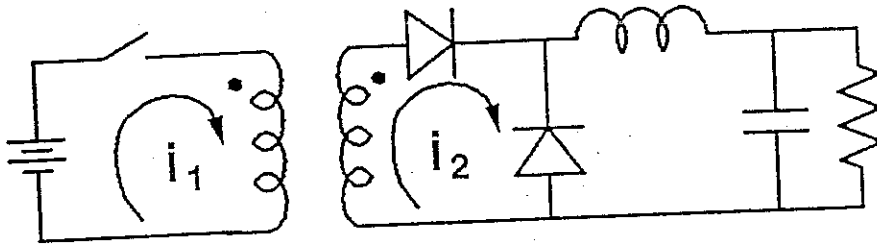


- Normally,  $i_2$  is much larger than  $i_1$
- Ringing frequency  $\approx 10$  --  $30$  MHz  
Without suppression or shielding,  
P.S. cannot pass FCC regulation.


# D.M. Radiation of Clock

$$E_{\text{rod.}} \propto f^2 I A$$


$$E \propto f^2$$

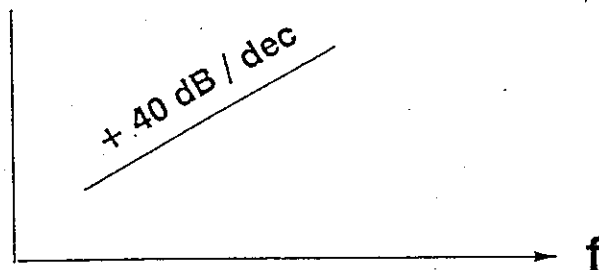

$I$

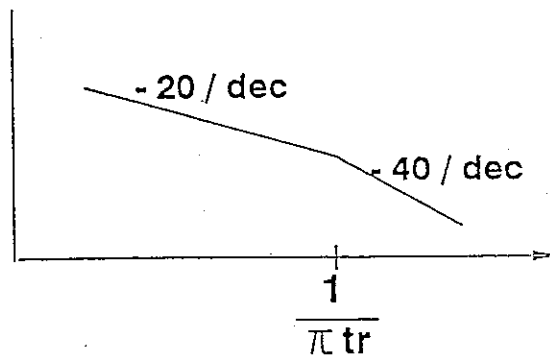


$E$  radiated

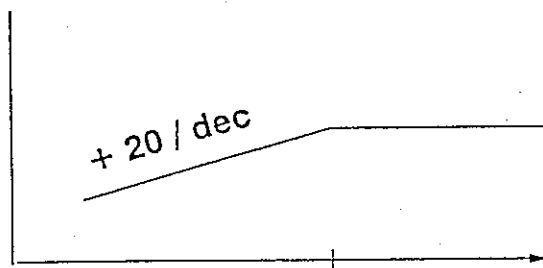



# Radiation Noise Sources in a Digital Circuit


Primary : Clock  
Line and Bus Driver

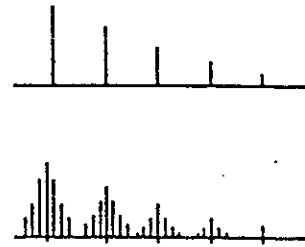

Secondary : Address Buses  
Data Buses



Power Supply : Transient Current

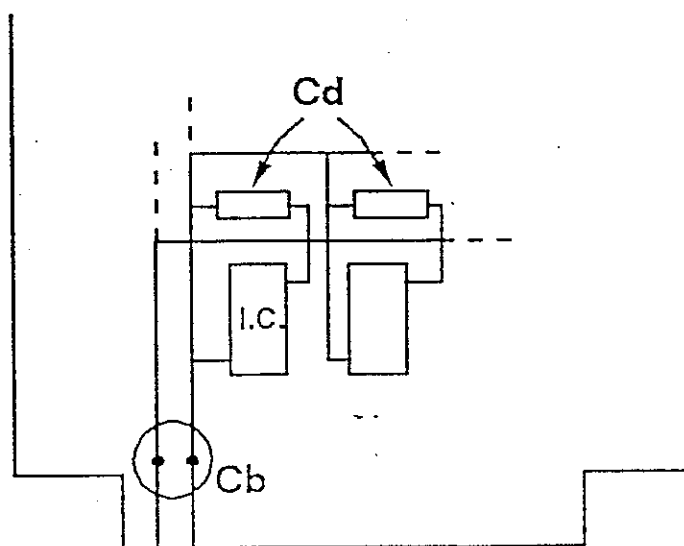


PCB


## Controlling D.M. Radiation

- Reduce Area of High - Frequency Loop


- PC board layout
- Use ground plane

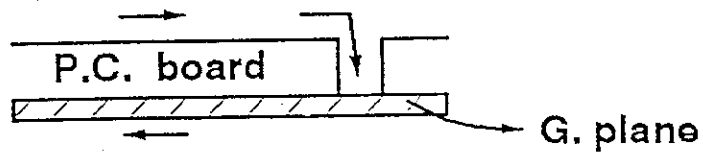

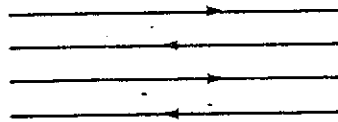- Alternate signal return in a ribbon connector





- Use decoupling capacitor for each I.C.

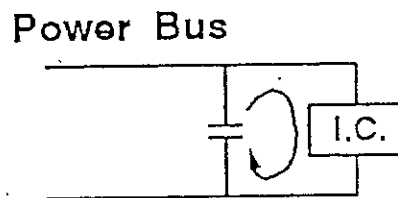


- Use coaxial if necessary

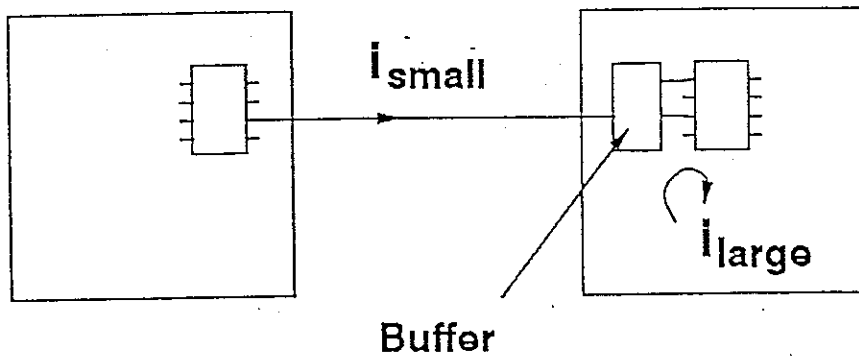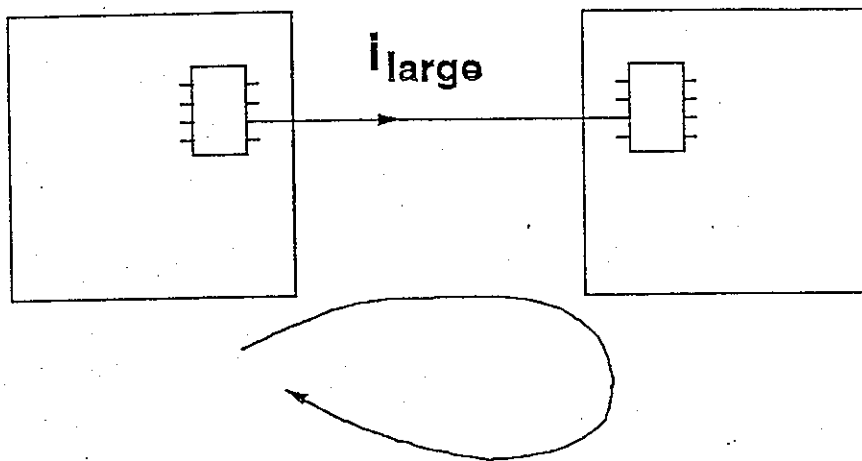
# Avoid Large Current Flowing in a Long Wire




# Backplane Layout

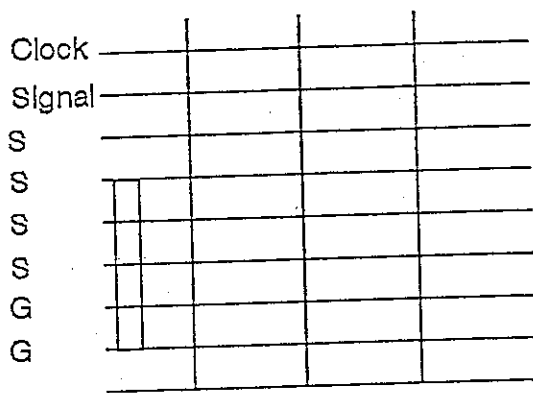


Bad

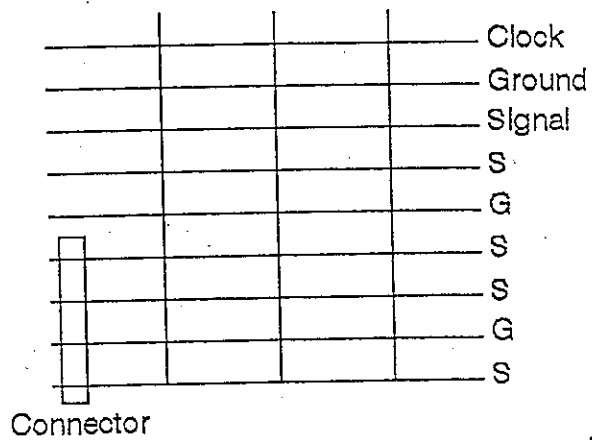

Better

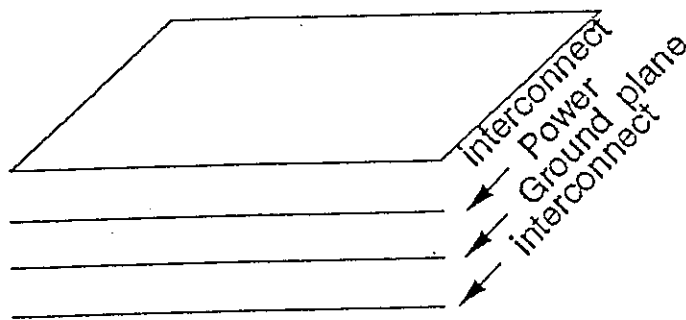


Multilayer Board

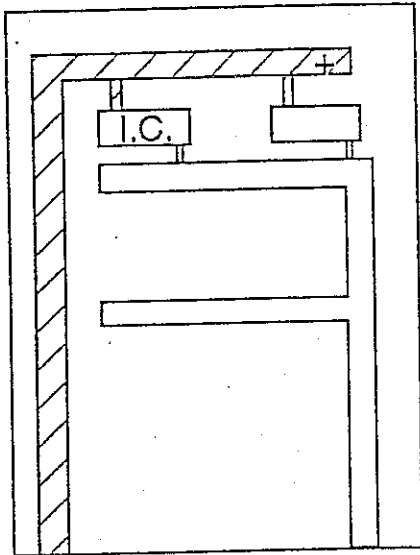

Vcc

Gnd

Bad

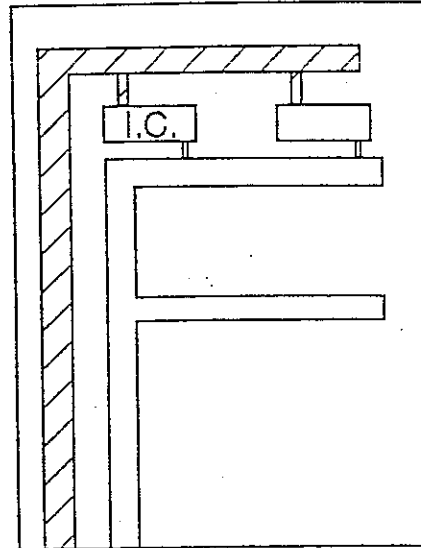

VccGnd


Good

Trace Length  $l < \frac{\lambda}{20}$


100MHz ----  $> l = 15 \text{ cm}$

- Reduce High Frequency Current


- Slow down switching rise time  $t_r$

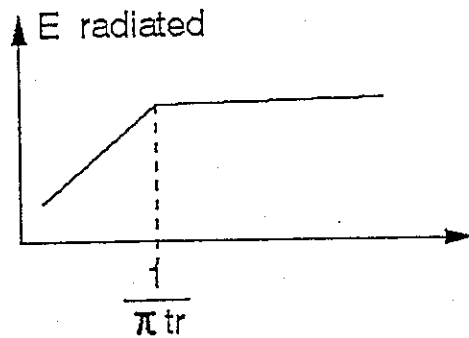


- Avoid high frequency ringing

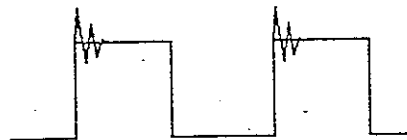

- Avoid cross conduction of transistors

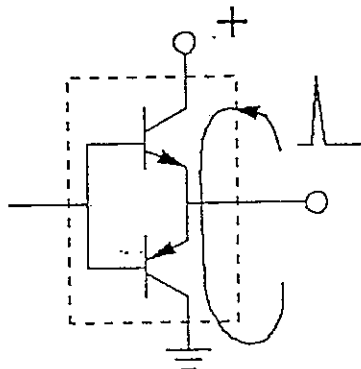

## Common - Mode Radiation

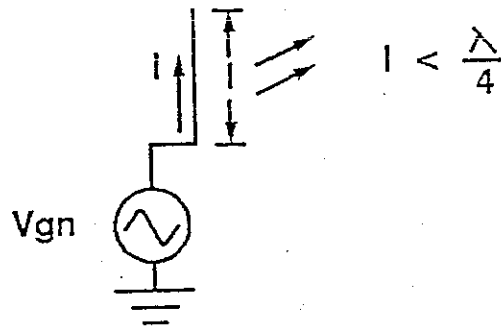

$L, r$  : meter


$I$  : Amp.

$E$  : v / m

$$E_{\max} = 12.6 * 10^{-7} (f L I) * \frac{1}{r}$$




- At  $f = 30$  MHz ,  $L = 1$  m ,  $I = 100$  mA  
 $r = 3$  m ,  $E_{\max} = 500 * 10^3$  uv / m  $\gg$  FCC Limit
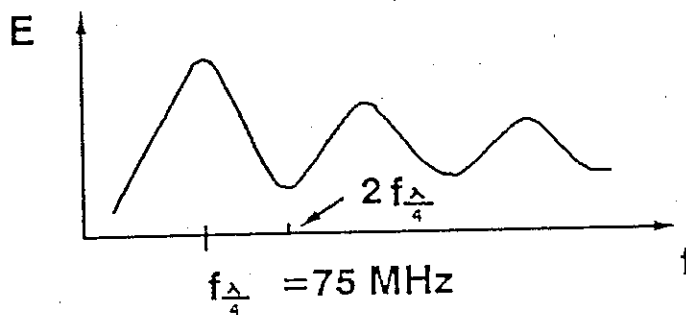
$$E \propto f \text{ if } l < \frac{\lambda}{4}, \quad E_{\max} \text{ occurs at } \frac{\lambda}{4}$$




- C.M. radiation  $\gg$  D.M. radiation  
 ( in general )

# Radiation Efficiency

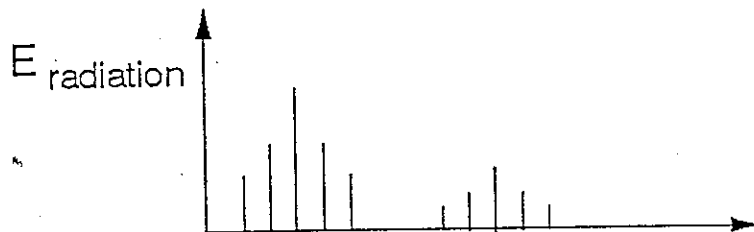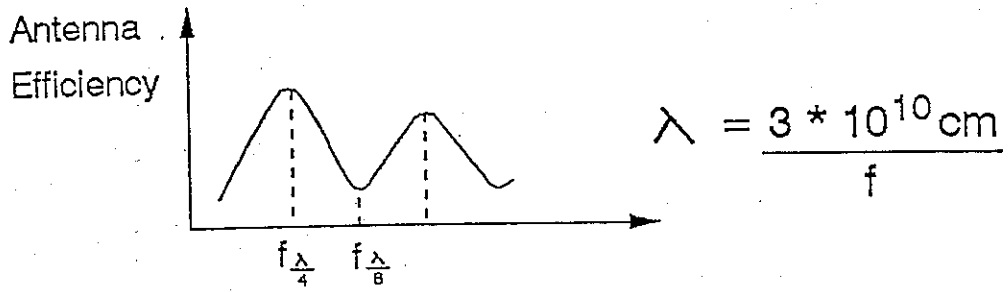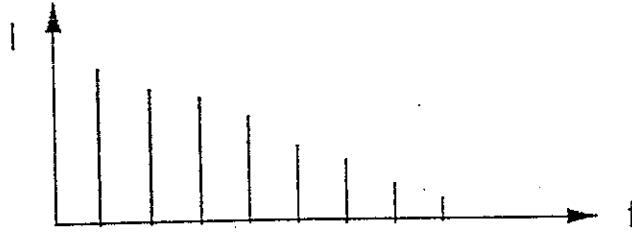



## Measurement of C.M. Current

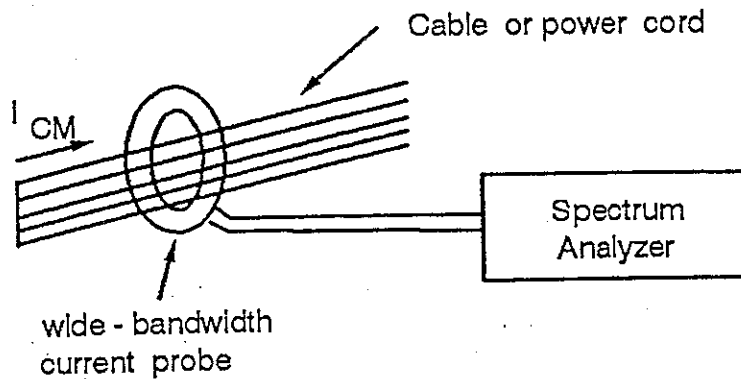

- $$I_{max} = \frac{0.8 E_s r}{f L}$$

$$I_{measure} < I_{max}$$

$$r = 3 \text{ m ,}$$


$E_s = \text{Spec . of FCC}$   
or VDE

For FCC CLASS B , at 50 MHz ,  $L = 1 \text{ m}$

$$I_{max} = 5 \text{ uA}$$


- Good diagnostic test in the Lab .
- Only millivolts of ground potential --->  $I > 5 \text{ uA}$

## Effectiveness of C.M. Choke

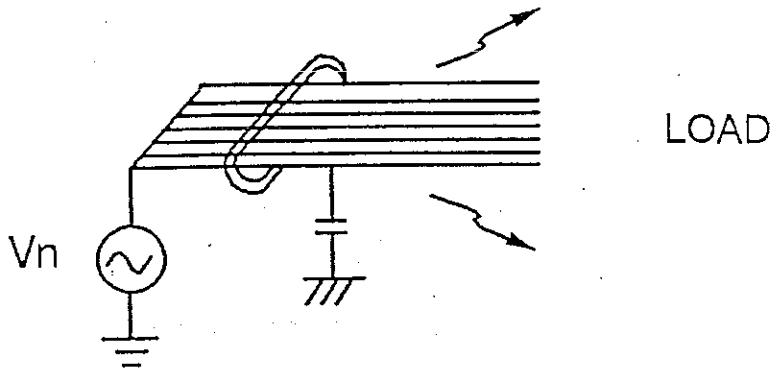


$$Z \approx 200 \Omega$$

$$Z_{L \max} \approx 1000 \Omega$$

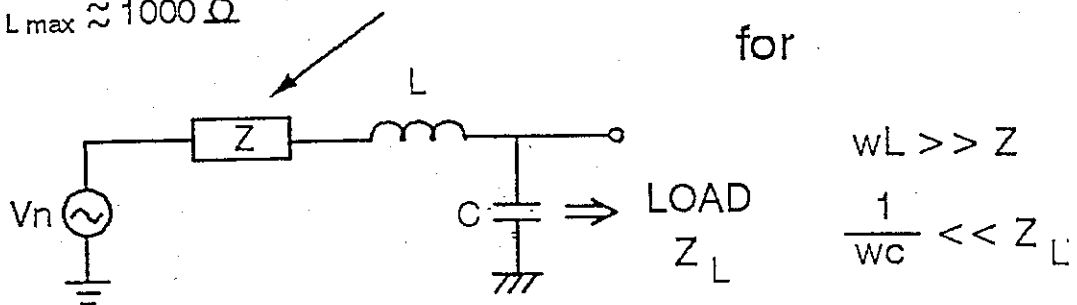


or

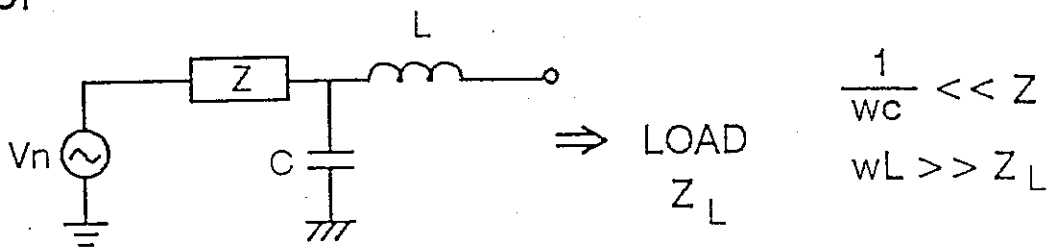


- Filter is effective for ESD protection also.

# Ferrite Chokes for Filtering

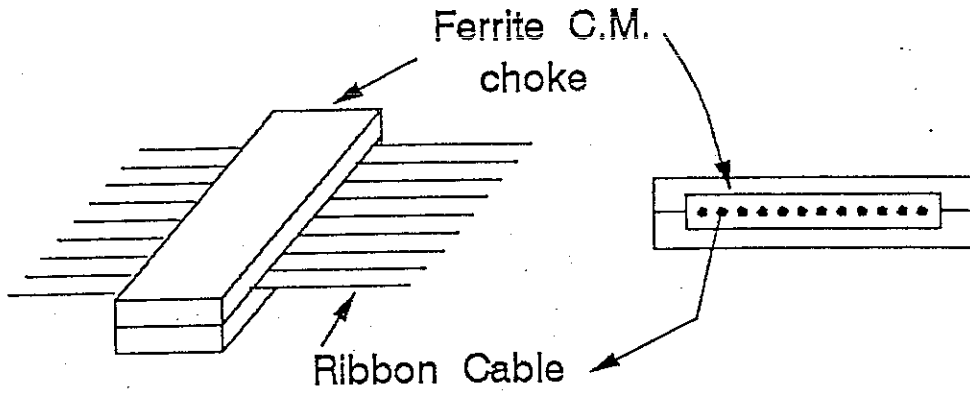


## Ferrite C.M. + D.M. chokes

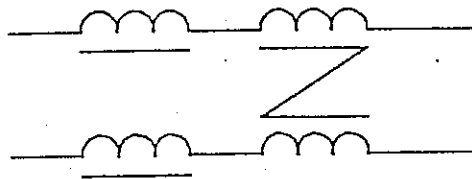
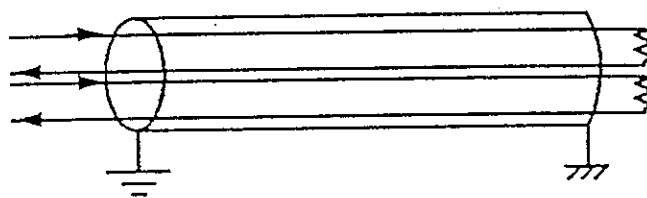
## Controlling C.M. Radiation from a Cable

- Reducing Ground Noise  $V_n$   
Use ground plane, ground grid,  
Separate ground for I/O
- Decoupling by Low ESL Capacitor
- Using Common - Mode Choke
- Using Shielded Cable ( or Tri - lead )



Ground both ends and terminate  
completely

# Ground Grid in PC Board


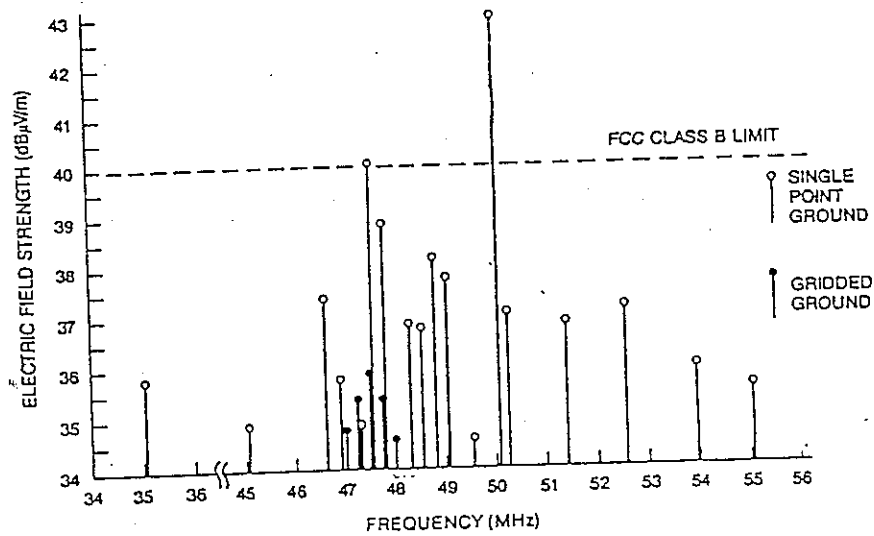
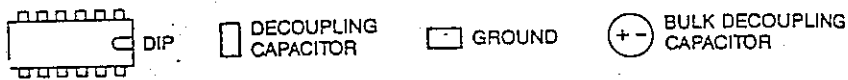
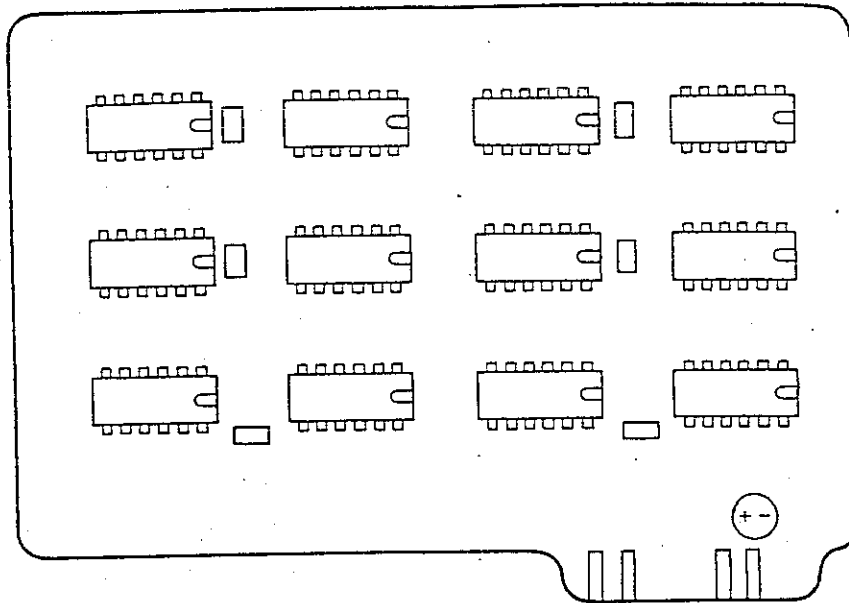



Figure 11-15. Measured radiated emissions from a printed wiring board, with and without a gridded ground (from German, 1985).

## Controlling C.M. Radiation

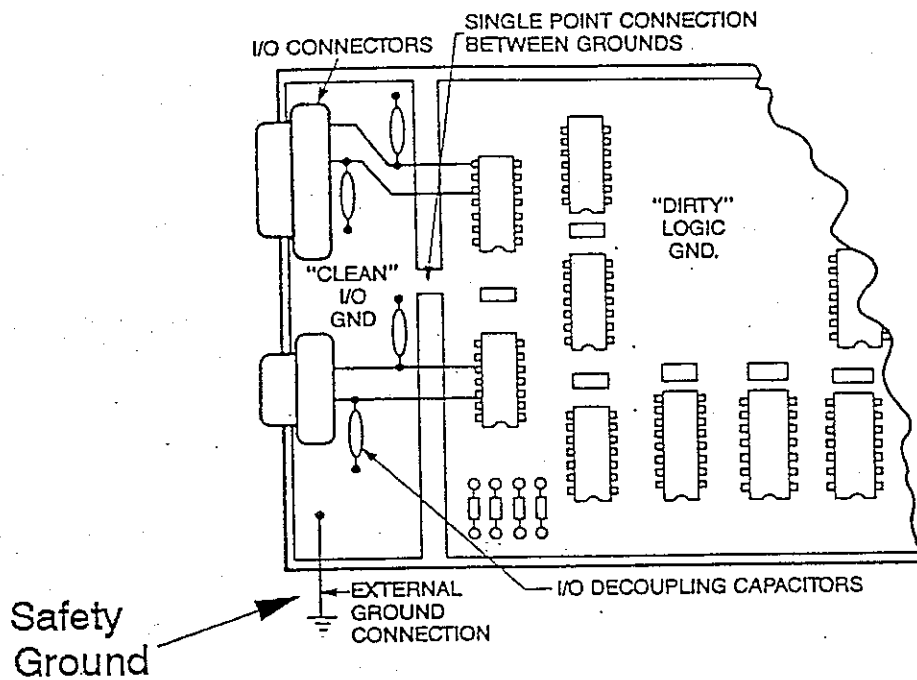


- I/O requires clean ground.
- All I/Os should be decoupled to clean ground before leaving system.

## Conducted Vs . Radiated

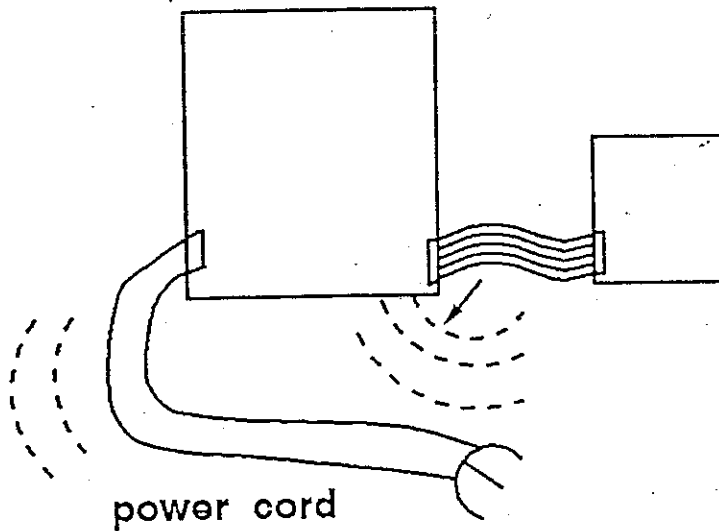

- Radiated noise may couple into Conducted measurement
- Conducted noise may couple into radiated measurement
- Both types of noises need to be taken into consideration at the same time
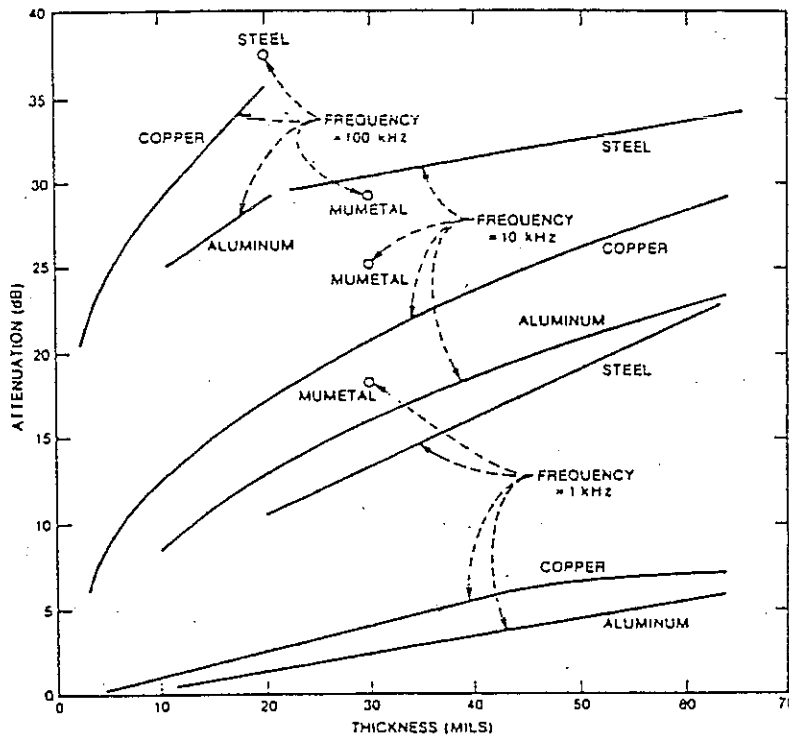
## Experimental Data on Magnetic Field Attenuation (Near Field)



- At Low freq. , Mumetal is most effective in reducing magnetic field .
- At high freq. , conductor make better shield than magnetic shield .
- At 100 KHz , Steel is only slightly better than copper .
- Permeability of magnetic material decreases with freq. Mumetal changes with freq. in a much drastic manner than steel .



## General Comments

- Using solid shield , it's relatively easy to obtain 90 dB of shielding effectiveness except for L.F. magnetic field .
- Shield discontinuity ( holes , seams ) has more effect on EMI than matreial .
- The amount of leakage depends on
  - max. linear dimension ( not area ) of opening
  - frequency of source
  - wave impedance
- Discontinuity has more effect on magnetic field leakage than electrical field leakage

## Controlling Leakage

H ←


- Large number of small holes produce less leakage than one long hole

- Avoid opening greater than  $1/20$  of  $\lambda$   
(this provides at least 20 dB)

MHz	max. length (in)
30	18
100	6
500	1.2

- Avoid having large number of holes on the same side

# Shielding Effectiveness of Slot

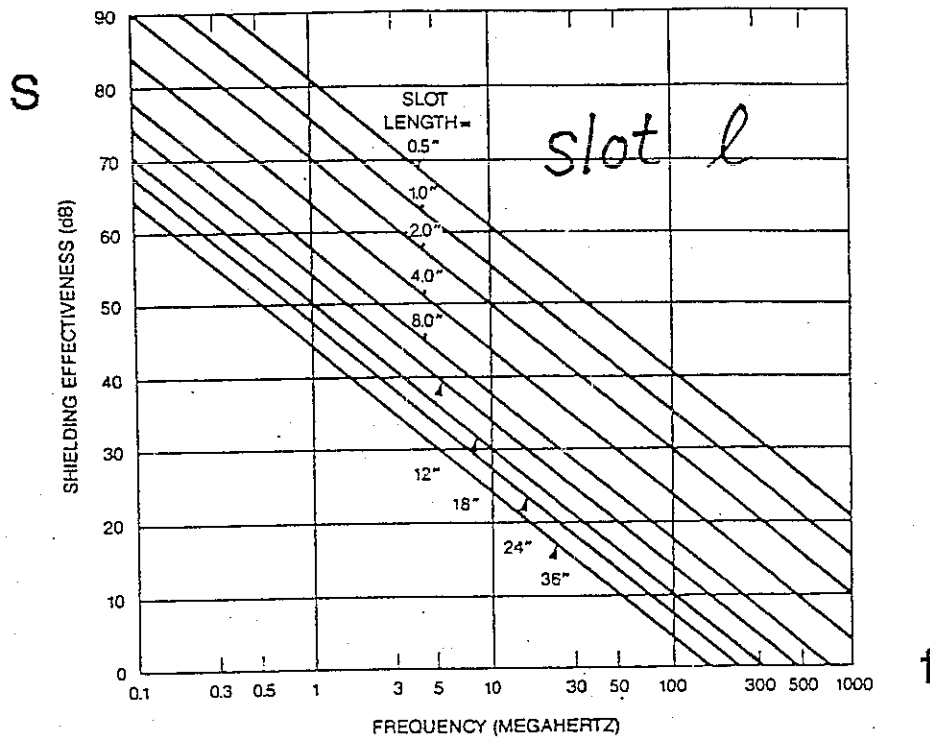

$$S = 20 \log \frac{\lambda}{2l}$$

- Applies if  $\frac{\lambda}{2l} > 1$  (when  $\frac{\lambda}{2l} < 1$ )  
 $S = 0$
- Single slot