

Full Wave Bridge Operation for $V_{inac} = 85V - 265V$

Appendix B

1. A rule of thumb for C_{in} selection:

$$2 \cdot \frac{mF}{W} - 3 \frac{mF}{W}$$

2. With $P_{in} := 75 \cdot W$, C_{in} should be:

$$C_{in} := 2 \cdot \frac{mF}{W} \cdot P_{in}$$

$$C_{in} = 150 mF$$

3. The discharge of C_{in} with the dischargingtime of $\frac{T}{2} - t_c$ provides all the energy

required by the load:

$$P_{in} \cdot \left(\frac{T}{2} - t_c \right) := \frac{1}{2} \cdot C_{in} \cdot (V_{1pk}^2 - V_{1min}^2) \quad (1)$$

T is the line switching period. With $F_{ac} := 50 \cdot \text{Hz}$, $T := 20 \cdot 10^{-3} \cdot \text{s}$

Charging time t_c of C_{in} is estimated as $t_c := 3 \cdot 10^{-3} \cdot \text{s}$

Minimum Peak input voltage at $V_{acmin} := 85 \cdot \text{V}$ is $V_{1pk} := V_{acmin} \cdot \sqrt{2}$, $V_{1pk} = 120.208 \text{ V}$

4. Calculate V_{1min} based on (1):

$$V_{1min} := \sqrt{V_{1pk}^2 - \frac{2 \cdot P_{in} \cdot \left(\frac{T}{2} - t_c \right)}{C_{in}}} \quad (2)$$

$$V_{1min} = 86.313 \text{ V}$$

