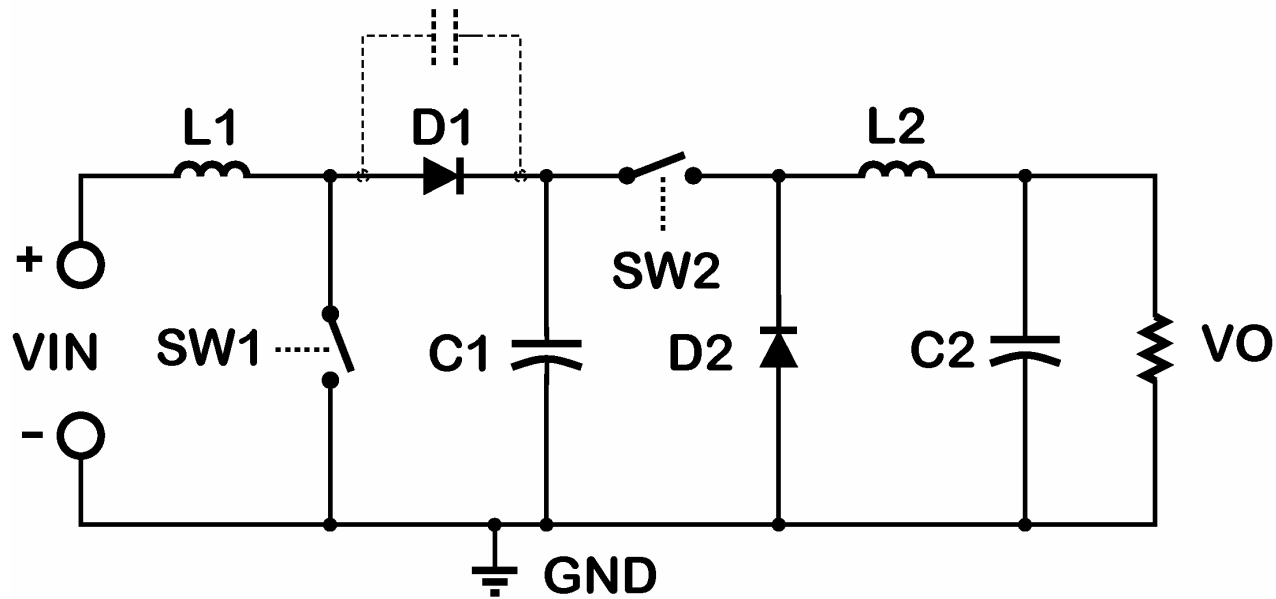


# Reduce the 400V Boost Capacitor



**A Cascade Boost-Buck Power Converter  
Without Synchronous Switching**


**Leading Edge Modulation PFC**

**+**

**Trailing Edge Modulation PWM**

- **to reduce the 400V Boost Capacitor value by 20%**
- **Bandwidth increases**
- **Higher Efficiency**
- **Better reliability**


## Reduce the 400V Boost Capacitor

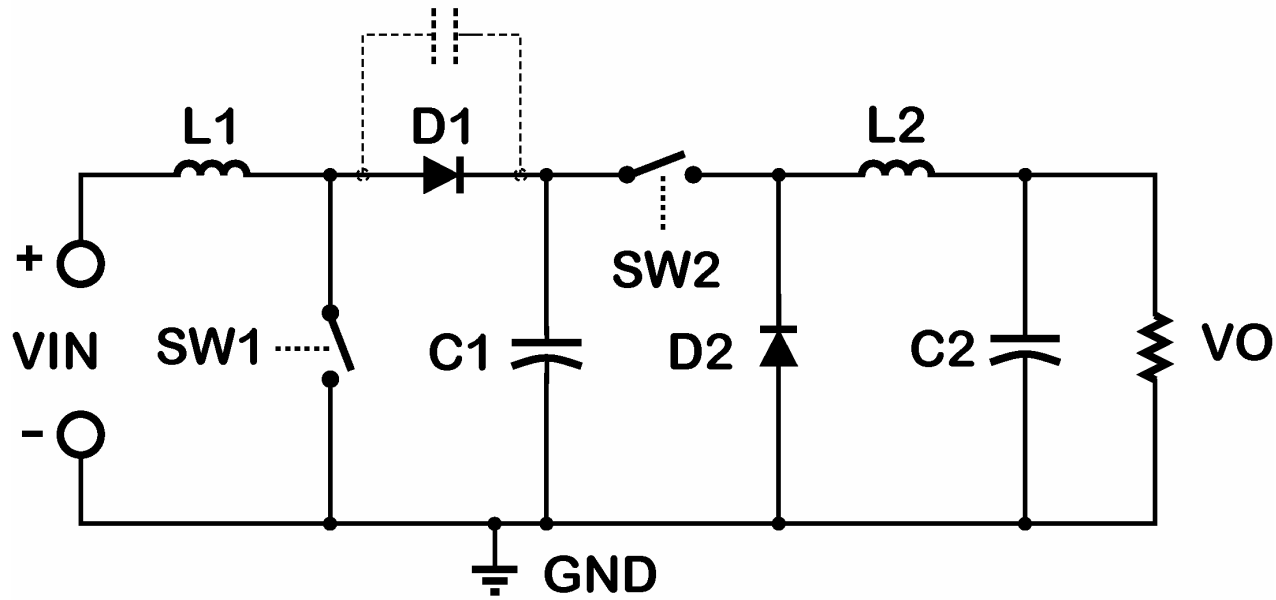

A Cascade Boost-Buck Power Converter  
Without Synchronous Switching

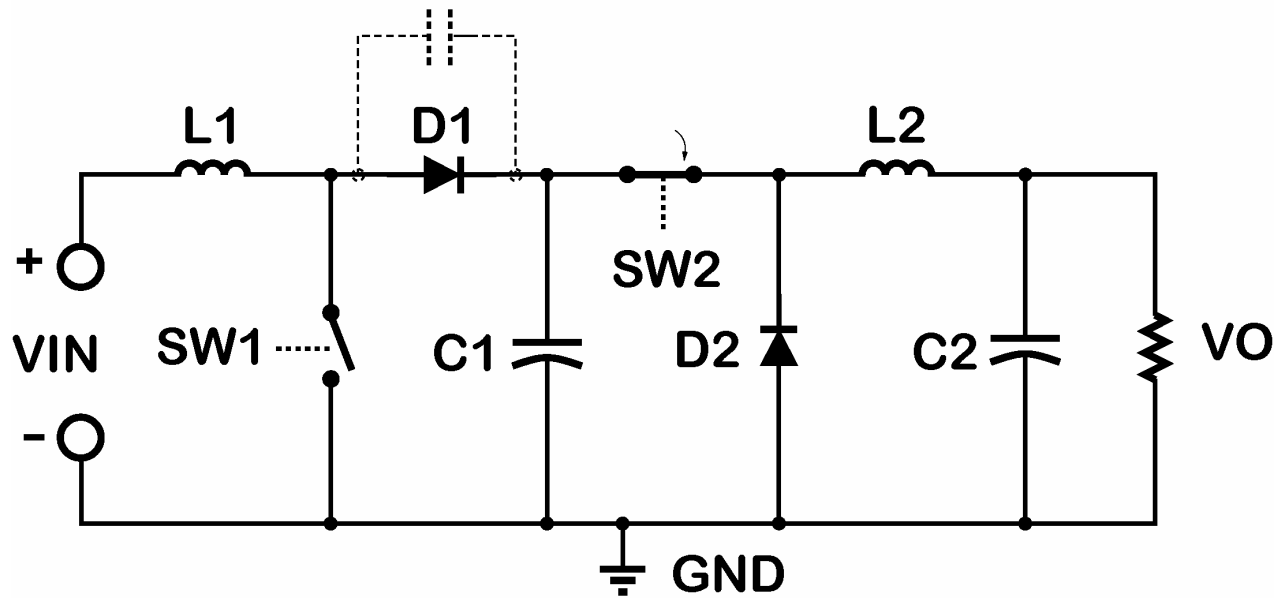
## Reduce the 400V Boost Capacitor

Leading Edge Modulation PFC and Trailing Edge Modulation PWM for PFC Output Ripple Reduction




Synchronous Switching Cascade Power Converter
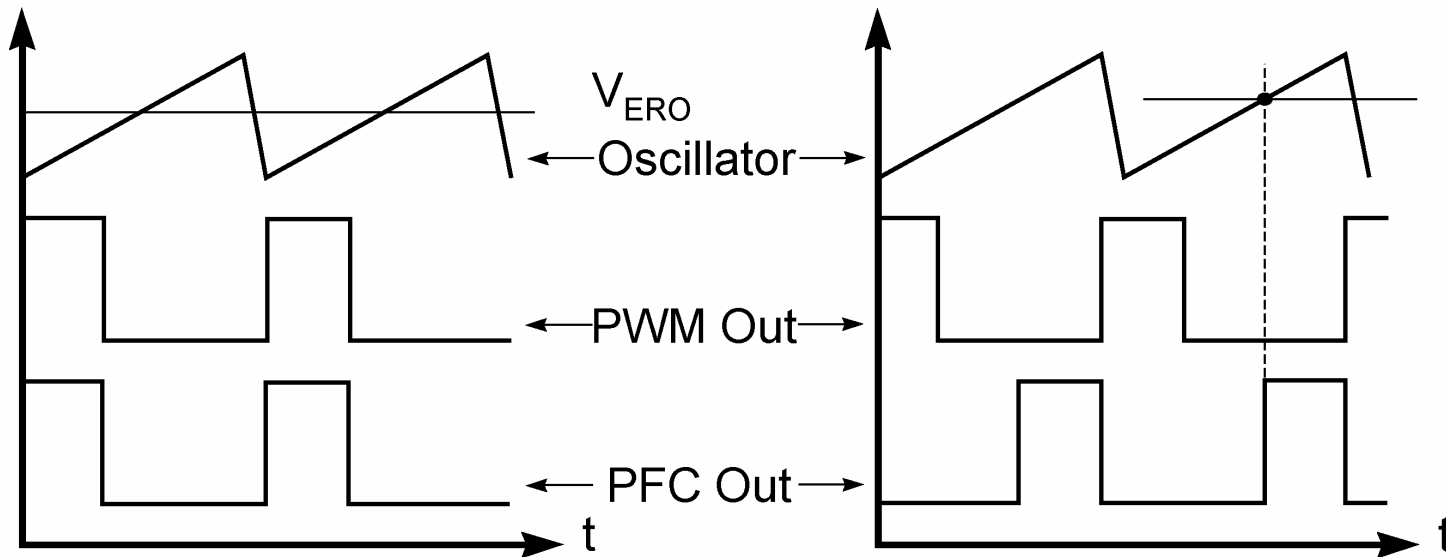
## The ML4824 vs "Other" Combo Controllers







Conventional Combos use Trailing/  
Trailing Edge Modulation Scheme.



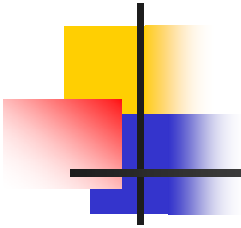
The ML4824 uses Trailing Edge  
PWM and Leading Edge PFC for  
Optimum PFC to PWM Inductor  
Charge Transfer.




## Reduce the 400V Boost Capacitor

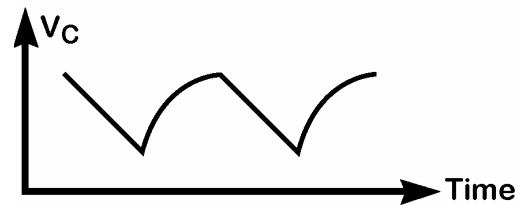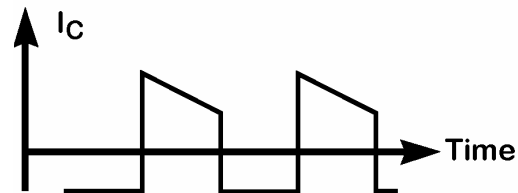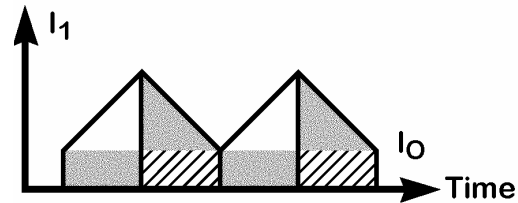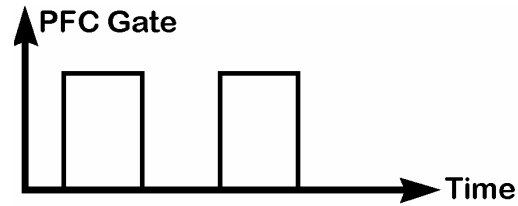

Boost Stage with a Constant Current Loss

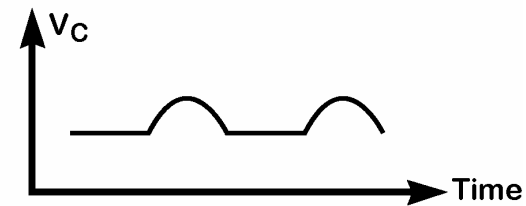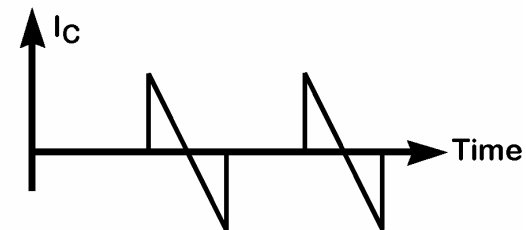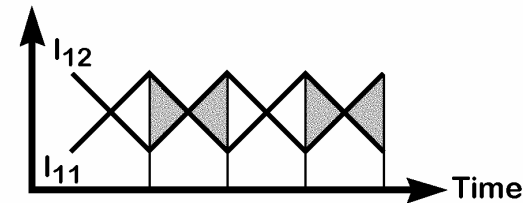

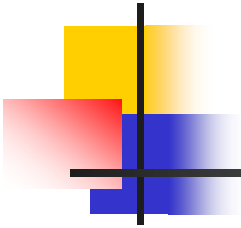Cascade Power Stage with Synchronous Switching




## Reduce the 400V Boost Capacitor


### ML4824 vs. ML4819 EXPERIMENTAL RESULTS

Test Conditions:  $V_{IN} = 220VAC$ ,  $P_{IN} = 75W$ ,  
 $f_{PFC} = 80kHz$ ,  $C_{PFC} = 50\mu F$ ,  $L_{PFC} = 1.5mH$

#### ML4824 TEST RESULTS

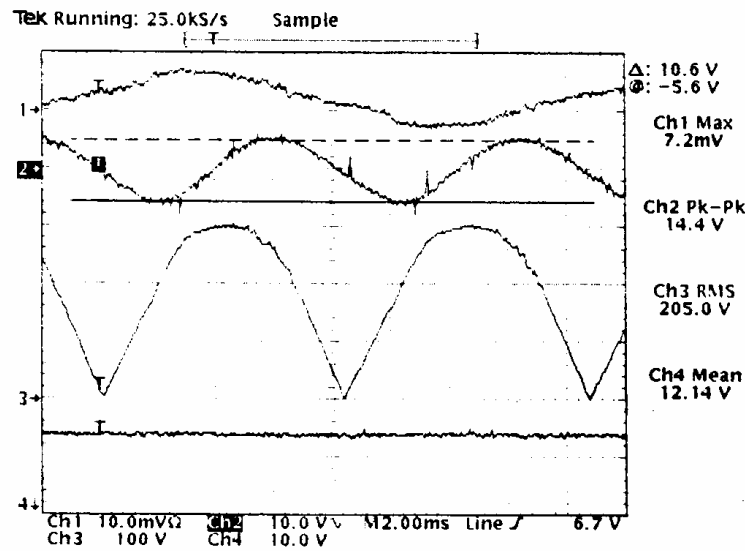


#### ML4819 TEST RESULTS

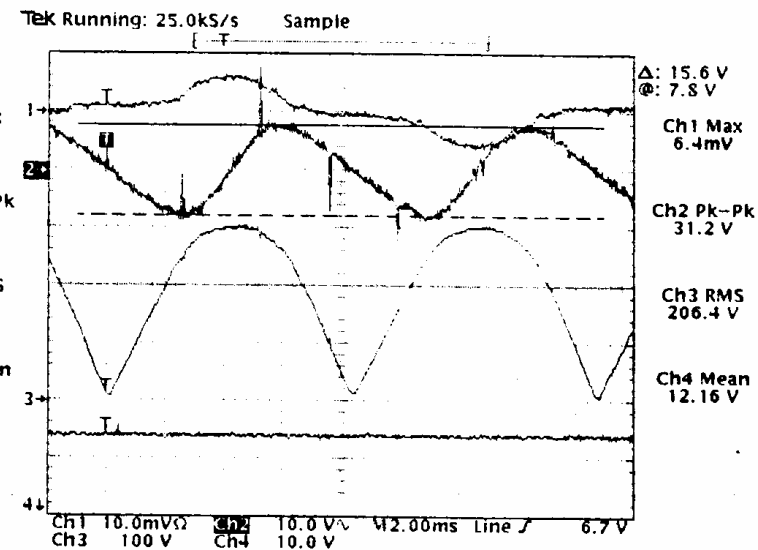


# 6800 Basic

## CM6800 Block


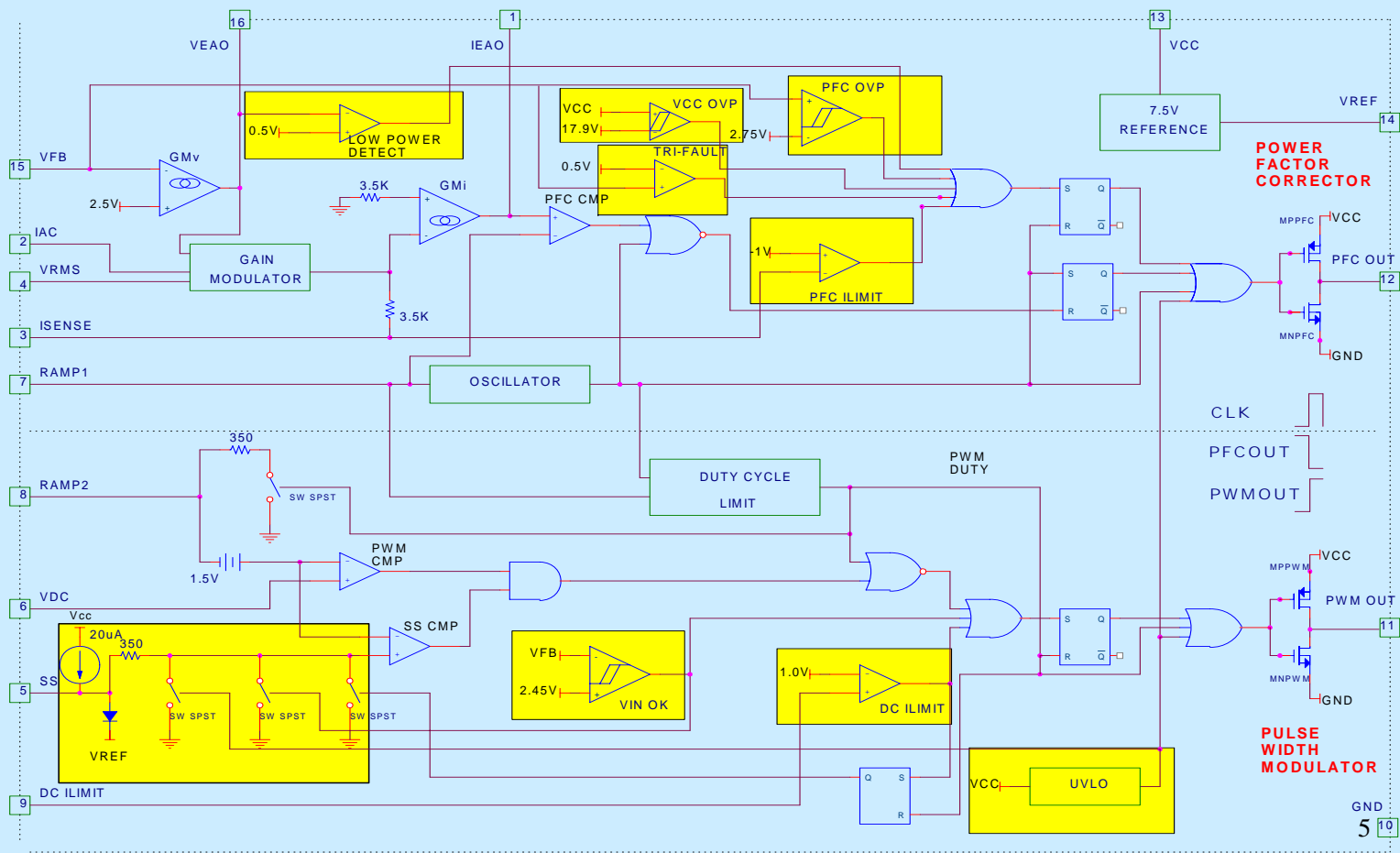





# PFC Block

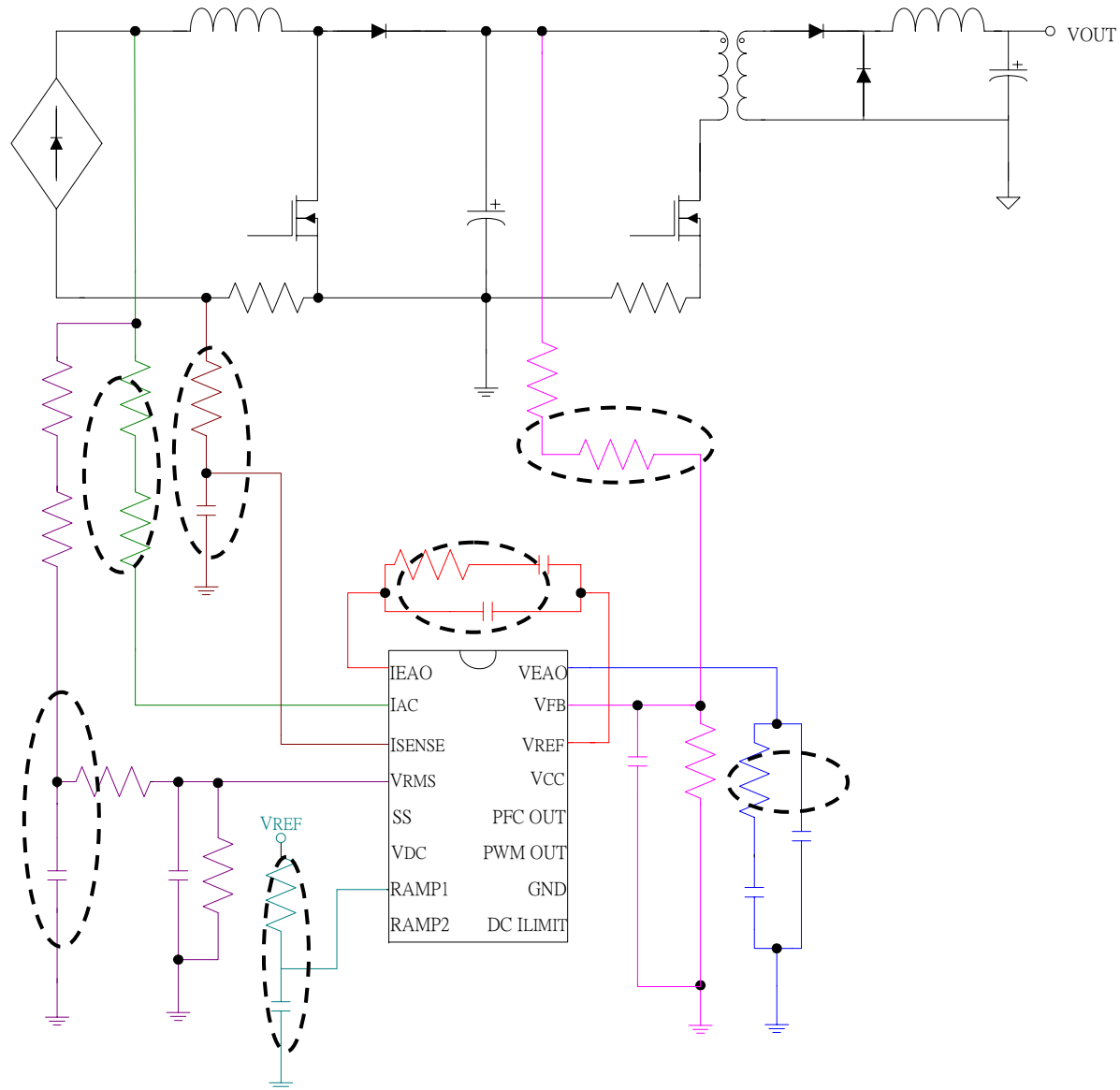


# PWM Voltage Mode

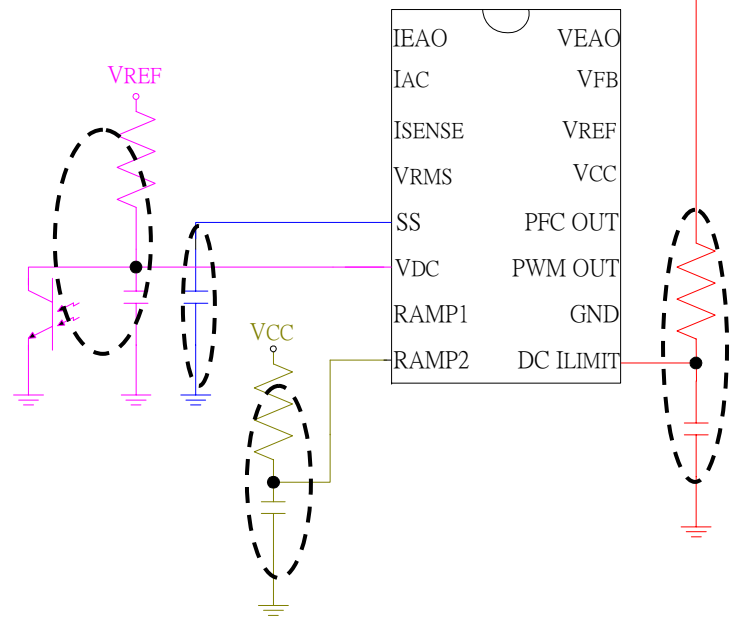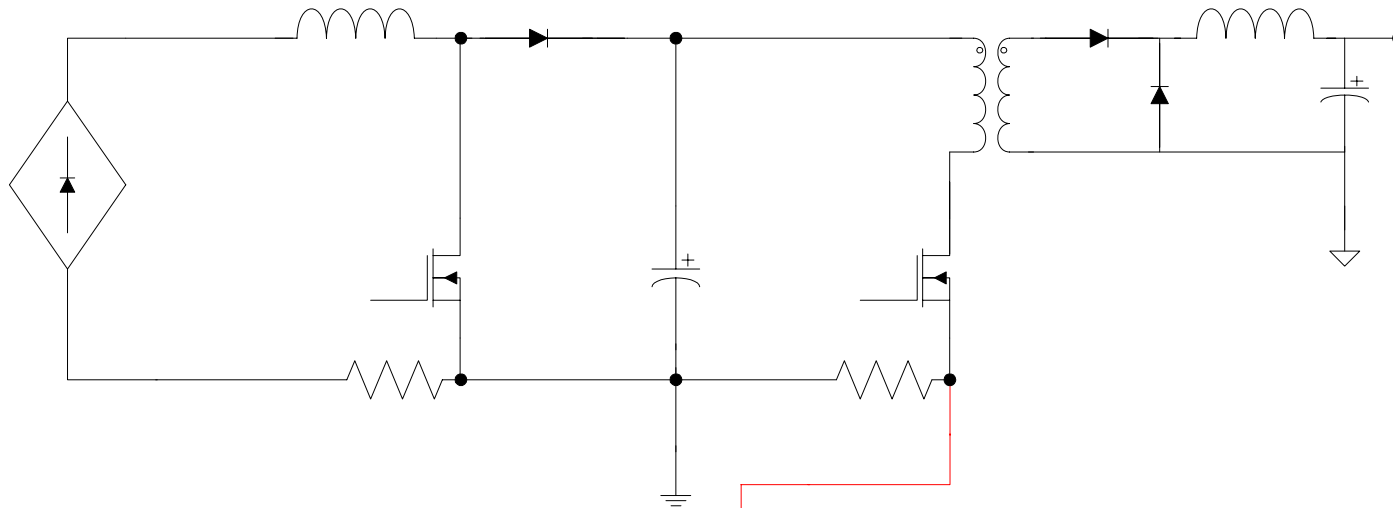



# PWM Current Mode

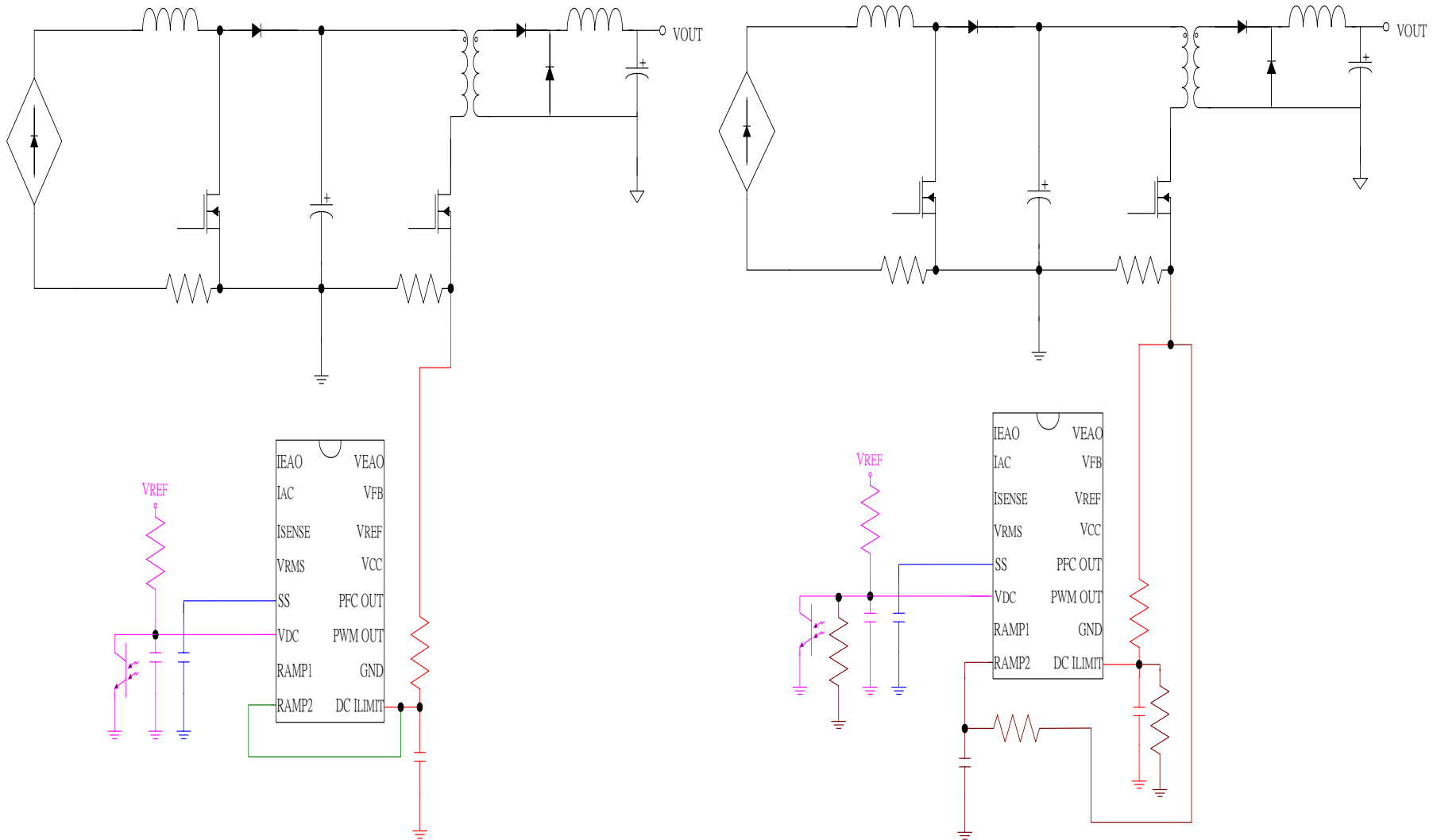

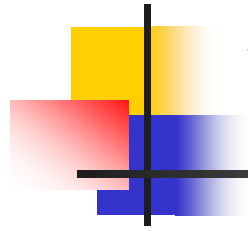


# Voltage與Current Mode比較

	Layout	Dynamic Transient
Voltage Mode	Good	Ordinary
Current Mode	Ordinary	Good

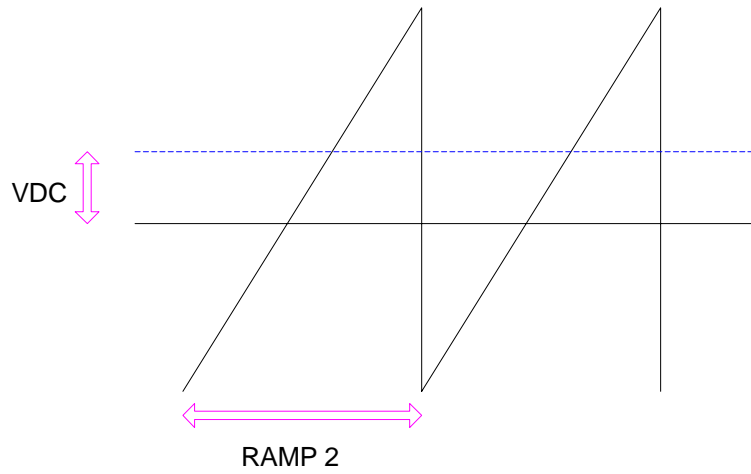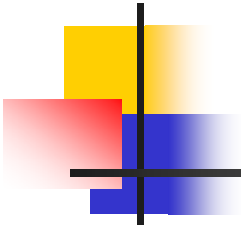

Voltage Mode

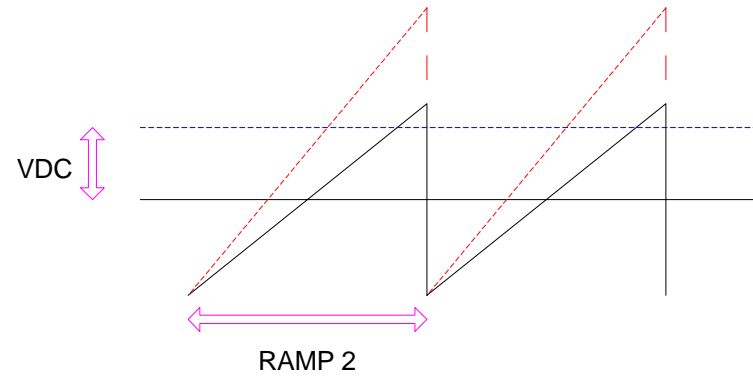

Current Mode



# Functions

---


PFC :

- PFC turn-on
- PFC turn-off
- VCC O.V.P
- VCC U.V.L.O

PWM :


- PWM stage
- Soft Start
- PWM current limit

# VCC O.V.P

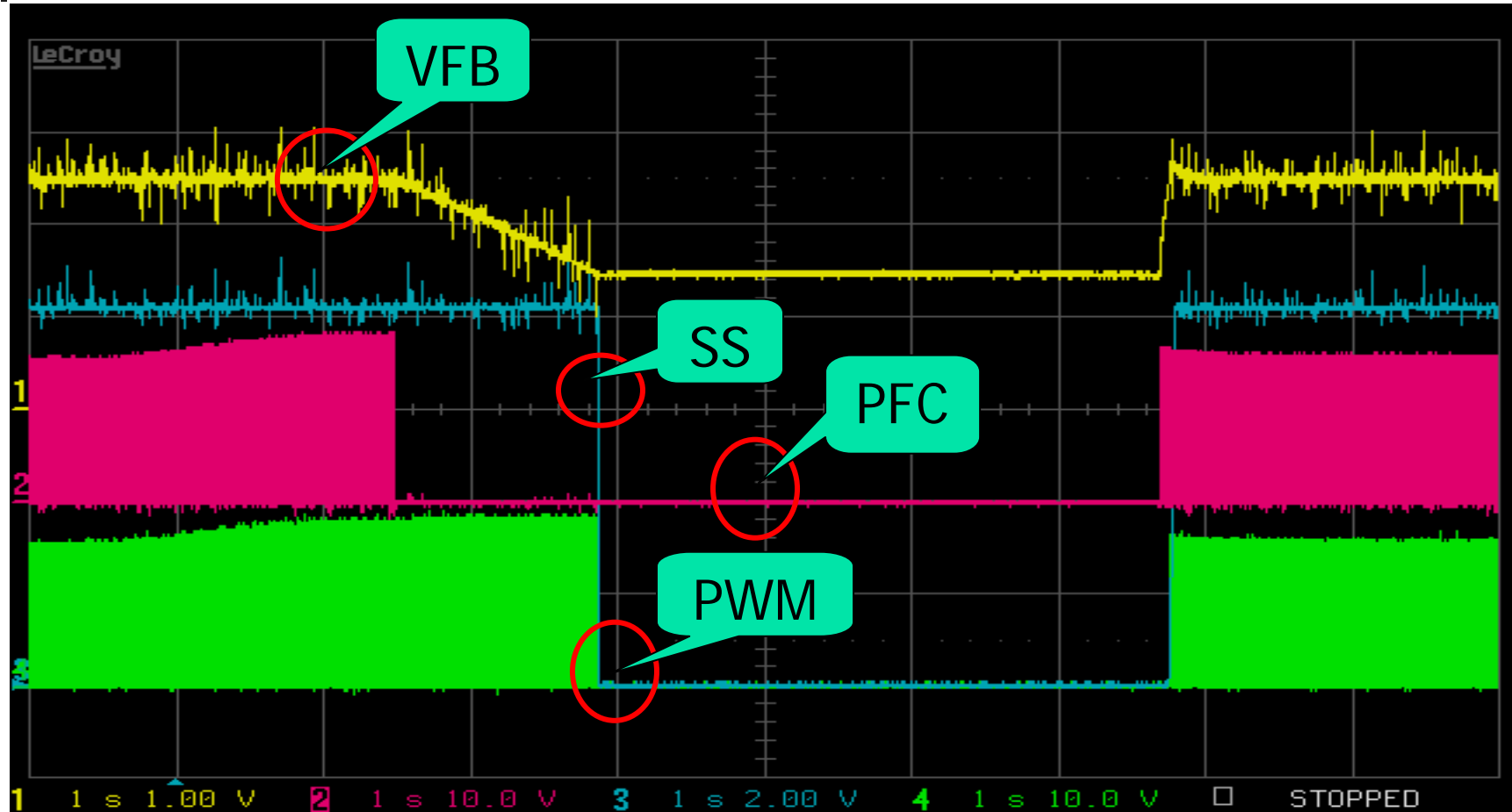

VCC=19V → PFC turn-off → Vin OK(X) → PWM turn-off  
(VCC OVP)


# VCC U.V.L.O

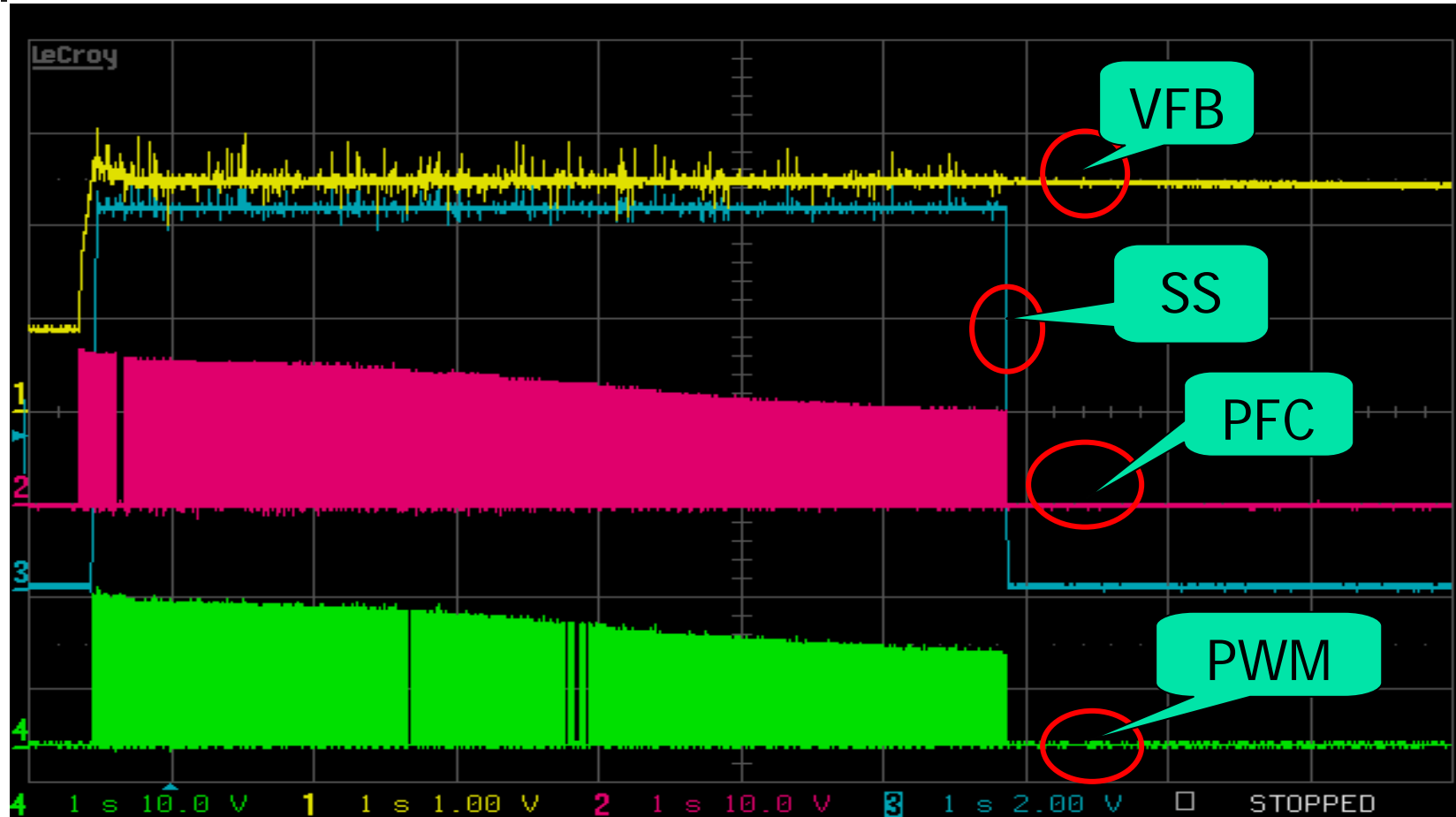

VCC=9V(U.V.L.O) → PFC turn-off  
PWM turn-off




# PFC turn-on

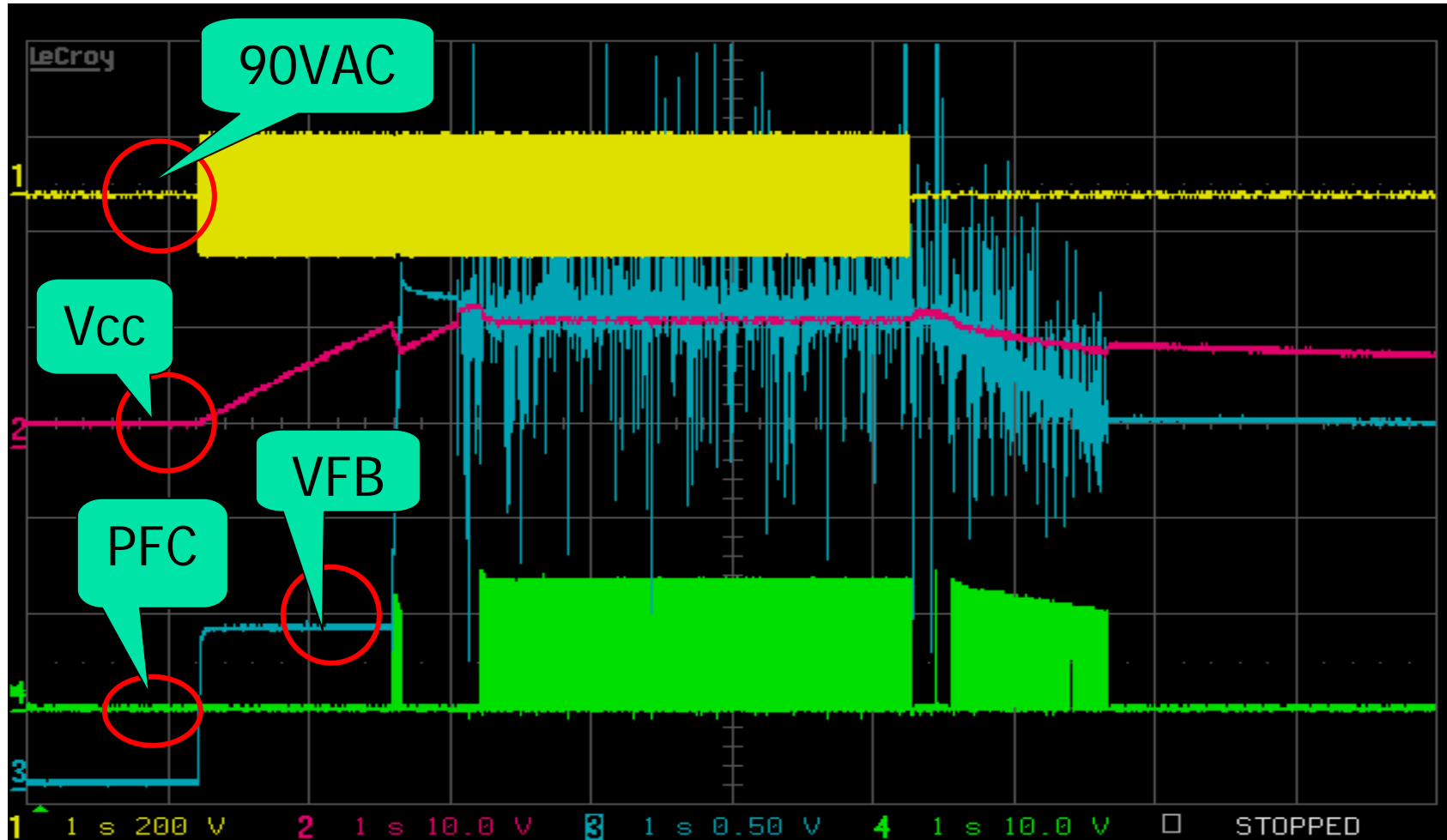


Vin OK → Vcc OK → VFB > 0.5V → PFC turn-on  
VFB = 2.5V → PFC stage OK

# PFC turn-off

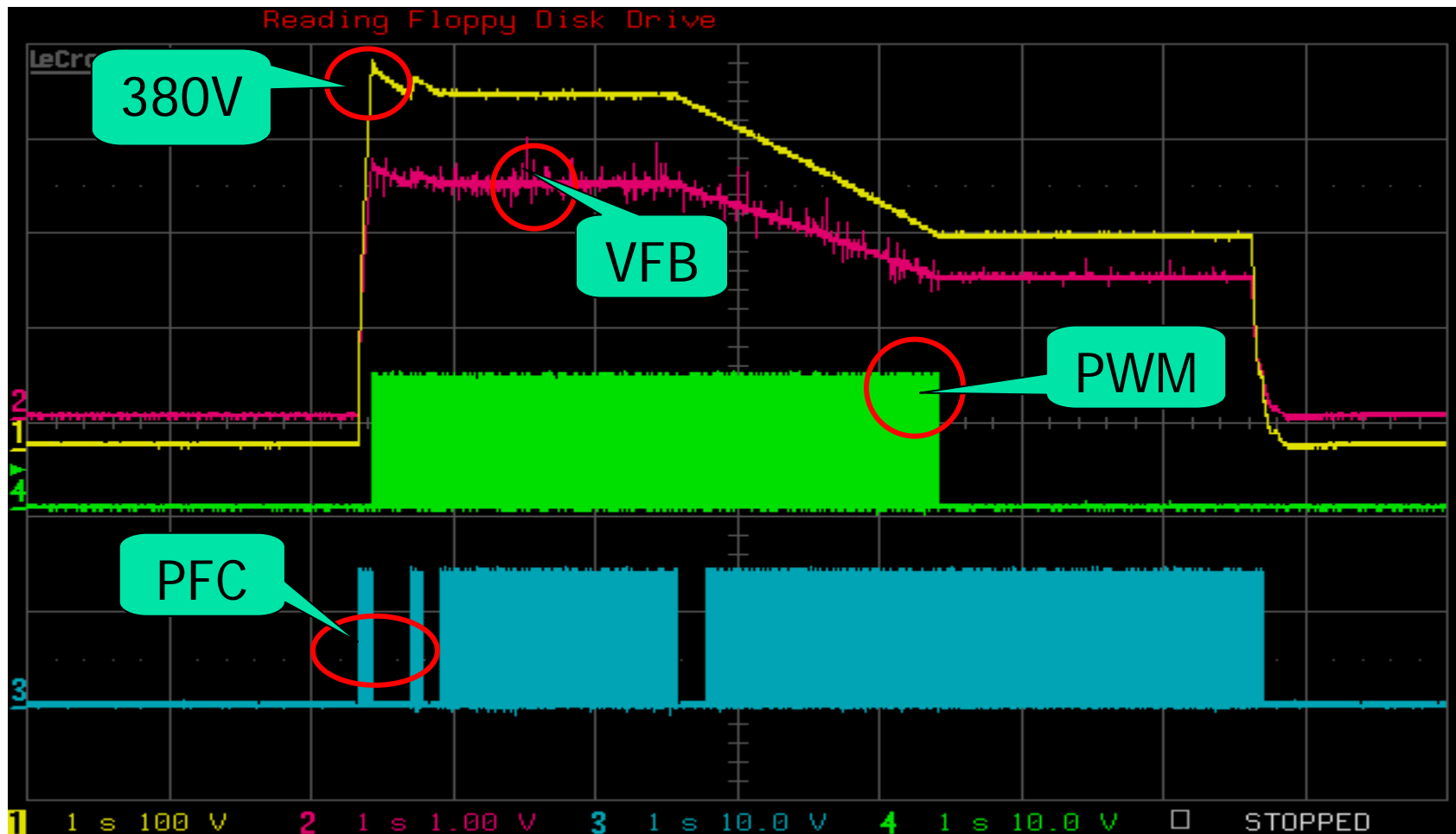

VFB < 0.5V → PFC turn-off


# PWM stage

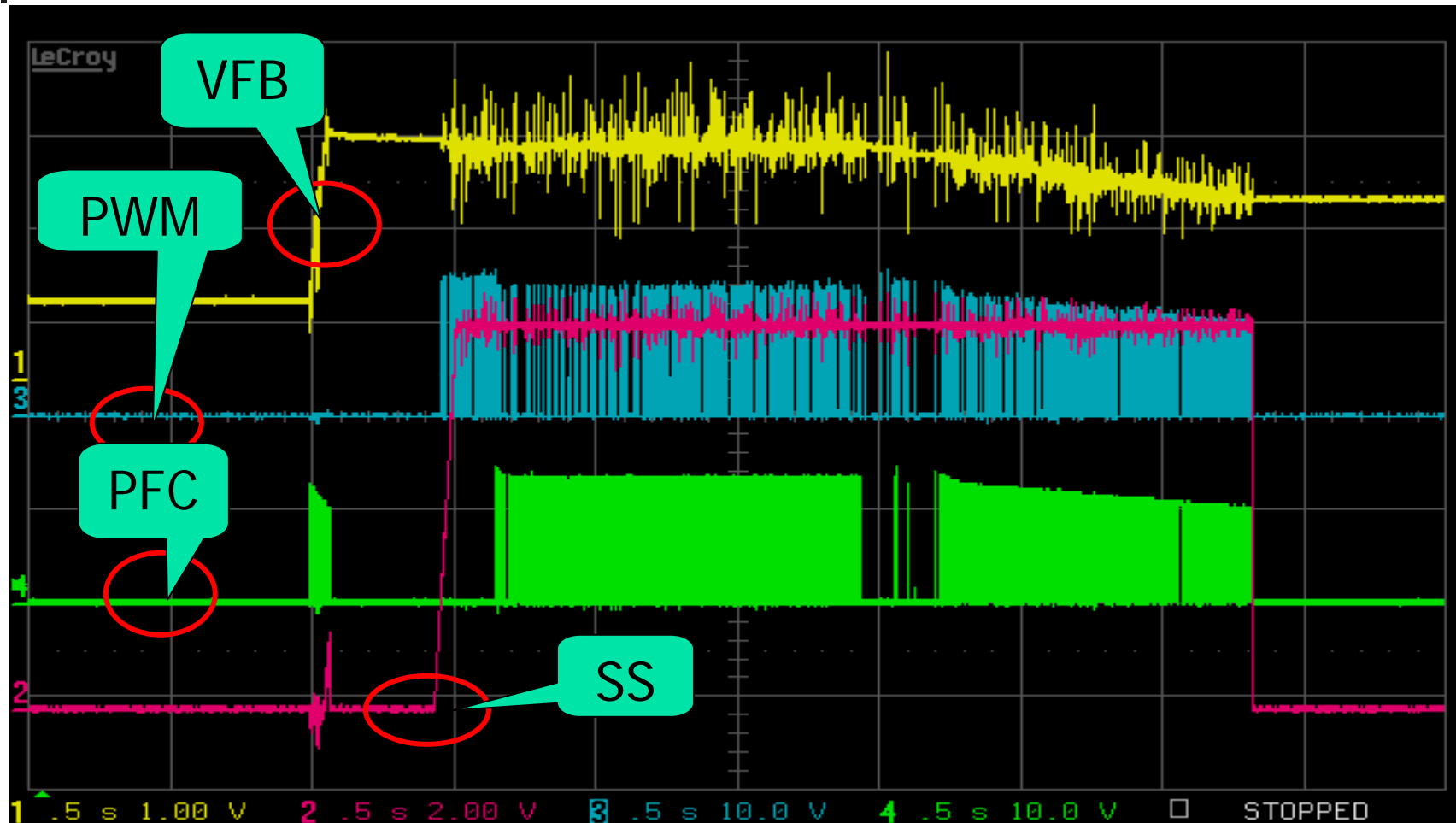


$V_{FB} > 2.45V \rightarrow V_{SS} > 1.25V \rightarrow$  PWM turn-on

$V_{FB} < 1.5V \rightarrow$  PWM turn-off

# Summary

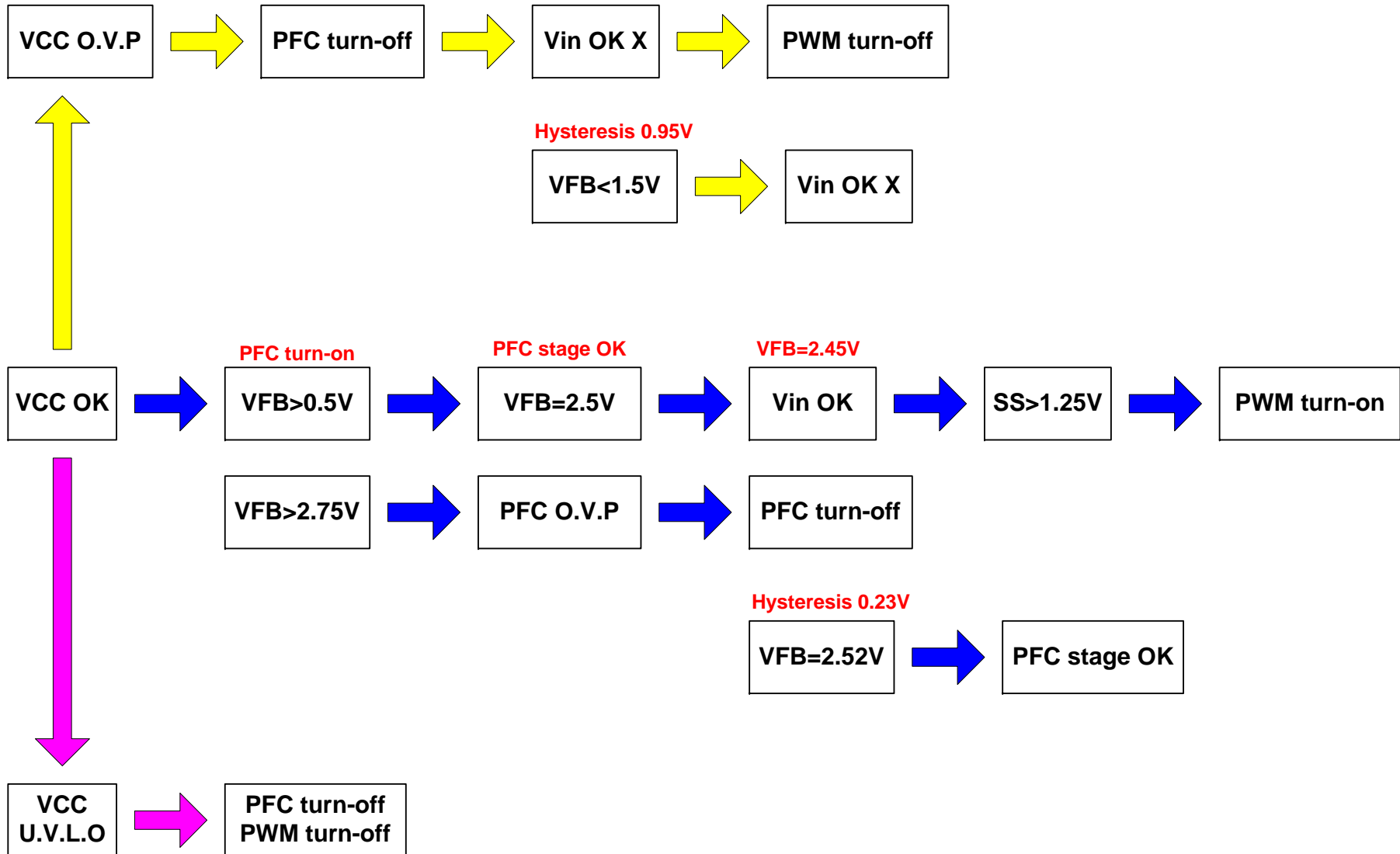


# Soft Start

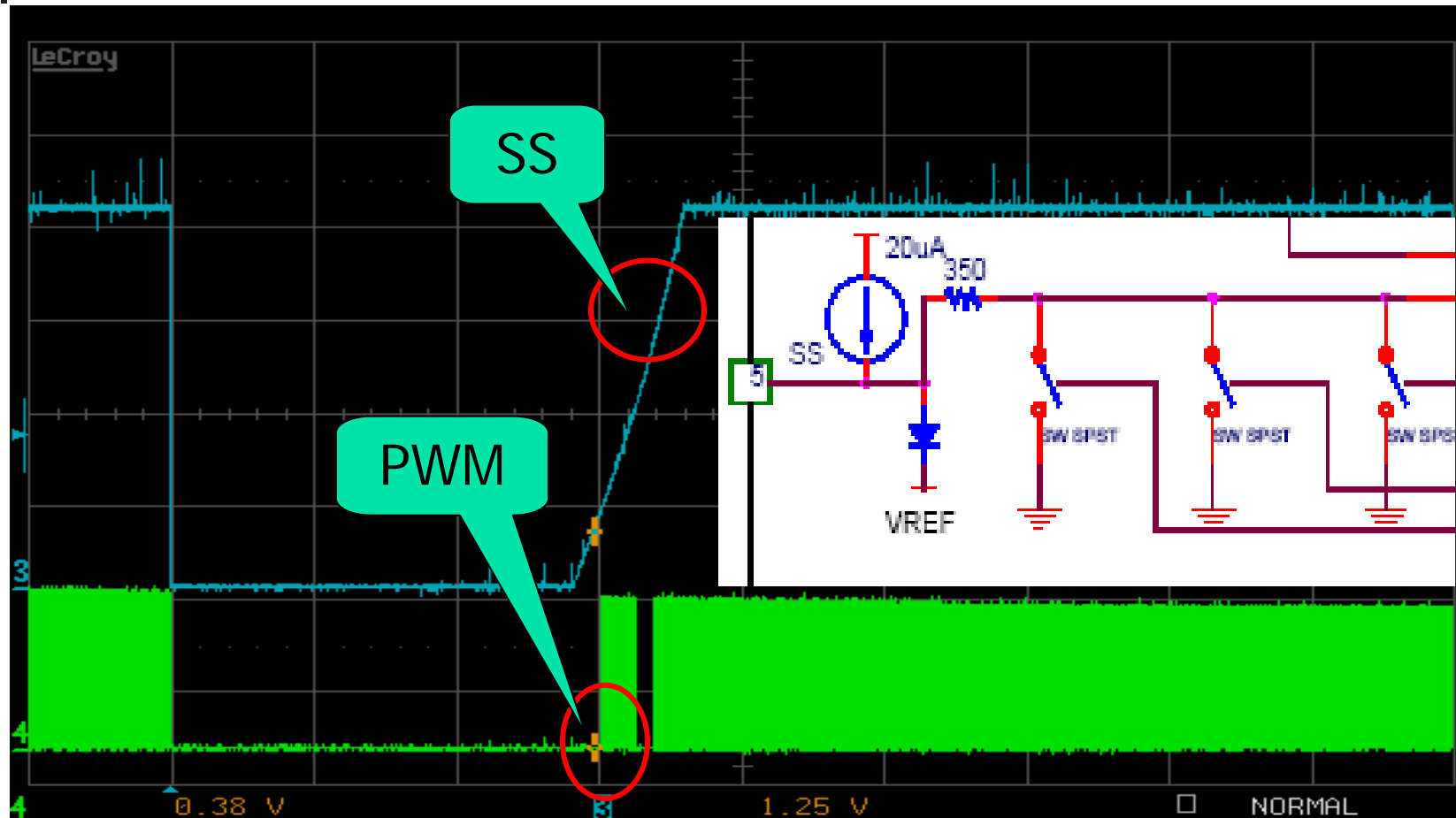

- UVLO
- SW SPST → VIN OK
- DC ILIMIT

# DC ILIMIT

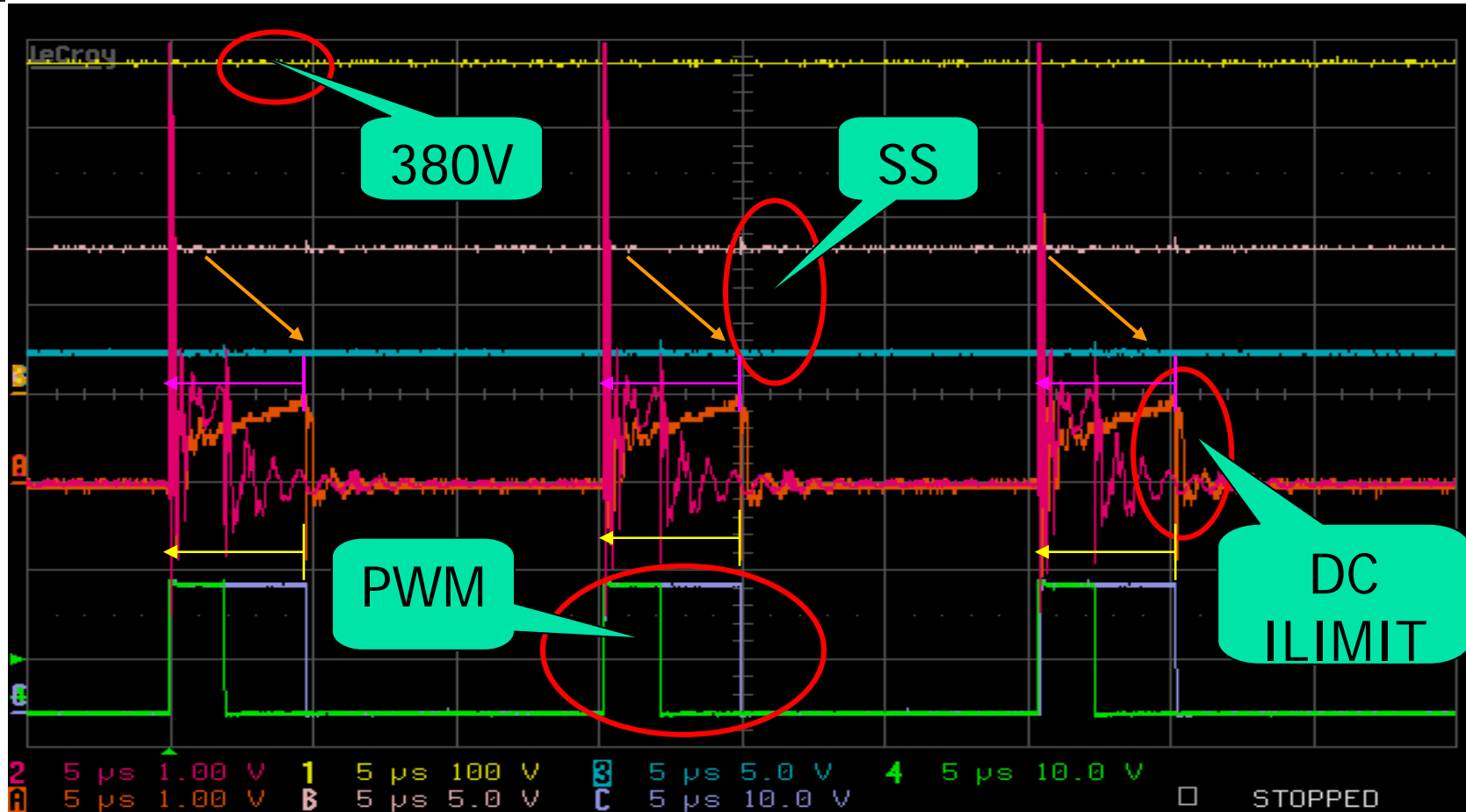

SS from 8V to 2V

Duty Cycle from 32% to 12%



# Speed up the PFC Voltage Loop 3X

---

Error Amplifier


Transconductance Amp, GM

vs.

Operational Amp, OP


# OP Integrator

PFC BOOST OUTPUT  
380V

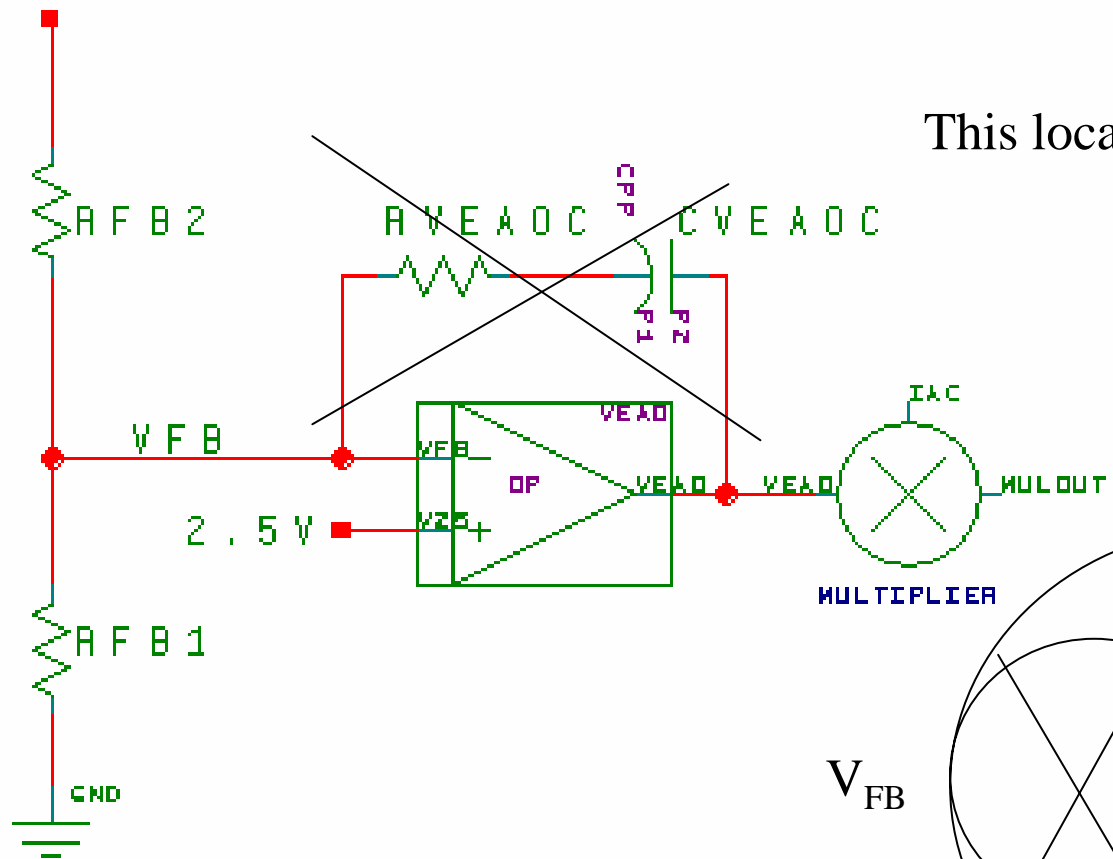

This local feedback is bad!

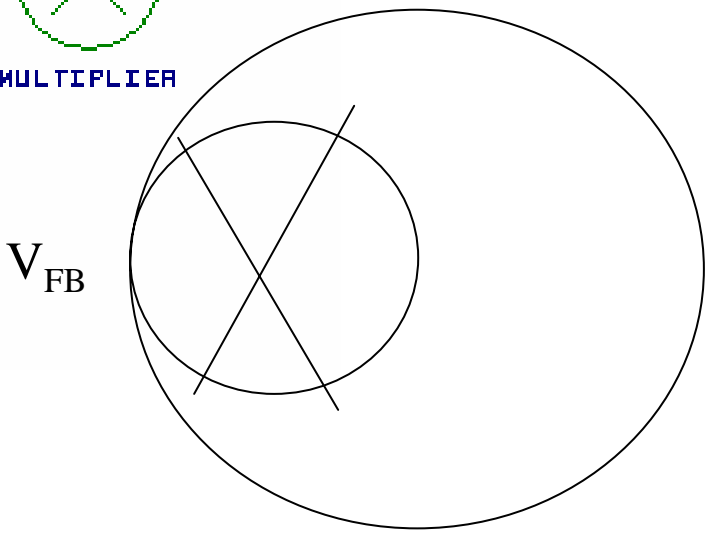
The Miller Effect slows down the  $V_{fb}$  node.  
Also, PFC Voltage Loop is very slow.  
The consequence:  $V_{fb}$  becomes very slow.






Speed up the PFC Voltage Loop 3X


PFC BOOST OUTPUT  
380V

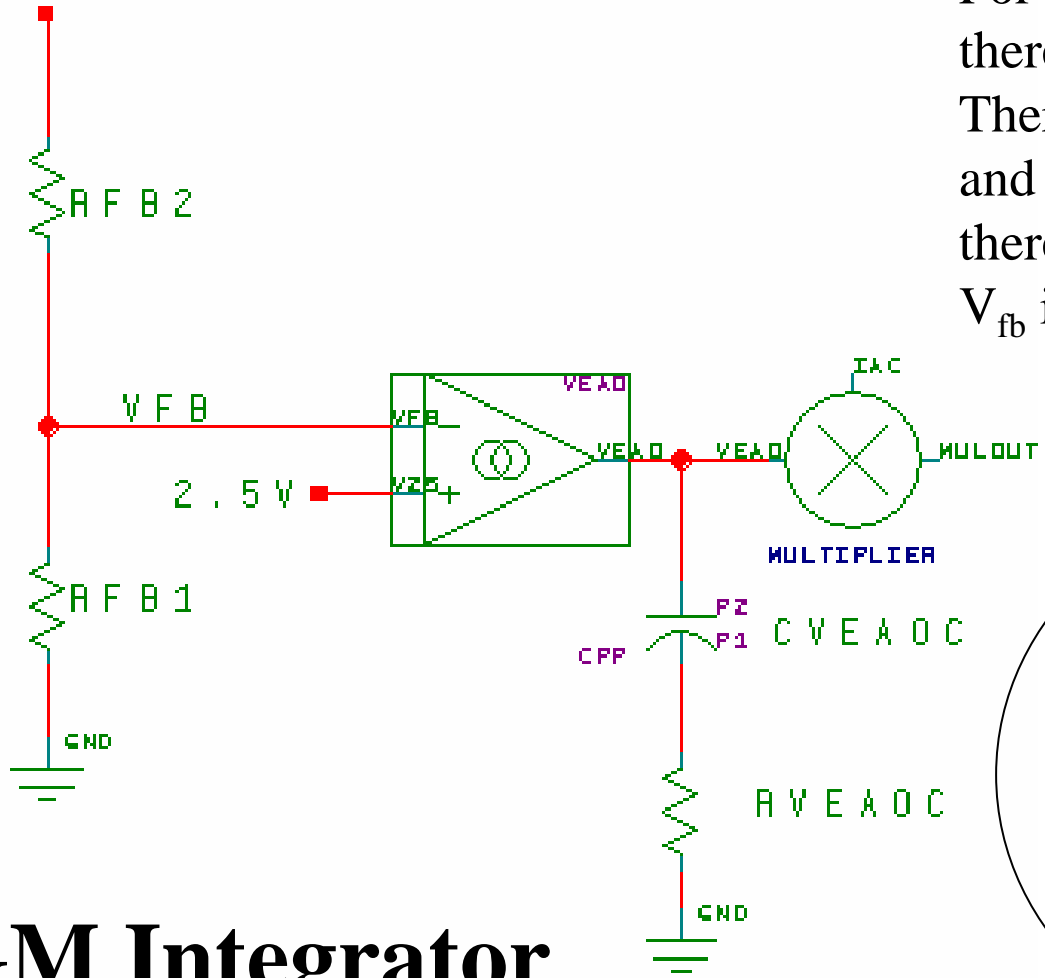

For GM,  
there is no local feedback.  
There is only one outer loop  
and  
there is no inner loop.  
 $V_{fb}$  is a much faster node.


**GM Integrator**

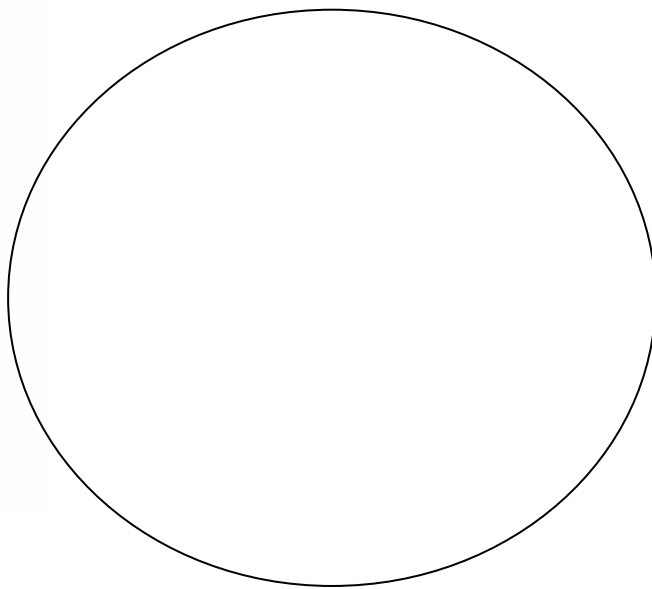


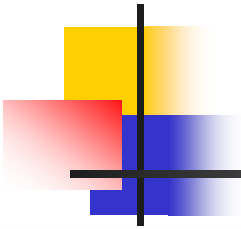


# Speed up the PFC Voltage Loop 3X



Easy to meet UL1950

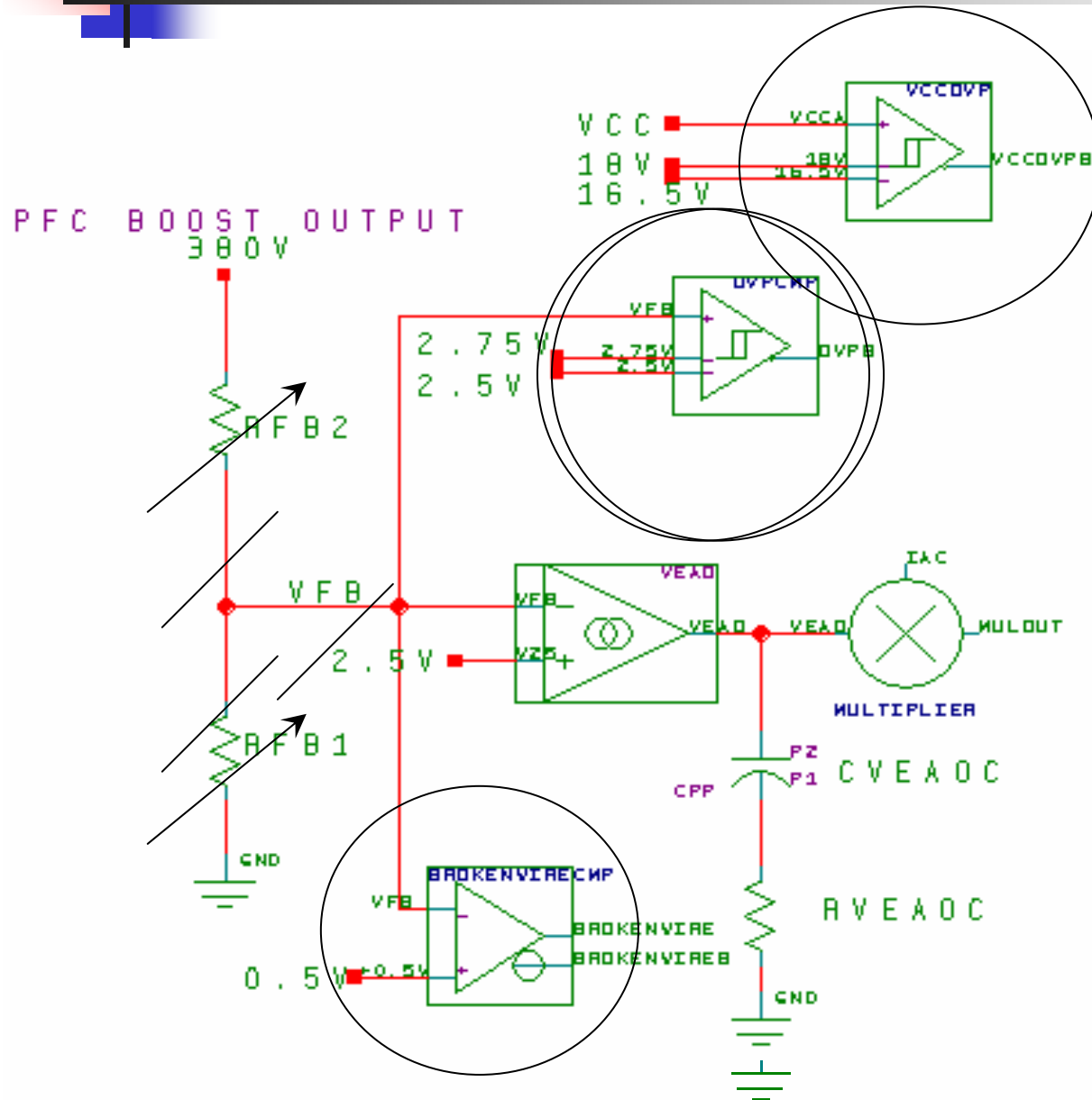



# CASE 1

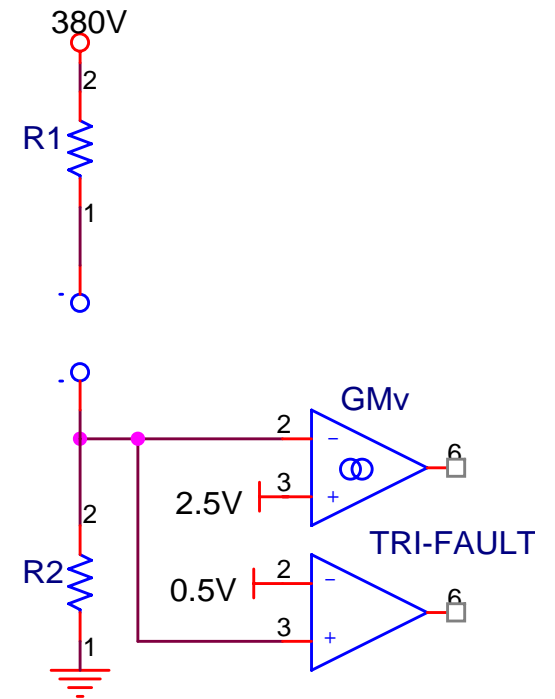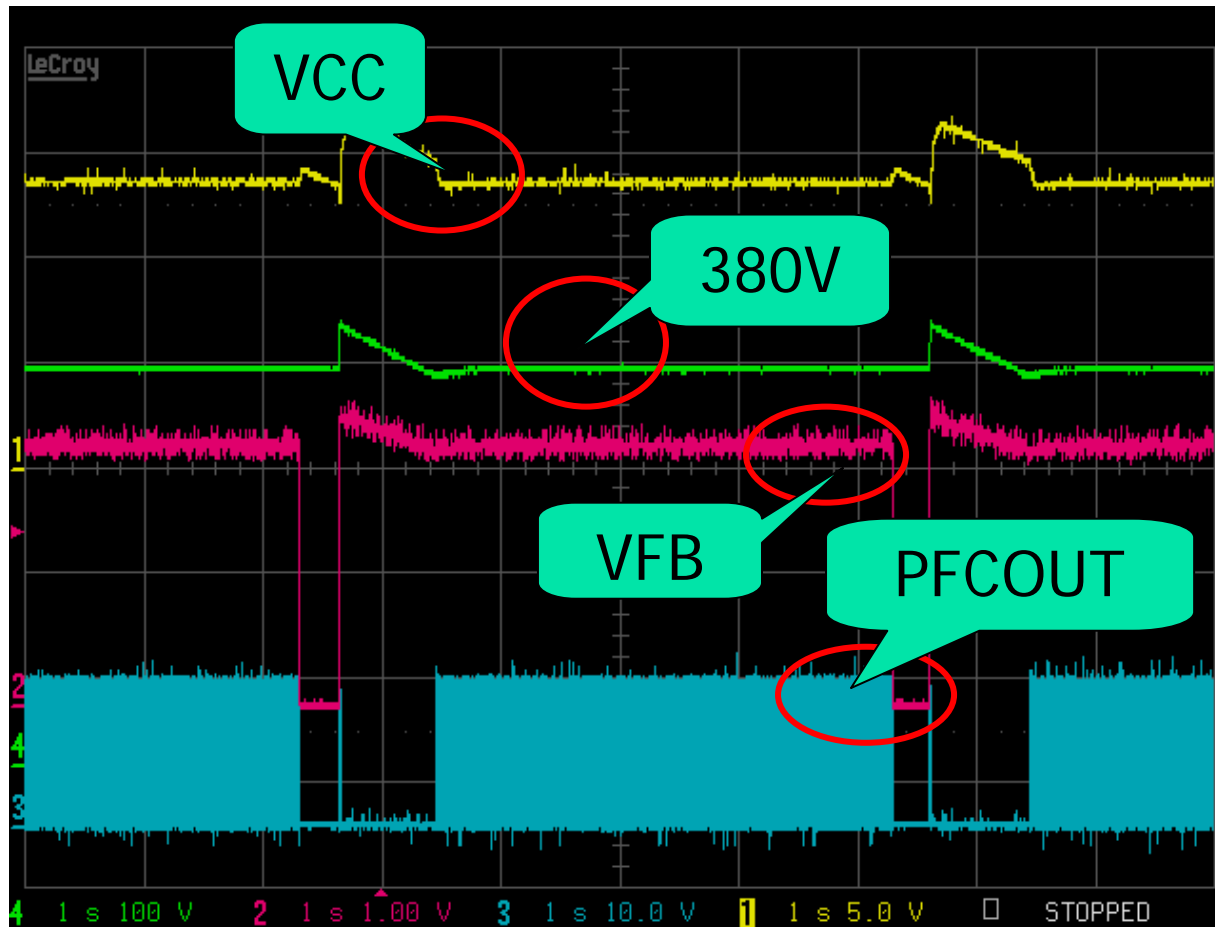

# CASE 2

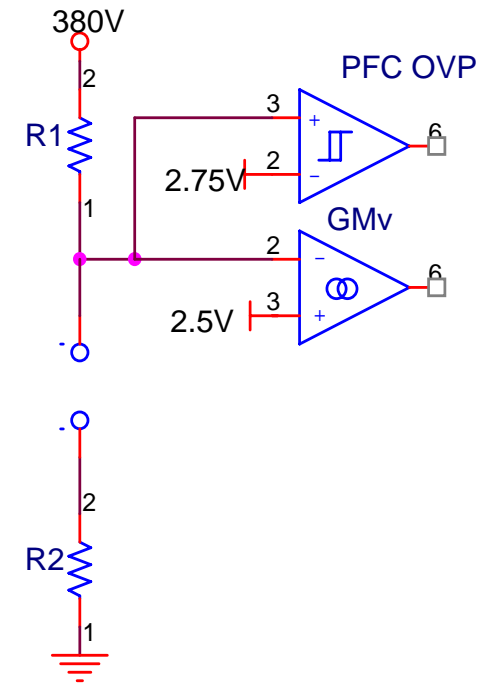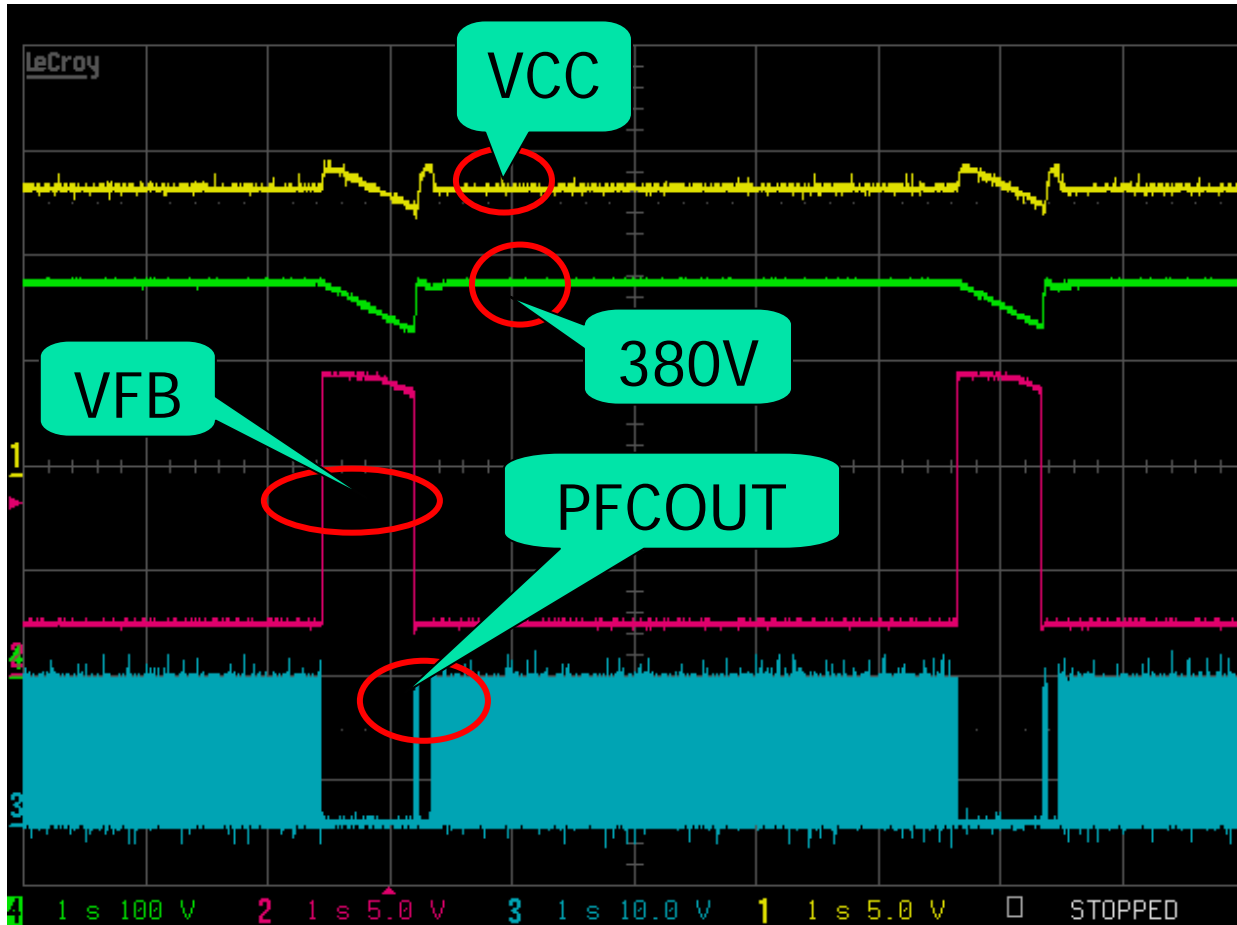

# CASE 3

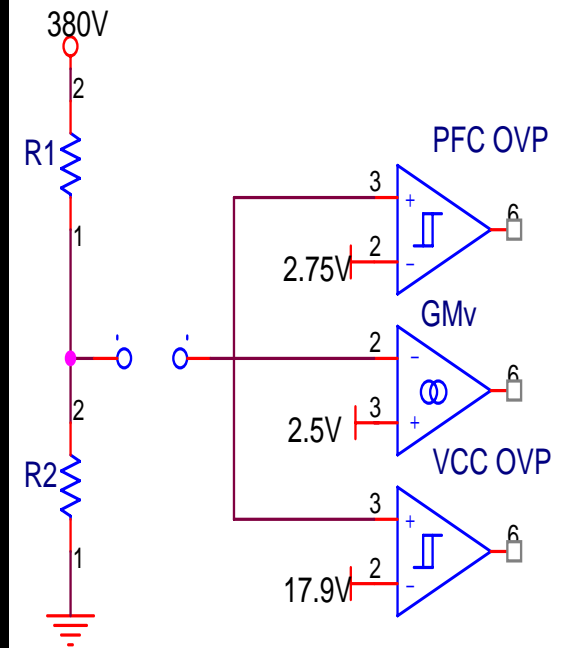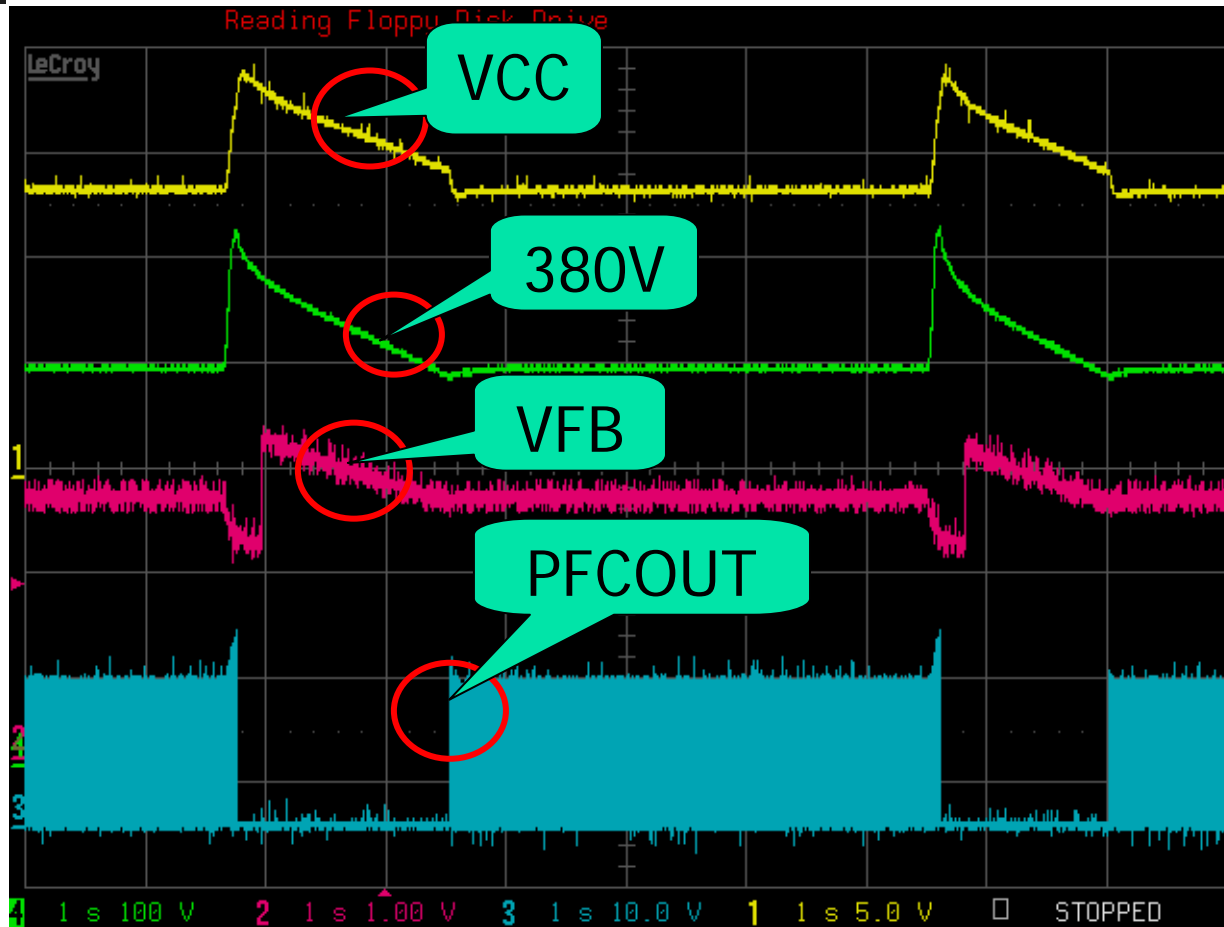



# Champion Design Center

---

- 24 hour WEBSIM:

you can design your power supply through [www.champion-micro.com](http://www.champion-micro.com).

In the Champion Design Center, you can run the full power supply system simulation without any cost.