

Appendix

Designed by kersey
 Frequency Response Analysis Tools for Push-pull Converter
 Original Rev. 12/22/05
 Revision 12/26/05

This Mathcad design tool was developed to design the compensator with the Push-pull converter.

Define the BodePlot function:

```

BodePlot(F, MinFreq, MaxFreq) := "ndk is number of points in each decade"
ndk ← 100
"n is total number of points"
n ← ndk·ceil(log( MaxFreq / MinFreq ))
r ← ln( MaxFreq / MinFreq )
for i ∈ 0..n
    ω ← MinFreq·ei·r/n
    Zi,0 ← ω / (2π)
    V ← F(j·ω)
    Zi,1 ← 20·log(|V|)
    Zi,2 ← arg(V)·180 / π
"Make -180 rollover"
for i ∈ 1..n
    Zi,2 ← Zi,2 - 360 if (|Zi,2 - Zi-1,2|) > 300
Z
    
```


Input Voltage : 22V~32V
Output Voltage : 24V
Max Output Currunt : 5A
Converter Topology : Push-pull converter
Control Mode : Peak current mode

Ro := Ro = 5 Io := $\frac{24}{Ro}$ Io = 4.8 **Change the load**


Vg := Vg = 28 **Change the input**

n := 3 k := 0.01 Ri := 10 Rc := 0.1
 μ := 10⁻⁶ Ts := 5μ Co := 100μ Lo := 60μ
 D := $\frac{24 + 1}{Vg \cdot n}$ D = 0.298

Establish small signal model:

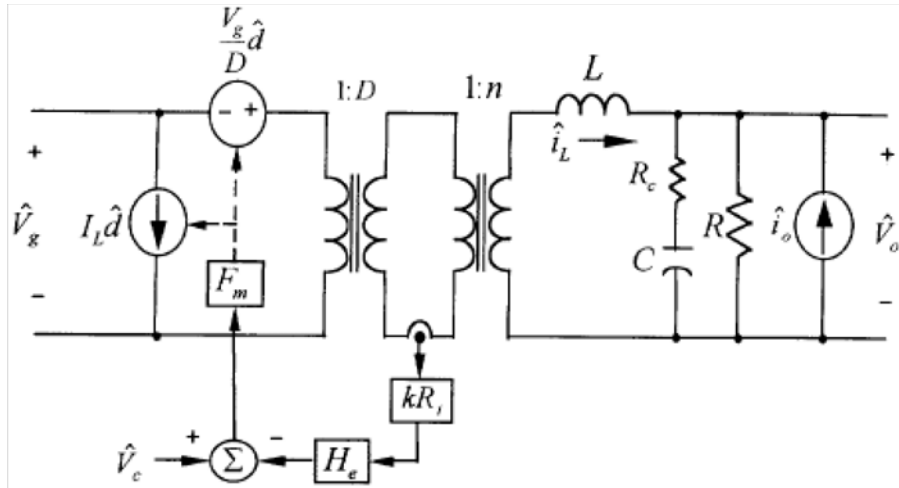

Small signal model of the converter

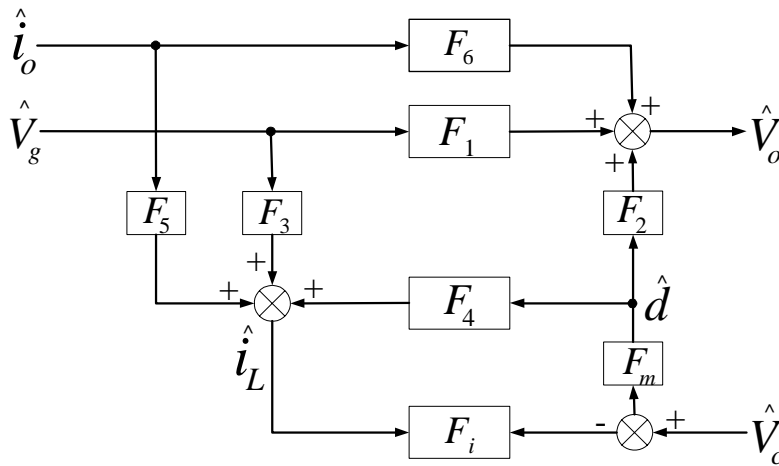

Transfer function model of the converter

S_n : the on-time slope of sensed-current

S_e : the slope of external current

$F_m(s)$: the gain function of current-mode control modulator

$H_e(s)$: transfer function used to model the sampling action of current mode control

$$S_n := \frac{n^2 \cdot k \cdot (1 - D) \cdot V_g \cdot R_i}{L_o}$$


$$S_e := 0.75 S_n \quad M_c := 1 + \frac{S_e}{S_n}$$

$$H_e(s) := 1 - \frac{s \cdot T_s}{2} + \left(\frac{T_s}{\pi}\right)^2 \cdot s^2$$

$$F_i(s) := n \cdot k \cdot R_i \cdot H_e(s)$$

$$F_m := \frac{1}{M_c \cdot S_n \cdot T_s}$$
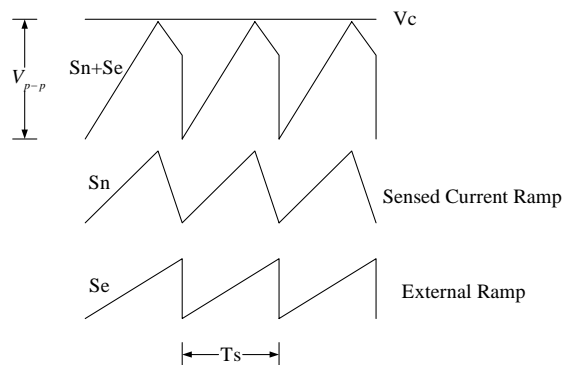
$$\Delta(s) := s^2 \cdot L_o \cdot C_o + s \cdot \left(\frac{L_o}{R_o} + C_o \cdot R_c\right) + 1$$



$$\frac{\hat{d}}{\hat{V}_c} = \frac{1}{V_{p-p}} \quad F_m = \frac{1}{(S_n + S_e) T_s} = \frac{1}{M_c S_n T_s}$$

$$F1(s) := n \cdot D \cdot \frac{1 + s \cdot Co \cdot Rc}{\Delta(s)}$$

$$F2(s) := n \cdot Vg \cdot \frac{1 + s \cdot Co \cdot Rc}{\Delta(s)}$$

$$F3(s) := n \cdot \frac{D}{Ro} \cdot \frac{1 + s \cdot Co \cdot Ro}{\Delta(s)}$$

$$F4(s) := n \cdot \frac{Vg}{Ro} \cdot \frac{1 + s \cdot Co \cdot Ro}{\Delta(s)}$$



$$F5(s) := \frac{-(1 + s \cdot Co \cdot Ro)}{\Delta(s)}$$


Current loop gain: $Ti(s) := F4(s) \cdot Fm \cdot Fi(s)$

Control to output gain: $Gco(s) := \frac{F2(s) \cdot Fm}{1 + Ti(s)}$


Control-to-output Bode Plot:

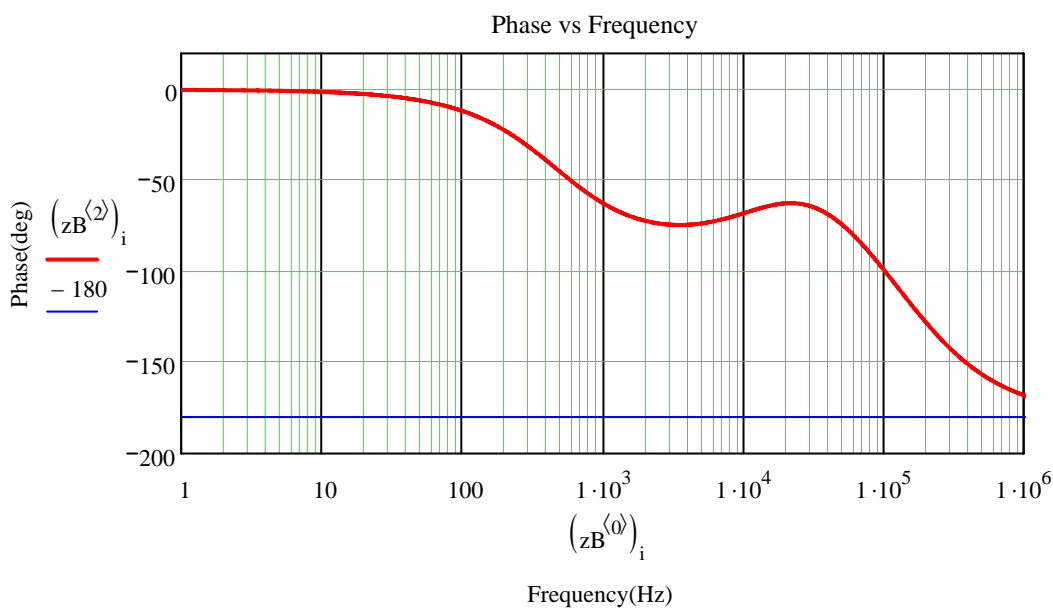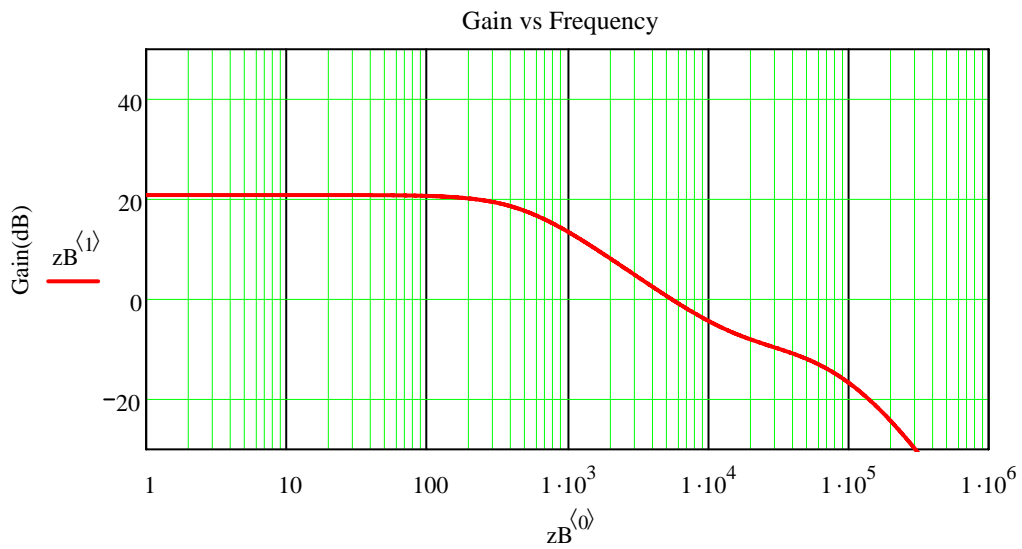$zB := \text{BodePlot}(Gco, 1, 1 \cdot 10^7)$ $i := 0 \dots \text{last}(zB^{(0)})$



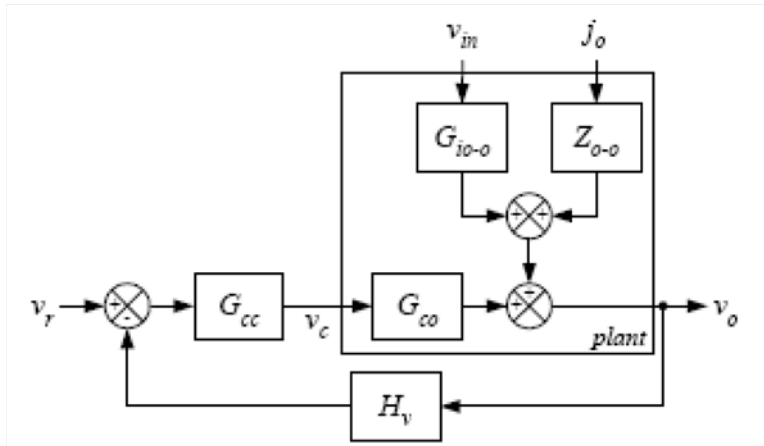

Control system block diagram of the SMPC

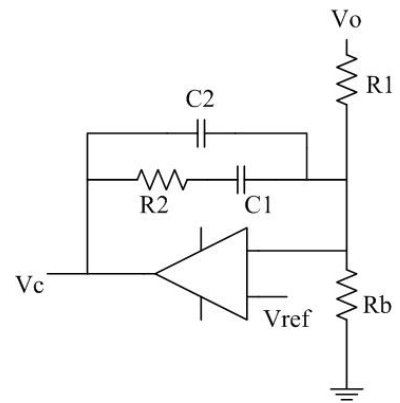

EA compensator

$$p := 10^{-12} \quad R2 := 51 \cdot 10^3 \quad C1 := 10000 \cdot p \quad C2 := 220p$$

$$R1 := \boxed{5000} \quad R1 = 5 \times 10^3$$

Calculate bias resistor : $R_b := \frac{5.1}{24 - 5.1} \cdot R1$ $R_b = 1.349 \times 10^3$

Eliminate output filter pole : $\frac{1}{2\pi \cdot R_o \cdot C_o} = 318.31$ $\frac{1}{2\pi R2 \cdot C1} = 312.069$

Eliminate ESR zero : $\frac{1}{2\pi R_c \cdot C_o} = 1.592 \times 10^4$ $\frac{C1 + C2}{2\pi R2 C1 \cdot C2} = 1.45 \times 10^4$

EA compensator transfer function :
$$G_{cc}(s) := \frac{\left(R2 + \frac{1}{s \cdot C1}\right) \cdot \frac{1}{s \cdot C2}}{\left(R2 + \frac{1}{s \cdot C1}\right) + \frac{1}{s \cdot C2}} \cdot \frac{1}{R1}$$

Feedback transfer function : $H_v := \frac{5.1}{24}$

Open-loop transfer function : $L_v(s) := G_{cc}(s) \cdot G_{co}(s) \cdot H_v$

Close-loop transfer function :
$$G_l(s) := \frac{G_{cc}(s) \cdot G_{co}(s)}{1 + L_v(s)}$$

Open-Loop Bode Plot:

$zB2 := \text{BodePlot}(G_{cc}, 1, 1 \cdot 10^7)$ $i := 0 \dots \text{last}(zB^{(0)})$

$zB3 := \text{BodePlot}(L_v, 1, 1 \cdot 10^7)$ $i := 0 \dots \text{last}(zB^{(0)})$

zB: Control to Output

zB2: EA Compensation

zB3: Overall Gain - Full Load

