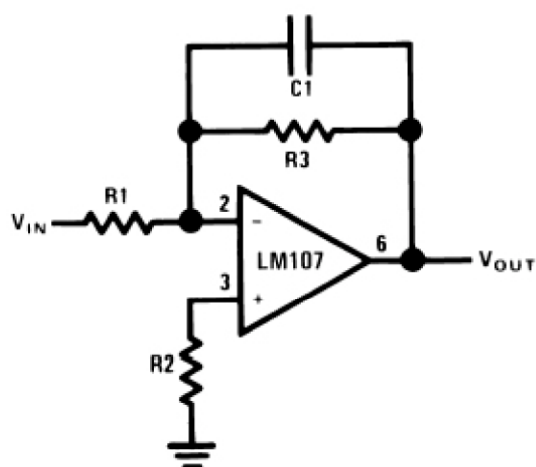


9. Simple Low-pass Filter

简单低通滤波器:

The simple low-pass filter is shown in Figure 11. This circuit has a 6 dB per octave roll-off after a closed-loop 3 dB point defined by f_c . Gain below this corner frequency is defined by the ratio of R_3 to R_1 . The circuit may be considered as an AC integrator at frequencies well above f_c ; however, the time domain response is that of a single RC rather than an integral. R_2 should be chosen equal to the parallel combination of R_1 and R_3 to minimize errors due to bias current. The amplifier should be compensated for unity-gain or an internally compensated amplifier can be used. A gain frequency plot of circuit response is shown in Figure 12 to illustrate the difference between this circuit and the true integrator.



00682211

$$f_L = \frac{1}{2\pi R_1 C_1}$$

$$f_c = \frac{1}{2\pi R_3 C_1}$$

$$A_L = \frac{R_3}{R_1}$$

FIGURE 11. Simple Low Pass Filter

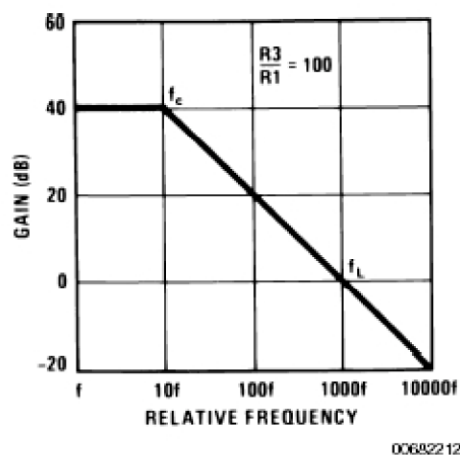


FIGURE 12. Low Pass Filter Response

简单低通滤波器的电路如图11。本电路在闭环3dB转折点为 f_c ，对高于 f_c 的信号有6dB/2倍频程的衰减。低于 f_c 频率的信号的增益由 $R3/R1$ 决定，在输入信号频率远大于 f_c 的情况下，电路可以看成是对交流信号的积分器；可以认为，在此时，从时域响应上看，比起积分来说，RC（的时间延迟特性）更明显。 $R2$ 的阻值应选为 $R1$ 和 $R3$ 的并联阻值，以减小输入偏置电流带来的误差。在这里可以选择带内部频率补偿的OP或者在外部对单位增益的频率特性进行补偿。电路的增益波特图见图12，本图说明了LPF和真正的积分器之间在频率特性上的区别。