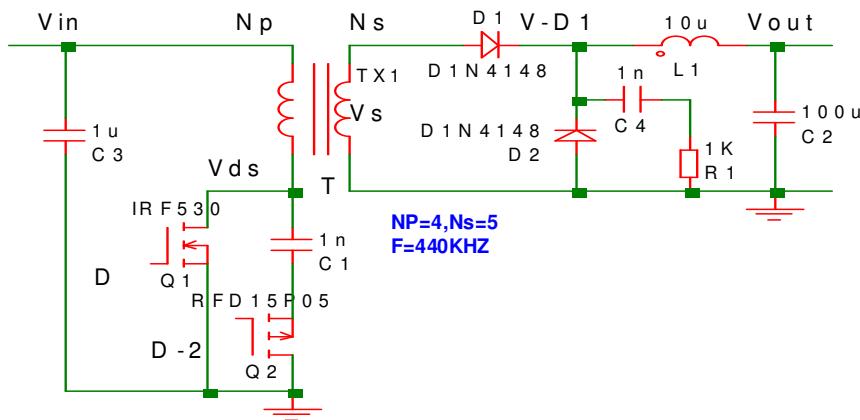


MATHCAD FOR forward(active clamp.plane core) 24V18A

liyongzhi 制作 JULY 13, 05



Purpose : This worksheet help to select the power components of forward series converter.

Usage of the worksheet : Please enter or change the value of parameters which highlighted in yellow color for the desired operating conditions.

Define the symbols

fs Switching frequency of the converter

Lp Primary inductance of power transformer

L1 inductor of inductance

D duty cycle of primary Q1,

Dpmax duty cycle of primary Q1 at Vin=Vimin

Npset Number of primary turns of power transformer

Nsset Number of secondary turns of power transformer

Vimax Input voltage of the converter

Vo Output voltage

Vs secondary voltage of power transformer winding

n Primary to secondary turn ratio of power transformer:Npset/Nsset

Poc output power limit:ocp

Po output power at full load

⊕ Reference:D:\My Documents\MATH\New Folder\Component_specification_Reference_with unit.mcd(R)

⊕ Reference:D:\My Documents\MATH\New Folder\WIRE_TABLE_UNIT_IMPROVED.MCD(R)

⊕ Reference:D:\My Documents\MATH\wire AWG calculation.mcd

contents page

1. Please enter or change the value of parameters which highlighted in yellow:

2 . n & T & Ton & Vs calculation:

3. T1 AP calculation:

4. T1 CORE select :

5. T1 Ns & Np calculation:

6.Np & Ns wire Current stress (at ViL full load):

7.T1 wire selection:

8.T1 Losses calculation:

9. inductor L1 calculation (at ocp):

10.L1(inductor- Cool mu)design:

11.component stress calculation (at Vinmax & full load):

12. FET loss calculation (for individual MOSFET-Q1):

13. output capacitor calculation :

14.converter loss list and efficiency (at full load):

15. converter review:

1. Please enter or change the value of parameters which highlighted in yellow:

Vimin := 36 Vimax := 58 fs := 400000 Vdio := 0.8 Vwinding := 0.2

Poc := 500 Vo := 24 Dpmax := 0.55 η := 0.92 Vorngfet := 0.1

$$T_{\text{avg}} := \frac{1}{fs} \quad T = 2.5 \times 10^{-6}$$

$$Dpmin := \frac{Vimin}{Vimax} \cdot Dpmax \quad Dpmin = 0.341$$

Dpmin: duty cycle of primary Q1
Q1,Q2,Q3,Q3 at Vimax 0.57

2 . n & T & Ton & Vs calculation:

$$Vs := Vo + Vdio + Vwinding \quad Vs = 25$$

secondary winding voltage:

$$\frac{Np}{Ns} = Vin \cdot Ton / Vs \cdot T = Vin \cdot Dp / Vs$$

so:

$$ncal := Vimax \cdot \frac{Dpmin}{Vs} \quad ncal = 0.792$$

n := 0.8

change Dpmin value make n is sharp such:n=3,n=3.5, OR n=3.2

$$THon := Dpmin \cdot T \quad THon = 8.534 \times 10^{-7}$$

primary Q1 turn on time:s

$$THoff := T - Dpmin \cdot T \quad THoff = 1.647 \times 10^{-6}$$

primary Q1 turn off time:s

$$Vx := 48$$

$$Dx := Dpmax \cdot \frac{Vimin}{Vx} \quad Dx = 0.413 \quad \text{Vin=Vx 时的占空比}$$

$$Vout_max := Vimax \cdot \frac{2 \times 0.44}{n} \quad Vout_max = 63.8 \quad \text{失控时最大输出电压 :V}$$

$$Ioc := \frac{Poc}{Vo} \quad Ioc = 20.833 \quad \text{current limit: A}$$

$$Po := \frac{Poc}{1.2} \quad Po = 416.667 \quad \text{output power: Watts}$$

$$Io := \frac{Po}{Vo} \quad Io = 17.361 \quad \text{FULL Load :A}$$

$$\eta = 0.92 \quad \text{DC DC converter efficiency: } \eta$$

3. T1 T2 AP calculation:

pcurrent := 1000 transformer winding current density : A/cm³
wind cooling: 600A TO 1000A/cm³
no wind : 300A TO 450A/cm³

K := 0.8

K winding utilization
DCDC: K=0.8
isolation (acdc): K=0.45

ΔB := 0.21

ΔB Flux density swing: Tesla

$$AP := \frac{0.5 \cdot Po}{(\eta Dpmax \cdot \Delta B \cdot fs \cdot pcurrent \cdot K) \cdot 10^{-4}} \quad AP = 0.061 \quad \text{transformer Aw * Ae: cm}^4$$

$$AP2 := \left(\frac{0.5 \cdot Po}{0.014 \cdot \Delta B \cdot fs} \right)^{\frac{4}{3}} \quad AP2 = 0.099 \quad \text{transformer Aw * Ae: cm}^4$$

4. T1 T2 CORE select :

select CORE : PQ20

enter the transformer core parameter :

Ae := 0.59


effective area Ae: cm²

$$\textcolor{green}{AP2} := \left(\frac{Po}{0.014 \cdot \Delta B \cdot fs} \right)^{\frac{4}{3}}$$

AP2 = 0.251

$V_e := 1.46 \cdot 2$	$V_e = 2.92$	effective Volume $V_e: \text{cm}^3$
$L_e := 4.7 \cdot 2$	$L_e = 9.4$	effective Length $L_e: \text{cm}^3$
$m_g := 3.5 \cdot 2$	$m_g = 7$	total weight $m: \text{g}$
$AL := 2200$		$3F3 AL: \text{nH}$
$P_v := 150$		see right fig ΔB_{fig} and fs: mW/cm^3
$Aw := 0.12$		winding area : cm^2

NUMBER OF SECTIONS	WINDING AREA (mm ²)	MINIMUM WINDING WIDTH (mm)	AVERAGE LENGTH OF TURN (mm)
1	27.7	13.5	34.1

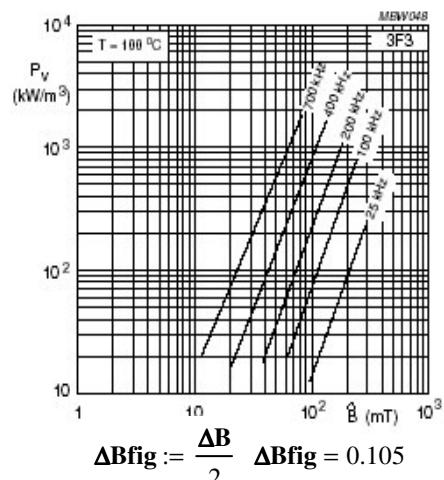

CORES

Effective core parameters

SYMBOL	PARAMETER	VALUE	UNIT
$\Sigma(I/A)$	core factor (C1)	1.52	mm^{-1}
V_e	effective volume	1460	mm^3
l_e	effective length	47.0	mm
A_e	effective area	31.0	mm^2
A_{\min}	minimum area	29	mm^2
m	mass of core half	≈ 3.5	g

note: the V_e is mase of core half

$$AP_{\text{ture}} := A_e \cdot Aw \quad AP_{\text{ture}} = 0.071 \quad AP = 0.061$$

$$AP_{\text{ture}} \geq AP$$

5. T1 Ns & Np calculation:

$$Ns := V_s \cdot \frac{T \cdot 10^4}{A_e \cdot \Delta B} \quad Ns = 5.044$$

$$Ns_{\text{set}} := 5$$

change ΔB value make Ns is sharp such: $Ns=3$, $Ns=4$

$$Np := n \cdot Ns_{\text{set}} \quad Np = 4$$

$$Np_{\text{set}} := 4$$

$$\Delta B_{\text{set}} := \Delta B \cdot \frac{Ns}{Ns_{\text{set}}} \quad \Delta B_{\text{set}} = 0.212$$

$$B_{\max} := \frac{\Delta B_{\text{set}} \cdot 0.75}{D_{\min}} \quad B_{\max} = 0.465$$

验算: $B_{\max} < 0.35$
 $0.7 = D_{\max}$

$$L_{\text{t1}} := \frac{Np^2 \cdot AL \cdot 10^{-9}}{10^{-6}}$$

$$L_{\text{t1}} = 35.2$$

transformer T1 inductance : uH

enter the transformer **bobbin** parameter :

$$Aw = 0.12$$

winding area : cm^2

$$Bw := 1.36$$

winding width : cm , 0.8cm

$$Hw := 0.4775$$

winding hidth : cm

$$MLT := 5.64$$

average Length : cm

6.Np & Ns wire Current stress (at ViL full load):

$$KL := 0.15$$

$$Io = 17.361$$

$$ILpp := 2KL \cdot Io$$

$$ILpp = 5.208$$

inductor L1 PEAK current:A

$$Ispk := Io + \frac{ILpp}{2}$$

$$Ispk = 19.965$$

Ns Peak current : A

$$Ispk_a := Ispk - \frac{ILpp}{2}$$

$$Ispk_a = 17.361$$

$$Isdc := Ispk_a \cdot Dpmin$$

$$Isdc = 5.927$$

Ns DC current : A

$$Isac := Ispk_a \cdot \sqrt{Dpmin \cdot (1 - Dpmin)}$$

$$Isac = 8.232$$

Ns AC current : A

$$Isrms := Ispk_a \cdot \sqrt{Dpmin}$$

$$Isrms = 10.144$$

Ns RMS current : A

$$Ipdc := \frac{Isdc}{n}$$

$$Ipdc = 7.408$$

Np DC current : A

$$Ipac := \frac{Isac}{n}$$

$$Ipac = 10.29$$

Np AC current : A

$$Ippk := \frac{Ispk}{n}$$

$$Ippk = 24.957$$

Np Peak current : A

$$Iprms := \frac{Isrms}{n}$$

$$Iprms = 12.68$$

Np RMS current : A

7.T1 wire selection:

8.T1 Losses calculation:

$$Rsdc := 0.007$$

$$Rsac := 2 \cdot Rsdc$$

$$Rpdc := 0.007$$

$$Rpac := 2 \cdot Rsdc$$

$$Pt1core := \frac{Pv \cdot Ve}{1000}$$

$$Pt1core = 0.438$$

core loss:W

$$Psloss := Rsdc \cdot Isdc^2 + Rsac \cdot Isac^2$$

$$Psloss = 1.195$$

次级 winding loss: Watts

$$Pploss := Rpdc \cdot Ipdc^2 + Rpac \cdot Ipac^2$$

$$Pploss = 1.867$$

初级 winding loss: Watts

$$Pt1total := Psloss + Pploss + Pt1core$$

$$Pt1total = 3.499$$

T1 total loss: Watts

transformer temperature rise calculation(fan speed=0)

$$RT := \frac{36}{Aw} \quad RT = 300$$

thermal resistance : °C/Watts

$$Crise := \frac{Pt1total \cdot RT}{2} \quad Crise = 524.89 \quad \text{one transformer temperaturre rise: } ^\circ\text{C}$$


9. inductor L1 calculation (at ocp): (refer to [inductor design](#), here is simple)

KL = 0.15 $KL = \Delta I/I_{oc}$ $KL: 0.1 \text{ to } 0.15$

RL1 := 0.002 inductor L1 resistor: Ω

ILpp := KL · Ioc inductor L1 Peak current:A

ILpp = 3.125

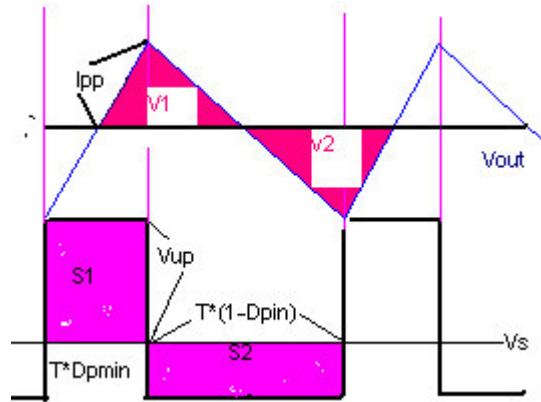

$$V_{up} \cdot T^* D_{pmin} = V_s \cdot T^*(1 - D_{pmin})$$

SO:

$$V_{up} := \frac{V_s \cdot (1 - D_{pmin})}{D_{pmin}} \quad V_{up} = 48.232$$

$$L1_H := \frac{V_{up} \cdot D_{pmin} \cdot T}{2 \cdot ILpp} \quad L1_H = 6.586 \times 10^{-6} \quad \text{inductor L1 :H}$$

$92\%: \text{core AL tolerance}$

$$L1 := L1_H \cdot 10^6$$

$$L1_SET := 92\% \cdot L1$$

$$L1_SET = 6.059 \quad \text{inductor L1 :uH}$$

Ae_L1 := 0.58

Bs := 0.3

$Bs < 0.35$

$$NL := V_{up} \cdot \frac{D_{pmin} \cdot T}{Ae_L1 \cdot 10^{-4} \cdot \frac{2 \cdot ILpp}{I_{oc}} \cdot Bs} \quad NL = 7.886 \quad \text{inductor L1 winding :turn}$$

$N = \Delta V \cdot \Delta T / (Ae \cdot \Delta B)$

OR:

$$NL1 := \frac{L1_H \cdot 2 \cdot ILpp}{\frac{2 \cdot ILpp}{I_{oc}} \cdot Bs \cdot Ae_L1 \cdot 10^{-4}} \quad NL1 = 7.886 \quad NL1_set := 8 \quad \text{inductor L1 winding :turn}$$

$$\text{gap} := 4 \cdot \pi \cdot 10^{-7} \cdot NL1_set^2 \cdot \frac{Ae_L1}{L1_H} \cdot 10^{-2} \cdot 1.35 \quad \text{gap} = 0.096 \quad \text{gap近似值 :cm}$$

RNL1set := 0.007

L1 :Ω

Pcu_L1 := Io² · RNL1set

Pcu_L1 = 2.11

L1 wire loss :W

$$AeL1 := 0.331 \cdot 10^{-4}$$

$$Vcore := 1.88$$

$$Vcore : \text{cm}^3$$

$$Pv_core := 800$$

$$Pv_core : \text{mw/cm}^3$$

$$Pcore_L1 := \frac{Pv_core \cdot Vcore}{10^3} \quad Pcore_L1 = 1.504$$

$$Pcore_L1 : \text{W}$$

$$Ptotal_L1 := Pcore_L1 + Pcu_L1 \quad Ptotal_L1 = 3.614$$

$$Ptotal_L1 : \text{W}$$

11.component stress calculation (at Vinmax & full load):

Q1-Vds Dio D1 D2 voltage stress:V:

$$VQ1 := Vimax + Vimax \cdot \frac{Dpmin}{1 - Dpmin} \quad VQ1 = 88.063 \quad \text{Q1-Vds voltage stress: V. at active clamp.}$$

$$Vd2 := Vs + Vup \quad Vd2 = 73.232$$

$$Vd2set := \frac{Vd2}{0.6} \quad Vd2set = 122.054 \quad \text{Dio D2 voltage stress:V.}$$

$$Vd1 := \frac{VQ1 - Vimax}{n} \quad Vd1 = 37.579$$

$$Vd1set := \frac{Vd1}{0.6} \quad Vd1set = 62.631 \quad \text{Dio D1 voltage stress:V.}$$

Dio D2 current stress:Ap-p:

$$Id2_pp := \left(Io + \frac{ILpp}{2} \right) \quad Id2_pp = 18.924 \quad \text{Dio D2 current stress:Ap-p.}$$

$$Id2_a := Id2_pp - \frac{ILpp}{2} \quad Id2_a = 17.361$$

$$D_d2 := 1 - Dpmin$$

$$Id2_ac := Id2_a \cdot \sqrt{D_d2 \cdot (1 - D_d2)} \quad Id2_ac = 8.232$$

$$Id2_dc := D_d2 \cdot Id2_a \quad Id2_dc = 11.434$$

$$Id2_rms := Id2_a \cdot \sqrt{D_d2} \quad Id2_rms = 14.089 \quad \text{Dio D2 current stress:A-rms.}$$

Dio D1 current stress:Ap-p.

$$Id1_pp := \left(Io + \frac{ILpp}{2} \right) \quad Id1_pp = 18.924 \quad \text{Dio D1 current stress:Ap-p.}$$


$$Id1_a := Id1_pp - \frac{ILpp}{2} \quad Id1_a = 17.361$$

$$Id1_ac := Id1_a \cdot \sqrt{Dpmin \cdot (1 - Dpmin)} \quad Id1_ac = 8.232$$

$$Id1_dc := Dpmin \cdot Id1_a \quad Id1_dc = 5.927$$

$$Id1_{rms} := Id1_a \cdot \sqrt{Dpmin}$$
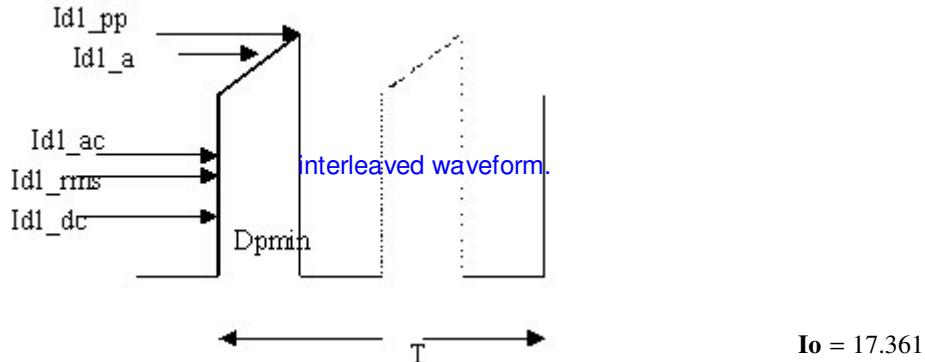
$$Id1_{rms} = 10.144 \quad \text{Dio D1 current stress:A-rms.}$$



$$Pd7loss := Vdio \cdot Io \cdot (1 - Dpmin)$$

$$Pd7loss = 9.148 \quad \text{Dio D7 loss:Watts.}$$

$$Pd1loss := Vdio \cdot Io \cdot Dpmin$$

$$Pd1loss = 4.741 \quad \text{Dio D1 loss:Watts.}$$

$$Pslobber := 0.5$$

Dio D1D7 snubber total loss:Watts

$$Precover := 0.5$$

Dio D1 D7 recover loss:Watts.

$$Roringfet := 0.0025$$

$$Poringloss := Roringfet \cdot Io^2$$

$$Poringloss = 0.754$$

$$Pd1d7loss := Pd1loss + Pd7loss + Precover + Pslobber \quad Pd1d7loss = 14.889$$

$$Pdiototalloss := Pd1d7loss + Poringloss \quad Pdiototalloss = 15.642 \quad \text{all Dio total loss:Watts.}$$

$$Iq1 := \frac{Id1_{pp}}{n} \quad Iq1 = 23.655 \quad \text{Q1-Vds current stress: Ap-p}$$

$$Iq1rms := \frac{Id1_{rms}}{n} \quad Iq1rms = 12.68 \quad \text{Q1-Vds current stress: ARMS}$$

12. FET loss calculation (for individual MOSFET-Q1):

Drain-Source On-State Resistance ^a	$r_{DS(on)}$	$V_{GS} = 10 \text{ V}, I_D = 5 \text{ A}$	0.041	0.050	Ω
---	--------------	--	-------	-------	----------

$$Rds25 := 0.06$$

Q1导通电阻at 25°C: Ω

$$Rds100 := (Rds25 \cdot 75 \cdot 0.035) + Rds25$$

$$Rds100 = 0.218$$

Q1导通电阻at 100°C: Ω

$$Vdr := 12$$

Drive Voltage:V

$$Vgsth := 3$$

turn Off Voltage:V

$$Rdron := 1$$

Drive 电阻: Ω

$$Qgs := 7.6 \cdot 10^{-9}$$

fet Qgs charge:C

$$Qgd := 14 \cdot 10^{-9}$$

fet Qgd (miller)charge:C

$$Coss := 300 \cdot 10^{-12}$$

all fet output capacitance:F

FETn := 4 fet 并联个数

VQ1 = 88.063 Q1-Vds voltage stress: V.
at active clamp.

Iq1 := $\frac{I_{spk}}{n}$ **Iq1 = 24.957** Q1-Vds current stress: Ap-p

Iq1_rms := $\frac{I_{srms}}{n}$ **Iq1_rms = 12.68** Q1-Vds current stress: ARMS

Pcond := $\left[R_{ds100} \cdot \left(\frac{Iq1_rms}{FETn} \right)^2 \cdot D_{pmax} \right] \cdot FETn$ **Pcond = 4.808** conduction loss:W

tsw := $Q_{gd} \cdot \frac{R_{dron}}{V_{dr} - V_{gsth}}$ **tsw = 1.556×10^{-9}** turn on time:sec

Psw := $\left[\left(tsw \cdot VQ1 \cdot \frac{Iq1}{FETn} \cdot fs \right) + \frac{C_{oss} \cdot VQ1^2 \cdot fs}{2} \right] \cdot FETn$ **$\frac{C_{oss} \cdot VQ1^2 \cdot fs}{2} = 0.465$**

Psw = 3.229 switching Loss:W

Igare := fs · Qgd **Igare = 5.6×10^{-3}** average drive current:A


Pgate := Igare · Vdr **Pgate = 0.067** average drive Loss:W

Pfet := (Pcond + Psw + Pgate) **Pfet = 8.104** one Fet total Loss:W

Pfetall := Pfet **Pfetall = 8.104** all Fet total Loss:W

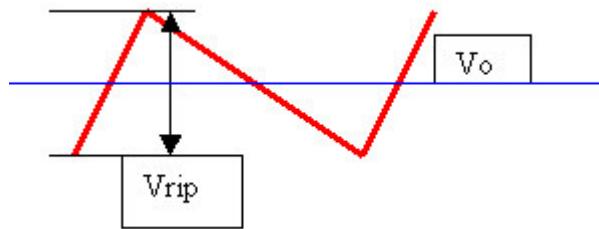13. output capacitor calculation :

Vrip := 0.005 · Vo **Vrip = 0.12** Output ripple voltage:Vp-p



电容放电能量=电感充电能量:
So : for forward: **C = $2I_{pp} \cdot T / (8 \cdot V_{ripple})$**

C2 := $1.25 \frac{2I_{pp} \cdot T}{8V_{rip}} \cdot 10^6$ **C2 = 20.345** Output Capacitance:uF
1.25 考虑电容利用率

ESRc1 := $\frac{V_{rip}}{2I_{pp}}$ **ESRc1 = 0.019** Omaximum ESR value:Ω

$$ILpprms := ILpp \cdot \sqrt{\frac{1}{3}} \quad ILpprms = 1.804 \quad \text{ripplecurrent(rms):A}$$

$$Pout_cap_loss := ILpprms^2 \cdot ESRc1 \quad Pout_cap_loss = 0.063 \quad \text{Output Capacitor loss:w}$$

实际上要用较大电容: 满足ESR要求:

14.converter loss list and efficiency (at full load):

Pfetall = 8.104	4FET total loss: Watts
Pdiototalloss = 15.642	ALL Dio total loss:Watts.
Pt1total = 3.499	T1T2 total loss: Watts
Ptotal_L1 = 3.614	L1 total loss: Watts
Pout_cap_loss = 0.063	Output Capacitance loss:w
Pclame := 2	Dio2,3,5,6 clame loss: Watts
Pcontrol := 2	control circuit total loss: Watts

$$Pot := Pclame + Pcontrol$$

$$Ptotalloss := Pfetall + Pdiototalloss + Pt1total + Ptotal_L1 + Pout_cap_loss + Pot$$

$$Ptotalloss = 34.922 \quad \text{converter total loss: Watts}$$

$$\eta := \frac{Vo \cdot Io}{Vo \cdot Io + Ptotalloss} \quad \eta = 0.923 \quad \text{converter total efficiency: } \eta$$

15. converter review:

$$VQ1 = 88.063 \quad Iq1_rms = 12.68 \quad Ippk = 24.957 \quad Pfetall = 8.104$$

$$Iprms = 12.68 \quad Ispk = 19.965 \quad Isrms = 10.144$$

$$ESRc1 = 0.019 \quad \text{for ripple:uf}$$

$$Rdron = 1$$

$$fs = 4 \times 10^5 \quad T = 2.5 \times 10^{-6} \quad Dpmax = 0.55$$

$$Lt1 = 35.2 \quad Nsset = 5 \quad Npset = 4$$

$$L1 = 6.586 \quad L1_SET = 6.059 \quad NL1_set = 8$$

$$Vd2set = 122.054 \quad \text{Dio D7 voltage stress:V.} \quad Id2_rms = 14.089$$

$$Vd1set = 62.631 \quad \text{Dio D7 voltage stress:V.} \quad Id1_rms = 10.144$$

