

PC power 线路分析及计算技巧

实例1: 1. $P_{out} = 300W$ $P_{in} = 90V - 264V$ $\eta = 65\%$, NO PFC
 $F = 70K$ $PF = 0.65$
2. output: $+12V/16A$ $+5V/30A$ $+3.3V/20A$ $-12V/0.5A$
 $-5V/0.5A$

3. 已知变压器 $N_p = 48T$.

$$N_S(+12V) = 9T$$

$$N_S(+5V) = 4T$$

$$N_S(+3.3V) = 3T$$

$$N_S(-12V) = 11T$$

4. 线路拓扑结构采用 Forward 线路形式.

下面是对各部分线路的分析和计算:

~ 输入功率：

1. FUSE:

$$\because U_2 \cos \theta \eta = P_{out}$$

$$I_{in} = \frac{P_{out}}{U \cos \theta \eta}$$

$$\eta = PF = 0.65$$

$$\eta = \cos \theta = 0.65 \quad \text{let: } I_{in} = \frac{300W}{90V \times 0.65 \times 0.65} = 7.8A$$

2. 安规限值电阻计算：

$$\text{放电公式: } V_t = V_0 e^{-\frac{t}{T}}$$

安规要求在1分钟内 $V_t = 37\% V_0$

$$GM\text{选}1\mu F \quad C_{X1} = 1\mu F$$

$$\therefore RC = T$$

$$t = 1 \text{ 分钟}$$

$$\therefore V_t = V_0 e^{-\frac{t}{RC}},$$
$$= V_0 e^{-\frac{1}{R \cdot C_{X1}}}$$


$$37\% V_0 = V_0 e^{-\frac{1}{R_1 \times 1\mu F}}$$

$$\ln 0.37 = -\frac{1}{R_1 \times 1\mu F}$$

$$-1 = \frac{-1}{R_1 \times 1\mu F}$$

$$R_1 = 1M\Omega$$

$\therefore R_1$ 选用 $1/2W, 1M\Omega$

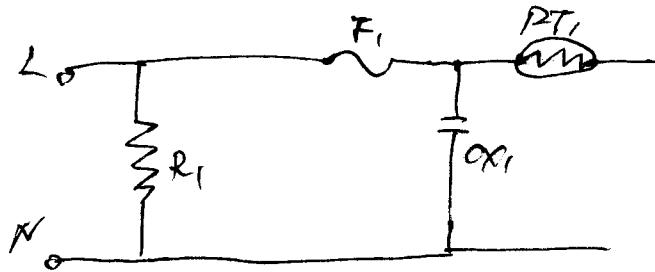

3. Thermistor:

若 Spec 要求限流 $< 60A$

$$\therefore R_{therm} = \frac{V_{in}}{60A} = \frac{264V}{60A} = 4.4\Omega$$

$\mu F Cap:$


$$C = \frac{It}{\Delta V}$$

C : 电容器 μF

I : 直流负载电流

t : 电容器能提供的电流时间 ms

ΔV : 允许的峰对峰纹波值 V

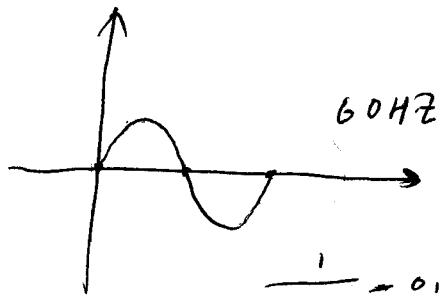

$$\frac{1}{60} = 0.0167 \text{ s}$$

半周期 = 8ms

若 $P_{out} = 300W$ $\eta = 65\%$. $\Delta V = 30V$. $t = 8ms$.

$$P_{in} = \frac{300}{65\%} = 460W$$

$$I = \frac{P_{in}}{E} = \frac{460}{2(90V \times \sqrt{2})} = 1.80A$$

$$\therefore C = \frac{1.80A \times 8ms}{30V} = 480\mu F$$

$\therefore C_6, C_7$ 为 $960\mu F$. 可选: $1000\mu F$, 或可选 $820\mu F$.

输入整流器: (input Rectifiers)


① 最大双向整流容许值: 2倍计算之最大电流值

② 峰值逆向电压阻隔值: 600V - 800V

③ 安流电流容许值

6.


倍压整流电路:

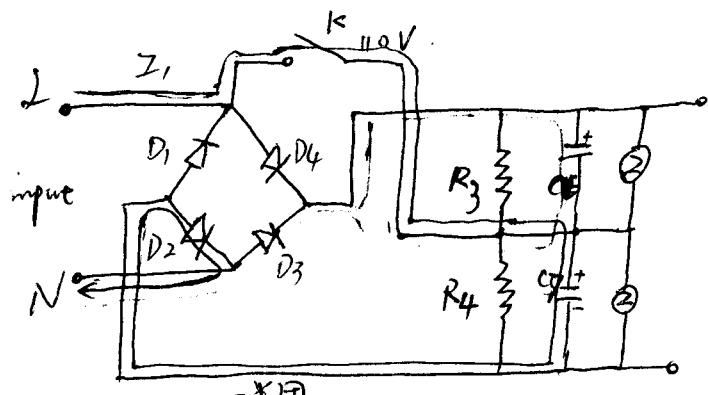

K off时 I₁ 经 K, C₇, D₂, 到 N.

K on时

K off时, I₂ 负半周经 D₃, C₆, K 到 L.

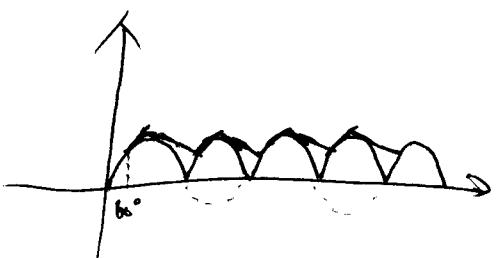


POWER MOSFET CHOOSE

①. CONSIDER DRAIN - SOURCE BREAKDOWN VOLTAGE BV_{DSS}

$$BV_{DSS} > V_{de(max)} \left(1 + \frac{N_p}{N_p'}\right)$$

$$BV_{DSS} > 2V_{dc(max)}$$

$$V_{DS} > 2V_{dc(max)}$$

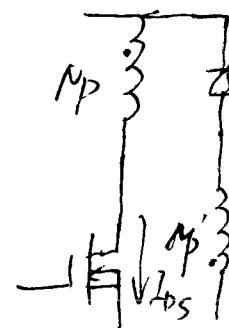

②. $I_{DS} > \frac{D_{max} I_{o(max)}}{N}$

③. $I_{om} (I_{ospeak}) > \frac{I_{o(max)} + I_{o(min)}}{N} + \frac{V_{de(min)} D_{max} \cdot T_s}{L_p}$

④. $R_{DS(on)}$

$V_{XP35131}: \frac{V_{DS}}{(1 + \frac{N_p}{N_p'})} \times V_{dc(max)}$

$$= 2V_{dc(max)}$$

$$= 2 \times 370 \text{ V} = 640 \text{ V}$$

Power off 3W + 12V output.
 $\therefore I_{omax} = \frac{300 \text{ W}}{12 \text{ V}} = 25 \text{ A}$

$$I_{DS} > \frac{D_{max} \cdot I_{omax}}{N} = \frac{\frac{0.45}{48} \times 25 \text{ A}}{\frac{9}{9}} = 2.12 \text{ A}$$

$$I_{om} > \frac{I_{c(max)} + I_{o(min)}}{N} + \frac{V_{de(min)} D_{max} \cdot T_s}{L_p}$$

$$= \frac{25 + 0.5}{5.3} + \frac{130 \times 0.45 \times \left(\frac{1}{70 \times 10^3}\right)}{5 \text{ mH}} \rightarrow +12 \text{ V 经阻为 } 5 \text{ mH}$$


$$= 4.96 \text{ A}$$

$\therefore \text{CHOOSE: } 500 \text{ V, } 15 \text{ A FUJI 2SK1016 * 2 } R_{DS(on)} = 5.5 \Omega$

put circuit:

1. out put diode:

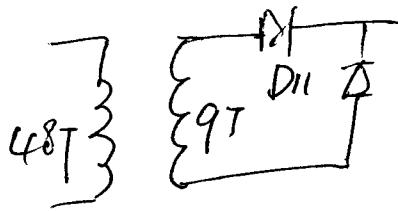A. FORWARD DIODE
①. $V_{RRM} > \frac{Ns}{Np} \times V_{de}$



②. $I_o(\text{avg}) = I_o(\text{max}) D_{\text{max}}$

③. $I_{FSM} > I_o(\text{max}) + I_o(\text{min})$

B. FREE WHEELING DIODE.

④. $V_{RRM} > \frac{Ns}{Np} \times V_{dc(\text{max})}$

⑤. $I_o(\text{avg}) > (1 - D_{\text{min}}) I_o(\text{max})$

⑥. $I_{FSM} > I_o(\text{max}) + I_o(\text{min})$

W_{PC35-040} = $D_{\text{max}} = 0.45, D_{\text{min}} = 0.2$ $Np = 48T$
+12V/16A $V_{dc(\text{max})} = 264 \times \sqrt{2} \approx 370V$ $Ns(+12V) = 9T$

$\therefore D. V_{RRM} > \frac{Ns(+12V)}{Np} \times V_{de(\text{max})}$

$$\geq \frac{9}{48} \times 370V$$

$$\Rightarrow 70.8V$$

⑦. $I_o(\text{avg}) > I_o(+12V) D_{\text{max}}$

$$\geq 16A \times 0.45$$

$$\geq 7.2A$$

$$\textcircled{3} \quad I_{\text{FSM}} > I_o(\text{max}) + I_o(\text{min})$$

$$\geq 16A + 0.5A$$

$$\geq 16.5A$$

B: FREE - WHEELING D20DE (+12v)

$$V_{RRM} > \frac{N_s}{N_p} \times V_{dc}$$

$$= \frac{9}{48} \times 370V$$

$$= 70V$$

$$I_o(\text{avg}) > (1 - D_{\text{min}}) I_o(+12v)$$

$$= (1 - 0.12) \times 16A$$

$$= 12.8A$$

$$I_{\text{FSM}} > I_o(\text{max}) + I_o(\text{min})$$

$$= 16 + 0.5A$$

$$= 16.5A$$

$$\text{从图上看出} \quad V_{RRM} = 200V \quad I_o(\text{avg}) = 30A$$

$$I_{\text{FSM}} = 50A$$

CAPACITOR :

$$1. C_0 \geq \frac{T_s^2 \times V_o}{8L_0 \times \Delta V_o(\text{max})}$$


2. CHOOSE CAPACITOR RATED VOLTAGE
W.V. > V_o

$$3. I_{\text{ripple (rms)}} > \frac{\Delta I_L}{2\sqrt{3}} = \frac{2I_o(\text{min})}{2\sqrt{3}} = \frac{I_o(\text{min})}{\sqrt{3}}$$

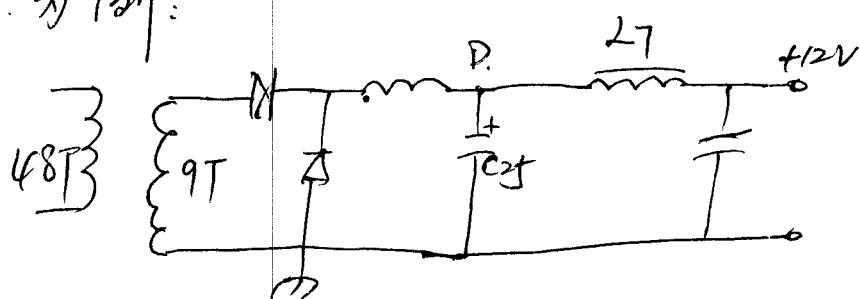4. ESR

$$\text{ESR}(\text{max}) < \frac{\Delta V_o(\text{max})}{\Delta I_L} = \frac{\Delta V_o(\text{max})}{2I_o(\text{min})}$$

W/ PC35-040 - +12V output. $\Rightarrow T_{3n}$:



$$D. C_0 \geq \frac{T_s^2 \times V_o}{8L_0 \times \Delta V_o}$$

$$\therefore C_{25} \geq \frac{\left(\frac{1}{70 \times 10^3}\right)^2 \times 12V}{8 \times 1.3 \times 10^{-6} \times 120 \times 10^{-3}} \times (1 - 0.2)$$

$$= \frac{1.96 \times 10^{-10} \times 12 \times 0.8}{8 \times 1.3 \times 10^{-6} \times 0.12} \times \cancel{10}$$

$$= 15.1 \times 10^{-4} F$$

$$= 1510 \mu F$$

$$\textcircled{3} \quad I_{\text{Ripple, rms}} \rightarrow \frac{\Delta I_L}{2N_3} = \frac{I_0(\text{max})}{N_3} = \frac{0.5A}{N_3} = \cancel{0.13A} \quad ?$$

$$\begin{aligned} i_{\text{ripple}} &= I_0 \times \cancel{N_3} \\ &= \cancel{16A} \times \cancel{10^3} \\ &= \cancel{160A} \end{aligned}$$

$$\textcircled{4} \quad ESR : \bar{ESR}(\text{max}) < \frac{\Delta V_0(\text{max})}{\Delta I_L} = \frac{\Delta V_0(\text{max})}{2I_0(\text{min})} \quad ?$$

$$= \frac{120mV}{2 \times 0.5A} = 120m\Omega$$

\therefore PC35 適用: $2200\mu F$ $16V$. or $25V$.


$2200\mu F$ 16V: Ripple current: $1.45A$

impedance: $0.15-$
(ESR)


$2200\mu F$ 25V: Ripple Current: $2.47A$

impedance: $0.027-$
(ESR)

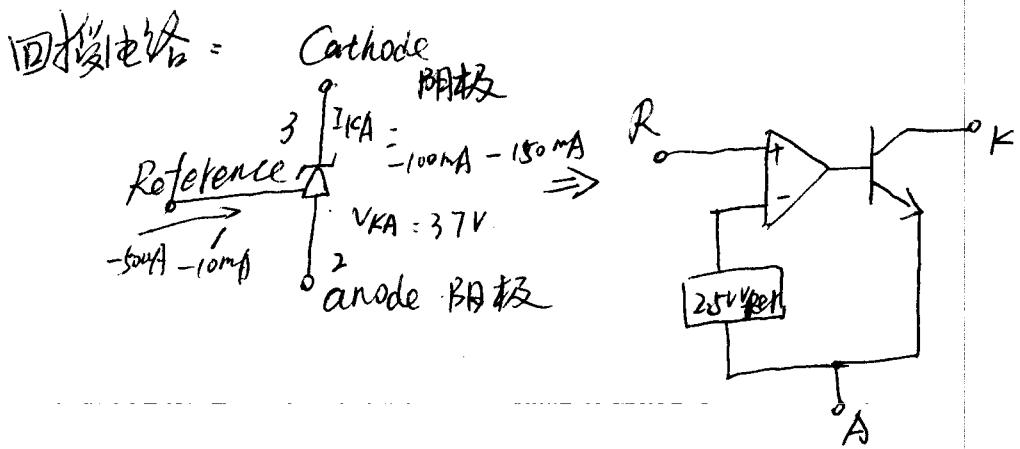\therefore 総合上面計算適用 25V. $2200\mu F$. ELE Cap.



实例二：

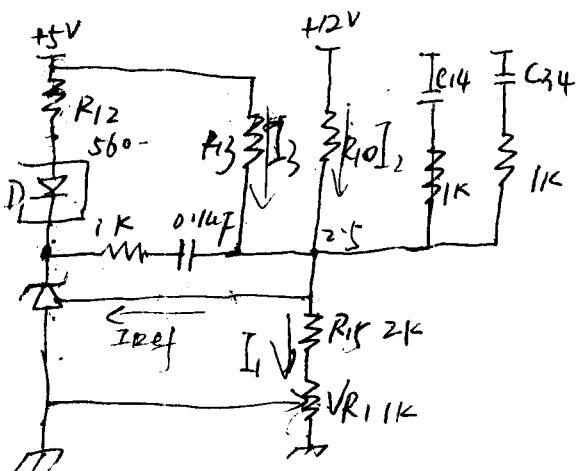

$$V_{0,t} + V_{\alpha} = \frac{V_{\min} p_S}{Np}, \quad (1)$$

由 $V_{ref} = 2.5V$, 故以 $R_{15} + VR_1$ 通常可取 $2.5k\Omega$, 则 $I_1 = \frac{2.5V}{2.5k\Omega} = 1mA$,

∴ I_{Ref} 为流过率为 $2-4 \mu A$ 所以 $I_3 + I_2 = I_1$


取 $I_3 = I_2 = 50\% 21$

$$\therefore R_{10} = \frac{12V - 2.5V}{0.5mA} = 19k$$

$$R_{13} = \frac{5V - 2.5V}{0.5mA} = 5k\Omega$$


$$若 I_{KA} = 3mA, V_{K/A} = 2.5V, V_{D_1} = 1V,$$
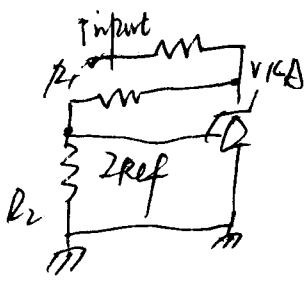
$$R_{12} = \frac{1.5V}{2mA} = 750\Omega - \text{答: } 750\Omega : 10mA : 12mA : R_{12} = 150\Omega -$$



$$V_{KFF} = V_{ref} \left(1 + \frac{P_1}{P_2} \right) + V_{ref} \times P_1$$

SNUBBER circuit :

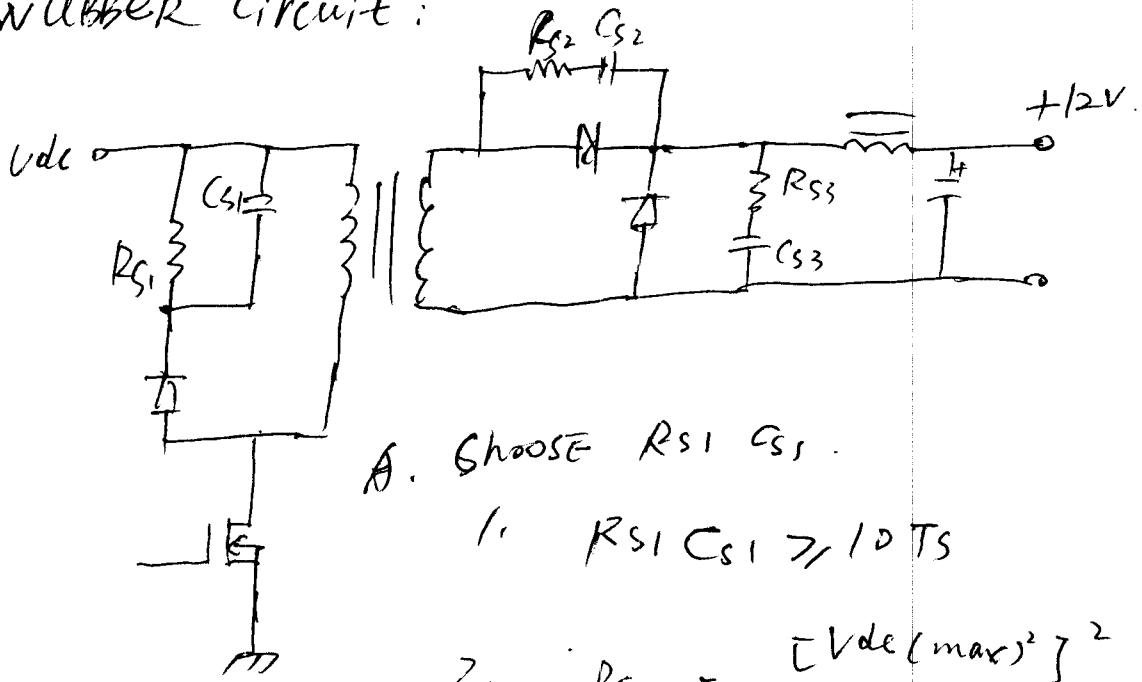

B. Choose R_{S2} , R_{S3}

$$R_{S2}, R_{S3} \leq \frac{V_{RRM}}{I_{RM}}$$

$$I_{RM} = \frac{2\alpha_{rr}}{\tau_{rr}}$$

$\alpha_{rr} = C_{jv}$: STORED CHARGE IN THE JUNCTION CAPACITANCE

err: DIODE RECOVERY

C. Choose C_{S2} , C_{S3}

$$C_{S2}C_{S3} \geq \frac{L_{LS} I_{RM}^2}{V_{RRM}^2}$$

D. R_{S2} , R_{S3} RAT^{ing}

$$P_{RS2} ; (P_{RS3}) = \frac{F_s \times C_{S2} \times V}{2}$$