



SYNC POWER CORP. >>>

<http://www.syncpower.com>

# Synchronous Rectifier in Forward Converter



## **A. Rectifier Circuit**

## **B. Rectifier Concept**

## **C. Synchronous Rectifier**

C -1 : RCD Clamp & Self - Driven SRs

C -2 : Active Clamp & Self - Driven SRs

C -3 : Control – Driven

## **D. Power Loss Comparisons**

## **E. Efficiency Curve**



## A. Rectifier Circuit

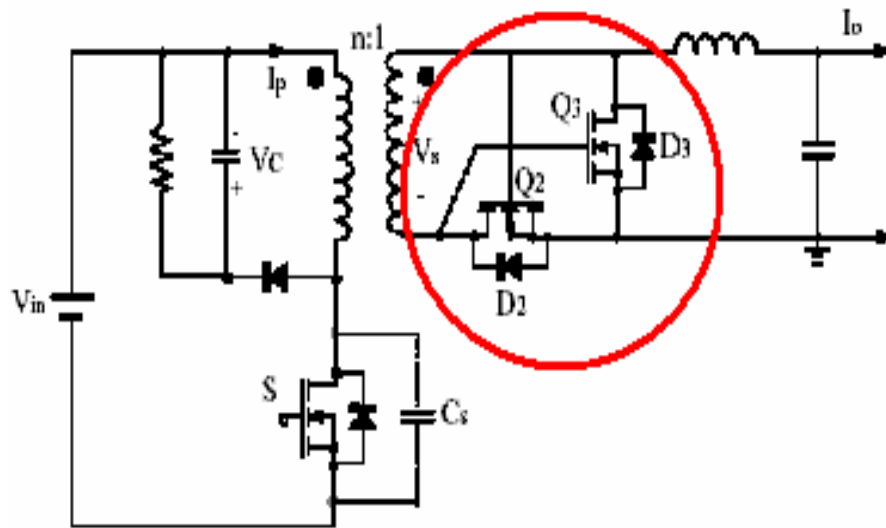


Fig1 : Forward Converter with MOSFET



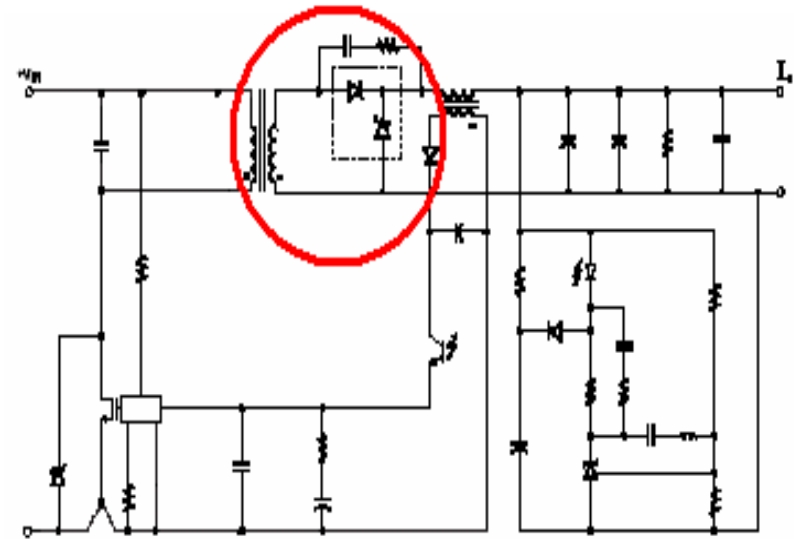


Fig2 : Forward Converter with Diode

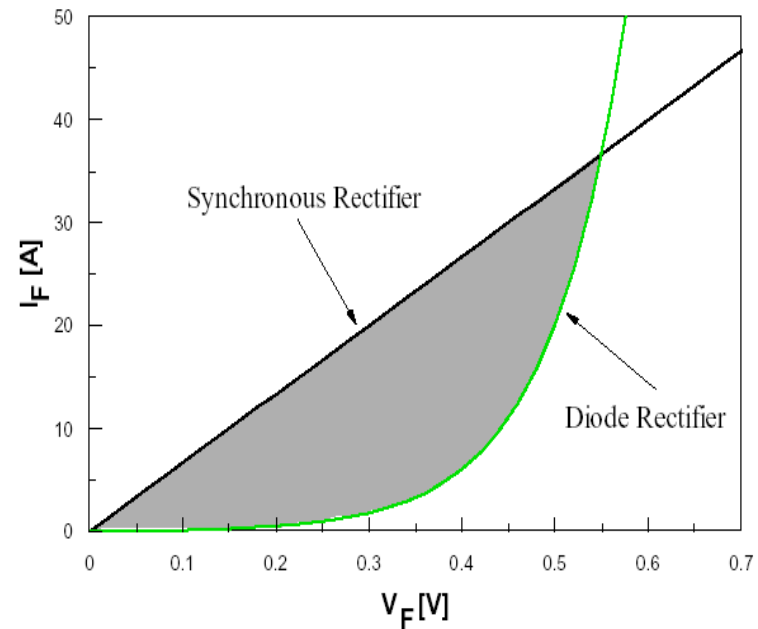

## B. Rectifier Concept

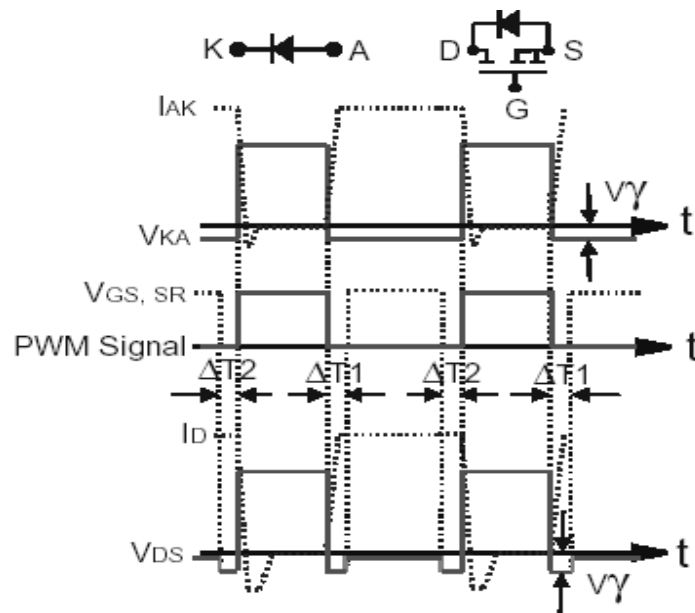


The switching losses caused by the reverse recovery current of the body - diode will be dependent of the carried current in the instant in the which the voltage between anode and cathode reverses become negative




# C. Synchronous Rectifier

## C-1 RCD Clamp & Self – Driven SRs

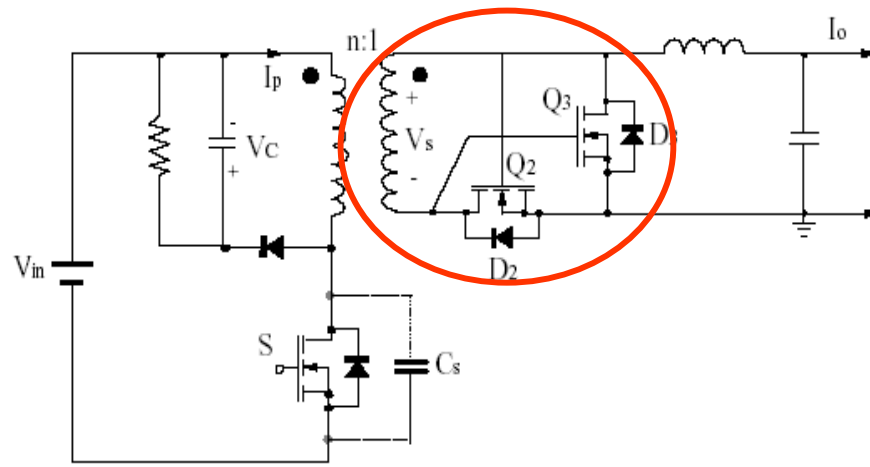

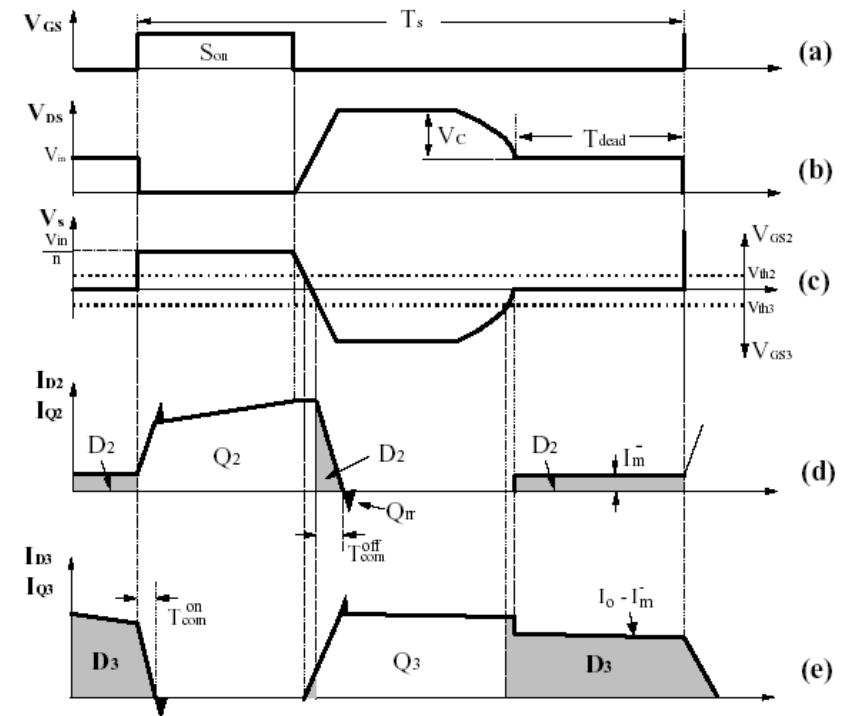
- (a) Gate –Driver signal
- (b) Drain to Source voltage of primary switch
- (c) Secondary winding voltage
- (d) Current through SR2
- (e) Current through SR3






# C. Synchronous Rectifier

## C-2 Active Clamp & Self – Driven SRs

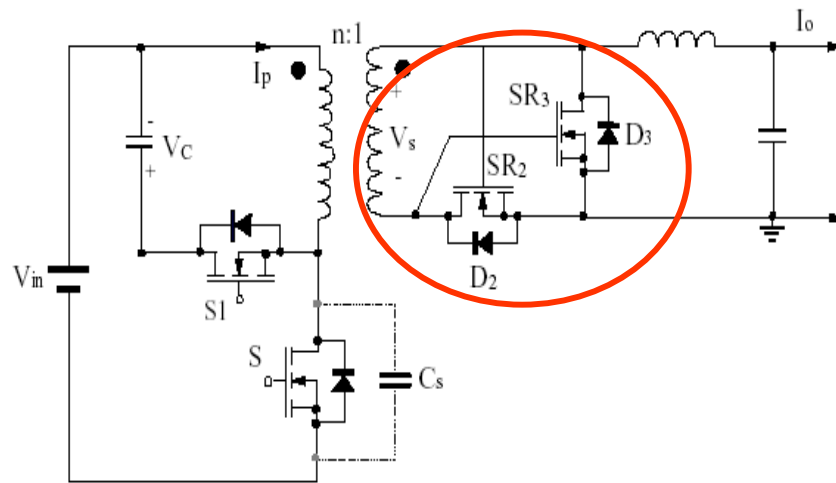

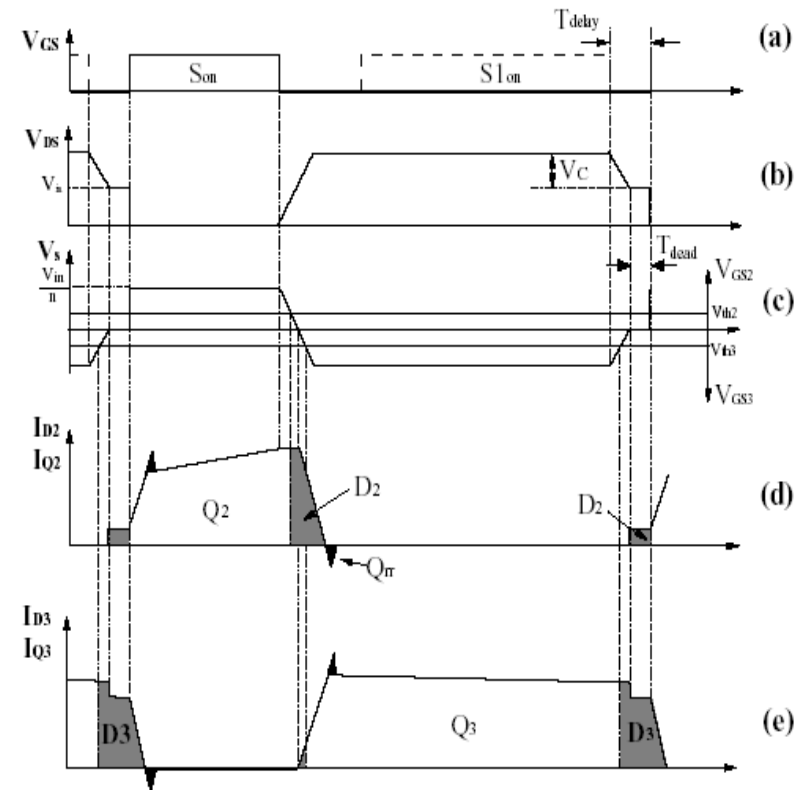- (a) Gate –Driver signal
- (b) Drain to Source voltage of primary switch
- (c) Secondary winding voltage
- (d) Current through SR2
- (e) Current through SR3









# C. Synchronous Rectifier

## C-3 Control – Driven SRs

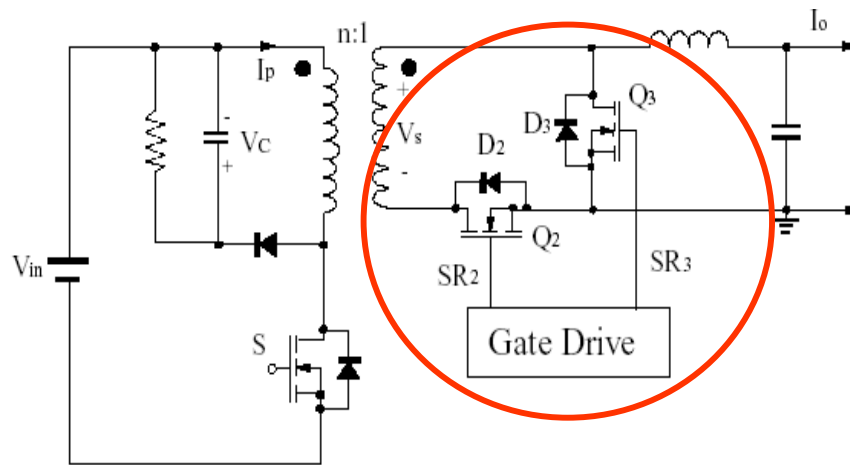

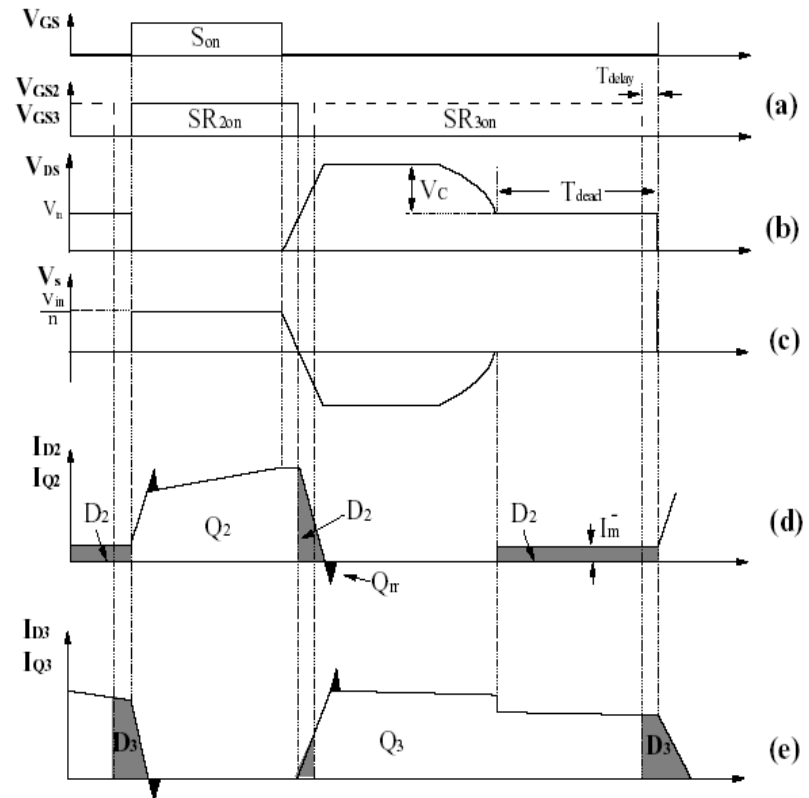
- (a) Gate –Driver signal
- (b) Drain to Source voltage of primary switch
- (c) Secondary winding voltage
- (d) Current through SR2
- (e) Current through SR3




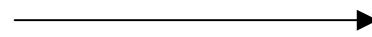
## D. Power Loss Comparisons

$$\eta = \frac{P_o}{P_o + P_{loss} + P_{REC}}$$




Converter efficiency

$$\eta_{SH} = \frac{P_o}{P_o + P_{loss} + P_{SH}}$$



Converter Efficiency  
( For Schottky Rectifiers )
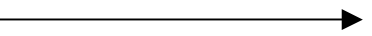
$$\eta_{SR} = \frac{P_o}{P_o + P_{loss} + P_{SR}}$$



Converter Efficiency  
( For Synchronous Rectifiers )

$P_o$  : Output Power  
 $P_{SH}$  : Schottky Rectifiers Loss

$P_{loss}$  : Total Loss ;  
 $P_{SR}$  : Synchronous Rectifiers Loss





## D. Power Loss Comparisons

$$P_{SH} = V_{SH} I_o \longrightarrow \text{Schottky Power Loss}$$

$$P_{SR}^{sd} = R_{DS(on)} I_o^2 (1 - D_{dead}) + V_D I_o D_{dead} + P_{gate} + P_{RREC} \longrightarrow \text{Self - Driven SR Loss}$$

$$P_{SR}^{cd} = R_{DS(on)} I_o^2 (1 - D_{dead}) + R_{DS(on)} (I_o - I_m^-)^2 (D_{dead} - D_{delay}) \longrightarrow \text{Control - Driven SR Loss}$$
$$+ V_D I_m^- D_{dead} + V_D (I_o - I_m^-) D_{delay} + P_{gate} + P_{RREC}$$



## D. Power Loss Comparisons

$$\frac{I}{\eta_{SR}^{sd}} = \frac{I}{\eta_{SH}} - \frac{V_{SH}}{V_o} \left[ 1 - \frac{R_{DS(on)} I_o}{V_{SH}} (1 - D_{dead}) - \frac{V_D}{V_{SH}} D_{dead} \right] \longrightarrow \text{Efficiency (RCD Self-Driven SRs)}$$



$$\frac{I}{\eta_{SR}^{acl}} = \frac{I}{\eta_{SH}} - \frac{V_{SH}}{V_o} \left[ 1 - \frac{R_{DS(on)} I_o}{V_{SH}} \right] \longrightarrow \text{Efficiency (Active Self-Driven SRs)}$$

$$\frac{I}{\eta_{SR}^{cd}} = \frac{I}{\eta_{SH}} - \frac{V_{SH}}{V_o} \left[ 1 - \frac{R_{DS(on)} I_o}{V_{SH}} (1 - D_{dead}) - \frac{R_{DS(on)} I_o}{V_{SH}} \left( 1 - \frac{I_m^-}{I_o} \right)^2 (D_{dead} - D_{delay}) - \frac{V_D}{V_{SH}} \frac{I_m^-}{I_o} D_{dead} - \frac{V_D}{V_{SH}} \left( 1 - \frac{I_m^-}{I_o} \right) D_{delay} \right] \longrightarrow \text{Efficiency (Control-Driven SRs)}$$

$V_D = V_{SH} = \text{Body Diode Voltage}$  ;  $D_{dead} = \text{dead time duty cycle}$  ;  $D_{delay} = \text{delay time duty cycle}$




## E. Efficiency Curve

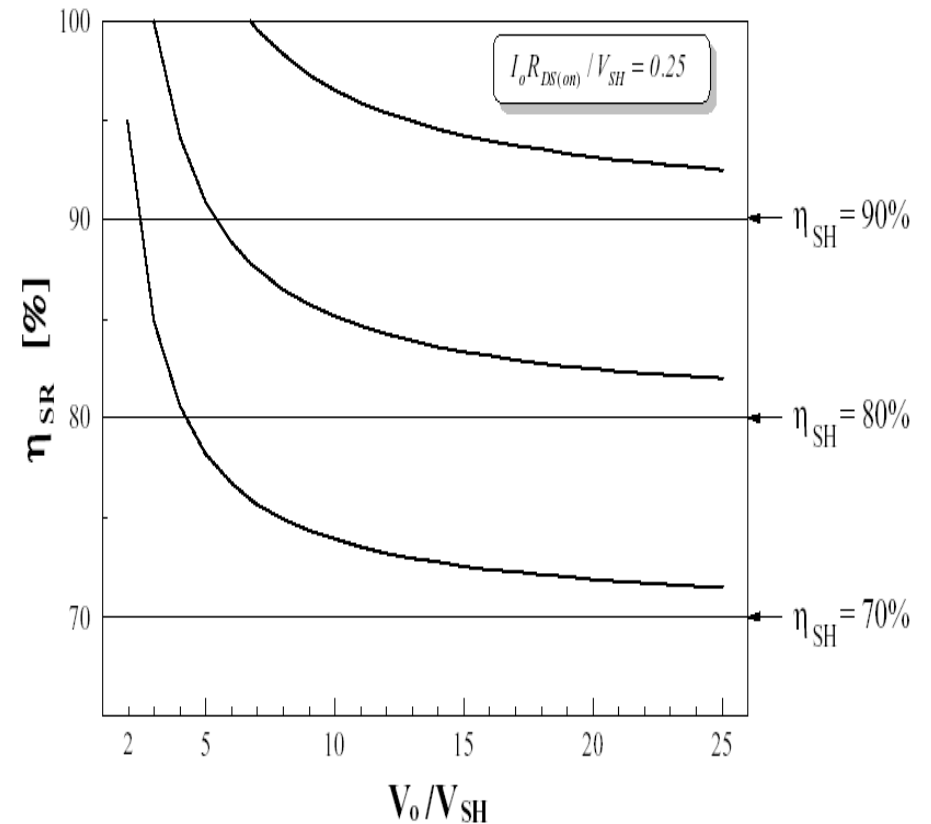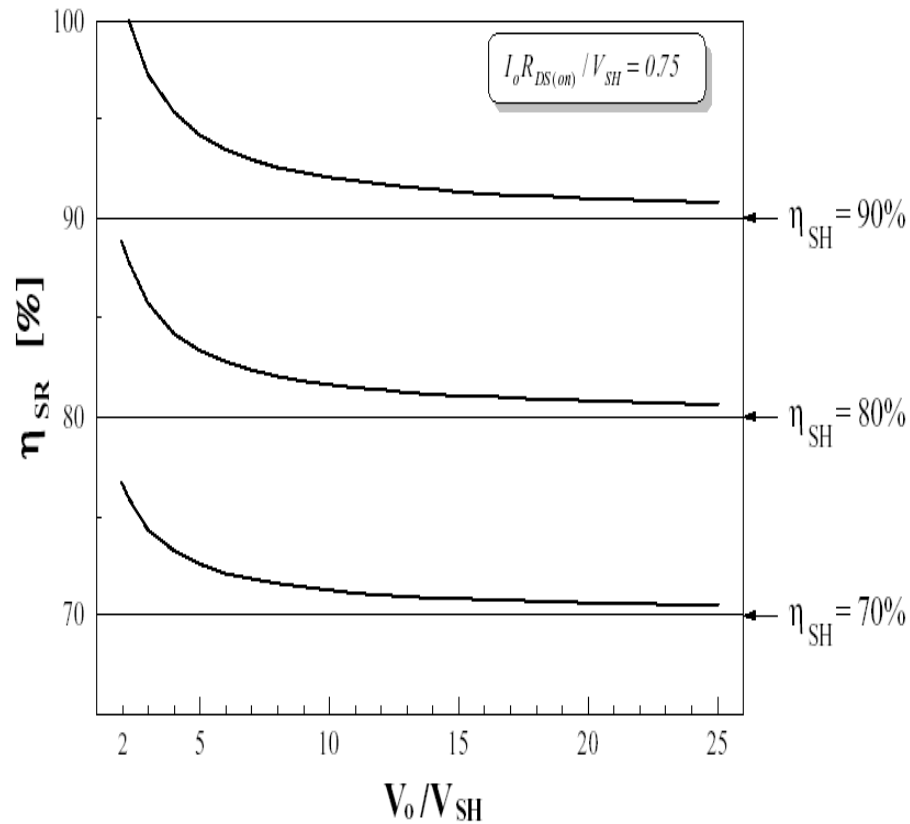

$$D_{\text{delay}} \approx 0$$



## E. Efficiency Curve

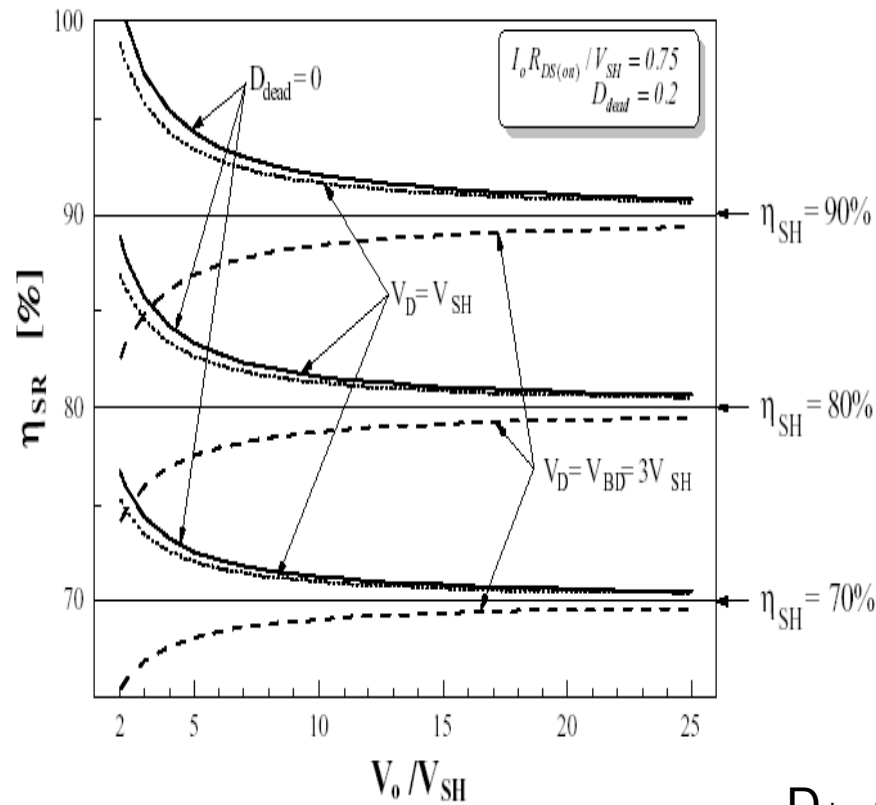

$D_{dead} \approx 0.2$

