

Lecture Notes

Snubber Circuits

Outline

- A. Overview of Snubber Circuits
- B. Diode Snubbers
- C. Turn-off Snubbers
- D. Overvoltage Snubbers
- E. Turn-on Snubbers
- F. Thyristor Snubbers

Overview of Snubber Circuits for Hard-Switched Converters


Function: Protect semiconductor devices by:

- Limiting device voltages during turn-off transients
- Limiting device currents during turn-on transients
- Limiting the rate-of-rise (di/dt) of currents through the semiconductor device at device turn-on
- Limiting the rate-of-rise (dv/dt) of voltages across the semiconductor device at device turn-off
- Shaping the switching trajectory of the device as it turns on/off


Types of Snubber Circuits

1. Unpolarized series R-C snubbers
 - Used to protect diodes and thyristors
2. Polarized R-C snubbers
 - Used as turn-off snubbers to shape the turn-on switching trajectory of controlled switches.
 - Used as overvoltage snubbers to clamp voltages applied to controlled switches to safe values.
 - Limit dv/dt during device turn-off
3. Polarized L-R snubbers
 - Used as turn-on snubbers to shape the turn-off switching trajectory of controlled switches.
 - Limit di/dt during device turn-on

Need for Diode Snubber Circuit

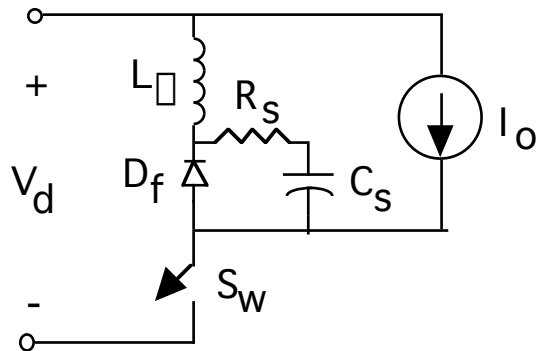


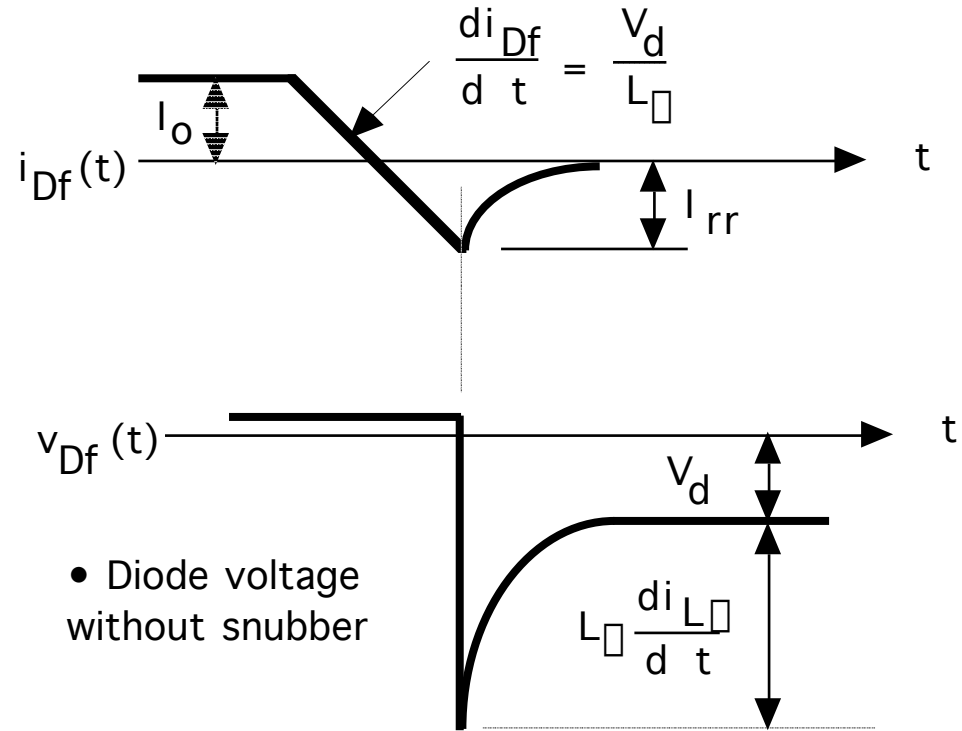- L_l = stray inductance
- S_W closes at $t = 0$
- $R_s - C_s$ = snubber circuit




- Diode breakdown if $V_d + L_l \frac{di_{L_l}}{dt} > BV_{BD}$

Equivalent Circuits for Diode Snubber

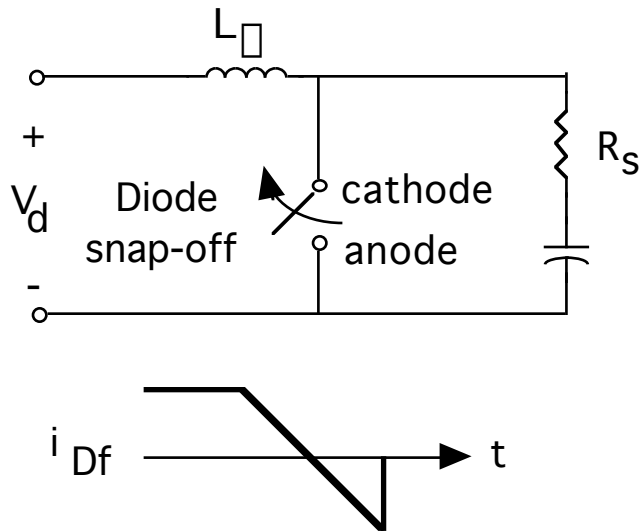

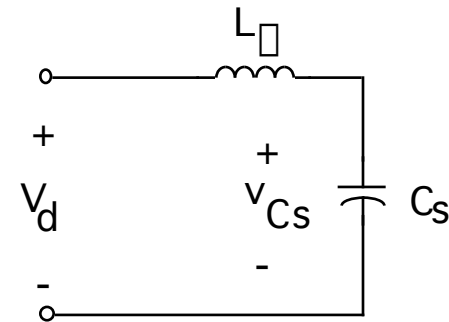- Simplified snubber - the capacitive snubber




- Worst case assumption - diode snaps off instantaneously at end of diode recovery

- $R_s = 0$
- $v_{Cs} = -v_{Df}$

- Governing equation -
$$\frac{d^2 v_{Cs}}{dt^2} + \frac{v_{Cs}}{L_{\square} C_s} = \frac{V_d}{L_{\square} C_s}$$
- Boundary conditions - $v_{Cs}(0^+) = 0$ and $i_{L_{\square}}(0^+) = I_{rr}$


Performance of Capacitive Snubber

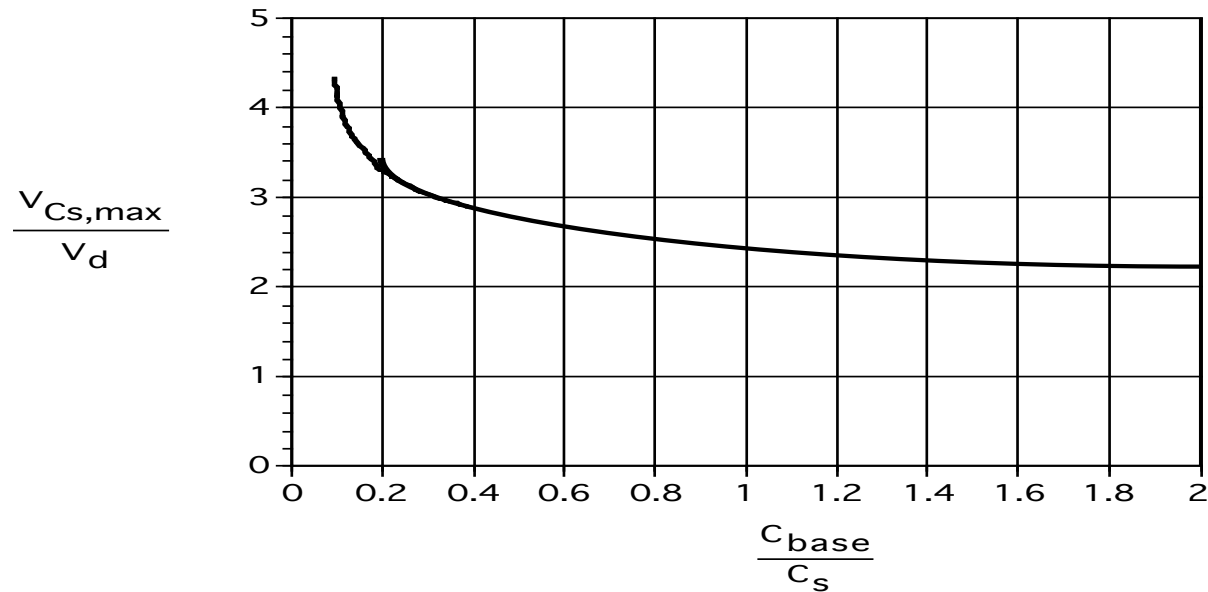- $$v_{Cs}(t) = V_d - V_d \cos(\omega_o t) + V_d \sqrt{\frac{C_{base}}{C_s}} \sin(\omega_o t)$$
- $$\omega_o = \frac{1}{\sqrt{L_{\sigma} C_s}} \quad ; \quad C_{base} = L_{\sigma} \frac{I_{rr}^2}{V_d^2}$$
- $$V_{Cs,max} = V_d \left[1 + \sqrt{1 + \frac{C_{base}}{C_s}} \right]$$



Effect of Adding Snubber Resistance

Snubber Equivalent Circuit

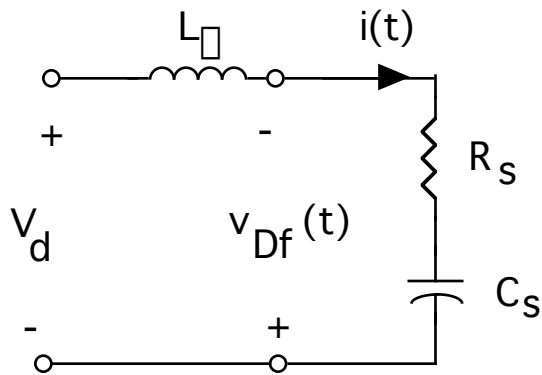

- Governing equation $L_s \frac{d^2 i}{dt^2} + R_s \frac{di}{dt} + \frac{i}{C_s} = 0$
- Boundary conditions
 $i(0^+) = I_{rr}$ and $\frac{di(0^+)}{dt} = \frac{V_d - I_{rr} R_s}{L_s}$

Diode voltage as a function of time


$$\frac{V_{df}}{V_d}(t) = -1 - \frac{e^{-\alpha t}}{\sqrt{1-x^2} \cos(\beta)} \sin(\alpha_a t - \beta + \beta) \quad ; \quad R_s \leq 2 R_b$$

$$\alpha_a = \alpha_o \sqrt{1 - \left(\frac{x}{\alpha_o}\right)^2} \quad ; \quad \beta = \frac{R_s}{2L_s} \quad ; \quad \alpha_o = \frac{1}{\sqrt{L_s C_s}} \quad ; \quad \beta = \tan^{-1} \frac{(2-x)\sqrt{1-x^2}}{\sqrt{4\alpha_o^2 x^2}}$$


$$\alpha = \frac{C_s}{C_b} \quad ; \quad x = \frac{R_s}{R_b} \quad ; \quad R_b = \frac{V_d}{I_{rr}} \quad ; \quad C_b = \frac{L_s [I_{rr}]^2}{V_d^2} \quad ; \quad \beta = \tan^{-1}(\beta/\alpha_a)$$

Performance of R-C Snubber

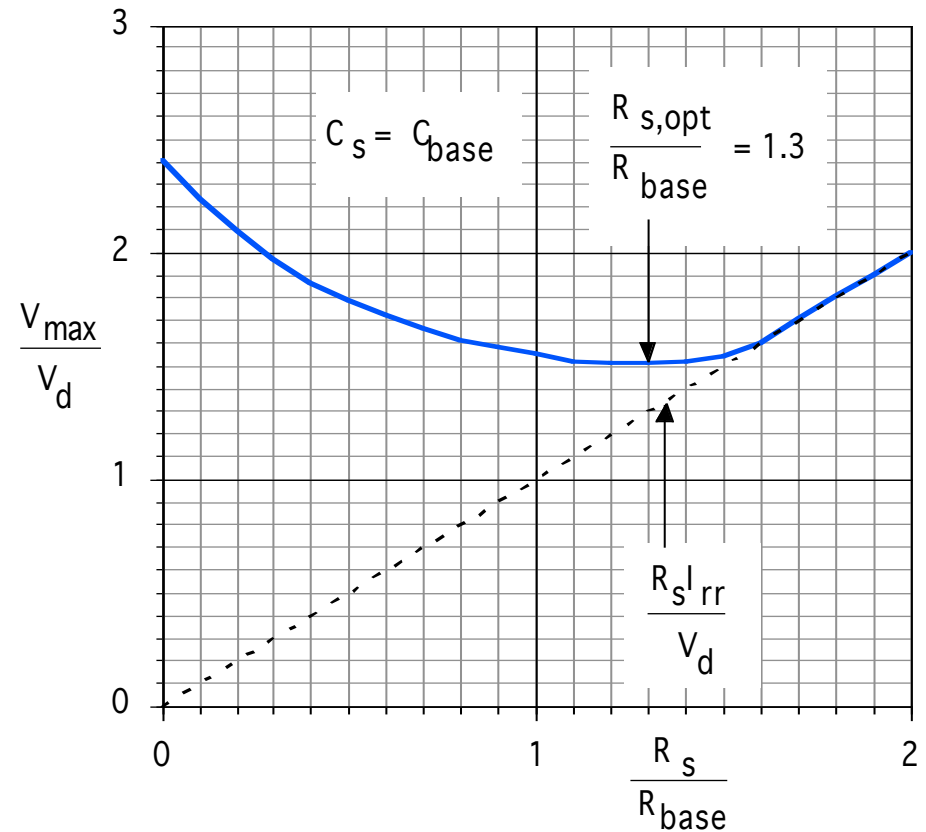- At $t = t_m$ $v_{Df}(t) = V_{max}$
- $t_m = \frac{\tan^{-1}(\omega_a/\omega)}{\omega_a} + \frac{\omega - \omega_a}{\omega_a} \geq 0$
- $\frac{V_{max}}{V_d} = 1 + \sqrt{1 + \omega^2 \omega^{-1} \omega - \omega} x \exp(-\omega t_m)$
- $\omega = \frac{C_s}{C_{base}}$ and $x = \frac{R_s}{R_{base}}$
- $C_{base} = \frac{L_s \omega I_{rr}^2}{V_d^2}$ and $R_{base} = \frac{V_d}{I_{rr}}$




Diode Snubber Design Nomogram

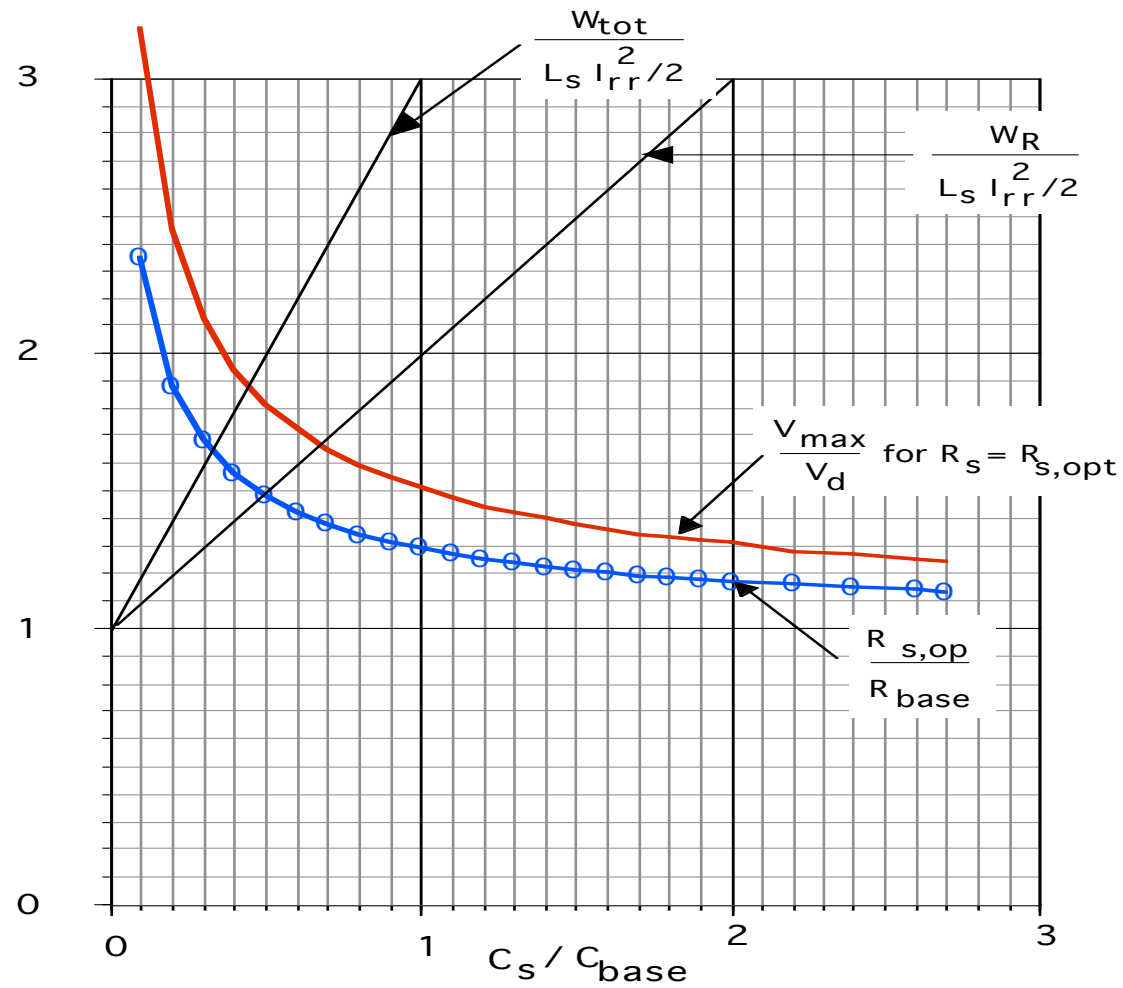


Need for Snubbers with Controlled Switches

Step-down converter

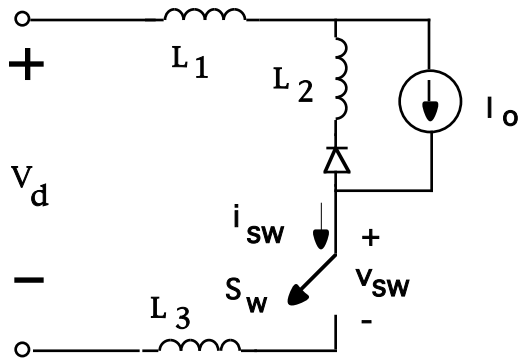


Switch current and voltage waveforms

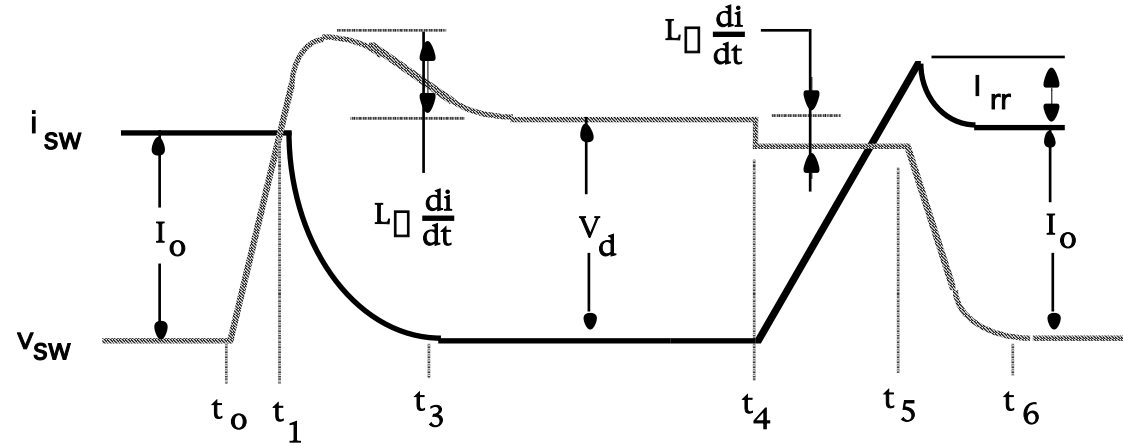

- $L_1, L_2, L_3 =$ stray inductances


Switching trajectory of switch

- $L_{\Sigma} = L_1 + L_2 + L_3$

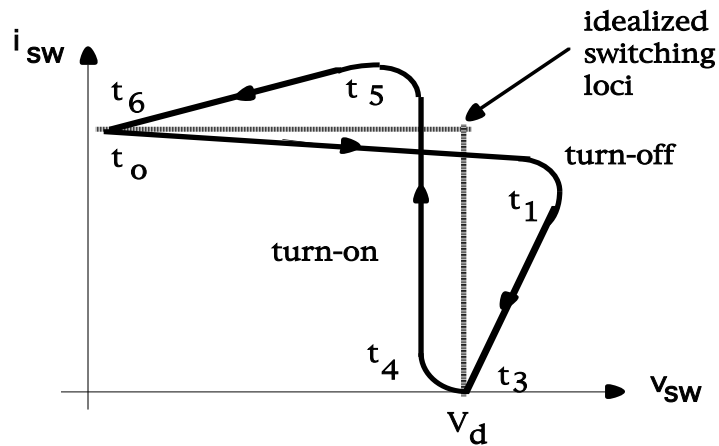


- Overvoltage at turn-off due to stray inductance
- Overcurrent at turn-on due to diode reverse recovery

Turn-off Snubber for Controlled Switches

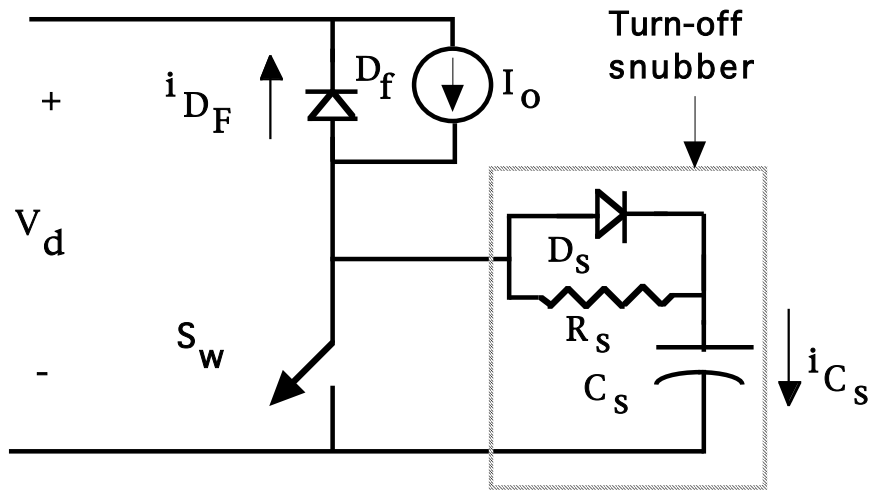

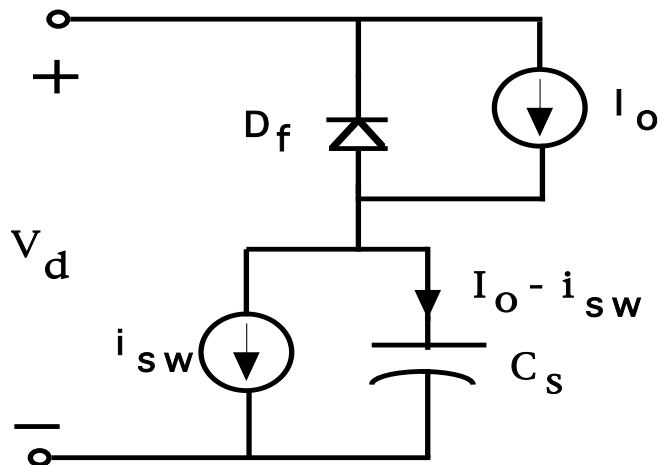Step-down converter with turn-off snubber




Equivalent circuit during switch turn-off.

- Simplifying assumptions
 1. No stray inductance.
 2. $i_{S_w}(t) = I_o(1 - t/t_{fi})$
 3. $i_{S_w}(t)$ unaffected by snubber circuit.


Turn-off Snubber Operation

- Capacitor voltage and current for $0 < t < t_{fi}$ $i_{C_s}(t) = \frac{I_o t}{t_{fi}}$ and $v_{C_s}(t) = \frac{I_o t^2}{2C_s t_{fi}}$
- For $C_s = C_{s1}$, $v_{C_s} = V_d$ at $t = t_{fi}$ yielding $C_{s1} = \frac{I_o t_{fi}}{2V_d}$


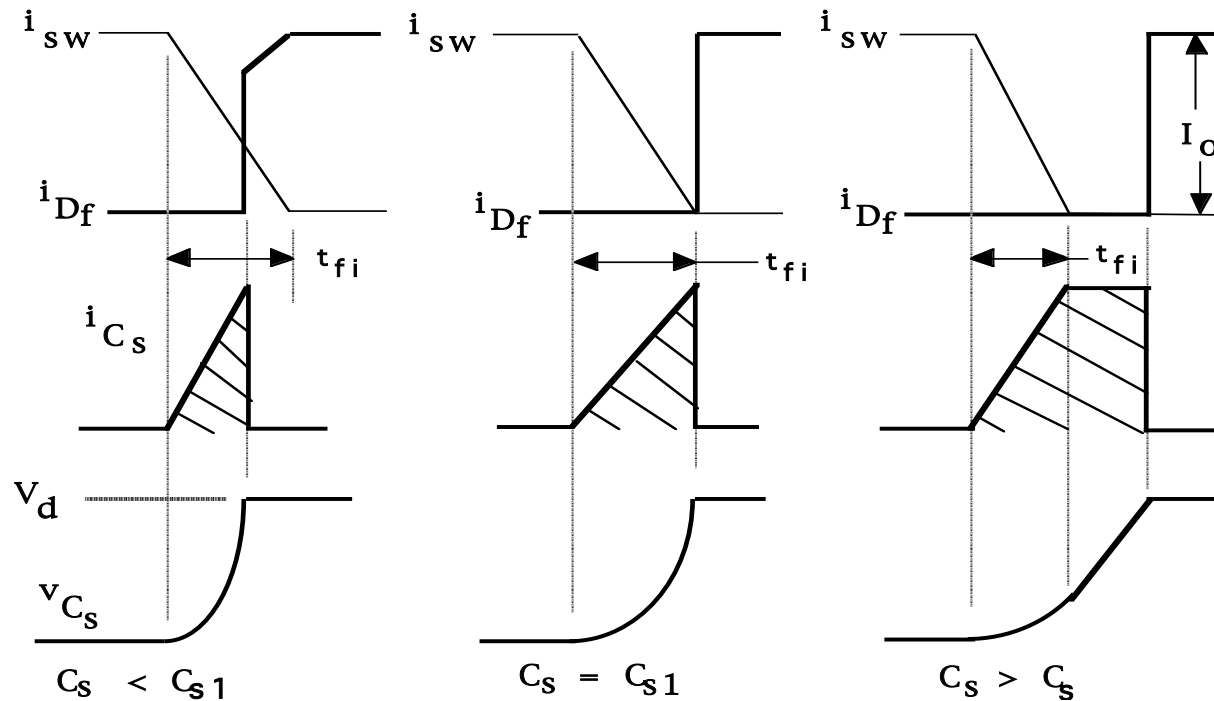
Circuit waveforms for varying values of C_s



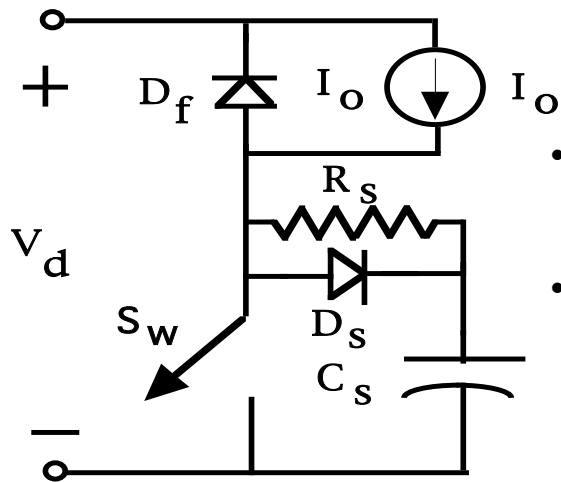Benefits of Snubber Resistance at Switch Turn-on



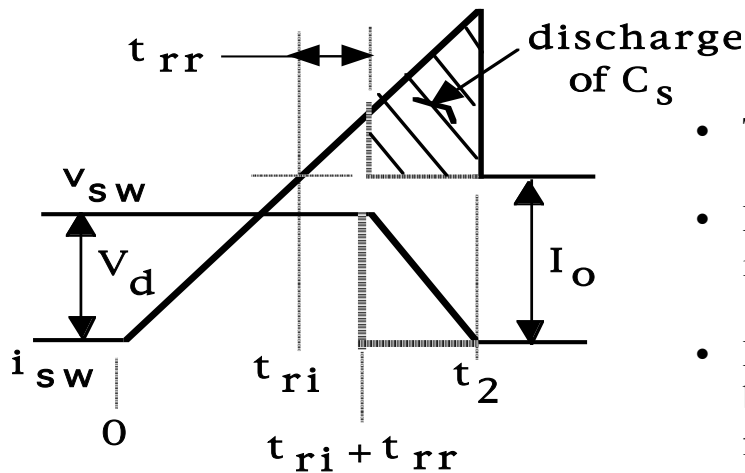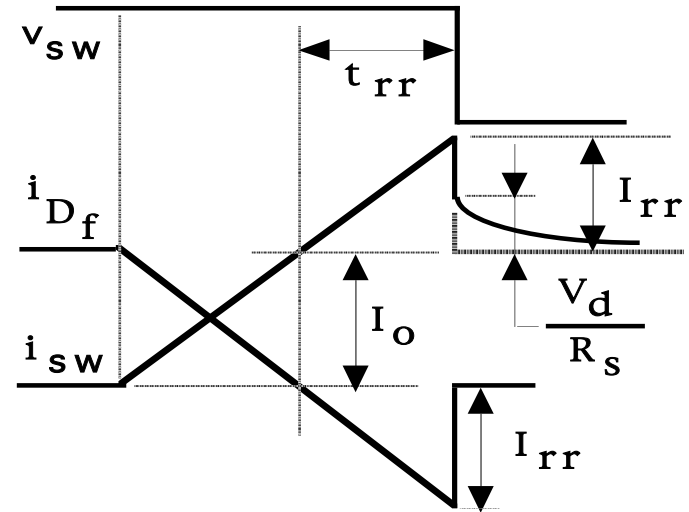
- D_s shorts out R_s during S_w turn-off.
- During S_w turn-on, D_s reverse-biased and C_s discharges thru R_s .



- Turn-on with $R_s = 0$
- Energy stored on C_s dissipated in S_w .
- Extra energy dissipation in S_w because of lengthened voltage fall time.

- Turn-on with $R_s > 0$
- Energy stored on C_s dissipated in R_s rather than in S_w .
- Voltage fall time kept quite short.

Effect of Turn-off Snubber Capacitance

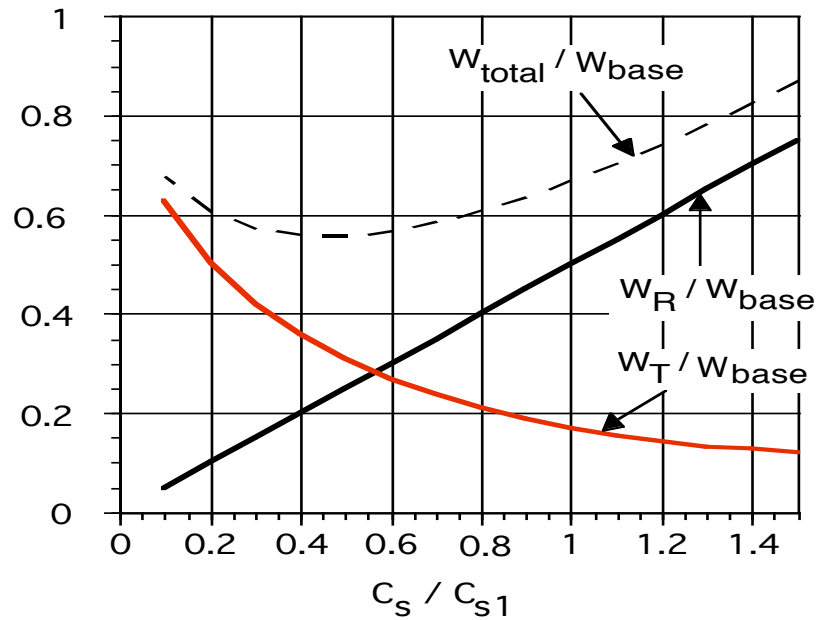

Energy dissipation


W_R = dissipation in resistor

W_T = dissipation in switch S_W

$$C_{s1} = \frac{I_o t_{fi}}{2V_d}$$

$$W_{total} = W_R + W_T$$

$$W_{base} = 0.5 V_d I_o t_{fi}$$

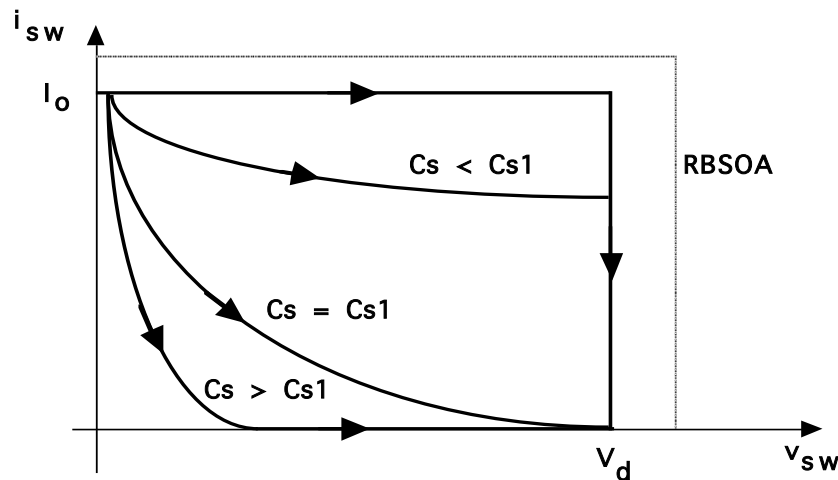

Switching trajectory

Turn-off Snubber Design Procedure

Selection of C_s

- Minimize energy dissipation (W_T) in BJT at turn-on
- Minimize $W_R + W_T$
- Keep switching locus within RBSOA
- Reasonable value is $C_s = C_{s1}$



Selection of R_s

- Limit $i_{cap}(0^+) = \frac{V_d}{R_s} < I_{rr}$
- Usually designer specifies $I_{rr} < 0.2 I_o$ so $\frac{V_d}{R_s} = 0.2 I_o$

Snubber recovery time (BJT in on-state)

- Capacitor voltage = $V_d \exp(-t/R_s C_s)$
- Time for v_{C_s} to drop to $0.1V_d$ is $2.3 R_s C_s$
- BJT must remain on for a time of $2.3 R_s C_s$

Overvoltage Snubber

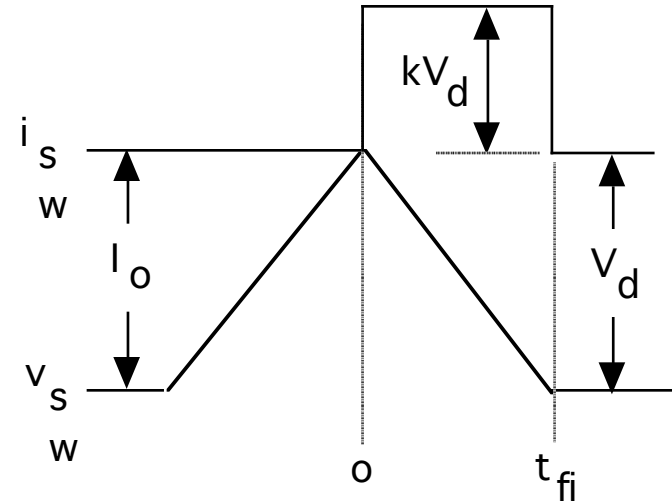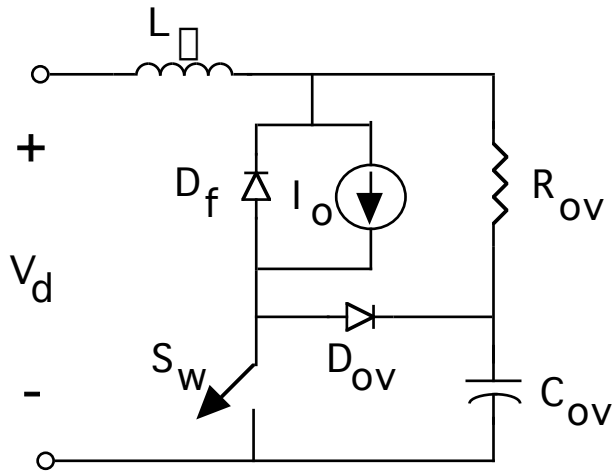

- Step-down converter with overvoltage snubber comprised of D_{ov} , C_{ov} , and R_{ov} .


- Overvoltage snubber limits overvoltage (due to stray inductance) across S_w as it turns off.

- Switch S_w waveforms without overvoltage snubber
- t_{fi} = switch current fall time ; kV_d = overvoltage on S_w

- $kV_d = L_{\square} \frac{di_{L_{\square}}}{dt} = L_{\square} \frac{I_o}{t_{fi}}$


- $L_{\square} = \frac{kV_d t_{fi}}{I_o}$

Operation of Overvoltage Snubber

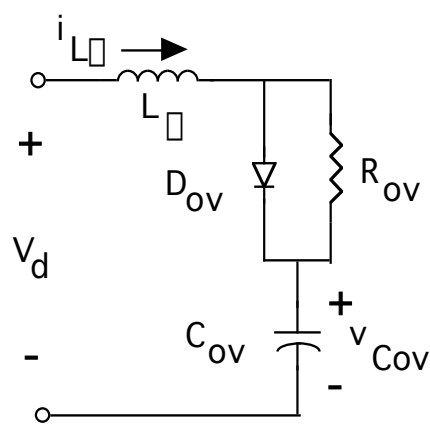

- D_{ov} on for $0 < t < \frac{\pi\sqrt{L_{\square}C_{ov}}}{2}$

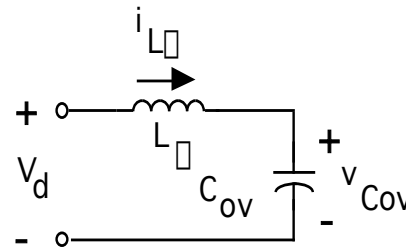- $t_{fi} \ll \frac{\pi\sqrt{L_{\square}C_{ov}}}{2}$




- Equivalent circuit while inductor current decays to zero

$$v_{Cov}(0^+) = V_d \quad i_{L_{\square}}(0^+) = I_o$$

$$i_{L_{\square}}(t) = I_o \cos\left[\frac{t}{\sqrt{L_{\square}C_{ov}}}\right]$$

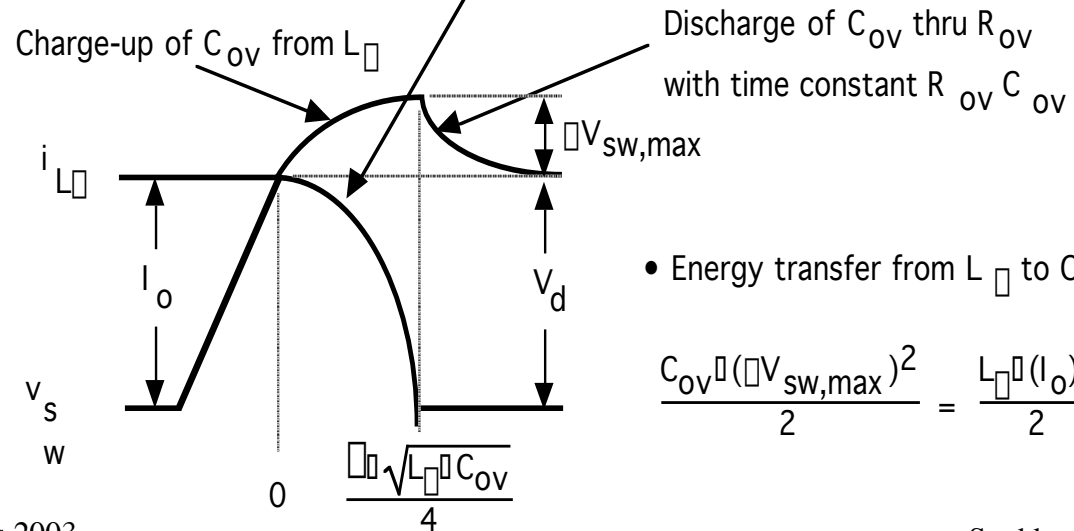- D_{ov}, C_{ov} provide alternate path for inductor current as S_w turns off.
- Switch current can fall to zero much faster than L_s current.
- D_f forced to be on (approximating a short ckt) by I_o after S_w is off.
- Equivalent circuit after turn-off of S_w .




- Energy transfer from L_{\square} to C_{ov}

$$\frac{C_{ov}(\Delta V_{sw,max})^2}{2} = \frac{L_{\square}(I_o)^2}{2}$$

Overvoltage Snubber Design


- $C_{OV} = \frac{L_S I_O^2}{(\Delta v_{sw,max})^2}$
- Limit $\Delta v_{sw,max}$ to $0.1V_d$
- Using $L_S = \frac{kV_d t_{fi}}{\Delta I_O}$ in equation for C_{OV} yields
- $C_{OV} = \frac{kV_d t_{fi} I_O^2}{\Delta I_O (0.1V_d)^2} = \frac{100k \Delta t_{fi} I_O}{\Delta V_d}$
- $C_{OV} = 200 k C_{S1}$ where $C_{S1} = \frac{t_{fi} I_O}{\Delta 2V_d}$ which is used in turn-off snubber
- Recovery time of C_{OV} ($2.3R_{OV}C_{OV}$) must be less than off-time duration, t_{off} , of the switch Sw.
- $R_{OV} \approx \frac{t_{off}}{2.3 \Delta C_{OV}}$

Turn-on Snubber

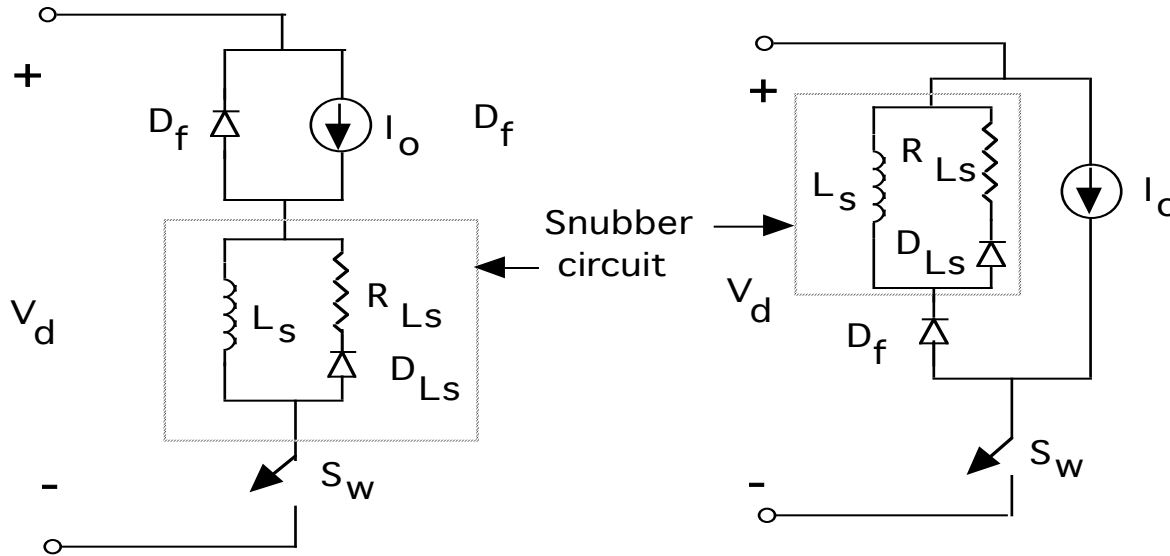

Step-down converter with turn-on snubber

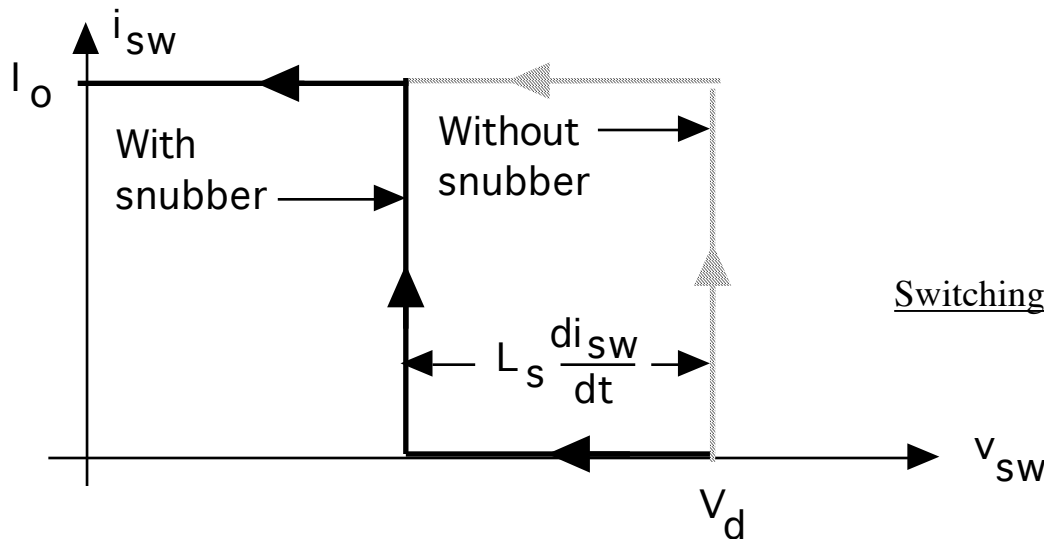- Snubber reduces V_{sw} at switch turn-on due drop across inductor L_s .
- Will limit rate-of-rise of switch current if L_s is sufficiently large.




Switching trajectory with and without turn-on snubber.

Turn-on Snubber Operating Waveforms

Small values of snubber inductance ($L_s < L_{s1}$)

- $\frac{di_{sw}}{dt}$ controlled by switch S_w and drive circuit.

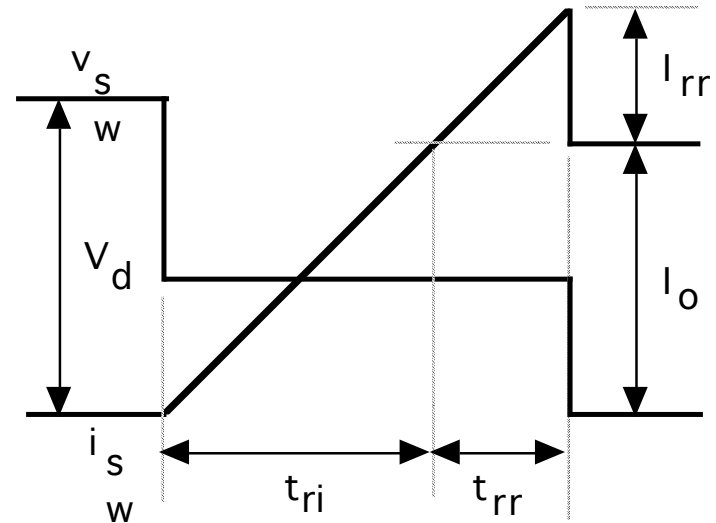- $\Delta v_{sw} = \frac{L_s I_o}{t_{ri}}$




Large values of snubber inductance ($L_s > L_{s1}$)



- $\frac{di_{sw}}{dt}$ limited by circuit to $\frac{V_d}{L_s} < \frac{I_o}{t_{ri}}$

- $L_{s1} = \frac{V_d t_{ri}}{I_o}$

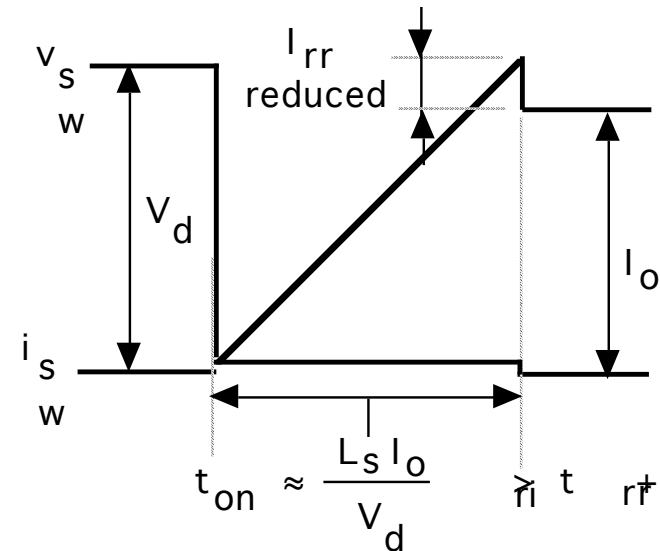- I_{rr} reduced when $L_s > L_{s1}$ because I_{rr} proportional to $\sqrt{\frac{di_{sw}}{dt}}$



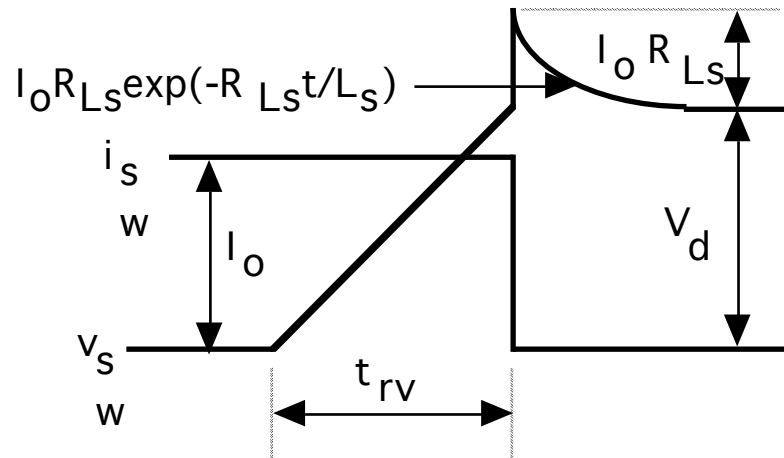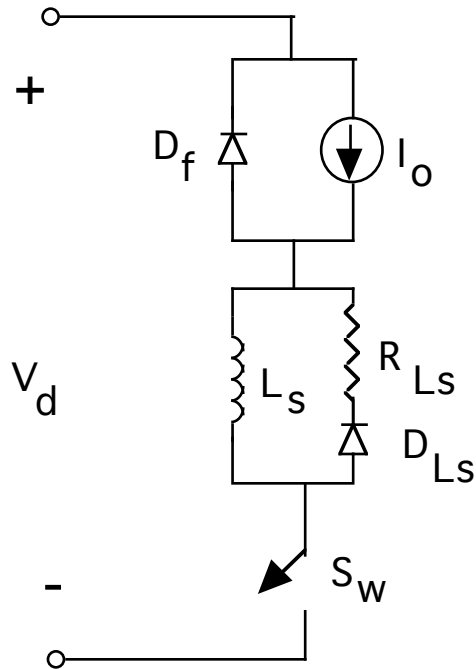Turn-on Snubber Recovery at Switch Turn-off



- Assume switch current fall time $t_{ri} = 0$.
- Inductor current must discharge thru D_{Ls} - R_{Ls} series segment.

- Switch waveforms at turn-off with turn-on snubber in circuit.
- Overvoltage smaller if t_{fi} smaller.
- Time of $2.3 L_s/R_{Ls}$ required for inductor current to decay to $0.1 I_o$
- Off-time of switch must be $> 2.3 L_s/R_{Ls}$

Turn-on Snubber Design Trade-offs

Selection of inductor

- Larger L_s decreases energy dissipation in switch at turn-on
 - $W_{sw} = W_B (1 + I_{rr}/I_o)^2 [1 - L_s/L_{s1}]$
 - $W_B = V_d I_o t_{fi}/2$ and $L_{s1} = V_d t_{fi}/I_o$
 - $L_s > L_{s1}$ $W_{sw} = 0$
- Larger L_s increases energy dissipation in R_{Ls}
 - $W_R = W_B L_s / L_{s1}$
- $L_s > L_{s1}$ reduces magnitude of reverse recovery current I_{rr}
- Inductor must carry current I_o when switch is on - makes inductor expensive and hence turn-on snubber seldom used


Selection of resistor R_{Ls}

- Smaller values of R_{Ls} reduce switch overvoltage $I_o R_{Ls}$ at turn-off
- Limiting overvoltage to $0.1V_d$ yields $R_{Ls} = 0.1 V_d/I_o$
- Larger values of R_{Ls} shortens minimum switch off-time of $2.3 L_s/R_{Ls}$

Thyristor Snubber Circuit


3-phase thyristor circuit with snubbers

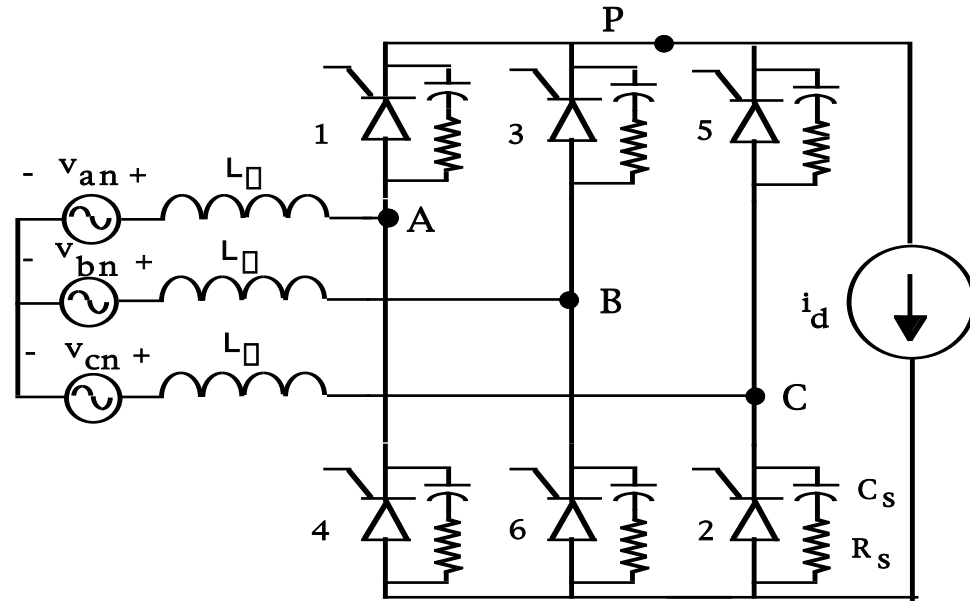- $v_{an}(t) = V_s \sin(\omega t)$, $v_{bn}(t) = V_s \sin(\omega t - 120^\circ)$,
 $v_{cn}(t) = V_s \sin(\omega t - 240^\circ)$



Phase-to-neutral waveforms

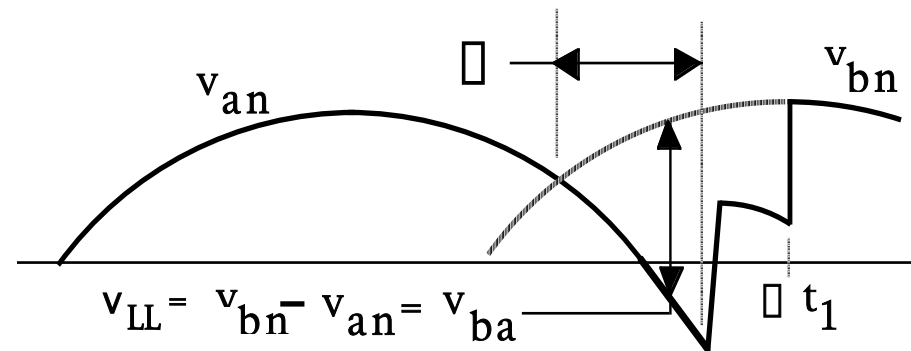- $v_{LL}(t) = \sqrt{3} V_s \sin(\omega t - 60^\circ)$
- Maximum rms line-to-line voltage $V_{LL} = \sqrt{\frac{3}{2}} V_s$




Equivalent Circuit for SCR Snubber Calculations

Assumptions

- Trigger angle $\alpha = 90^\circ$ so that $v_{LL}(t) = \text{maximum} = \sqrt{2} V_{LL}$
- Reverse recovery time $t_{rr} \ll$ period of ac waveform so that $v_{LL}(t)$ equals a constant value of $v_{ba}(\alpha t_1) = \sqrt{2} V_{LL}$
- Worst case stray inductance L_\square gives rise to reactance equal to or less than 5% of line impedance.
- Line impedance $= \frac{V_s}{\sqrt{2}I_{a1}} = \frac{\sqrt{2}V_{LL}}{\sqrt{6}I_{a1}} = \frac{V_{LL}}{\sqrt{3}I_{a1}}$
where I_{a1} = rms value of fundamental component of the line current.
- $\square L_\square = 0.05 \frac{V_{LL}}{\sqrt{3}I_{a1}}$

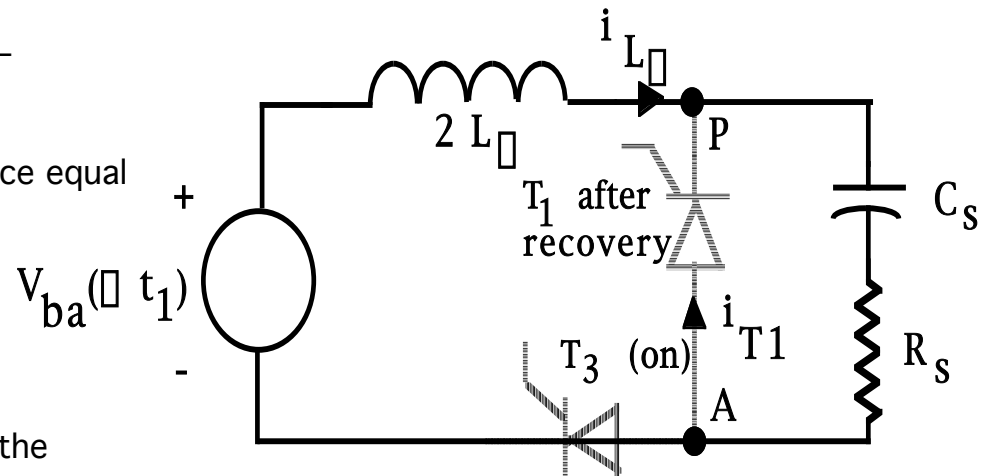Equivalent circuit after T1 reverse recovery



Component Values for Thyristor Snubber

- Use same design as for diode snubber but adapt the formulas to the thyristor circuit notation

- Snubber capacitor $C_S = C_{base} = L \frac{I_{rr}}{V_d}$

- From snubber equivalent circuit $2 L \frac{di_{L}}{dt} = \sqrt{2} V_{LL}$

- $I_{rr} = \frac{di_{L}}{dt} t_{rr} = \frac{\sqrt{2} V_{LL}}{2L} t_{rr} = \frac{\sqrt{2} V_{LL}}{0.05 \sqrt{3} V_{LL}} t_{rr} = 25 \frac{V_{LL}}{\sqrt{3} I_{a1}} t_{rr}$

- $V_d = \sqrt{2} V_{LL}$

- $C_S = C_{base} = \frac{0.05 \sqrt{3} I_{a1} t_{rr}}{\sqrt{3} I_{a1}} \left(\frac{25 \sqrt{3} I_{a1} t_{rr}}{\sqrt{3} V_{LL}} \right)^2 = \frac{8.7 \sqrt{3} I_{a1} t_{rr}}{V_{LL}}$

- Snubber resistance $R_S = 1.3 R_{base} = 1.3 \frac{V_d}{I_{rr}}$

- $R_S = 1.3 \frac{\sqrt{2} V_{LL}}{25 \sqrt{3} I_{a1} t_{rr}} = \frac{0.07 \sqrt{2} V_{LL}}{\sqrt{3} I_{a1} t_{rr}}$

- Energy dissipated per cycle in snubber resistance = W_R

- $W_R = \frac{L I_{rr}^2}{2} + \frac{C_S V_d^2}{2} = 18 \sqrt{3} I_{a1} V_{LL} (t_{rr})^2$