

Active Clamp Forward Converters

Design Using UCC2897



Hong Huang



August 2007

1

Presentation Content

- Review of Active Clamp and Reset Technique in Single-Ended Forward Converters
- Design Material/Tools
- Design procedure and concern
- Common Problems in Self-driven Sync Rectifier
- Control-driven and TPS28225
- Main switch ZVS / VVS
- Comparison ACFC and HB in telecom applications
- Gate Drive Signals
- Solution to the problem of power-off oscillation

Review of Active Clamp Reset Technique

 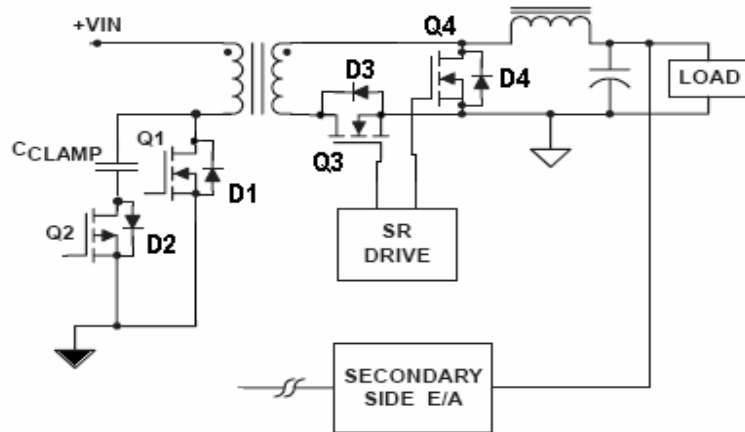

Typical configurations (a) Low side clamp

(b) high side clamp

- Detailed comparison can be found in TI Application Note ([SLUA322](#))
Active Clamp Transformer Reset: High Side or Low Side?
- Main differences:
 - (a) Gate driving scheme
 - (b) Clamp and Reset voltage ratings
 - (c) MOSFET type for clamping

Review of Active Clamp Reset Technique



Behind Your Designs

PARAMETER	HIGH-SIDE CLAMP	LOW-SIDE CLAMP
V_{DS}	$\left(\frac{1}{1-D}\right) \times V_{IN}$	$\left(\frac{1}{1-D}\right) \times V_{IN}$
V_{RESET}	$\left(\frac{D}{1-D}\right) \times V_{IN}$	$\left(\frac{D}{1-D}\right) \times V_{IN}$
V_C	$\left(\frac{D}{1-D}\right) \times V_{IN}$	$\left(\frac{1}{1-D}\right) \times V_{IN}$
C_{cl} (applied voltage)	Lower voltage by V_{IN} Volts Highest V_{cl} occurs at D_{MAX} Careful attention for wide V_{IN} applications	Higher voltage by V_{IN} Volts Transformer turns ratio critical at for limiting V_{cl} Careful attention for off-line, high voltage applications
C_{cl} (component value)	Same value as low side for given ripple voltage	Same value as high side for given ripple voltage
AUX MOSFET	N-Channel Must be used for 400-V (off-line) input applications	P-Channel Can't be used for 400V applications due to limited V_{DS} rating of available devices
Gate drive	Gate drive transformer required AUX MOSFET V_{GS} out of phase with main MOSFET V_{GS} – UCC2893 PWM Controller	Simple RCD clamp gate drive AUX MOSFET V_{GS} in phase with main MOSFET V_{GS} – UCC2891 PWM Controller

Comparison of High- and Low-Side Clamp

Review of Active Clamp Reset Technique


Behind Your Designs

 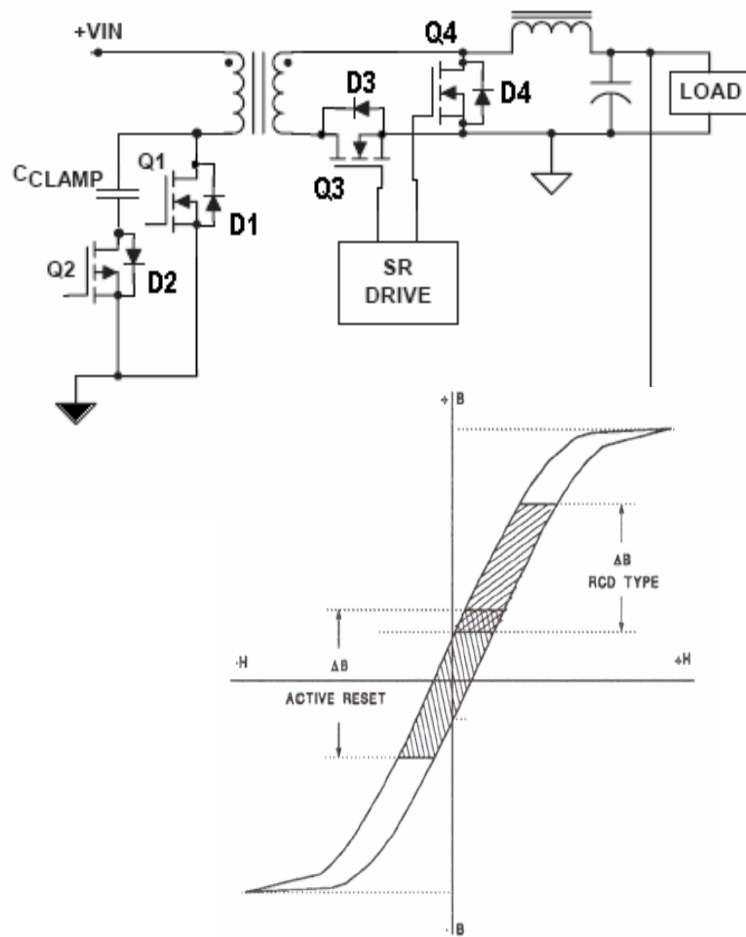


- Voltage Clamp
- Transformer reset

- Step-by-Step Design Procedure
 - Designing for High Efficiency with the Active Clamp UCC2891 PWM Controller ([SLUA303](#))
 - Advances / Differences of UCC2897 from UCC2891
 - (a) 20 –pin, QFN
 - (b) LineOV
 - (c) PGND
 - (d) Hiccup OCP
 - (e) Bi-directional f-sync
 - (d) FB and SS 2.5V instead of 1.25V
- MathCad Design Files (Power stage and Loop design)
- EVMs (UCC2891, UCC2897, UCC2894)

 - EVM Specs: $V_{in} = 36V$ to $75V$, $V_o = 3.3V$, $I_o = 30A$, $P_o = 100W$





UCC2891 EVM

 

UCC2897 EVM

 
 
Input voltage: 390Vdc
Rated Power: 320W
Output voltage: 12Vdc
Output current: 26A



- Power stage design
- Program IC
- Switching frequency, magnetizing inductance, two resonant frequencies, and dead-time
- Switching losses and ZVS/VVS
- Capacitance at Vref and VDD should be minimum ratio 1:10 (e.g. if Vref cap is .1uF then VDD cap minimum 1.0uF)
- Observing Vref maximum load capability, less than 5mA. If tie a resistor between FB and Vref, that resistor typical value is about 2k ohm.

- Duty cycle (D) and turns ratio (N) to balance MOSFET voltage ratings
 - $N \uparrow \rightarrow D \uparrow \rightarrow$ **more stress on main FET (primary)**
 - $N \downarrow \rightarrow D \downarrow \rightarrow$ **more stress on catch FET (secondary)**
 - (a) forward FET $V_{ds} = (V_{in}/N) \times D/(1-D) + V_o$;
 - (b) catch FET $V_{ds} = V_{in}/N$;
 - (c) primary main FET $V_{ds} = V_{in} \times 1/(1-D)$;
 - (d) clamp FET $V_{ds} = V_{in} \times 1/(1-D) - V_{in} = V_{in} \times D/(1-D)$

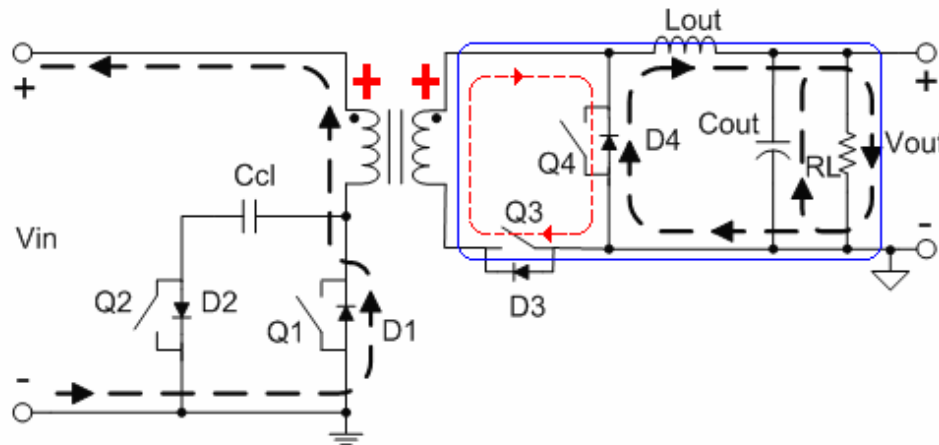
 
How to achieve primary main switch ZVS / VVS



- If the secondary side leakage is small the magnetizing energy necessary to turn D1 on will be diverted through D3 (Q3) during the reverse recovery of D4 (or Q4 reverse conduction)
- After the reverse recovery of D4, the magnetizing energy will continue discharging through the loop shown in blue
- Since there is no energy to turn D1 ON, ZVS of Q1 does not take place.

Principle of ZVS/VVS turning on


Behind Your Designs

 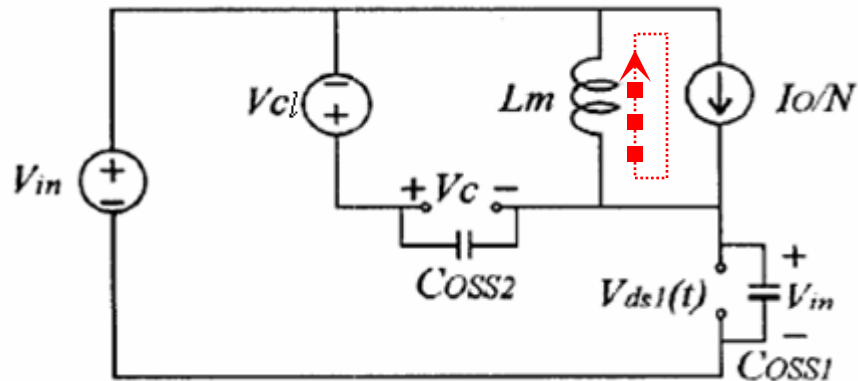


Vds reversed and clamped by the body diode.

$$I_M^+ = \frac{NV_o}{2L_m f_s}$$

 
$$\sqrt{\frac{L_m}{C_s}} \left(\frac{NV_o}{2L_m f_s} \cos \frac{1}{\sqrt{L_m C_{cl}}} t_{off} - \frac{I_o}{N} \right) \geq V_{in} + V_{cl}$$



(b) Theoretical waveforms

 

 - LC resonance as its nature can recycle the energy back to the source.
- MOSFET turn-on at reduced voltages will make less power losses.
- Efficiency is then improved.




UCC2891/2/3/4/7 achieves ZVS / VVS

Two resonance present:

- Magnetizing inductance and clamp capacitor
- Magnetizing inductance and equivalent Cds

$$\omega_{CL} = \frac{1}{\sqrt{L_M \times C_{CL}}}$$


 
$$\omega_R = \frac{1}{\sqrt{L_M \times C_{DS}}}$$




$$\sqrt{\frac{L_M}{C_{DS}}} \left(\frac{N \times (V_O + V_{O,misc})}{2 \times L_M \times f_{sw}} \left| \cos\left(\frac{1}{\sqrt{L_M \times C_{CL}}} \times t_{off}\right) \right| - \frac{I_O}{N} \right) \geq V_{in} + V_{CL}$$

Review of Active Clamp Reset Technique

Vds reversed, body diode clamped

 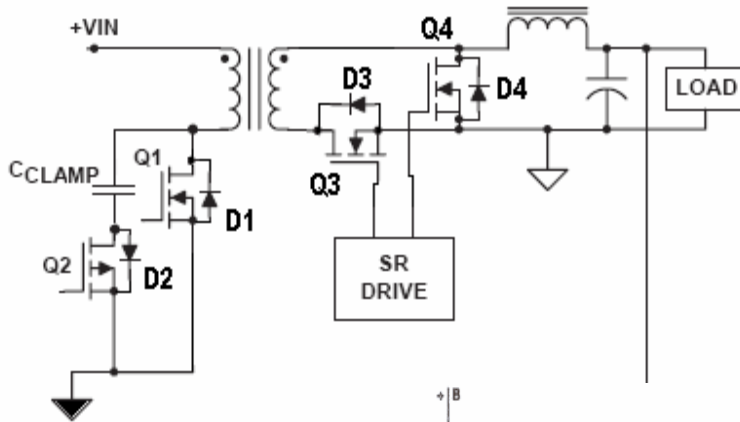

- Voltage Clamp
- Transformer reset

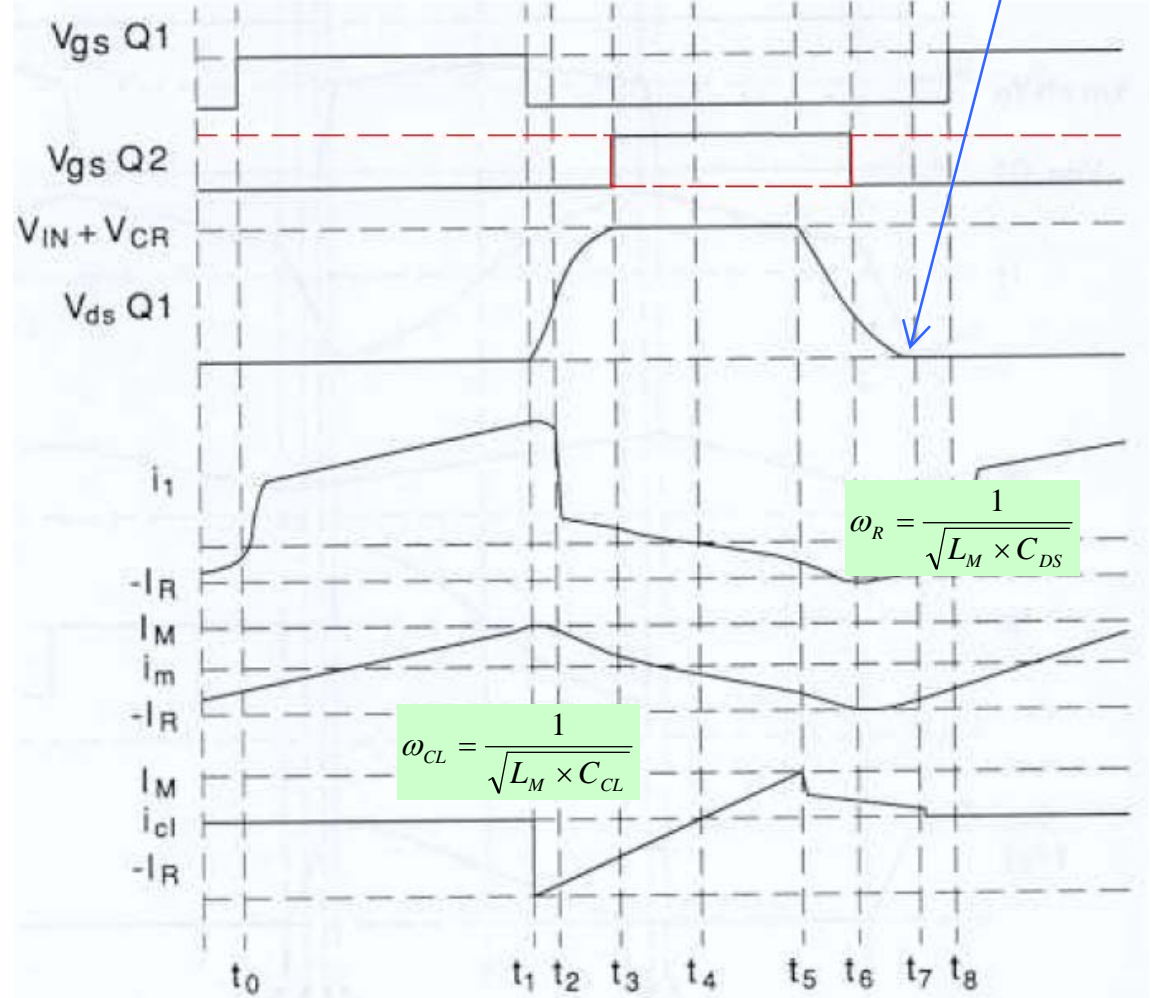

How to get ZVS?


- **Magnetizing current direction reversed before clamp FET turns off**
- **Magnetic field energy (current) sufficient:**
 - lower the magnetizing inductance
- **Primary side:**
 - a higher primary leakage or an external saturable inductor (MagAmp)
- **Secondary side:**
 - an external saturable inductor (MagAmp) to block magnetizing current discharging from the secondary loop for a short time.

Switching Power Loss due to Cds Energy Discharged at Turn-on with respect to the Vds

The efficiency drops when turn on at different Vds from a 300W converter at 20% load level:

- Turn on at Vds = 350V, -2.64%
- Turn on at Vds = 150V, -0.71%

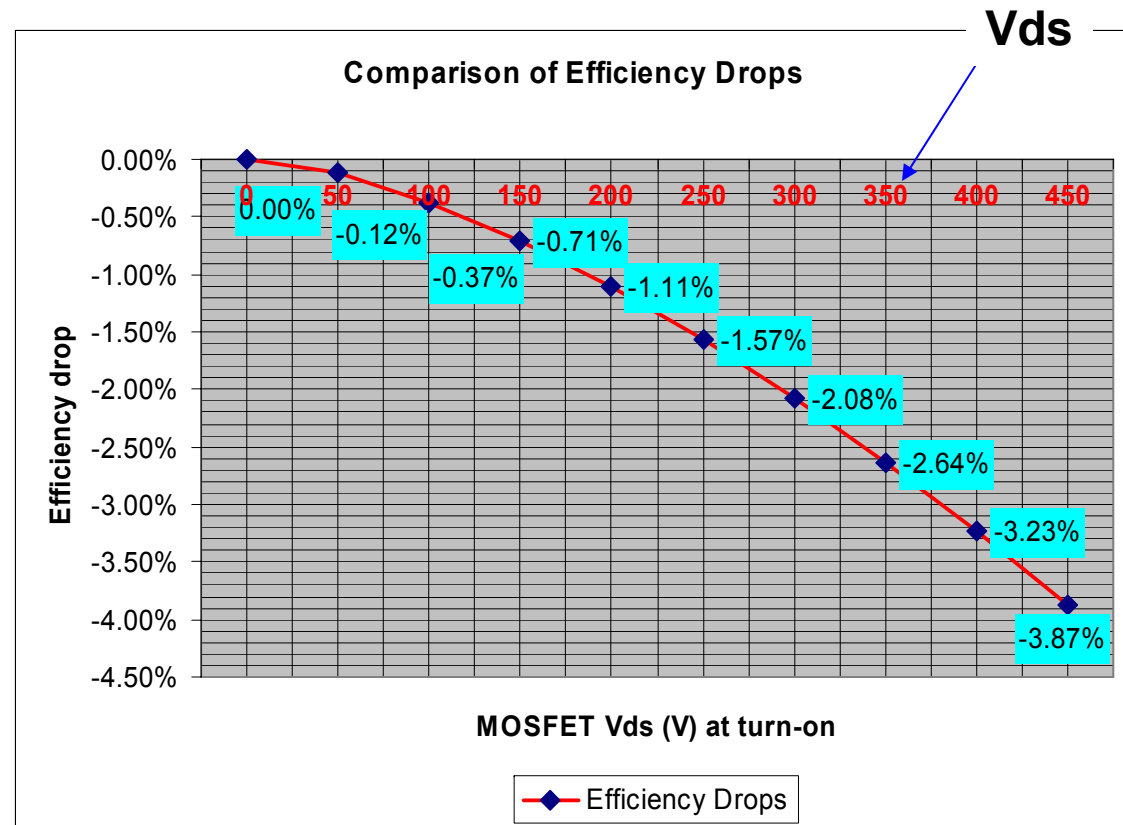In lower voltage applications, efficiency improvement may not be significant.



- Efficiency drop vs Vds variation.


$f_{sw} = 200\text{kHz}$ and $C_{ds} = 500\text{pF}$ @ $V_{ds} = 25\text{V}$.

ZVS / VVS Observation Using UCC2984


ZVS/VVS can be achieved by properly and adequately lowering the magnetizing inductance L_m to improve the efficiency in off-line applications.

$V_{in} = 390V$, $V_o = 12V$, $L_m = 0.65\text{ mH}$

ZVS achieved at $I_o = 1.5A$

 


VVS achieved at $I_o = 26A$

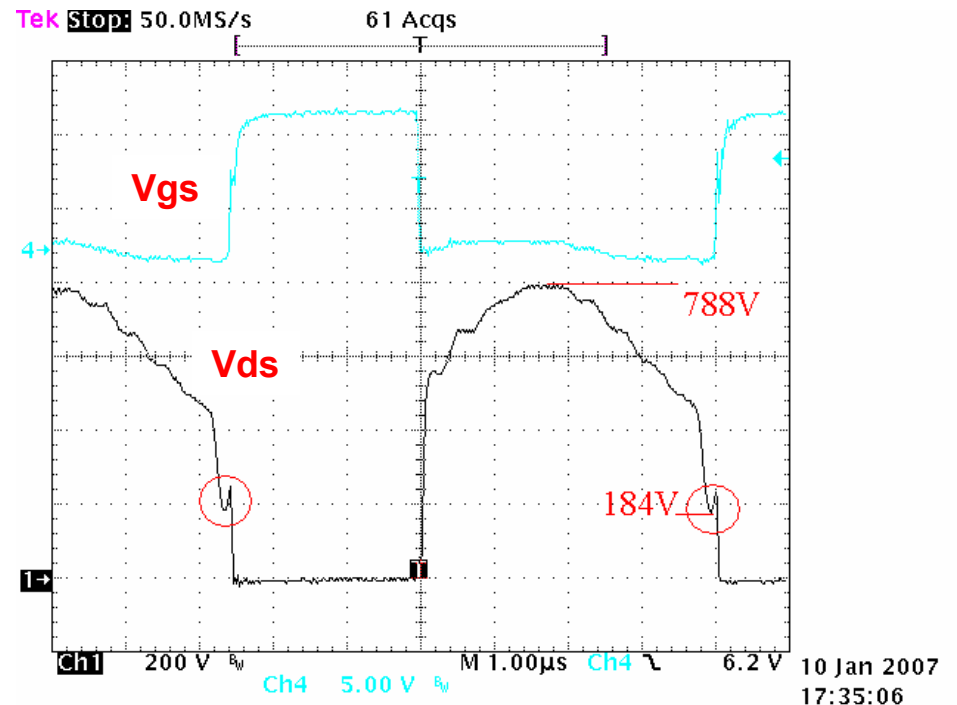

UCC2984 EVM Efficiency Test Results and Comparison

Efficiency results from different design of magnetizing inductance:

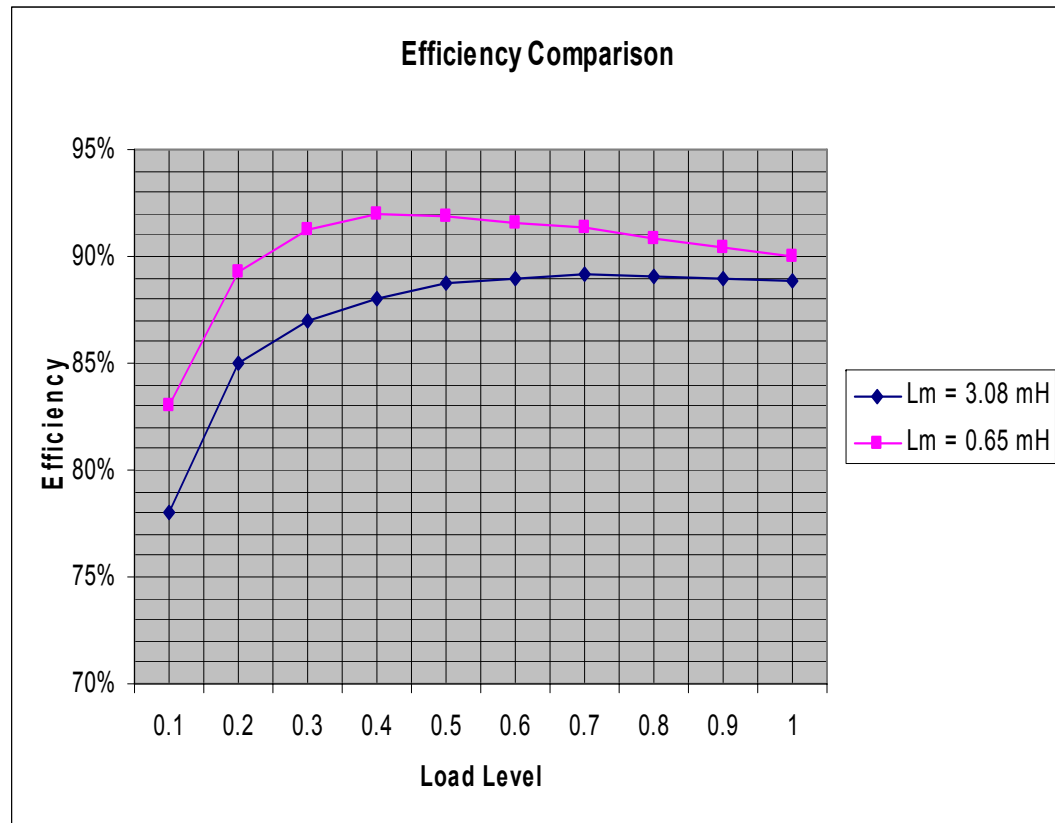- $L_m = 3.08\text{mH}$, valley voltage about 350V
- $L_m = 0.65\text{mH}$, valley voltage about 180V
- test conditions:
 - $f_{sw} = 160\text{kHz}$
 - $V_{in} = 390\text{V}$
 - $V_o = 12\text{V}$
 - Full load = 320W




Load Level = 1 representing full load 320W

ZVS observations on ACFC (UCC2891/7 EVM)

Behind Your Designs


$L_m = 95 \mu\text{H}$

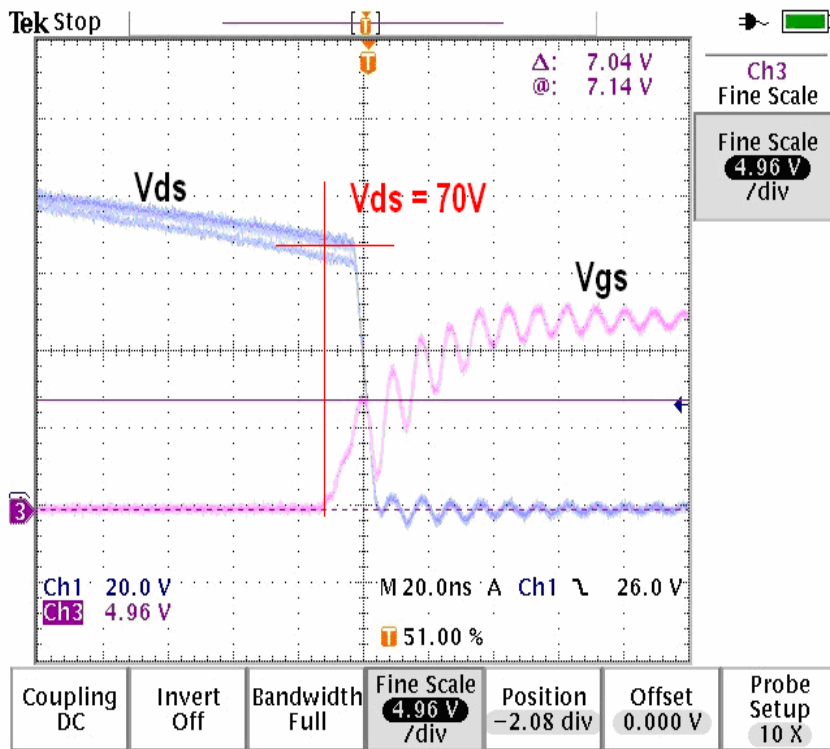$V_{in} = 42\text{V}, V_o = 3.3\text{V}, I_o = 0\text{A}$




$L_m = 25 \mu\text{H}$

 $V_{in} = 40\text{V}, V_o = 3.3\text{V}, I_o = 0\text{A}$




$L_m = 95 \mu\text{H}$

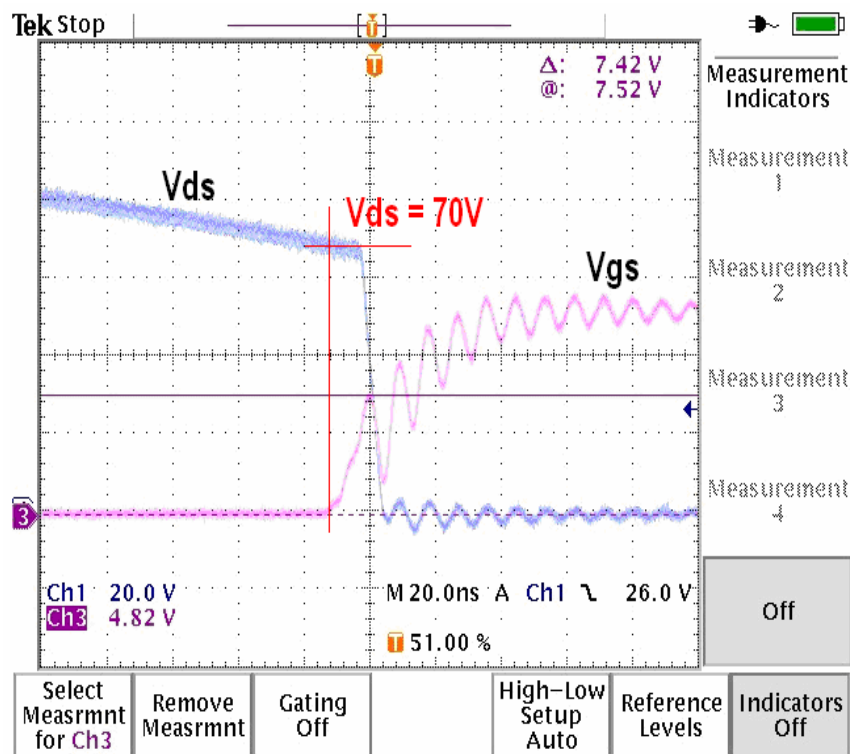$V_{in} = 42\text{V}$, $V_o = 3.3\text{V}$, $I_o = 15\text{A}$




$L_m = 25 \mu\text{H}$

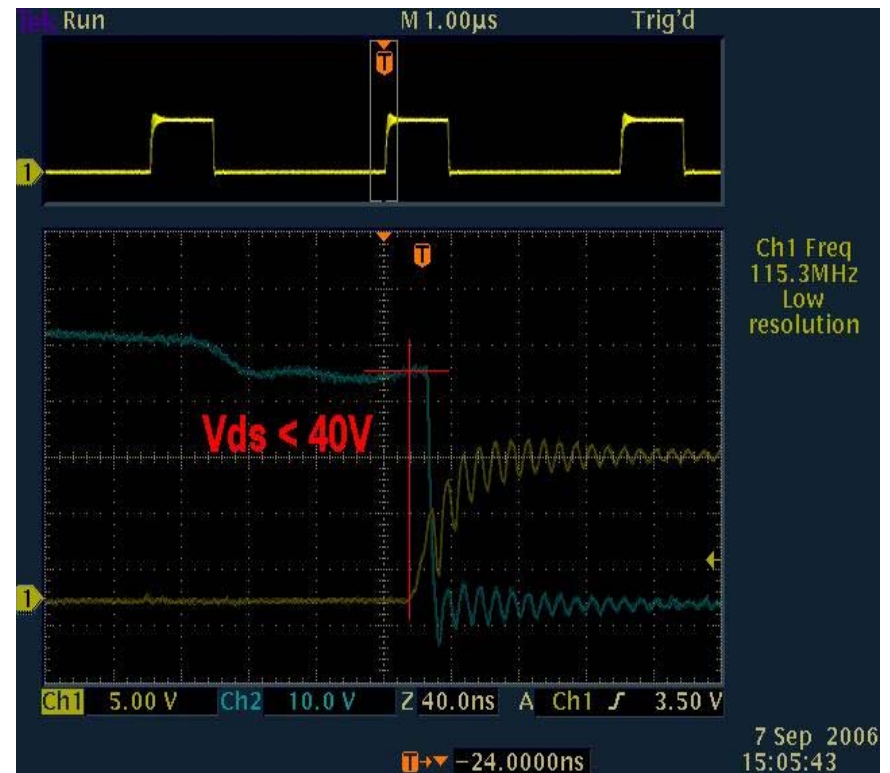$V_{in} = 40\text{V}$, $V_o = 3.3\text{V}$, $I_o = 10\text{A}$



- **Power shutdown oscillation**
 - * cause: self-driven SR feedback the capacitor stored energy to the primary
 - * solutions:
 - soft stop to control secondary capacitor discharge – most effective way
 - using control-driven SR
 - rating the avalanche energy high enough ($\frac{1}{2}C_oV_o^2$), or the voltage rating high enough
- **Oscillation from fast load step down change**
 - * cause:
 - control lost after duty cycle reached zero from the load step down change
 - self-driven SR feedback the capacitor stored energy to the primary
 - * solutions:
 - slower loop response design;
 - higher Dmax design
- **Reversing current at light load and no load**
 - * cause: self-driven SR catch FET conducting
 - * Solutions:
 - Using control-driven SR
 - Turning off SR

- Observations

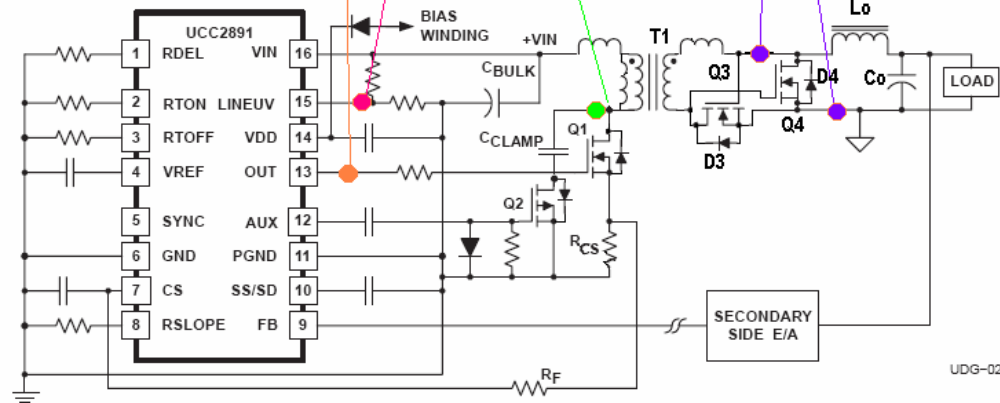

Mechanism of the Oscillation during Power Shutdown

Behind Your Designs

- Oscillation from secondary energy feedback to the primary from self-driven SR during power shutdown

LineUV (power shutdown) →

T1 a(+) and c(+) →

Q4 on and reverse L_o current →



T1 b(+) and d(+) →



Q3 on (energy transfer to primary) →

Magnetizing current reduction →

T1 a(+) and c(+) → Loop...

 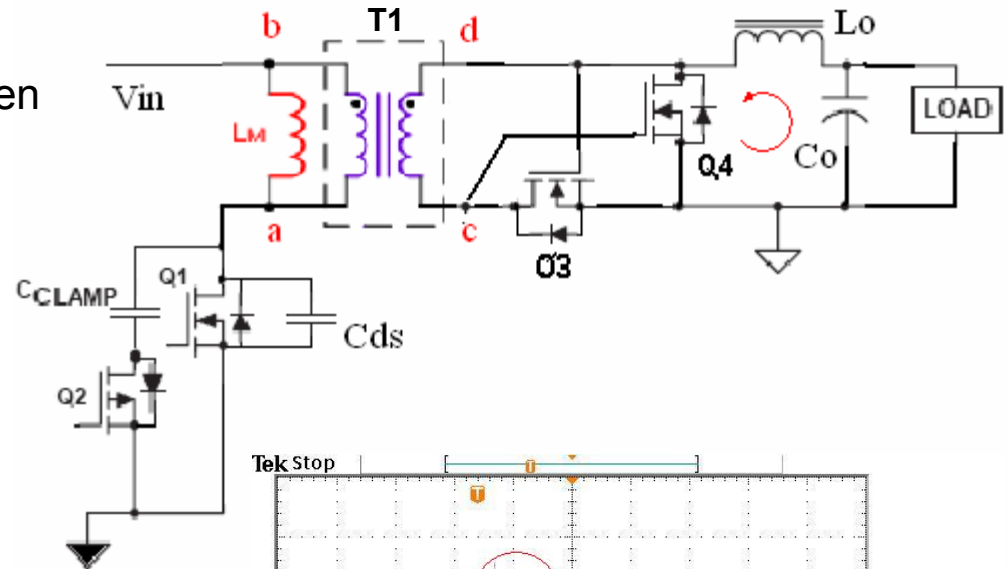With soft stop, both Q1 and Q2 are controlled during power down. The secondary stored energy will be discharged in control manner. The oscillation then will be eliminated, refer to the 2nd slide.



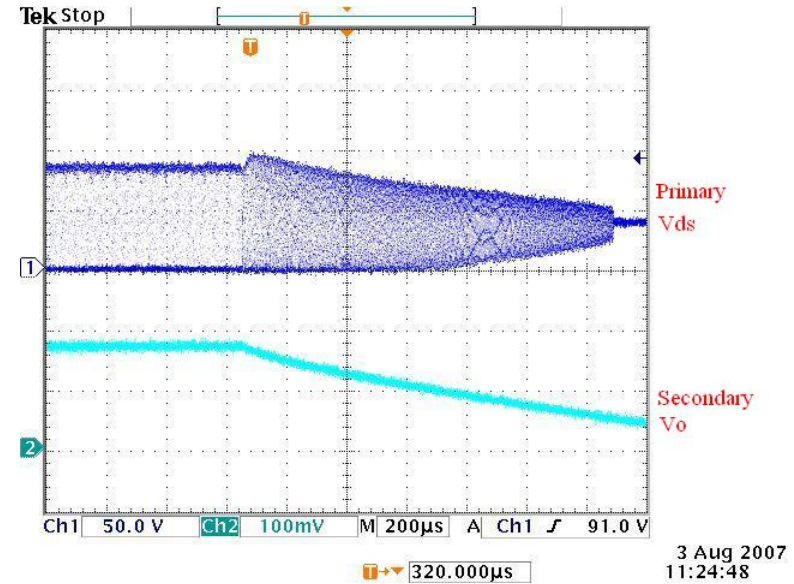
 


- Oscillation appears during power shutdown without soft stop
- Oscillation does not appear during power shutdown with soft stop
 - using SS/SD pin and a comparator
 - feature to be added

Load Transient Ringing



Behind Your Designs

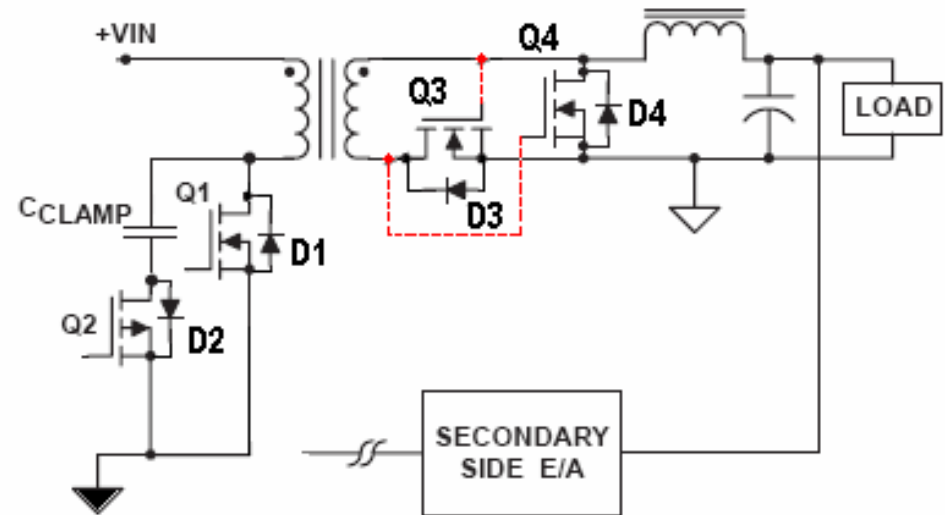 - Load step down change (30A to 3A) at 72Vin, 3.3Vo:
High voltage swing across Q1 drain and source




- Mechanism
 - control lost after duty cycle reached zero from load step down change
 - secondary self-driven SR oscillation
- Fast loop compensation, or
- High maximum duty cycle setup

  - With slower loop compensation or reduced maximum duty cycle
 - Vds swing peak reduced
 - Vo load transient response becomes slower







TPS28225 used for the control drive

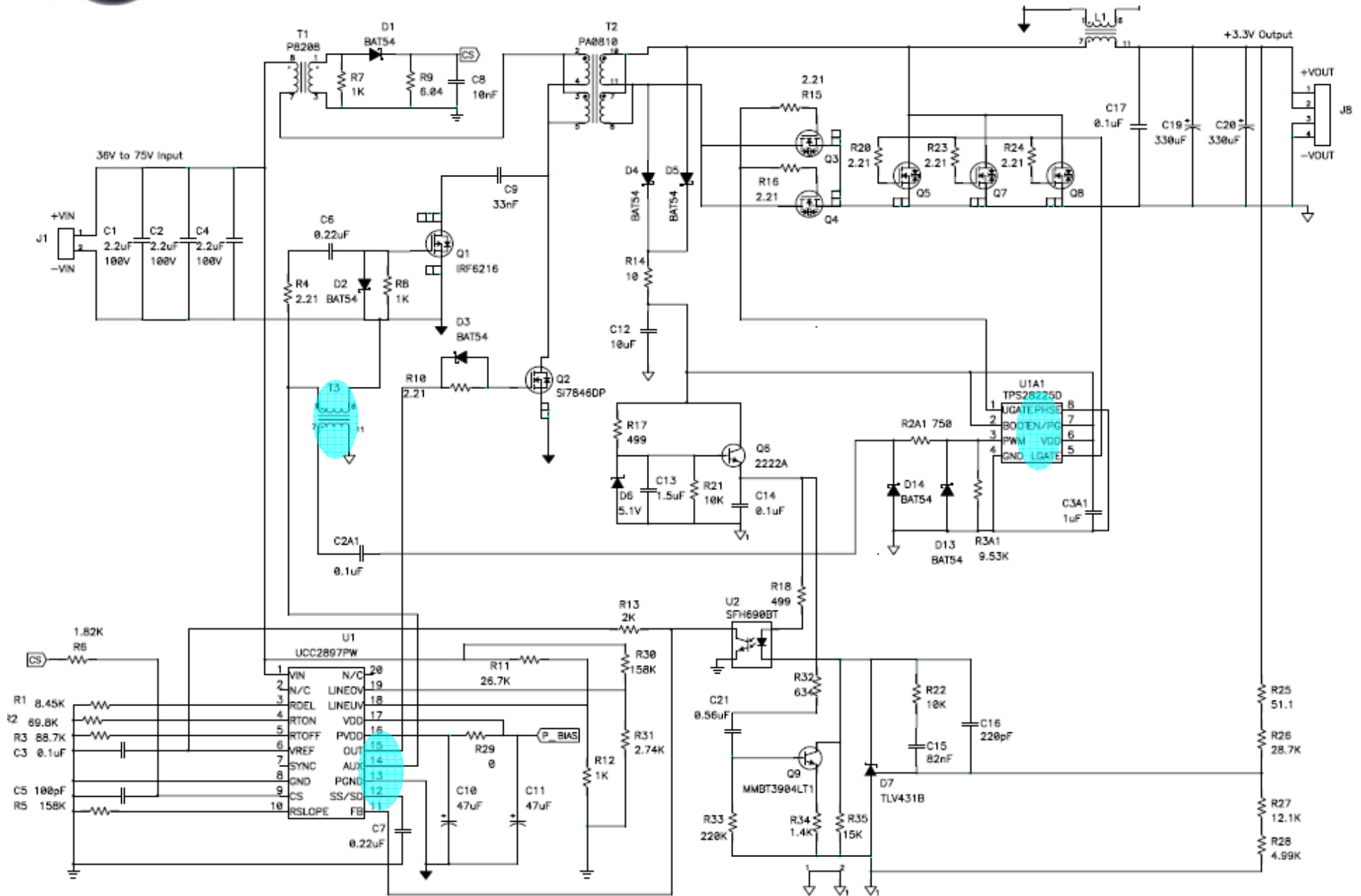

  
- Jitter: 120 ns ($V_{DD} \geq 9.2V$)
- Jitter 12 ns ($V_{DD} < 9.2V$)




External Solution: set up VDD between 8.5V and 9.2V

Gate Signal Jitter (root cause) – fixed and tested

Persistence = 13.2ns (rising edge)

 

Persistence = 10.2ns (falling edge)

 



New Silicon (UCC2897)

Behind Your Designs

- Fix gate signal jitter
- Keep LineUV as before (latch off)
- Add soft stop feature

Volt x second clamp: external solution

Off-time and On-time

- inversely proportional to I_{ch1} and I_{ch2} , respectively

$$I_{ch1} = I_2 - I_1$$


$$= \frac{2.5V}{R_{OFF1}} - \frac{V_{in} - 2.5V}{R_{OFF2}}$$

$V_{in} \uparrow \rightarrow I_{ch1} \downarrow \rightarrow t_{off} \uparrow$

$$I_{ch2} = I_3 + I_4$$

$$= \frac{2.5V}{R_{ON1}} + \left(\frac{R_{ON3} \times V_{IN}}{R_{ON3} + R_{ON4}} - V_{BE} \right) \times \frac{1}{R_{ON2}}$$

 $V_{in} \uparrow \rightarrow I_{ch2} \uparrow \rightarrow t_{on} \downarrow$



Volt x second clamp: external solution

Behind Your Designs

Off-time and On-time

- inversely proportional to I_{ch1} and I_{ch2} , respectively

$$I_{ch1} = I_2 - I_1$$


$$= \frac{2.5V}{R_{OFF1}} - \frac{V_{in} - 2.5V}{R_{OFF2}}$$

$V_{in} \uparrow \rightarrow I_{ch1} \downarrow \rightarrow t_{off} \uparrow$

$$I_{ch2} = I_3 + I_4$$



$$= \frac{2.5V}{R_{ON1}} + \left(\frac{R_{ON3} \times V_{IN}}{R_{ON3} + R_{ON4}} \right) \times \frac{1}{R_{ON2}}$$

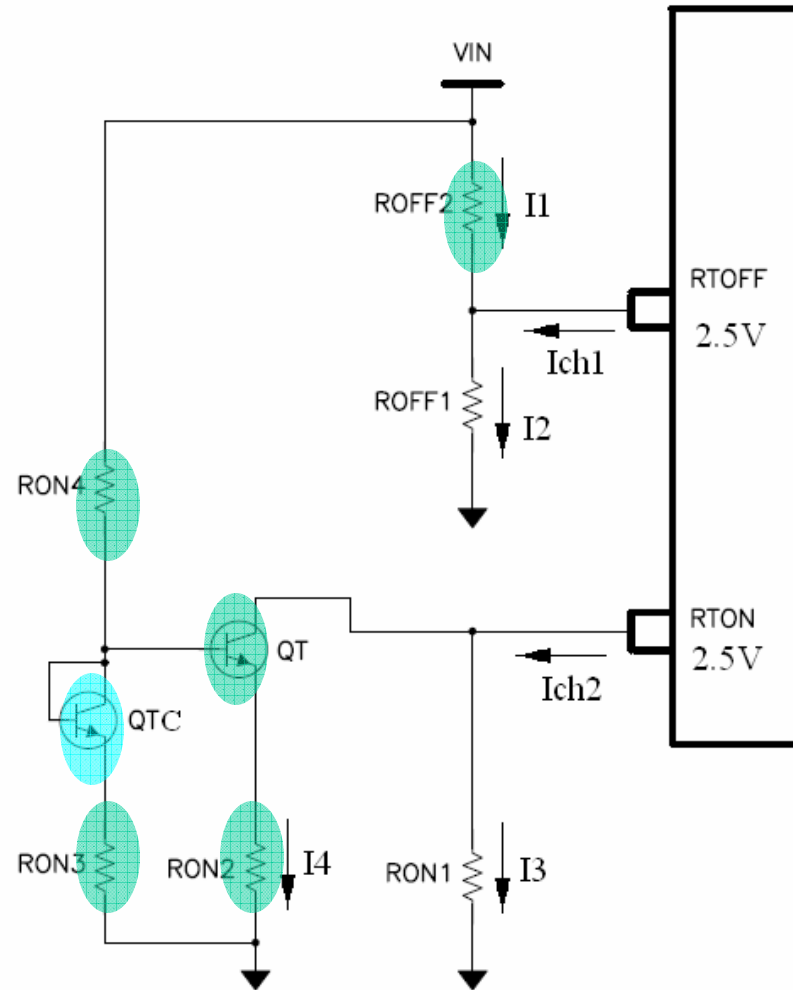$V_{in} \uparrow \rightarrow I_{ch2} \uparrow \rightarrow t_{on} \downarrow$




Vref-pin Glitch 1V During Power Up

 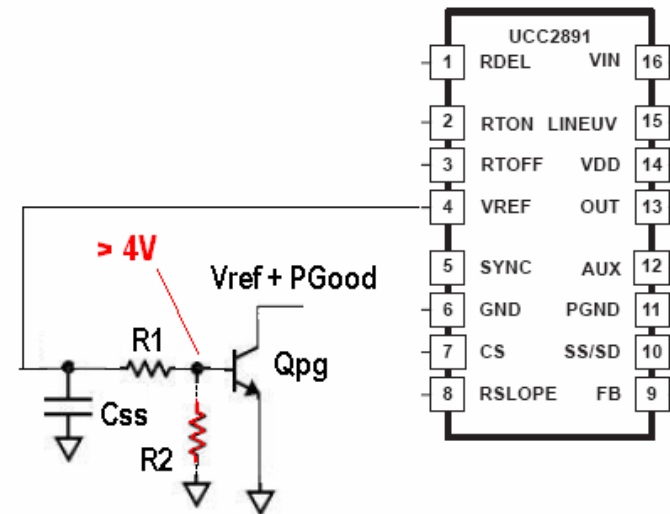
- Vref has a 1-Volt spike when VDD arises about 4V during start
- When using Vref+PGood for power good signal, this may cause false Power-Good signal without R2.
- By adding R2, the 1-V spike influence on the transistor can be eliminated.



 Comparison between Active Clamp Forward and HB in telecom applications



Low-side Active Clamp Forward Converter

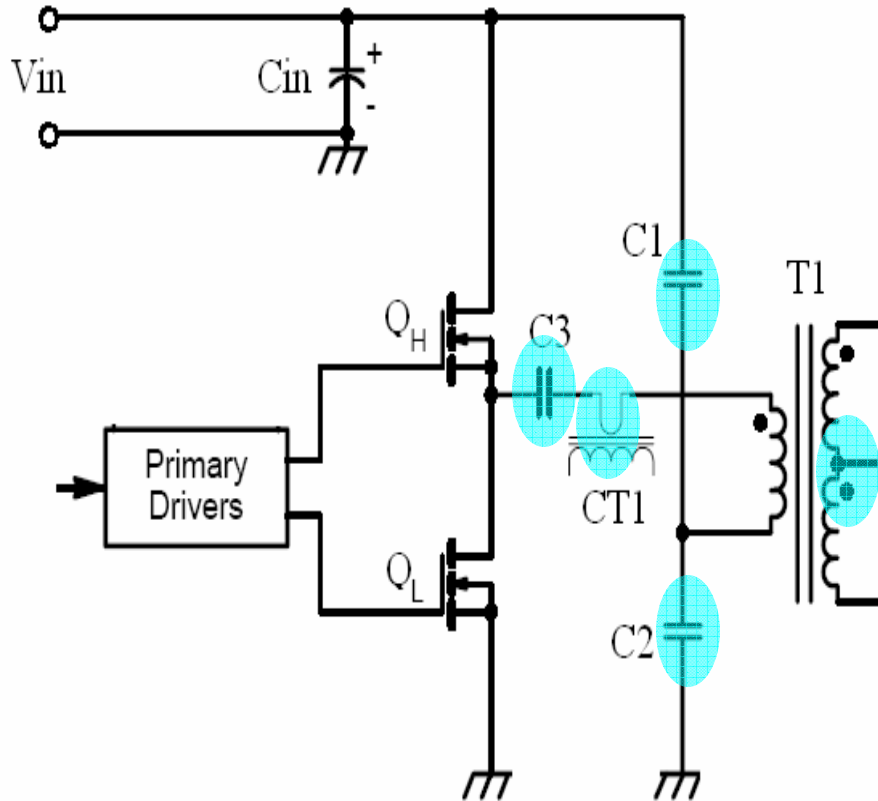

Symmetrical HB Converter

- **Efficiency**
 - Symmetrical HB may not provide ZVS
 - ACFC ZVS/MVS
 - Critical with higher switching frequency and power density in 1/4 or 1/8 bricks
- **Switching frequency:**
 - HB doubled FET's frequency seen at input and output – may help to reduce the caps but the switching losses proportional to $0.5 \times V_{in}$ hard switching
 - ACFC: MOSFET freq seen at input/output. VV Switching losses – partially soft
- **Components and board space**
 - HB: (a) High side gate driver, (b) flux imbalance caps, (c) caps for center tap point, (d) same size of high- and low side MOSFETs
 - ACFC: (a) - (b) no, (c) clamp cap, (d) clamp FET smaller one, (e) x2 voltage rating
- **Cost**
 - HB: cost for (a) – (c)
 - ACFC: cost for (c) - (e)
- **Secondary Sync Rectifier (control-driven SR)**

Comparison between Active Clamp Forward and HB in telecom applications

- **Current sensing:**
 - HB: current sensing transformer or floating sensing resistor (OpAmp may need)
 - ACFC: CT or resistor – flexibility, cost and board space
- **Transformer:**
 - HB: two windings at secondary – PCB design complication, center-tap, more space
 - ACFC: single winding at secondary
 - Critical with higher switching frequency and power density in 1/4 or 1/8 bricks
- **Transient response:**
 - HB may be faster than ACFC (clamp cap)
- **Secondary Sync Rectifier**
 - HB: not able to make self-driven (extra winding may need)
 - ACFC: self-driven ok (control-driven available with TPS28225 or similar)
- **Summary:**
 - (a) Similar total cost with ACFC slightly lower
 - (b) ACFC slightly less component count
 - (c) ACFC higher efficiency and less board space – higher power density possible for the same cost and board space

THANK YOU!

Contact Info:
Hong Huang
+(603)-222-8533
hong_huang@ti.com