

SWITCHMODE POWER SUPPLY HANDBOOK

KEITH
BILLINGS



Other McGraw-Hill Reference Books of Interest

Handbooks

Avalone and Baumeister • STANDARD HANDBOOK FOR MECHANICAL ENGINEERS
Beeman • INDUSTRIAL POWER SYSTEMS HANDBOOK
Coombs • BASIC ELECTRONIC INSTRUMENT HANDBOOK
Coombs • PRINTED CIRCUITS HANDBOOK
Croft and Summers • AMERICAN ELECTRICIANS' HANDBOOK
Di Giacomo • VLSI HANDBOOK
Fink and Beaty • STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS
Fink and Christiansen • ELECTRONICS ENGINEERS' HANDBOOK
Harper • HANDBOOK OF ELECTRONIC SYSTEMS DESIGN
Harper • HANDBOOK OF THICK FILM HYBRID MICROELECTRONICS
Harper • HANDBOOK OF WIRING, CABLING, AND INTERCONNECTING FOR ELECTRONICS
Hicks • STANDARD HANDBOOK OF ENGINEERING CALCULATIONS
Inglis • ELECTRONIC COMMUNICATIONS HANDBOOK
Johnson and Jasik • ANTENNA ENGINEERING HANDBOOK
Juran • QUALITY CONTROL HANDBOOK
Kaufman and Seidman • HANDBOOK FOR ELECTRONICS ENGINEERING TECHNICIANS
Kaufman and Seidman • HANDBOOK OF ELECTRONICS CALCULATIONS
Kurtz • HANDBOOK OF ENGINEERING ECONOMICS
Perry • ENGINEERING MANUAL
Stout • HANDBOOK OF MICROPROCESSOR DESIGN AND APPLICATIONS
Stout and Kaufman • HANDBOOK OF MICROCIRCUIT DESIGN AND APPLICATION
Stout and Kaufman • HANDBOOK OF OPERATIONAL AMPLIFIER DESIGN
Tuma • ENGINEERING MATHEMATICS HANDBOOK
Williams • DESIGNER'S HANDBOOK OF INTEGRATED CIRCUITS
Williams and Taylor • ELECTRONIC FILTER DESIGN HANDBOOK

Power Electronics Books

Antognetti • POWER INTEGRATED CIRCUITS
Chryssis • HIGH-FREQUENCY SWITCHING POWER SUPPLIES
Flanagan • HANDBOOK OF TRANSFORMER APPLICATIONS
Grossner • TRANSFORMERS IN ELECTRONIC CIRCUITS
Mitchell • DC/DC SWITCHING REGULATOR ANALYSIS
Rombaut • POWER ELECTRONIC CONVERTERS: AC/AC
Seguier • POWER ELECTRONIC CONVERTERS: AC/DC CONVERSIONS

Encyclopedias

CONCISE ENCYCLOPEDIA OF SCIENCE AND TECHNOLOGY
ENCYCLOPEDIA OF ELECTRONICS AND COMPUTERS
ENCYCLOPEDIA OF ENGINEERING

Dictionaries

DICTIONARY OF COMPUTERS
DICTIONARY OF ELECTRICAL AND ELECTRONIC ENGINEERING
DICTIONARY OF ENGINEERING
DICTIONARY OF SCIENTIFIC AND TECHNICAL TERMS
Markus • ELECTRONICS DICTIONARY

For more information about other McGraw-Hill materials,
call 1-800-2-MCGRAW in the United States. In other
countries, call your nearest McGraw-Hill office.

SWITCHMODE POWER SUPPLY HANDBOOK

Keith H. Billings, C.Eng., M.I.E.E.

*Vice President, Engineering
Hammond Manufacturing Company, Ltd.*

McGraw-Hill, Inc.

New York St. Louis San Francisco Auckland Bogotá
Caracas Lisbon London Madrid Mexico City Milan
Montreal New Delhi San Juan Singapore
Sydney Tokyo Toronto

To Diana
For more than four years of
quiet encouragement

Library of Congress Cataloging-in-Publication Data

Billings, Keith H.

Switchmode power supply handbook / Keith H. Billings.

p. cm.

ISBN 0-07-005330-8

1. Electronic apparatus and appliances—Power supply—Handbooks.
manuals, etc. I. Title.

TK7881.15.B55 1989

621.381'044—dc19

88-32774
CIP

Copyright © 1989 by McGraw-Hill, Inc. All rights reserved.
Printed in the United States of America. Except as permitted
under the United States Copyright Act of 1976, no part of this
publication may be reproduced or distributed in any form or by
any means, or stored in a data base or retrieval system, without
the prior written permission of the publisher.

567890 WHT WHT 909876543

ISBN 0-07-005330-8

The editors for this book were Daniel A. Gonneau and Susan Thomas,
the designer was Naomi Auerbach, and the production
supervisor was Dianne L. Walber. It was set in Times Roman
by the McGraw-Hill Publishing Company, Professional and Reference
Division Composition Unit.

Information contained in this work has been obtained by McGraw-Hill, Inc., from sources believed to be reliable. However, neither McGraw-Hill nor its authors guarantees the accuracy or completeness of any information published herein and neither McGraw-Hill nor its authors shall be responsible for any errors, omissions, or damages arising out of use of this information. This work is published with the understanding that McGraw-Hill and its authors are supplying information but are not attempting to render engineering or other professional services. If such services are required, the assistance of an appropriate professional should be sought.

For more information about other McGraw-Hill materials,
call 1-800-2-MCGRAW in the United States. In other
countries, call your nearest McGraw-Hill office.

TAB BOOKS Inc. offers software for sale. For information and a catalog, please
contact TAB Software Department, Blue Ridge Summit, PA 17294-0850.

CONTENTS

Preface xvi

Acknowledgments xviii

Units, Symbols, Dimensions, and Abbreviations Used in this Book xix

PART 1 FUNCTIONS AND REQUIREMENTS COMMON TO MOST DIRECT-OFF-LINE SWITCHMODE POWER SUPPLIES

1. COMMON REQUIREMENTS: AN OVERVIEW 1.3

1.1 Introduction. 1.2 Input Transient Voltage Protection.
1.3 Electromagnetic Compatibility. 1.4 Differential-Mode Noise.
1.5 Common-Mode Noise. 1.6 Faraday Screens. 1.7 Input Fuse
Selection. 1.8 Line Rectification and Capacitor Input Filters.
1.9 Inrush Limiting. 1.10 Start-Up Methods. 1.11 Soft Start.
1.12 Start-Up Overvoltage Prevention. 1.13 Output Overvoltage
Protection. 1.14 Output Undervoltage Protection. 1.15 Overload
Protection (Input Power Limiting). 1.16 Output Current Limiting.
1.17 Base Drive Requirements for High-Voltage Bipolar Transistors.
1.18 Proportional Drive Circuits. 1.19 Antisaturation Techniques.
1.20 Snubber Networks. 1.21 Cross Conduction. 1.22 Output
Filtering, Common-Mode Noise, and Input-To-Output Isolation.
1.23 Power Failure and Power Good Signals. 1.24 Power Good
Signals. 1.25 Dual Input Voltage Operation. 1.26 Power Supply Hold-
up Time. 1.27 Synchronization. 1.28 External Inhibit. 1.29 Forced
Current Sharing. 1.30 Remote Sensing. 1.31 P-Terminal Link.
1.32 Low-Voltage Cutout. 1.33 Voltage and Current Limit
Adjustments. 1.34 Input Safety Requirements.

2. AC POWERLINE SURGE PROTECTION 1.17

2.1 Introduction. 2.2 Location Categories. 2.3 Likely Rate of Surge
Occurrences. 2.4 Surge Voltage Waveforms. 2.5 Transient
Suppression Devices. 2.6 Metal Oxide Varistors (MOVs, Voltage-
Dependent Resistors). 2.7 Transient Protection Diodes. 2.8 Gas-filled
Surge Arresters. 2.9 Line Filter, Transient Suppressor Combinations.
2.10 Category A Transient Suppression Filters. 2.11 Category B
Transient Suppression Filters. 2.12 A Case for Full Transient
Protection. 2.13 The Cause of "Ground Return Voltage Bump" Stress.
2.14 Problems.

3. ELECTROMAGNETIC INTERFERENCE (EMI) IN SWITCHMODE POWER SUPPLIES 1.31

3.1 Introduction. 3.2 EMI/RFI Propagation Modes. 3.3 Powerline
Conducted-Mode Interference. 3.4 Safety Regulations (Ground Return
Currents). 3.5 Powerline Filters. 3.6 Suppressing EMI at Source.

| | |
|---|-------------|
| 3.7 Example. 3.8 Line Impedance Stabilization Network, (LISN). 3.9 Line Filter Design. 3.10 Common-Mode Line-Filter Inductors. 3.11 Design Example For Common-Mode Line-Filter Inductors. 3.12 Series-Mode Inductors. 3.13 Problems. | |
| 4. FARADAY SCREENS | 1.43 |
| 4.1 Introduction. 4.2 Faraday Screens as Applied to Switching Devices. 4.3 Transformer Faraday Screens and Safety Screens. 4.4 Faraday Screens on Output Components. 4.5 Reducing Radiated EMI in Gapped Transformer Cores. 4.6 Problems. | |
| 5. FUSE SELECTION | 1.49 |
| 5.1 Introduction. 5.2 Fuse Parameters. 5.3 Types of Fuses. 5.4 Selecting Fuses. 5.5 SCR Crowbar Fuses. 5.6 Transformer Input Fuses. 5.7 Problems. | |
| 6. LINE RECTIFICATION AND CAPACITOR INPUT FILTERS FOR "DIRECT-OFF-LINE" SWITCHMODE POWER SUPPLIES | 1.54 |
| 6.1 Introduction. 6.2 Typical Dual-Voltage Capacitor Input Filter Circuits. 6.3 Effective Series Resistance R_s . 6.4 Constant-Power Load. 6.5 Constant-Current Load. 6.6 Rectifier and Capacitor Waveforms. 6.7 Input Current, Capacitor Ripple, and Peak Currents. 6.8 Effective Input Current I_e and Power Factor. 6.9 Selecting Inrush- Limiting Resistance. 6.10 Resistance Factor R_{sf} . 6.11 Design Example. 6.12 DC Output Voltage and Regulation for Rectifier Capacitor Input Filters. 6.13 Example of Rectifier Capacitor Input Filter DC Output Voltage Calculation. 6.14 Selecting Reservoir and/or Filter Capacitor Size. 6.15 Selecting Input Fuse Ratings. 6.16 Power Factor and Efficiency Measurements. 6.17 Problems. | |
| 7. INRUSH CONTROL | 1.73 |
| 7.1 Introduction. 7.2 Series Resistors. 7.3 Thermistor Inrush Limiting. 7.4 Active Limiting Circuits (Triac Start Circuit). 7.5 Problems. | |
| 8. START-UP METHODS | 1.76 |
| 8.1 Introduction. 8.2 Dissipative (Passive) Start Circuit. 8.3 Transistor (Active) Start Circuits. 8.4 Impulse Start Circuits. | |
| 9. SOFT START AND LOW-VOLTAGE INHIBIT | 1.80 |
| 9.1 Introduction. 9.2 Soft-Start Circuit. 9.3 Low-Voltage Inhibit. 9.4 Problems. | |
| 10. TURN-ON VOLTAGE OVERSHOOT PREVENTION | 1.85 |
| 10.1 Introduction. 10.2 Typical Causes of Turn-on Voltage Overshoot in Switchmode Supplies. 10.3 Overshoot Prevention. 10.4 Problems. | |

| | |
|--|--------------|
| 11. OVERVOLTAGE PROTECTION | 1.89 |
| 11.1 Introduction. 11.2 Types of Overvoltage Protection. 11.3 Type 1, SCR "Crowbar" Overvoltage Protection. 11.4 "Crowbar" Performance. 11.5 Limitations of "Simple" Crowbar Circuits. 11.6 Type 2, Overvoltage Clamping Techniques. 11.7 Overvoltage Clamping With SCR "Crowbar" Backup. 11.8 Selecting Fuses for SCR "Crowbar" Overvoltage Protection Circuits. 11.9 Type 3, Overvoltage Protection by Voltage Limiting Techniques. 11.10 Problems. | |
| 12. UNDERVOLTAGE PROTECTION | 1.101 |
| 12.1 Introduction. 12.2 Undervoltage Suppressor Performance Parameters. 12.3 Basic Principles. 12.4 Practical Circuit Description. 12.5 Operating Principles (Practical Circuit). 12.6 Transient Behavior. 12.7 Problems. | |
| 13. OVERLOAD PROTECTION | 1.107 |
| 13.1 Introduction. 13.2 Types of Overload Protection. 13.3 Type 1, Overpower Limiting. 13.4 Type 1, Form A, Primary Overpower Limiting. 13.5 Type 1, Form B, Delayed Overpower Shutdown Protection. 13.6 Type 1, Form C, Pulse-by-Pulse Overpower/Current Limiting. 13.7 Type 1, Form D, Constant Power Limiting. 13.8 Type 1, Form E, Foldback (Reentrant) Overpower Limiting. 13.9 Type 2, Output Constant Current Limiting. 13.10 Type 3, Overload Protection by Fuses, Current Limiting, or Trip Devices. 13.11 Problems. | |
| 14. FOLDBACK (REENTRANT) OUTPUT CURRENT LIMITING | 1.113 |
| 14.1 Introduction. 14.2 Foldback Principle. 14.3 Foldback Circuit Principles as Applied to a Linear Supply. 14.4 "Lockout" in Foldback Current-Limited Supplies. 14.5 Reentrant Lockout with Cross- Connected Loads. 14.6 Reentrant Current Limits in Switchmode Supplies. 14.7 Problems. | |
| 15. BASE DRIVE REQUIREMENTS FOR HIGH-VOLTAGE BIPOLAR TRANSISTORS | 1.121 |
| 15.1 Introduction. 15.2 Secondary Breakdown. 15.3 Incorrect Turn- Off Drive Waveforms. 15.4 Correct Turn-Off Waveform. 15.5 Correct Turn-On Waveform. 15.6 Antisaturation Drive Techniques. 15.7 Optimum Drive Circuit for High-Voltage Transistors. 15.8 Problems. | |
| 16. PROPORTIONAL DRIVE CIRCUITS FOR BIPOLAR TRANSISTORS | 1.126 |
| 16.1 Introduction. 16.2 Example of a Proportional Drive Circuit. 16.3 Turn-On Action. 16.4 Turn-Off Action. 16.5 Drive Transformer Restoration. 16.6 Wide-Range Proportional Drive Circuits. 16.7 Turn-Off Action. 16.8 Turn-On Action. 16.9 Proportional Drive with High-Voltage Transistors. 16.10 Problems. | |
| 17. ANTISATURATION TECHNIQUES FOR HIGH-VOLTAGE TRANSISTORS | 1.132 |
| 17.1 Introduction. 17.2 Baker Clamp. 17.3 Problems. | |

| | |
|--|--------------|
| 18. SNUBBER NETWORKS | 1.134 |
| <i>18.1 Introduction. 18.2 Snubber Circuit (with Load Line Shaping). 18.3 Operating Principles. 18.4 Establishing Snubber Component Values by Empirical Methods. 18.5 Establishing Snubber Component Values by Calculation. 18.6 Turn-Off Dissipation in Transistor. 18.7 Snubber Resistor Values. 18.8 Dissipation in Snubber Resistor. 18.9 Miller Current Effects. 18.10 The Weaving Low-Loss Snubber Diode. 18.11 "Ideal" Drive Circuits for High-Voltage Bipolar Transistors. 18.12 Problems.</i> | |
| 19. CROSS CONDUCTION | 1.144 |
| <i>19.1 Introduction. 19.2 Preventing Cross Conduction. 19.3 Cross-Coupled Inhibit. 19.4 Circuit Operation. 19.5 Problems.</i> | |
| 20. OUTPUT FILTERS | 1.149 |
| <i>20.1 Introduction. 20.2 Basic Requirements. 20.3 Parasitic Effects in Switchmode Output Filters. 20.4 Two-Stage Filters. 20.5 High-Frequency Choke Example. 20.6 Resonant Filters. 20.7 Resonant Filter Example. 20.8 Common-Mode Noise Filters. 20.9 Selecting Component Values for Output Filters. 20.10 Main Output Inductor Values (Buck Regulators). 20.11 Design Example. 20.12 Output Capacitor Value. 20.13 Problems.</i> | |
| 21. POWER FAILURE WARNING CIRCUITS | 1.161 |
| <i>21.1 Introduction. 21.2 Power Failure and Brownout. 21.3 Simple Power Failure Warning Circuits. 21.4 Dynamic Power Failure Warning Circuit. 21.5 Independent Power Failure Warning Module. 21.6 Power Failure Warning in Flyback Converters. 21.7 Fast Power Failure Warning Circuit. 21.8 Problems.</i> | |
| 22. CENTERING (ADJUSTMENT TO CENTER) OF AUXILIARY OUTPUT VOLTAGES ON MULTIPLE-OUTPUT CONVERTERS | 1.170 |
| <i>22.1 Introduction. 22.2 Example. 22.3 Saturable Reactor Voltage Adjustment. 22.4 Reactor Design. 22.5 Problems.</i> | |
| 23. AUXILIARY SUPPLY SYSTEMS | 1.174 |
| <i>23.1 Introduction. 23.2 60-Hz Line Transformers. 23.3 Auxiliary Converters. 23.4 Operating Principles. 23.5 Stabilized Auxiliary Converters. 23.6 High-Efficiency Auxiliary Supplies. 23.7 Auxiliary Supplies Derived from Main Converter Transformer. 23.8 Problems</i> | |
| 24. PARALLEL OPERATION OF VOLTAGE: STABILIZED POWER SUPPLIES | 1.179 |
| <i>24.1 Introduction. 24.2 Master-Slave Operation. 24.3 Voltage-Controlled Current Sources. 24.4 Forced Current Sharing. 24.5 Parallel Redundant Operation. 24.6 Problems.</i> | |

PART 2 DESIGN: THEORY AND PRACTICE

| | |
|--|-------------|
| 1. MULTIPLE-OUTPUT FLYBACK SWITCHMODE POWER SUPPLIES | 2.3 |
| <i>1.1 Introduction. 1.2 Expected Performance. 1.2.1 Output Ripple and Noise. 1.2.2 Synchronization. 1.3 Operating Modes. 1.3.1 Transfer Function. 1.3.2 Current-Mode Control. 1.4 Operating Principles. 1.5 Energy Storage Phase. 1.6 Energy Transfer Modes (Flyback Phase). 1.7 Factors Defining Operating Modes. 1.7.1 Complete Energy Transfer. 1.7.2 Incomplete Energy Transfer. 1.8 Transfer Function Anomaly. 1.9 Transformer Throughput Capability. 1.10 Specification Notes. 1.11 Specification Example for a 110-W Direct-Off-Line Flyback Power Supply. 1.11.1 Specification. 1.11.2 Power Circuit. 1.11.3 Transformer Design. 1.12 Problems.</i> | |
| 2. FLYBACK TRANSFORMER DESIGN | 2.16 |
| <i>2.1 Introduction. 2.2 Core Parameters for the Effect of an Air Gap. 2.3 General Design Considerations. 2.4 Design Example for a 110-W Flyback Transformer. 2.5 Flyback Transformer Saturation and Transient Effects. 2.6 Conclusions. 2.7 Problems.</i> | |
| 3. REDUCING TRANSISTOR SWITCHING STRESS | 2.32 |
| <i>3.1 Introduction. 3.2 Self-Tracking Voltage Clamp. 3.3 Flyback Converter "Snubber" Networks. 3.4 Problems.</i> | |
| 4. SELECTING POWER COMPONENTS FOR FLYBACK CONVERTERS | 2.37 |
| <i>4.1 Introduction. 4.2 Primary Components. 4.3 Secondary Power Components. 4.4 Output Capacitors. 4.5 Capacitor Life. 4.6 General Conclusions Concerning Flyback Converter Components. 4.7 Problems.</i> | |
| 5. THE DIAGONAL HALF-BRIDGE FLYBACK CONVERTER | 2.44 |
| <i>5.1 Introduction. 5.2 Operating Principle. 5.3 Useful Properties. 5.4 Transformer Design. 5.5 Drive Circuitry. 5.6 Operating Frequency. 5.7 Snubber Components. 5.8 Problems.</i> | |
| 6. SELF-OSCILLATING DIRECT-OFF-LINE FLYBACK CONVERTERS | 2.49 |
| <i>6.1 Introduction. 6.2 Classes of Operation. 6.3 General Operating Principles. 6.4 Isolated Self-Oscillating Flyback Converters. 6.5 Control Circuit (Brief Description). 6.6 Squagging. 6.7 Summary of the Major Parameters for Self-Oscillating Flyback Converters. 6.8 Problems.</i> | |
| 7. APPLYING CURRENT-MODE CONTROL TO FLYBACK CONVERTERS | 2.58 |
| <i>7.1 Introduction. 7.2 Power Limiting and Current-Mode Control as Applied to the Self-oscillating Flyback Converter. 7.3 Voltage Control Loop. 7.4 Input Ripple Rejection. 7.5 Using Field-Effect Transistors in Variable-Frequency Flyback Converters. 7.6 Problems.</i> | |

| | |
|---|--------------|
| 8. DIRECT-OFF-LINE SINGLE-ENDED FORWARD CONVERTERS | 2.63 |
| 8.1 Introduction. 8.2 Operating Principles. 8.3 Limiting Factors for the Value of the Output Choke. 8.4 Multiple Outputs. 8.5 Energy Recovery Winding (P2). 8.6 Advantages. 8.7 Disadvantages. 8.8 Problems. | |
| 9. TRANSFORMER DESIGN FOR FORWARD CONVERTERS | 2.70 |
| 9.1 Introduction. 9.2 Transformer Design Example. 9.3 Selecting Power Transistors. 9.4 Final Design Notes. 9.5 Transformer Saturation. 9.6 Conclusions. | |
| 10. DIAGONAL HALF-BRIDGE FORWARD CONVERTERS | 2.80 |
| 10.1 Introduction. 10.2 Operating Principle. | |
| 11. TRANSFORMER DESIGN FOR DIAGONAL HALF-BRIDGE FORWARD CONVERTERS | 2.84 |
| 11.1 General Considerations. 11.2 Design Notes. | |
| 12. HALF-BRIDGE PUSH-PULL DUTY-RATIO-CONTROLLED CONVERTERS | 2.90 |
| 12.1 Introduction. 12.2 Operating Principles. 12.3 System Advantages. 12.4 Problem Areas. 12.5 Current-Mode Control and Subharmonic Ripple. 12.6 Cross-Conduction Prevention. 12.7 Snubber Components (Half-Bridge). 12.8 Soft Start. 12.9 Transformer Design. 12.10 Optimum Flux Density. 12.11 Transient Conditions. 12.12 Calculating Primary Turns. 12.13 Calculate Minimum Primary Turns (N_{mpp}). 12.14 Calculate Secondary Turns. 12.15 Control and Drive Circuits. 12.16 Flux Doubling Effect. 12.17 Problems. | |
| 13. BRIDGE CONVERTERS | 2.103 |
| 13.1 Introduction. 13.2 Operating Principle. 13.3 Transformer Design (Full Bridge). 13.4 Transformer Design Example. 13.5 Staircase Saturation. 13.6 Transient Saturation Effects. 13.7 Forced Flux Density Balancing. 13.8 Problems. | |
| 14. LOW-POWER SELF-OSCILLATING AUXILIARY CONVERTERS | 2.116 |
| 14.1 Introduction. 14.2 General Operating Principles. 14.3 Operating Principle, Single-Transformer Converters. 14.3 Transformer Design. | |
| 15. SINGLE-TRANSFORMER TWO-TRANSISTOR SELF-OSCILLATING CONVERTERS | 2.121 |
| 15.1 Introduction. 15.2 Operating Principles (Gain-Limited Switching). 15.3 Defining the Switching Current. 15.4 Choosing Core Materials. 15.5 Transformer Design (Saturating Core Type Converters). 15.6 Problems. | |

| | |
|--|--------------|
| 16. TWO-TRANSFORMER SELF-OSCILLATING CONVERTERS | 2.132 |
| 16.1 Introduction. 16.2 Operating Principles. 16.3 Saturated Drive Transformer Design. 16.4 Selecting Core Size and Material. 16.5 Main Power Transformer Design. 16.6 Problems. | |
| 17. THE DC-TO-DC TRANSFORMER CONCEPT | 2.137 |
| 17.1 Introduction. 17.2 Basic Principle of the DC-to-DC Transformer Concept. 17.3 DC-to-DC Transformer Example. 17.4 Problems. | |
| 18. MULTIPLE-OUTPUT COMPOUND REGULATING SYSTEMS | 2.141 |
| 18.1 Introduction. 18.2 Buck Regulator, Cascaded with a DC-to-DC Transformer. 18.3 Operating Principles. 18.4 Buck Regulator Section. 18.5 DC Transformer Section. 18.6 Synchronized Compound Regulators. 18.7 Compound Regulators with Secondary Post Regulators. 18.8 Problems. | |
| 19. DUTY-RATIO-CONTROLLED PUSH-PULL CONVERTERS | 2.147 |
| 19.1 Introduction. 19.2 Operating Principles. 19.3 Snubber Components. 19.4 Staircase Saturation in Push-Pull Converters. 19.5 Flux Density Balancing. 19.6 Push-Pull Transformer Design (General Considerations). 19.7 Flux Doubling. 19.8 Push-Pull Transformer Design Example. 19.9 Problems. | |
| 20. DC-TO-DC SWITCHING REGULATORS | 2.160 |
| 20.1 Introduction. 20.2 Operating Principles. 20.3 Control and Drive Circuits. 20.4 Inductor Design for Switching Regulators. 20.5 Inductor Design Example. 20.6 General Performance Parameters. 20.7 The Ripple Regulator. 20.8 Problems. | |
| 21. HIGH-FREQUENCY SATURABLE REACTOR POWER REGULATORS (Magnetic Duty Ratio Control) | 2.174 |
| 21.1 Introduction. 21.2 Operating Principles. 21.3 The Saturable Reactor Power Regulator Principle. 21.4 The Saturable Reactor Power Regulator Application. 21.5 Saturable Reactor Quality Factors. 21.6 Selecting Suitable Core Materials. 21.7 Controlling the Saturable Reactor. 21.8 Current Limiting the Saturable Reactor Regulator. 21.9 Push-Pull Saturable Reactor Secondary Power Control Circuit. 21.10 Some Advantages of the Saturable Reactor Regulator. 21.11 Some Limiting Factors in Saturable Reactor Regulators. 21.12 The Case for Constant-Voltage or Constant-Current Reset (High-Frequency Instability Considerations). 21.13 Saturable Reactor Design. 21.14 Design Example. 21.15 Problems. | |
| 22. CONSTANT-CURRENT POWER SUPPLIES | 2.191 |
| 22.1 Introduction. 22.2 Constant-Voltage Supplies. 22.3 Constant-Current Supplies. 22.4 Compliance Voltage. 22.5 Problems. | |

| | |
|--|--------------|
| 23. VARIABLE LINEAR POWER SUPPLIES | 2.195 |
| <i>23.1 Introduction. 23.2 Basic Operation (Power Section). 23.3 Drive Circuit. 23.4 Maximum Transistor Dissipation. 23.5 Distribution of Power Losses. 23.6 Voltage Control and Current Limit Circuit. 23.7 Control Circuit. 23.8 Problems.</i> | |
| 24. SWITCHMODE VARIABLE POWER SUPPLIES | 2.204 |
| <i>24.1 Introduction. 24.2 Variable Switchmode Techniques. 24.3 Special Properties of Flyback Converters (in Variable Supplies). 24.4 Operating Principle. 24.5 Practical Limiting Factors. 24.6 Practical Design Compromises. 24.7 Initial Conditions. 24.8 The Diagonal Half Bridge. 24.9 Block Schematic Diagram (General Description). 24.10 Overall System Operating Principles. 24.11 Individual Block Functions. 24.12 Primary Power Limiting. 24.13 Conclusions.</i> | |
| 25. SWITCHMODE VARIABLE POWER SUPPLY TRANSFORMER DESIGN | 2.220 |
| <i>25.1 Design Steps. 25.2 Variable-Frequency Mode. 25.3 Problems.</i> | |

PART 3 APPLIED DESIGN

| | |
|---|-------------|
| 1. INDUCTORS AND CHOKES IN SWITCHMODE SUPPLIES | 3.3 |
| <i>1.1 Introduction. 1.2 Simple Inductors. 1.3 Common-Mode Line-Filter Inductors. 1.4 Design Example of a Common-Mode Line-Filter Inductor (Using a Ferrite E Core and a Graphical Design Method). 1.5 Calculating Inductance (for Common-Mode Inductors Wound on Ferrite E Cores). 1.6 Series-Mode Line-Input-Filter Inductors. 1.7 Chokes (Inductors with DC Bias). 1.8 Design Example of a Gapped Ferrite E-Core Choke (Using an Empirical Method). 1.9 Design Example of Chokes for Buck and Boost Converters (by Area Product Graphical Methods and by Calculation). 1.10 Choke Design Example for a Buck Regulator (Using a Ferrite E Core and Graphical AP Design Method). 1.11 Ferrite and Iron Powder Rod Chokes. 1.12 Problems.</i> | |
| 2. HIGH-CURRENT CHOKES USING IRON POWDER CORES | 3.29 |
| <i>2.1 Introduction. 2.2 Energy Storage Chokes. 2.3 Core Permeability. 2.4 Gapping Iron Powder E Cores. 2.5 Method Used to Design Iron Powder E-Core Chokes (Graphical Area Product Method). 2.6 Example of Iron Powder E-Core Choke Design (Using the Graphical Area Product Method).</i> | |
| 3. CHOKE DESIGN USING IRON POWDER TOROIDAL CORES | 3.41 |
| <i>3.1 Introduction. 3.2 Preferred Design Approach (Toroids). 3.3 Swinging Chokes. 3.4 Winding Options. 3.5 Design Example (Option A). 3.6 Design Example (Option B). 3.7 Design Example (Option C). 3.8 Core Loss. 3.9 Total Dissipation and Temperature Rise. 3.9.1 Calculate Winding Resistance. 3.10 Linear (Toroidal) Choke Design.</i> | |

| | |
|---|--------------|
| <i>Appendix 3A, Derivation of Area Product Equations. Appendix 3B, Derivation of Packing and Resistance Factors. Appendix 3C, Derivation of Nomogram 3.3.1.</i> | |
| 4. SWITCHMODE TRANSFORMER DESIGN: GENERAL PRINCIPLES | 3.64 |
| <i>4.1 Introduction. 4.2 Transformer Size (General Considerations). 4.3 Optimum Efficiency. 4.4 Optimum Core Size and Flux Density Swing. 4.5 Calculating Core Size in Terms of Area Product. 4.6 Winding Packing Factor K_u. 4.7 Primary Area Factor K_p. 4.8 RMS Current Factor K_r. 4.9 The Effect of Frequency on Transformer Size. 4.10 Flux Density Swing ΔB. 4.11 The Impact of Agency Specifications on Transformer Size. 4.12 Calculation of Primary Turns. 4.13 Calculating Secondary Turns. 4.14 Half Turns. 4.15 Wire Sizes. 4.16 Skin Effects and Optimum Wire Thickness. 4.17 Winding Topology. 4.18 Temperature Rise. 4.19 Efficiency. 4.20 Higher Temperature Rise Designs. 4.21 Eliminating Breakdown Stress in Bifilar Windings. 4.22 RFI Screens and Safety Screens. 4.23 Transformer Half-Turn Techniques. 4.24 Transformer Finishing and Vacuum Impregnation. 4.25 Problems. Appendix 4A, Derivation of Area Product Equations for Transformer Design. Appendix 4B, Skin and Proximity Effects in High-Frequency Transformer Windings.</i> | |
| 5. OPTIMUM 150-W TRANSFORMER DESIGN EXAMPLE USING NOMOGRAMS | 3.108 |
| <i>5.1 Introduction. 5.2 Core Size and Optimum Flux Density Swing. 5.2.1 Use of Nomogram 3.4.3. 5.3 Core and Bobbin Parameters. 5.4 Calculate Primary Turns. 5.5 Calculate Primary Wire Size. 5.6 Primary Skin Effects. 5.7 Secondary Turns. 5.8 Secondary Wire Size. 5.9 Secondary Skin Effects. 5.10 Design Notes. 5.11 Design Confirmation. 5.12 Primary Copper Loss. 5.13 Secondary Copper Loss. 5.14 Core Loss. 5.15 Temperature Rise. 5.16 Efficiency.</i> | |
| 6. TRANSFORMER STAIRCASE SATURATION | 3.115 |
| <i>6.1 Introduction. 6.2 Methods of Reducing Staircase Saturation Effects. 6.3 Forced Flux Balancing in Duty-Ratio-Controlled Push-Pull Converters. 6.4 Staircase Saturation Problems in Current-Mode Control Systems. 6.5 Problems.</i> | |
| 7. FLUX DOUBLING | 3.121 |
| 8. STABILITY AND CONTROL-LOOP COMPENSATION IN SMPS | 3.122 |
| <i>8.1 Introduction. 8.2 Some Causes of Instability in Switchmode Supplies. 8.3 Methods of Stabilizing the Loop. 8.4 Stability Testing Methods. 8.5 Test Procedure. 8.6 Transient Testing Analysis. 8.7 Bode Plots. 8.8 Measurement Procedures for Bode Plots of Closed-Loop Power Supply Systems. 8.9 Test Equipment for Bode Plot Measurement. 8.10 Test Techniques. 8.11 Measurement Procedures for Bode Plots of Open-Loop Power Supply Systems. 8.12 Establishing Optimum Compensation Characteristic by the "Difference" Method. 8.13 Some Causes of Stubborn Instability. 8.14 Problems.</i> | |

- 9. THE RIGHT-HALF-PLANE ZERO** 3.136
 9.1 Introduction. 9.2 Explanation of the Dynamics of the Right-Half-Plane Zero. 9.3 The Right-Half-Plane Zero—A Simplified Explanation. 9.4 Problems.
- 10. CURRENT-MODE CONTROL** 3.142
 10.1 Introduction. 10.2 The Principles of Current-Mode Control. 10.3 Converting Current-Mode Control to Voltage Control. 10.4 Performance of the Complete Energy Transfer Current-Mode-Controlled Flyback Converter. 10.5 The Advantages of Current-Mode Control in Continuous-Inductor-Current Converter Topologies. 10.6 Slope Compensation. 10.7 Advantages of Current-Mode Control in Continuous-Inductor-Current-Mode Buck Regulator. 10.8 Disadvantages Intrinsic to Current-Mode Control. 10.9 Flux Balancing in Push-Pull Topologies When Using Current-Mode Control. 10.10 Asymmetry Caused by Charge Imbalance in Current-Mode-Controlled Half-Bridge Converters and Other Topologies Using DC Blocking Capacitors. 10.11 Summary. 10.12 Problems.
- 11. OPTOCOUPLERS** 3.161
 11.1 Introduction. 11.2 Optocoupler Interface Circuit. 11.3 Stability and Noise Sensitivity. 11.4 Problems.
- 12. RIPPLE CURRENT RATINGS FOR ELECTROLYTIC CAPACITORS IN SWITCHMODE POWER SUPPLIES** 3.166
 12.1 Introduction. 12.2 Establishing Capacitor RMS Ripple Current Ratings From Published Data. 12.3 Establishing the Effective RMS Ripple Current in Switchmode Output-Filter Capacitor Applications. 12.4 Recommended Test Procedures. 12.5 Problems.
- 13. NONINDUCTIVE CURRENT SHUNTS** 3.172
 13.1 Introduction. 13.2 Current Shunts. 13.3 Resistance/Inductance Ratio of a Simple Shunt. 13.4 Measurement Error. 13.5 Construction of Low-Inductance Current Shunts. 13.6 Problems.
- 14. CURRENT TRANSFORMERS** 3.176
 14.1 Introduction. 14.2 Types of Current Transformers. 14.3 Core Size and Magnetizing Current (All Types). 14.4 Current Transformer Design Procedure. 14.5 Unidirectional Current Transformer Design Example. 14.6 Type 2, Current Transformers (for Alternating Current Push-Pull Applications). 14.7 Type 3, Flyback-Type Current Transformers. 14.8 Type 4, DC Current Transformers (DCCT). 14.9 Using Current Transformers in Flyback Converters.
- 15. CURRENT PROBES FOR MEASUREMENT PURPOSES** 3.193
 15.1 Introduction. 15.2 Special-Purpose Current Probes. 15.3 The Design of Current Probes for Unidirectional (Discontinuous) Current Pulse Measurements. 15.4 Select Core Size. 15.5 Calculate Required

- Core Area. 15.6 Check Magnetization Current Error. 15.7 Current Probes in Applications with DC and AC Currents. 15.8 High-Frequency AC Current Probes. 15.9 Low-Frequency AC Current Probes. 15.10 Problems.
- 16. THERMAL MANAGEMENT (In Switchmode Power Supplies)** 3.201
 16.1 Introduction. 16.2 The Effect of High Temperatures on Semiconductor Life and Power Supply Failure Rates. 16.3 The Infinite Heat Sink, Heat Exchangers, Thermal Shunts, and Their Electrical Analogs. 16.4 The Thermal Circuit and Equivalent Electrical Analog. 16.5 Heat Capacity C_h (Analogous to Capacitance C). 16.6 Calculating Junction Temperature. 16.7 Calculating the Heat Sink Size. 16.8 Methods of Optimizing Thermal Conductivity Paths, and Where to Use "Thermal Conductive Joint Compound". 16.9 Convection, Radiation, or Conduction? 16.10 Heat Exchanger Efficiency. 16.11 The Effect of Input Power on Thermal Resistance. 16.12 Thermal Resistance and Heat Exchanger Area. 16.13 Forced-Air Cooling. 16.14 Problems.
- Glossary 3.222
 References 3.231
 Index