

Recent Developments in EMI Filters

By Prof. Dan Chen

-Introduction


**-Several Recent Techniques for EMI
reduction**

-Prediction/Simulation of Conducted EMI

-Effects of Parasitic Coupling

-Integration of Filters



Noise Sources and Coupling Path

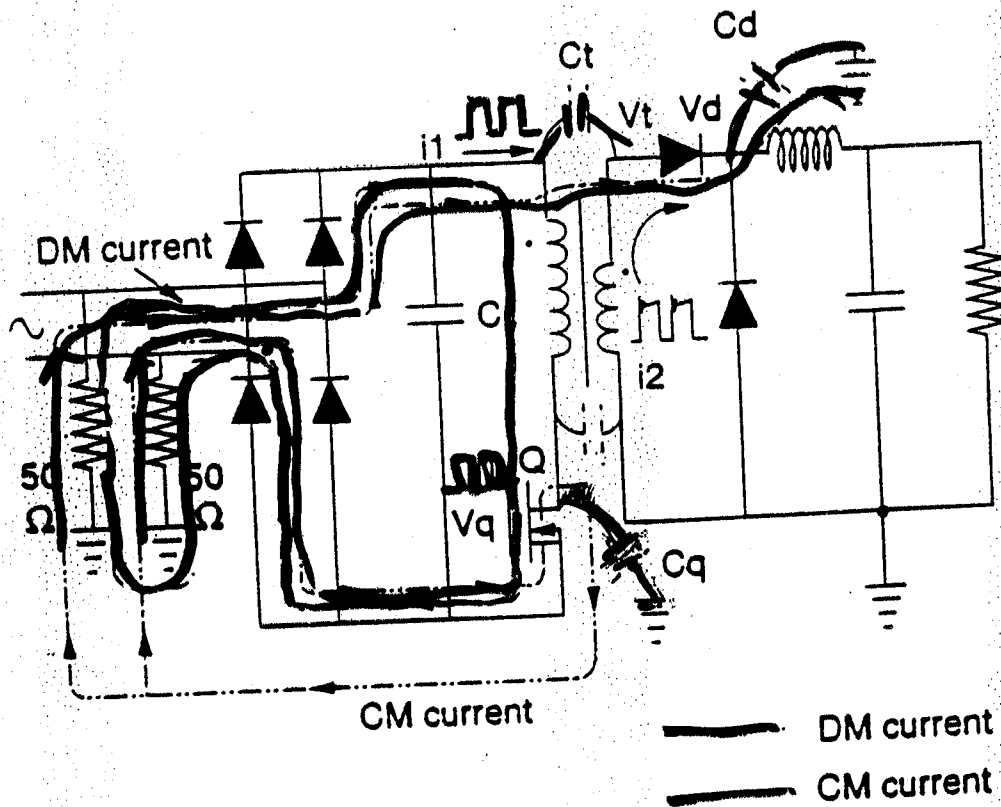

D.M. Noise - Caused by i_1


C.M. Noise - Caused by Parasitic Capacitances

Filtering

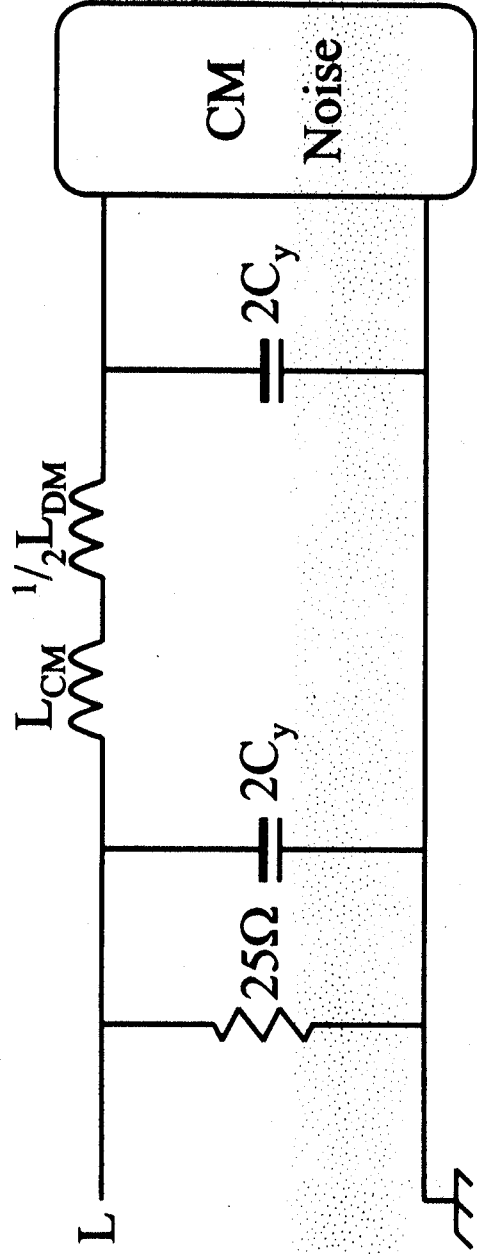
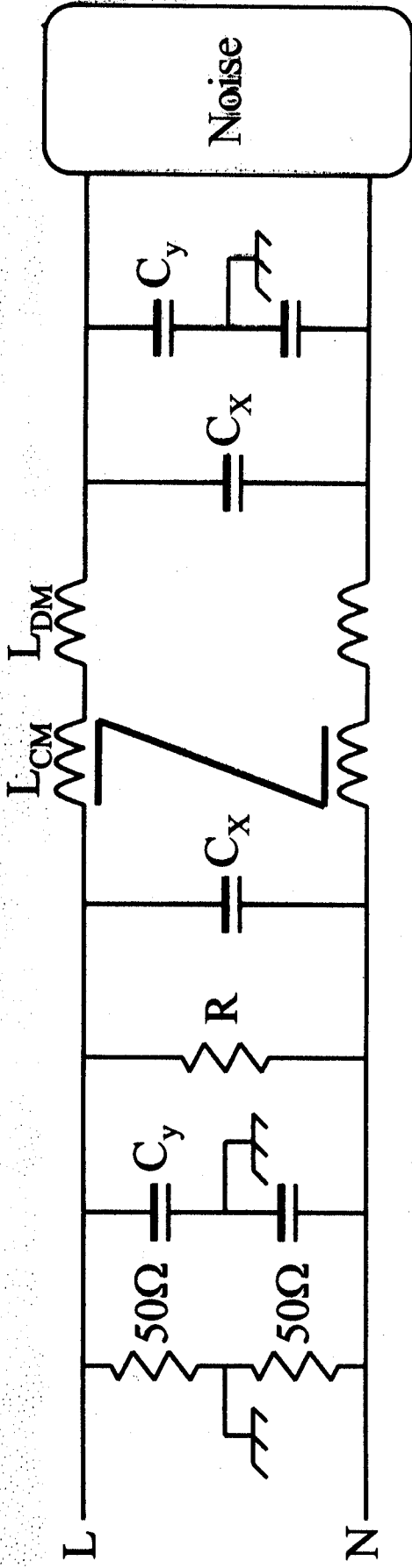


Conducted EMI Reduction by Frequency Modulation


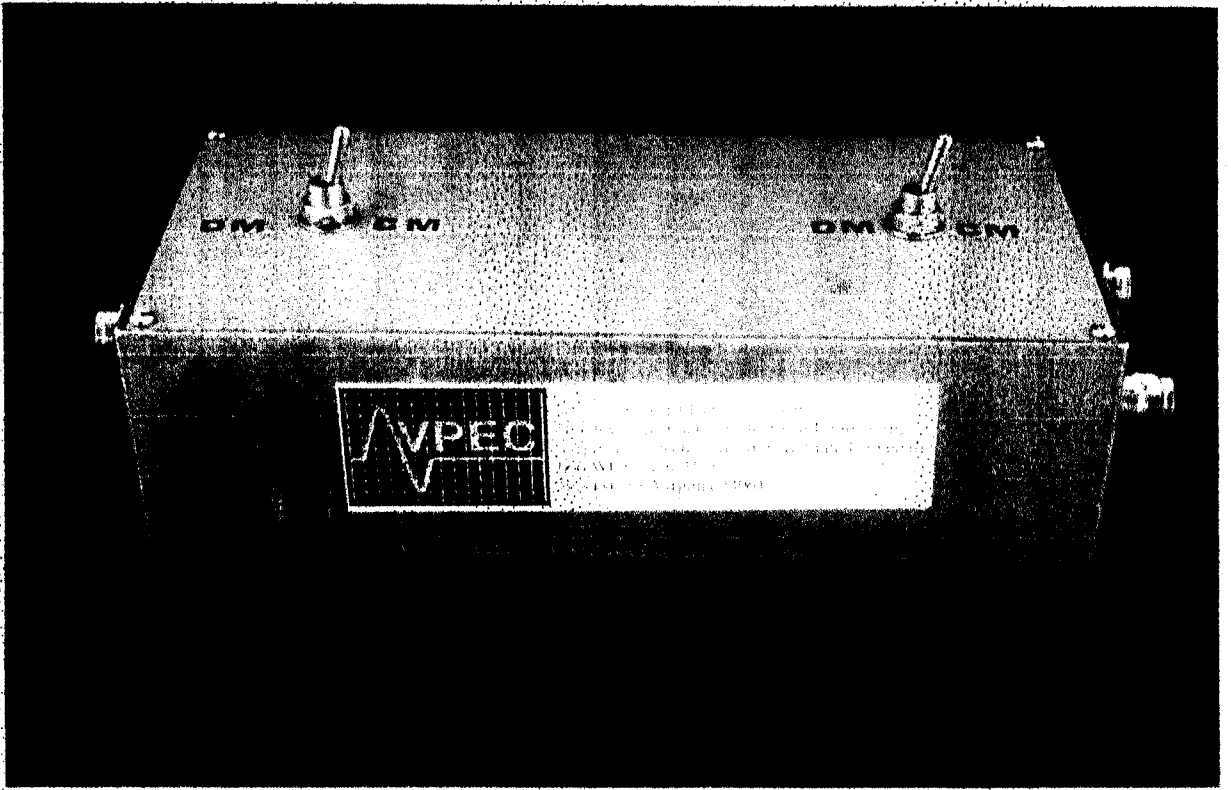
- Suppression
- Decoupling
- Filtering / Shielding
- Frequency Modulation



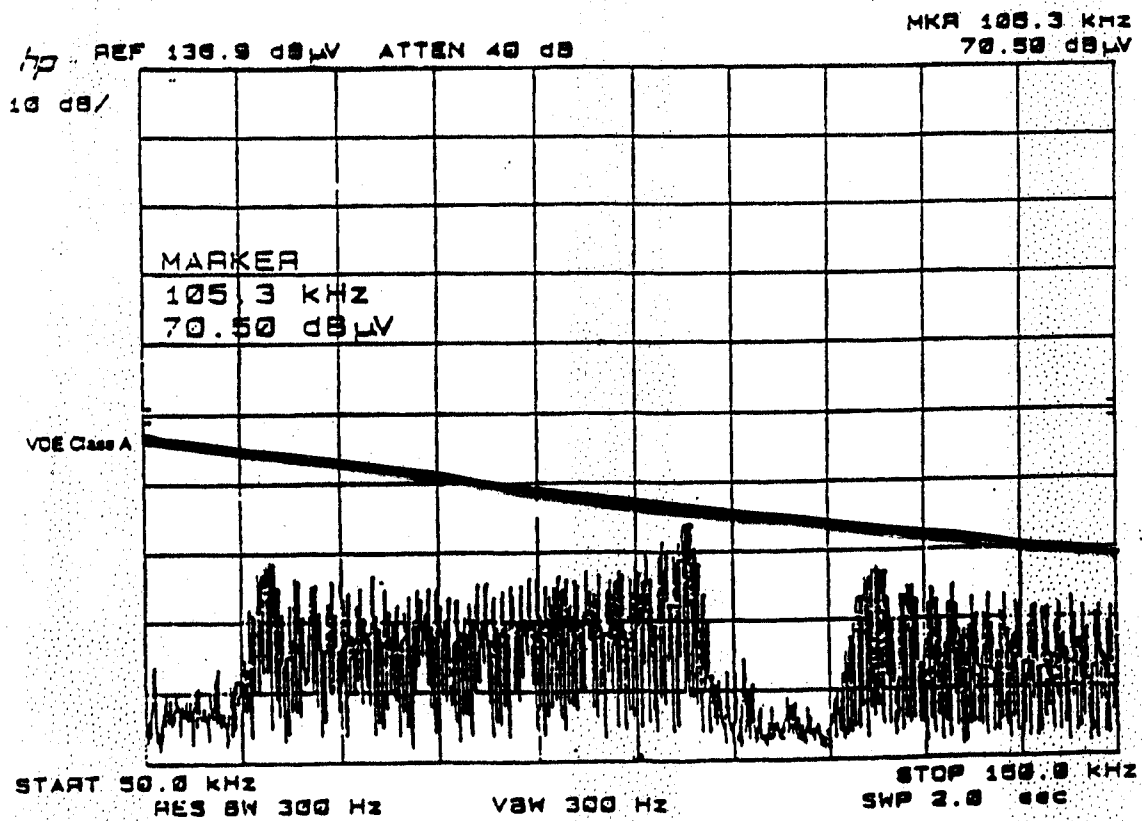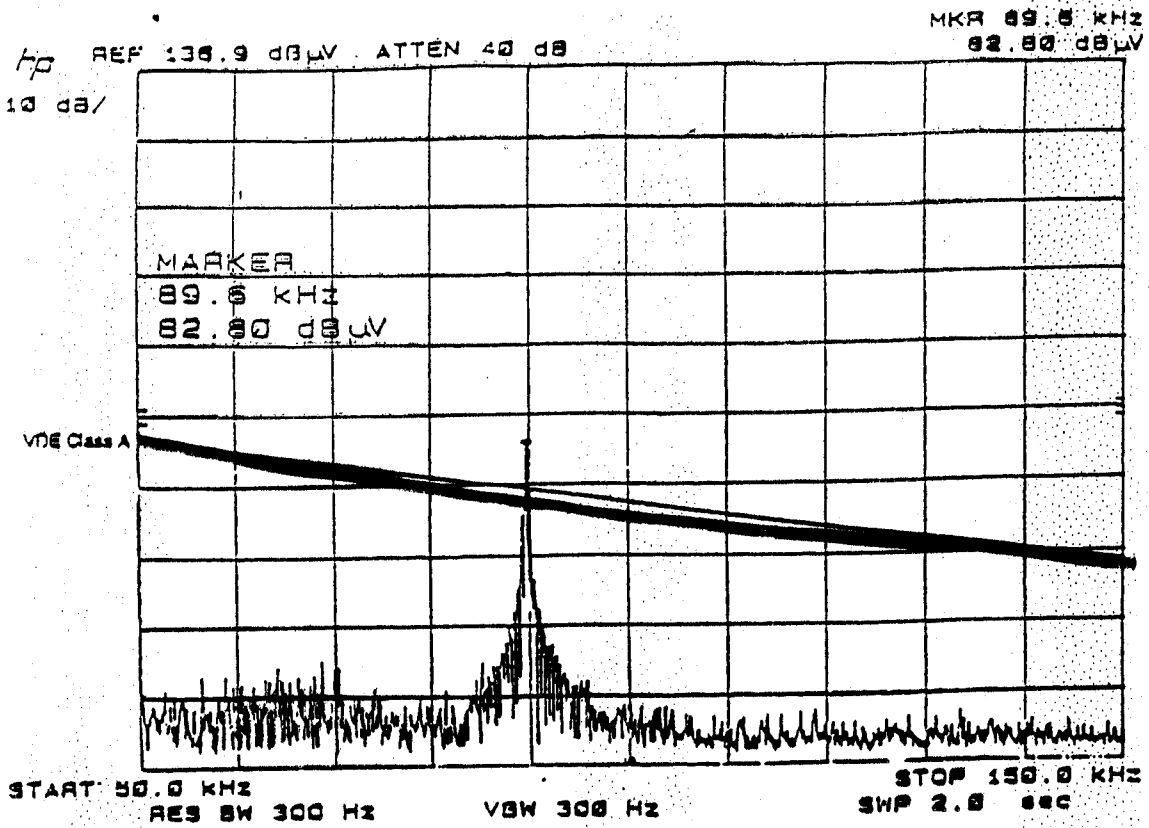VENTILATOR PUMP ELECTRIC CONTROL
120V AC 50/60 Hz
1.5L/min - 120L/min
100% Oxygen




Frequency Spectrum of FM Signals

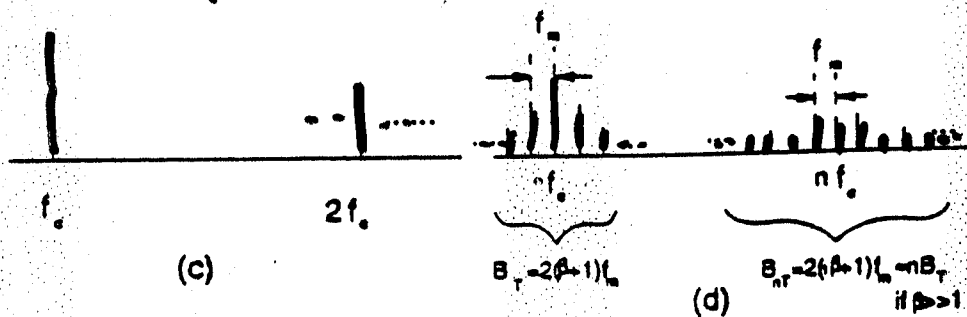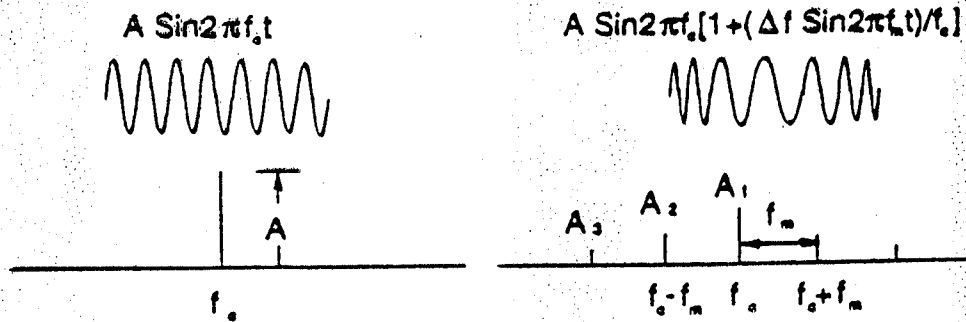




Passive Cancellation Concept

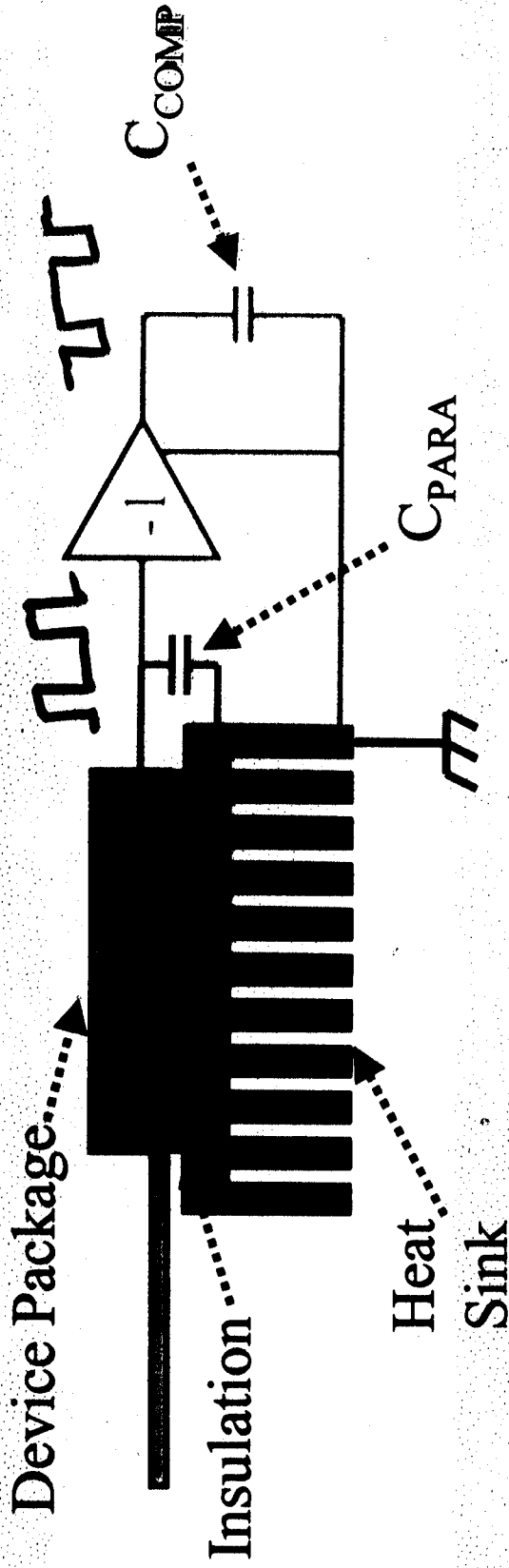


- Use transformer winding to capture switch dv/dt and reverse polarity
- Generate equal and opposite noise current with C_{COMP}




Noise Paths in a Converter

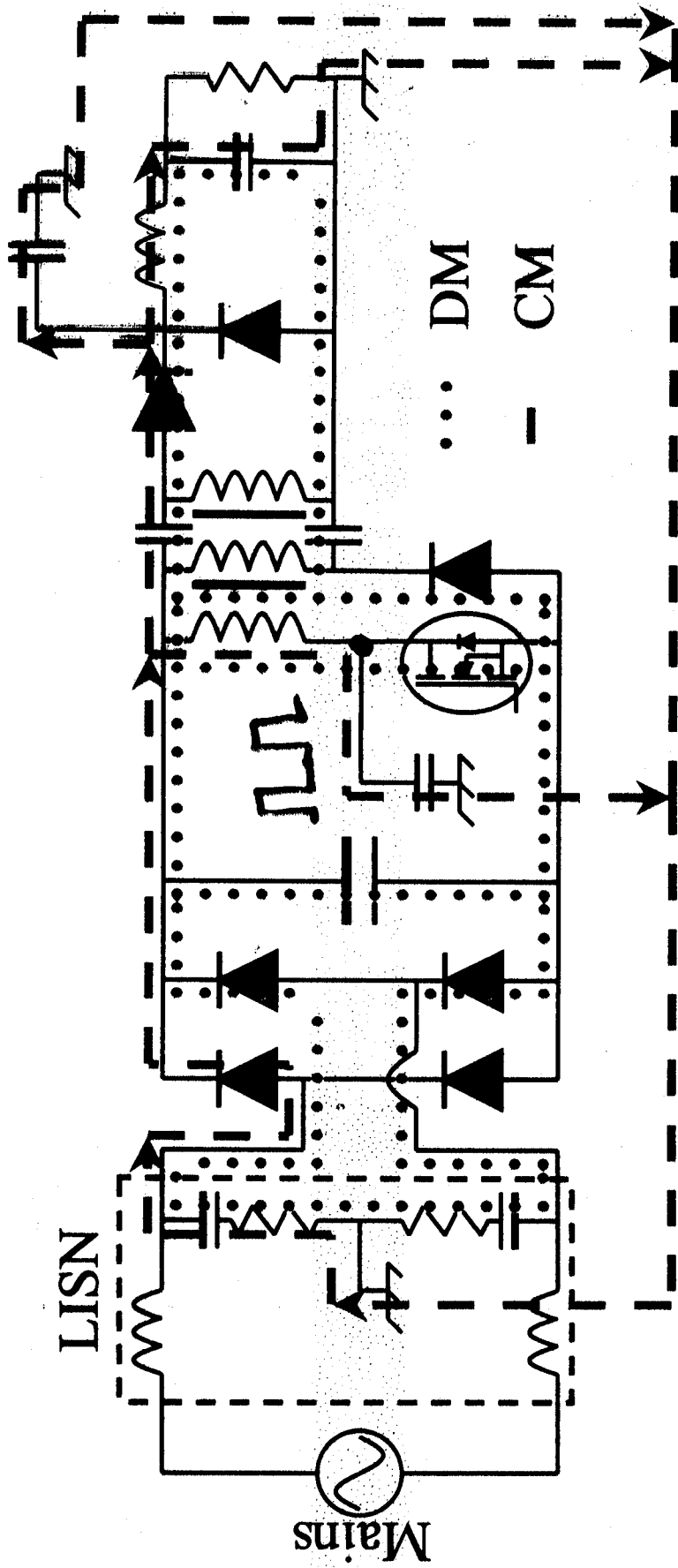

Forward Converter

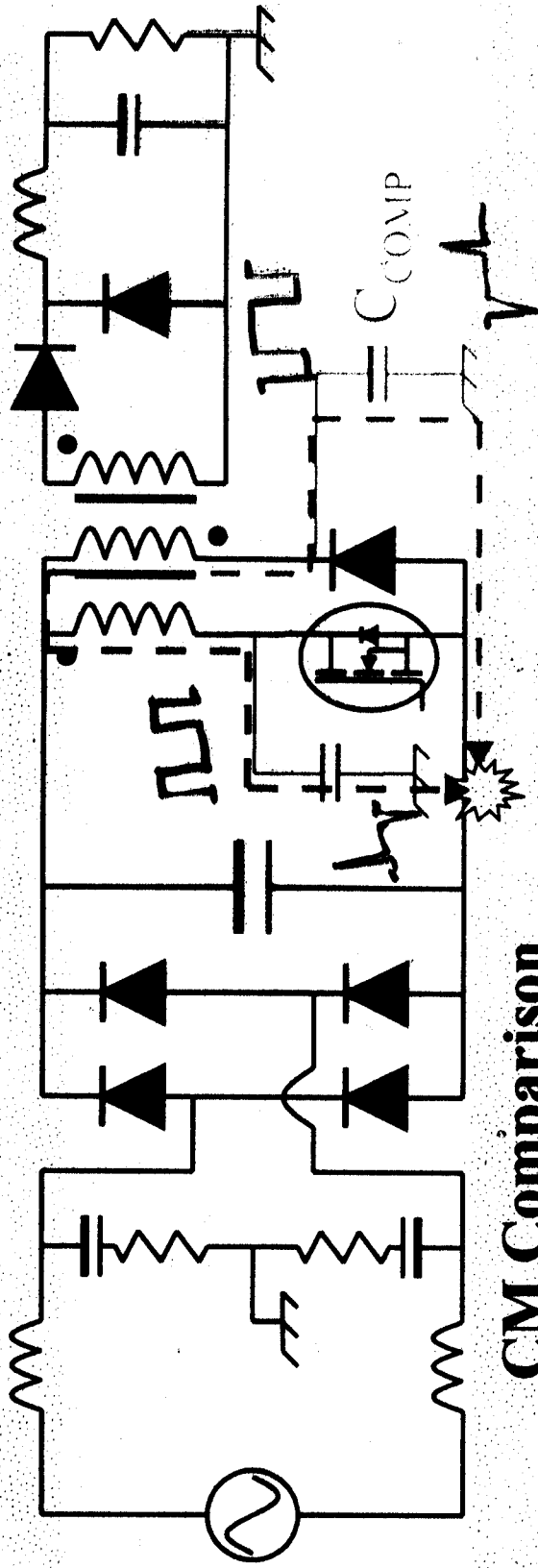

CM Comparison

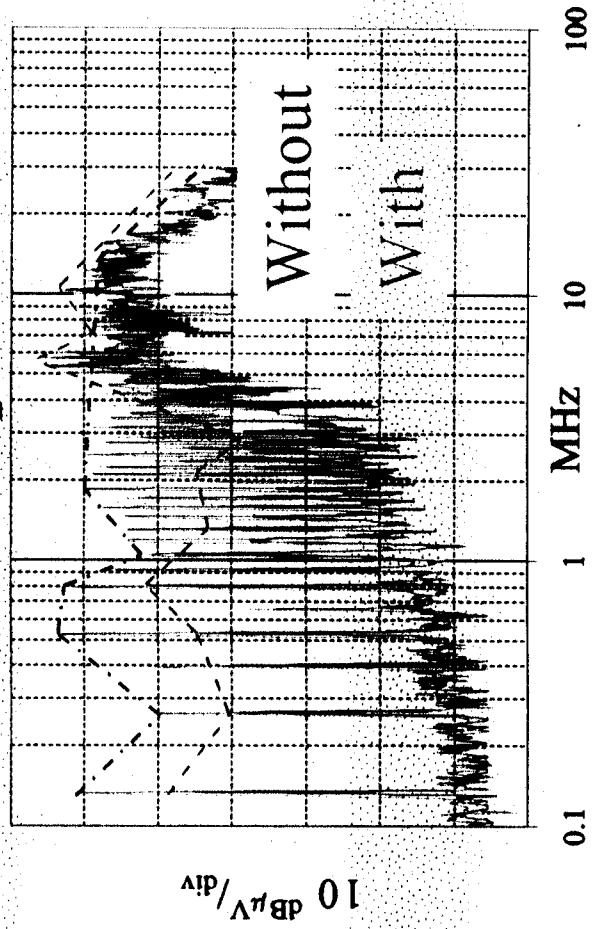



Input Voltage: 120 VAC

Output Voltage: 12 V

Output Power: 100 W

Switching Frequency: 110 kHz


Half-Bridge DC/DC

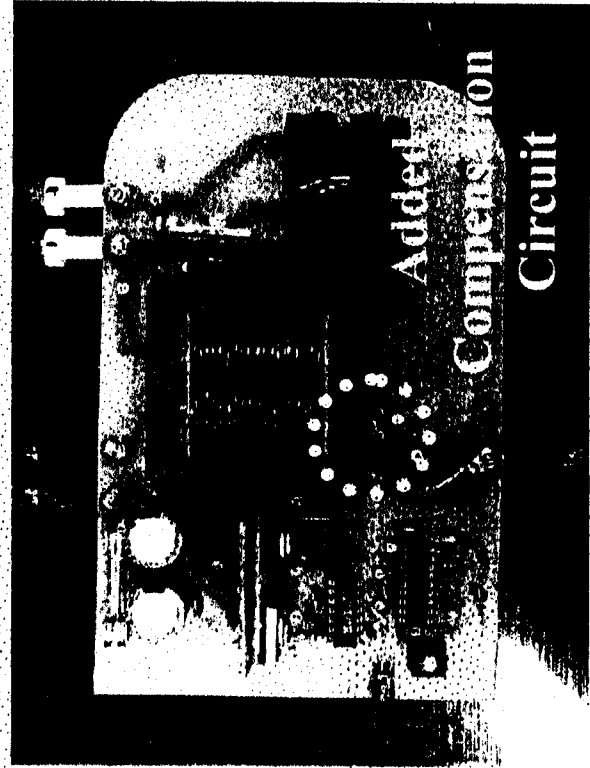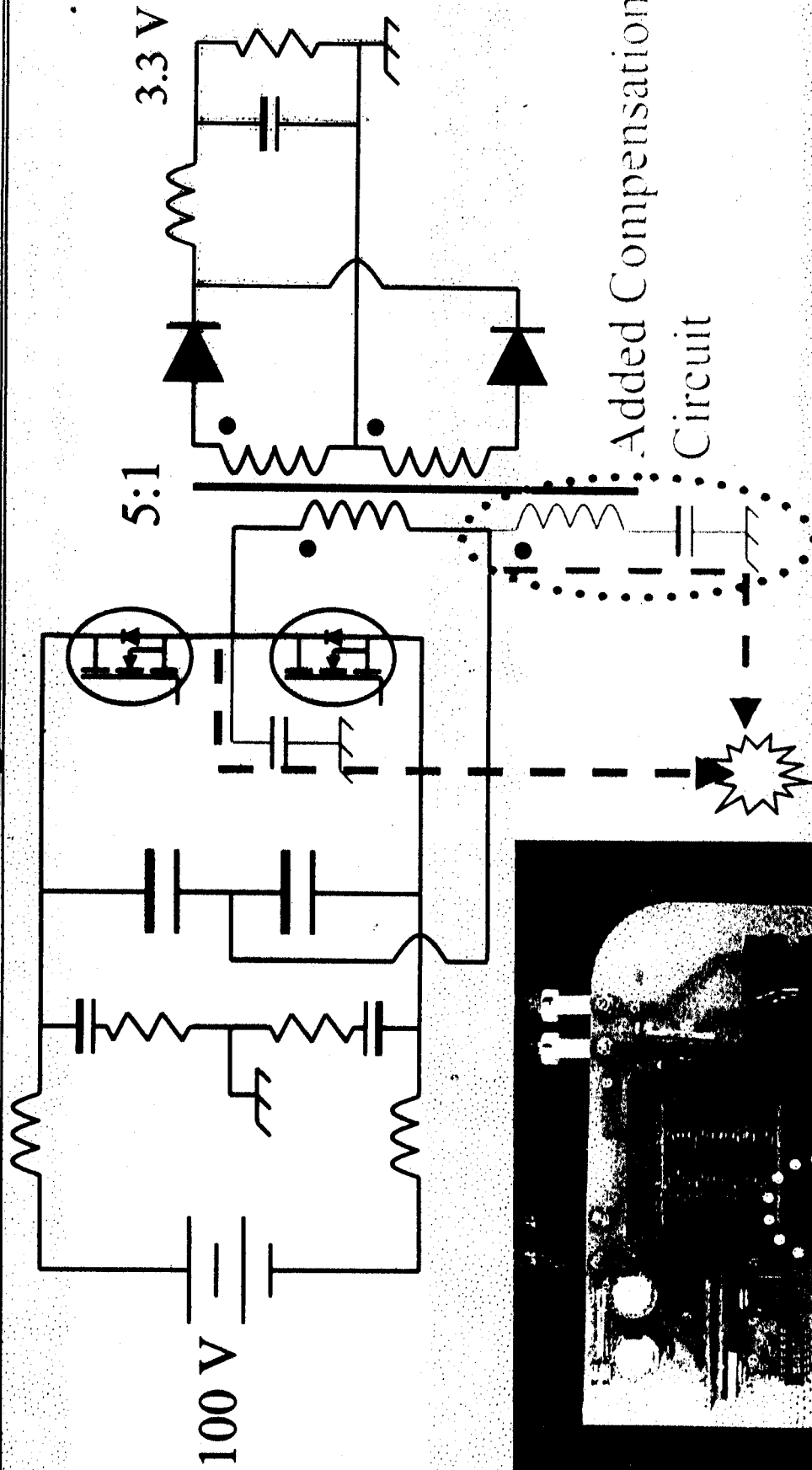

Switching Frequency: 110 kHz


Output Power: 30 W

Half-Bridge Results

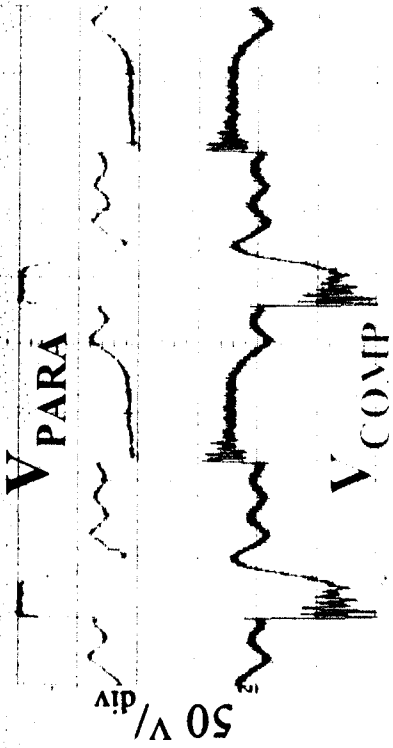


2 μ s/div


CM Comparison

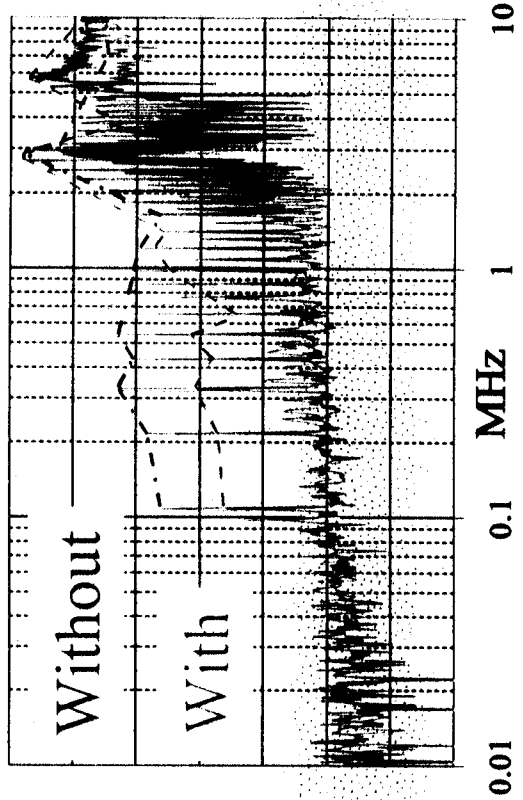

DM Comparison

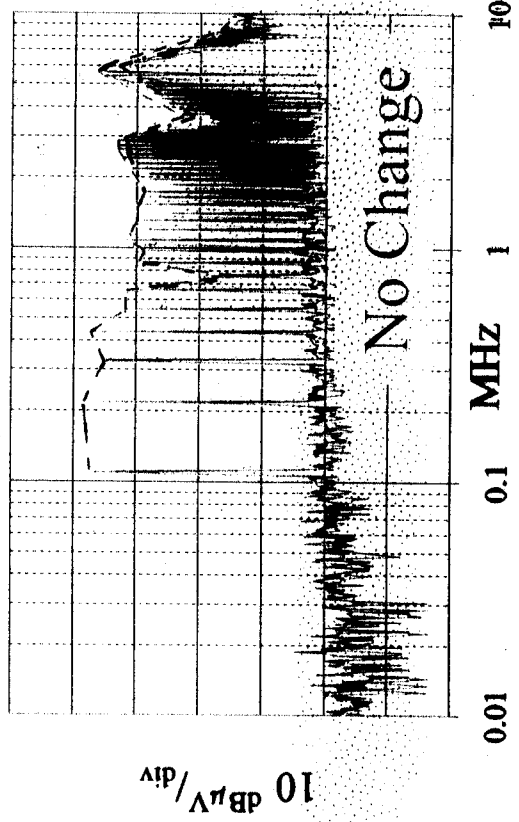


Problems Caused by Common Mode Current

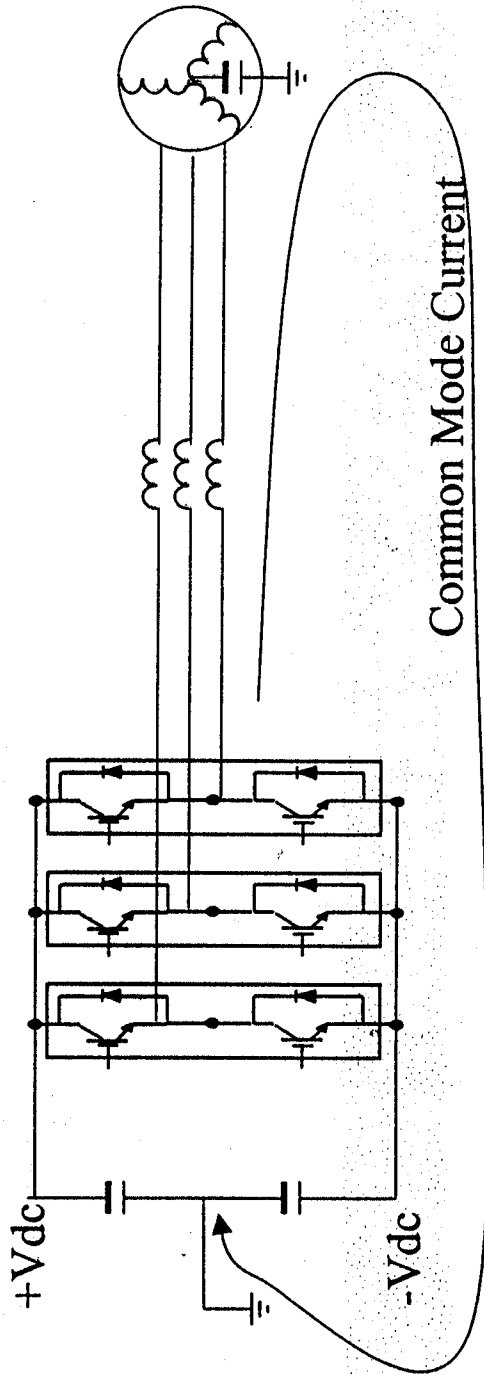


- Conducted EMI
- Damage to motor bearings
- Shortening of insulation life of motors and transformers
- Activation of ground fault detection circuit

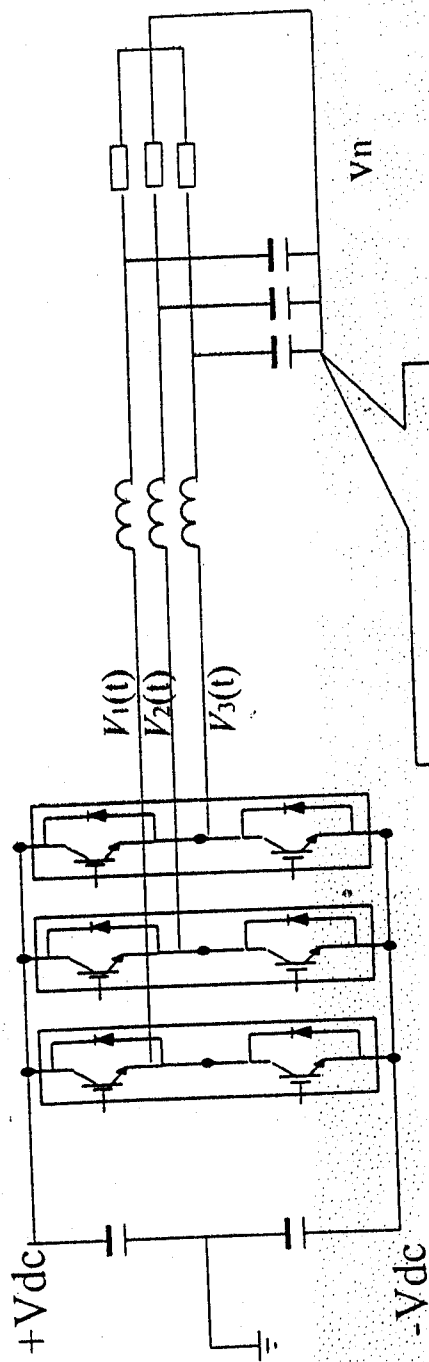
3-leg inverter with floating load neutral point


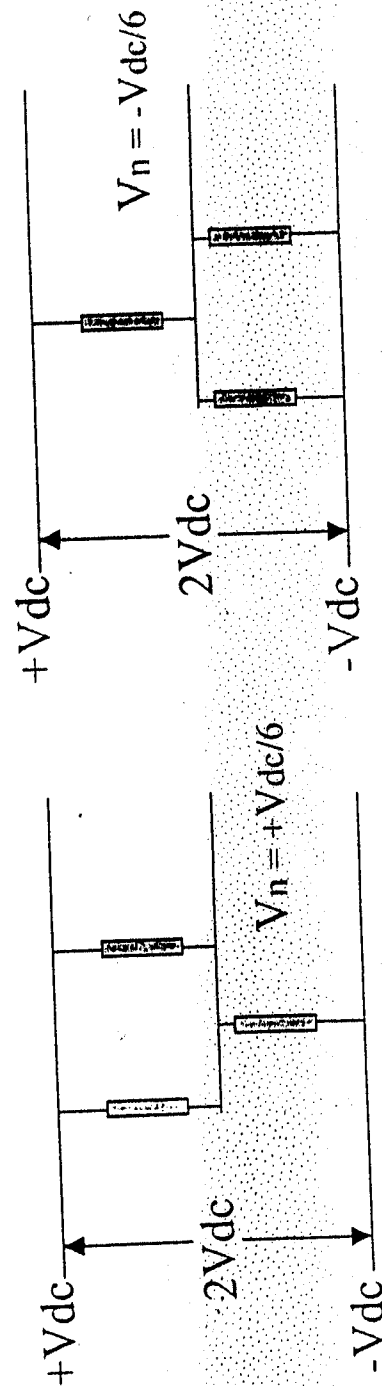
$$V_n(t) = \frac{V_1(t) + V_2(t) + V_3(t)}{3}$$




Active Cancellation

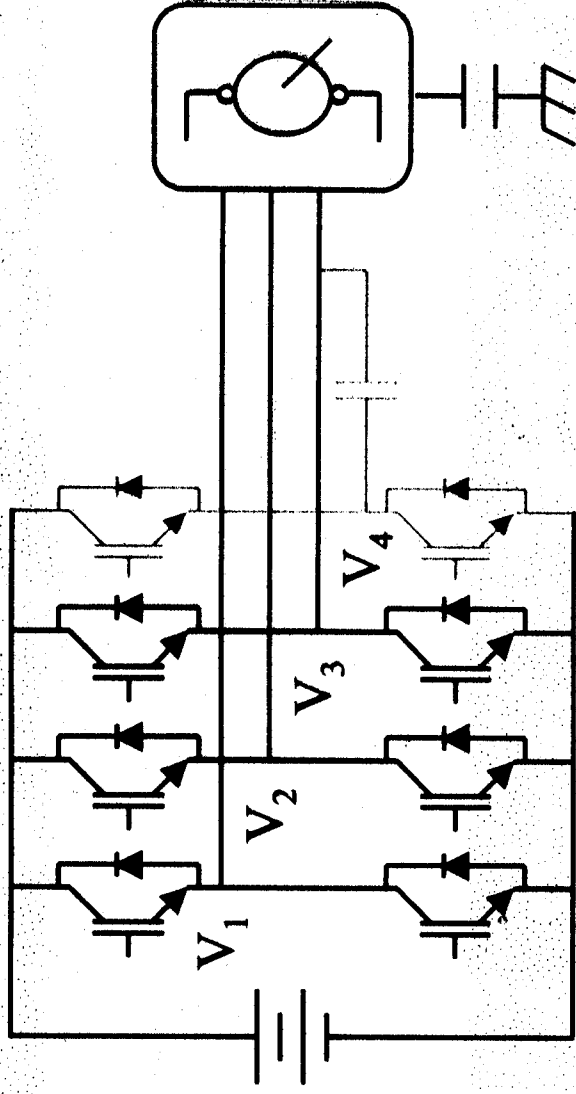

Modulate such that $V_1 + V_2 + V_3 + V_4 = 0$

Orti, Julian, Lipo, "A New Space Vector Modulation Strategy for Common Mode Voltage Reduction", PESC '97

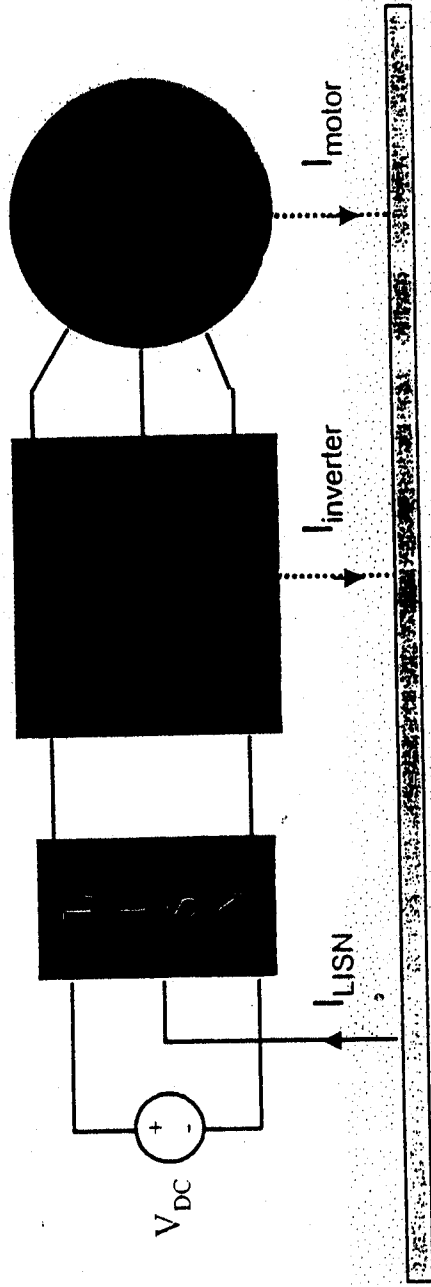3-Phase PWM inverter-fed AC motor drive system




$$I_{CM} = I_{LISN} = I_{inverter} + I_{motor}$$

- Undesirable influence on the motor current control
- Incorrect operation of current-operated circuit breakers
- Cause electromagnetic interference


Make V_{N1} equal to V_{N2}

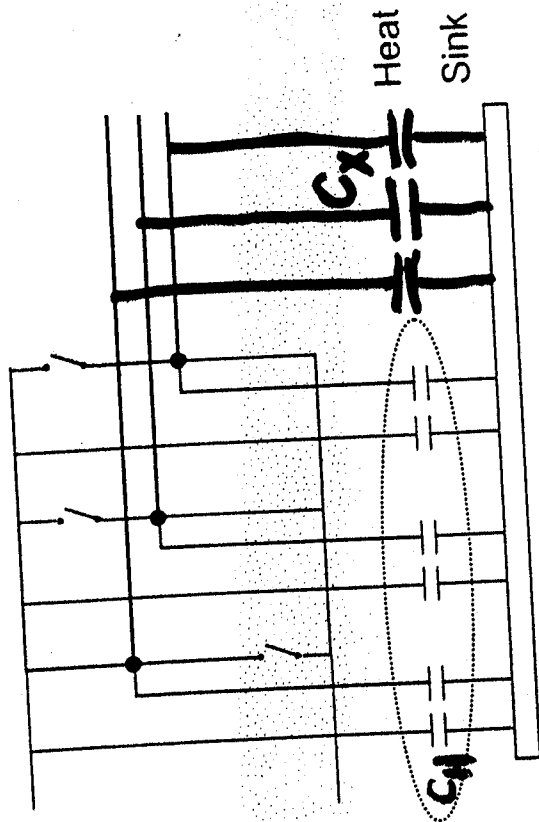Method C: Add compensation capacitors to heat sink




V_{N1} = Noise voltage on heat sink

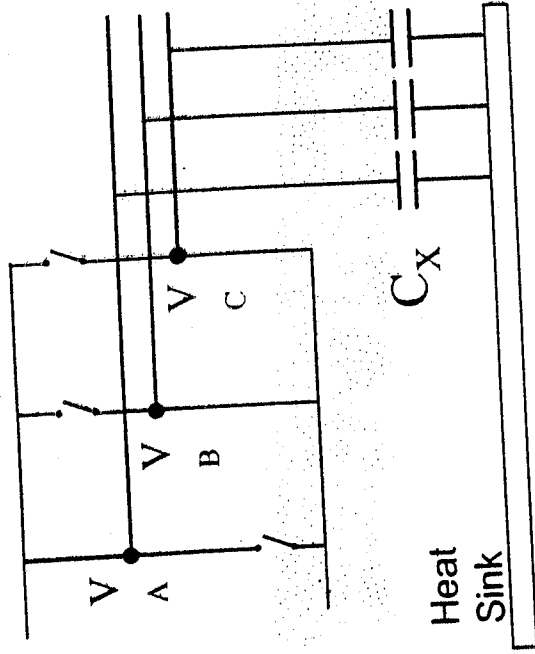$C_X \gg C_H \rightarrow C_H$ can be neglected



$$V_{N1} = (V_A + V_B + V_C) / 3 = V_{N2}$$


Equivalent Circuit of CM Current Loop

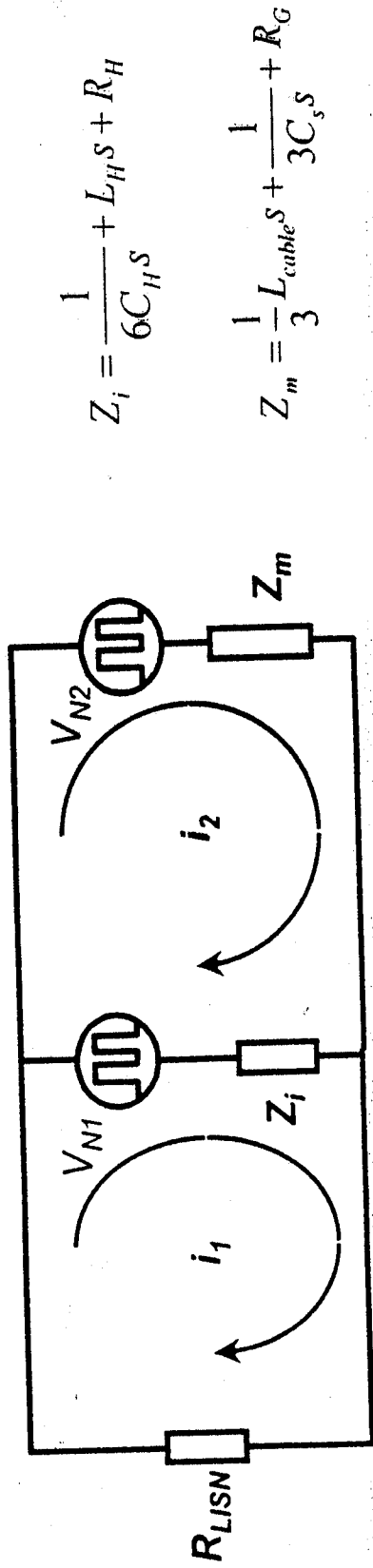

$$i_{LISN} = i_1 = \frac{V_{n1}}{Z_i R_{LISN} + Z_i + R_{LISN}} + \frac{V_{n2}}{Z_m R_{LISN} + Z_m + R_{LISN}}$$

$$i_{motor} = i_2 = -\frac{V_{n1}}{Z_i Z_m + Z_i + Z_m} + \frac{V_{n2}}{Z_i R_{LISN} + Z_i + R_{LISN}}$$

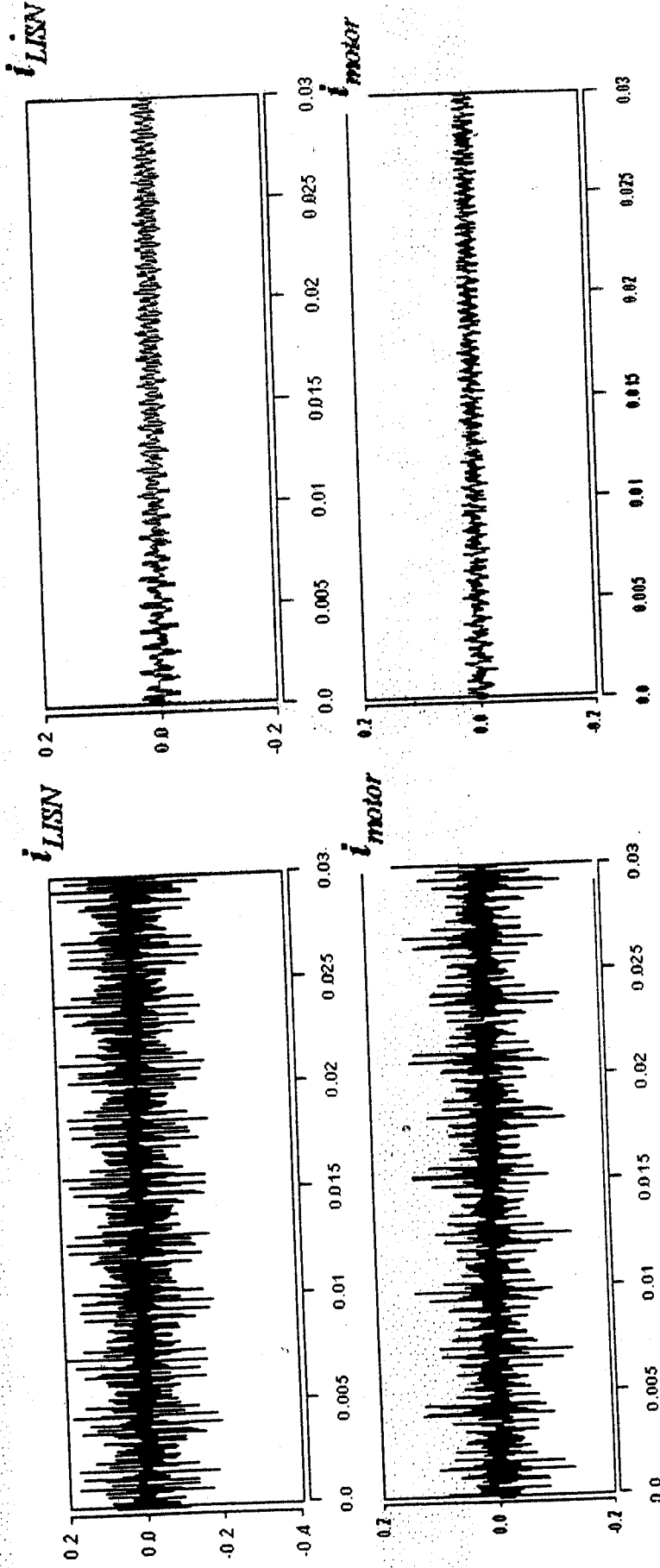Compare simulation results of Method A and C



method C

method A


Compared with method A and C, method C significantly attenuate CM currents

Power Circuit EMI Simulation Steps

- **Component modeling (impedance analyzer)**
- **Layout Modeling (Ansoft "Maxwell")**
- **Time -Domain simulation (SPICE ect)**
- **Conversion to Freq. Domain info. (Fast-Fourier Transform)**



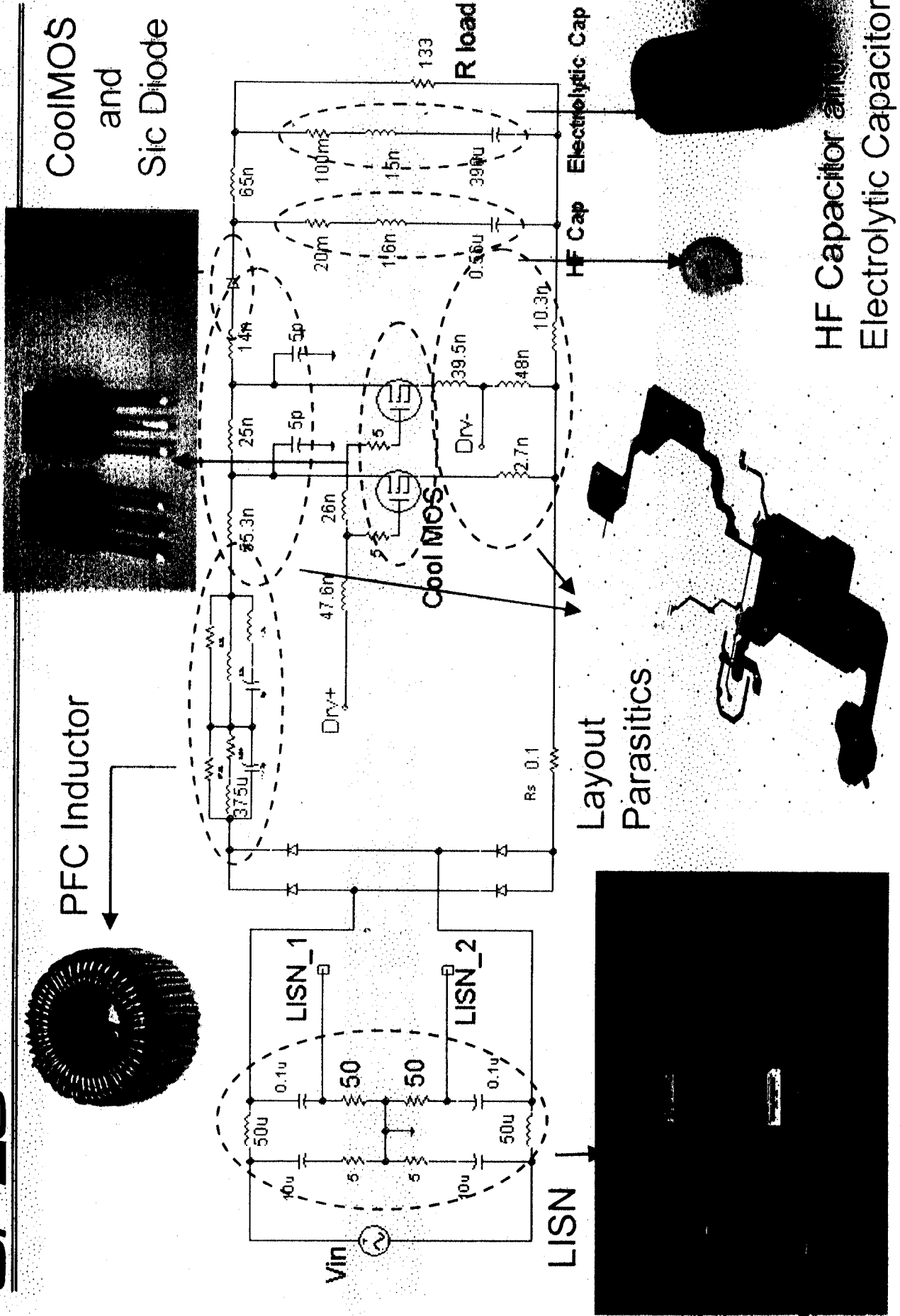
System Simulation Circuit for Conducted EMI



HF Capacitor and Electrolytic Capacitor



Problems in DM noise measurement

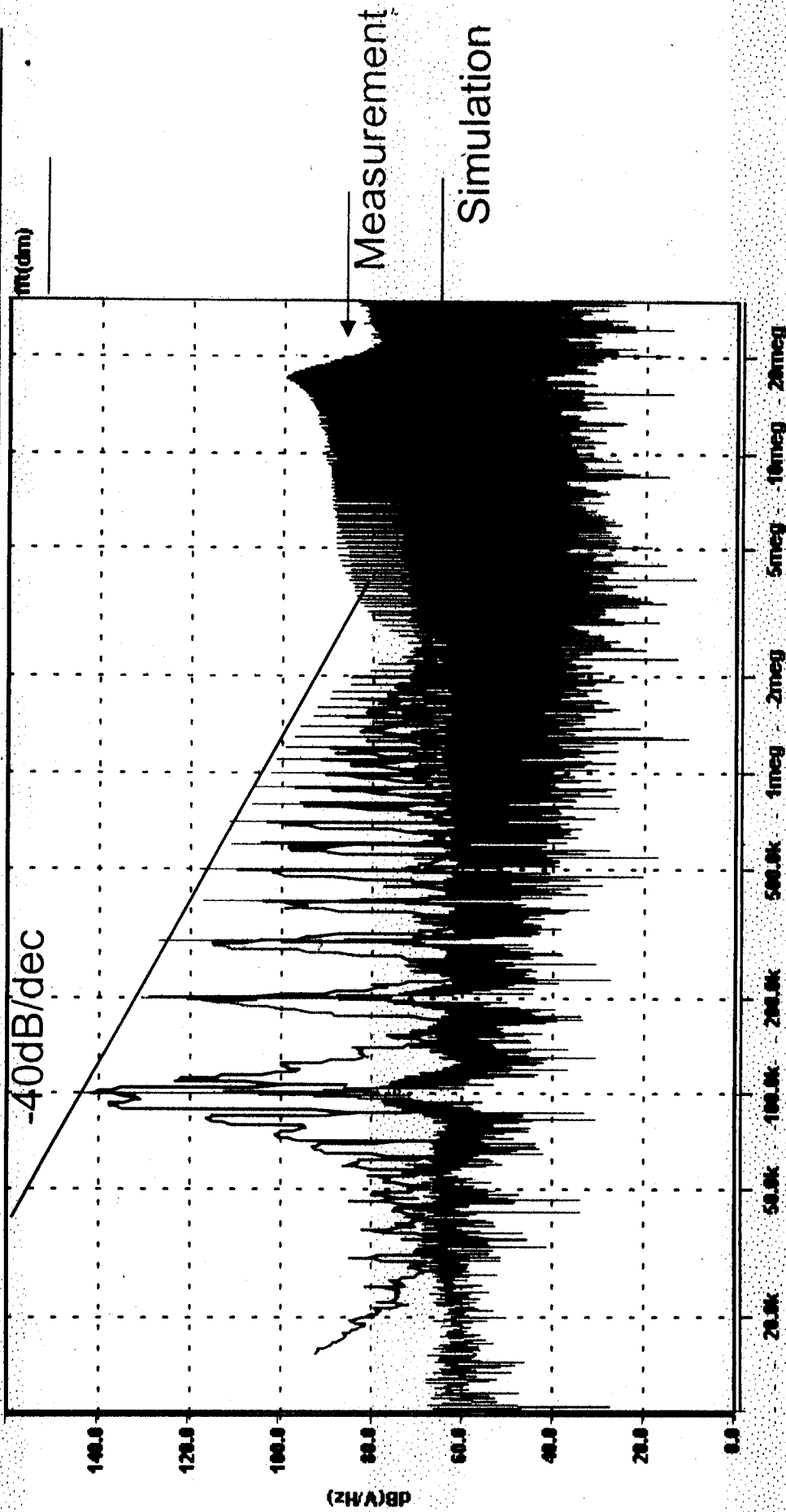

Problems:

- Noise level in low frequency cannot match the simulated level.
- The slope in low frequency is not -40dB/dec .



Verification of Model in Single-Leg Testing

CPES




Single-leg Testing

LISN

Single-leg Simulation

Bus bar model





IGBT model with parasitic

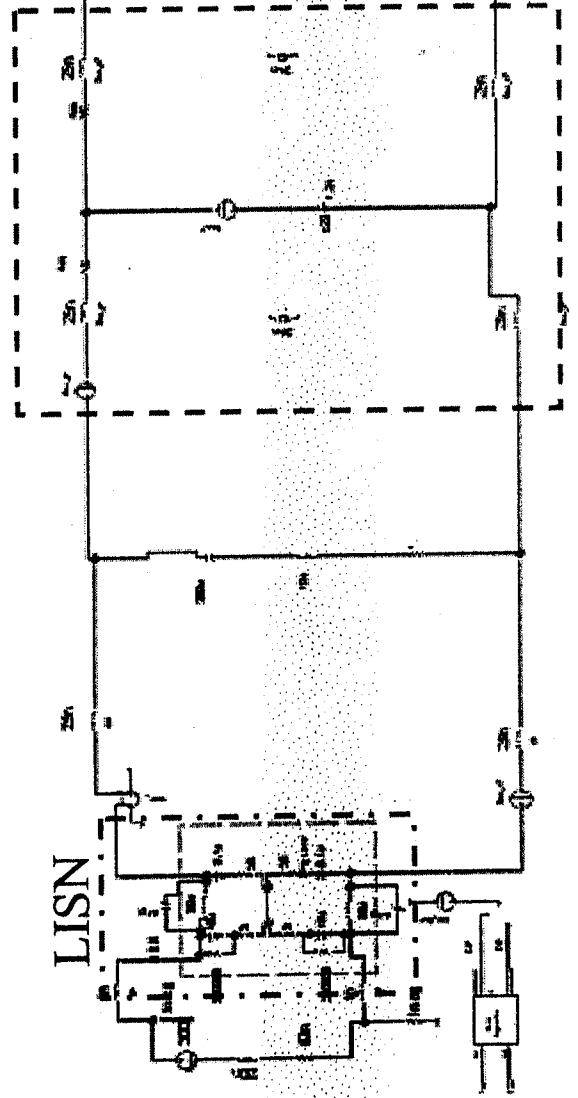




CPES

Comparison of LISN Measurement Noise

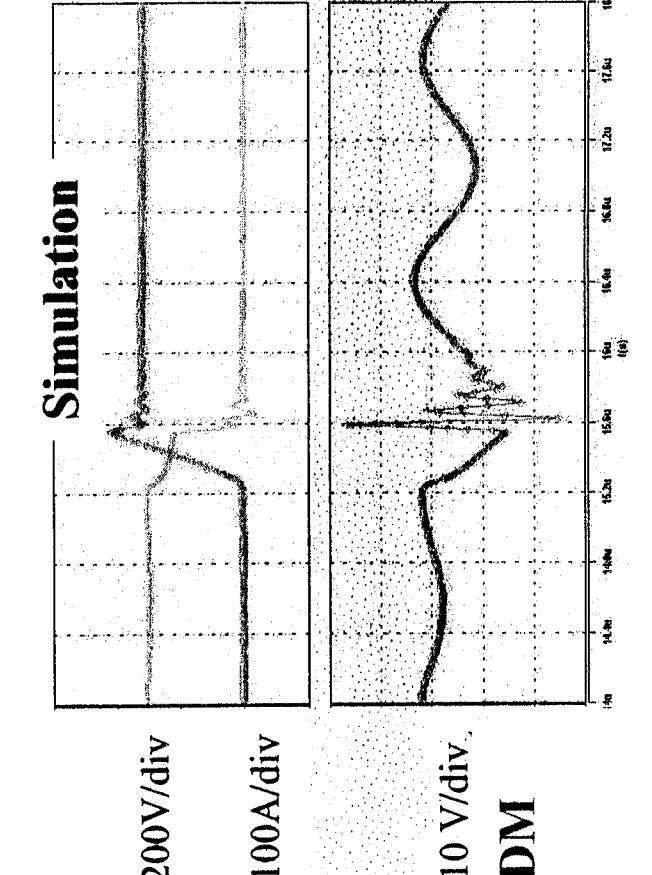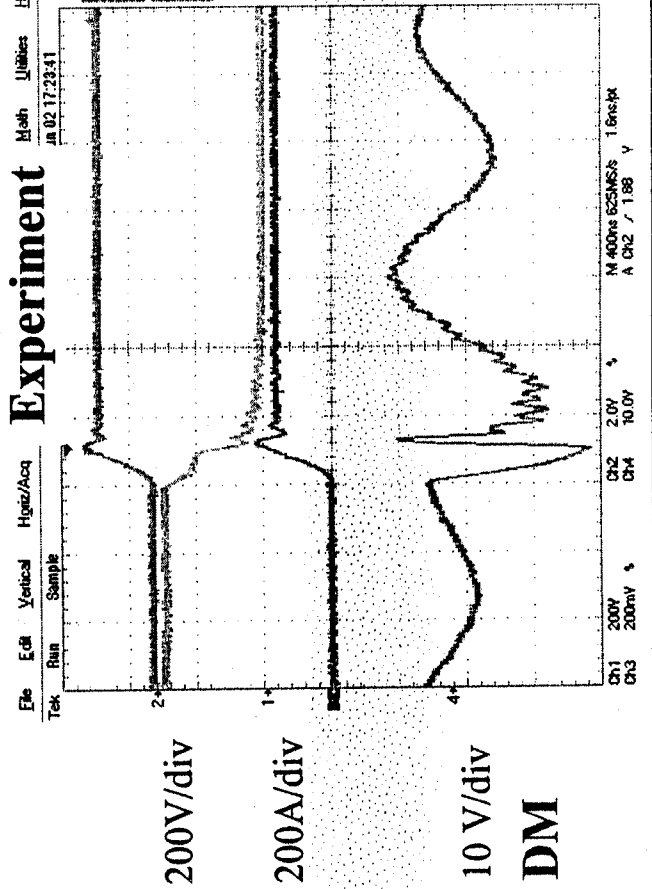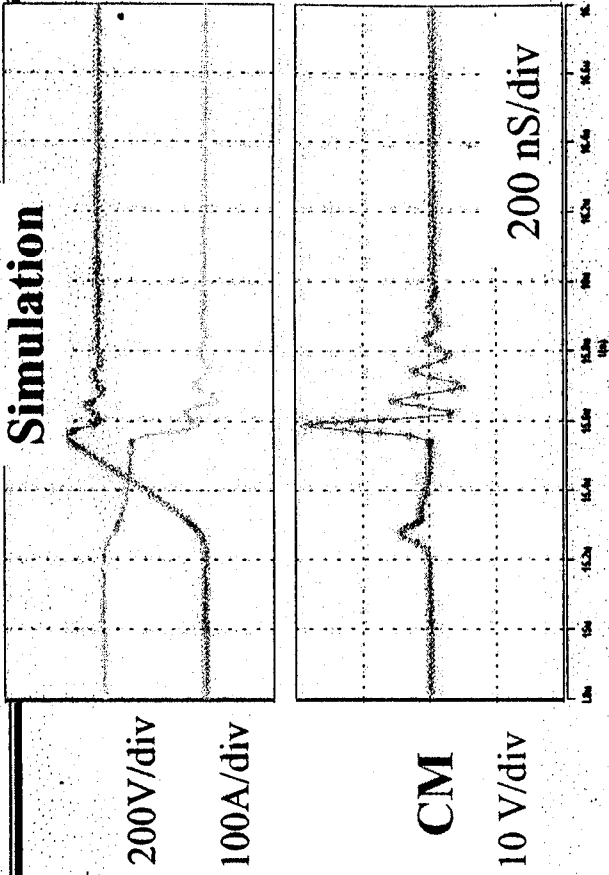
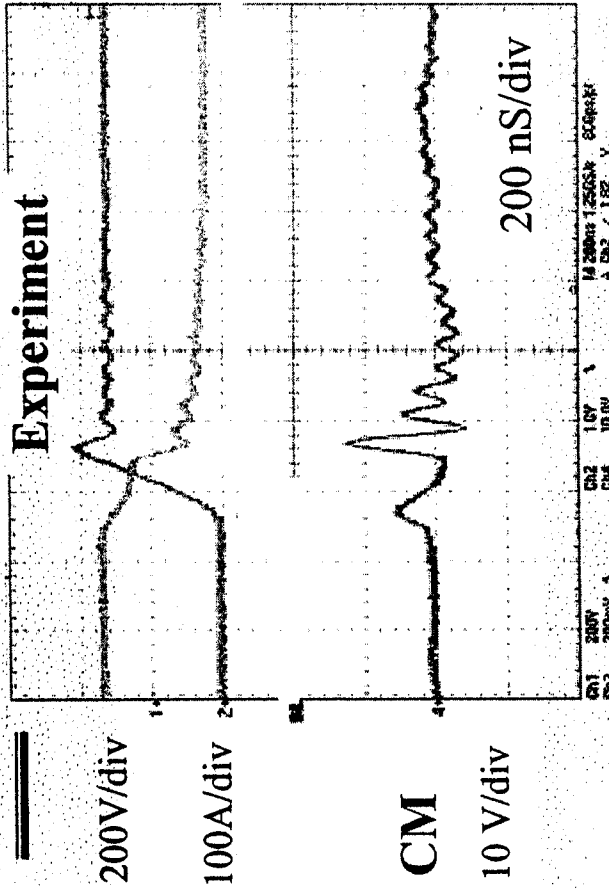


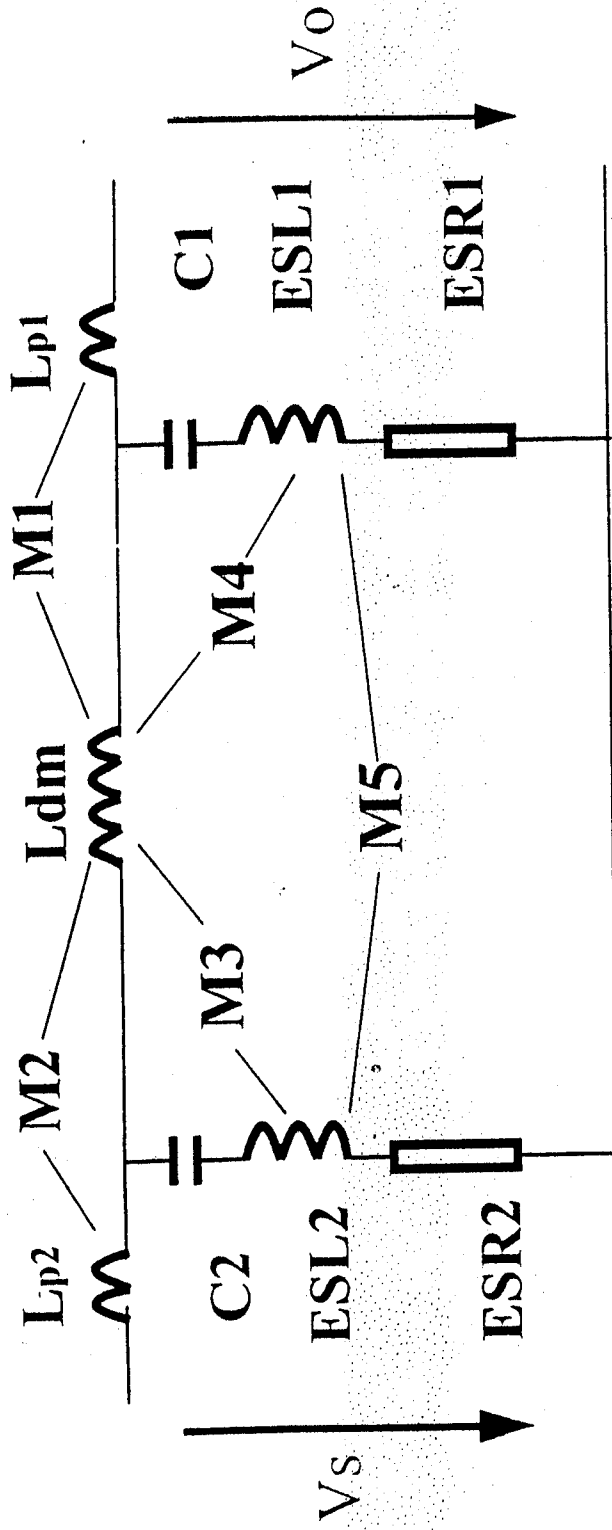The Inductive couplings existing in DM filters




All couplings would affect the capacitor branches;
 The filter performance is affected by these couplings.

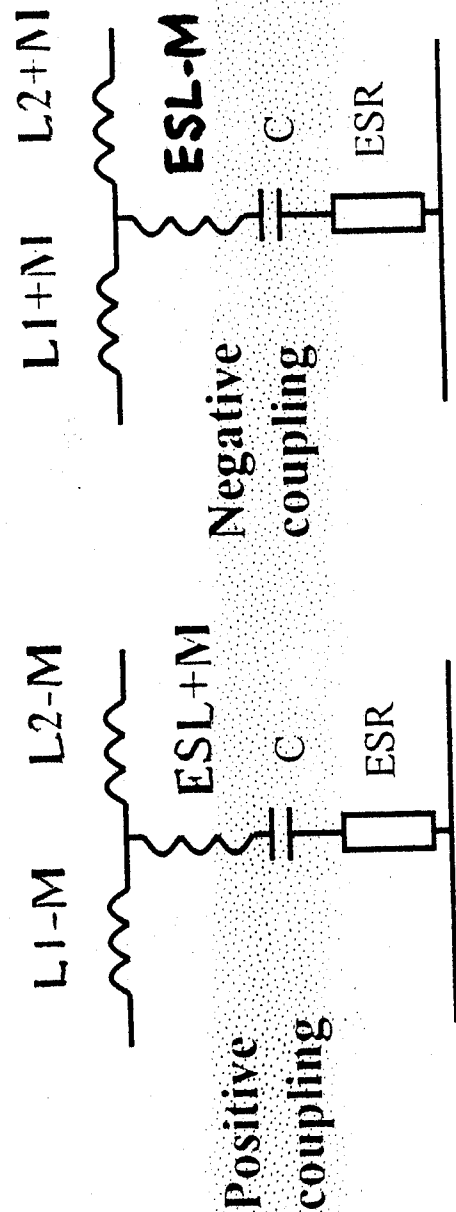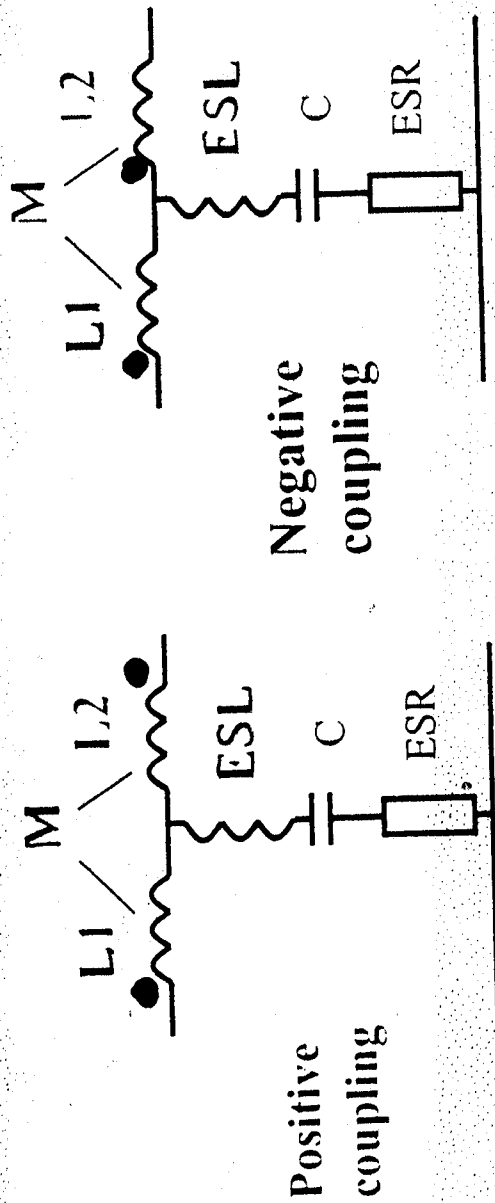The coupling effects in the T filter network




The transfer gain comparison

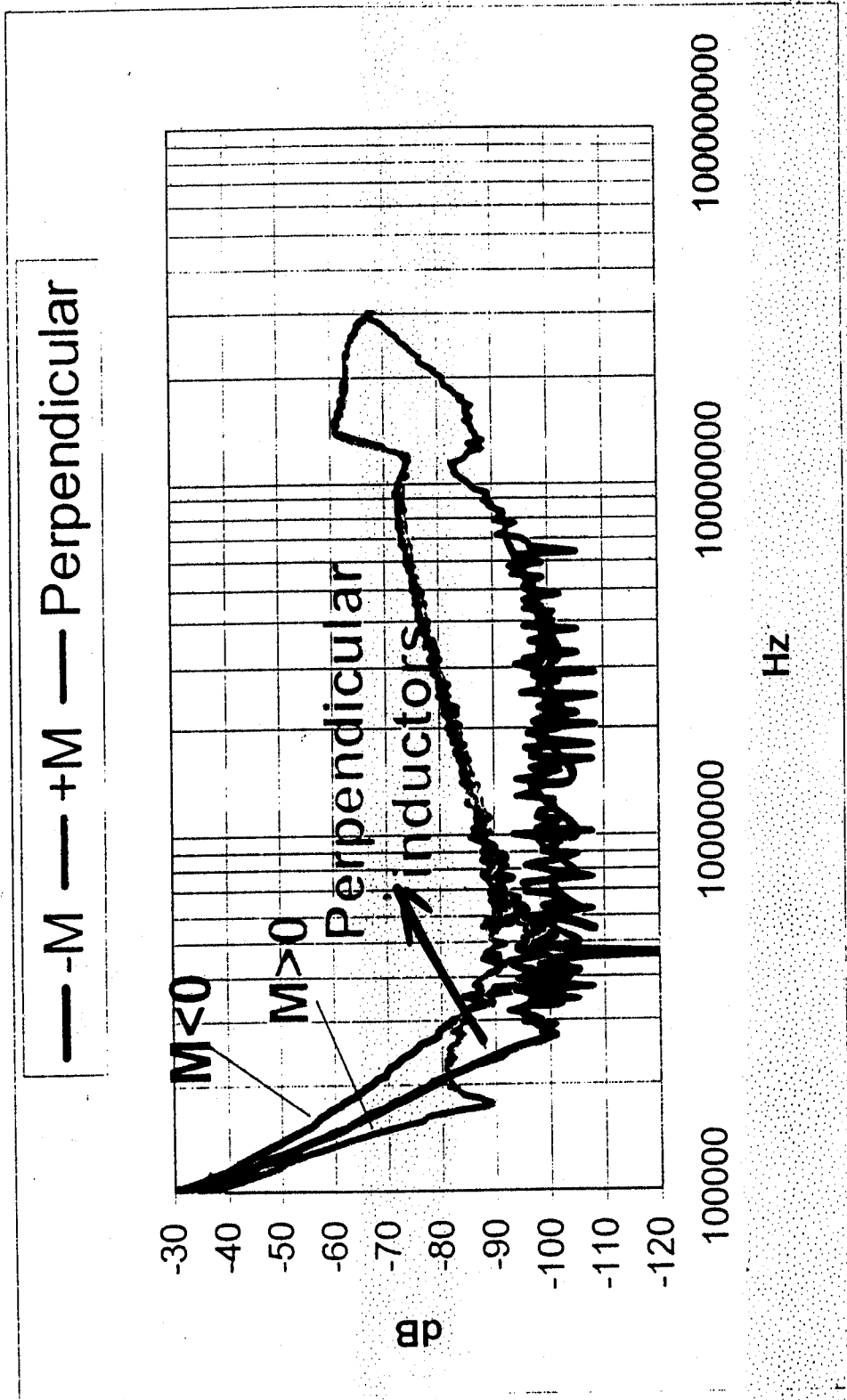



Perpendicular inductors offer the best performance
 at the expense of larger space

The coupling between capacitor branches

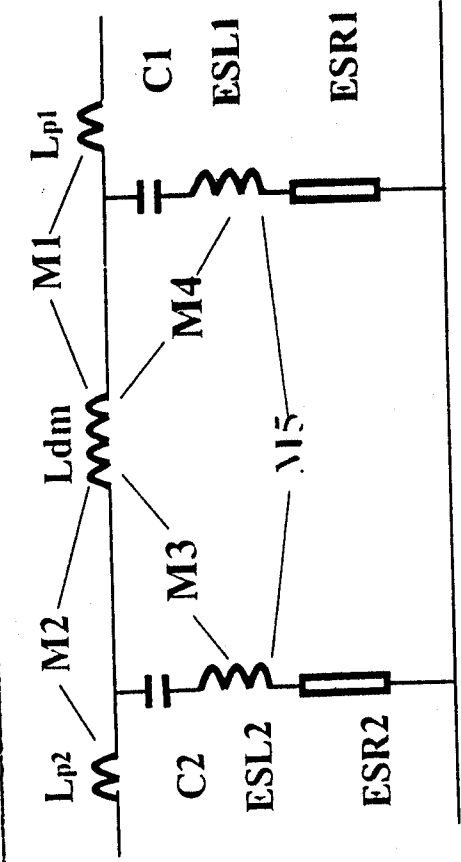

M5 caused by:

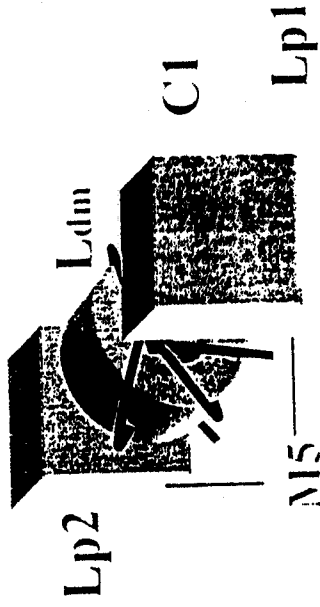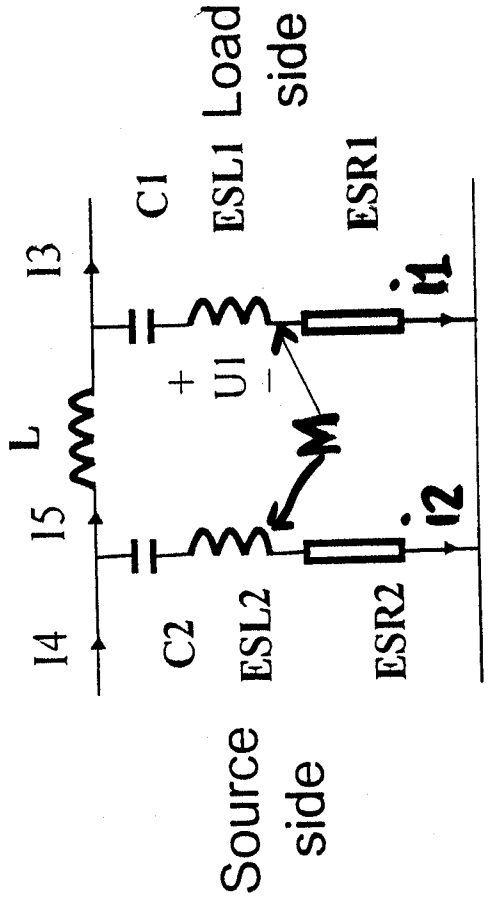- a. Capacitor structure
- b. Pin and layout




$$U_1 = j\omega I_1 \cdot ESL1 + j\omega I_2 \cdot M = j\omega I_1 (ESL1 + \frac{I_2}{I_1} M)$$


$I_2 \gg I_1$, M is amplified by I_2/I_1 times




The coupling between capacitor branches

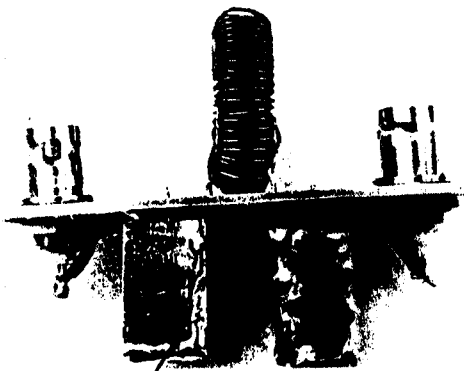


3mil nickel

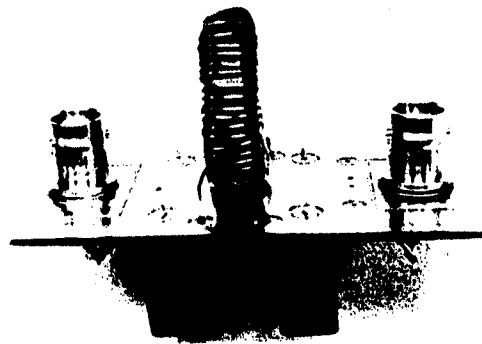


Original

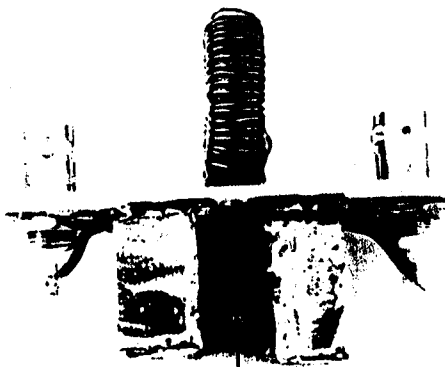

3mil nickel+Magnetic shield


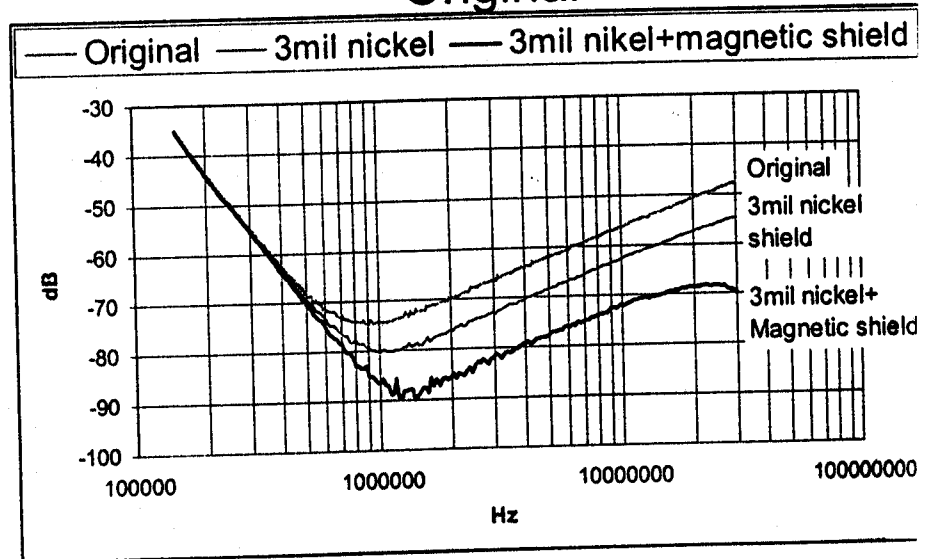


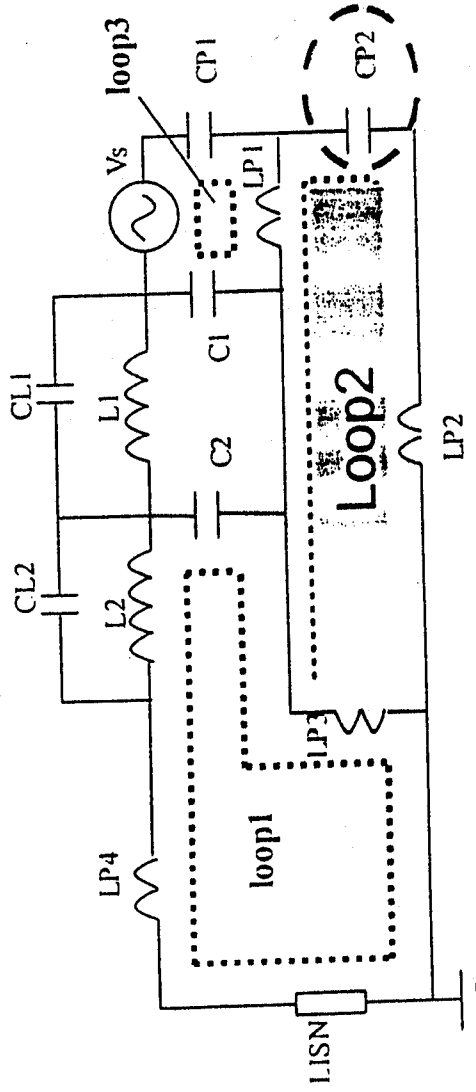CM coupling through the ground-loop resonance




With smaller distance:
Larger Cp2

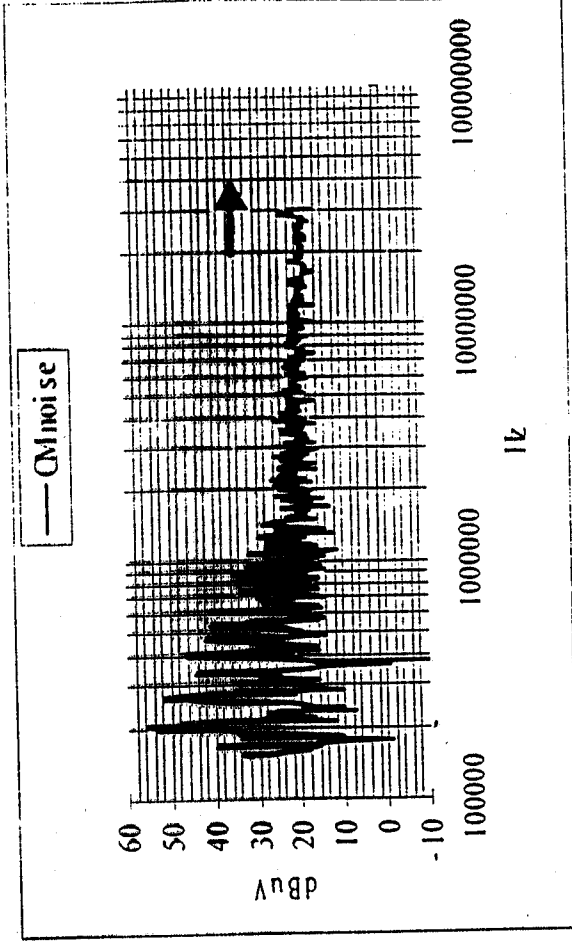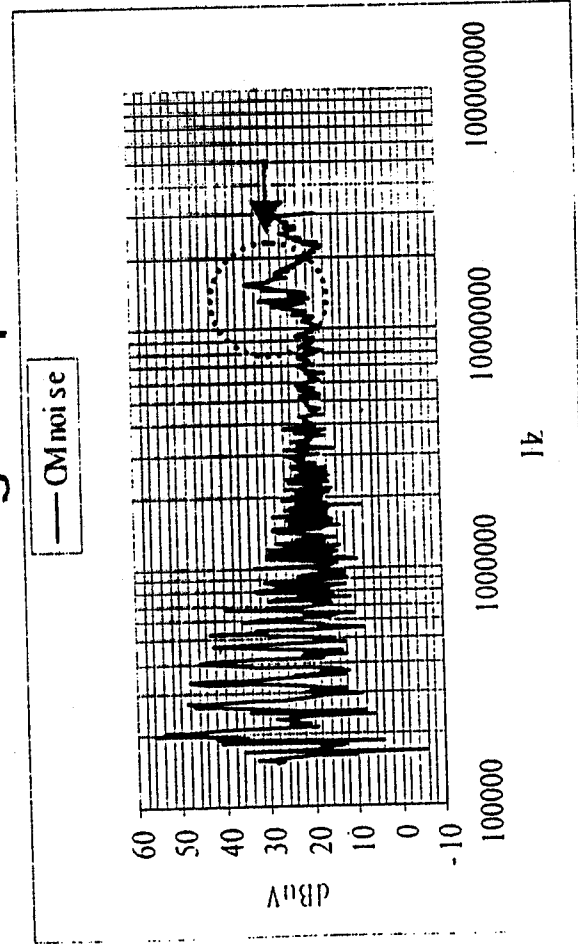With smaller loop2 area:
smaller inductance






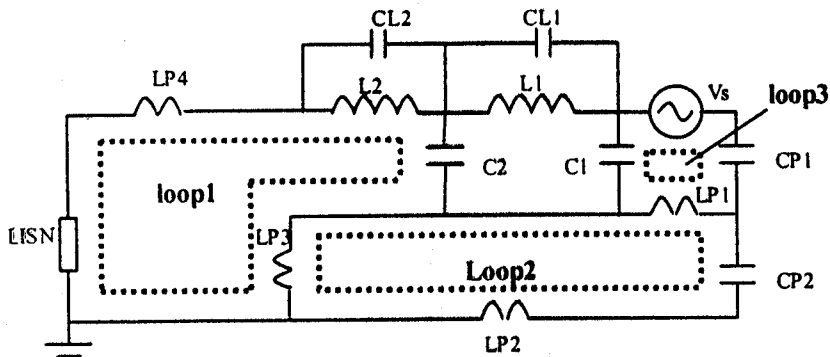CM coupling through the ground-loop resonance



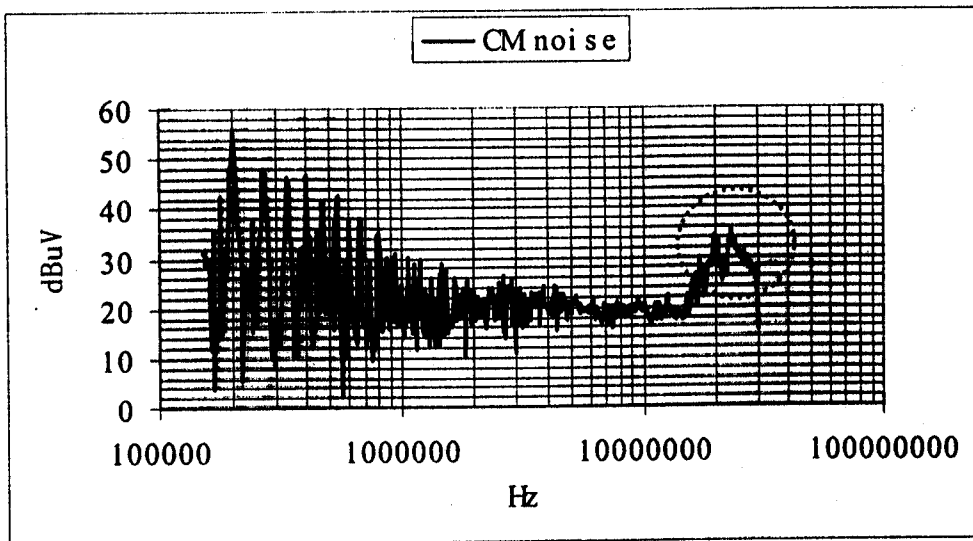
$$f = \frac{1}{2\pi\sqrt{(L_{p1} + L_{p2} + L_{p3})C_{p2}}}$$





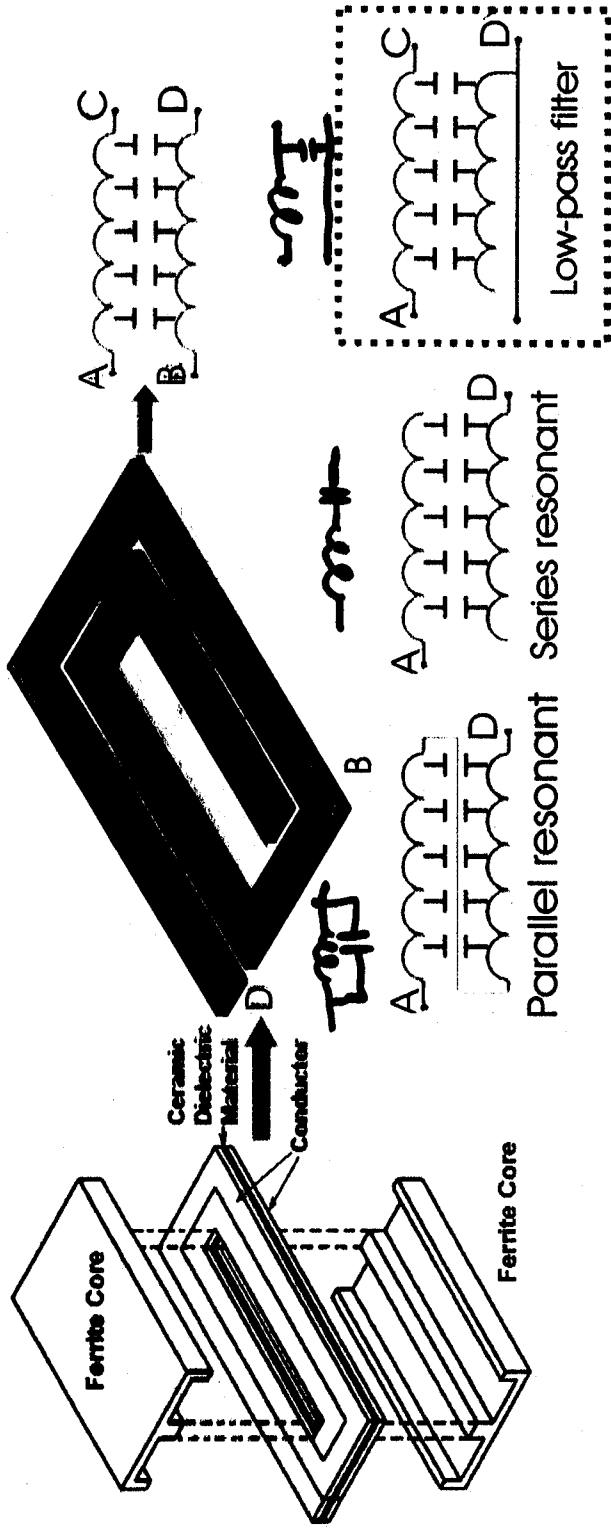Passive Integration Technology: Spiral Winding Planar Integrated L-C




- High permittivity dielectric material between two planar conductive windings
- Distributed structure - multiple resonance points
- Terminal characteristics changeable
- Internal current distribution dependent on termination




Compared with Discrete EMI Filter: Initial Results

CPES

Integrated

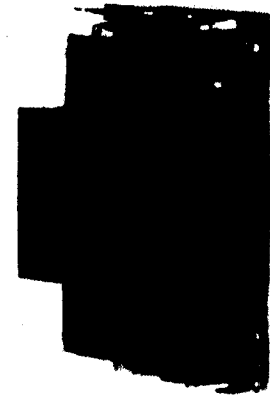


Discrete

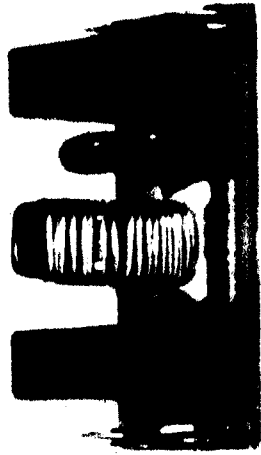


Parameter Comparison

Parameters	Integrated	Discrete
EPC (pF)	3	12
No. of Components	1	5
Profile (cm)	1.6	2.6
Volume (cm ³)	27.4	39.8

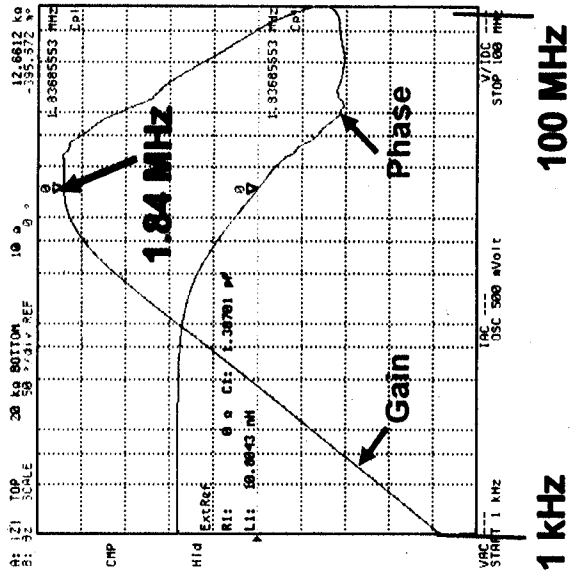
Impedance of Integrated CM Choke (EPC = 3 pF)



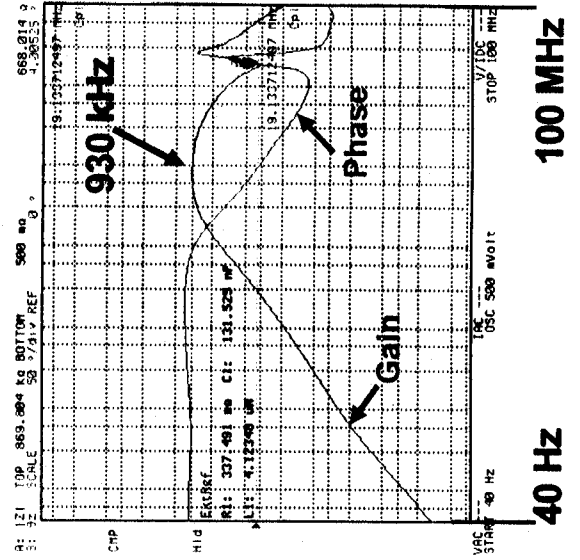
Impedance of Discrete CM Choke (EPC = 12 pF)



Mechanism of Mix-Mode Noise Coupling

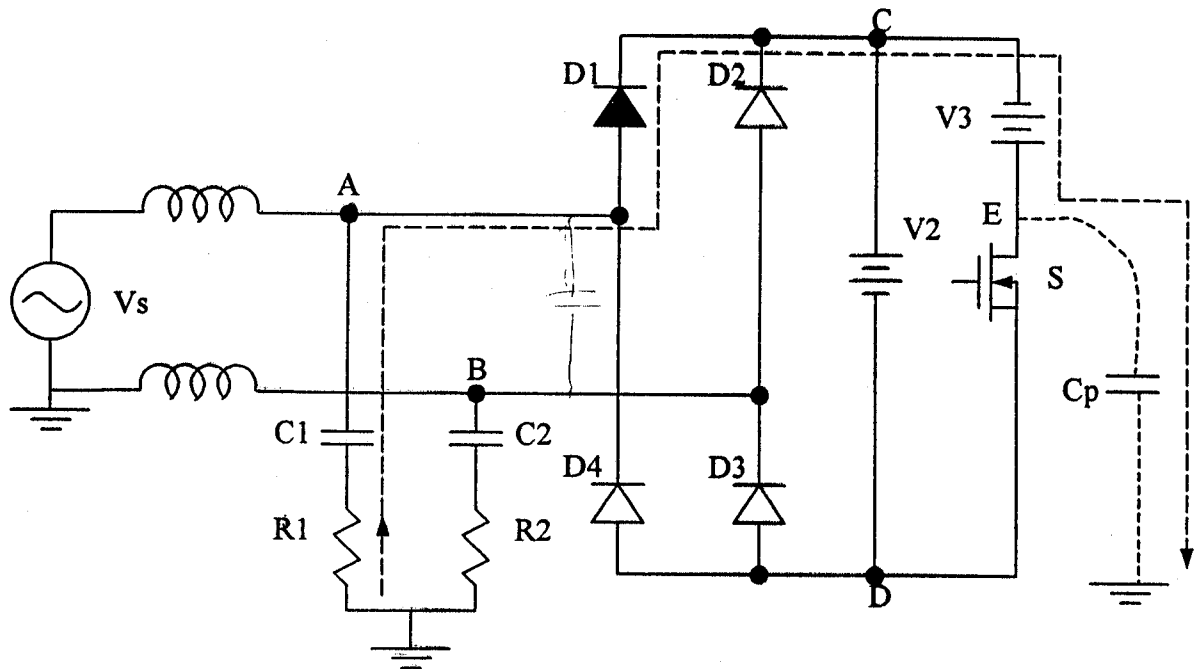


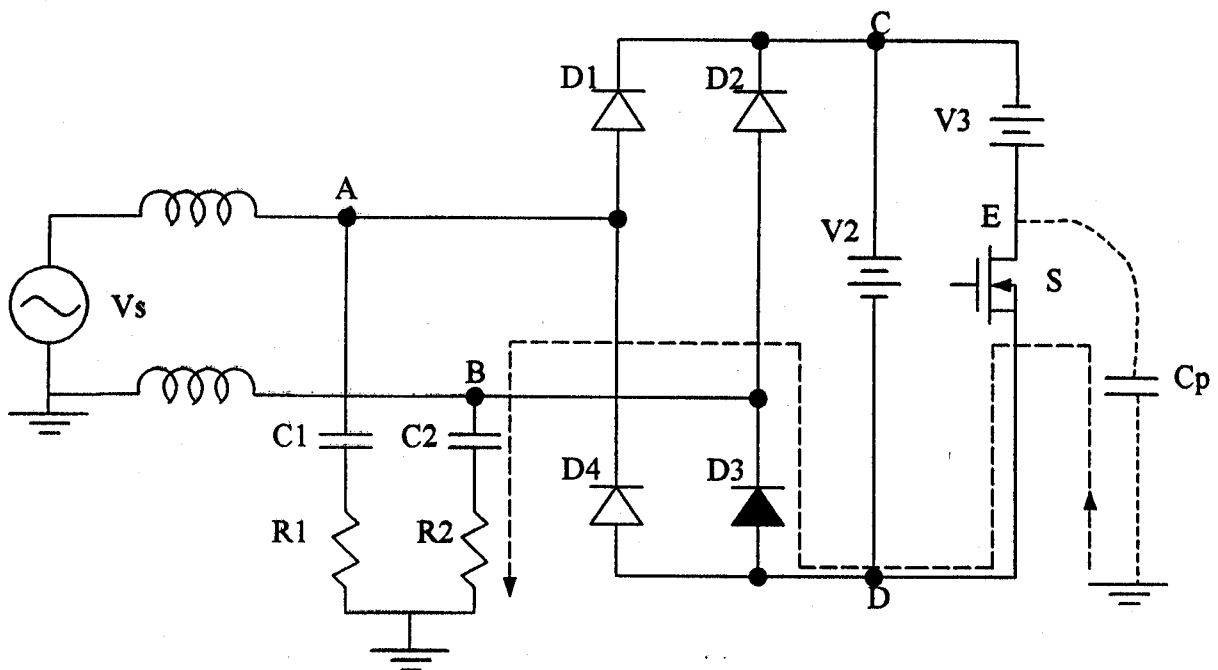Diodes off, MOSFET turned off, C_p charged




Diodes off, MOSFET turned on, C_p discharged

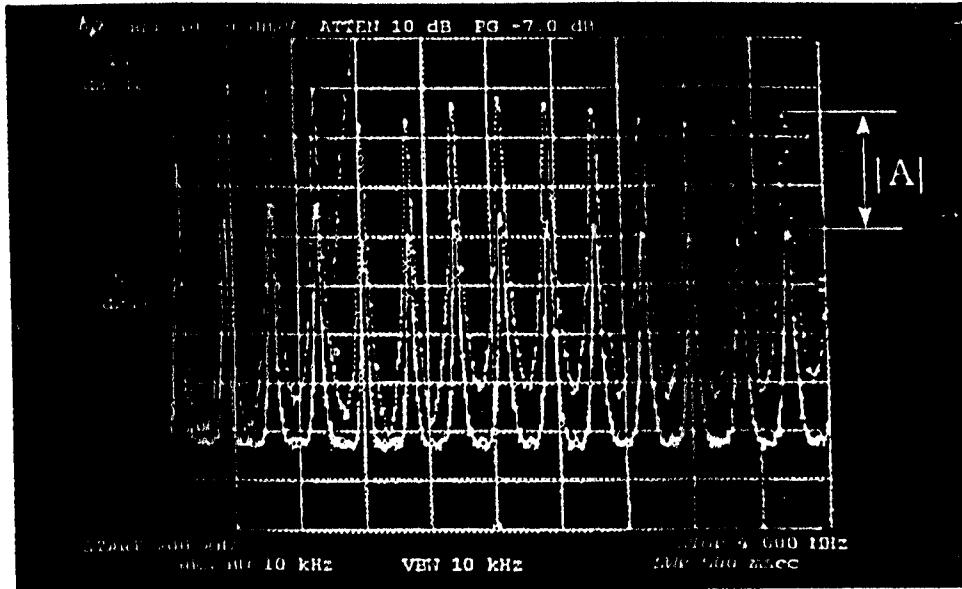EMI Measurement of an Off-line Power Supply



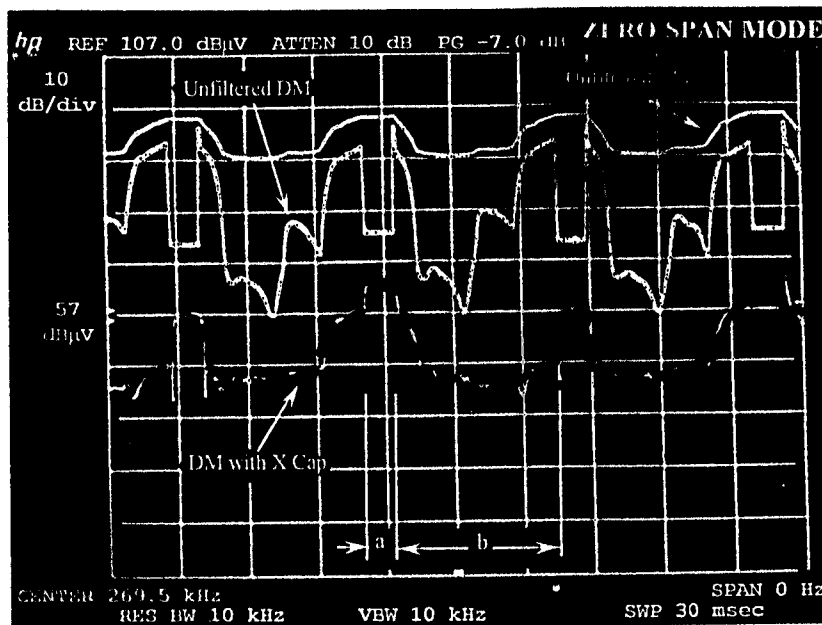- Sweep in the time-domain reserves only maximum values.



Which Side Should the X Cap Be Placed?

Symmetrical Choke

