


One Cycle Control µPFC Circuit Featuring the IR1150S IC


Operating Conditions:

Input		Output	
Min Input Voltage:	85 V	Switching Frequency:	80 kHz
Max Input Voltage:	264 V	Hold-up Time:	20 ms
Input AC Frequency:	50 Hz	Choke Ripple Current:	20 %
Start-up Time:	50 ms		
Target Efficiency:	92 %		


Calculation Result:

Output Conditions		Component Values		
		Component	Ref Des	Std Value
Max Input Power	543 W	High Freq Input Cap	Cin	680 nF
Input RMS Current	6.39 A	Boost Choke Value	Lbst	620 uH
Input Peak Current	9.04 A	Output Capacitor	Cout	470 µF
Input Average Current	5.76 A	Output Voltage Rset	Rfb3	18.7 kOhm
Input Pk Voltage (min)	120 V	Output OVP Rset	Rovp3	18.2 kOhm
Duty Cycle - low line	0.69	Current Sense Res	Rs	0.072 Ohm
Ripple Current	1.81 A	Zero Capacitor	Cz	330 nF
Peak Inductor Current	9.95 A	Gain Resistor	Rgm	3.01 kOhm
V Current Sense	0.76 V	Pole Capacitor	Cp	3.9 nF
Peak Current Limit	13.82 A	Current Sense Filter Capacitor	Csf	1 nF
Input Pk Ovld Current	10.44 A	Current Sense Filter Resistor	Rsf	100 Ohm
Power Distribution		Timing Resistor	Rf	102 kOhm
Power Dissipation Rfb	71.6 mW	Rfb1, Rfb2, Rovp1 and Rovp2 are 499 kOhms each		
Power Diss Rovp	71.4 mW			
Power Rs	2.96 W			

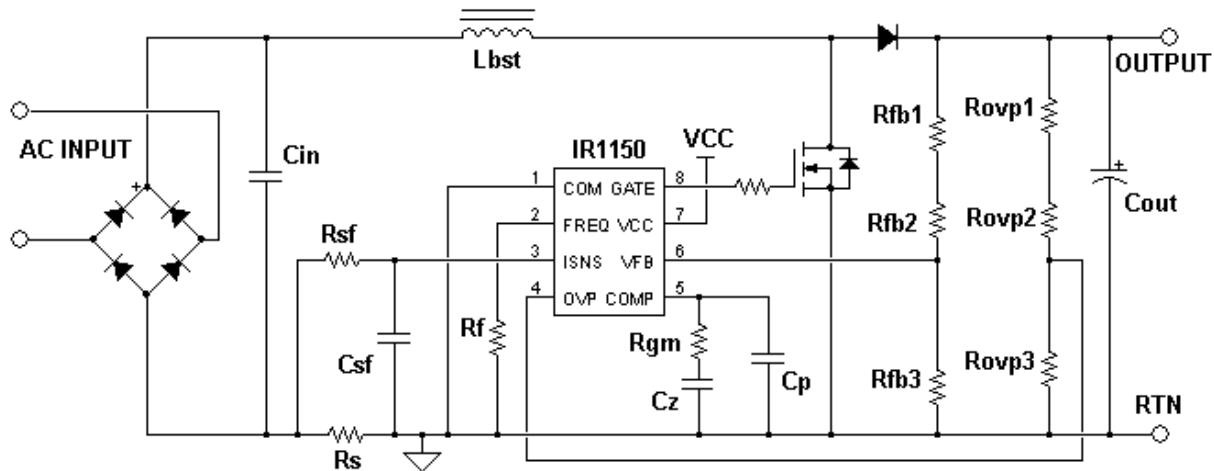


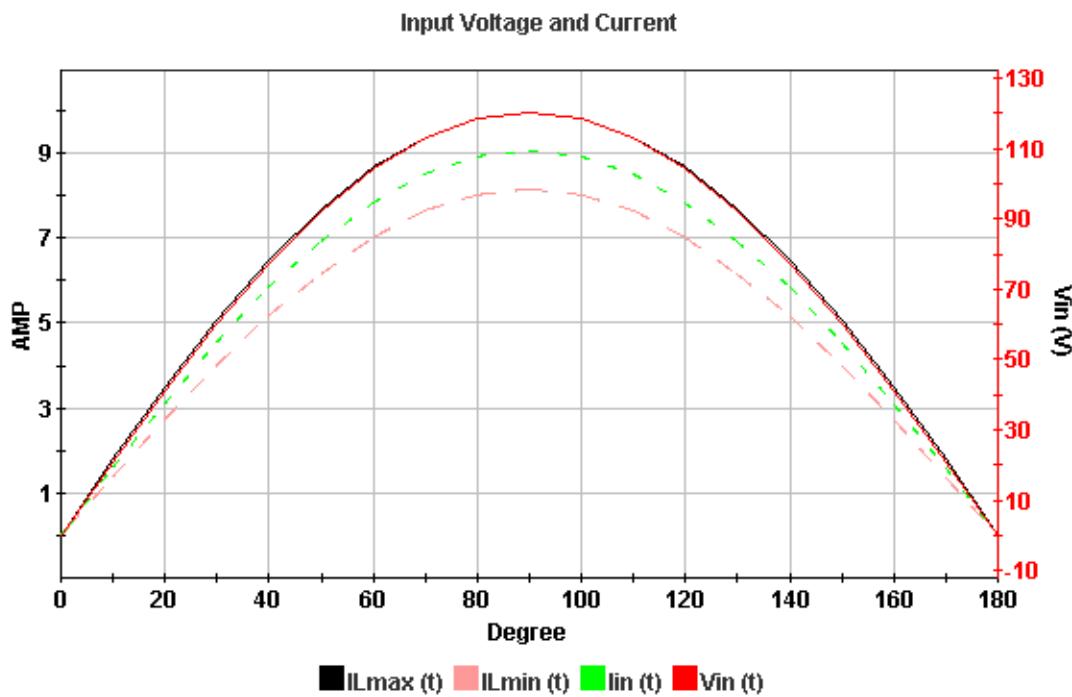


Graph 1: Input voltage and current relationship for this IR1150 power factor correction circuit.

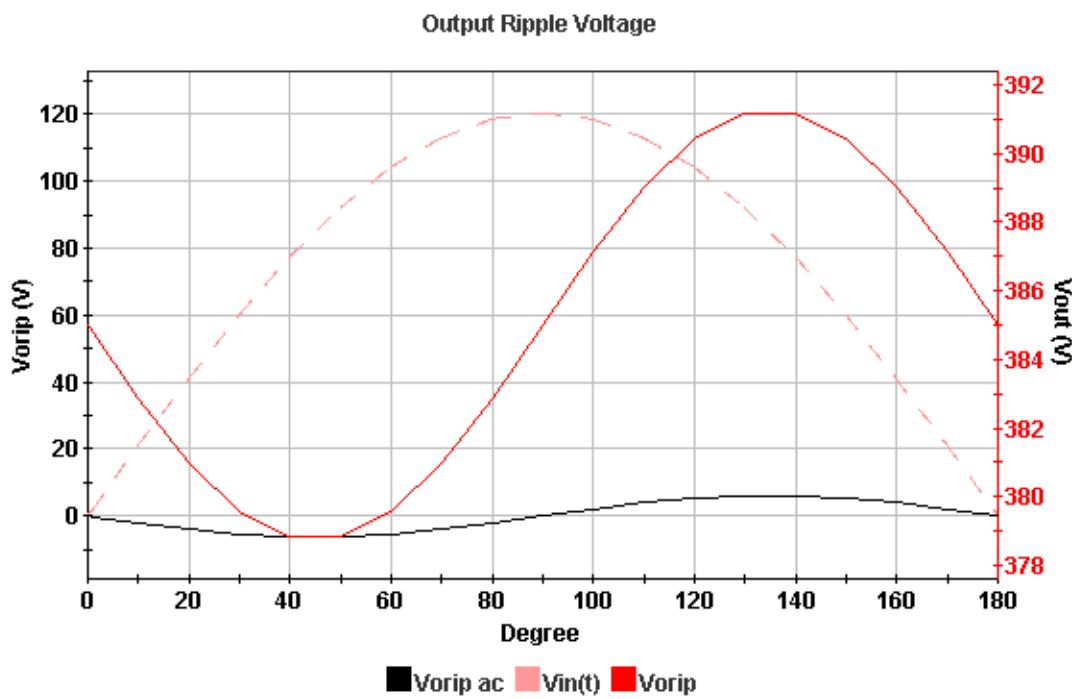


Graph 2: Output voltage ripple amplitude relative to the AC input voltage for this design.

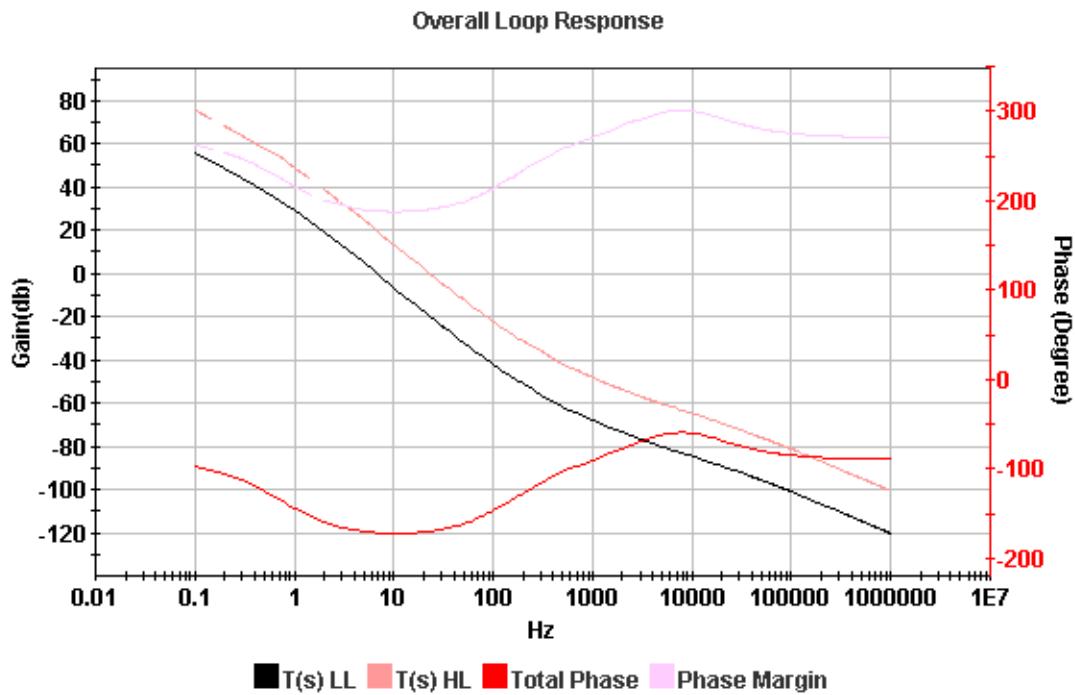

Graph 3: This is the overall feedback loop response of the power factor correction circuit showing phase and gain.

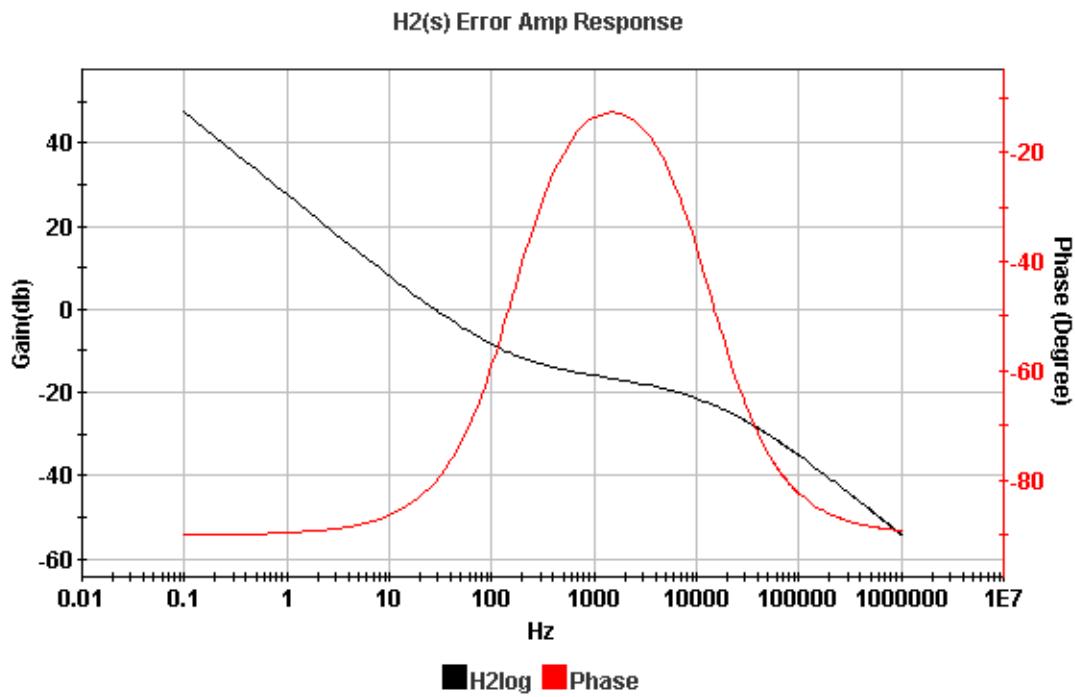

Graph 4: This is the error amplifier response of the power factor correction circuit showing phase and gain.

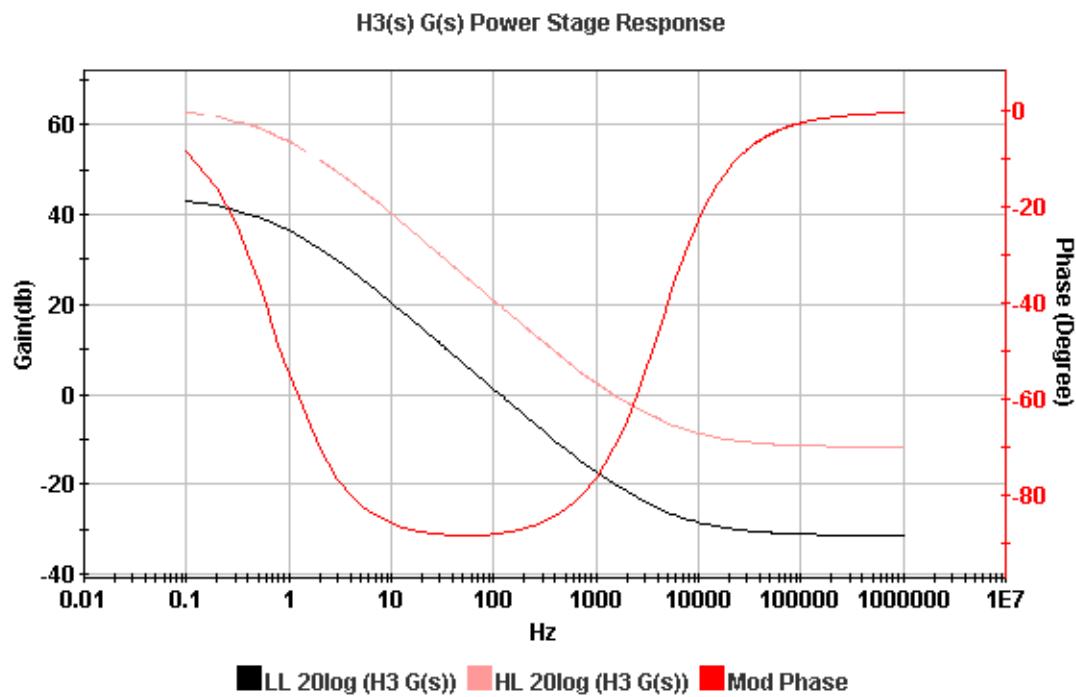

Graph 5: This is the power stage response of the power factor correction circuit showing phase and gain.

Please click [here](#) to send us your comments or suggestions.

[myPowerHome](#)