

# **The Effects of Leakage Inductance on Multi-Output Flyback Circuits**

*by Lloyd Dixon*

**TOPIC 2**

# THE EFFECTS OF LEAKAGE INDUCTANCE ON MULTI-OUTPUT FLYBACK CIRCUITS

Lloyd H. Dixon, Jr.

A similar topic dealing with buck-derived regulators was presented at previous Unitrode seminars (see Section P2). Leakage inductance is also the major cause of poor cross-regulation in flyback circuits, but the circuit analysis is quite different. This topic shows how to predict and minimize the effects of leakage inductance and wiring inductance in continuous and discontinuous mode flyback regulators.

**Introduction:** A typical flyback regulator circuit with two outputs is shown in Figure 1. The flyback "transformer" is actually an inductor with multiple windings. While the transistor switch is ON, the inductor draws increasing current from the input and stores this energy. During the ON time, the output rectifiers are reverse biased (note the polarity dots). When the transistor turns OFF, the inductor ampere-turns cannot instantaneously change. The voltages across all inductor windings reverse or "fly back" forcing the ampere-turns that were flowing in the primary to transfer to the secondary windings. The previously stored energy is then delivered to the outputs.

 


Figure 1 - FLYBACK CONVERTER

A flyback regulator may be operated in the continuous or discontinuous inductor current modes. Idealized current waveforms for the discontinuous mode (at full load) are shown in Figure 2a, which assumes a 1:1 turns ratio. By definition, the inductor current starts at zero at the beginning of each switching period. All of the energy stored during the ON time is delivered to the outputs and the current is back to zero before the end of each period. In the continuous mode shown in Figure 2b, the inductor current is never zero during normal operation, and the inductor holds much more energy than is taken from the input and delivered to the output each switching cycle.

 


Figure 2 - Inductor Current Modes

These two inductor current operating modes have radically different operating characteristics, with divergent opinions by experienced designers as to which mode is better. Note that for the same average output current (same power output), the discontinuous mode reaches nearly twice the peak current required in the continuous mode. However, as indicated by the relative inductor current slopes, the continuous mode typically employs 10 times the inductance value and requires  $10/1.8^2 = 3$  times the inductor energy storage capability as the discontinuous mode.

**Non-Ideal Aspects:** All flyback circuits depend upon inductive energy storage. This is usually accomplished by introducing a small non-magnetic gap in series with the inductor core. Unfortunately, the inductor windings cannot all be equally well coupled to the energy storage gap because of the physical separation between the windings. Additional amounts of magnetic energy are also stored between and within the windings. These amounts of energy are represented in the circuit as leakage inductances.

When the transistor turns off, leakage inductance between transformer primary and secondaries will fight the transfer of current to the secondaries, causing a large voltage spike to occur across the transistor. This inductive spike must be clamped to a voltage level less than the transistor rating or the transistor will be destroyed. (Figure 1 does not show this necessary clamp.) There are many possible clamping methods -- with some, the energy put into the clamp is lost, hurting circuit efficiency, with other methods the clamp energy is conserved. The two-transistor 150 Watt Flyback Regulator Design Review (Section A3) saves this energy by returning it to the input.

Leakage inductance between secondaries, together with wiring inductances from each secondary to its respective filter capacitor, are the main cause of poor cross-regulation between the outputs.

Circuit diagrams such as Figure 1 seldom show these many parasitic inductive elements which play such an important role in flyback circuit performance. Circuit analysis becomes complex and confusing when all these elements are included, compounded by the differing turns ratios between the windings.

**The Normalized Equivalent Circuit:**

Considerable simplification is possible as shown in the normalized equivalent circuit of Figure 3. In the normalized circuit, the actual circuit values associated with each winding have been translated according to the actual turns ratios into equivalent circuit values with 1:1 turns ratios. Since input-output isolation is not relevant to this analysis, the ideal 1:1 transformer may then be discarded and the windings directly interconnected. When the analysis is completed, the resulting values may be "de-normalized" to their actual values according to the turns ratios.

 


Figure 3 - Normalized Circuit

For example, assume an off-line regulator with a 30:1 turns ratio between primary and 5V secondary, and a 3:1 turns ratio between 15V secondary and the 5V secondary. Normalization may be with respect to any winding. In this case, all windings are normalized to the 5V winding by dividing each voltage and multiplying current by the actual turns ratio. Inductance and resistance are divided and capacitance multiplied by the turns ratio squared. Referred to the 5V secondary, a  $V_{in}$  of 300V divided by the turns ratio of 30 translates to  $V_{in}'$  of 10V. Primary inductance of 450 $\mu$ H divided by 30<sup>2</sup> becomes 0.5 $\mu$ H. The V2 of 15V at 4A secondary becomes V2' of 5V at 12A, etc.

The normalized circuit of Figure 3, mutual inductance  $L_C$  represents energy stored in the gap,  $L_{CA}$  represents leakage inductance between primary and secondary A, and  $L_{AB}$  is the leakage inductance between secondaries A and B. Mutual inductance  $L_C$  is connected directly to  $V_{in}'$  through the transistor or to  $V_{CL}'$  through the clamp diode, whereas outputs V1 and V2' are coupled to  $L_C$  through leakage inductances and secondary wiring inductances  $L_{W1}$  and  $L_{W2}$ . Primary wiring inductance is negligible because it is divided by 30<sup>2</sup>. This Figure 3 configuration applies when the primary winding is closest to the gap -- either inside the secondaries with the centerleg gapped or outside the secondaries with the outer leg gapped. If the primary were on the other side of the secondaries opposite the gap, the equivalent circuit would have  $L_C$  connected to point B instead of point C.

To further simplify the analysis, output ripple voltages are assumed to be zero. The error caused by this assumption is small in a practical power supply and its effect nearly averages out over a complete switching period.

Energy Lost to the Clamp: The continuous mode waveforms of Figure 4 show two non-ideal occurrences, both caused by leakage and wiring inductances which fight the transfer of current from primary to secondary when the transistor switches on and off. The leakage inductances plus wiring inductances are normally a small fraction of the primary inductance  $L_C$ . Assuming V1 and V2' are substantially equal, the leakage and wiring inductances may be combined:

$$L_{ps} = L_{CA} + \frac{L_{W1}(L_{AB}+L_{W2}')}{L_{W1}+L_{AB}+L_{W2}'}$$

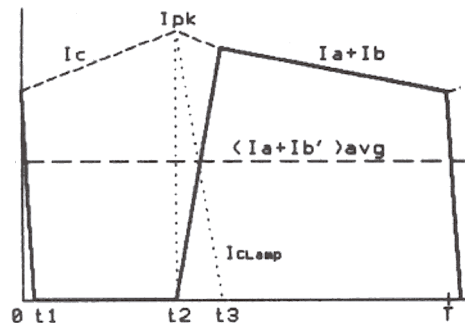


Figure 4 - Current Transfer

Immediately before the transistor turns on at  $t_0$ , inductor current  $I_C$  equals  $I_{CA}$  and flows through  $L_{ps}$  to the outputs. At  $t_0$ , the transistor pulls point C down to  $-V_{in}'$ . However,  $I_{CA}$  cannot instantaneously decrease, which prevents  $I_C$  from immediately transferring to the input. The time required for  $I_{CA}$  to reach zero and  $I_C$  transfer to be completed is (neglecting diode drops):

$$t_1 = (V_{in}' + V_1) / L_{ps}$$

Some of the energy in  $L_{ps}$  when the transistor turns on transfers to  $L_C$ , the rest goes to the output - none is lost.

This turn-on transfer problem cannot occur in the discontinuous inductor current mode because  $I_{ca}$  is always zero before the transistor switches on.

A much more serious transfer delay occurs when the transistor switches off at time  $t_2$ . At  $t_2$ , inductor current  $I_C$  is at its maximum peak value, but current  $I_{ca}$  through  $L_{ps}$  is zero. The voltage across  $L_C$  reverses in an attempt to force  $I_C$  through  $L_{ps}$ .  $I_{ca}$  cannot change instantaneously, so  $L_C$  forces its current into the clamp.  $I_{ca}$  rises according to the voltage  $V_{CL}' - V_1$  across  $L_{ps}$ , and  $I_{CL}'$  decreases in a complementary manner as shown in Figure 4. The transfer time is:

$$t_3 - t_2 = I_C(pk) \frac{L_{ps}}{V_{CL}'(1 + L_{ps}/L_C) - V_1} \quad (2)$$

With  $V_1 = V_2' = V_{out}$ , the energy transferred into the clamp is:

$$W_{clamp} = \frac{L_{ps} I_{pk}^2}{2} \cdot \frac{1}{1 + L_{ps}/L_C - V_1/V_{CL}'} \quad (3)$$

This equation also applies to the discontinuous inductor current mode. It also may be used (with a small error) when the primary winding is opposite the gap, or when the primary is split and interleaved on both sides of the secondaries. (Interleaving will reduce  $L_{ca}$  by a factor of 3 and accordingly reduce the energy lost to the clamp.)

The energy diverted from the output to the clamp hurts open loop load regulation, but this is not very significant because the closed loop feedback easily corrects for this. But in order to maintain reasonable efficiency in flyback supplies of more than a few Watts output this energy must be recovered in some way rather than allow it to be dissipated. The two-transistor circuit shown in Section A3 accomplishes this quite easily with a pair of cross-connected diodes which return the energy to the  $V_{in}$  source. Single transistor flyback circuits usually employ a single diode with an added winding bifilar with the primary. Even when the clamp energy is conserved, it should be minimized because it increases the current in the transistor and the energy storage requirement of the flyback transformer.


As equation (3) reveals, the energy delivered to the clamp equals the energy stored in the primary-secondary leakage inductance,  $L_{ps}$ , increased by the fraction on the right whose denominator is usually considerably less than 1. The  $L_{ps}/L_C$  term is almost negligible, but  $V_1/V_{CL}'$  is 0.5 when the clamp voltage is twice  $V_1$  (as in the example used). In this case, the energy sent to the clamp is twice the energy stored in  $L_{ps}$ . In order to minimize the energy diverted to the clamp, it is important to (1) minimize  $L_{ps}$  which consists of leakage inductances and wiring inductances, (2) make the clamp voltage  $V_{CL}'$  as large as possible compared to  $V_1$  (but this will increase the transistor  $V_{CE}$  requirements).

Table I shows that in the same application -- 100 W, 100 kHz -- the continuous mode circuit puts only 8.48 Watts into the clamp vs. 15.99 Watts

for the continuous mode. Even though  $I_{pk}$  in the discontinuous mode is almost twice as large, primary-secondary inductance  $L_{ps}$  is 6 times smaller which gives the advantage to the discontinuous mode. The  $L_{ps}$  would be even smaller favoring the discontinuous mode even more but the wiring inductance which is the same in both circuits is a much more significant portion of the discontinuous mode  $L_{ps}$ .

Cross-Regulation in the Continuous Mode:

Figure 5 shows the secondary current waveforms of the two-output flyback circuit of Fig. 3 operated in the continuous inductor current mode and with equal normalized output voltages ( $V_1 = V_2'$ ).  $L_C + L_{CA}$  together force current  $I_C$  into both outputs. The division of this current between the two outputs is determined by the inductances  $L_{w1}$  and  $L_{ab} + L_{w2}'$  in series with the outputs.

 

Let output #1 inductance  $L_1 = L_{w1}$ , and output #2 inductance  $L_2 = L_{ab} + L_{w2}'$ . Figure 5 - Two Outputs,  $V_1 = V_2'$   
 At the beginning of the off time, point C is at  $V_{clamp}$ . The voltages across  $L_1$  and  $L_2$  are equal. At the beginning of the OFF time ( $t_3$ ), peak  $I_C$  divides into  $I_a$  and  $I_b$ :

$$I_a = \frac{I_C \cdot L_2}{L_1 + L_2} ; \quad I_b = \frac{I_C \cdot L_1}{L_1 + L_2} \quad (4)$$

Let  $L_t = L_C + L_{CA}$ . After current transfer to the secondaries is completed at  $t_3$ ,  $L_t$  freewheels across  $V_1 (=V_2')$ , forcing current  $I_C$  into the parallel combination of  $L_1$  and  $L_2$ . The downslope of  $I_C$  and the average  $I_C (=I_a + I_b)$  is determined by  $V_{out}$  across  $L_t$ .  $L_1$  and  $L_2$  have almost no effect on the total output current because  $L_t$  is very much larger than  $L_1$  and  $L_2$  in parallel. The total output current  $I_C$  ( $I_a + I_b$ ) is maintained by the control loop at the level required to keep the output voltages in regulation.

With  $V_1 = V_2'$ , the voltages across  $L_1$  and  $L_2$  are equal during the entire OFF time, so that not only are the peak  $I_a$  and  $I_b$  values proportioned to peak  $I_C$  according to the inductor ratios of equation 4, but their current slopes and average output currents have the same proportional relationships.

So with zero output voltage differential, the average currents  $I_a$  and  $I_b$  are apportioned strictly by  $L_1$  and  $L_2$  as per equation 3 and their ratio is inversely proportional to the inductances:

$$I_a / I_b = L_2 / L_1$$

However, the actual load currents cannot be expected to observe the ratio established above. To change the  $I_a / I_b$  ratio consistent with actual load current requirements requires a small differential voltage,  $\Delta V_{12}$ , between output voltages  $V_1$  and  $V_2$ . This differential is so small compared to  $V_1$  and  $V_2$  that it has negligible effect on the total current  $I_a$  and  $I_b$ , but it will cause the current slopes in  $L_1$  and  $L_2$  to diverge, changing the apportionment of average current between  $I_a$  and  $I_b$ .

Figure 6 shows what happens when  $I_b$  is reduced by 25% below the value set by the inductor ratio. The dash line shows the current waveforms when  $V_1 = V_2'$ , as in Figure 5. Suppose  $I_b=6A$ ,  $I_a=12A$  so that  $I_c=18A$ . If the load on output #2 changes causing  $I_b$  to drop 25% to 6A but  $I_a$  stays at 12A, then  $I_c$  must drop by the same 2A to 16A. The control loop will make this happen. However, if  $V_1$  remains equal to  $V_2'$   $I_a$  and  $I_b$  will drop proportionately, by 1.333A and .667A respectively, as shown by the dotted lines. In order to reduce  $I_b$  by 2A and keep  $I_a$  at the original level, a small differential voltage  $\Delta V_{12}$  will appear between  $V_1$  and  $V_2$ .  $V_2$  will become more positive than  $V_1$ , increasing the  $I_b$  downslope and in this case causing  $I_a$  to slope upwards. The solid lines in Figure 5 show the resulting waveforms. Note that the slopes change but not the initial peak values.

 


Figure 6 - Two Outputs,  $\Delta V_2 = 2\%$

The voltage differential  $\Delta V_{12}$  is the output voltage cross-regulation error accompanying the change in load current on one output. The error will appear in whichever output is not sensed and regulated by the control circuit, regardless of which output experiences the load change. The magnitude of the cross-regulation error is:

$$\Delta V_{12} = \frac{2\Delta I_b \cdot L_2}{\pi(1-D)^2} = - \frac{2\Delta I_a \cdot L_1}{\pi(1-D)^2} \quad (1-D) = V_{in}/(V_o+V_{in}) \quad (5)$$

Where  $D$  is the duty cycle and  $T$  the switching period =  $1/f_s$ . In the continuous mode example given in Table I,  $L_1$  is .02  $\mu H$  while  $L_2$  is .07+.012 = .082  $\mu H$ . With  $\Delta V_{12} = 0$ ,  $I_a/I_b = .082/.02 = 4/1$ . Having  $I_a$  4 times greater than  $I_b$  with  $\Delta V_{12} = 0$  is probably acceptable if output #1 has most of the load power requirement of the supply, because a relatively small  $\Delta V_{12}$  can make the necessary adjustment. (Normalized load currents are proportional to load power because the normalized voltages are the same.)

With  $D=.36$  and  $T=10\mu sec$ , equation 5 predicts  $\Delta V_{12}$  of .01V for a 1A change in  $I_a$  (10 m $\Omega$ ). This is a 0.2% change in voltage for an 8.33% change in current. For a 1A change in  $I_b$  the voltage differential is -.04V (40 m $\Omega$ ). This is a .8% change in voltage for a 16.7% change in current. If the #1 output is actually 15V with a 3:1 turns ratio, the latter translates to an actual .12V differential for a 1/3 A change, or 0.36 $\Omega$ .

Note that equation 5 shows a linear relationship between current and voltage changes. But be careful. If  $\Delta V_{12}$  becomes too large, the  $I_1$  or  $I_2$  downslope may reach zero current before the end of the switching period. The output reaching zero becomes discontinuous and the cross-regulation becomes much worse. Equation 5 no longer applies. If the output that becomes discontinuous is sensed for closed loop control, the loop gain characteristics probably change (this has not been evaluated).

Equation 5 also shows that cross-regulation improves when duty cycle  $D$  smaller, which occurs with high  $V_{in}$ .

Cross-regulation in the Discontinuous Mode:

The waveforms of Figure 7 show the secondary currents of the Figure 3 flyback circuit operated in the discontinuous mode with  $V_1 = V_2'$  ( $\Delta V_{12} = 0$ ). The peak values, the downslope and the average current values are all proportioned the same as determined by  $L_1$  and  $L_2$ , just as with the continuous mode. Equation 4 applies to the discontinuous mode, as well. However, in the discontinuous mode, all the inductor values are much smaller (except for wiring inductance) so that the slopes are much steeper, and the peak current is nearly twice the discontinuous mode. Transfer time  $t_3 - t_2$  is much shorter and less energy goes to the clamp.

 


Figure 7 - Two Outputs,  $V_1$

In the discontinuous mode example given in Table I,  $L_1$  and  $L_2$  are both  $.02\mu\text{H}$ , dominated by winding inductances. This means that with  $V_1 = V_2$ ,  $I_a$  and  $I_b$  are equal (not as shown in Figure 7). If  $\Delta V_{12}$  is changed to decrease  $I_a$  and increase  $I_b$ , the current waveforms in an actual flyback circuit will look like Figure 8. The current in one secondary looks like a spike, while the other secondary has a rounded waveform. The curvature is because of small voltage changes across the output capacitors and their ESRs. In spite of the strange shape, the normalized currents add up to the expected triangular waveform.

 


Figure 8

Figure 9 shows the situation of Figure 7 with  $I_b$  reduced in current and  $I_a$  constant. The explanation of its behavior is similar to the continuous mode example of Figure 6. If  $I_b$  is decreased by 2A and  $I_a$  stays the same, then the control circuit must reduce  $I_c$  by 2A. But this will cause the average  $I_b$  and  $I_a$  to decrease proportionately by .667A and 1.33A respectively as shown by the dotted lines. So an output voltage differential  $\Delta V_{12}$  is necessary in order to decrease the downslope of  $I_a$  to maintain its original average value, and increase the downslope of  $I_b$  to reduce its average value by the desired 2A.

 


Figure 9 - Two Outputs  $\Delta V_2' = 2\%$



Compared to the continuous mode, there is one big difference: In the discontinuous mode, one triangle becomes a trapezoid ( $I_a$ ), while the other triangle gets a smaller base. The relationship between voltage changes and current changes is much more complex and non-linear:

$$\Delta I_a = \frac{I_{a0}}{(V_1 \cdot L_p / (\Delta V_{12} L_t) + 1)}, \quad \Delta I_b = \frac{I_{b0}}{(V_1 \cdot L_p / (\Delta V_{12} L_t) + 1)} \quad (6)$$

Where  $L_p$  is the parallel combination of  $L_1$  and  $L_2$ .  $\Delta I$  is solved in terms of  $\Delta V$  rather than the other way around because the equation is much simpler. Because of the non-linearity of the  $\Delta V$ - $\Delta I$  relationship, the changes must all be calculated from a specific starting condition, which is with  $V_1 = V_2$  ( $\Delta V=0$ ), as depicted in Figure 7.  $I_{a0}$  and  $I_{b0}$  are the average values under this condition, which must be predefined.

For the example given in Table I,  $I_{a0}/I_{b0} = L_2/L_1 = .02/.02$ . Therefore  $I_{a0}$  equals  $I_{b0}$ . Taking an arbitrary starting point of 9A total normalized output current,  $I_{a0}$  and  $I_{b0}$  will both equal 4.5A. Using equation 6,  $\Delta V_{12}$  calculates to be .019V (.019m $\Omega$ ). Note from the form of equation 6 that  $\Delta I_a$  changes proportional to the starting value of  $I_{a0}$  with  $\Delta V_{12}$  fixed. Thus a  $\Delta V_{12}$  of .019V will support a 2A  $\Delta V_{12}$  if  $I_{a0}$  and  $I_{b0}$  are raised to 9A (.0095m $\Omega$ ).

TABLE I -- DISCONTINUOUS VS. CONTINUOUS MODE EXAMPLE

Input: 100 W ,  $f_s$ : 100 kHz Refer to Figure 3

	<u>Continuous Mode</u>		<u>Discontinuous Mode</u>	
	<u>Actual</u>	<u>Normalized</u>	<u>Actual</u>	<u>Normalized</u>
Core Type, (Area Product	EC35 (AP=.94)		LP22/13 (AP=.33)	
Primary: Turns	180	6	60	2
$V_{in}$	-300	-10	-300	-10
$I_{in}(pk)$	1.1	33	2.0	60
$V_{CL}$ (clamp)	300	10	300	10
Output 1: Turns	6	6	2	2
$V_1$	5	5	5	
$I_1$	12	12	12	
Output 2: Turns	18	6	6	
$V_2$	15	5	15	
$I_2$	2	6	2	
Windings are <u>not</u> interleaved				
$L_c$		5 $\mu H$		0.5 $\mu H$
$L_{ca}$		.14 $\mu H$		.016 $\mu H$
$L_{w1}$	.02	.02	.02	.02
$L_{ab}$		.07		.008
$L_{w2}$	11	.012	.11	.012
$L_{ps}$		.156		.026
$L_{12}$		.1		.04
Watts into clamp:	15.99	15.99	8.48	8.48 W

How to Calculate the Amount of Leakage Inductance: Leakage inductance represents the energy storage between two windings. It may be roughly calculated from the winding geometry, using the inductance formula:

$$L = N^2 \mu_0 \mu_r \cdot \text{Area} / \text{Length} \times 10^{-2}$$

In the S.I. system of units,  $\mu_0 = 4\pi \cdot 10^{-7}$ . For the non-magnetic materials between and within the windings,  $\mu_r = 1$ . For concentric coils, "Area" is the cross-section in  $\text{cm}^2$  of the hollow cylindrical shape between the windings (the distance from the middle of one winding to the middle of the other, multiplied by the average length of one turn). "Length" is the length of the cylindrical shape -- the length of the winding in  $\text{cm}^2$ , or the breadth of the winding window. N is the number of turns in the whichever winding the leakage inductance will be referenced to. With the windings normalized, it doesn't make any difference.

How to Minimize Leakage Inductance:

1. Windings must be long and thin (few layers) for intimate coupling. Pot cores have very poor window form factor - windings are short and thick. Ferrite ETD and LP cores are good. Mo-Permalloy powder toroids provide the best winding form factor but they are probably too lossy for use in discontinuous mode applications because of the large flux swings involved.

2. Secondaries must be tightly coupled to get good cross-regulation. Wind multifilar, otherwise as close together as possible. Don't sandwich the primary between two secondaries. This reduces eddy current losses but hurts cross-regulation.

3. Primary to secondary leakage inductance does not hurt cross-regulation, but it does divert much of the inductor energy into the clamp. In off-line applications, insulation requirements force significant area between primary and secondary windings which can make the leakage inductance quite large. If necessary, interleave the primary and secondaries by putting on half the primary turns, then all the secondaries, then the other half of the primary turns outside the secondaries. The primary halves must be series connected. (Never parallel windings that are at different levels in the winding structure or large circulating current will result.) Interleaving will reduce primary-secondary leakage inductance by a factor of three, but it reduces the leakage inductance between secondaries very little and therefore has little effect on cross-regulation.

How to Minimize Wiring Inductance: Wiring inductance is especially critical in low voltage, high current outputs.

1. Minimize the area enclosed by the loop from the transformer secondary through the rectifier to the filter capacitor and back to the secondary. Keep the distances as short as possible and keep the outward and return conductors very close to each other. A ground plane is no good for the return path unless the outward conductor is held very close to it.

2. Don't use round wire, use flat strip or braid with their breadths facing each other as closely as possible. Two copper strips 1 cm wide and 10 cm long spaced 0.3 cm apart have a total inductance of 20 nH. Spread apart, the inductance will rise to 100 nH.

What Sequence for the Secondaries: Referring to Figure 3, with zero differential between the normalized output voltages, the output currents will divide according to the ratio of inductances  $L_{w1}$  vs.  $L_{ab}+L_{w2}$ '. A high voltage output will usually have much lower normalized wiring inductance (because it is reduced by  $N^2$ ). If the high voltage output is in position 1 with the closest coupling to the primary, it will take most of the normalized current (and power output). A large differential offset will be required to force power to output #2 to achieve a better balance.

Because the low voltage output has higher normalized wiring inductance, it usually makes sense to put it in the #1 position closest to the primary, where its wiring inductance helps to balance out leakage inductance  $L_{ab}$ . This will provide better distribution of power without requiring as much output voltage offset. Better balance can be achieved by deliberately increasing wiring inductance selectively, but this will hurt cross-regulation.

9/86

## IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Customers are responsible for their applications using TI components.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, license, warranty or endorsement thereof.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations and notices. Representation or reproduction of this information with alteration voids all warranties provided for an associated TI product or service, is an unfair and deceptive business practice, and TI is not responsible nor liable for any such use.

Resale of TI's products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service, is an unfair and deceptive business practice, and TI is not responsible nor liable for any such use.

Also see: [Standard Terms and Conditions of Sale for Semiconductor Products](http://www.ti.com/sc/docs/stdterms.htm). [www.ti.com/sc/docs/stdterms.htm](http://www.ti.com/sc/docs/stdterms.htm)

### Mailing Address:

Texas Instruments  
Post Office Box 655303  
Dallas, Texas 75265