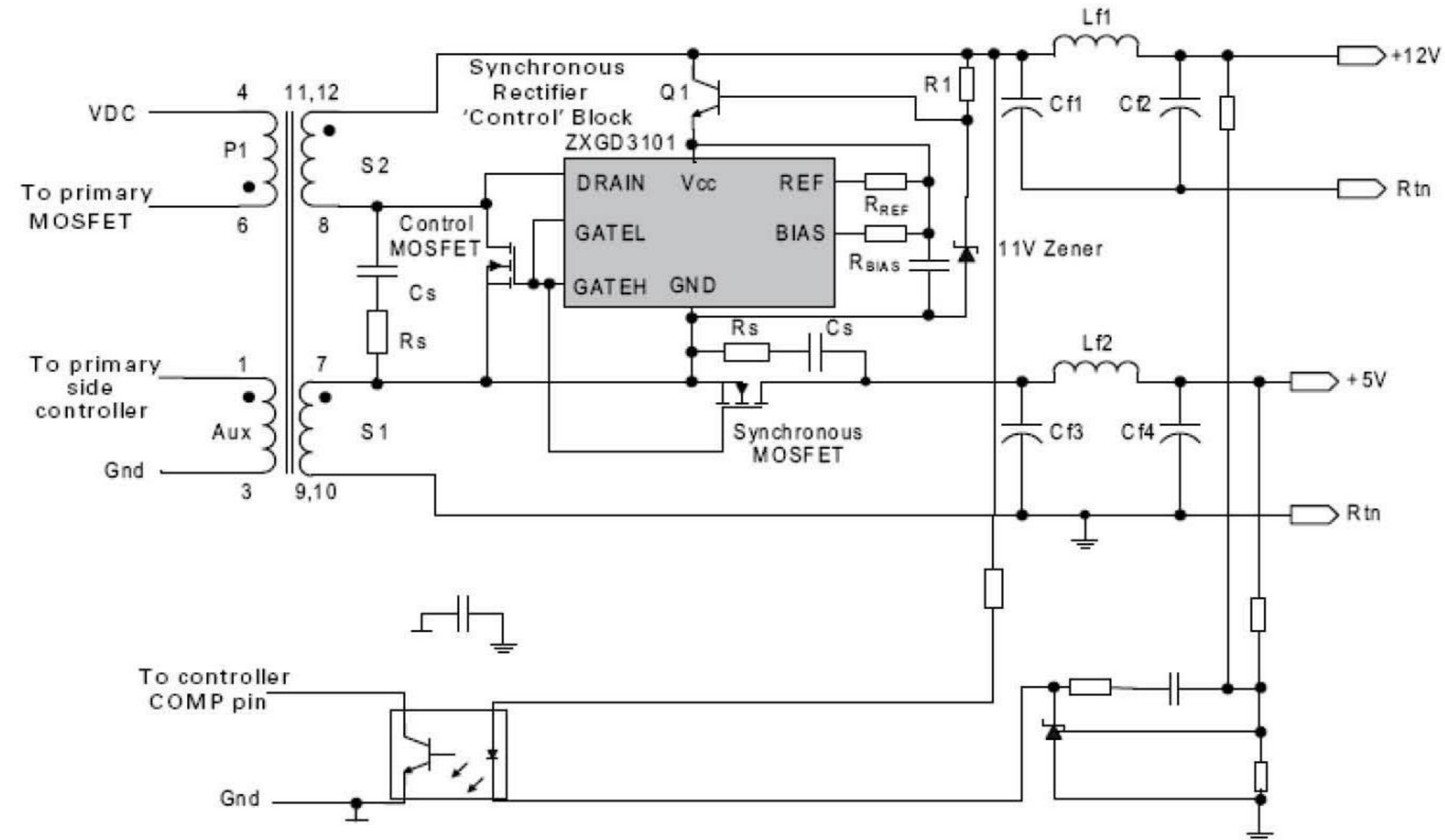


ZXGD3101

***Synchronous Rectifier MOSFET Driver
for SMPS Secondary Side***

Dual Output PSU for LCD monitors


Discrete and Analog Solutions for Advancing Technologies



Proposed configuration of ZXGD3101 in a dual-output Flyback SMPS

5V Output rail for Server PSU

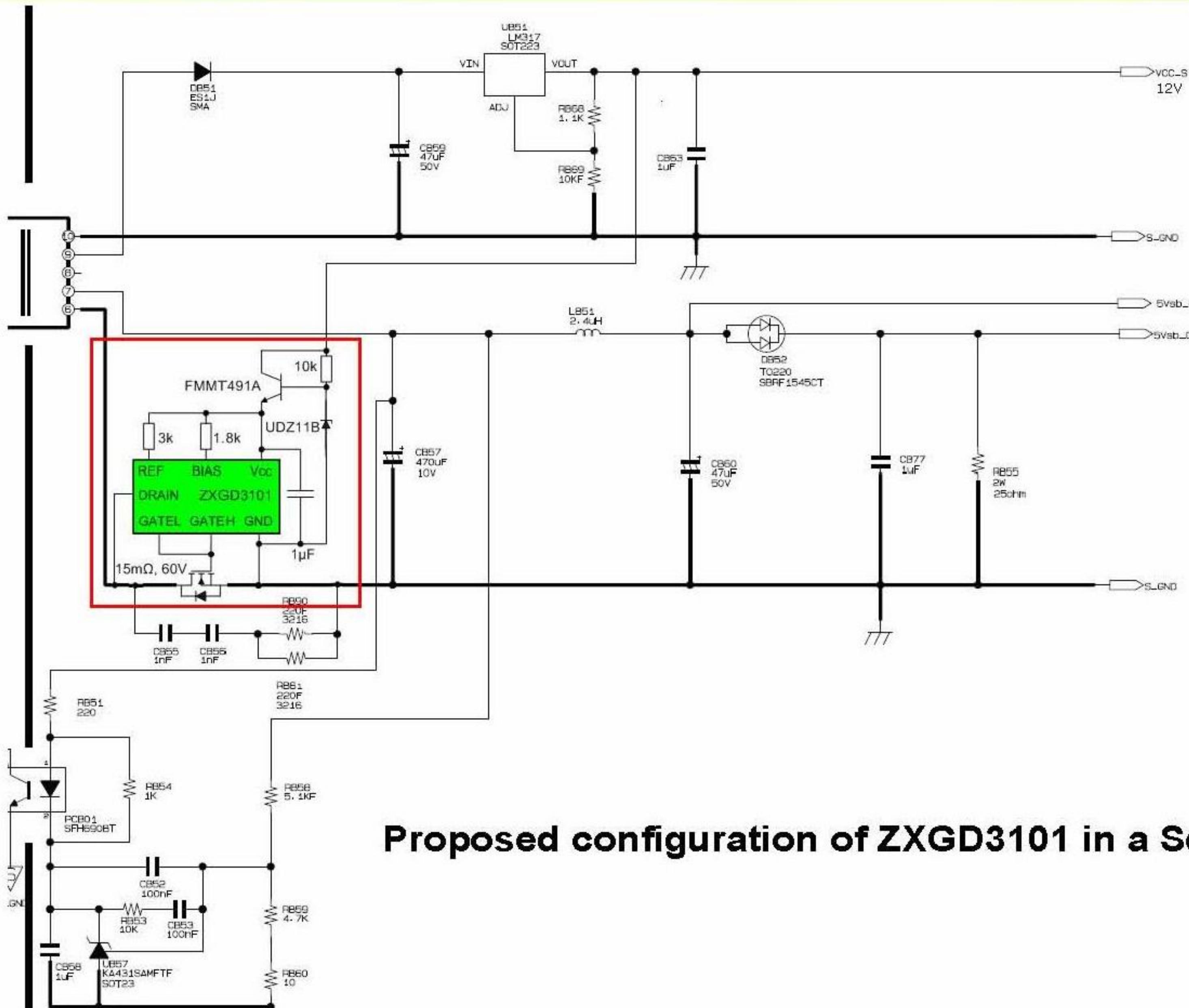
Discrete and Analog Solutions
for Advancing Technologies



Proposed configuration of ZXGD3101 in a Server SMPS

Set Top Box PSU

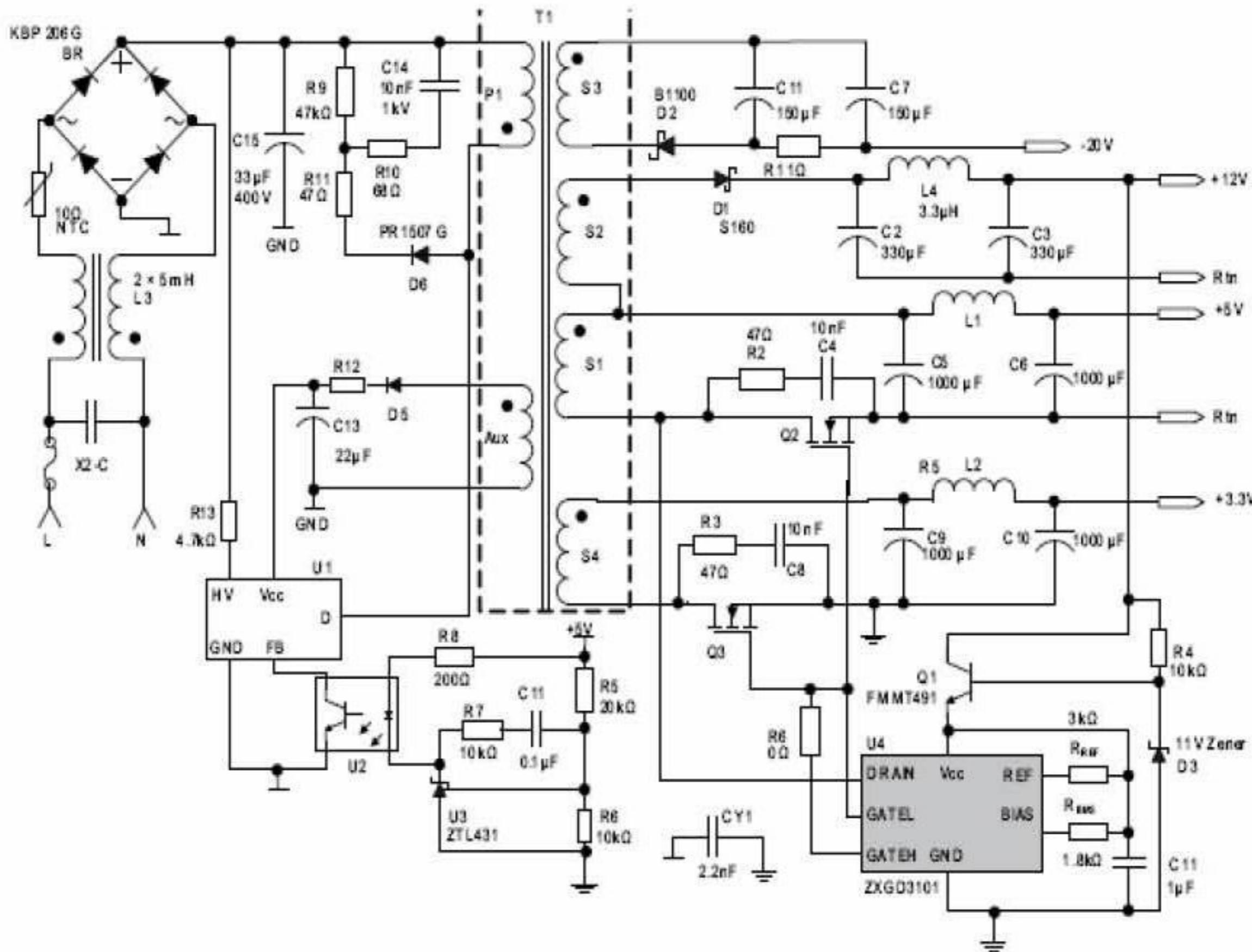
Discrete and Analog Solutions for Advancing Technologies



Proposed configuration of ZXGD3101 in a Set Top Box SMPS


Basic Flyback topology

ZXGD3101 would be used here

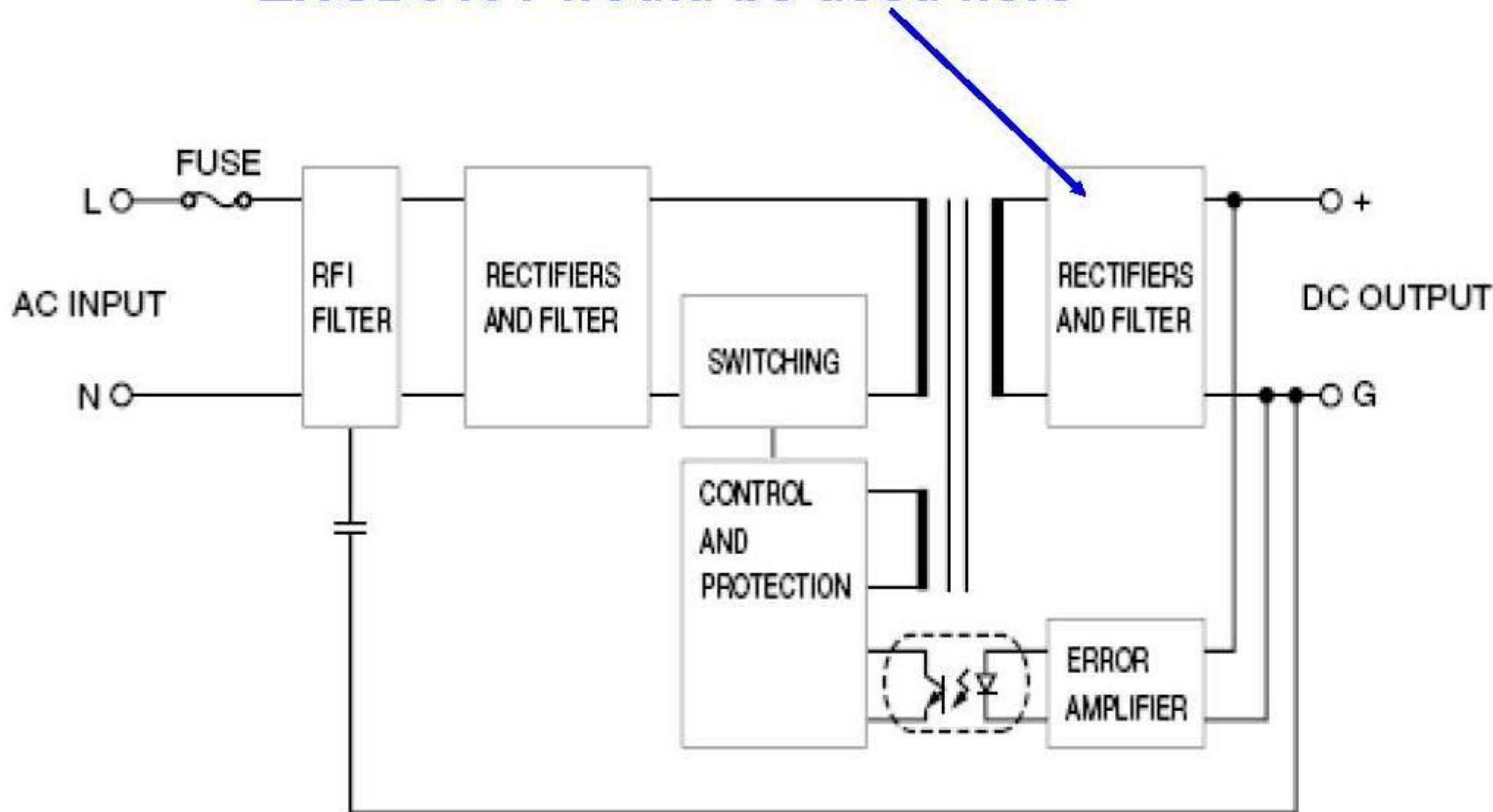

Flyback Topology for Desk Top Adapters

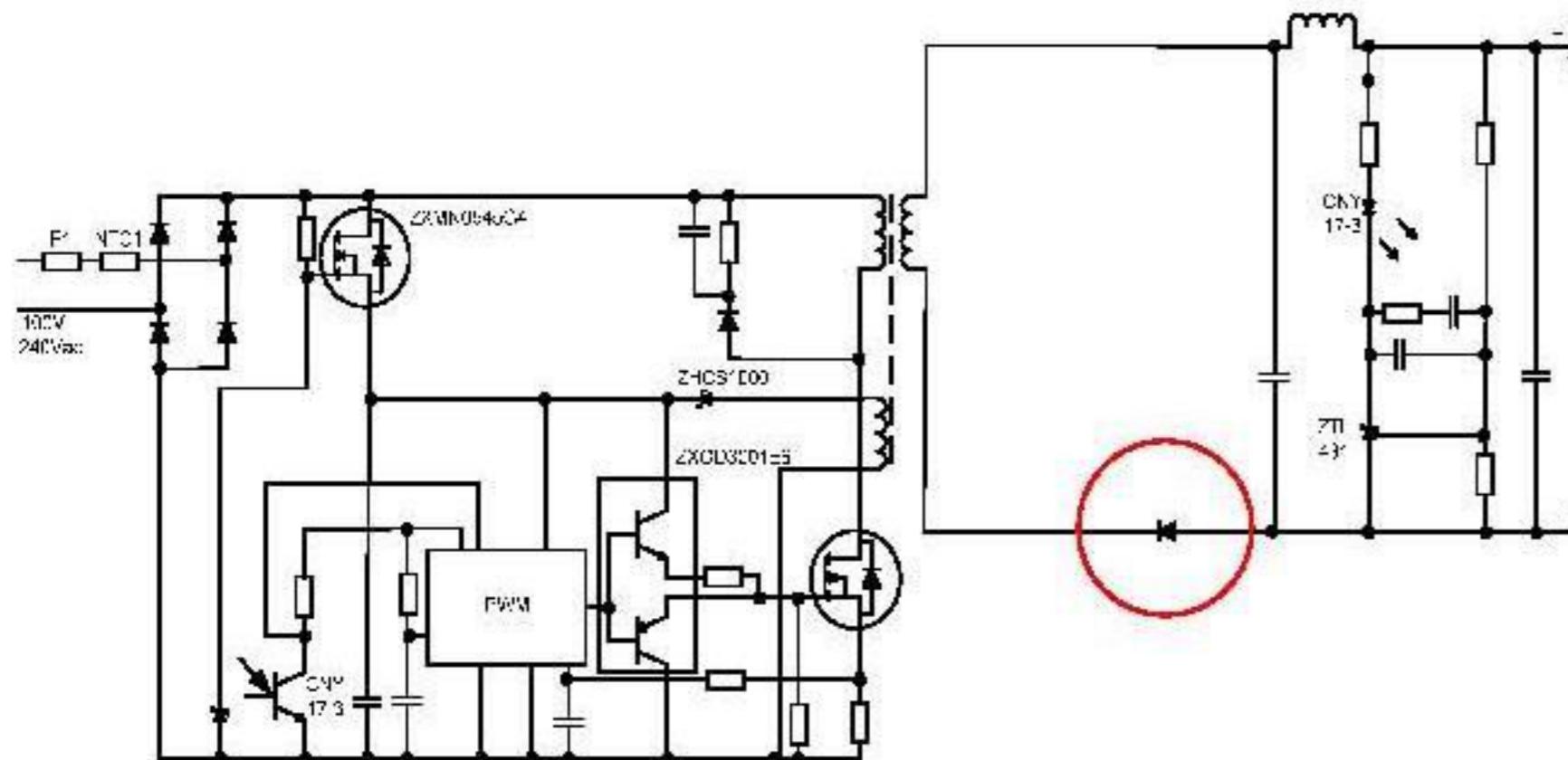Discrete and Analog Solutions
for Advancing Technologies




Diode Solution

- Efficiency 83 ~ 86%
- Bulky heat sinks
- < 0.5W standby



Synchronous Rectifier Solution

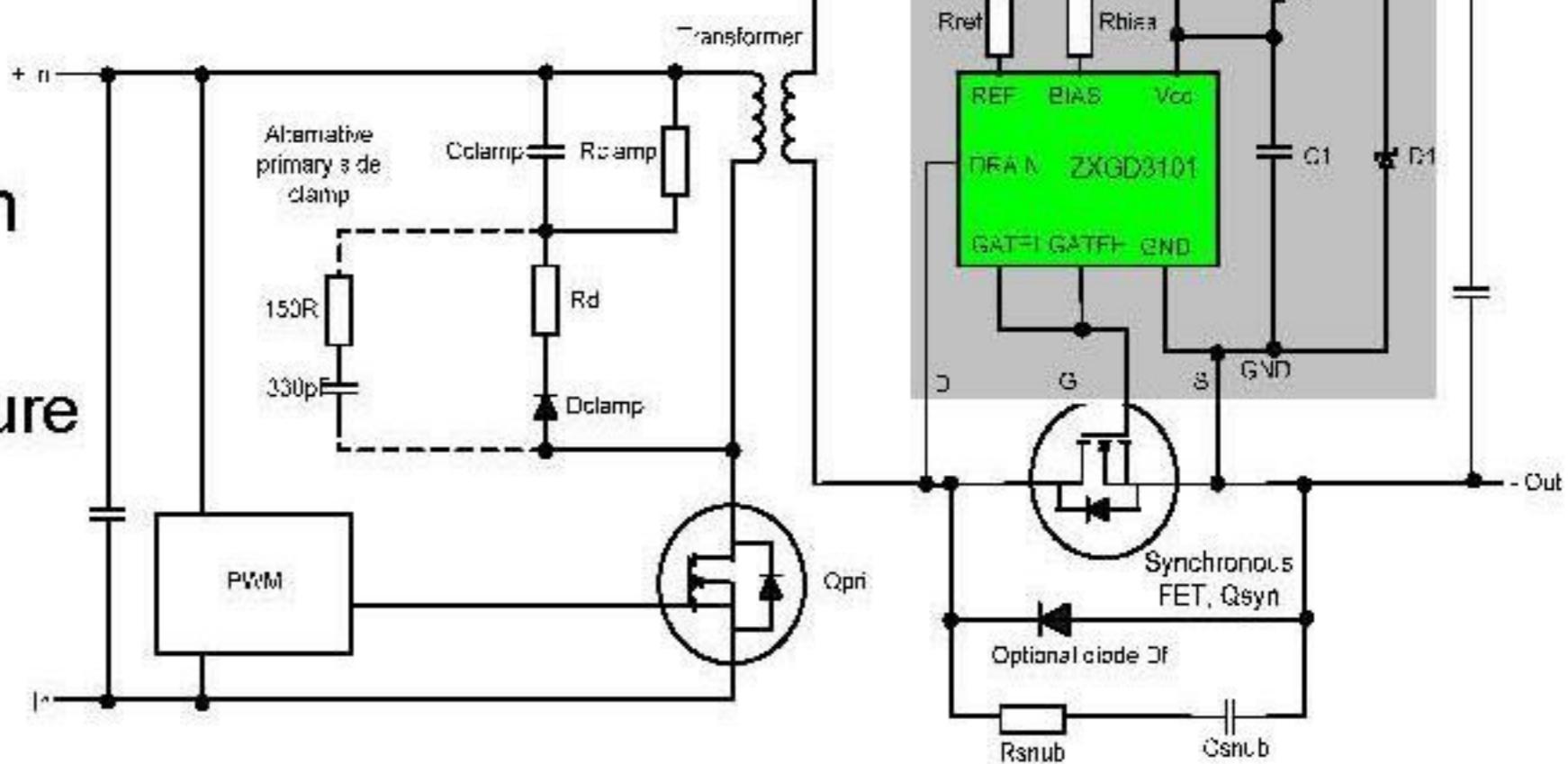- Efficiency > 87%
- Lower operating temperature
- < 0.5W standby




Synchronous MOSFET controller / driver

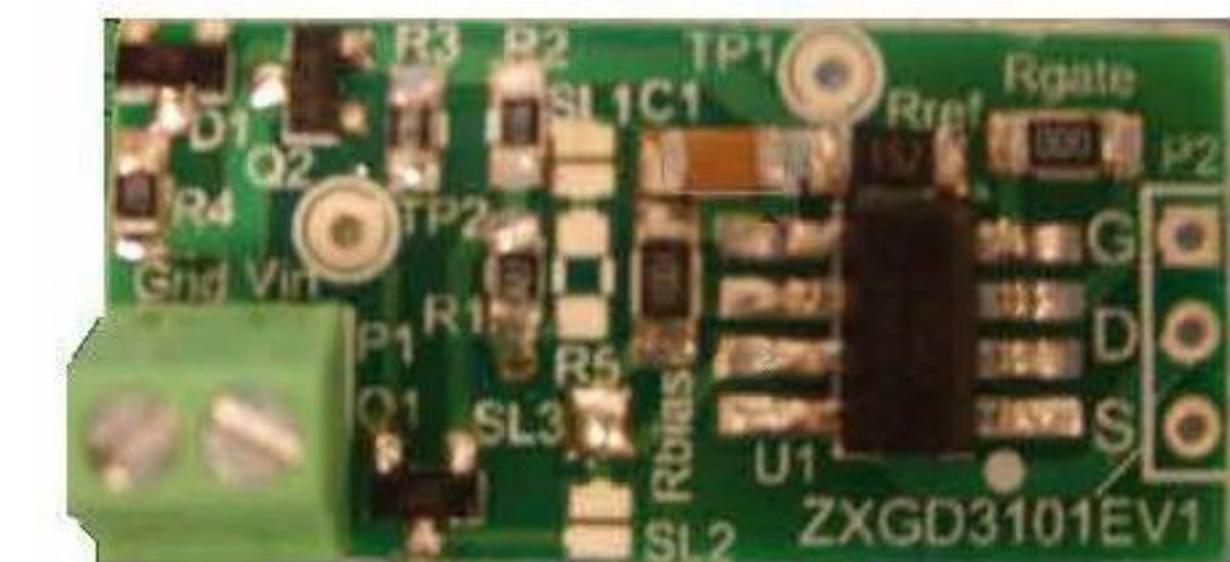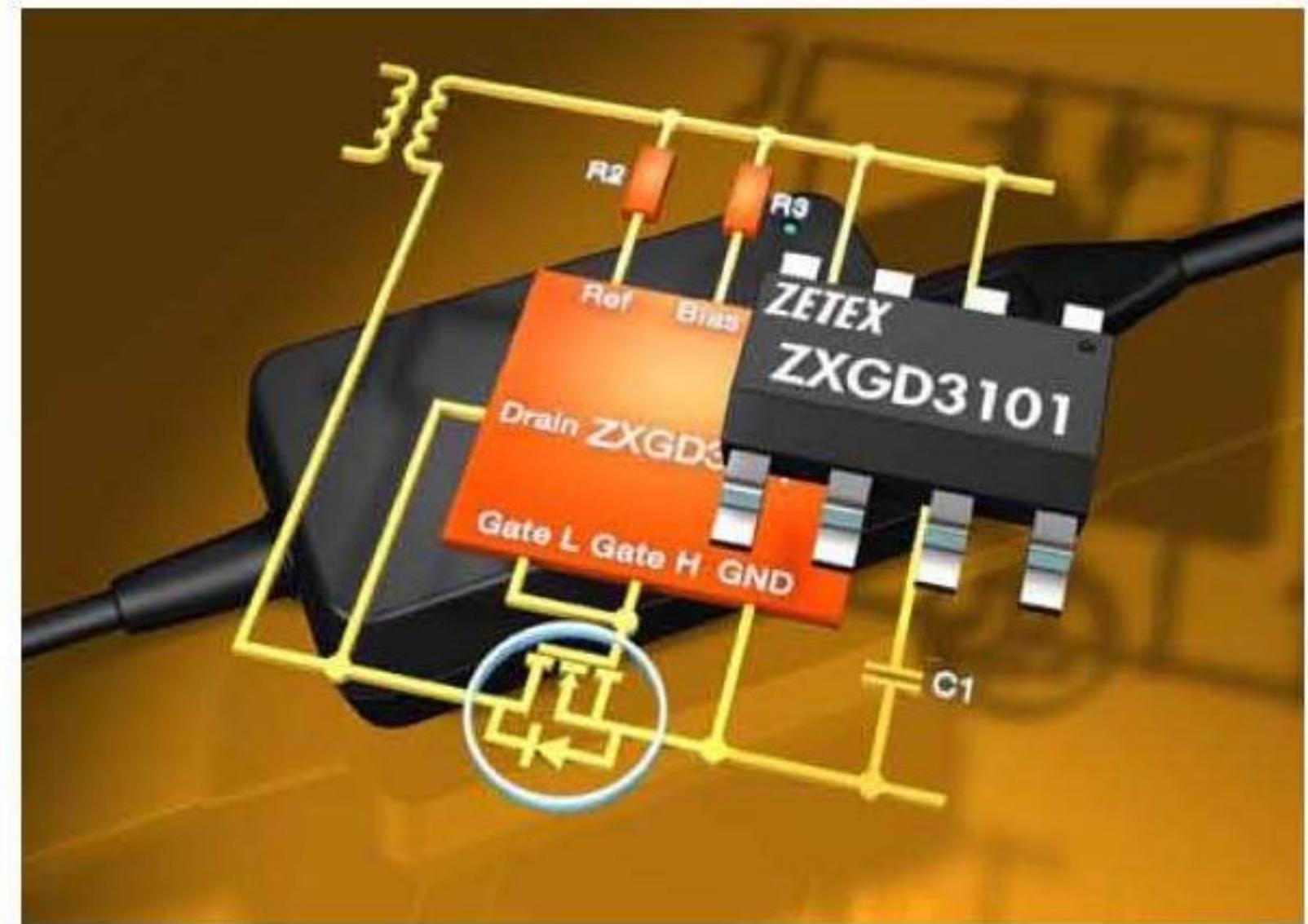- Senses the point at which secondary current reaches zero
- High voltage differential amplifier & high current MOSFET driver
- Source & sink currents typ. 2.5A
- Needs just 3 external components
- Simple: no timing info from primary side, no timing components on secondary side




ZXGD3101 Switching waveforms in CCM and CrCM

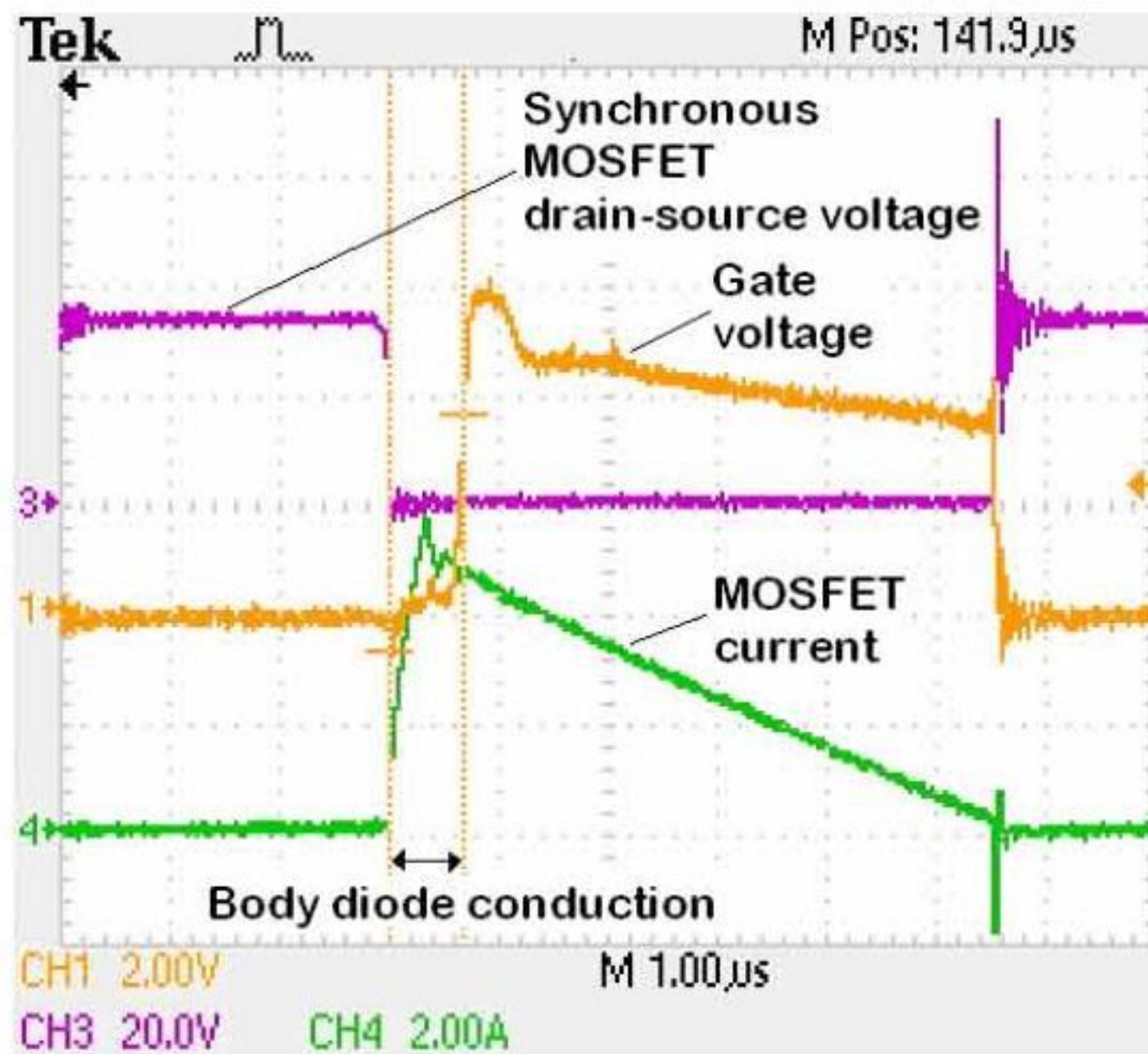Discrete and Analog Solutions
Advancing Technologies



(a) Critical conduction mode (CrCM)

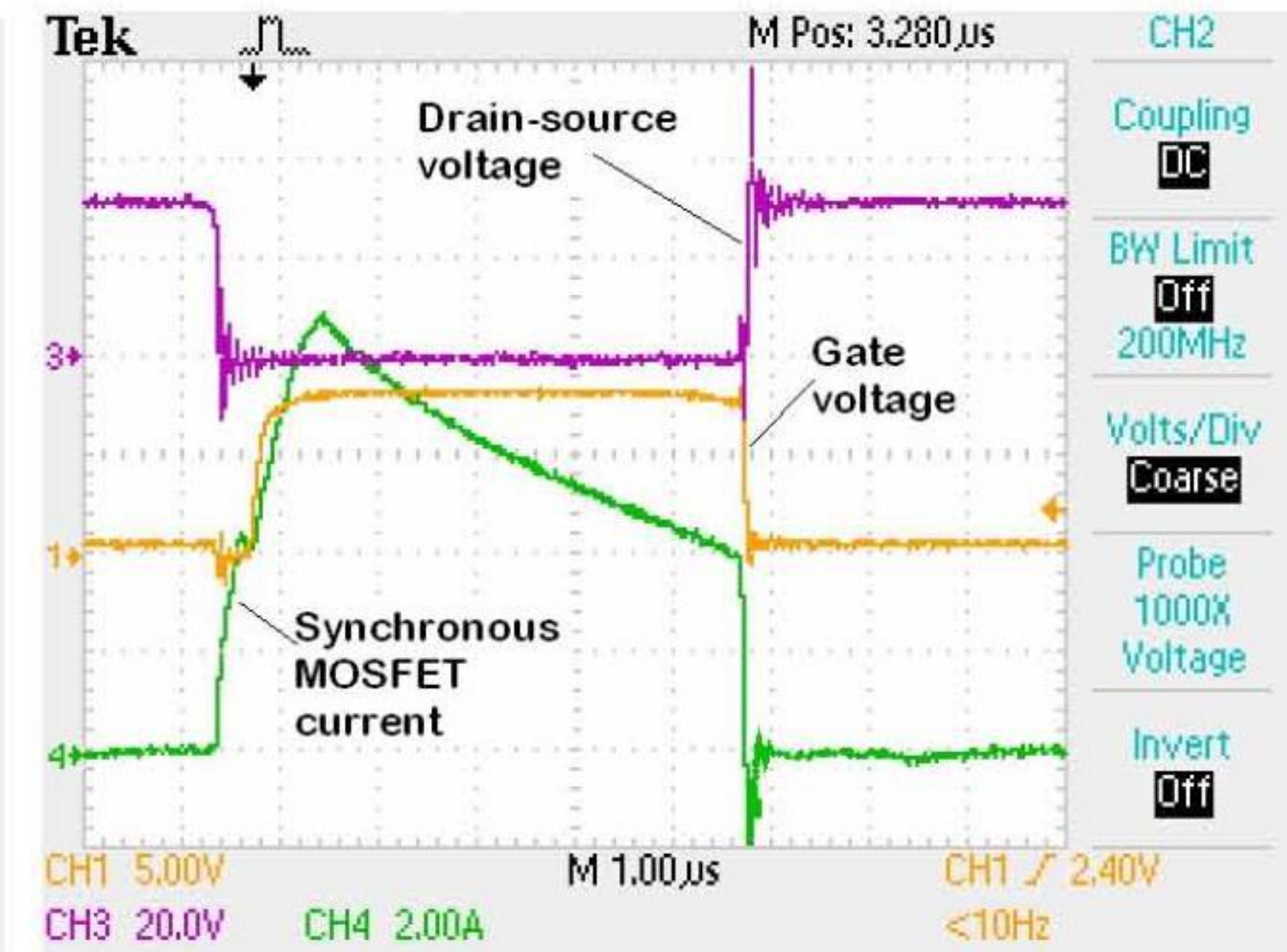


(b) Continuous conduction mode (CCM)

Energy efficiency initiatives

Discrete and Analog Solutions
for Advancing Technologies



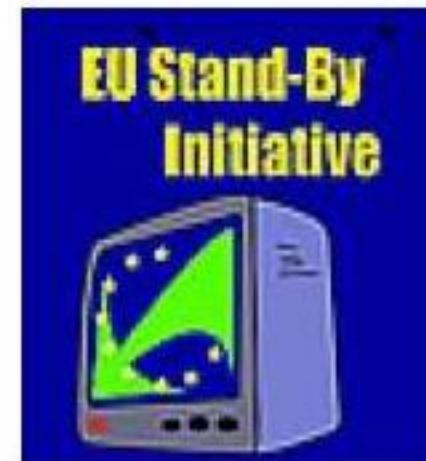Powered by an
ENERGY STAR®
qualified adapter
for a better
environment



For Single Voltage External AC-DC and AC-DC Power Supplies

Specification	US Energy & Conservation Act	Energy Star® V2.0	Eu Code of Conduct Ver 3
Implementation Date	July 1, 2008	November 1, 2008	January 1, 2009
Average Efficiency in Active Mode	$\geq 85\%$ $(> 51W)$	$\geq 87\%$ $(> 49 W)$	$\geq 87\%$ $(36 < W \leq 250)$
Maximum Power in No-load	$\leq 0.5W$ $(\geq 50 \text{ to } \leq 250W)$	$\leq 0.5W$ $(\geq 50 \text{ to } \leq 250W)$	$\leq 0.5W$ $(\geq 50 \text{ to } \leq 250W)$
PFC requirement	-	≥ 0.9 $(\geq 100W)$	-


Results on 60W adapter using ZXGD3101

	No-Load	Active Mode				
	0%	25%	50%	75%	100%	Average
Percentage of name plate current	0%	25%	50%	75%	100%	Average
DC Output Current (A)		0.792	1.599	2.406	3.220	
DC Output Voltage (V)		19.94	18.76	18.71	18.63	
DC Output Power (W)		15	30	45	60	
AC Input Voltage (V)	115	115	115	115	115	
AC Input Power (W)	0.36	17.05	33.77	50.93	68.2	
Power Consumed by UUT (W)	0.36	2.05	3.77	5.93	8.2	
Efficiency (%)		87.97	88.84	88.36	87.98	88.29

Additional benefits of using sync. rectification


- **Less heat generation**
 - Lower operating temperatures
 - Improved reliability

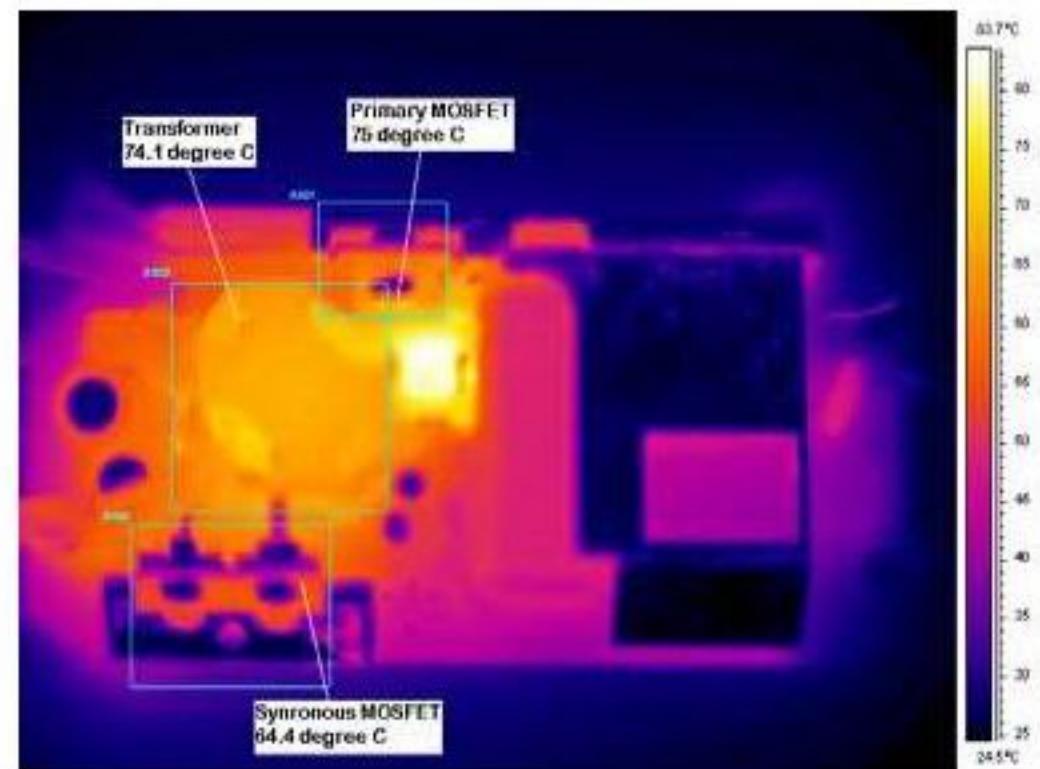- **Allows surface mount sync rectifiers (MOSFETs)**
 - Smaller or even no heat sinks
 - Size reduction of power supply
 - Increased current capability
 - Weight reduction
 - Reduced assembly time



High Side Configuration

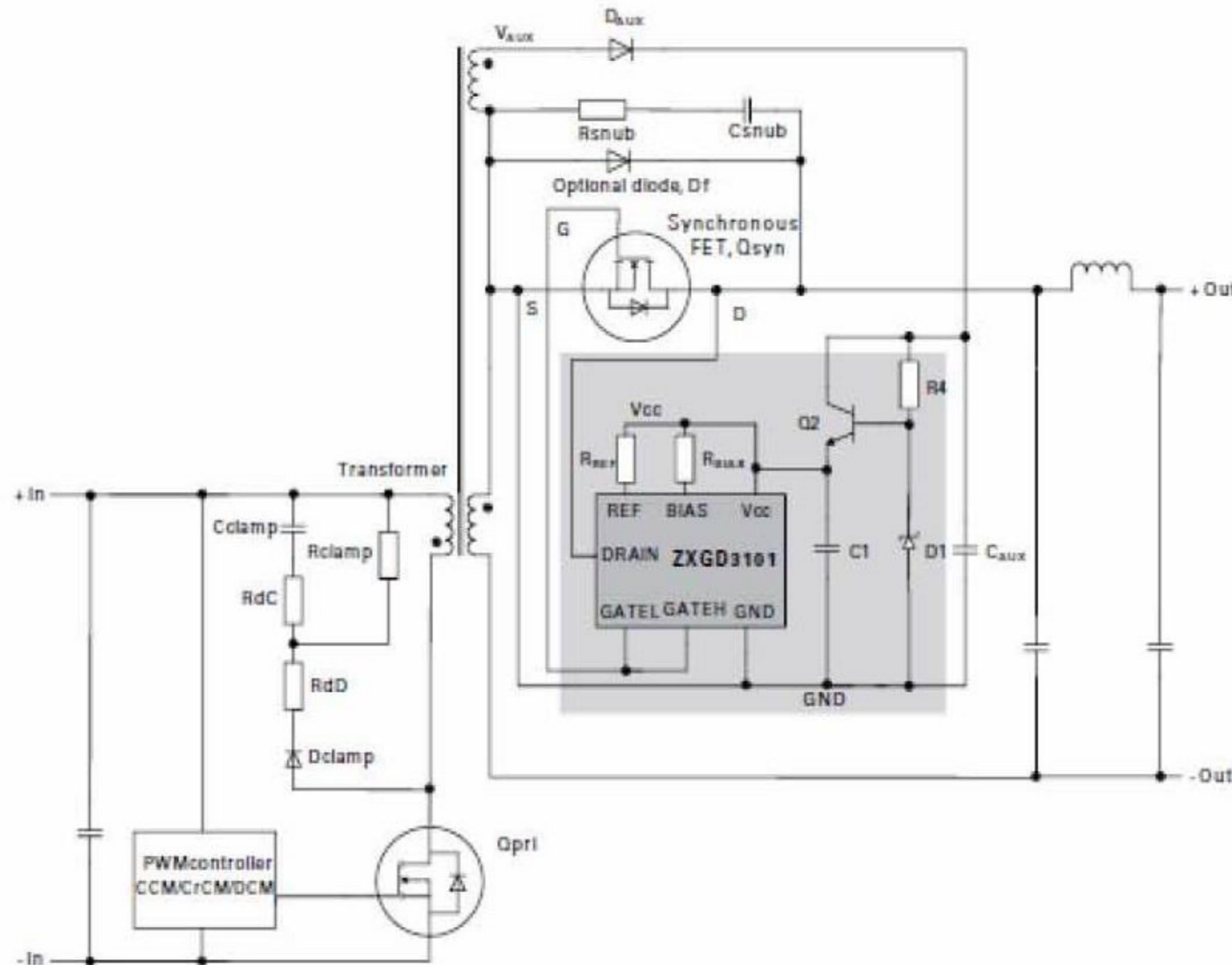
Discrete and Analog Solutions
for Advancing Technologies



Proposed configuration of ZXGD3101 for high-side rectification

ZXGD3101/IR1167B evaluation circuit

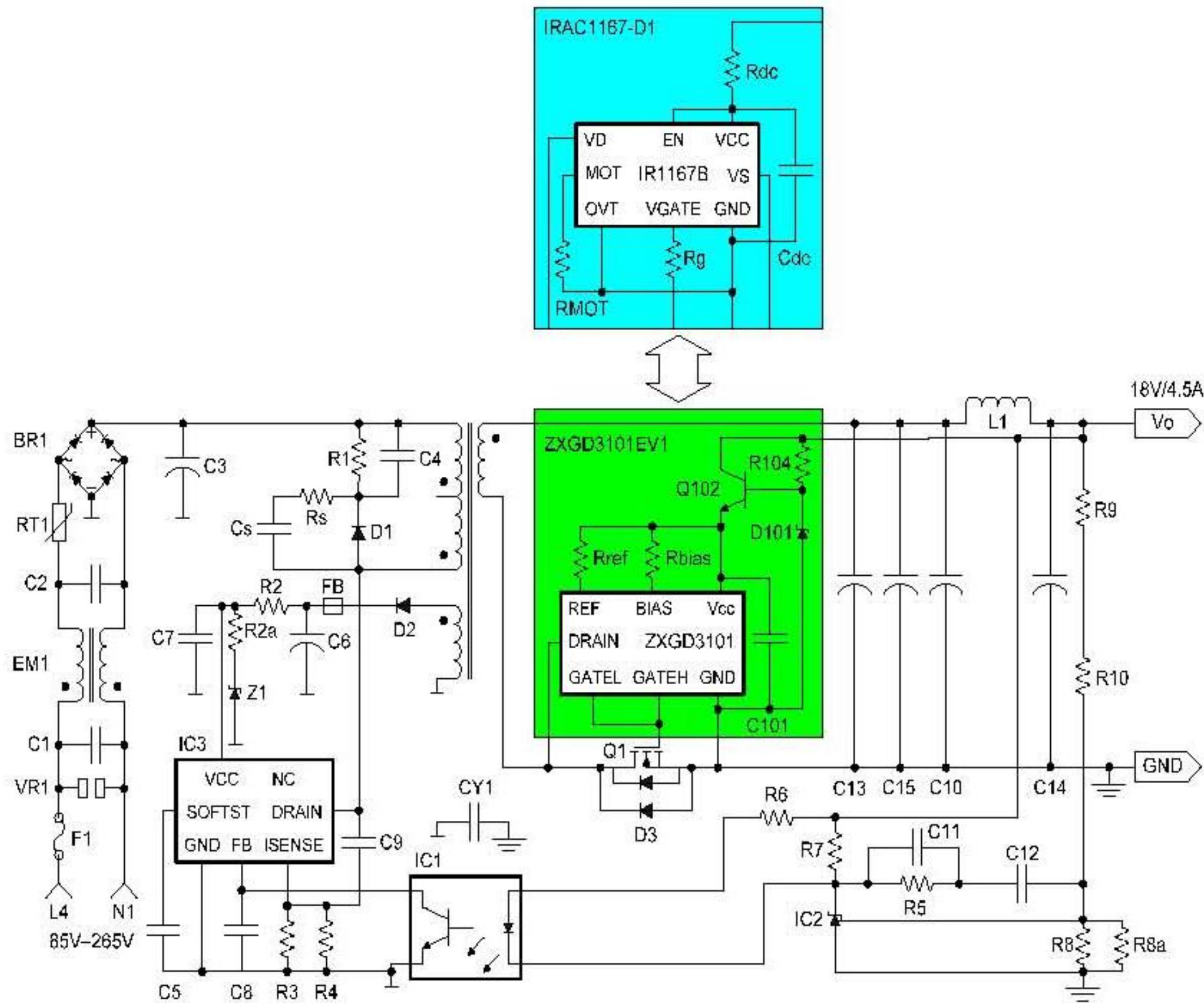Discrete and Analog Solutions
for Advancing Technologies



Efficiency Comparison

Discrete and Analog Solutions
for Advancing Technologies

Comparison between Ultra-fast diode and Synchronous MOSFET
in a 80W (18V, 4.5A) DCM Flyback laptop adapter

