

Explanation of Electromagnetic Interference (EMI) in Switching Power Supply

Speakers

Franki Poon, Bryan M.H. Pong

Power^eLab

The Power Electronics Lab., Hong Kong University

© copyright 2002



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

1

*A brief introduction to the **Power^eLab***

Our Mission : To advance switching power converter technologies

- **To develop excellence in power electronics technologies**
- **To apply the technologies to products and foster cooperation with industries**

Contact Person : Dr. Bryan M.H. Pong
Power Electronics Lab., Department of Electrical & Electronic Engineering,
Hong Kong University, Pokfulam Road,
Hong Kong
Tel : (852) 2859 7099
Email : mhp@eee.hku.hk

Fax : (852) 28597099 or 2559 8738
Web site : www.eee.hku.hk/power_electronics_lab/



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


www.eee.hku.hk/power_electronics_lab/

2

Our work in the **Power^eLab**



High Power 120W
AC/DCAadapter Platform

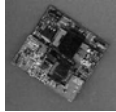

Half brick DCDC
Converter Platform




High current Converter
Platform 1V5 200A



ACDC Converter
Platform 1V5 40A



Battery charger
Platform 12V 65W

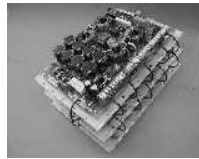

4.5kVA Power Amplifier

More in the
Power^eLab
website



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

3

What you are going to learn today. . . .

- Easy – EMI Basics. What and how people test your product.
- Not so easy – General attitude of an EMI engineer.
- Difficult – How EMI is produced.
- More difficult – How EMI comes and goes.




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/


4

Basic Blocks

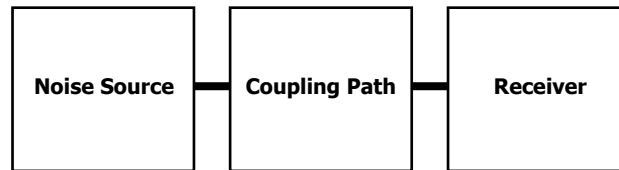- Every EMI issue has the following 3 basic blocks









Noise Sources

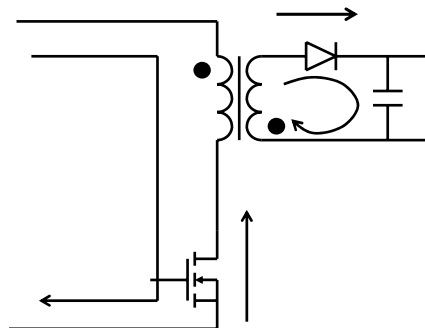





- Switching voltage and current waveforms in a switching power supply



Waveform produces frequency spectrum

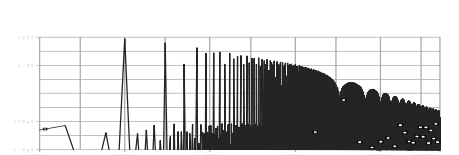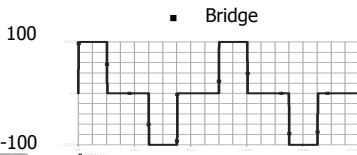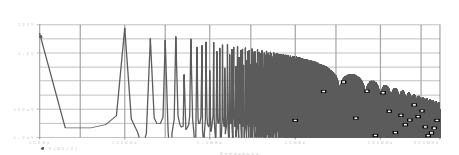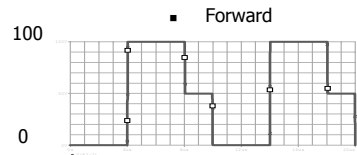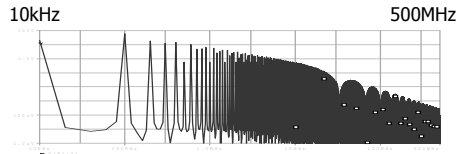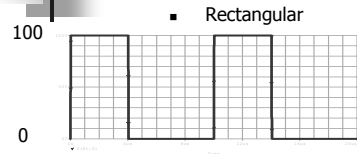


Waveform produces frequency spectrum

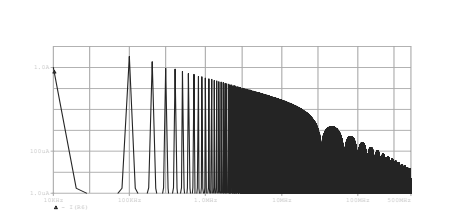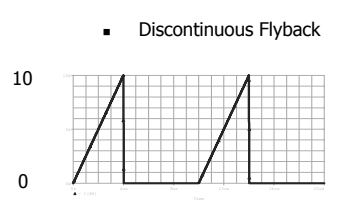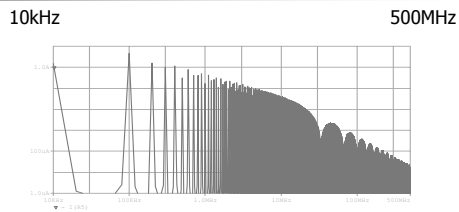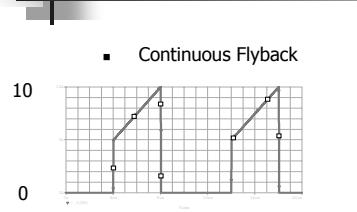


Effect of duty cycle

- Duty cycle = 0.2


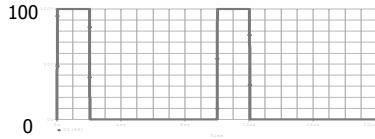


- Duty cycle = 0.6

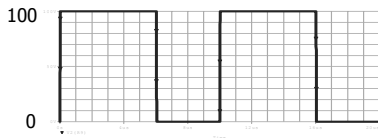

10kHz


500MHz

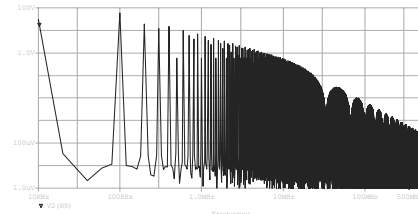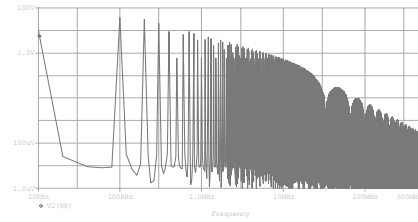


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Effect of waveform slope (dv/dt)

- 30ns rise and fall time


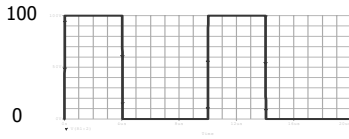


- 300ns rise and fall time

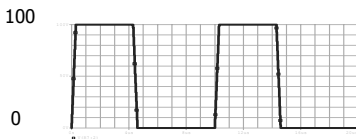


10kHz

500MHz

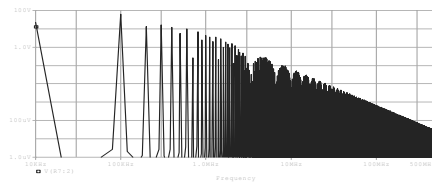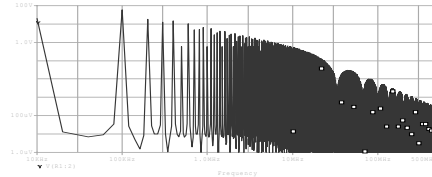

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Snubber circuit reduces dv/dt

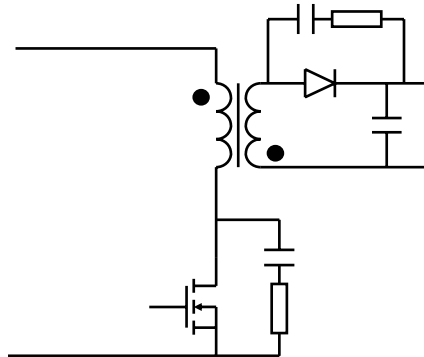


Notes on Noise Sources

- Voltage and current waveforms
- Noise sources in switching power supply has little effect beyond 200MHz
- Waveshape affect base band frequencies
- Rising and falling edges affect high frequency spectrum
- Duty cycle has little effect on the spectrum




Basic Blocks

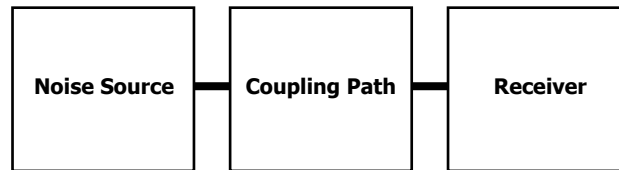- Every EMI issue has the following 3 basic blocks



Coupling Paths

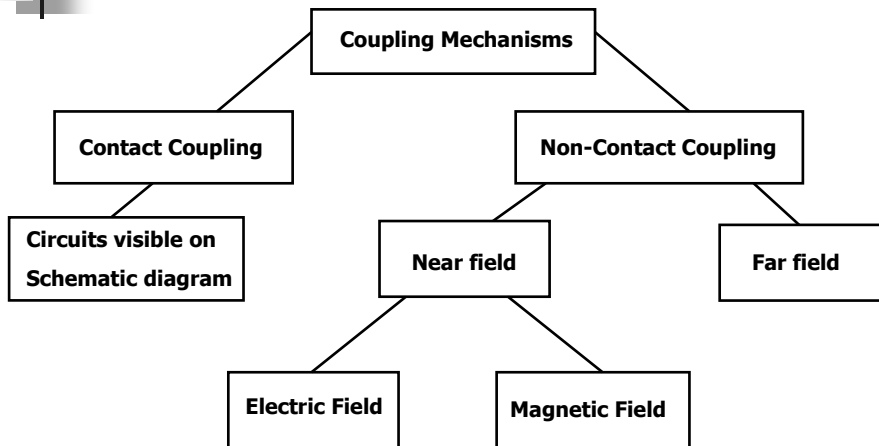


Receiver


- Standard test equipment set up
 - Conducted Measurement set up
 - Radiated Measurement set up



EMI standards

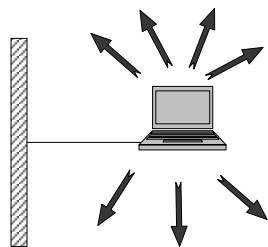

Electromagnetic Emission
(Our Interest)

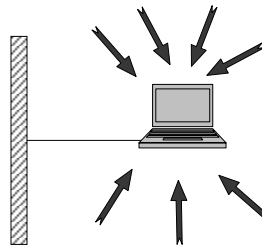

Electromagnetic Immunity



Emission standards

Reference	Description (Emission Standard)
CISPR13 /EN55013	Limits and methods of measurement of radio interference characteristics of sound and TV broadcast receivers and associated equipment.
CISPR14 /EN55014	Limits and methods of measurement of radio interference characteristics of electric motor operated and thermal appliances for household and similar purposes, electric tools and similar electrical apparatus. (Latest revision cover all electrical household appliances)
CISPR15 /EN55015	Limits and methods of measurement of radio interference characteristics of electrical lighting and similar equipment.
CISPR22 /EN55022	Limits and methods of measurement of radio interference characteristics of information technology equipment.
IEC61000-3-2 /EN61000-3-2	Limits for harmonic current emission ($\leq 16A$ per phase)
IEC61000-3-3 /EN61000-3-3	Limitation of voltage fluctuations and flicker in low voltage supply system ($\leq 16A$ per phase)
EN50081-1	Generic residential emission standards
EN50081-2	Generic industrial emission standards
FCC 15B	USA National EMI Standard



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

17

Immunity standards

Reference	Description(Immunity Standards)
CISPR20 /EN55020	Limits and methods of measurement of immunity characteristics of sound and TV broadcast receivers and associated equipment.
IEC61000-4-2 /EN61000-4-2	Electrostatic discharge immunity test
IEC61000-4-3 /EN61000-4-3	Radiated radio frequency electromagnetic field immunity test
IEC61000-4-4 /EN61000-4-4	Electrical fast transient immunity test
IEC61000-4-5 /EN61000-4-5	Surge immunity test
IEC61000-4-6 /EN61000-4-6	Immunity to conducted disturbances induced by radio frequency fields above 9kHz.
IEC61000-4-11 /EN61000-4-11	Voltage dips, short interruptions and voltage variations immunity test.
EN50082-1	Generic residential immunity standard
EN50082-2	Generic industrial immunity standard




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

18

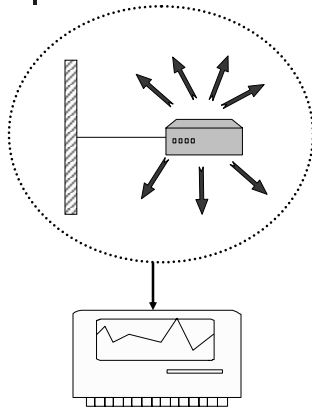Measurement – use what type of equipment ?



Spectrum Analyzer

① Cheap

① One is enough – 10kHz – 1GHz


② Less accurate



EMI Receiver

① Expensive

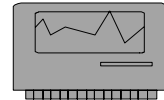① Two are needed – 10kHz to 30MHz,
30MHz to 1GHz




② More accurate



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


Measurement Set Up – Conducted (< 30MHz)

No Shield Room is Needed !!

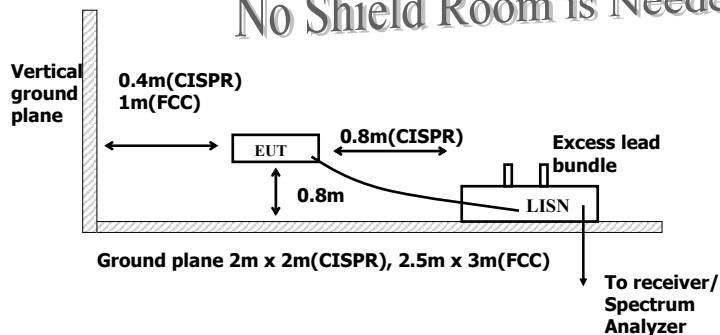


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

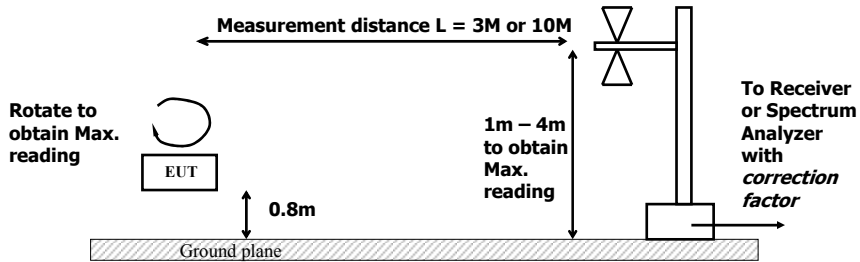Measurement Set Up – Radiated EMI (> 30MHz)



Radiated Set Up – Open site Grounding


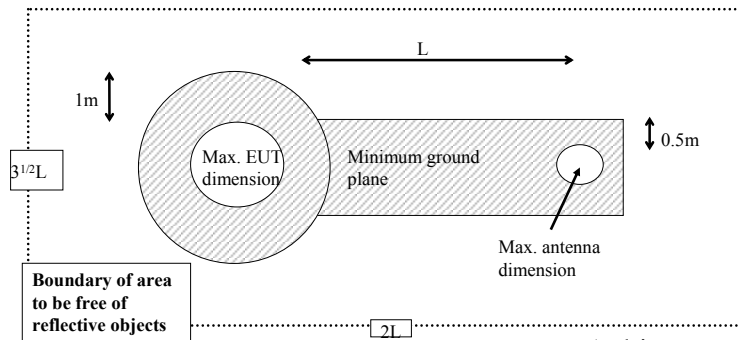


Anechoic chamber is Needed in practice!!



Radiated Set Up - diagnosis

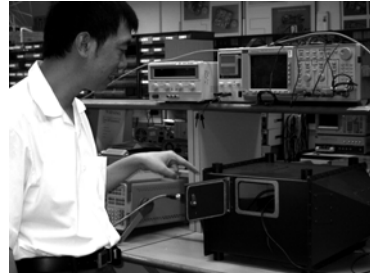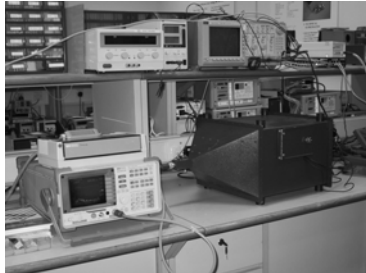- Anechoic chamber filled with ferrite absorbers to absorb EM reflections
- Small TEM cell provides convenient way to diagnose EMI problem



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

23

Measurement – Limit level

	0.15MHz – 0.5MHz	0.5MHz – 5MHz	5MHz – 30MHz
	<i>CISPR22 conducted emission limit</i>		
<i>Average limit (B)</i>	56 dBuV – 46 dBuV 630 uV - 200 uV	46 dBuV 200 uV	50 dBuV 316 uV
<i>Quasi peak limit (B)</i>	66 dBuV – 56 dBuV 2000 uV – 630 uV	56 dBuV 630 uV	60 dBuV 1000 uV

Can you make an amplifier which receives signal from 150kHz to 1GHz at 200uV signal level ??

	30MHz – 230MHz	230MHz – 1G
	<i>CISPR22 radiated emission limit</i>	
<i>Quasi peak limit(10m class A)</i>	40dBuV/m 100 uV/m	47dBuV/m 223 uV/m
<i>Quasi peak limit(10m class B)</i>	30dBuV/m 31uV/m	37dBuV/m 70 uV/m



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

24

Measurement – about error

According to "EMC for product Designers" - Tim Williams

<i>RF measuring receiver -</i>	<i>+/- 2.5dB (worse for spectrum analyzer)</i>
<i>Impedance mismatch</i>	<i>+/- 1dB</i>
<i>Antenna</i>	<i>+/- 4dB</i>
<i>Antenna cable</i>	<i>+/- 2.5dB</i>
<i>Anechoic chamber</i>	<i>+/-3dB</i>
<i>Test engineer</i>	<i>+/- 4dB</i>

Total = **17 dB !**



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

25

Measurement – short summary

- Spectrum Analyzer is cheaper for in house pre-compliance test.
- Conducted measurement is rather simple.
- Radiated measurement is difficult.
- Different test Laboratory will give you different results.



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

26

Most Important Concept - LOG

- Equipment reading are in LOG scale, it lies in our mind that

$$Reading = 20 \text{Log} \left(\frac{Measured}{10^{-6}} \right) \text{dBuV}$$

Can you imagine what a number will become when it is divided by 10^{-6} , then take **LOG**, and finally multiplied by 20 ??



Most Important Concept - LOG & Sum

$$500\mu\text{V} = 54 \text{ dBuV}$$

$$1000\mu\text{V} = 60 \text{ dBuV}$$

$$2000\mu\text{V} = 66 \text{ dBuV}$$

$$500 \mu\text{V} + 1000 \mu\text{V} + 2000 \mu\text{V} = 3500 \mu\text{V} = 71 \text{ dBuV}$$

Generic human intuitive comparison

Compare linear result $3500 / 500 = 7$ times

Compare LOG result $71/54 = 1.3$ times

What does 1.3 times tell us ?



Most Important Concept - LOG & Subtract

$$3500\mu\text{V} = 71 \text{ dBuV}$$

$$2000\mu\text{V} = 66 \text{ dBuV}$$

$$1000\mu\text{V} = 60 \text{ dBuV}$$

$$3500 \mu\text{V} - 2000 \mu\text{V} - 1000 \mu\text{V} = 500 \mu\text{V} = 54 \text{ dBuV}$$

Generic human intuitive comparison tells us

Compare linear result $500 / 3500 = 0.143$ times


Compare LOG result $54/71 = 0.76$ times

What does 0.76 times tell us ?





LOG Reading – an example

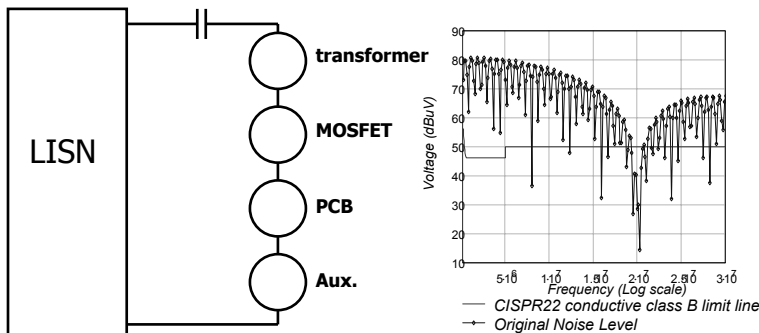Assume that noise is produced by four contributors





Example – eliminate effect of the transformer

Conclusion – Little effect

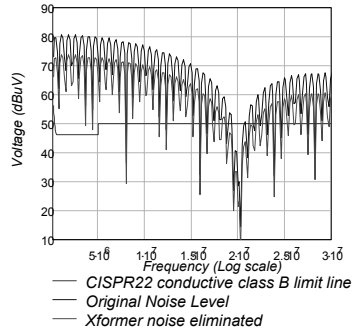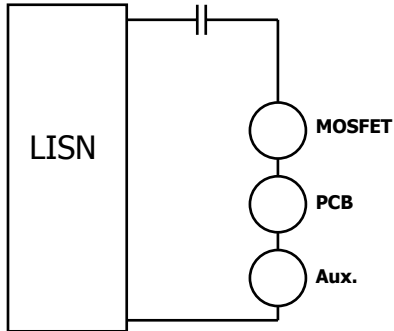


Example – eliminate effect of the MOSFET

Conclusion – Very Little effect

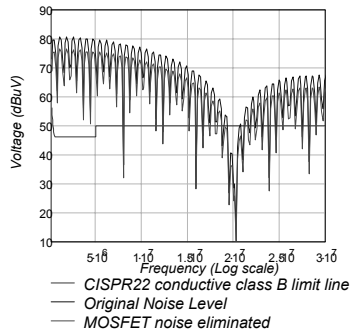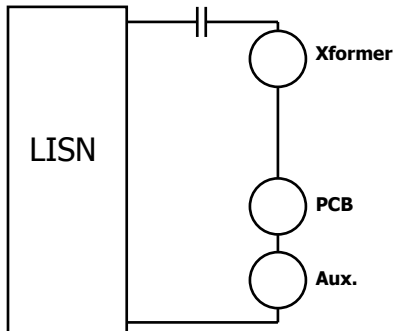


Example – eliminate effect of the PCB

Conclusion – No effect

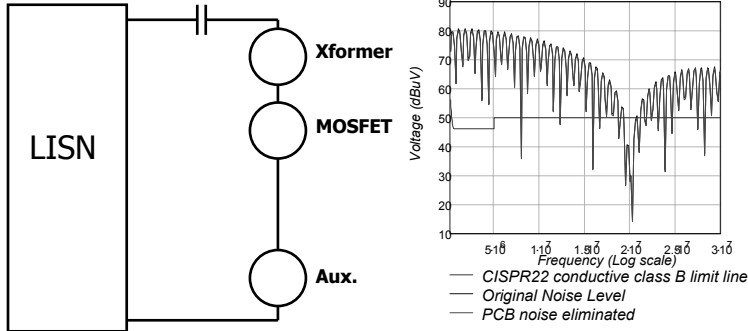


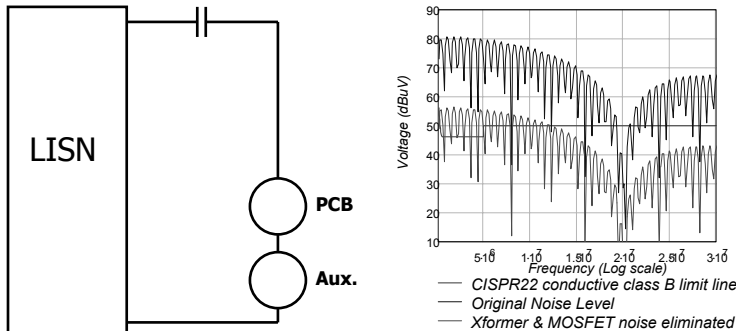Example – eliminate the little and the very little


Conclusion – Hopeless, still exceeds the limit




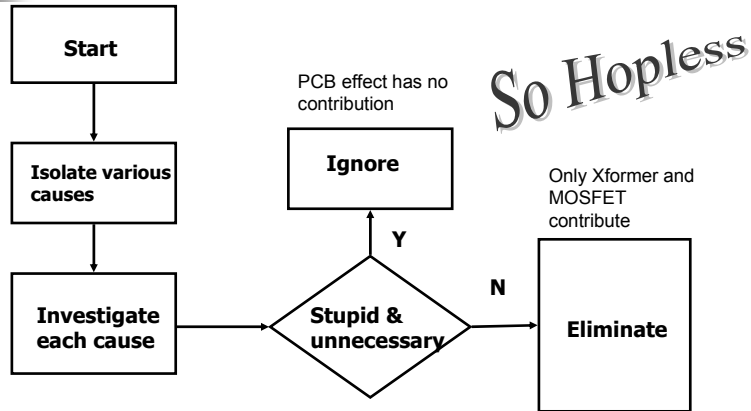
Example – already in a professional way ?



Wait a minute.....

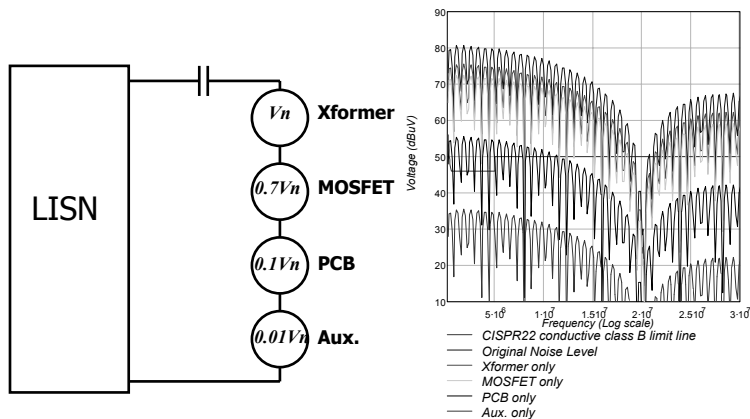

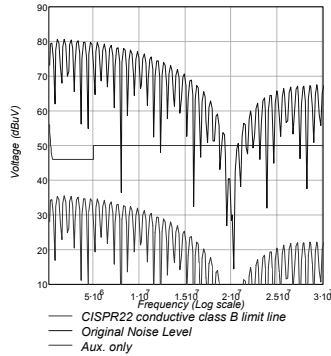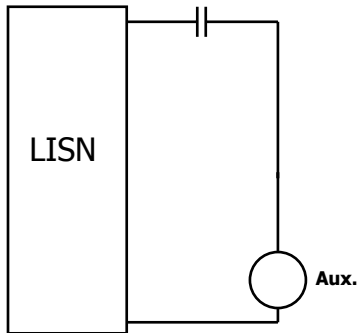
We're wrong twice – eliminate the No Effect



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Wrong three times ?

~~So PCB is important~~

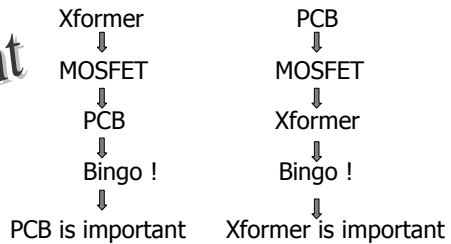

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Wrong Concepts

- There is a dominant noise mechanism or path – *Wrong!*
- Some other noise mechanism can be ignored as it shows no effect – *Wrong!*
- Yesterday EMI solution did not work in today's problem – *Wrong!*



Right Concept

- "You will not see a result until you have eliminated the **LAST** problem"

Peter Bardos



Remember

- Two equal noise level add together only make a 6 dB difference

$$\text{Reading} = 20\text{Log}\left(\frac{\text{Measured} + \text{Measured}}{10^{-6}}\right)\text{dBuV}$$

$$\text{Reading} = \left(20\text{Log}\left(\frac{\text{Measured}}{10^{-6}}\right) + 20\text{Log}(2)\right)\text{dBuV}$$

$$\text{Reading} = \left(20\text{Log}\left(\frac{\text{Measured}}{10^{-6}}\right) + 6\right)\text{dBuV}$$



Take a break

Any Short Question?




Picking up the noise - LISN

Line Impedance Stabilization Network – ac Only



Simple Mission –
50 Ω to Earth

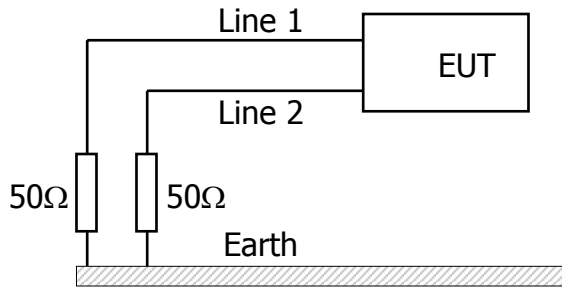


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

43

LISN – a little bit more detail

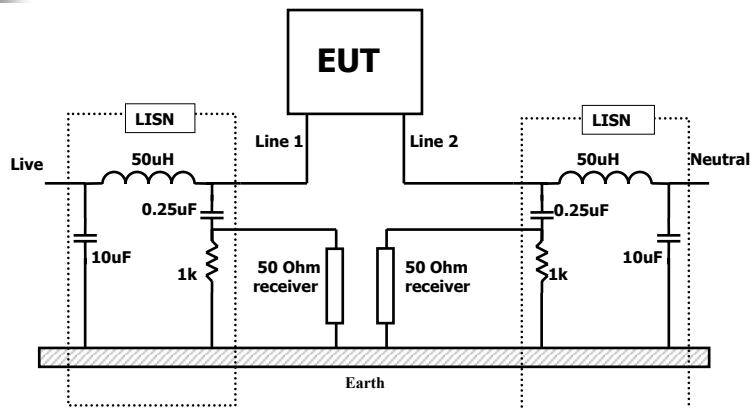


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


www.eee.hku.hk/power_electronics_lab/

44


LISN – detects line to line noise

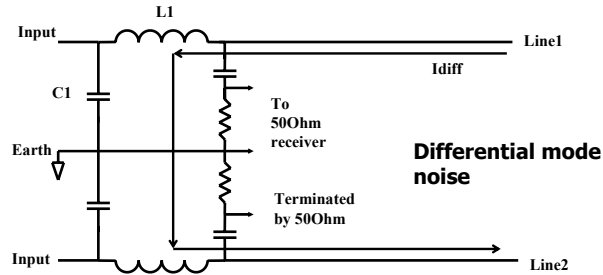

LISN – detects line to earth noise

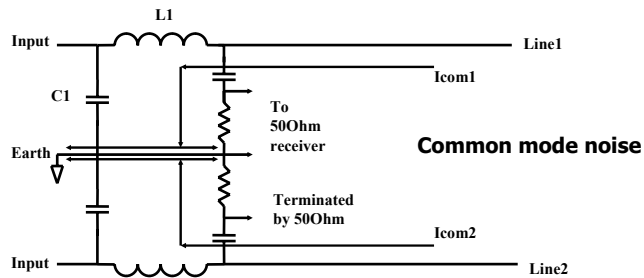

Picking up the noise in space - Antenna

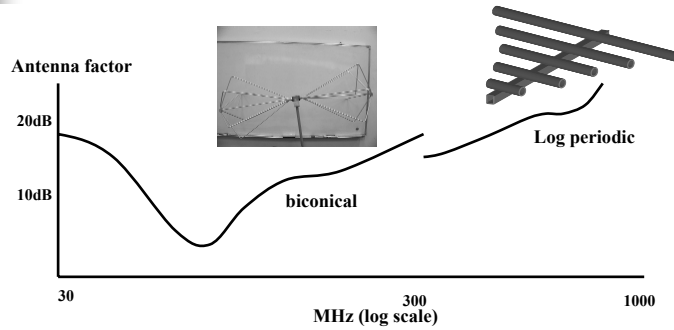


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

47

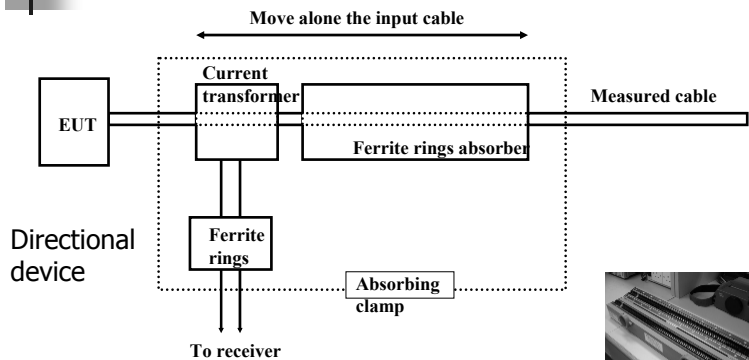Predicting noise to space- Absorption clamp




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

48

Nature of EM Noise

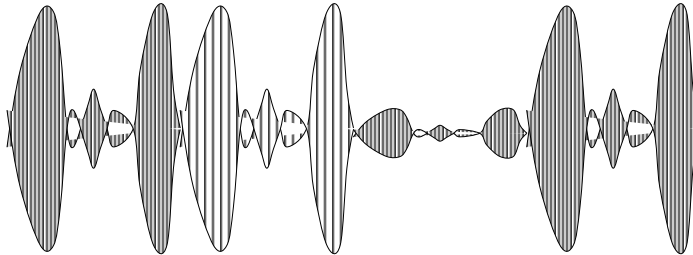

- Time varying
- Amplitude varying
- Frequency varying

It changed – After we have measured it !




Nature of EM noise– Worse, normal and good


- Peak measurement – the worse, measure the peak noise within a period of time.
- Average measurement – the good, measure the averaged noise within a period of time
- Quasi-peak measurement – the normal, between peak and average measurements.



Peak, Quasi-peak, average

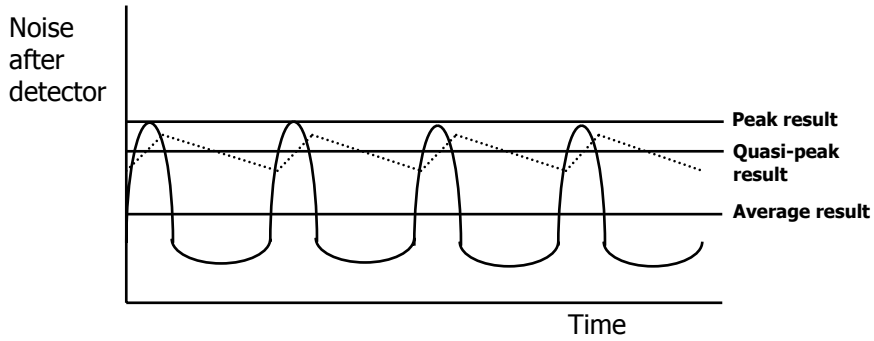


Peak detector – simplified

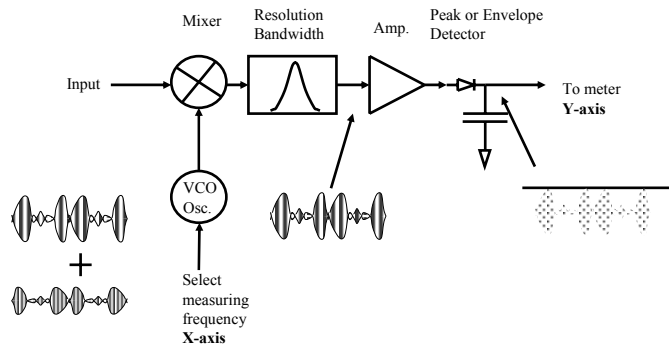

Simplified Peak EMI receiver



Quasi-peak detector – simplified

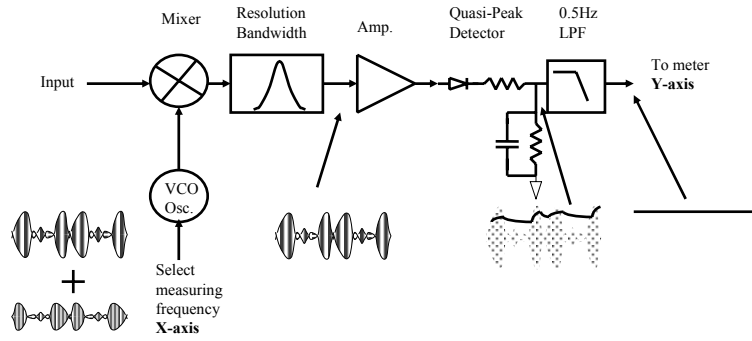

Quasi-Peak EMI receiver




Quasi-peak constant

QP-detector	10 - 150kHz	0.15 - 30MHz	30 - 300MHz	0.3 - 1GHz
6dB bandwidth	0.2kHz	9kHz	120kHz	120kHz
Charge time	45mS	1mS	1mS	1mS
Discharge time	500mS	160mS	550mS	550mS

What happens if the noise occurrence time is less than the charge time ?



Average detector – simplified

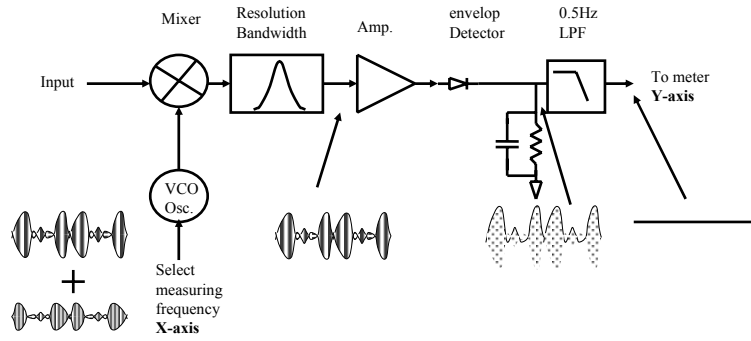


Peak constant ?

QP-detector	10 - 150kHz	0.15 - 30MHz	30 - 300MHz	0.3 - 1GHz
6dB bandwidth	0.2kHz	9kHz	120kHz	120kHz
Charge time	?	?	?	?
Discharge time	?	?	?	?

Don't forget every detector has a charging time constant.



Detector – how long does a signal exist

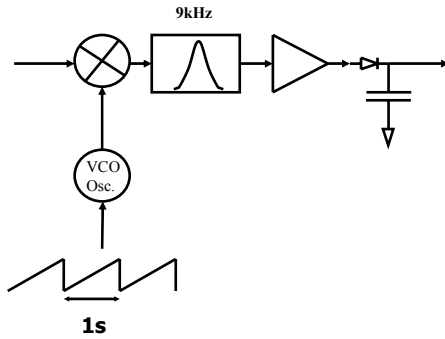

Period for detection at a certain frequency


$$T_{charge} = \frac{BW}{f_{stop} - f_{initial}} T_{sweep}$$

For conducted EMI range and sweep is 1s


$$T_{charge} = 0.3ms$$



Detector – fast and slow sweep

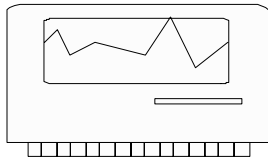

Sweep time = 10 s

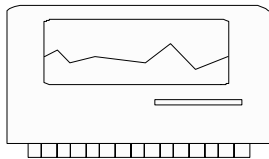

Sweep time = 1 s



Short summary

- LISN, spectrum, receiver, antenna, absorption clamp are introduced.
- Peak detector is used for screen display as it gives fastest response.
- Quasi-peak and average are used in most standards.
- You can cheat the detector or display screen if the noise pop out faster than the charge time.
- Don't be cheated by the screen if sweep time is too fast.




Any Short Question?

From easy to not so easy





Invisible coupling – capacitive

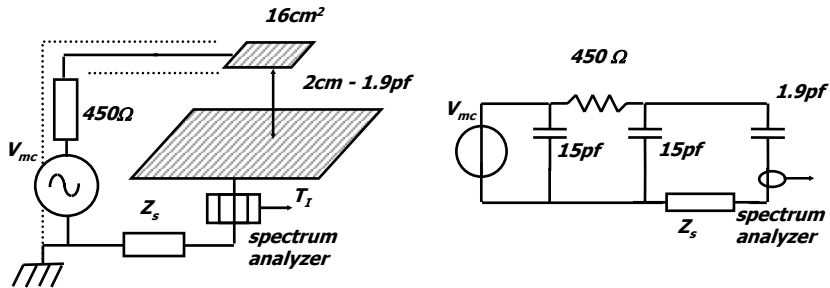


Does a capacitive object work like a capacitor in a circuit ?



Capacitor is capacitor

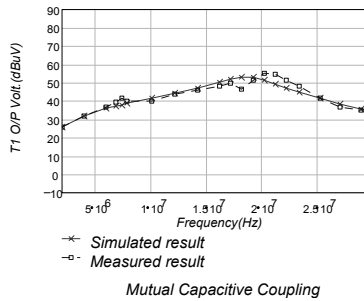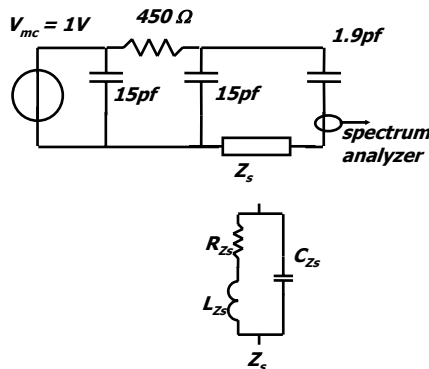

Mutual inductive coupling – transformer

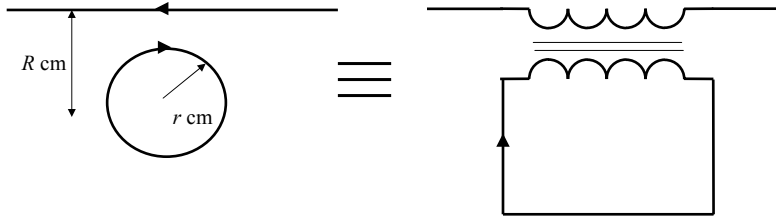


$$L_m = Z_{M_line_loop} = \mu_0 \left[\frac{R}{100} \sqrt{\left(\frac{R}{100}\right)^2 - \left(\frac{r}{100}\right)^2} \right]$$




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Inductive coupling – equivalent model

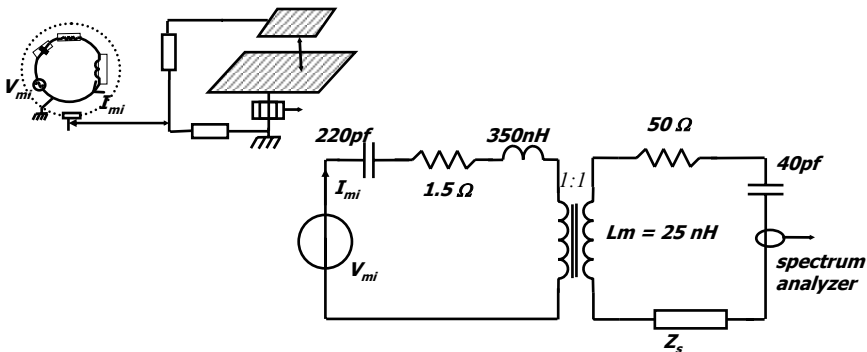


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

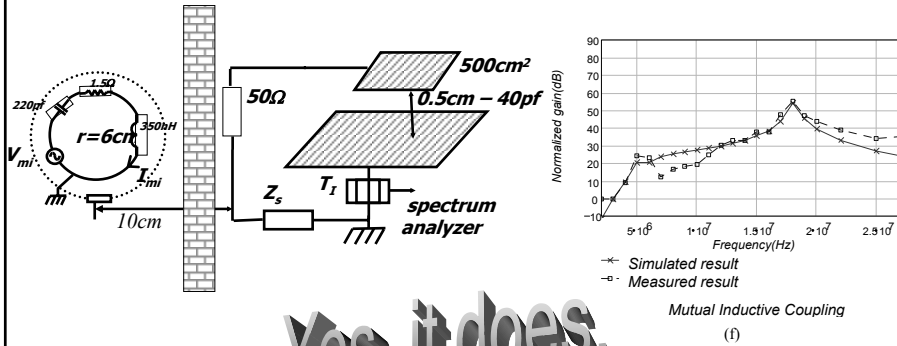Mutual inductive coupling = transformer ?




As an EMI engineer

You don't see this

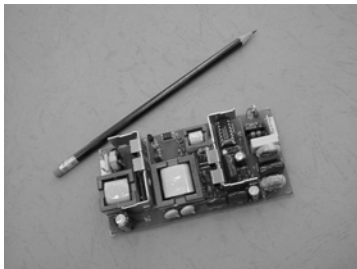

You see this

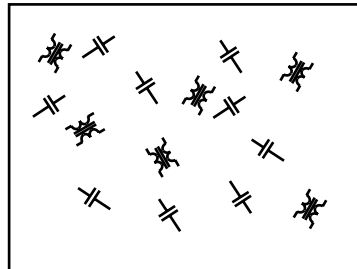


Reminder

- Any two nodes, two objects, two components, two traces ... etc, has an invisible capacitance and capacitive coupling effect
- Any two segments, two loops, two traces, two paths ...etc, produce an invisible transformer and have inductive coupling effect.
- Is there any combination of capacitive-inductive effect?




Capacitive-Inductive effect

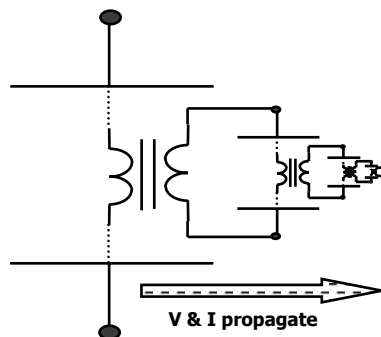

Simple idea of
Electro-Magnetic
wave propagation.



Capacitive coupling – trace to trace

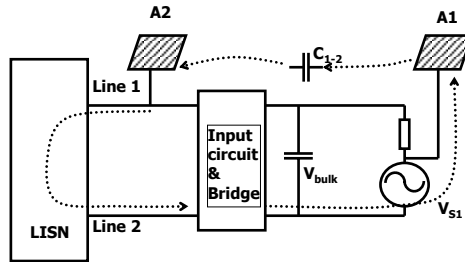

Say


$$C_{1-2} = 0.1\text{pf}$$

$$V_{SI} = 300\text{V}$$

C_{bulk} is blocked by
Input circuit & Bridge



Capacitive coupling – trace to trace

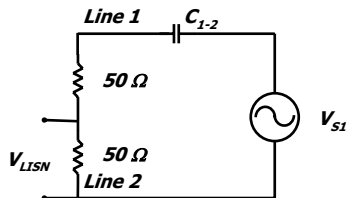

As

$$C_{1-2} = 0.1\text{pf}$$

$$V_{SI} = 300\text{V}$$

At 150kHz

$$V_{LISN} = 1400\text{uV}$$


EN55022 B limit at 150kHz is
630uV

$$V_{LISN} = \frac{50}{50 + 50 + \frac{1}{2\pi f C_{1-2}}} \times 300$$


Already exceeds limit just because of 0.1pf




Capacitive coupling

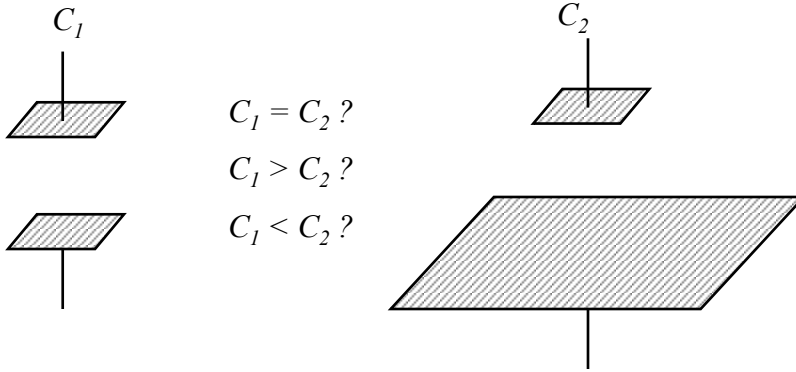

Capacitive coupling – which is bigger

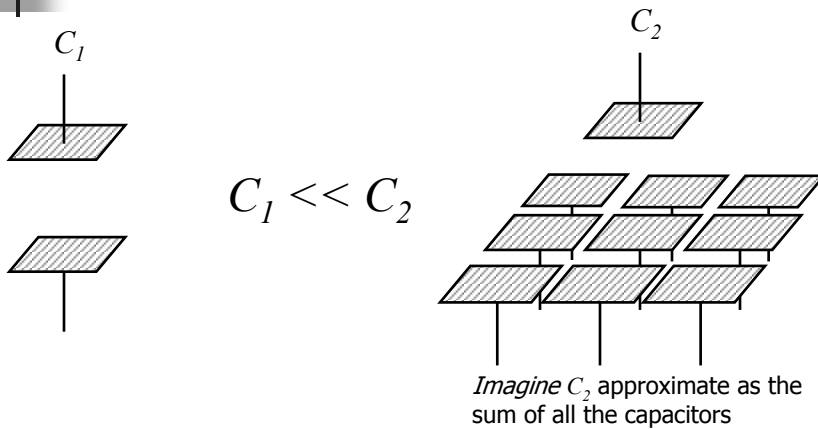

Capacitive coupling – trace to ground

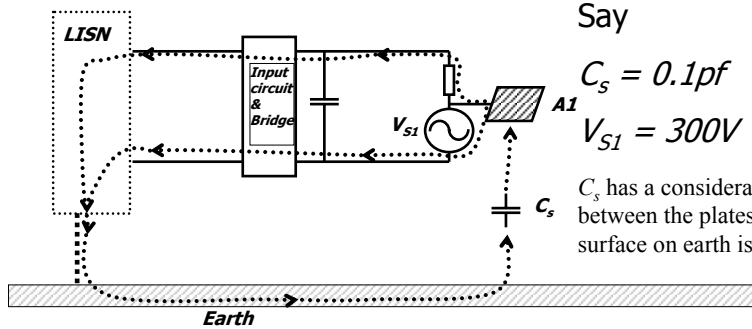

Say


$$C_s = 0.1\text{pf}$$

$$V_{S1} = 300\text{V}$$

C_s has a considerable length between the plates but the surface on earth is very large



Capacitive coupling – trace to ground

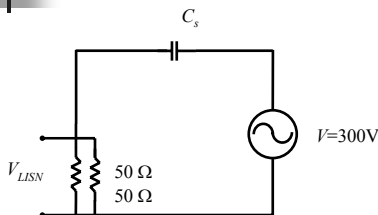

Assume

$$C_s = 0.1\text{pf}$$

$$V_{S1} = 300\text{V}$$

At 150kHz

$$V_{LISN} = 700\mu\text{V}$$


EN55022 B limit at 150kHz is 630 μV

$$V_{LISN} = \frac{50/2}{50/2 + \frac{1}{2\pi f C_s}} \times 300$$


Exceed limit again !




HVHF circuits

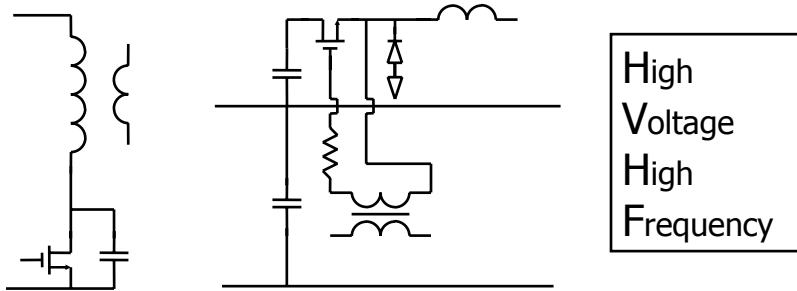

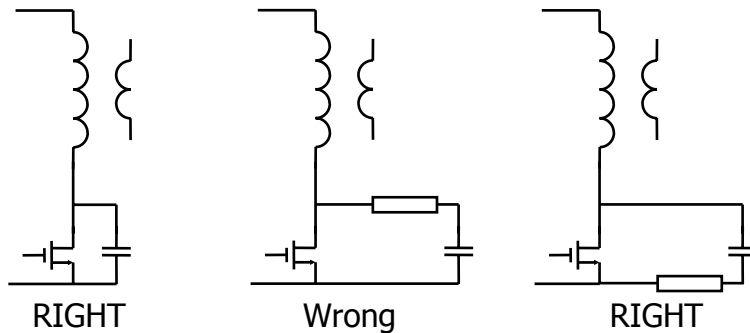
HVHF circuits – reduce to a size As Small As Possible ASAP



Capacitive coupling – PCB trace rule

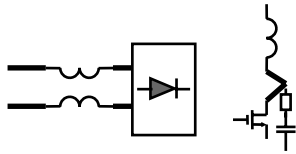


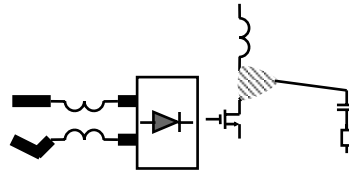
Good – small trace area, symmetrical, good separation



Bad – large trace area, asymmetrical, not enough separation and long connection wire.




Inductive coupling – trace to trace

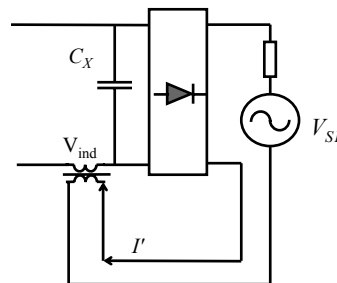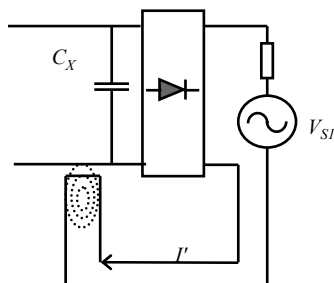

Although the loop has low voltage, it generates other kind of noise.



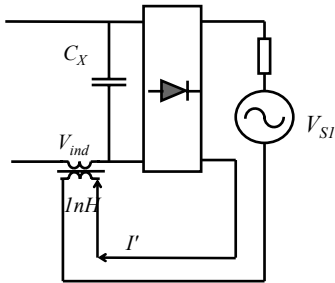Inductive coupling – trace to trace induction



Say

$$L_m = 1nH$$

$$I' = 1A @ 150kHz$$


$$V_{ind} = I' 2 \pi f L_m$$

$$V_{ind} = 940 \mu V$$

C_x gives a low impedance path for the induced current to flow



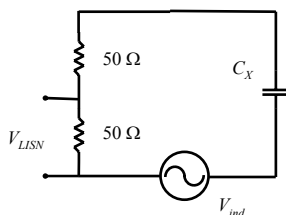Inductive coupling – trace to trace result



Say

$$C_x = 0.1 \mu F$$

At 150kHz

$$V_{LISN} = 460 \mu V$$

EN55022 B limit at 150kHz is
630 μV


$$V_{LISN} = \left| \frac{50}{50 + 50 + \frac{1}{2\pi f C_x}} \right| \times 940 \mu V$$

Very close to limit!




Inductive coupling – the trace itself

• Self inductance

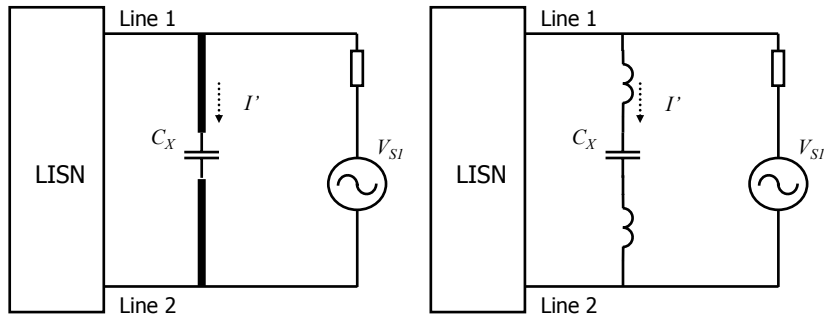

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

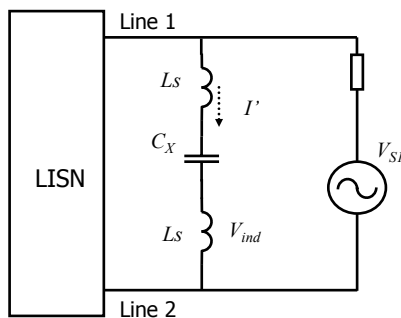Inductive coupling – trace induced voltage



Let say

$$L_m = 10nH$$

$$I' = 1A @ 150kHz$$

$$V_{ind} = I' 2 \pi f L_s$$

$$V_{ind} = 9400 \mu V$$


EN55022 B limit at 150kHz is
630uV

Is it horrible ?



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Inductive coupling – PCB trace rule

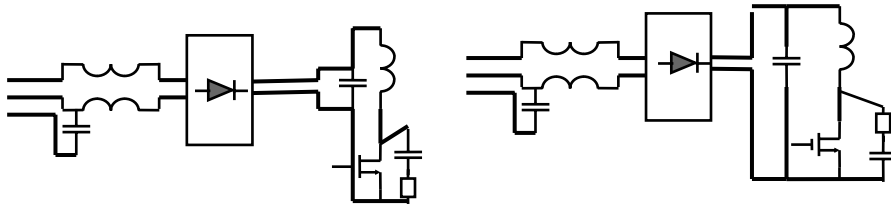


Good – small loop area, good separation between loops, node terminated at capacitor terminals

Bad – large loop area, short separation between loops, nodes are not terminated at capacitor terminals




Typical capacitor and inductor parameter values

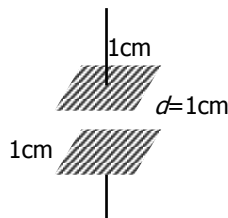
$$C = 0.085A/d \text{ pf} \quad L = 0.002(\ln(2l/r) - 0.75) \text{ uH} \quad Lm = 0.002(\ln(2l/D) - 1 + D/l) \text{ uH}$$



C = 0.0885pf

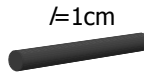

L_{avg18} = 5.8nH

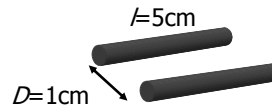

Lm_{avg18} = 15nH



Short conclusion

- Very small capacitor may cause serious capacitive coupling effect
- Very small inductor may cause serious inductive coupling effect, either mutual or self inductive coupling.
- Very small pieces of object may cause devastating magnitude of capacitance or inductance.




Any Short Question?

From not so easy to difficult




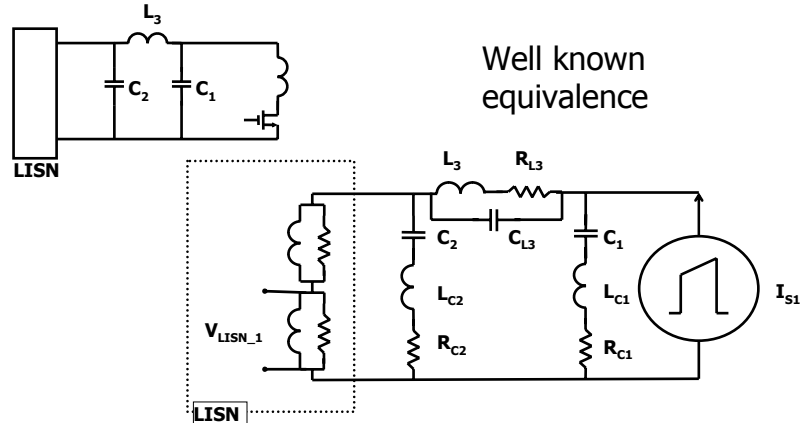An obvious noise source – input ripple current




Input ripple current – simulation

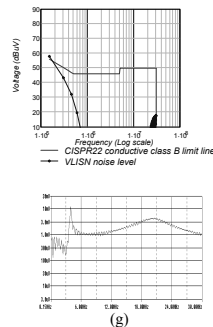
- Don't be scared by complicated circuit.
- You don't need to calculate for the answer.
- You ONLY need to simulate it's result. SPICE, Math software. . . etc may help



Input ripple current – typical result

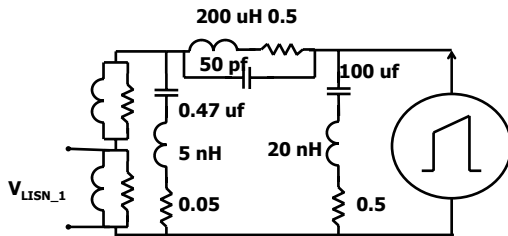


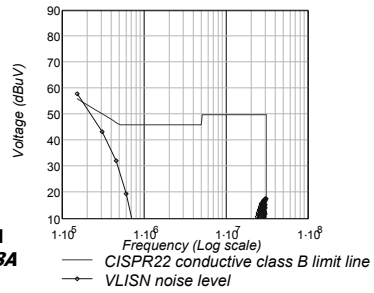$I_{S1_inj} = 0.5A$
 $I_{S1_peak} = 0.8A$
 $t_r = 50 ns$
 $t_{on} = 2 us$
 $T = 6.6 us$




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input ripple current – ideal C_1


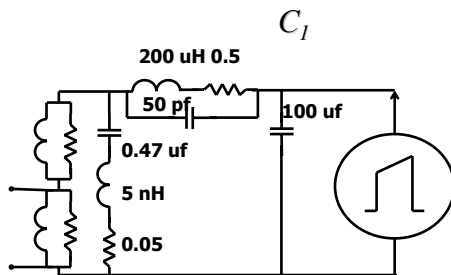


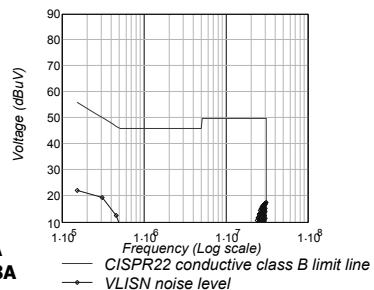$I_{S1_inj} = 0.5A$
 $I_{S1_peak} = 0.8A$
 $t_r = 50 ns$
 $t_f = 50 ns$





Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input ripple current – ideal C_2

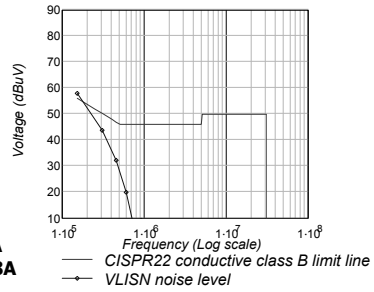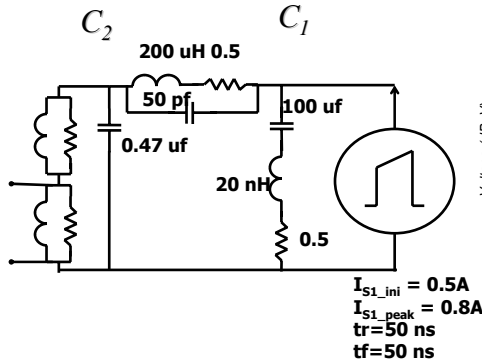

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


Input ripple current – ideal L_3

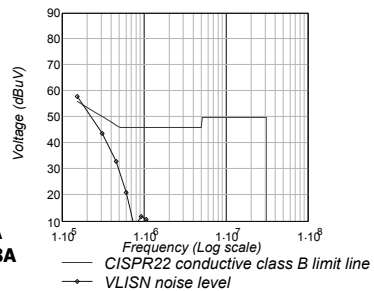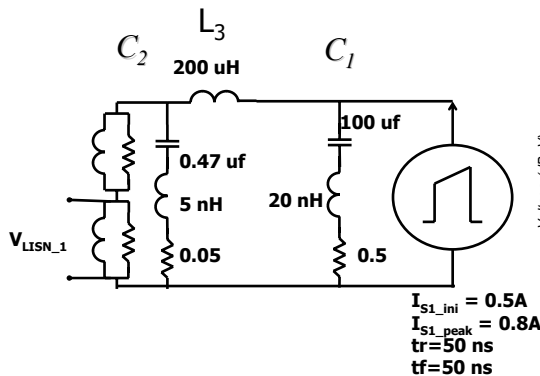


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input ripple current – swap C_1 , C_2



L_3 less rms current

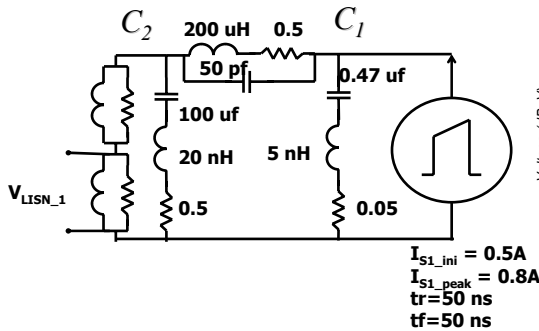


Not much difference

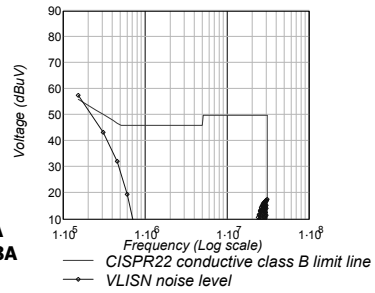

Input ripple current – ideal C_1 again

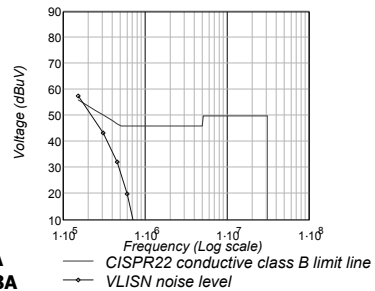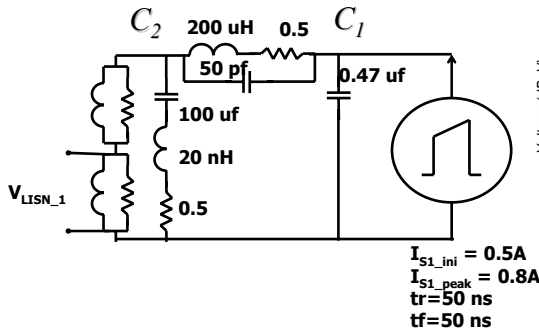

Input ripple current – ideal C_2 again

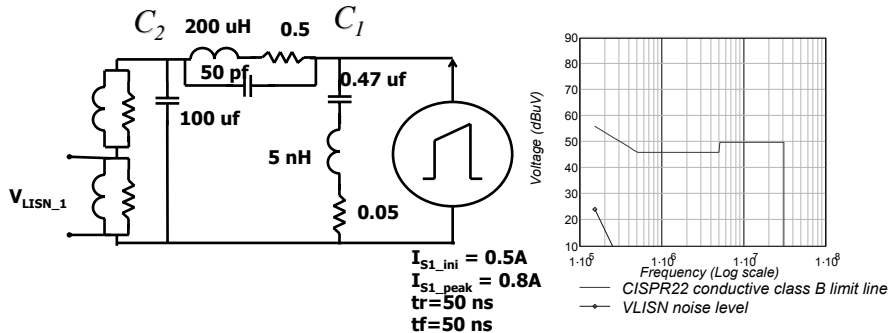

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

97

Input ripple current – short summary

- Realistic equivalent circuit has difference with ideal elements.
- Equivalent series resistance of a capacitor contribute to low frequency EMI.
- Equivalent series inductance of a capacitor contribute to high frequency EMI.
- Perfect the components with largest value is very effective. E.g. 100 μF




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/


98

Input ripple current – two stage design

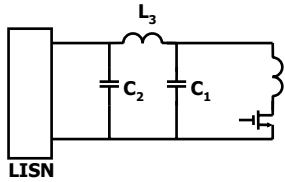


Add one more stage ?

Wait a minute !

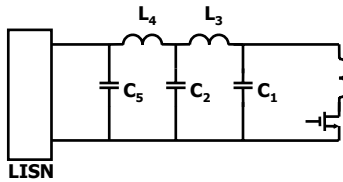


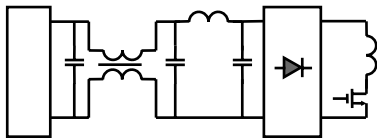Input ripple current – make use of leakage




There is a Common Mode Choke (CMC) anyway.

Make use of it's leakage inductance !

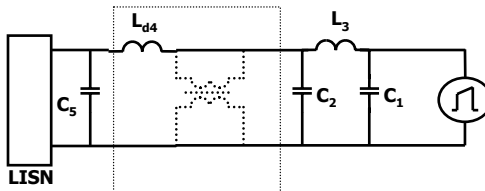


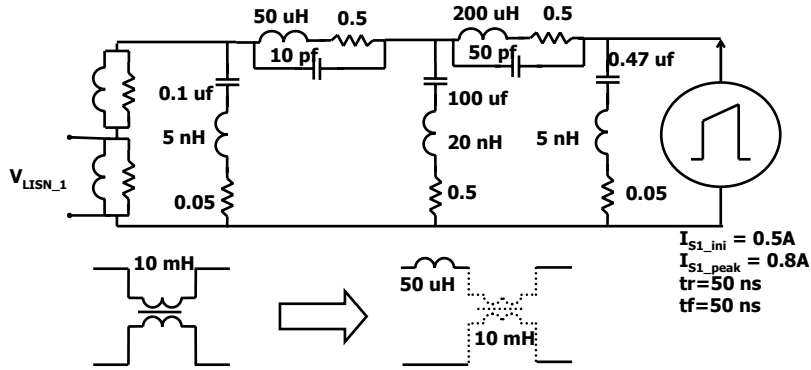Input ripple current – two stage equivalence




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input ripple current – two stage result

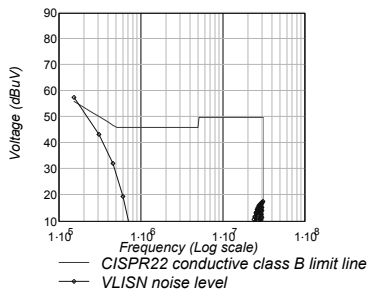

Single Stage Filter

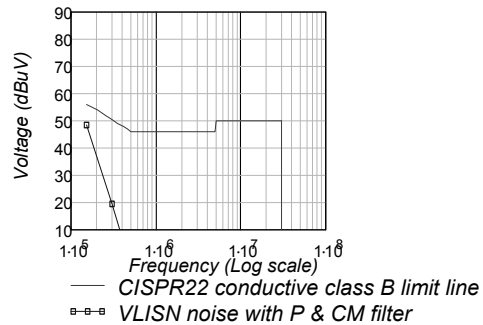


Two Stage Filter




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input ripple current – common trick

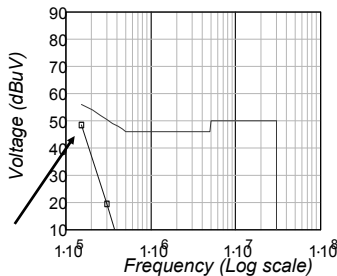

— CISPR22 conductive class B limit line
 □-□-□ VLISN noise with P & CM filter

$f_s = 150\text{kHz}$, 8 dB margin



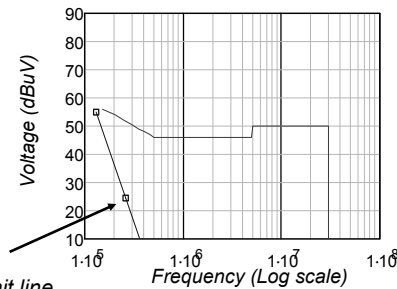


— CISPR22 conductive class B limit line
 □-□-□ VLISN noise with P & CM filter


$f_s = 130\text{kHz}$, 30 dB margin



Input ripple current – Disappears

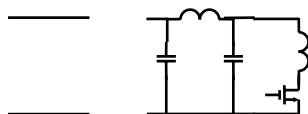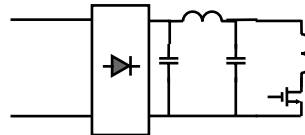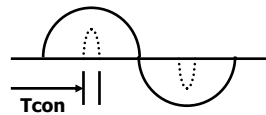


Beyond conduction time $t \neq T_{con}$

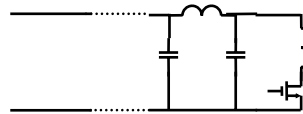

During conduction time $t = T_{con}$



Input ripple current – average result

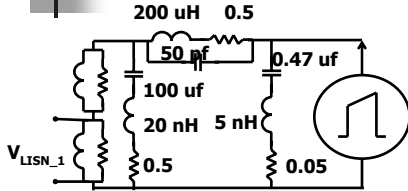


$$V_{LISN_peak} = V_{LISN_dc}$$

$$V_{LISN_quasi-peak} = V_{LISN_dc}$$


$$V_{LISN_average} = V_{LISN_dc} \frac{2T_{con}}{T_{line}}$$

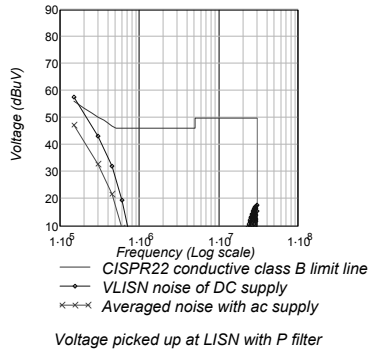Assuming conduction time $T_{con} = 3 \text{ ms}$





Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

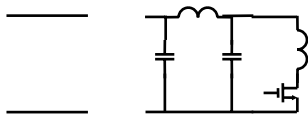
At different time – different equivalent circuit



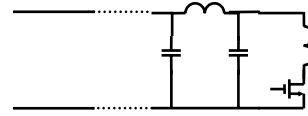
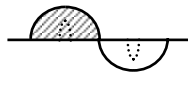
Beyond conduction time $0 < t < \pi$
and $t \neq T_{con}$



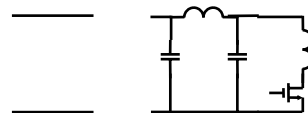During conduction time $0 < t < \pi$
and $t = T_{con}$



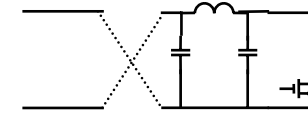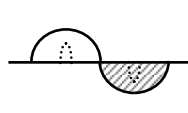Beyond conduction time $\pi < t < 2\pi$
and $t \neq T_{con}$




During conduction time $\pi < t < 2\pi$
and $t = T_{con}$

Apply to all analysis !!



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input ripple current – stability

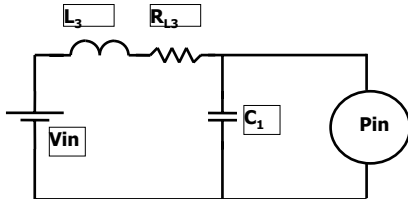

- big C_1 is good
- big R_{L3} is good
- small V_{in} is bad
- large L_3 is bad



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

As input of converter is a power source P_{in} .


Approximate the differential Eqn.

$$\frac{d^2 v_{C1}}{dt^2} + \left[\frac{R_{L3}}{L_3} - \frac{P_{in}}{v_{C1}^2 C_1} \right] \frac{dv_{C1}}{dt} + \frac{v_{C1}}{L_3 C_1} = \frac{V_{in}}{L_3 C_1}$$

Keep first order coefficient > 0

$$\frac{R_{L3}}{L_3} > \frac{P_{in}}{v_{C1}^2 C_1}$$

Input filter – stability issue

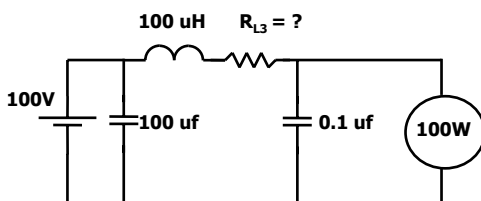

$V_{in} = v_{C1}$ approximately

$$\frac{R_{L3}}{L_3} > \frac{P_{in}}{v_{C1}^2 C_1}$$

$R_{L3} > 10\Omega !!$

Usually winding resistance
 $R_{L3} = 0.2 \Omega$

Every converter should oscillate !! But . . .




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input filter – why usually stable ?


- Because skin effect increases the winding resistance – WRONG
- Because proximity effect increases the winding resistance – WRONG
- Because parasitic capacitor inhibits the oscillation – WRONG
- Because the inductor is no longer an inductor – Meaningless



Input filter – what ac inductor is

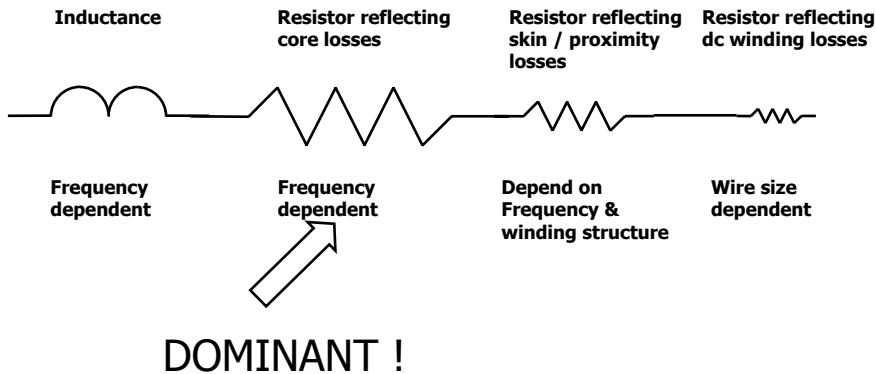

Input filter – core losses issue

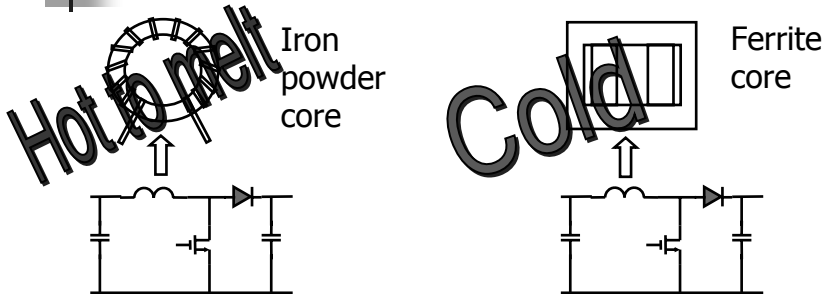

Every engineer know core losses is significant, don't ignore the ac resistor reflecting core losses.




Input filter – why usually stable ? again

- Because core losses of the filtering inductor provide extra resistance – RIGHT.
- Because the higher the inductance, the higher the core losses resistance – RIGHT.
- Because the capacitor C_1 is usually bigger than the example – RIGHT.
- Because the oscillating frequency may fall out of regulating region of the converter, and becomes a circuit with positive resistance – MAY BE.




Input filter = Input magnetic receiver

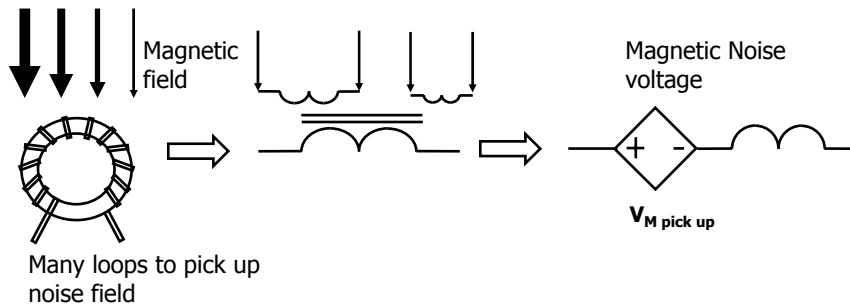- Recall the idea of inductive coupling and mix it with the filter.



Input filter = Input electric receiver

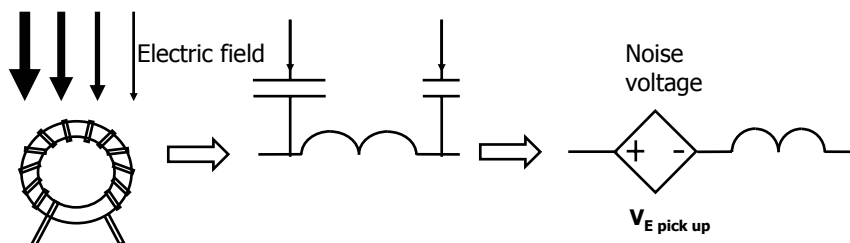- Recall the idea of capacitive coupling and mix it with the filter.




Input filter – summary


- Leakage inductance can be made used for ripple current filtering.
- Choose low ESR for big capacitor.
- Conduction angle or boost PFC yield lower average value than seen on screen.
- Input filtering circuit is also a receiver circuit.
- Core losses resistor is introduced



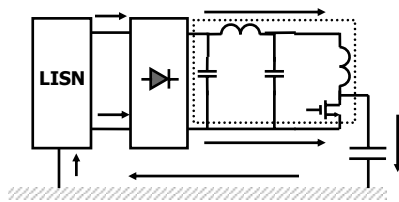Invisible path – drain to earth capacitor






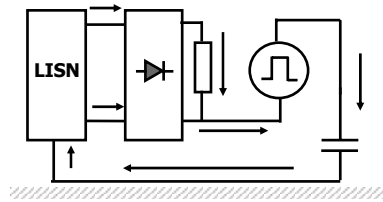
Simplified circuit showing drain to earth capacitor causing invisible current flow




Equivalent circuit using equivalent input resistance and equivalent voltage source



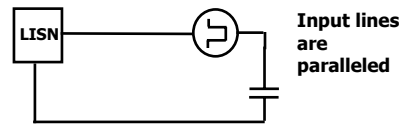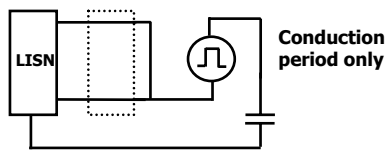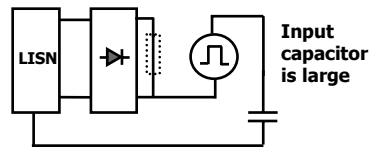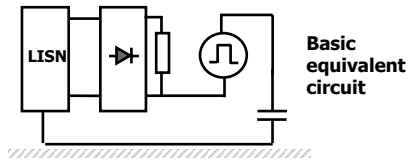Drain to earth capacitor – equivalent model



Drain to earth capacitor – how large?

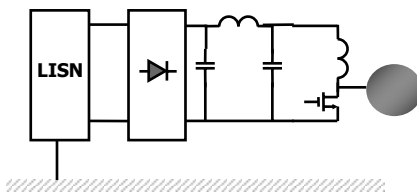

Let the total surface area attach to the drain is equal to a sphere with 1cm² surface area.

Equivalent radius r


$$r = 0.28\text{cm}$$

As the self capacitance of a sphere of r cm

$$C_{\text{sphere}} = 4\pi \cdot 0.0885r \text{ pf}$$

The equivalent drain self capacitance is

$$C_{\text{drain}} = 0.31 \text{ pf}$$

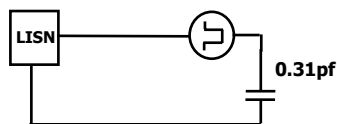

Drain to earth capacitor – simulation


V_{peak} = 400 V

Tr = 50 ns


Tf = 50 ns

Pw = 2 us

Per = 6.6 us

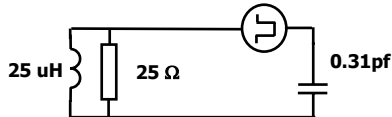

Fails just because of 0.31 pf !

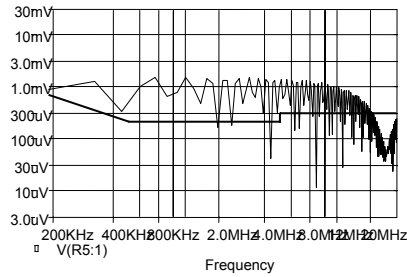

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

119

Filtering – doesn't work ?


V_{peak} = 400 V

Tr = 50 ns


Tf = 50 ns

Pw = 2 us

Per = 6.6 us

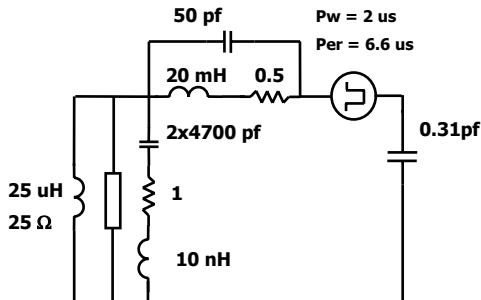

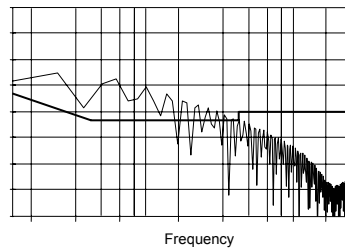What's wrong? It must be the CMC stray capacitor.




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


www.eee.hku.hk/power_electronics_lab/

120

Filtering – parasitics not crucial

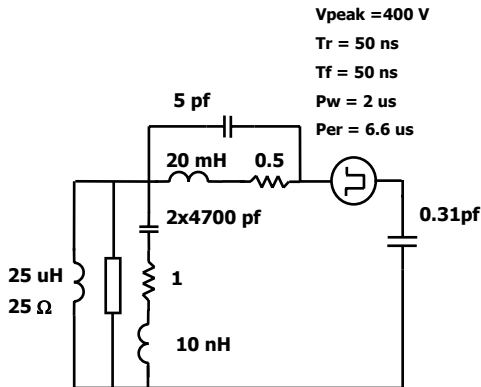


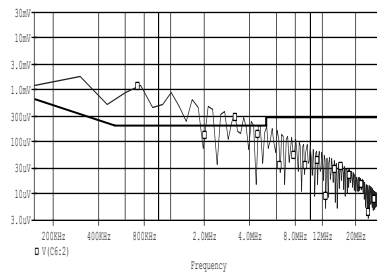What's wrong? Beware of the LISN impedance




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Filtering – right filter design

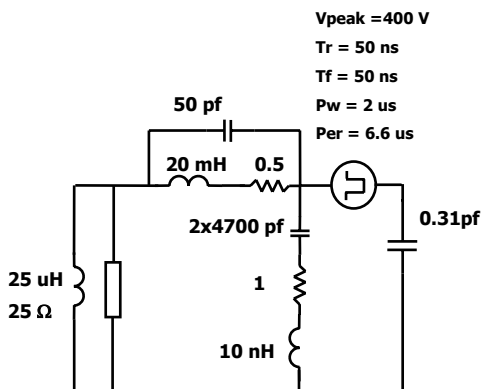


DONE !

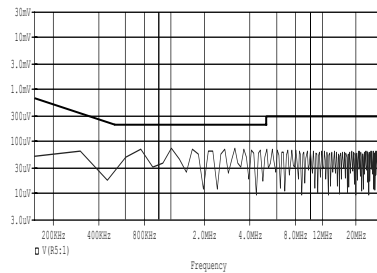


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Filtering – wrong filter design again

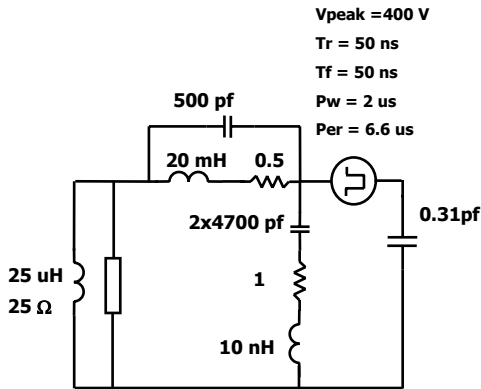


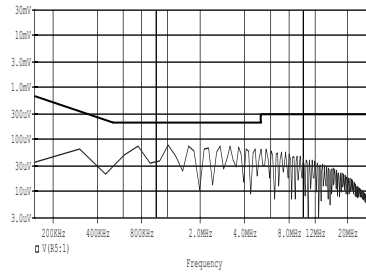Don't always blame the parasitic elements




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Filtering – how small it can be ?

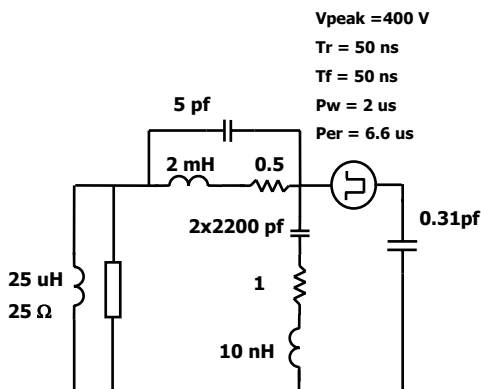


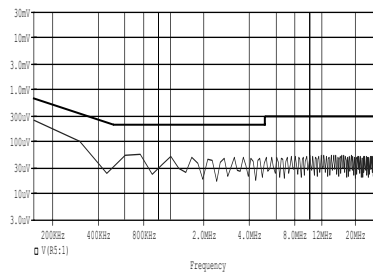A very small filter can filter out the noise !!




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


Filtering – simplified view

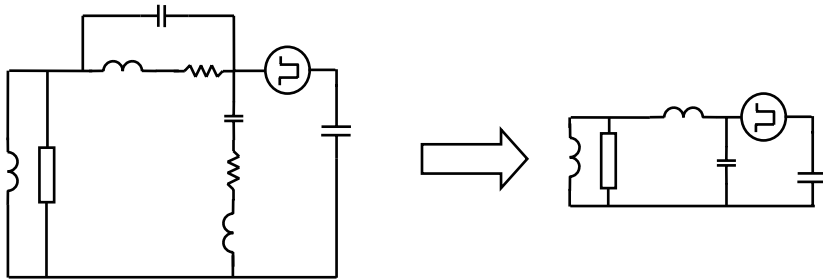



Filtering – get back to the real circuit

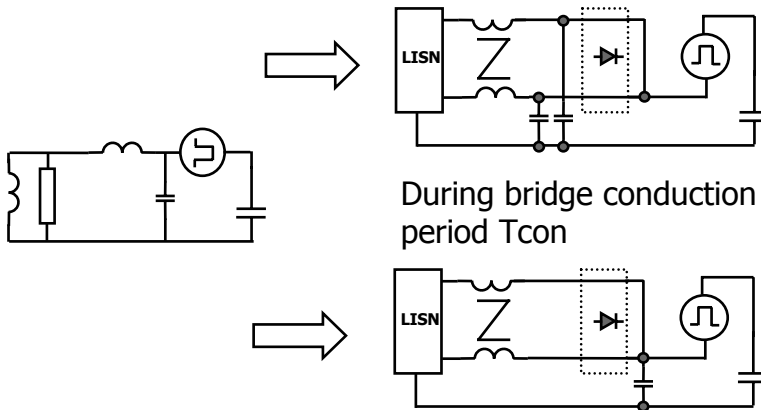


Filtering – get back to the real circuit

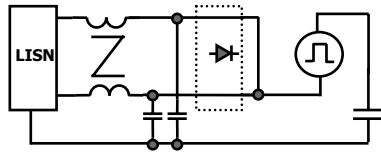


During bridge conduction period T_{con}

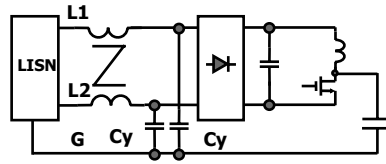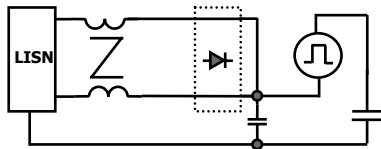



Practical Look

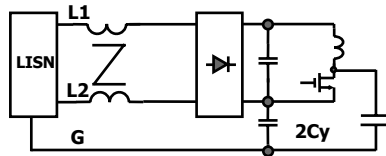

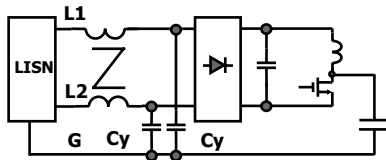
Filtering – are the two practical circuit equivalent?




Practical Look

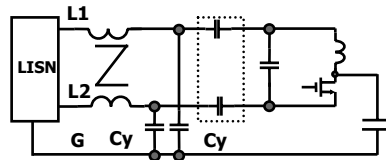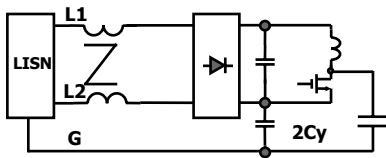

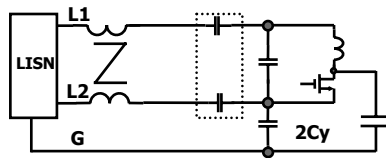
During bridge non-conduction period $t \neq T_{con}$



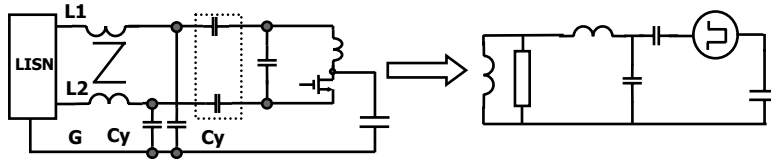Two different filters – go to their equivalence




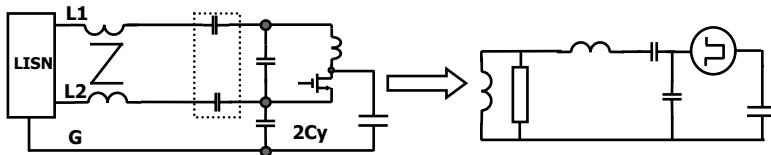During bridge non-conduction period $t \neq T_{con}$





Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

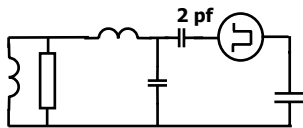Two different filter – Cy on the left hand side




Not bad during non-conduction period

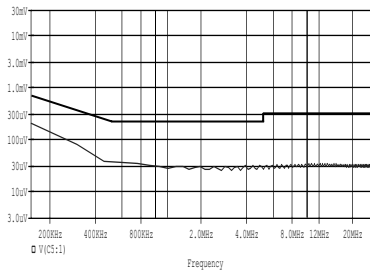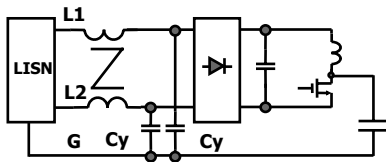


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

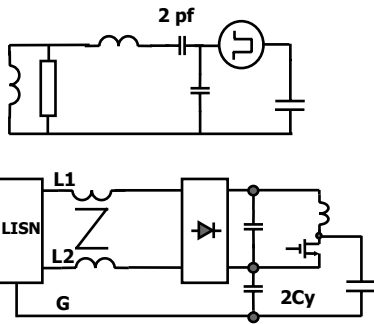Two different filter – Cy on the right hand side





Better during non-conduction period


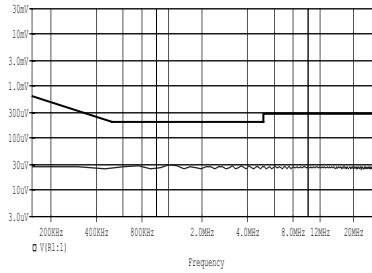


Two different filters – left and right


High Z loop High Z loop

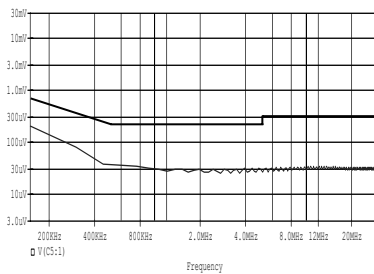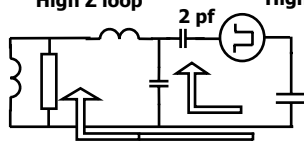


High Z loop Low Z loop

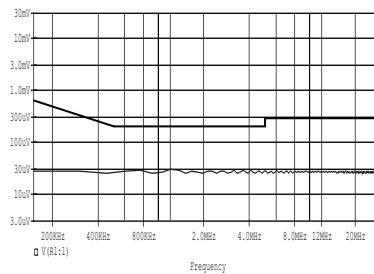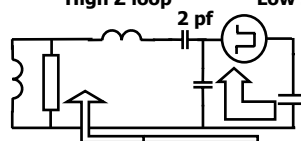

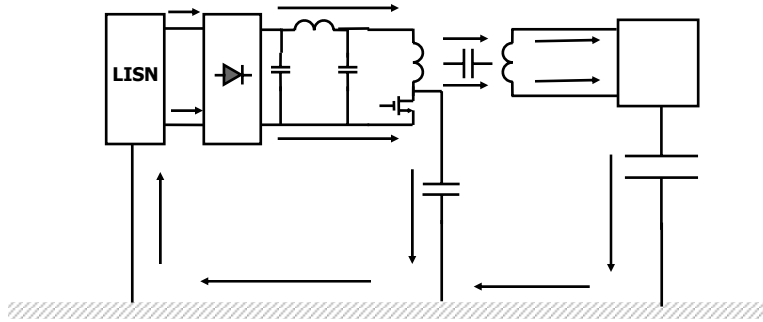
Invisible path – Secondary to earth capacitor



Sec. to earth capacitor – circuit model

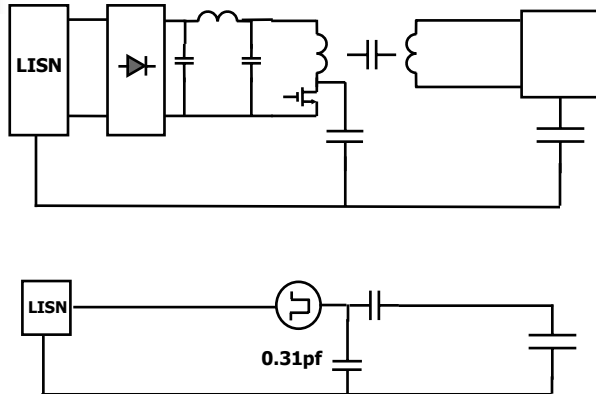


Sec. to earth capacitor – how big ?

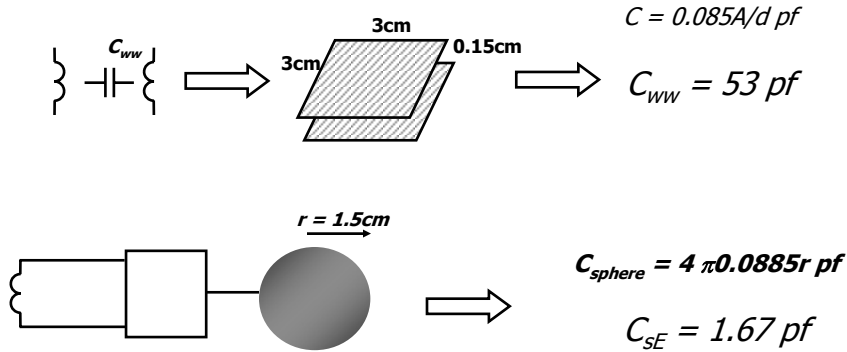


Sec. to earth capacitor – rare noise

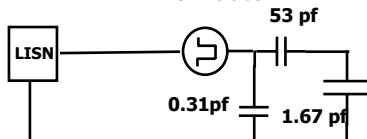
V_{peak} = 400 V
T_r = 50 ns
T_f = 50 ns
P_w = 2 us
Per = 6.6 us



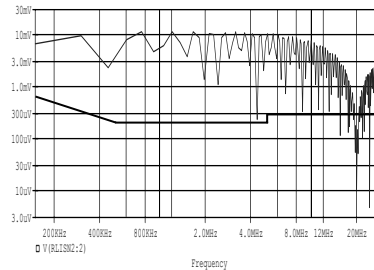
Greatly exceeds limit – usually come across in bad designs.



Sec. to earth capacitor – with filter

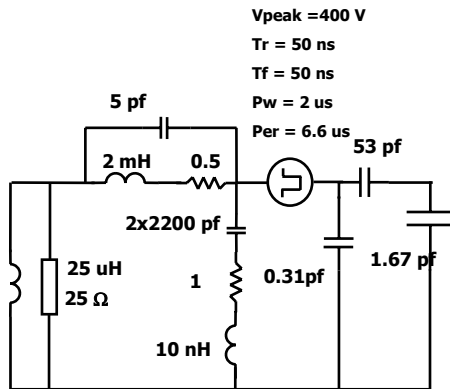


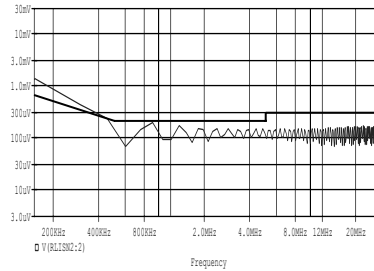Still exceeds limit even after filter is added.



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

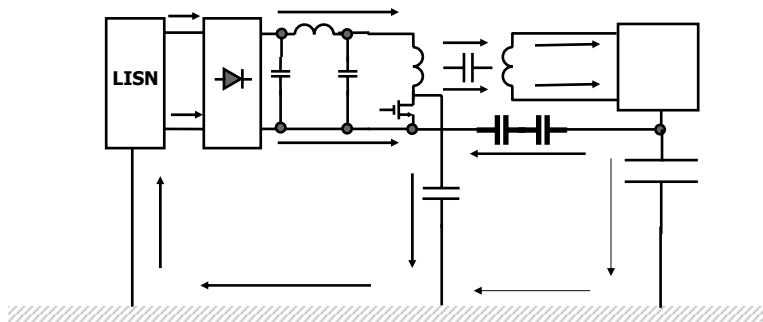Sec. to earth capacitor – Pri. To Sec. Capacitor




The primary to secondary capacitor can pass the noise current generated from the primary side.




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Pri. To Sec. Capacitor – circuit model

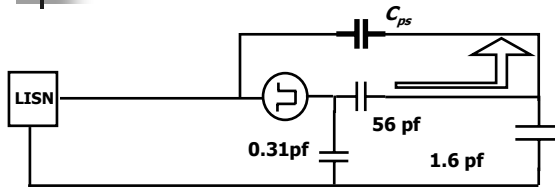

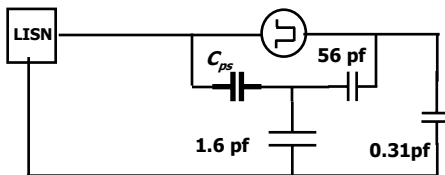Provide a low impedance path to shunt or by pass the current flowing to earth




Or you can interpret C_{ps} as dividing down the noise voltage




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Pri. To Sec. Capacitor – save power

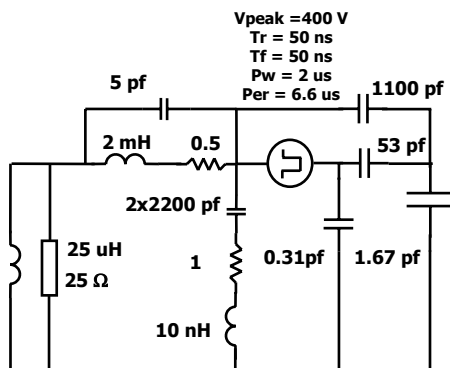


$V_{peak} = 400\text{ V}$
 $T_r = 50\text{ ns}$
 $T_f = 50\text{ ns}$
 $P_w = 2\text{ us}$
 $Per = 6.6\text{ us}$

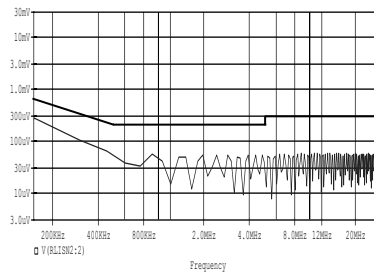Much better solution as no extra power losses is produced.




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


Pri. To Sec. Capacitor – drawback

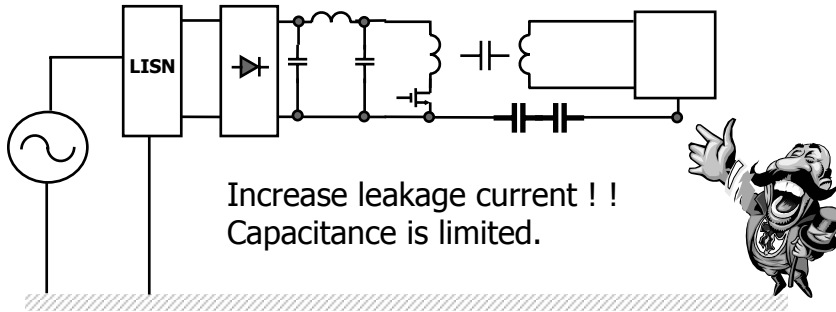

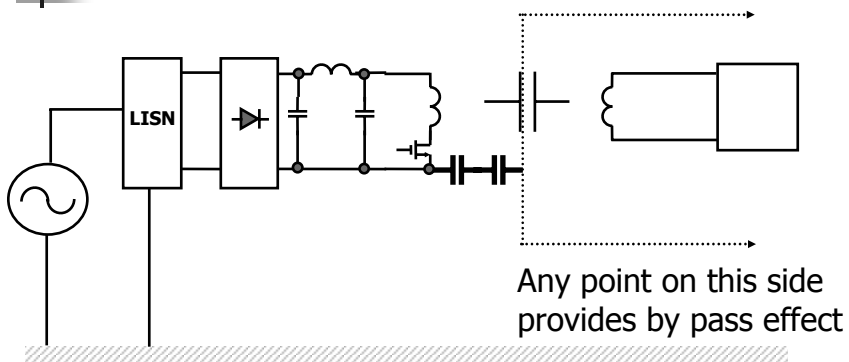Sec. to earth capacitor – by pass elsewhere



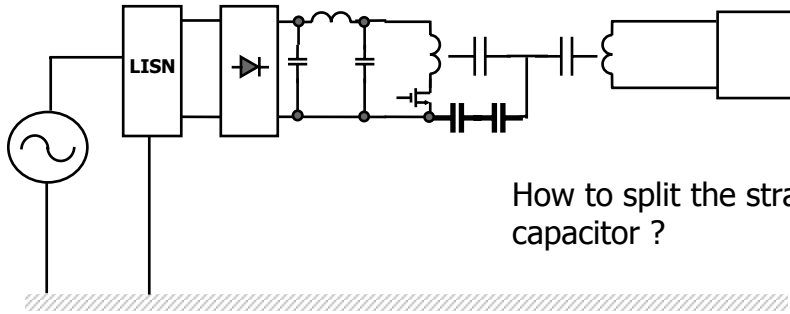
Sec. to earth capacitor – by pass inside ?




How to split the stray capacitor ?




Sec. to earth capacitor – F.5 physics

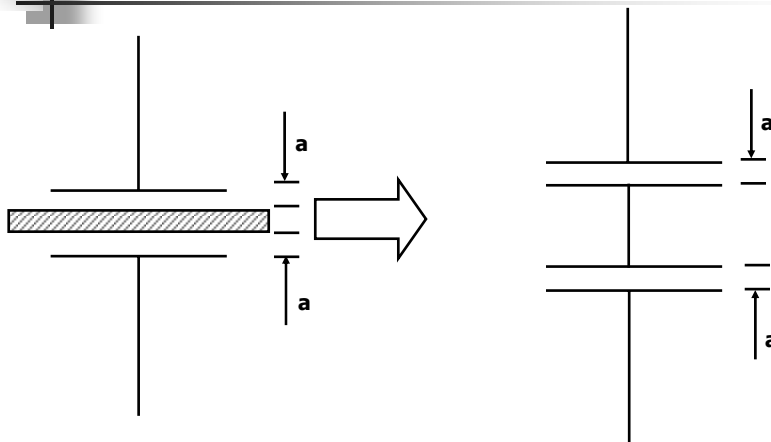

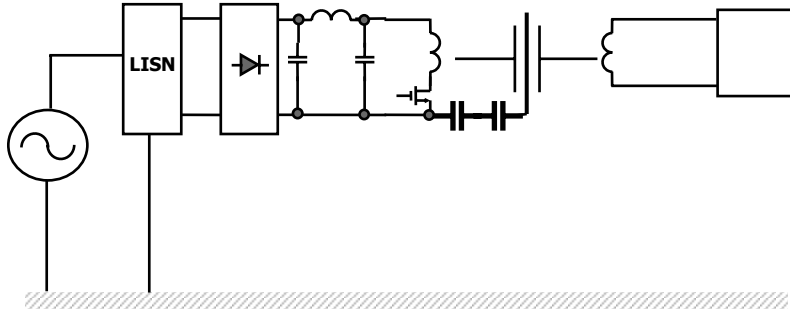
Sec. to earth capacitor – add one more plate



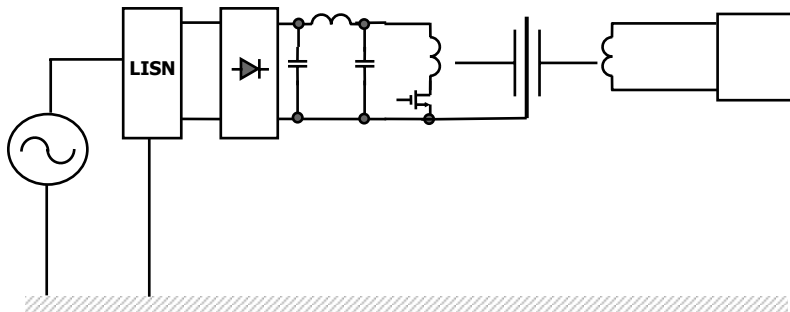
Sec. to earth capacitor – better way to by pass



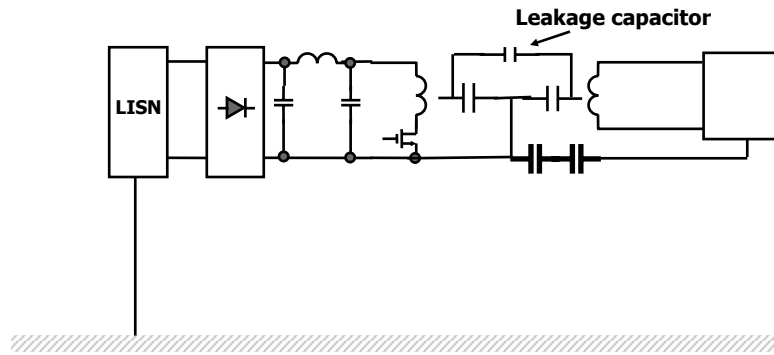
Sec. to earth capacitor – use both methods



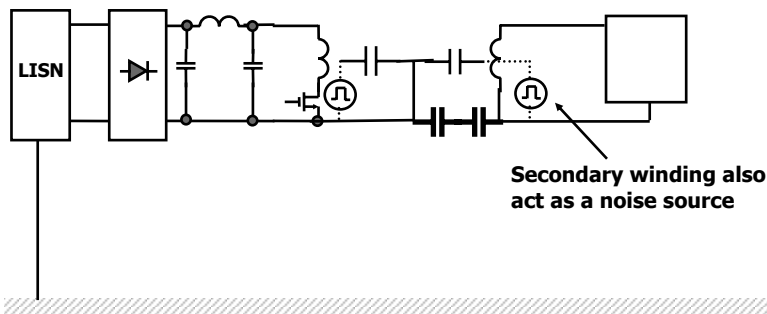
Sec. to earth capacitor – another noise source



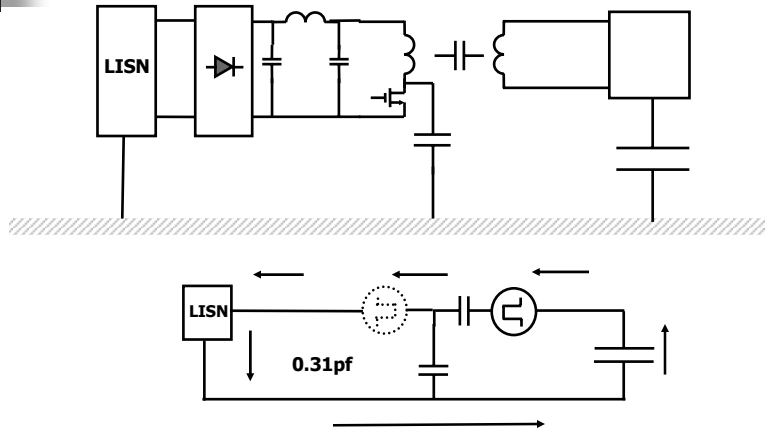
Sec. to earth capacitor – noise source on Sec. side




Sec. to earth capacitor – final solution

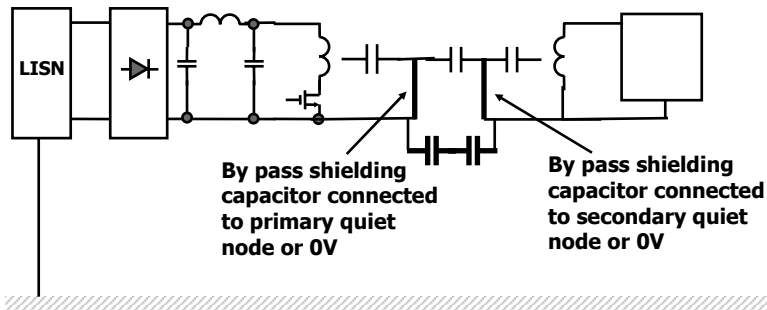


By pass or simply short circuit

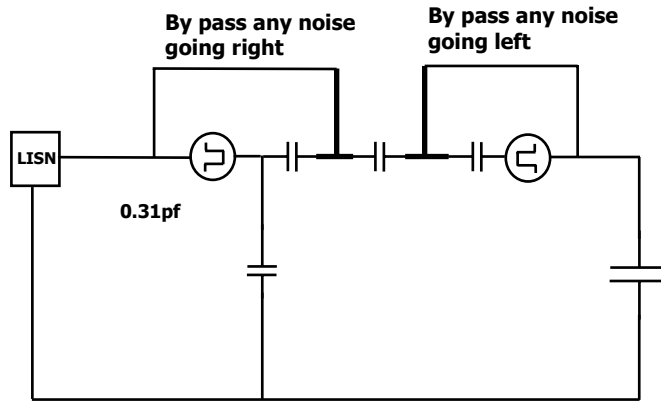

Don't forget the leakage capacitors

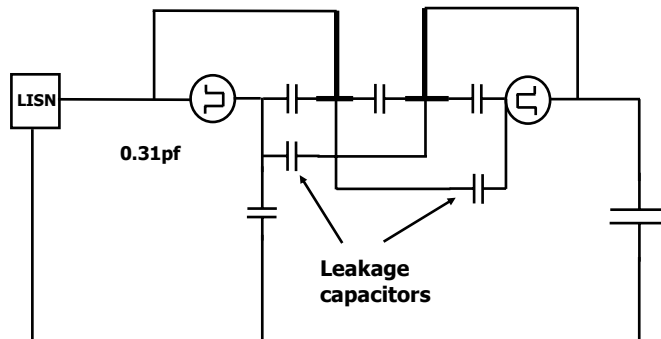


Shielding, by pass or short circuit ?

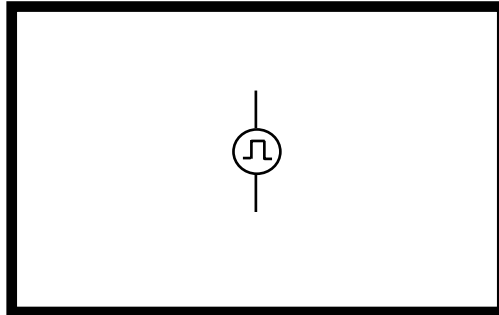


Does it "shield" all the noise going out ?



Revision again - 1

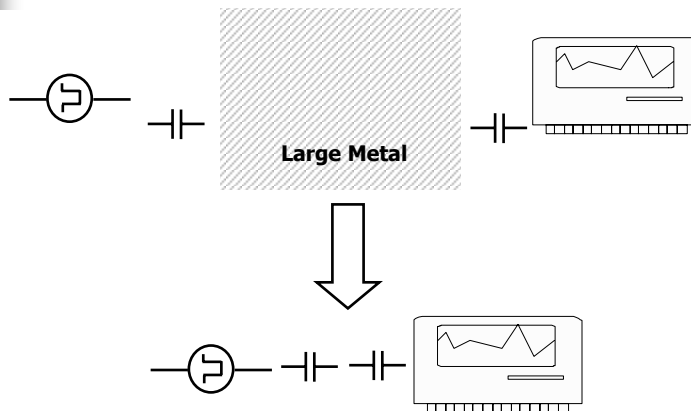


Revision again - 2

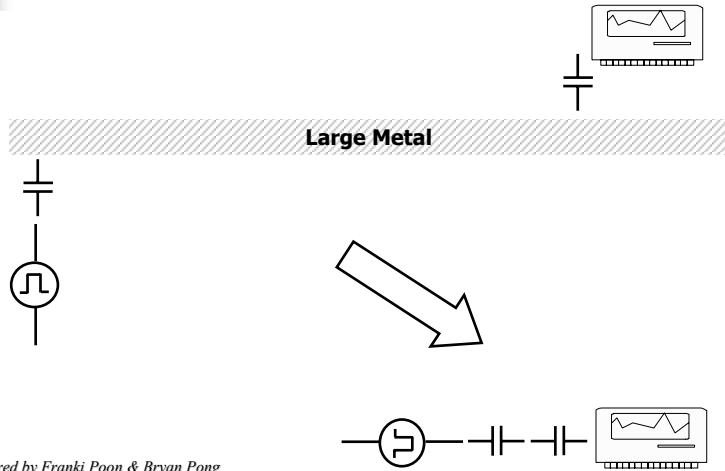


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Don't float the metal plate

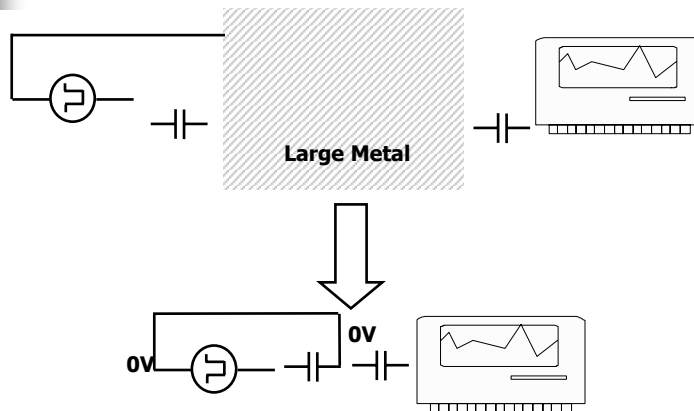


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

By pass and short circuit

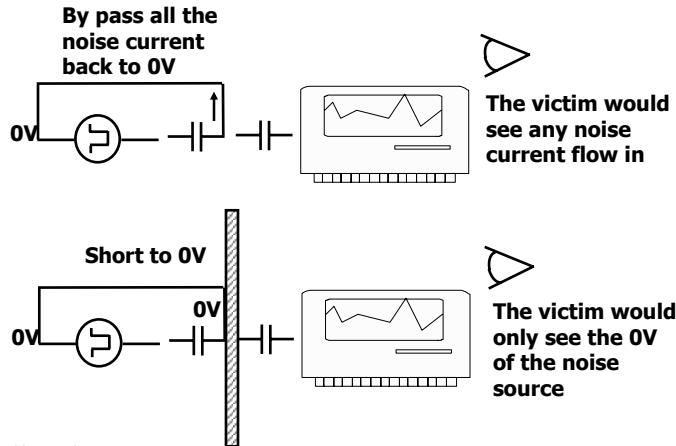

Wait a minute

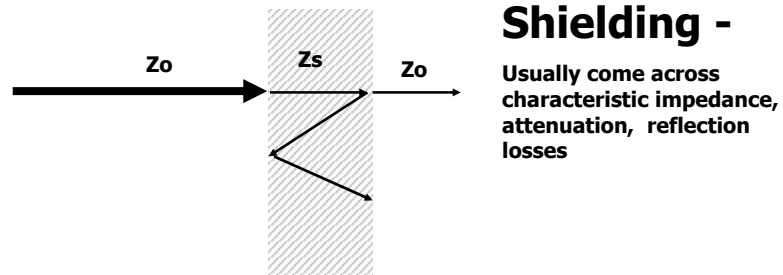


The Truth is -

Plane wave propagation, or noise source is located at a far distance from the shield.



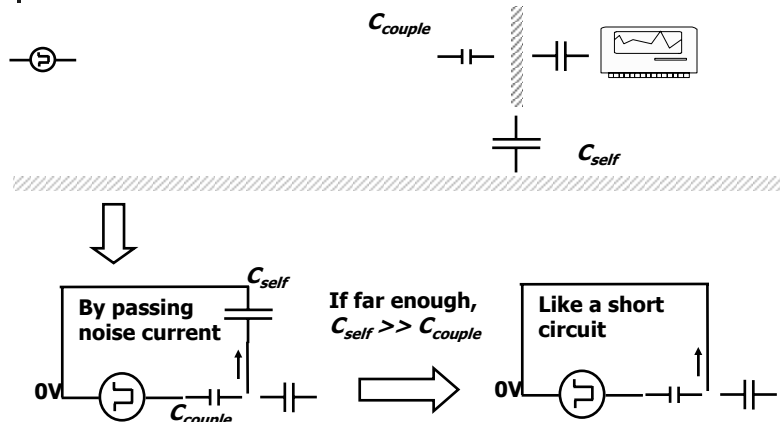Still use by pass and short circuit concept



Short summary


- Lump element circuit is possible to simulate EMI behavior.
- Parasitic elements is not enough to explain all cases. (More concept will be introduced.)
- So call electric field shielding must be terminated one end to a quiet node or 0V of the noise source. NO FLOATING !
- So call electric field shielding is a kind of by pass, shunt or short circuit equivalent in a lump element model.



Any short question ?




Input terminal – conduction period

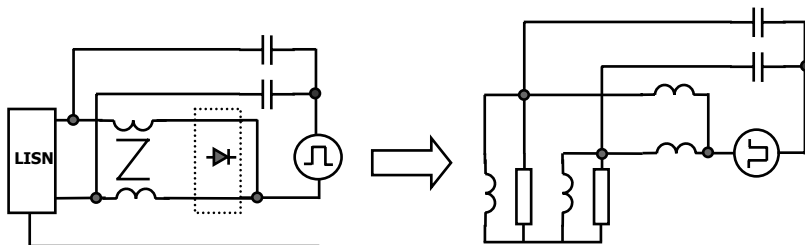

During bridge conduction
period $t = T_{con}$



Input terminal – non-conduction period

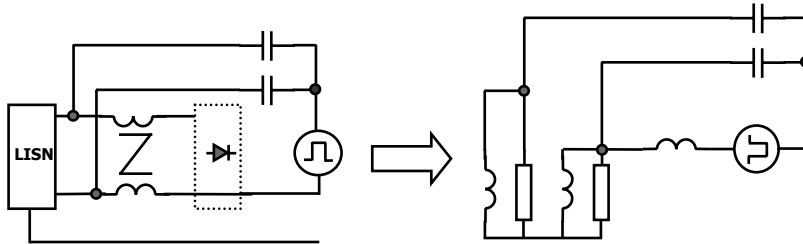


During bridge non-conduction period $t \neq T_{con}$

Even worse




Input terminal – coupling capacitor

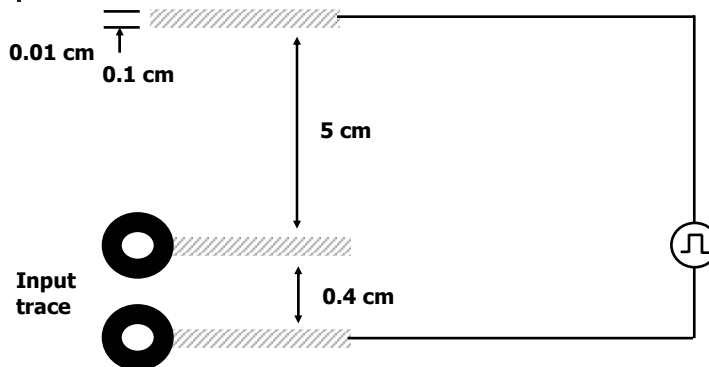

Input terminal – coupling capacitor value




$$C_{trace_trace} = \frac{0.0885\pi(\epsilon_r + 1)l^2}{2 \ln\left(\frac{\pi S}{W + t}\right)} 10^{-14}$$

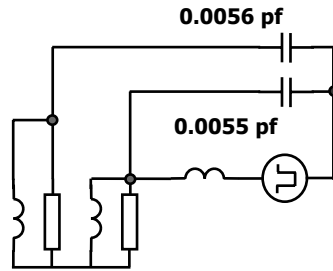S1 = 5 cm
S2 = 5.4 cm
W = 0.1 cm
t = 0.01 cm
 $\epsilon_r = 4$




Prepared by Franki Poon & Bryan Pong
 EMI in Switching Power Supply

Input terminal – simulation

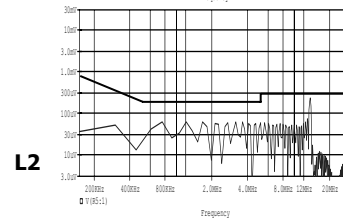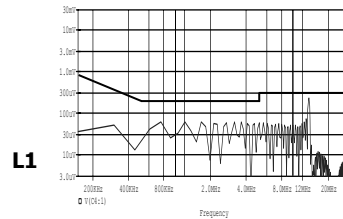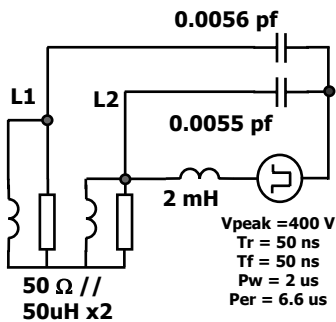


Prepared by Franki Poon & Bryan Pong
 EMI in Switching Power Supply

Input terminal – imbalance impedance

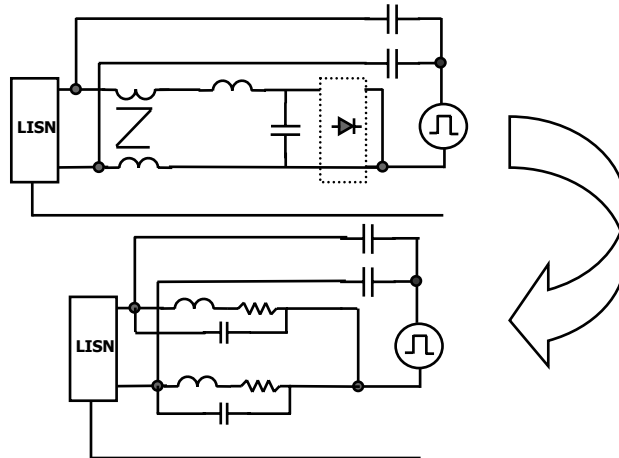


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input imbalance impedance – simulation

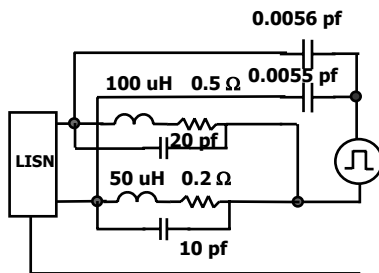


Limit Exceeded !!

L1



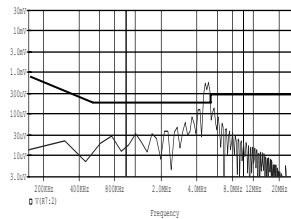


L2

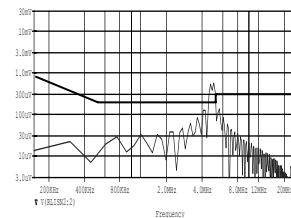

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input imbalance impedance – solution

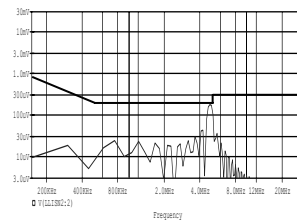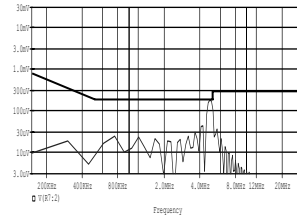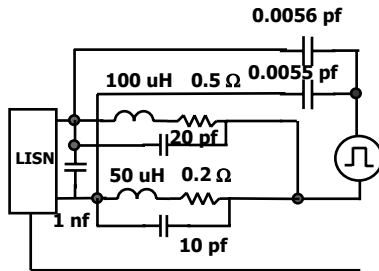


Pass in simulation ?




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

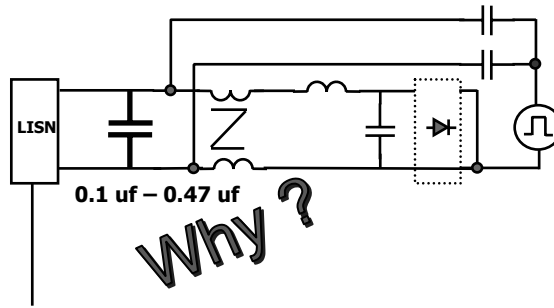Input imbalance impedance solution – Real?



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


Don't forget

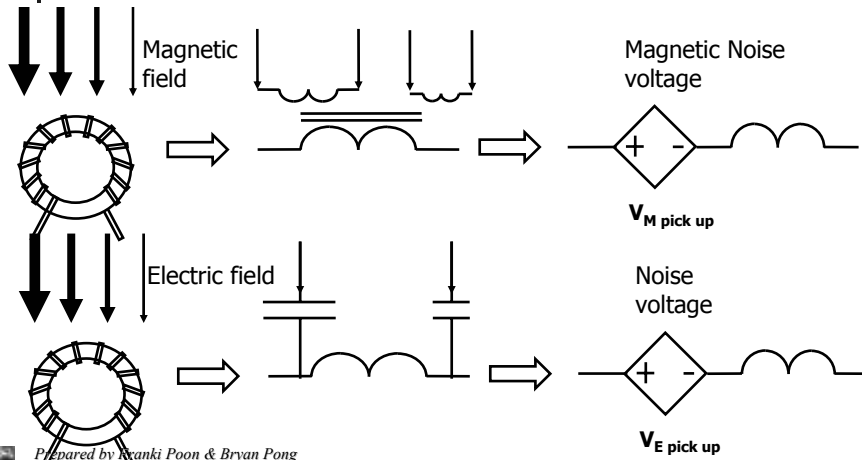

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


Input imbalance impedance solution – hence

Reason

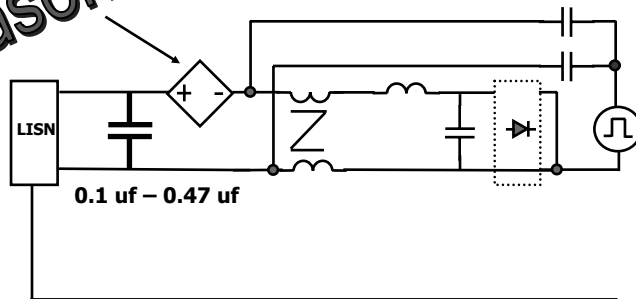

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


Input imbalance impedance – bad CMC

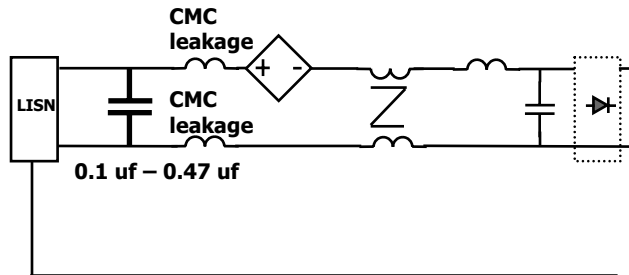


A filter is formed by the leakage inductance of the CMC to provide extra attenuation on the noise picked up by CMC




Input again – is everything fine?

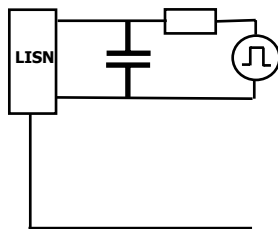

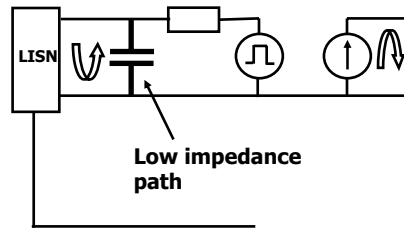
The large input X-capacitor provides a final low impedance loop with the LISN. Magnetic couple will contribute to noise pick up by the LISN



Input again – mutual inductance

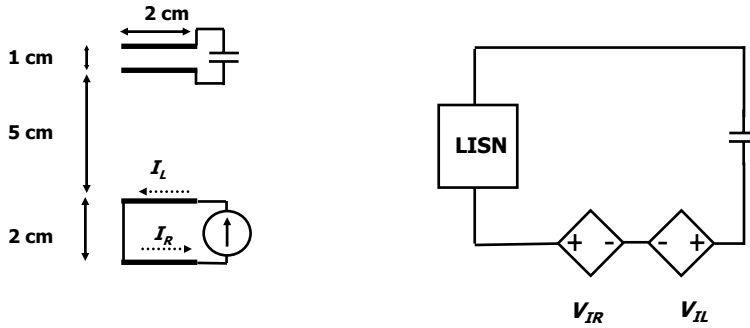

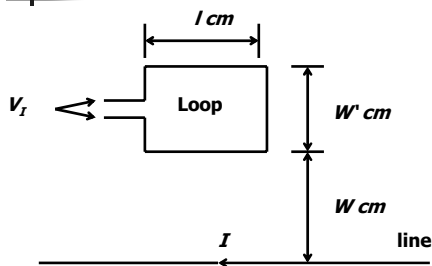Approximated line to loop mutual inductance



$$W' = 1 \text{ cm}$$

$$W = 5 \text{ cm}$$

$$L = 2 \text{ cm}$$

$$L_{line_loop} = 0.73 \text{ nH}$$

$$W' = 1 \text{ cm}$$

$$W = 7 \text{ cm}$$

$$L = 2 \text{ cm}$$



$$L_{line_loop} = 0.53 \text{ nH}$$

$$L_{line_loop} = 0.002l \left(\ln \left(\frac{W + W'}{W} \right) \right) \mu\text{H}$$

$$L_{line_loop_Eqv.} = 0.2 \text{ nH}$$




Input loop noise – example

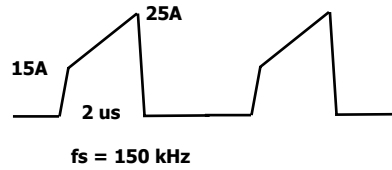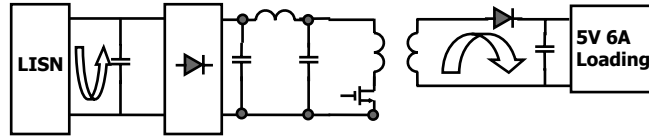


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input loop noise – magnetic induction

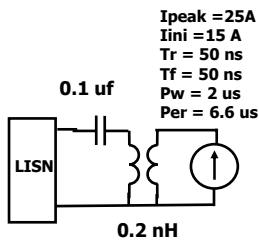


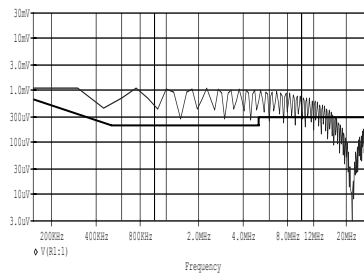Exceed limit because of small input loop.




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


Other noise loop ?

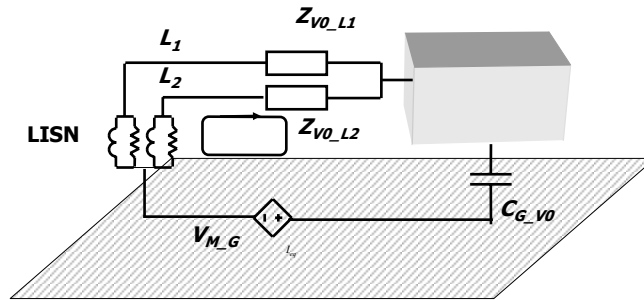

Converter to earth Loop

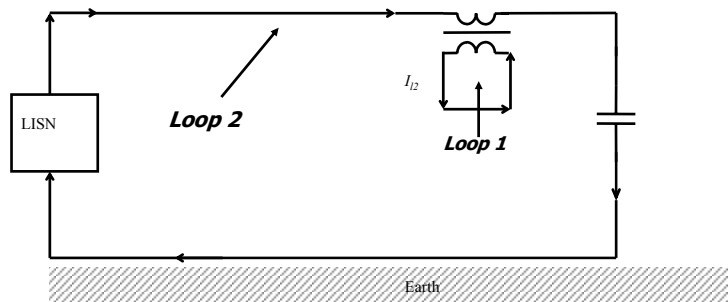

Converter to earth Loop – capacitor

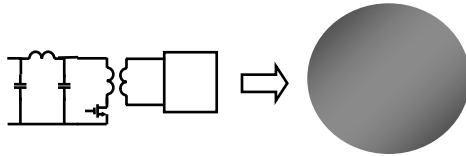

Let the total surface area of the whole converter is equal to a sphere with equivalent radius r

$$r = 5 \text{ cm}$$

As the self capacitance of a sphere of $r \text{ cm}$


$$C_{\text{sphere}} = 4 \pi 0.0885 r \text{ pf}$$

The equivalent drain self capacitance is

$$C_{\text{drain}} = 5.5 \text{ pf}$$



Converter to earth Loop – typical value

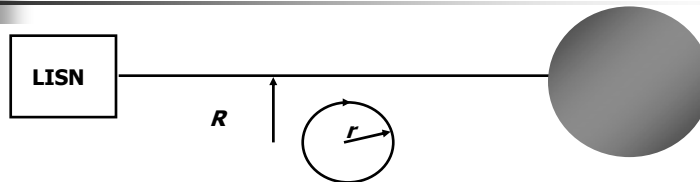

$$r = 1 \text{ cm}$$

$$R = 2 \text{ cm}$$


$$M_{\text{line_loop}} = u_0 \left[\frac{R}{100} - \sqrt{\left(\frac{R}{100}\right)^2 - \left(\frac{r}{100}\right)^2} \right]$$

The mutual inductance is


$$Z_{\text{line_circle}} = 3.3 \text{ nH}$$



Converter to earth Loop – raw noise

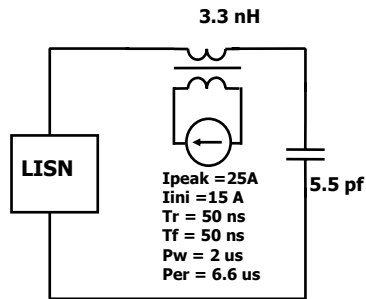

25A still can't fail it!

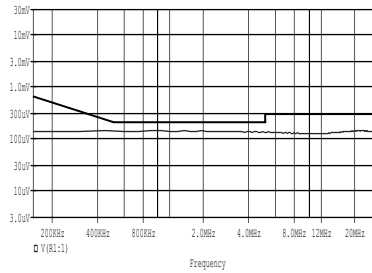


Be careful, really close !




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Converter to earth Loop – resonate loop

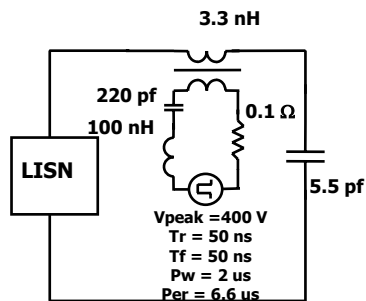

300 uA fail it by 30 dB !!

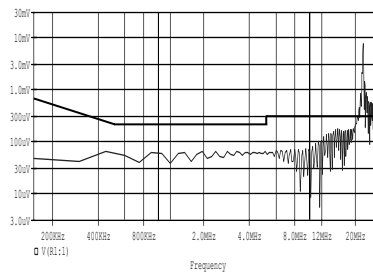


Fail, much worse than the 25A case !




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Resonate loop – CMC choke

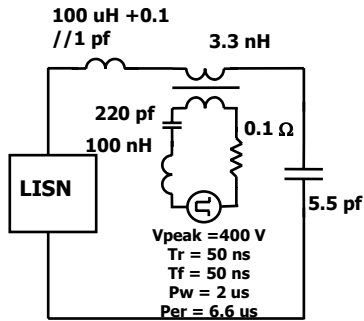

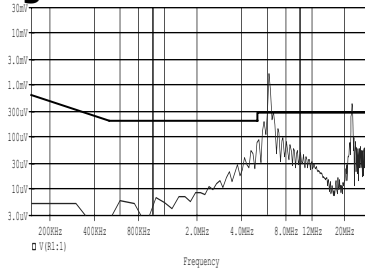Kill the original resonant circuit but generate another one



Inductor only drift the resonate point.




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

185

Resonate loop – RESISTOR

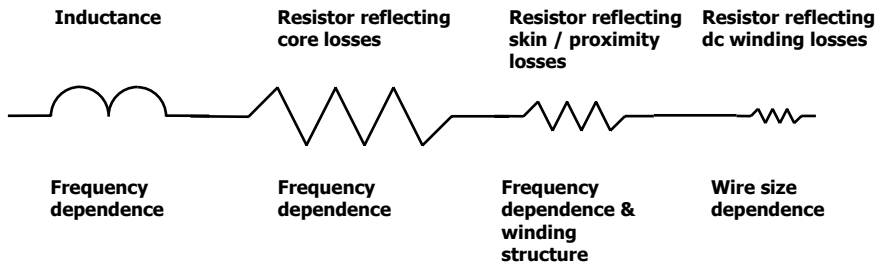

Remember this ?




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


www.eee.hku.hk/power_electronics_lab/

186


Resonate loop – increase resistance

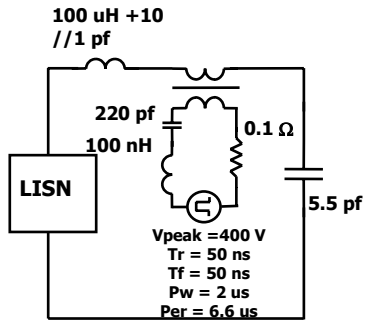


Unfortunately, not much better.

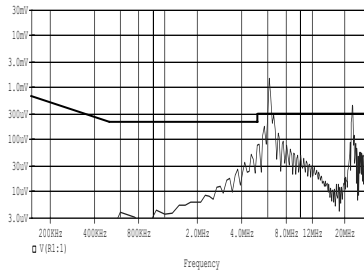

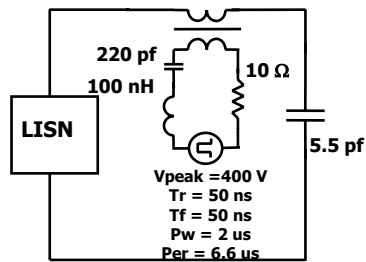
Increasing resistance – at the right place



Much better, but how ?


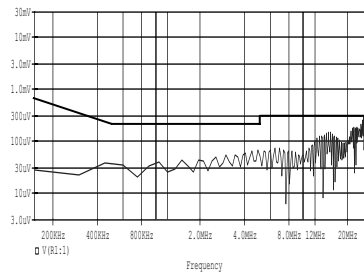


Increasing resistance – lossy ferrite

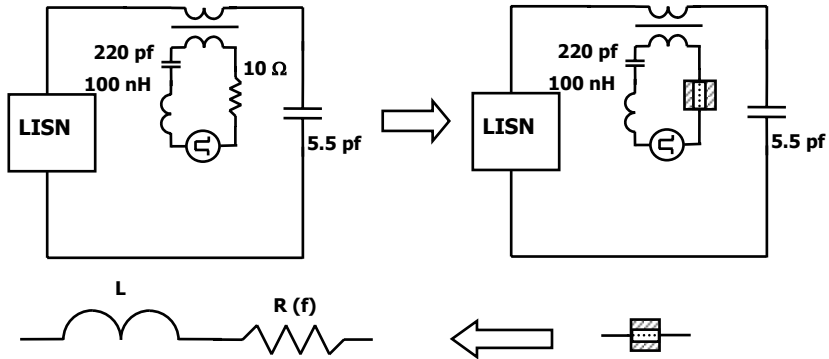


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Ferrite beads

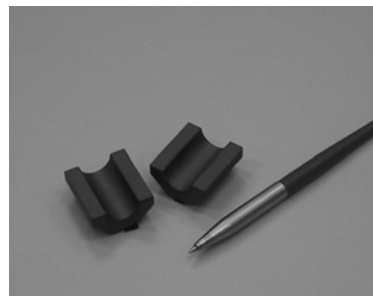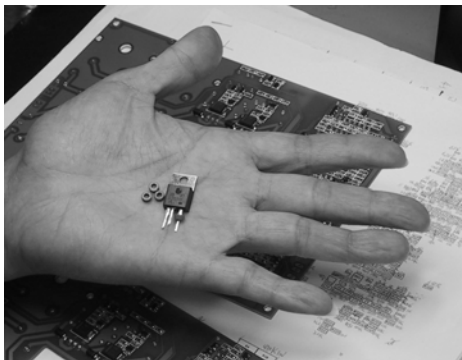

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Invisible loop – inside xformer

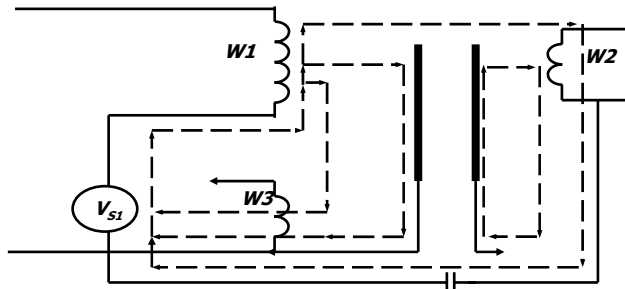


Xformer is tightly packed and has large stray capacitor to introduce many loops inside.



Short summary

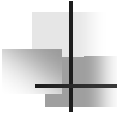- Capacitive coupling to input terminal causes EMI.
- Solutions for capacitive coupling lead to more magnetic coupling effect.
- The whole converter to earth has a large capacitor.
- Magnetic coupling causes EMI due to the loop form by the converter to earth capacitor.
- Resonance causes unexpected EMI level.
- Damping, not inductor, is the solution for resonance.






Any short question?




How does EMI come out?

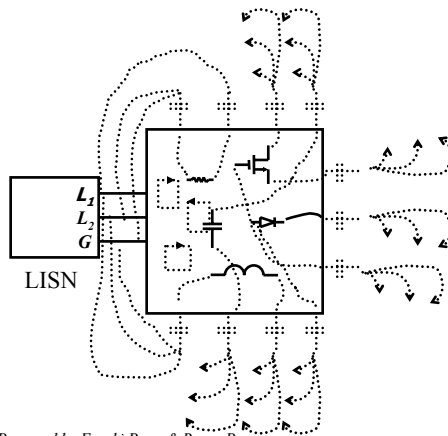


Contacted -
can be understood
through circuit diagram
Non-Contacted -
Mutual invisible
capacitor & Mutual
invisible inductor



V & I Only

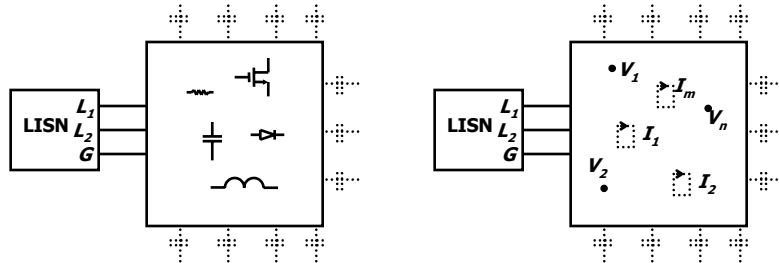

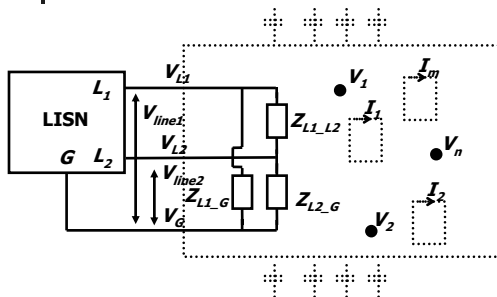
Only LISN terminals voltage are concerned



- No matter how complicated a circuit, EMI are voltage measurements, V_{Line1} and V_{Line2} across LISN terminals.
- $V_{line1} = VL1 - VG$
- $V_{Line2} = VL2 - VG$
- Is there a simple way to look at it?



Circuit theory – voltage node

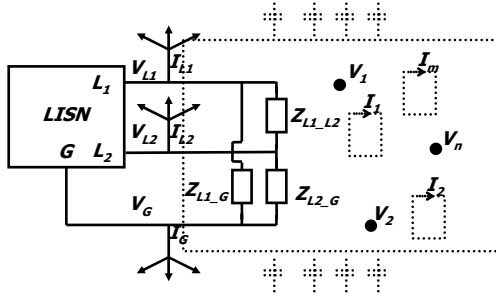


$$I_{L1} = \sum_{i=1}^n \frac{V_i - V_{L1}}{Z_{L1_i}}$$

$$I_{L2} = \sum_{i=1}^n \frac{V_i - V_{L2}}{Z_{L2_i}}$$

$$I_G = \sum_{i=1}^n \frac{V_i - V_G}{Z_{G_i}}$$



Equivalent voltage source

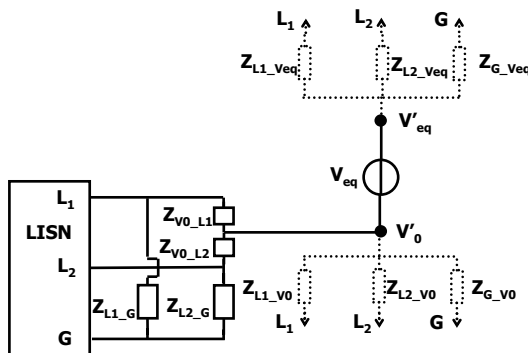

$$I_{L1} = \frac{V'_{eq} - V_{L1}}{Z_{L1_Veq}} + \frac{V'_0 - V_{L1}}{Z_{L1_V0}}$$


$$I_{L2} = \frac{V'_{eq} - V_{L2}}{Z_{L2_Veq}} + \frac{V'_0 - V_{L2}}{Z_{L2_V0}}$$

$$I_G = \frac{V'_{eq} - V_G}{Z_{G_Veq}} + \frac{V'_0 - V_G}{Z_{G_V0}}$$

One voltage source and six mutual impedances



Simple circuit theory – current node

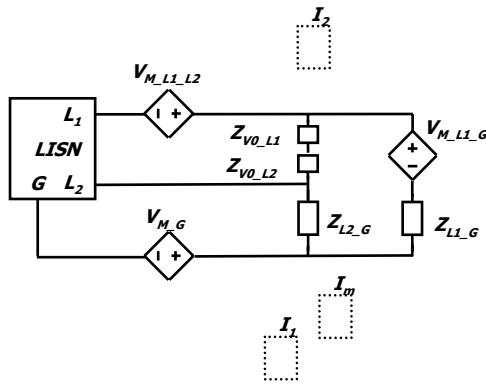

$$V_{M_L1_L2} = \sum_{i=1}^m I_i Z_{M_L1_L2_i}$$


$$V_{M_L1_G} = \sum_{i=1}^m I_i Z_{M_L1_G_i}$$

$$V_{M_G} = \sum_{i=1}^m I_i Z_{M_G_i}$$



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Equivalent current source

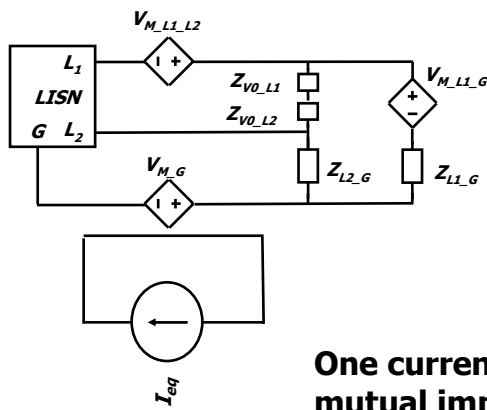

$$V_{M_L1_L2} = I_{eq} Z_{M_L1_L2_ieq}$$

$$V_{M_G} = I_{eq} Z_{M_G_ieq}$$

$$V_{M_L1_G} = I_{eq} Z_{M_L1_G_ieq}$$


One current source and three mutual impedance




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Minimum Coupling Model

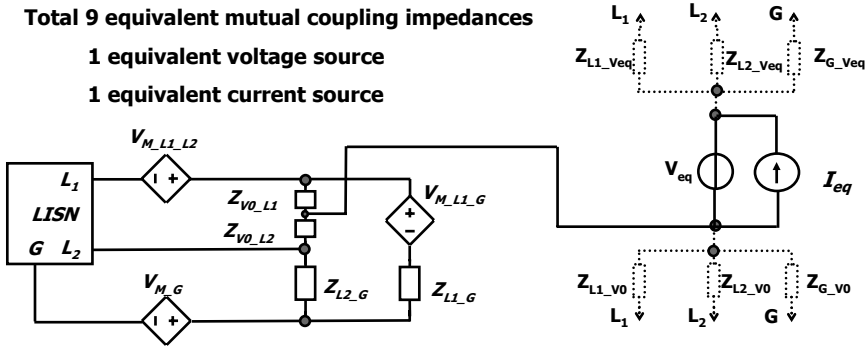- Total 9 equivalent mutual coupling impedances
- 1 equivalent voltage source
- 1 equivalent current source




Physical meaning – C_{G_Veq}

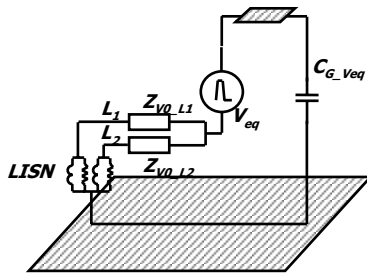

C_{G_Veq} –
Hot switching
node to earth
equivalent
capacitor



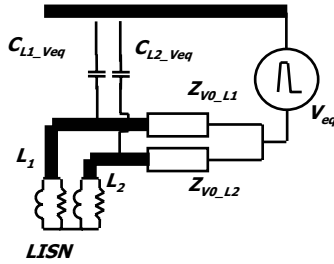
Physical meaning – C_{L1_Veq} & C_{L2_Veq}



C_{L1_Veq} & C_{L2_Veq} –
Hot switching node
to input traces
represented by
equivalent
capacitors



Physical meaning – C_{L1_V0} & C_{L2_V0}

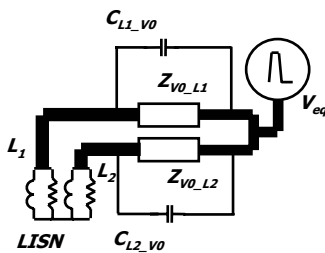


C_{L1_V0} & C_{L2_V0} –
0V node to input
traces have
equivalent
capacitors

Absorbed in the
input impedance.



Physical meaning – C_{G_V0}

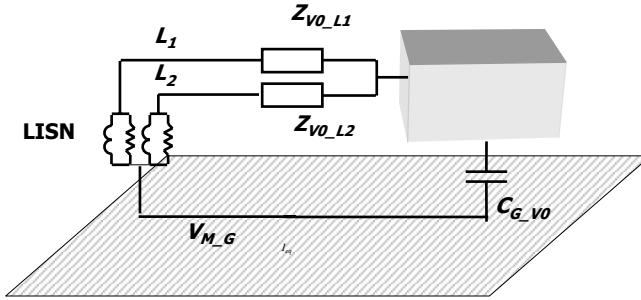


C_{G_V0}
**Converter
 to earth
 equivalent
 capacitor**



Physical meaning – $Z_{M_L1_L2_Ieq}$

$$V_{M_L1_L2} = I_{eq} Z_{M_L1_L2_Ieq}$$

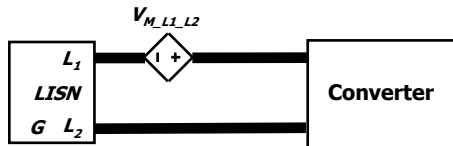


$Z_{M_L1_L2_Ieq}$
**Input lines loop
 mutual inductive
 impedance**



Physical meaning – $Z_{M_G_Ieq}$

$$V_{M_G} = \sum_{i=1}^m I_i Z_{M_G_i}$$

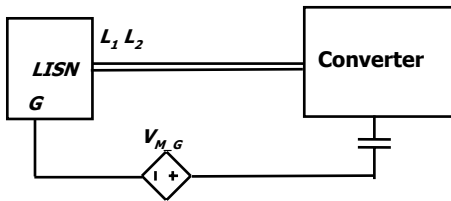


$$Z_{M_G_Ieq}^-$$

**Earth to
converter loop
mutual inductive
impedance**



Physical meaning – $Z_{M_L1_G_Ieq}$

$$V_{M_L1_G} = I_{eq} Z_{M_L1_G_Ieq}$$

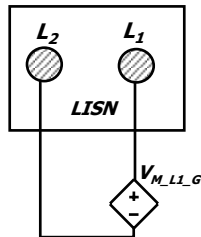


$$Z_{M_L1_G_Ieq}^-$$


**Cross section of
Line 1, line 2 and
earth loop mutual
inductive
impedance**



Overall simulation


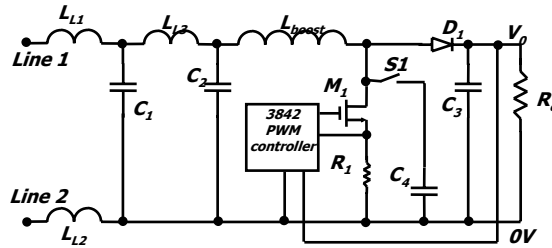


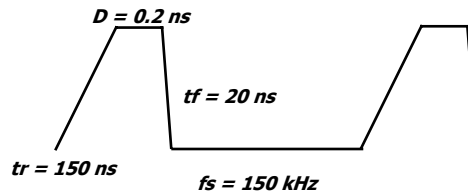$V_p = 400V$
 $tr = 150 ns$
 $tf = 20 ns$
 $D = 0.2$
 $Fs = 150 kHz$



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Realistic parameter - C_{G_Veq}

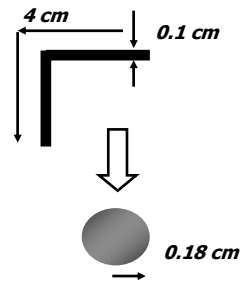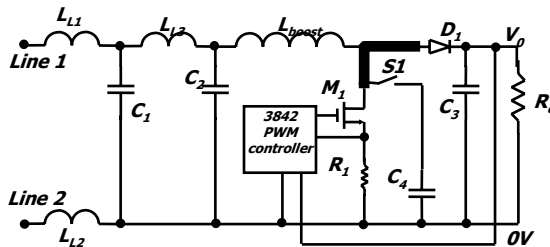


$$C_{sphere} = \frac{4\pi \cdot 0.085}{\frac{1}{r}} pf$$

$$C_{G_Veq} = 0.2 pf$$




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

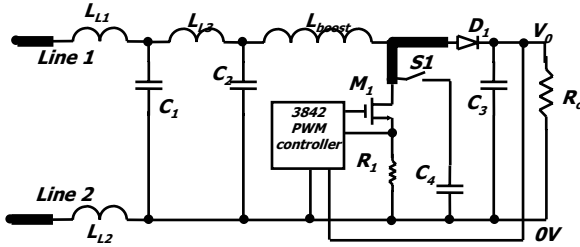Realistic parameter - C_{L1_Veq} & C_{L2_Veq}



$t = 0.01 \text{ cm}$

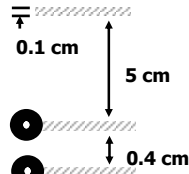

$S1 = 5 \text{ cm}$

$S2 = 5.4 \text{ cm}$

$W = 0.1 \text{ cm}$

$t = 0.01 \text{ cm}$

$\epsilon r = 4$

$C_{L1_Veq} = 0.0056 \text{ pf}$


$C_{L2_Veq} = 0.0055 \text{ pf}$

$$C_{trace_trace} = \frac{0.0885\pi(\epsilon_r + 1)l^2}{2 \ln\left(\frac{\pi S}{W + t}\right)} 10^{-14}$$




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

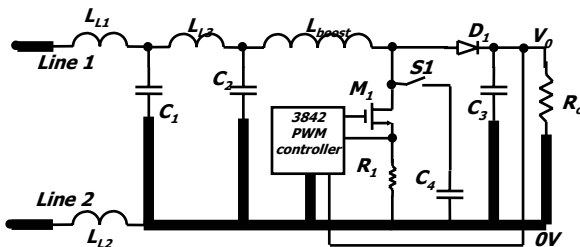
Realistic parameter - C_{L1_V0} & C_{L2_V0}



**Absorbed in
input
impedance.**

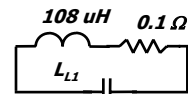

27 pf

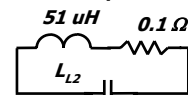


14 pf




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Realistic parameter - C_{G_V0}

Measured as

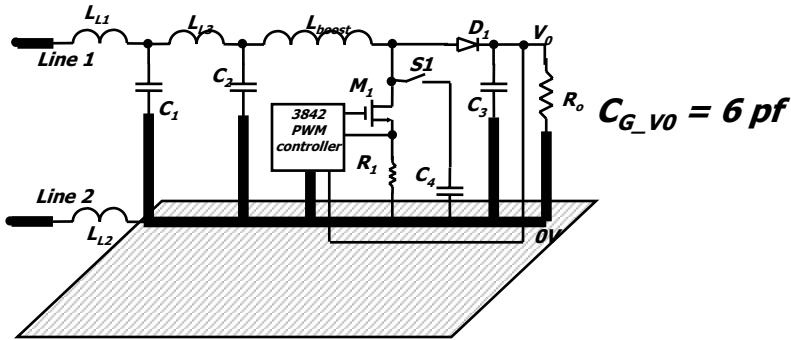


Realistic parameter - $Z_{M_G_Ieq}$

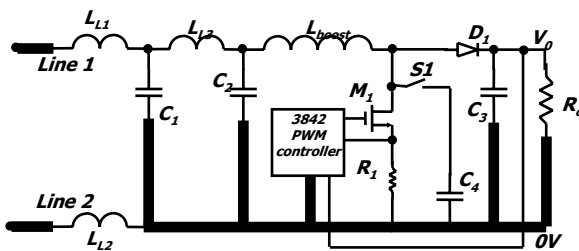

$$M_{line_loop} = \mu_0 \left[\frac{R}{100} - \sqrt{\left(\frac{R}{100}\right)^2 - \left(\frac{r}{100}\right)^2} \right]$$

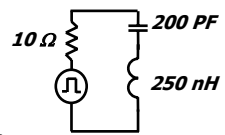$V_p = 400V$
 $t_r = 150 \text{ ns}$
 $t_f = 20 \text{ ns}$
 $D = 0.2$



$r = 2 \text{ cm}$
 $R = 1.9 \text{ cm}$
The mutual inductance is
 $Z_{M_G_Ieq} = 17 \text{ nH}$



Realistic parameter - $Z_{M_L1_G_Ieq}$ / $Z_{M_L2_G_Ieq}$

As the input loops are small and having quite a high input impedance, hence for simplicity,


Just set

$$Z_{M_L1_G_Ieq} = 0$$


$$Z_{M_L2_G_Ieq} = 0$$



PSPICE Simulation

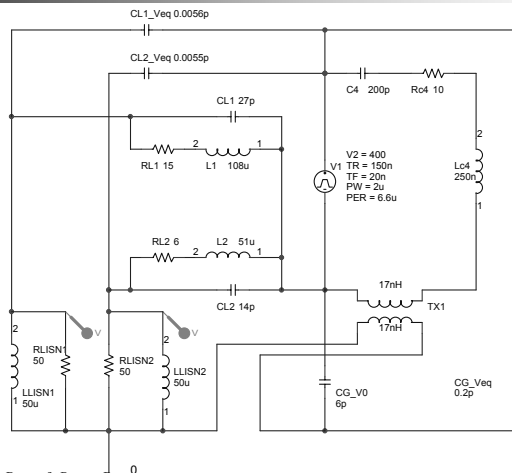


Simulation & Measured Results – S1 open

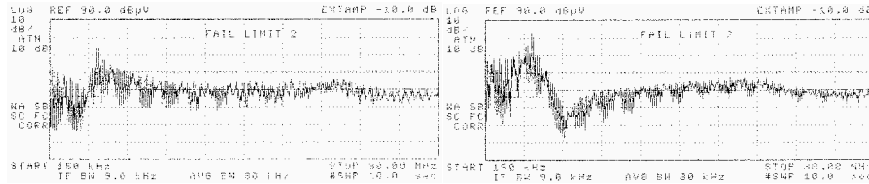


Line 1 measured result S1 open

Line 2 measured result S1 open

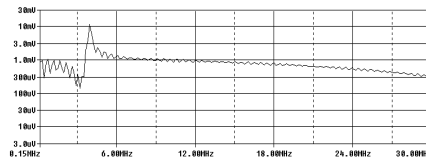

Line 1 simulated result S1 open

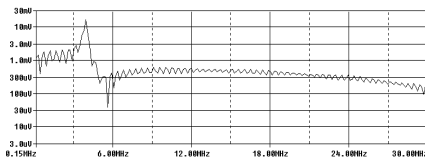

Line 2 simulated result S1 open




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/


217

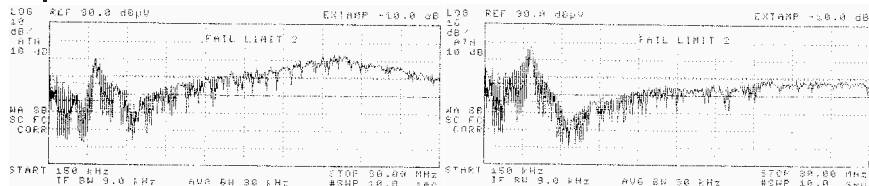Simulation & Measured Results – S1 closed




Line 1 measured result S1 close

Line 2 measured result S1 close

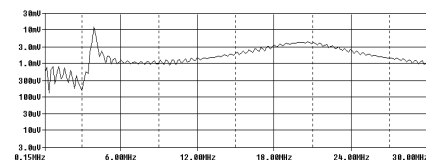

Line 1 simulated result S1 close

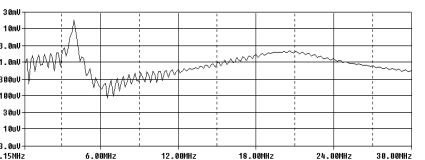

Line 2 simulated result S1 close




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/


218

S1 open – Capacitive coupling only

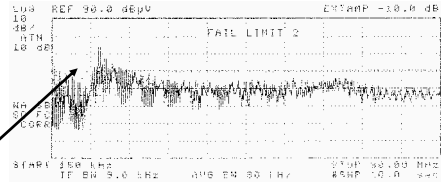Resonate behavior between the input equivalent impedances



Line 1 measured result S1 open

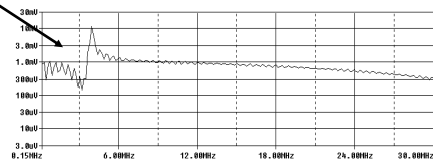


Line 1 measured result S1 open




S1 close – Capacitive & inductive coupling

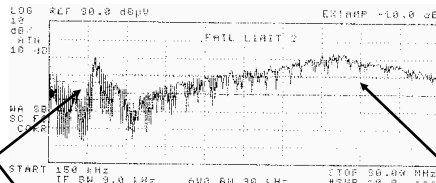Resonate behaviors between the input equivalent impedance



Line 1 measured result S1 close

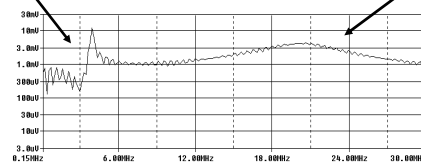

Line 1 measured result S1 close

Resonate behaviors of the source loop and mutual inductive coupling



Minimum Coupling Model


- A minimum of *six* capacitive mutual coupling impedance is concluded.
- A minimum of *three* inductive mutual coupling impedance is concluded.
- Complicated EMI waveform can be simulated by simple lump element circuit.
- It is a minimum model, not maximum !
- Good for diagnosis purpose.



Any short question ?




Shielding – Purpose

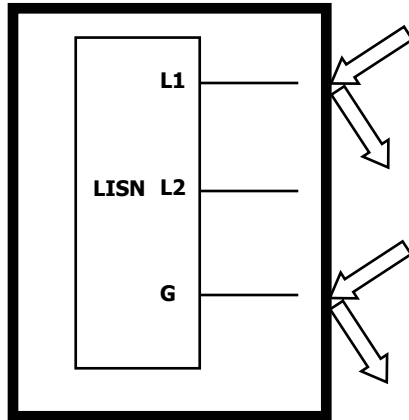

Don't let any current flow into the LISN




Shield or being shielded

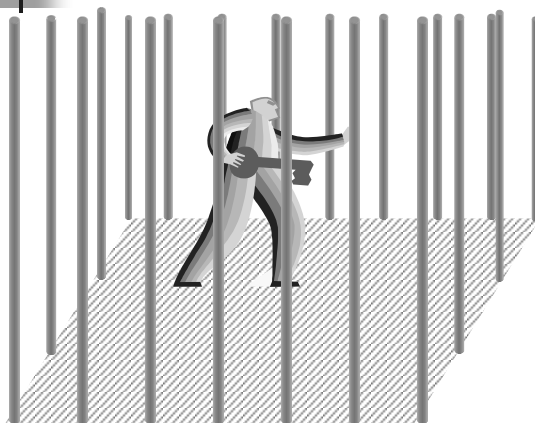

I lock up the whole world. Ha, ha . . .




Shielding – wrong idea 1

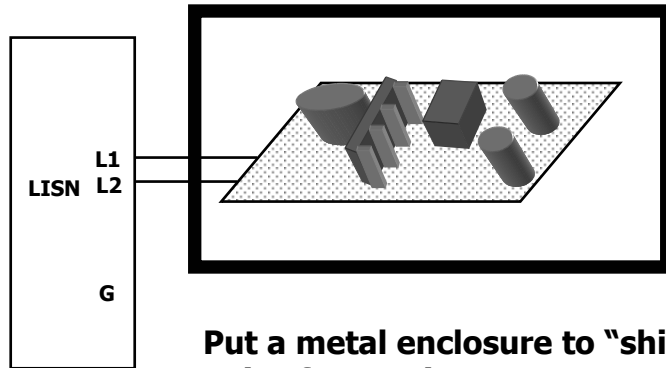


Put a metal enclosure to “shield” noise from going out - Wrong



Shielding – total recall 1

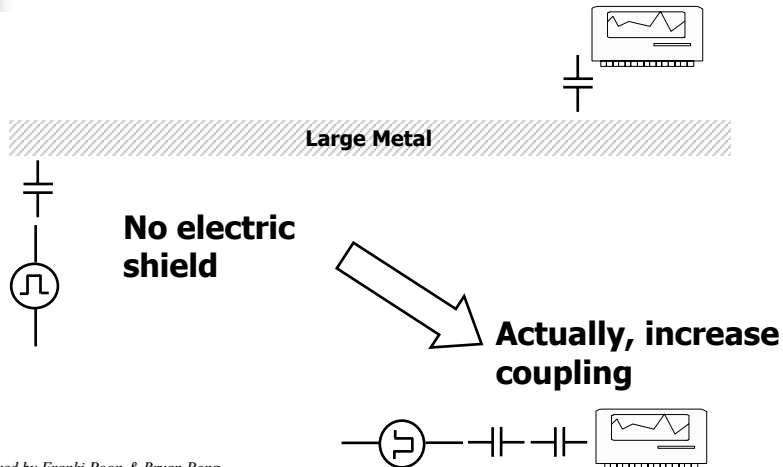


Shielding – wrong idea 1

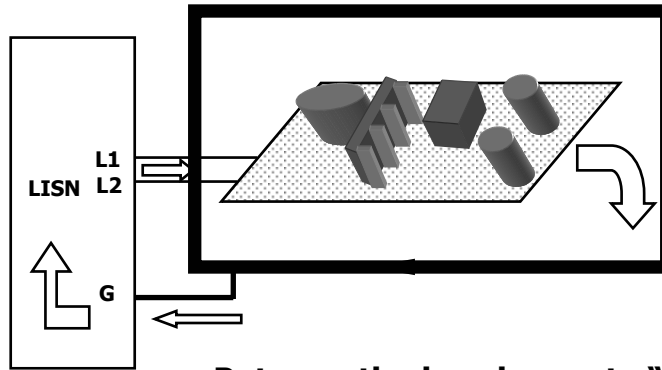

Put a earthed enclosure to “shield” noise from going out - Wrong




Shielding – total recall 2

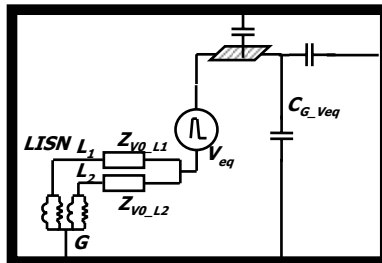


An earthed enclosure actually increases the equivalent hot node to earth capacitance C_{G_Veq} and increases noise.



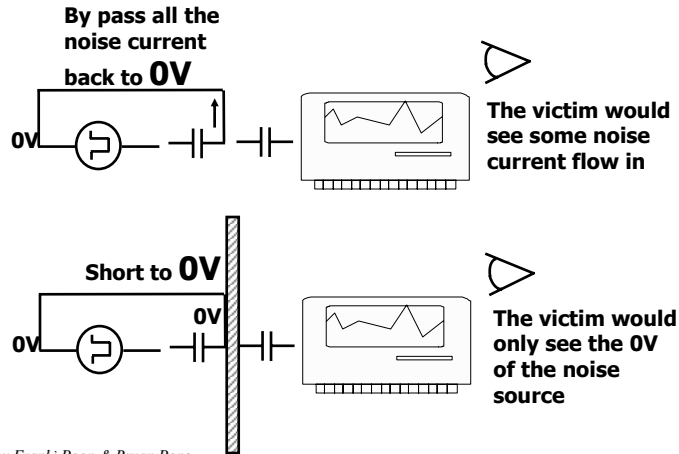
Shielding is all about by passing or short circuit



0V is the point

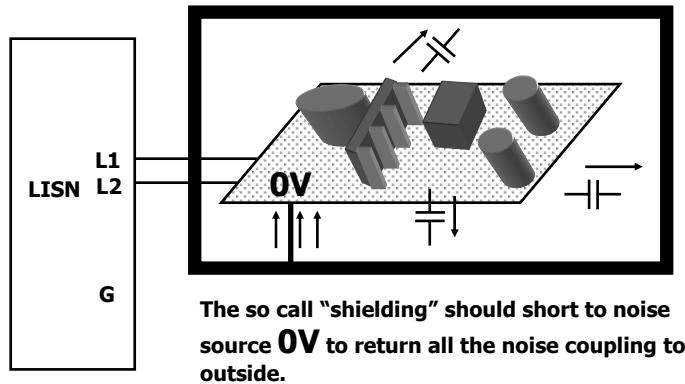


0V is the point - Xformer

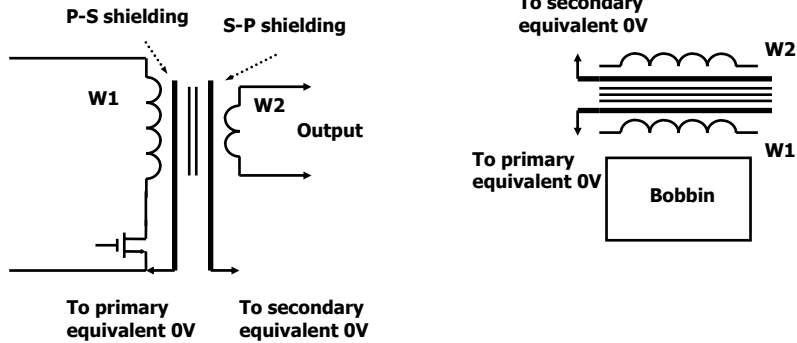


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

0V is the point - MOSFET

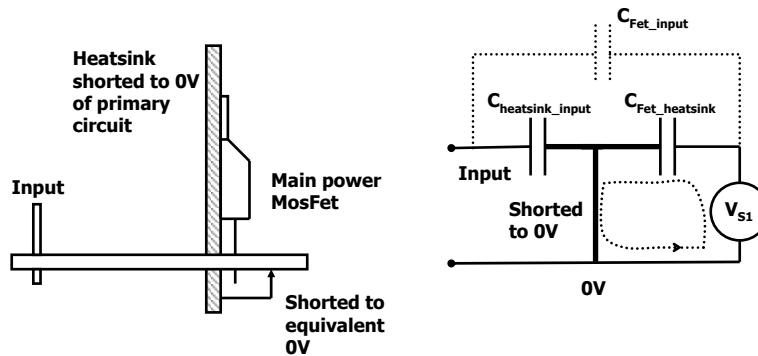

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


Grounded Case ?

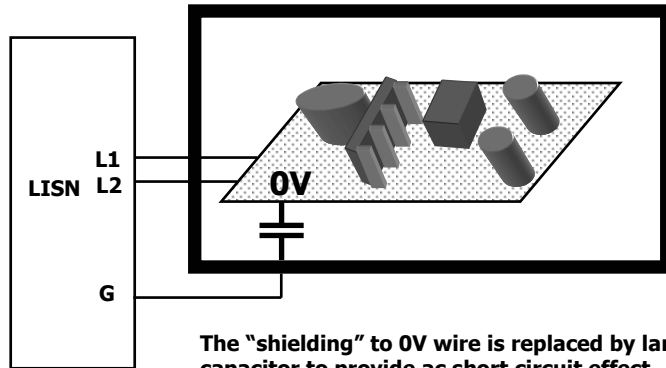

The "shielding" to 0V wire is replaced by large capacitor to provide ac short circuit effect. Then the case can be shorted to earth for safety purpose.




Grounding wire

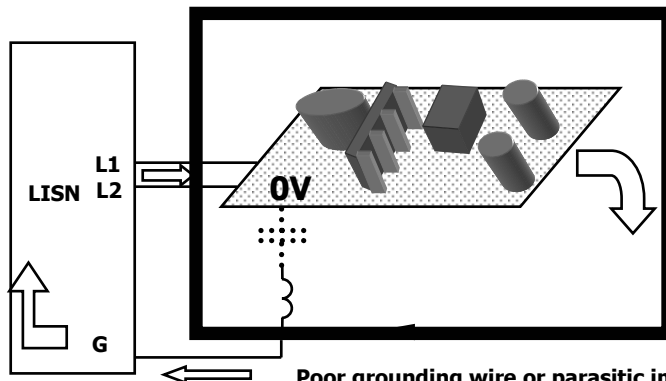

Poor grounding wire or parasitic impedance of the grounding capacitor force the coupling current flow back to G terminal of LISN.




Grounding choke

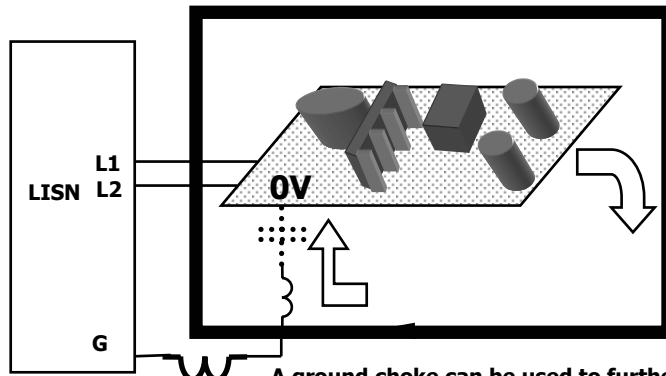


A ground choke can be used to further increase the impedance of the ground path to avoid noise current flowing in.




Magnetic shielding ?

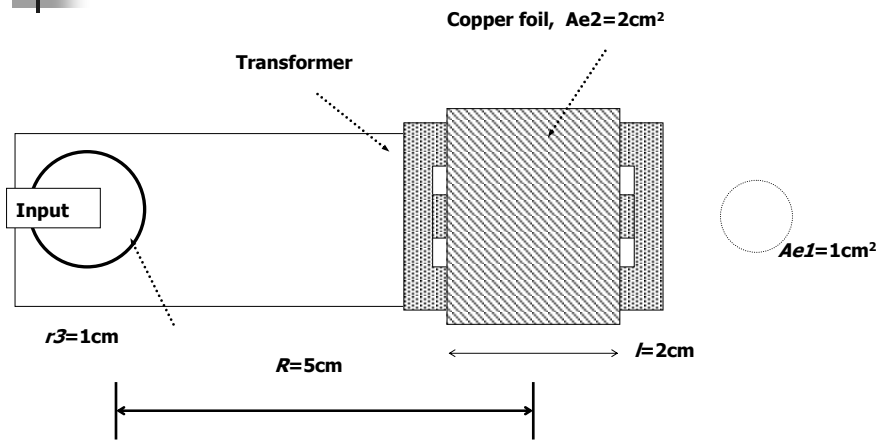

Flux band - modeling


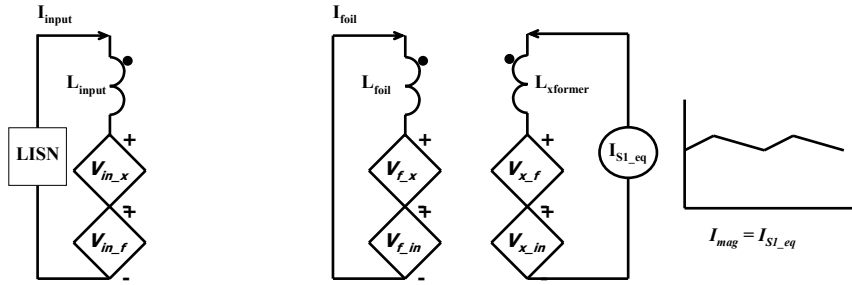


3 Xformers

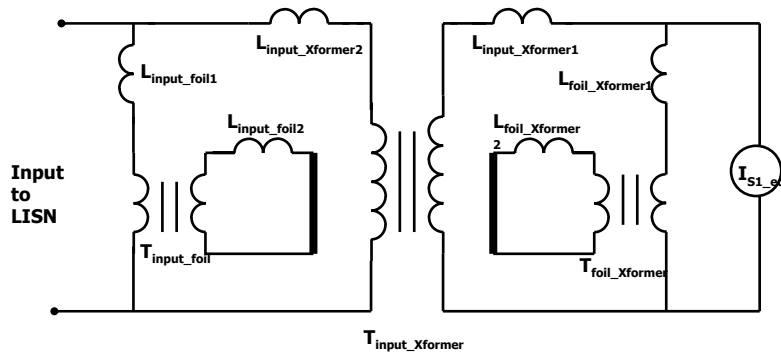


Simulation

Only 6 dB reduction !

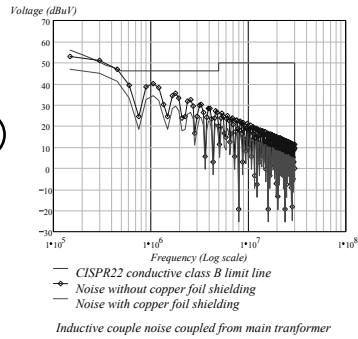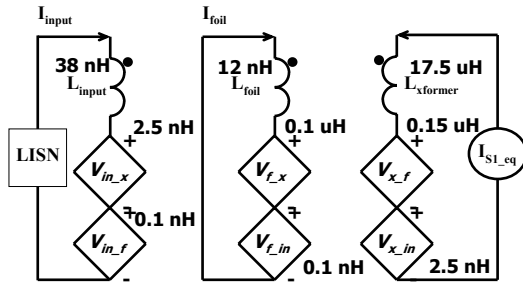



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Flux concept – Believe it or Not?

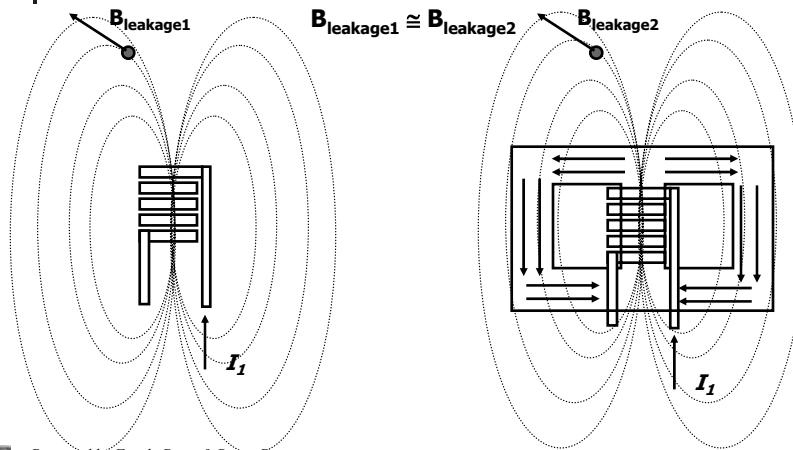

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


Flux concept – air core is core

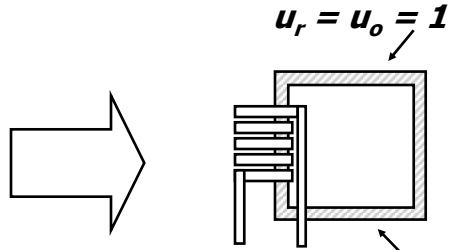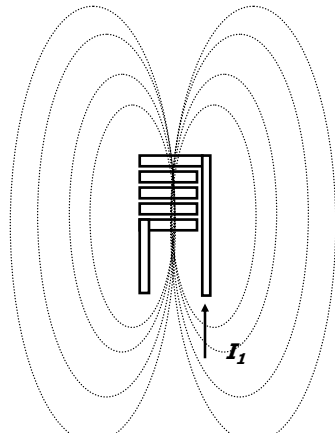


You can't take it away ! It exist even in empty space!!




Flux concept – air core and ferrite core

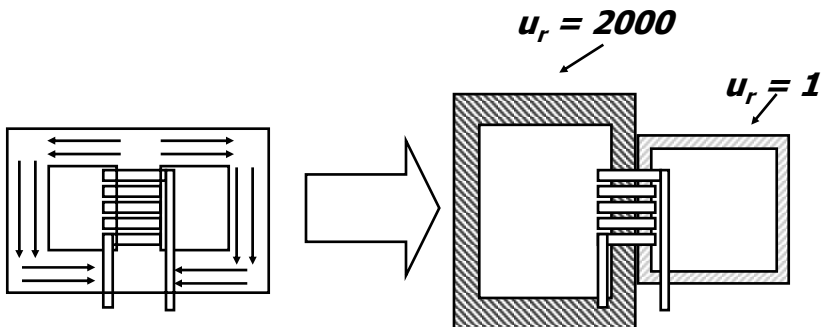

Flux concept – as a result

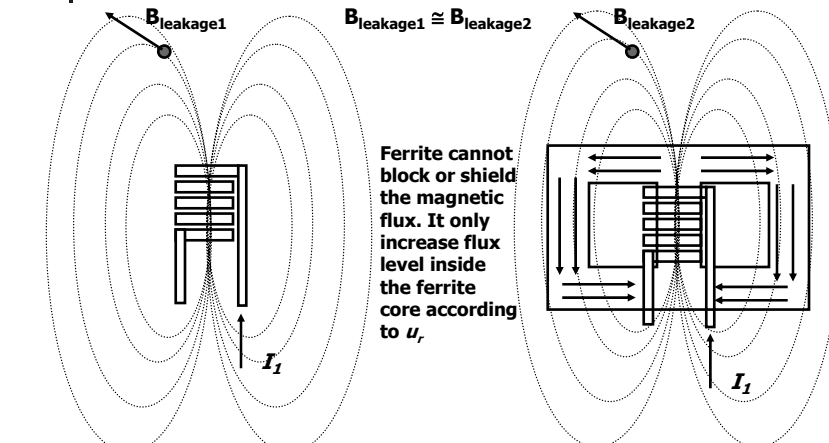


Flux concept – general coupling

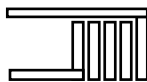

Noise Source




Short Ring

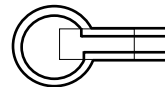


Pick up

General coupling - Xformer model

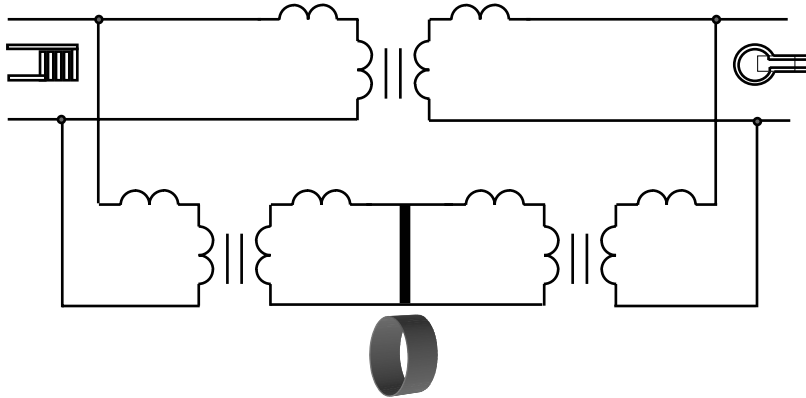


General coupling - close to noise source

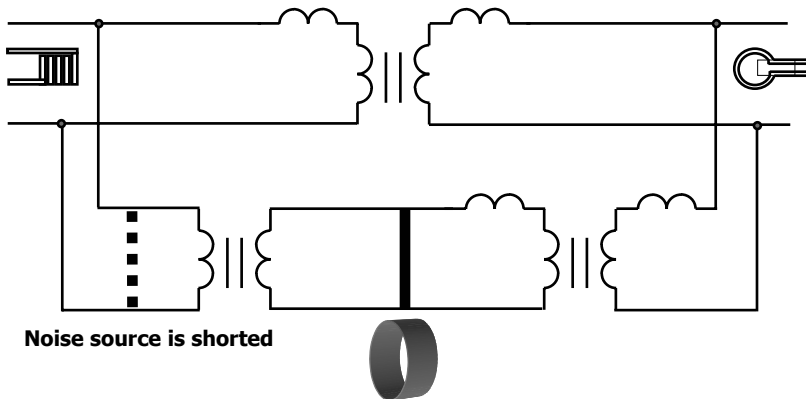

Noise source is shorted



General coupling - close to pick up

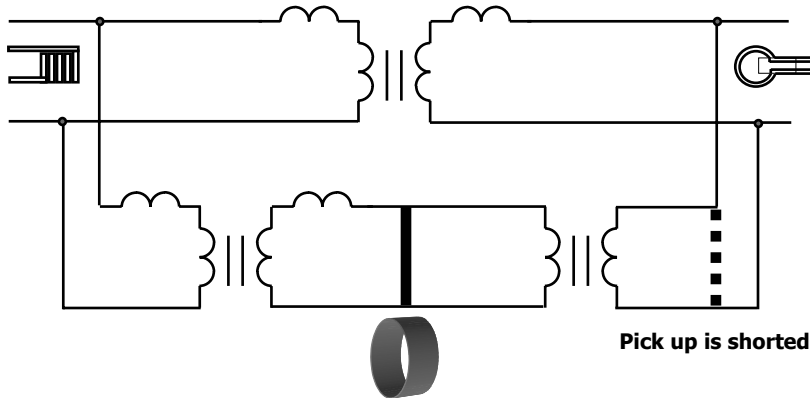

Pick up is shorted




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

247

General coupling - somewhere in between

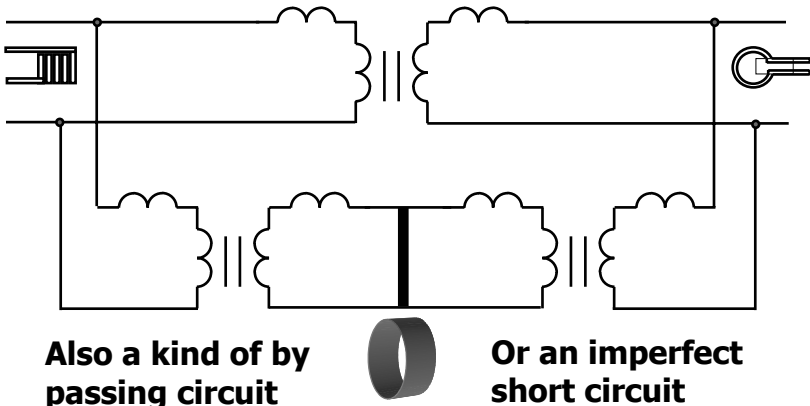

**Also a kind of
passing circuit**

**Or an imperfect
short circuit**



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

248

Short Summary


- By pass or short circuit is a basic concept for electric or magnetic "shielding".
- Easier to by pass capacitive coupling effect.
- Surrounding the noise source with ground or earth is **NOT** a general "shielding" concept.



Any short question?




Inductor Model – not only parasitics

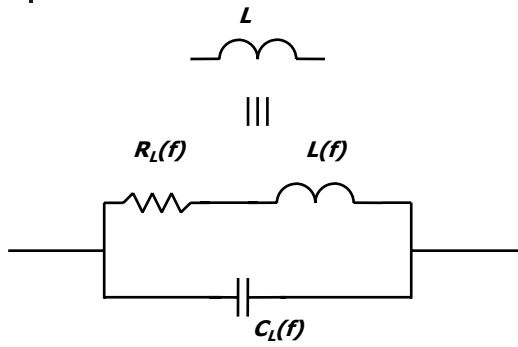


**Things
change
with
operating
frequency**




Inductor Model – permeability $\mu_r(f)$

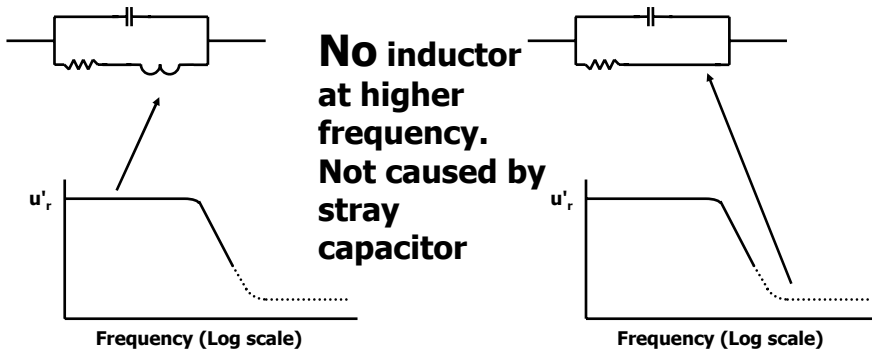

Inductor Model – losses

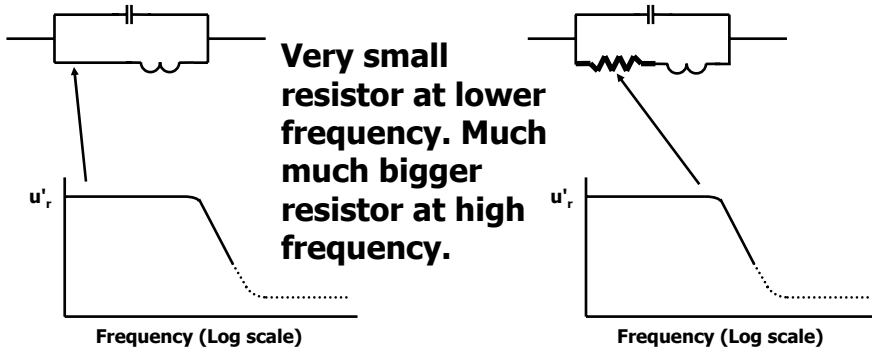

Permeability – interpolation

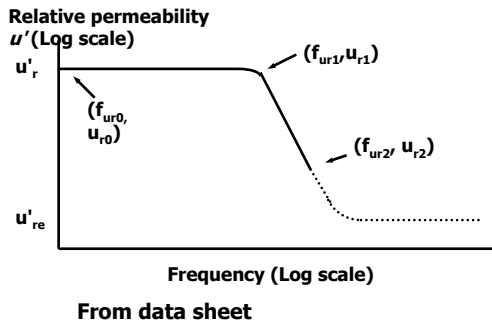

Interpolate the permeability against frequency with the following relation

$$u_i(f) = \frac{u_{re}(jf^m - f_{ur1}^m \frac{u_{r0}}{u_{re}})}{jf^m - f_{ur1}^m}$$

Where m should satisfy the following relation

$$u_{r2} - \frac{u_{re}(jf_{ur2}^m - f_{ur1}^m \frac{u_{r0}}{u_{re}})}{jf_{ur2}^m - f_{ur1}^m} = 0$$




Permeability interpolation – an example


H5C2 TDK data is sampled from data sheet as

$$\begin{aligned} \mu_{r0} &= 10^4, & f_{ur1} &= 0.2 \times 10^6, \\ \mu_{r1} &= 0.7 \times 10^4, & f_{ur2} &= 0.55 \times 10^6, \\ \mu_{r2} &= 2200, & & \end{aligned}$$

Hence m can be calculated as
 $m = 1.47$

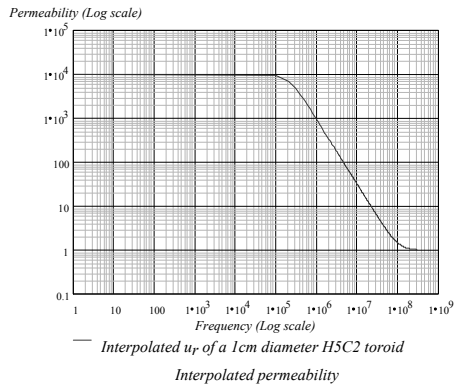

We start with losses

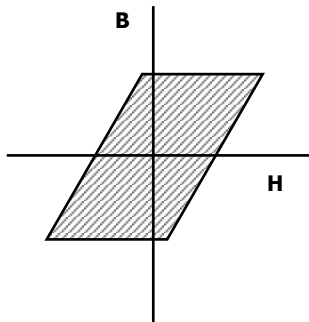

Hysteresis losses -
Losses \propto Area of B/H loop
Losses $\propto B^2$

Or

$$W_h = k_h V_{vol} B^2 f_s$$



Hysteresis losses series resistor

As

$$W_h = k_h Vol_s B_{rms}^2 f$$

Approximate flux level is dominated by injecting current, or

$$B = u_o u_r \frac{N}{l_{eq}} I$$

Hence


$$W_h = k_h \frac{u_o u_r N^2 Vol_s}{l_{eq}^2} f I_{rms}^2$$

$$W_h = R_h I_{rms}^2$$




Eddy current losses


× Flux

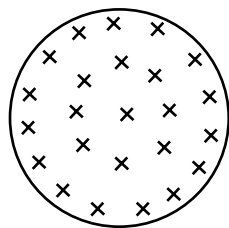

Flux penetrate the ferrite core

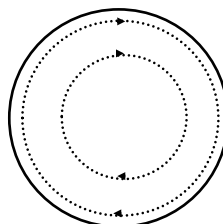


Induced current flowing round the core

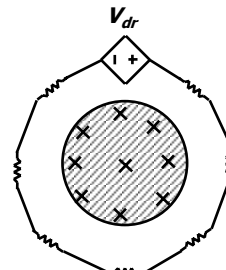


Equivalent voltage source and distributed resistor



Eddy current losses – physical meaning

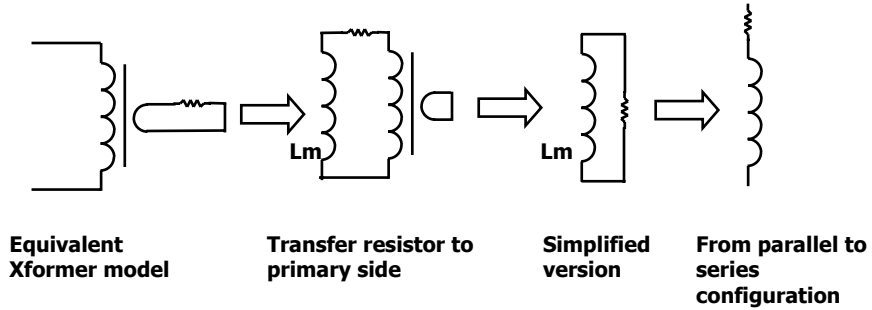

Eddy current series resistor

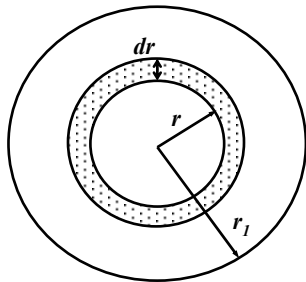

Cross section of a toroid

The equivalent voltage generated at the ferrite ring dr

$$V_{dr} = \frac{d\phi_{Ae}}{dt} \frac{r^2}{r_1^2}$$

Or

$$V_{dr} = Ae_s \frac{dB}{dt} \frac{r^2}{r_1^2}$$

For sine wave excitation, the rms equivalent voltage is

$$V_{dr_rms} = Ae_s \omega B_{rms} \frac{r^2}{r_1^2}$$



Finding eddy current series resistor

The equivalent resistance of the ring can be described as

$$R_{dr} = \frac{2\pi r}{k_R l_{es}} \times dr \quad l_{es} = \text{effective length of the magnetic circuit}$$

The overall losses is the summation of each ring, hence

$$W_e = \int_0^{r_1} \frac{k_R \left(Ae_s \omega B_{rms} \frac{r^2}{r_1^2} \right)^2 l_{es}}{2\pi r} dr$$



Eddy current series resistor is

Overall eddy current losses becomes

$$W_e = k_e Vol_s Ae_s B_{rms}^2 f^2$$

Approximate flux level is dominated by injecting current, or

$$B = u_o u_r \frac{N}{l_{eq}} I$$

hence

$$W_e = k_e \frac{u_o u_r N^2 Vol_s Ae_s}{l_{eq-s}^2} f^2 I_{rms}^2 \quad W_e = R_e I_{rms}^2$$




Ferrite losses – explained as resistor

Total losses becomes

$$W_t = (R_h + R_e)I_{rms}^2$$

and
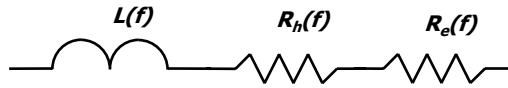
$$R_h(f) = k_h \frac{u_o u_r N^2 Vol_s}{l_{eq_s}^2} f \quad R_e(f) = k_e \frac{u_o u_r N^2 Vol_s A e_s}{l_{eq_s}^2} f^2$$




Ferrite losses provide the coefficients

$$k_e = \frac{W_{core2} f_1 B_{p1}^2 - W_{core1} f_2 B_2^2}{f_1 f_2^2 B_{p1}^2 B_{p2}^2 A e_s Vol_s - f_1^2 f_2 B_{p1}^2 B_{p2}^2 A e_s Vol_s}$$


$$k_h = \frac{W_{core1} f_2^2 B_{p2}^2 - W_{core2} f_1^2 B_1^2}{f_1 f_2^2 B_{p1}^2 B_{p2}^2 Vol_s - f_1^2 f_2 B_{p1}^2 B_{p2}^2 Vol_s}$$



Ferrite losses- some approximated idea

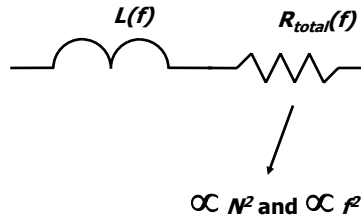


Ferrite losses resistor

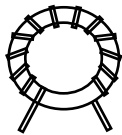

$N=10T$
 $H5C2$ 10mm toroid
 $A_e = 0.07 \text{ cm}^2$
 $L_e = 2.2 \text{ cm}$

Series resistor can be much higher than winding resistance.

Inductance fall at around 200 kHz

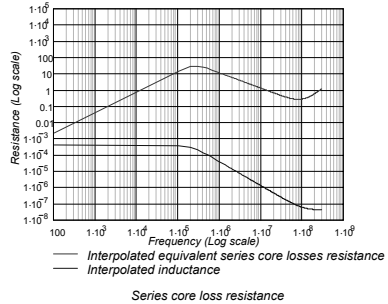



Frequency dependent – any difference ?

$N=10T$


10mm toroid

$A_e = 0.07 \text{ cm}^2$

$L_e = 2.2 \text{ cm}$

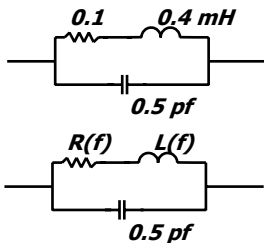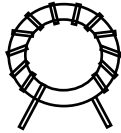

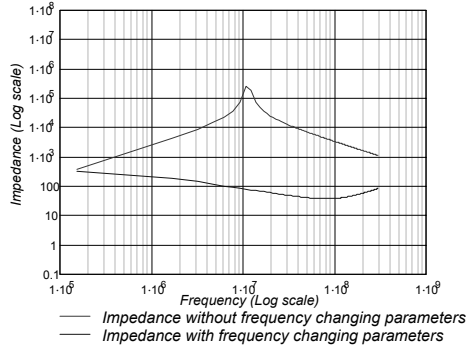
1,000 times difference between fixed and frequency varying parasitic



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Inductor's impedance
www.eee.hku.hk/power_electronics_lab/ 267

Frequency dependent – is EMI different ?

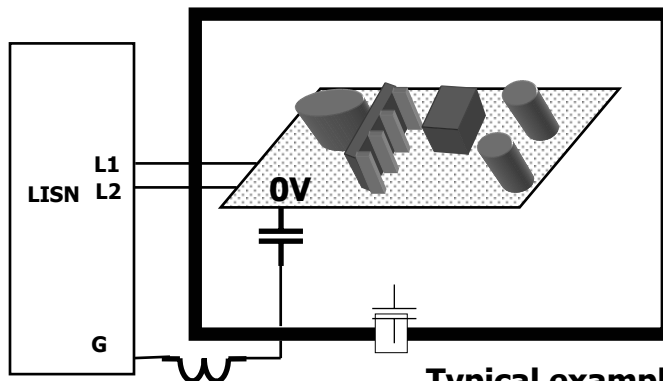


Typical example




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/ 268

EMI is different – typical example

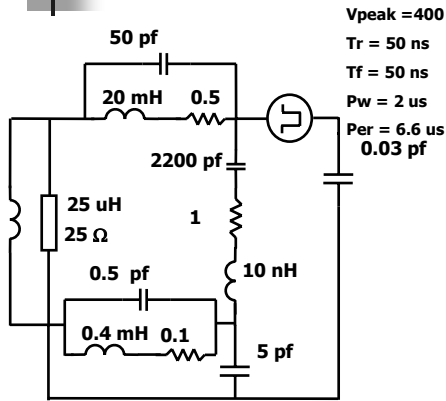


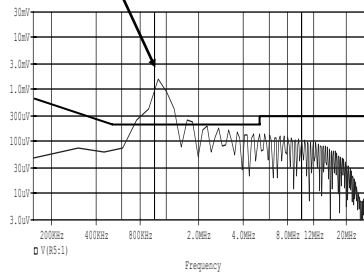Resonate occurs due to L and C. But you seldom see resonance after adding ground choke.




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

EMI is different – changing L and C

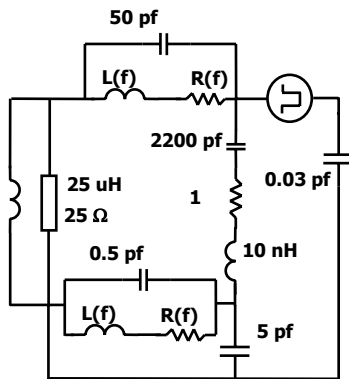

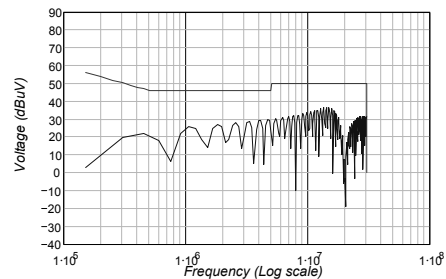The inductor change it's value at where it should resonate. Damping resistor increase at resonate frequency




CM noise with Freq. dependent filter



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

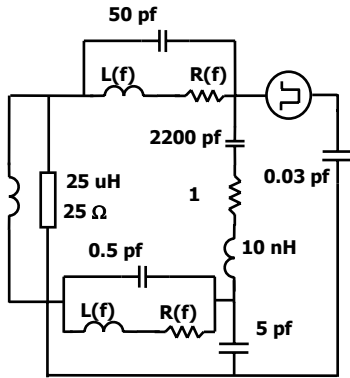Changing L and C – no more simple prediction




- Filter design
- Step 1 – determine the resonance
- Step 2 – choose the order
- Step 3 – choose damping factor
- Step 4 –




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Example 2 – ferrite bead

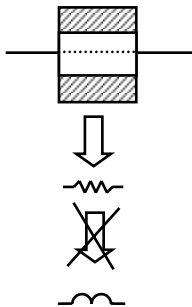

Resistance & Inductance(Log scale)

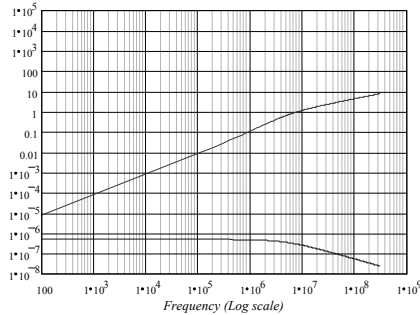

A small ferrite bead gives almost 10 Ω at 100 MHz, while keeping 0.01 Ω only at 100 kHz.



— Equivalent core loss series resistance
— Effective inductance against frequency

Core loss series resistance & Inductance against frequency




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Example 3 – series CMC

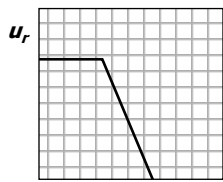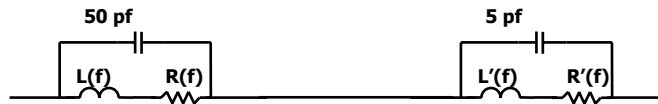

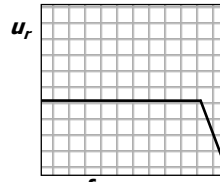
High u_r for high impedance at low frequency




Low u_r for high impedance at high frequency



Series CMC – cheap alternative

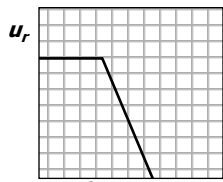

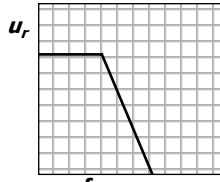High u_r for high impedance at low frequency



Low stray capacitance for medium impedance at high frequency



Short Summary


- Permeability of a high permeability ferrite usually start to roll off at around 200kHz.
- So it usually give maximum impedance at that frequency
- Resistive Losses can be very high depending on N^2 and f^2 .
- The equivalent loss resistor pay a great role in filtering design to provide damping effect.
- Magnetic material do not work on the way I approximate. It is more complicated and highly non-linear.



Any short question?




Radiated emission

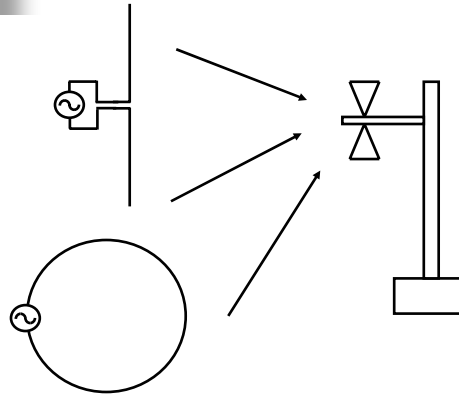

Radiated emission is transmitted and received by an antenna.




Antenna theory 1

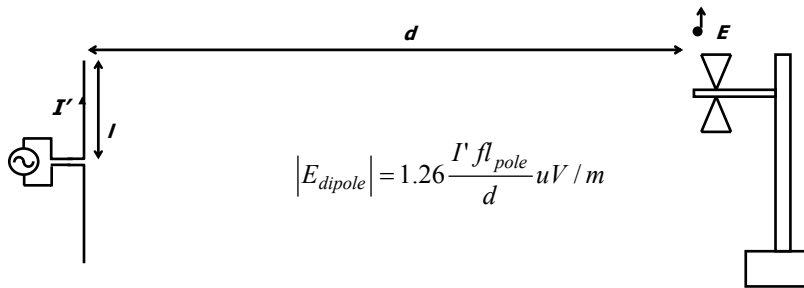


$$|E_{dipole}| = 1.26 \frac{I' \sin \theta}{d} \text{ uV/m}$$



Antenna theory 2

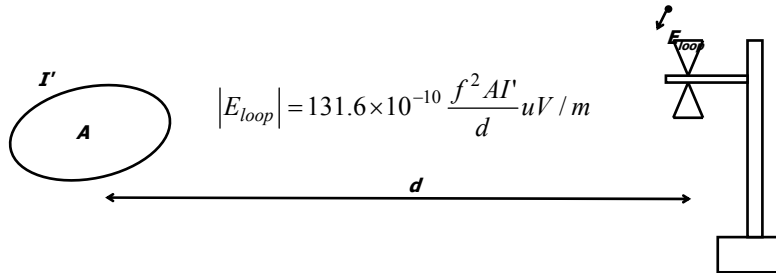


Dipole – capacitive like antenna

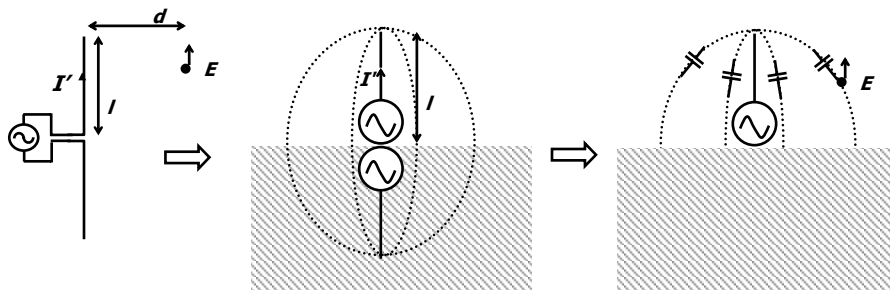

$$|E_{dipole}| = 1.26 \frac{I' f l_{pole}}{d} \text{ uV / m}$$




Dipole – cable and converter

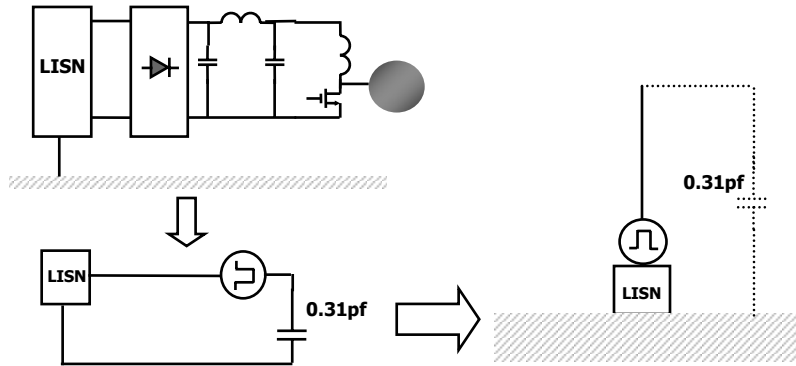

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


Cable and converter – 10m simulation

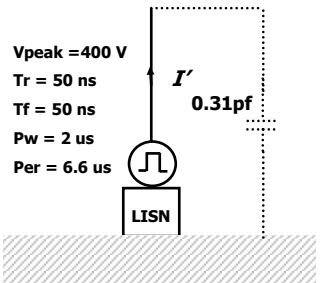

V_{peak} = 400 V
Tr = 50 ns
Tf = 50 ns
Pw = 2 us
Per = 6.6 us

$$|E_{dipole}| = 1.26 \frac{I' f l_{pole}}{d} \text{ uV/m}$$

Limit Exceeded !!

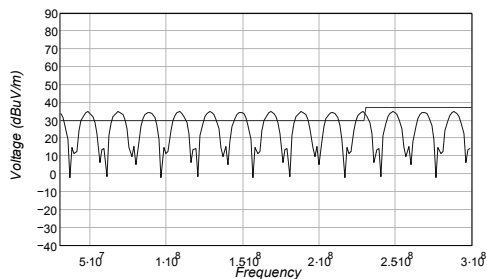


— CISPR22 radiated class B limit line
- - - 10m radiated noise emit from dipole

10m radiated noise generated by cable



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


Loop – inductive like antenna

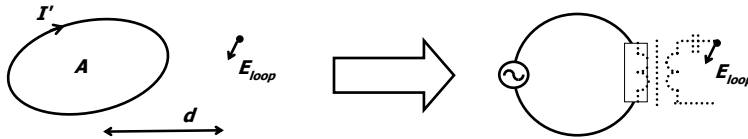

$$|E_{loop}| = 131.6 \times 10^{-10} \frac{f^2 AI'}{d} \text{ uV/m}$$




Loop antenna – current source excitation

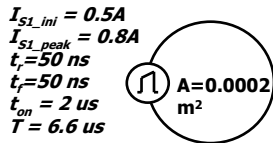

$$|E_{loop}| = 131.6 \times 10^{-10} \frac{f^2 AI'}{d} \text{ uV/m}$$


Very very little noise is generated

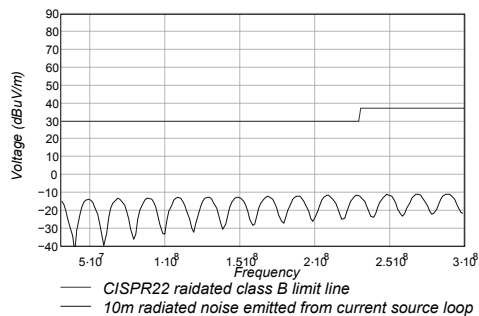

10m radiated noise by loop antenna




Loop antenna – voltage source excitation

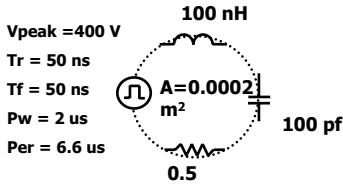


$$|E_{loop}| = 131.6 \times 10^{-10} \frac{f^2 A I'}{d} \text{ uV/m}$$

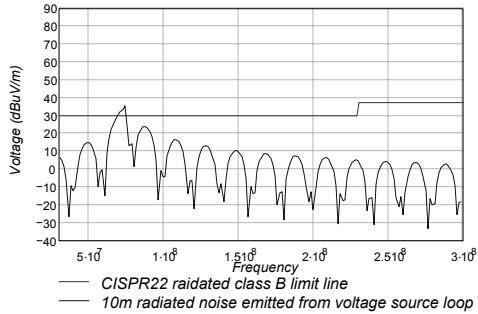Limited excessive emission due to resonance of the loop




10m radiated noise by loop antenna

Dipole antenna – an amplifier

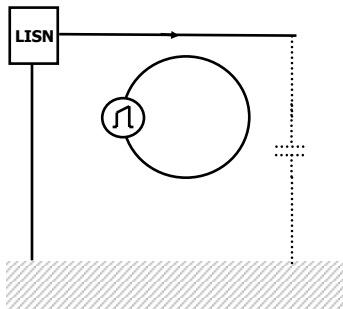


Converter cable will pick up the noise current by mutual inductive couple.

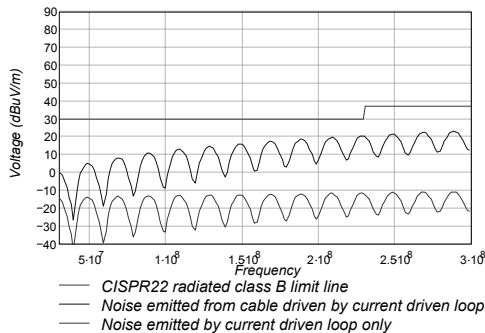Converter cable will amplify the loop noise and becomes the dominant emission antenna




Cable radiated noise by inductive couple

Cable and converter – suppression

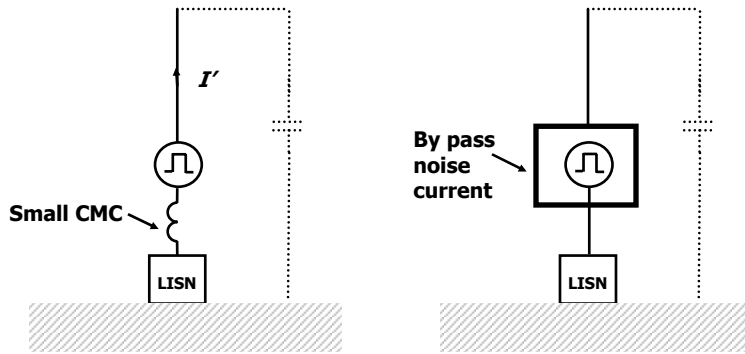

Loop antenna – suppression

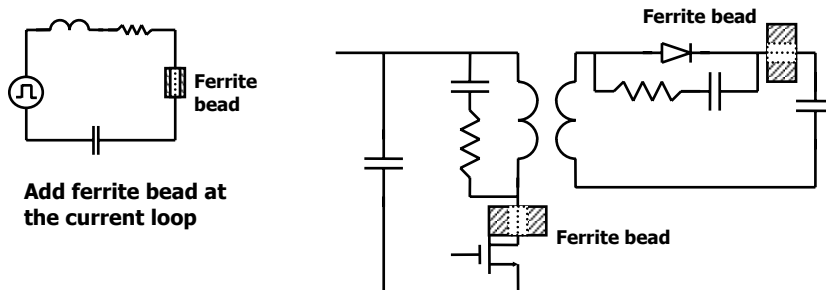


Short summary


- Cables generally emit more noise than loop
- A loop can emit substantial noise at resonate condition.
- A cable acts as an amplifier & picks up noise from a loop close by and emits at a much greater level.
- Impedance with small stray capacitance and high resistance can reduce radiated noise.



Misc. – Predicting radiated EMI

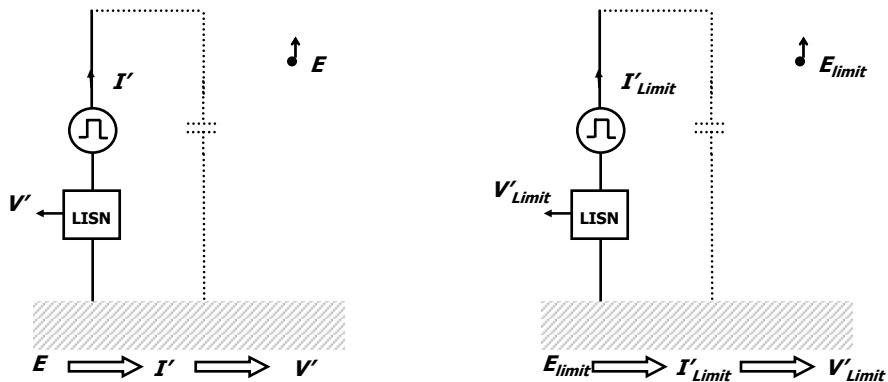

Misc. – Predicting radiated EMI

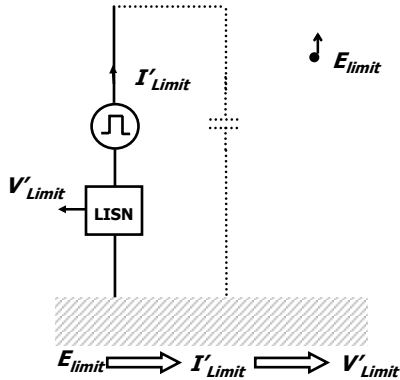

As E field is generated by a dipole

$$|E_{dipole}| = 1.26 \frac{I' fl_{pole}}{d} \mu V / m$$

The corresponding current limit flowing in the input cable is

$$I_{Limit} = \frac{E_{Limit} d}{1.26 fl_{cable}} 10^6$$

The corresponding voltage limit measured at the LISN

$$V_{Limit} = \frac{E_{Limit} d Z_{LISN-cm}}{1.26 fl_{cable}} 10^6$$




Misc. – Predicting radiated EMI

Assuming input and output cable are the same and the receiving antenna is 10m away

$$V_{LISN_RF_Limit} = \frac{250 E_{Limit}}{1.26 fl_{cable}} 10^6$$

	30MHz – 230MHz	230MHz – 1G
CISPR22 radiated emission limit		
Quasi peak limit(10m class B)	30dBuV /m	37dBuV /m

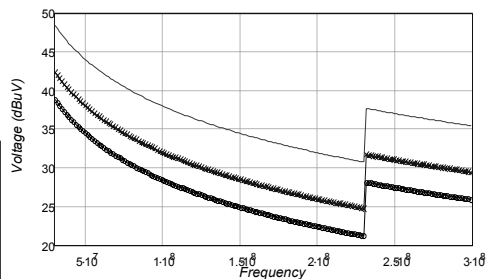Artificial Limit line of CISPR22 measured at LISN



— Artificial class B limit line for 1m cable
 x-x-x Artificial class B limit line for 2m cable
 o-o-o Artificial class B limit line for 3m cable


Artificial radiated class B limit line



Any short question?




MISC - Cancellation

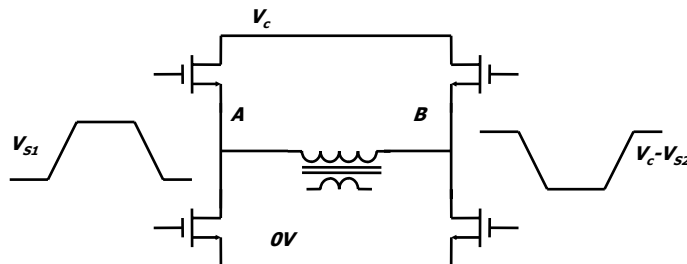

A full-bridge configuration has an inherent cancellation of voltage swing. The left leg will have an equal but opposite swing compared with the right leg.



MISC – capacitive coupling cancellation

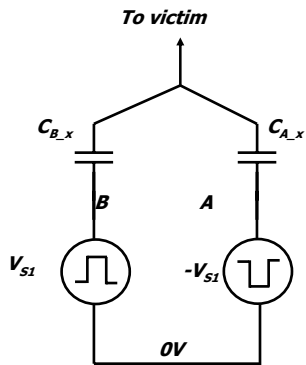

If


$$C_{B_x} = C_{A_x}$$

Then,

$$V_{victim} = 0$$




MISC – capacitive coupling cancellation

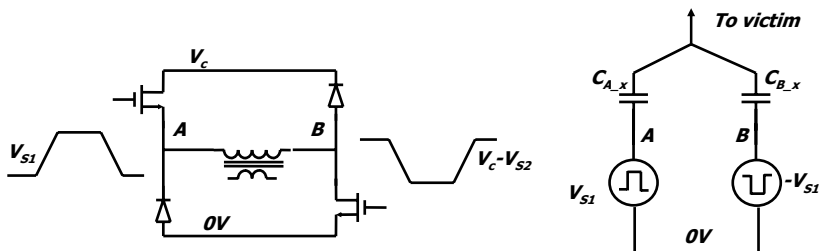


A two wheeler forward or flyback configuration has an inherent cancellation of voltage swing. The left leg has an equal but opposite swing compared with the right leg.



MISC – capacitive coupling cancellation

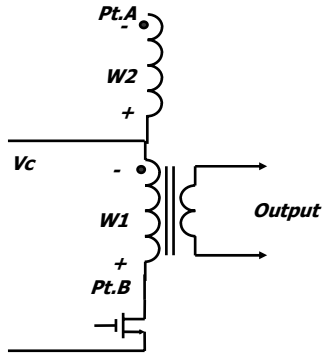


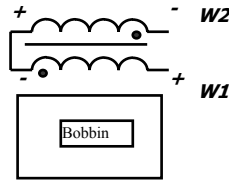A general method for voltage cancellation can make use of an anti phase winding to complete the task.



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


MISC – capacitive coupling cancellation

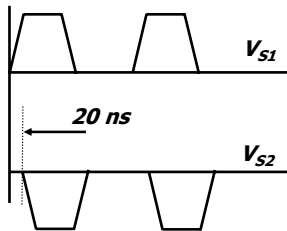

$$V_{S2}(t) = V_{S1}(t+20\text{ ns})$$

Be careful with time delay !

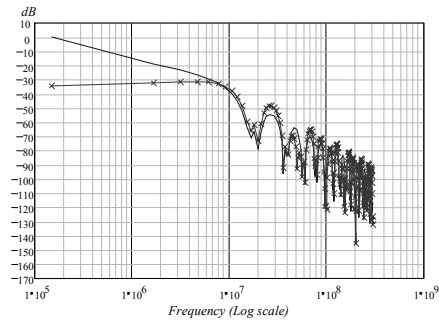A 20 ns delay will eliminate the cancellation effect at 10 MHz




— Normalized spectrum of V_{S1}
 × Normalized spectrum of $V_{S1}(t)-V_{S1}(t-T_d)$

Normalized noise source spectrum



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


Misc - Frequency jittering

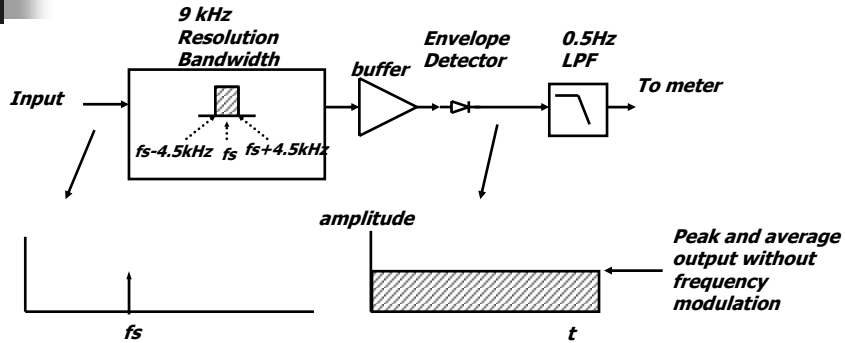

A single frequency injection into a receiver make the detector produce a dc voltage output with ripple where the peak, quasi-peak and average are the same




Misc - Frequency jittering

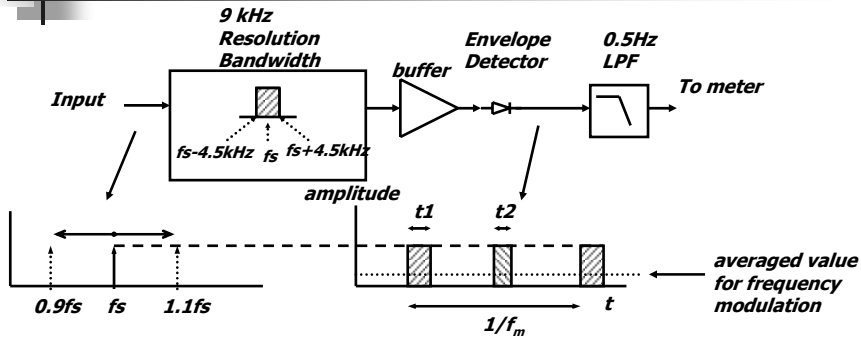

A changing frequency injection into the receiver make the detector produce a pulsing output voltage where the average value will have much lower value.



Misc - Frequency jittering

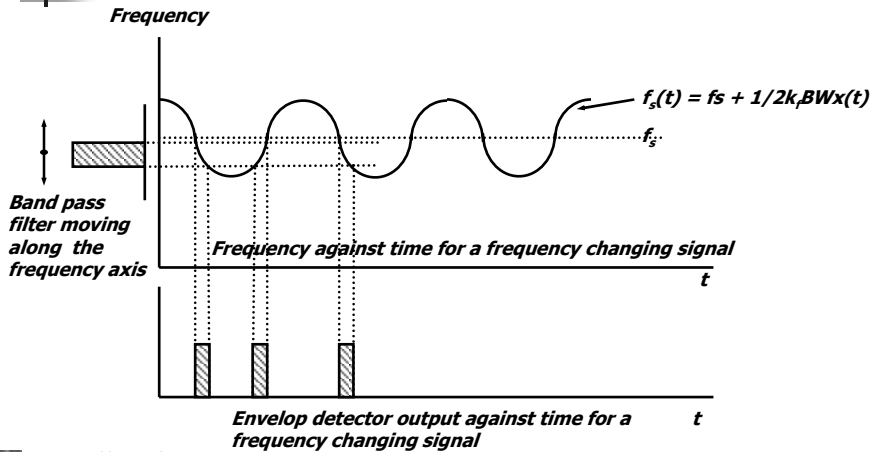

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Misc - Frequency jittering

$D_{on}(f_{BW})$ = normalized average value at the detector output

$$D_{on}(f_{BW}) = \int_{f - \frac{BW}{2}}^{f + \frac{BW}{2}} Pdf(f) df$$


The frequency jitter in a way

$$f = f_s + 1/2k_f BW \sin(2\pi f_m t)$$

The probability density function of the operating frequency is


$$Pdf(f) = \frac{1}{\sqrt{1 - \frac{2\pi(f - f_s)^2}{k_f BW}}}$$

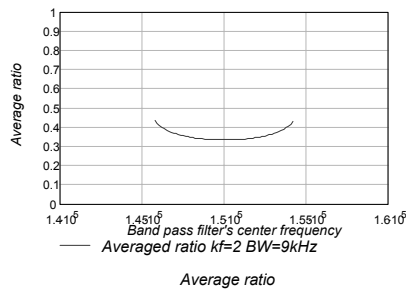The average value under a sine wave modulation will have a factor shown below




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


Misc - Frequency jittering

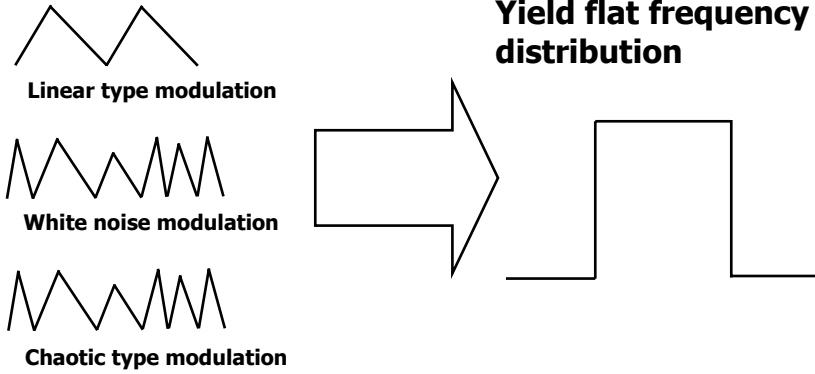

Misc - Frequency jittering

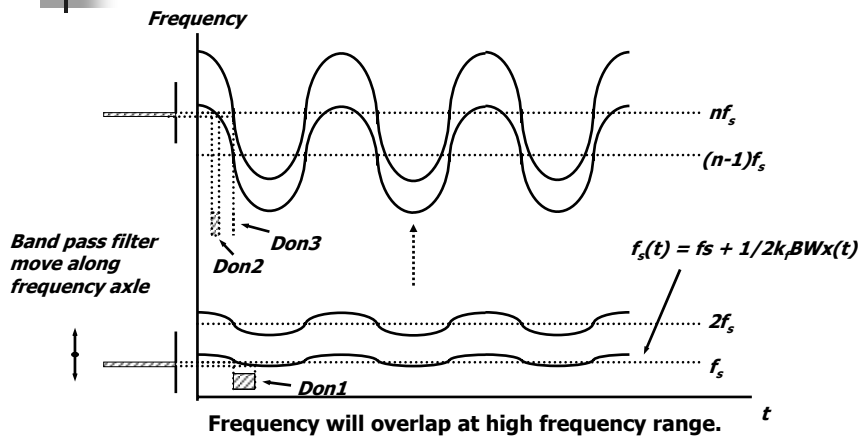

Misc - Frequency jittering

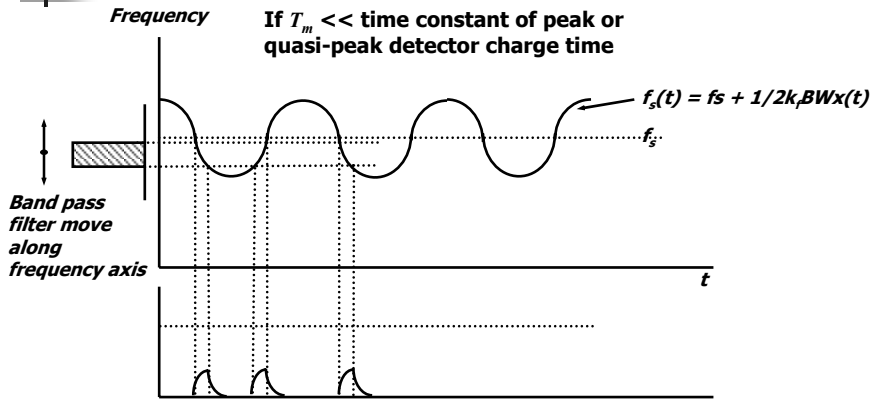

Don't be cheated by the spectrum screen !



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply


www.eee.hku.hk/power_electronics_lab/

305

Input cable

Refresh

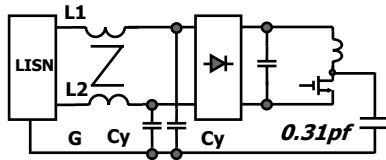
$CMC = 20\text{ mH} + 0.5\ \Omega$
// 50 pf



$Cy = 2200\text{ pf}$

No input cable parameter is considered.

No problem !

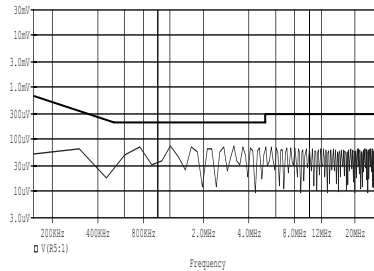


Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

www.eee.hku.hk/power_electronics_lab/

306

Input cable

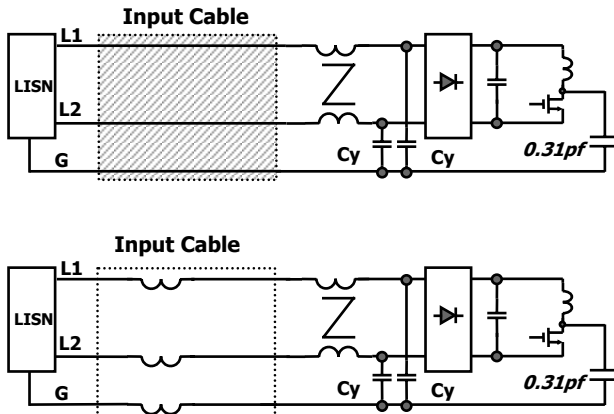


Consider the inductance of each wire



Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input cable

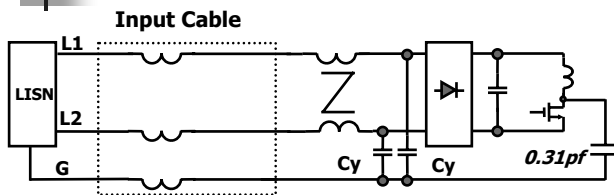

Consider the inductance of the each wire

$$L = 0.002l \left(\ln \left(\frac{4l}{d} \right) - 0.75 \right) \mu H$$

For a 1m cable

$l = 100 \text{ cm}$

$d = 0.1 \text{ cm}$





hence

$L = 1.5 \mu H$




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input cable – cable inductance

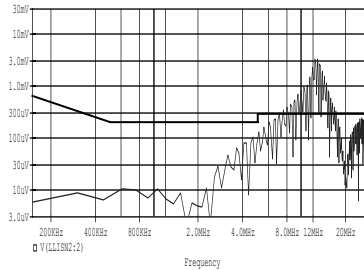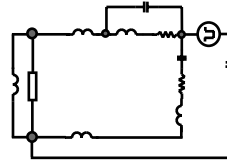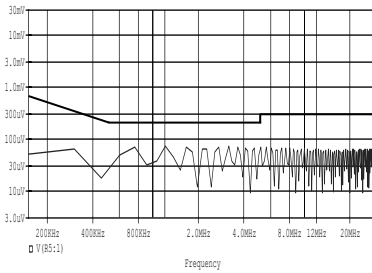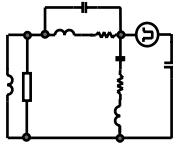

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input cable – mutual & self inductance

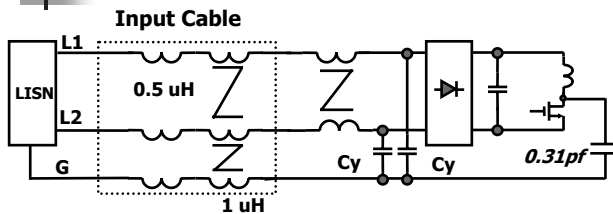

Consider the mutual and self inductance of the input cable

$$L_{12} = 0.002l \left(\ln\left(\frac{2l}{W}\right) - 1 + \frac{W}{l} \right) \mu H$$

For a 1m cable

$$l = 100 \text{ cm}$$

$$W = 0.4 \text{ cm}$$





hence

$$L_{12} = 1 \mu H$$




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input cable – mutual & self inductance

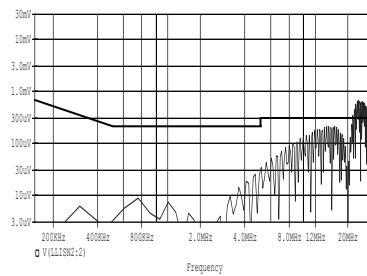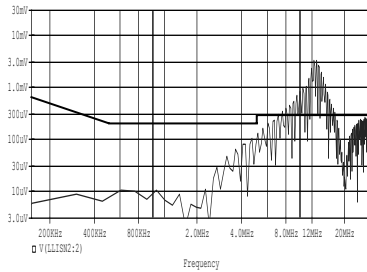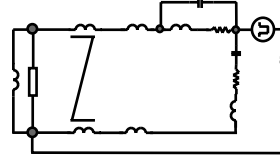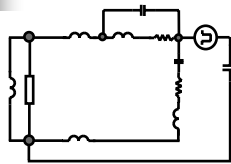

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input cable – inductance & capacitor

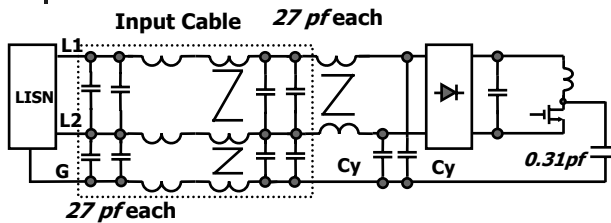

Consider the mutual capacitor, mutual and self inductance of the input cable

$$C = \frac{0.0885l\pi\epsilon_r}{\ln\left(2\frac{W}{d}\right)} \text{ pF}$$

For a 1m cable

$l = 100 \text{ cm}$

$W = 0.4 \text{ cm}$





hence

$C = 54 \text{ pf}$




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input cable – inductance & capacitance

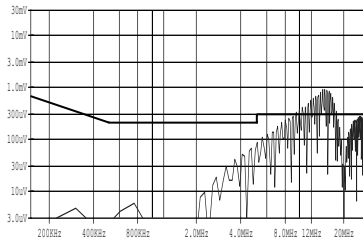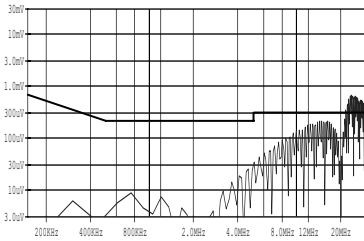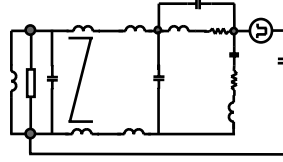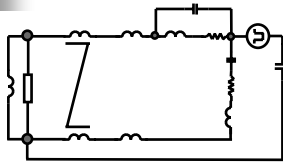

Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Input cable – inductance & capacitance

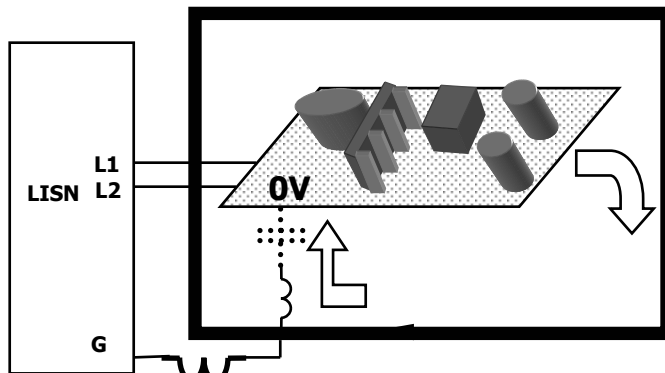

Solution




Prepared by Franki Poon & Bryan Pong
EMI in Switching Power Supply

Short Summary

- An anti-phase noise source is a possible solution to eliminate noise.
- Frequency jittering or modulation can reduce average reading.
- Input cable construction contributes to noise distribution pick up by the LISN.




Good or Bad ?

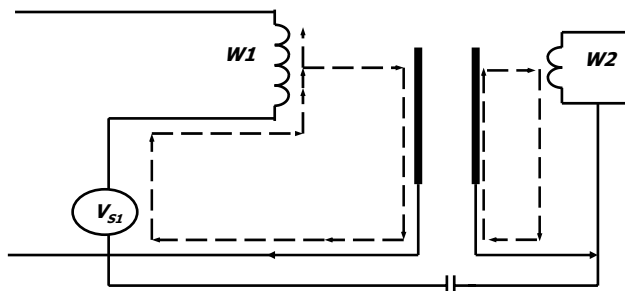

Faraday shield produces more invisible loops




Good or Bad ?

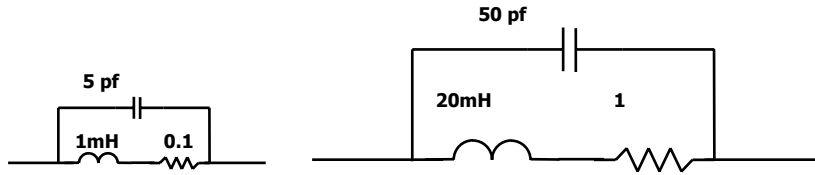

Increase number of turns will increase stray capacitance



Good or Bad ?

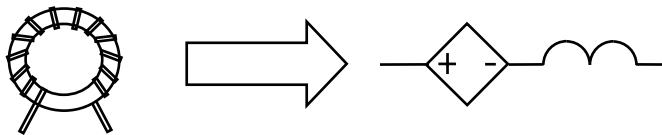

Add choke or CMC will pick up more noise



Conclusion ?

All Good things can cause
BAD EFFECTS



Question ?

Can **BAD** things cause
GOOD EFFECT ?



Simple logic


Statement 1 - All my correct solution doesn't work

Statement 2 - If there exist a solution

**Logic derivation - The solution must
be incorrect !**



Sometimes we have to

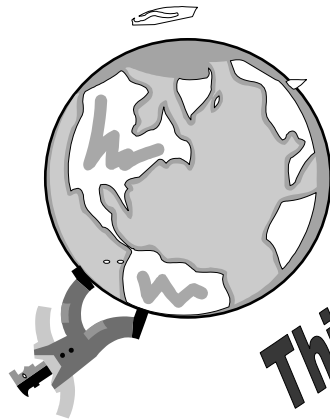

Think in a wrong way



Overall Summary

- EMI behavior is, at least, a summation of all of the above discussions.
- It is never an easy task to predict EMI result.
- Better understanding help prevention and diagnosis.



Reference

- [1]. **Tim William, EMC for Product Designers, Butterworth-Heinemann Ltd. 1994**
- [2]. **Jeffrey P.Mill, Electro-magnetic Interference Reduction in Electronic Systems, PTR Prentice Hall, Englewood Cliffs, New Jersey 07632, 1993**
- [3]. **Mark D. Herema, Designing for Electromagnetic Compatibility, HP11949B Hewlett Packard.**
- [4]. **Dongbing Zhang; Dan Chen; Sable, D. Non-intrinsic differential mode noise caused by ground current in an off-line power supply, Power Electronics Specialists Conference, 1998. PESC 98 Record. 29th Annual IEEE Volume: 2, 1998, Page(s): 1131 -1133 vol.2**
- [5]. **Wei Zhang; Zhang, M.T.; Lee, F.C.; Roudet, J.; Clavel, E., Conducted EMI analysis of a boost PFC circuit, Applied Power Electronics Conference and Exposition, 1997. APEC '97 Conference Proceedings 1997., Twelfth Annual Volume: 1, 1997, Page(s): 223 -229 vol.1.**



Reference

- [6]. Ferreira, J.A.; Willcock, P.R.; Holm, S.R., Sources, paths and traps of conducted EMI in switch mode circuits, Industry Applications Conference, 1997., Thirty-Second IAS Annual Meeting, IAS '97., Conference Record of the 1997 IEEE, Volume: 2, 1997, Page(s): 1584 -1591 vol.2.
- [7]. Qing Chen, Electromagnetic interference (EMI) design considerations for a high power AC/DC converter, Power Electronics Specialists Conference, 1998. PESC 98 Record. 29th Annual IEEE Volume: 2, 1998, Page(s): 1159 -1164 vol.2.
- [8]. Pong, B.M.H.; Lee, A.C.M., A method to measure EMI due to electric field coupling on PCB, Power Conversion Conference - Nagaoka 1997., Proceedings of the Volume: 2, 1997, Page(s): 1007 -1012 vol.2
- [9]. Pong, M.H.; Lee, C.M.; Wu, X., EMI due to electric field coupling on PCB, Power Electronics Specialists Conference, 1998. PESC 98 Record. 29th Annual IEEE, Volume: 2, 1998, Page(s): 1125 -1130 vol.2
- [10]. David K. Cheng, Field and Wave Electromagnetics, Addison Wesley second edition, :1989



Reference

- [11]. Ninomiya, T.; Shoyama, M.; Chun-Feng Jin; Ge Li, EMI issues in switching power converters, Power Semiconductor Devices & ICs, 2001. ISPSD '01. Proceedings of the 13th International Symposium on, 2001, Page(s): 81 -86
- [12]. Rossetto, L.; Buso, S.; Spiazzi, G., Conducted EMI issues in a 600-W single-phase boost PFC design, Industry Applications, IEEE Transactions on, Volume: 36 Issue: 2, March-April 2000, Page(s): 578 -585
- [13]. Gitau, M.N., Modeling conducted EMI noise generation and propagation in boost converters, Industrial Electronics, 2000. ISIE 2000. Proceedings of the 2000 IEEE International Symposium on, Volume: 2, 2000, Page(s): 353 -358 vol.2
- [14]. Cacciato, M.; Cavallaro, C.; Scarcella, G.; Testa, A., Effects of connection cable length on conducted EMI in electric drives, Electric Machines and Drives, 1999. International Conference IEMD '99, 1999, Page(s): 428 -430
- [15]. Joshi, M.; Agarwal, V., Generation and propagation of EMI waves in power electronic circuits, Power Electronics Specialists Conference, 1998. PESC 98 Record. 29th Annual IEEE, Volume: 2, 1998, Page(s): 1165 -1171 vol.2





Reference


- [16]. Okyere, P.F.; Heinemann, L., Computer-aided analysis and reduction of conducted EMI in switched-mode power converter, Applied Power Electronics Conference and Exposition, 1998. APEC '98. Conference Proceedings 1998., Thirteenth Annual , Volume: 2 , 1998, Page(s): 924 -928 vol.2
- [17]. Ferreira, J.A.; Willcock, P.R.; Holm, S.R., Sources, paths and traps of conducted EMI in switch mode circuits, Industry Applications Conference, 1997. Thirty-Second IAS Annual Meeting, IAS '97., Conference Record of the 1997 IEEE , Volume: 2 , 1997, Page(s): 1584 -1591 vol.2
- [18]. Wei Zhang; Zhang, M.T.; Lee, F.C.; Roudet, J.; Clavel, E., Conducted EMI analysis of a boost PFC circuit, Applied Power Electronics Conference and Exposition, 1997. APEC '97 Conference Proceedings 1997., Twelfth Annual , Volume: 1 , 1997 Page(s): 223 -229 vol.1,
- [19]. Bardos, P., Predicting the EMC performance of high frequency inverters, Applied Power Electronics Conference and Exposition, 2001. APEC 2001. Sixteenth Annual IEEE , Volume: 1 , 2001, Page(s): 213 -219 vol.1




Reference

- [20]. Laboure, E.; Costa, F.; Gautier, C.; Melhem, W., Accurate simulation of conducted interferences in isolated DC to DC converters regarding to EMI standards, Power Electronics Specialists Conference, 1996. PESC '96 Record., 27th Annual IEEE , Volume: 2 , 1996, Page(s): 1973 -1978 vol.2
- [21]. Knurek, D.F., Reducing EMI in switch mode power supplies, Telecommunications Energy Conference, 1988. INTELEC '88., 10th International , 1988, Page(s): 411 -420
- [22]. Poon, N.K.; Liu, C.P.; Pong, M.H, Least coupling paths model for non-contact EMI base on lump element approach in switch mode converter, Power Electronics Specialists Conference, 2001. PESC. 2001 IEEE 32nd Annual , Volume: 2 , 2001 Page(s): 577 -582 vol.2
- [23]. Paolo Tenti, Giorgio Spiazzi, One-day Course on electromagnetic Compatibility in Industrial Equipment: Standard, Problems and Solution, IEEE Hong Kong Joint Chapter of Power Engineering, Industry Application, Power Electronics and Industrial Electronics Societies, 25 Feb. 2002



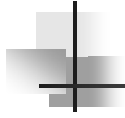

Bye bye, I miss you all

