

TK5401 Application Note (Ver.1.3)

Takion Co.,Ltd

http://www.takion.jp/

The contents in this document have a case to change without notice.

Aug,2009 Ver.1.3

<u>Contents</u>

0.Update History	3
1.General Description	4
2.Features	4
3.Block Diagram	4
4.Pin Functional Description	5
5.Package Outline	5
6.Electrical Characteristics	<u>6~8</u>
7.Power Supply IC Circuit Connection Example	9
8.Functional Description 10	<u>)~16</u>
8.1.Operating Oscillation	10
8.2.Power supply and Start-up Circuit 12	1~12
8.3.Constant Current Control Circuit	13
8.4.Adjustment Over Current Protection Circuit	14
8.5.COMP Pin Function	15
8.6.Latch Function	15
8.7.Thermal Shut Down Circuit	15
8.8.Over Voltage Protection Circuit	16
9.Application Circuit Example for LED Driver 1'	7~18
9.1.Application Circuit Example 1(Application for non-isolated, universal AC line, 3W to 8W)	17
9.2.Application Circuit Example 2(Application for isolated, universal AC line, 3W to 8W)	17
9.3.Application Circuit Exmaple 3(Application for phase-controlled dimming,AC100V,3W to 8W	<u>v) 18</u>
10.Typical Data's	9~20
11.Attentions 2	1~23

Takion TK5401 Application note

Revision	Description & changes	Date
Ver1.0	First edition	Mar.2009
Ver1.2	Full-scale revision	May.2009
Ver1.3	 Added to update history Added to TBD values Added to derating curve Revised circuit condition for application ex1 Added to application circuit ex2 Added to application circuit ex3 Added to typical data's 	Aug.2009

0.Update History


1. General Description

The TK5401 is a power supply IC for LED driver that had a characteristic to operate without electrolytic capacitors which is necessary for the DC power supply structure.

The IC has the high voltage power MOSFET and the control circuit built-in one package. And it is realized miniaturization, low cost by removing electrolytic capacitors. Moreover, it is realized long operating life and high energy efficiency of LED lamp.

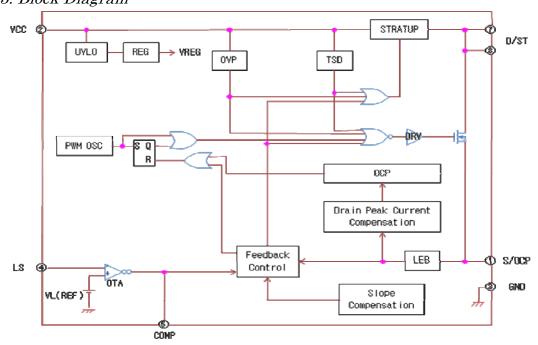2. Features

- Built-in the high voltage power MOSFET $(650V / 1.9\Omega)$
- •Supports the universal AC input voltage (AC85V~AC265V)
- Supplies low power with built-in the start-up circuit
- •PWM controls the power MOSFET at average oscillator frequency (67kHzTyp), feedback controls that assumed reference voltage (0.3VTyp) a standard to keep a fixed LED output current. Stop operating when a VCC voltage became less than Operating Supply Voltage.
- Over Voltage Protection / Thermal Shut Down (Stop operating by latch mode)
 Adjustable Over Current Protection
- Doing the input voltage monitor level in the 0V neighborhood by intermittent operation and operating repeatedly (In the case of the use to have power factor or dimming function, it is possible by adjustment of the voltage monitor)




3. Block Diagram

Aug,2009 Ver.1.3


4. Pin Functional Description

Pin #	Symbol	Function			
		Power MOSFET source connection			
1	S/OCP	Current limit sense			
2	Vcc	Power supply voltage			
3	GND	Ground			
4	LS	LED output current sense			
5	COMP	Erramp output \nearrow Phase compensation			
7	D/ST	Power MOSFET drain connection			
8	D/51	Input for start-up current			

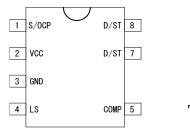

Top View

5. Package Outline

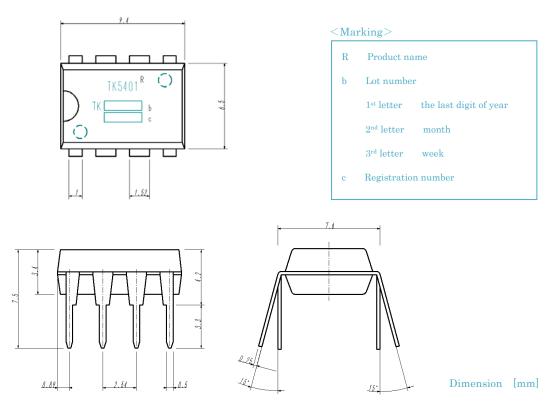

Aug,2009 Ver.1.3

Parameter	Symbol	ol Ratings Unit Conditions				
1 arameter	Symbol	natiligs	Om	Conditions		
Peak Drain Current	IDpeak 🎘 1	4.0	А	Single pulse		
Single Pulse	EAS ²	86	mJ	Single pulse		
Avalanche Energy	ILpeak	2.7	А	VDD=99V, L=20mH		
S/OCP Pin Voltage	VOCP	-2~6	V			
Power Supply Voltage	Vcc	32	V			
LS Pin Voltage	VLS	-0.3~6	V			
COMP Pin Voltage	VCOMP	-0.3~6	V			
Power Dissipation	PD1%3	1.0	W	₩4		
Operation Temperature	Topr	$-20 \sim +125$	W			
Storage Temperature	Tstg	$-40 \sim +125$	°C			
Channel Temperature	Tch	+150	°C			

Notes $\$ 1 Refer to MOSFET ASO curve

%2 $\,$ Refer to avalanche energy derating curve $\,$

3 Refer to power dissipation curve

2 Mounted on board size 15mm $\times 15$ mm, DIP8 package


Parameter	Symbol	Values			TT:4	Con litions
		MIN	TYP	MAX	Unit	Conditions
Drain to Source Breakdown	Wagg	650			V	
Voltage	VDSS	VDSS 650			v	
OFF-State Drain to Source	Ingg			300	۸	
Leakage Current	IDSS			300	μA	
Static Drain to Source	P DQ(ON)			1.0	Ω	
On-Resistance	RDS(ON)	(N) — —		1.9	52	
Delay time	td			250	ns	
Thermal Resistance	θ ch-c			22	°C/W	※ 4
(Channel to Case)	0 ch ⁻ c			22	C/W	※ 4


Aug,2009	Ver.1.3
----------	---------


Deveryoten	Symbol	Values			TT	Condition
Parameter		MIN	TYP	MAX	Unit	Conditions
●Power Source ∕ Start-up Fo	unctions					
Operating Supply Voltage	VCC(ON)	13.8	15.3	16.8	V	
Stop Supply Voltage (Undervoltage Lockout)	VCC(OFF)	7.3	8.1	8.9	V	
Operating Circuit Current	ICC(ON)			6	mA	
Start-up Supply Voltage	VST(ON)	26	31	36	V	
Start-up Supply Current	Istartup	-3.7	-2.5	-1.0	mA	Vcc=13.7V
Supply Threshold Voltage	VCC(BIAS)	7.5	9.5	10.5	V	
Oscillator Functions		1	1	1	1	I
Average Oscillator Frequency	fosc(ave)	60	67	74	kHz	
Oscillator Frequency modulation	Δf	1	5	9	kHz	
Maximum On Duty	Dmax	77	83	89	%	
Minimum On Time	TON(MIN)		420		ns	
•Over Current Protection Fun	ctions					
Leading Edge Blanking Time	TLEB	_	280	_	ns	
Drain Peak Current Adjustment Value	DPC		20		mV/ μ s	
Drain Peak Current Adjustment Limit Duty	Ddpc		36		%	
OCP Threshold Voltage (at Zero On Duty)	VOCP(L)	0.70	0.78	0.86	V	
OCP Threshold Voltage (at 36% Duty)	Vocp(h)	0.81	0.9	0.99	V	
●Reference Source ∕ Erramp	Functions					
Reference Voltage	VL(REF)	270	300	330	mV	
Erramp Gain	gm	33	67	100	μ S	
Erramp Source Current	ICOMP(SO)	-30	-20	-10	μA	V _{L(REF)} -0.3V
Erramp Sink Current	ICOMP(SINK)	10	20	30	μA	$V_{L(REF)}$ +0.3V
●Over Voltage Protection / 2	Thermal Shut	t Down	Functio	ns		
OVP Threshold Voltage	VCC(OVP)	26	29	32	V	
Latch Keep Current	IST(LATCH)		0.65	1.5	mA	
TSD Junction Temperature	Tj(TSD)	135			°C	


6.3. Electrical Characteristics of Control $(Vcc=18V,Ta=25^{\circ}C, unless otherwise noted)$


Aug,2009 Ver.1.3

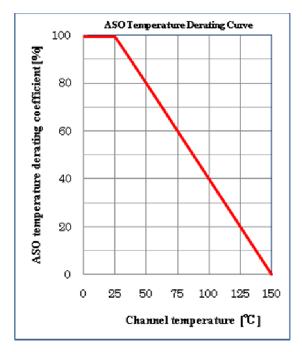

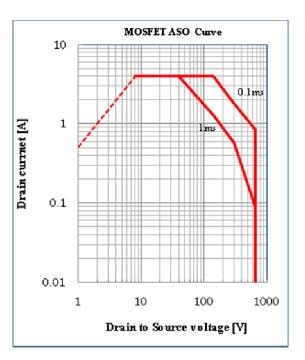

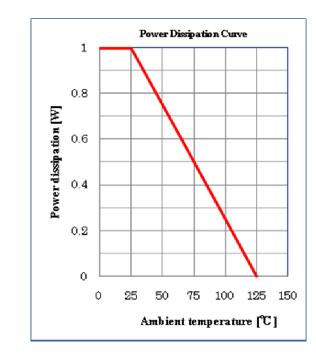

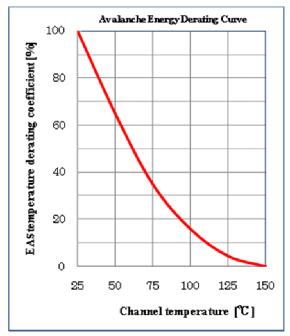

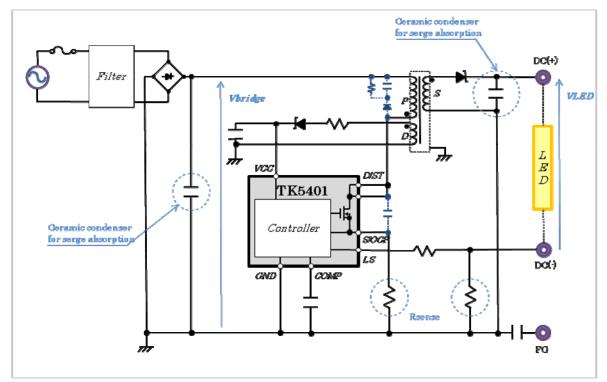


7. Power Supply IC Circuit Connection Example

8. Functional Description

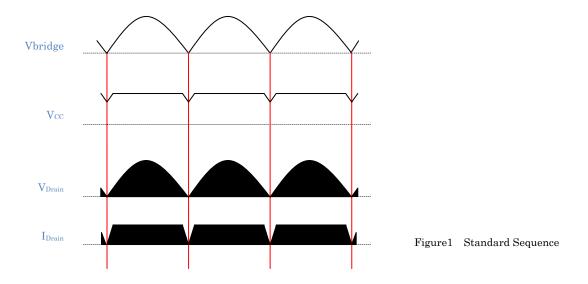8.1. Operating Oscillation

The general power supply IC has large capacitors which is essential to DC power supply structure. There is the input voltage monitor intermittent operation as the LED driver type which does not need large capacitors. The source of supply operating of the IC itself becomes a bridge output. The IC is possible to watches intermittent of this supply voltage and controls transformer and LED output. For the present conditions of the IC, this monitor level is set in the 0V neighborhood and operate repeatedly, and it is considered to lose a visual blink by LED driving pulse.

PWM controls the power MOSFET at average oscillator frequency, and feedback controls that assumed reference voltage a standard to keep a fixed LED output current. The inside reference voltage to use for this current control regards it as low voltage 0.3VTyp to reduce a loss of current sense resistance.



In addition, the typical oscillator frequency fosc(ave) is set to an average of 67kHz, and it is equipped with a random switching function for noise reduction of the same frequency.

<Random Switching Function>

The IC is equipped with a random switching function in PWM control. According to the statement above, it can simplify to noise filters of input so that noise reduction of the same frequency. During switching operation, it lets slightly change in typically 5kHz peak-to-peak for average frequency at random. Generally, the inside comparator replies to a sudden surge to occur when the power MOSFET turned on with current control mode. Therefore, there is the case that the power MOSFET turn off. The IC is equipped with a leading edge blanking function to prevent this phenomenon.

<Leading Edge Blanking Function>


This function arranges the blanking time of 280nSTyp from the moment when the power MOSFET turned on, and evades an above phenomenon.


8.2. Power supply and Start-up Circuit

Vcc(2pin) is a terminal for the energy supply that is necessary for the control circuit. The start-up circuit is connected to D/ST(7,8pin) in the IC inside. The start-up current charges condenser connected to Vcc pin. When Vcc pin rises to operating supply voltage Vcc(ON)=15.3VTyp, the IC operates. The start-up time is decided to capacity connected Vcc pin, can demand it by next type.

 $\underline{TSTART} = C \times (VCC(ON) - VCC(int)) / ISTARTUP$

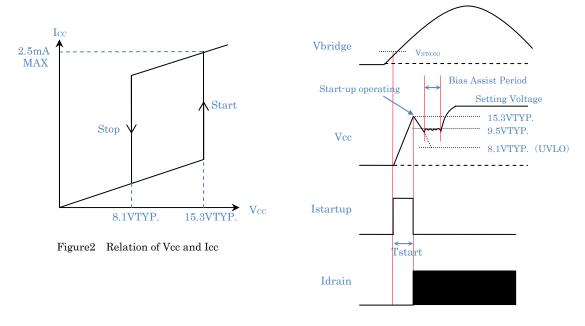*TSTART : Start-up time [S], VCC(int) : VCC initial voltage [V], C : Capacity connected Vcc pin[F]
The start-up circuit after starting-up disappear loss by itself to intercept automatically.



 



Shown in figure 2 is relation of Vcc voltage and circuit current. When the Vcc voltage reaches to 15.3V typical and the control circuit starts operating, the circuit current

increases. When the Vcc voltage reaches to 8.1V typical, the control circuit stops by under voltage lockout and comes back to the state before start-up again.

After the control circuit operating, the Vcc voltage gets a power supply by doing rectification flatness of winding voltage of a winding D. Please adjust of a winding D at around 20V from 15V so that the Vcc voltage becomes $\underline{\text{Vcc(OFF)=8.9VMAX} < \text{Vcc} <}$ $\underline{\text{Vcc(OVP)=26.0VMIN}$. Shown in figure 3 is start-up sequence. The voltage of a winding D does not rise to the setting voltage after the control circuit start operating immediately. Because the Vcc voltage begins to descend, and a bias assist function works when the Vcc voltage becomes less than 9.5V typical. During a bias assist function operation, it controls to drop of the Vcc terminal voltage, because the start-up current is supplied from the start-up circuit again.

Shown it in figure 4, there is the case that the Vcc voltage changes by a value of output current in the real power supply circuit. Because it is charged peak capacity connected Vcc pin by a surge voltage to occur when the MOSFET turned off. It is effective to add a resistance in series with a zener diode to prevent this phenomenon. It is really necessary for the most suitable value of this resistance to adjust a transformer to use in different by transformer structure to use.

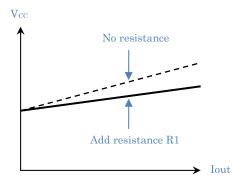


 

In addition, the rate of change of the Vcc voltage for output voltage turns worse so that transformer combination is bad. Therefore, this peak charge is relaxed by reducing under the influence of the surge voltage from primary winding P to a winding D. From the point of view, it is necessary to attention the scroll position of winding D in the transformer design.

Shown in figure5, figure6 is the reference example of the scroll position of a winding D.

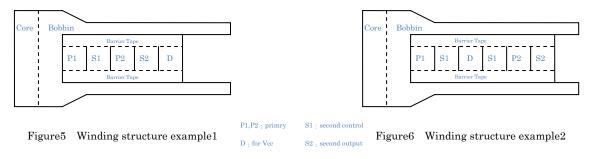- Separate distance with winding D and primary winding P (figure5)
- Structure to sandwich winding D in second side control winding S (figure6)



8.3. Constant Current Control Circuit

The IC converts this current into a voltage for current sense resistance to control output current of the LED and input it into LS(4pin) terminal. The IC controls so that makes constant voltage to this voltage.

Shown in figure 7 is constant feedback waveform. This control voltage is input into the Feedback Control circuit and generates the target voltage of the comparator by adding slope adjustment more. In addition, the Feedback Control circuit operates so that the drain peak current approach to above-mentioned target voltage. As a result, the IC compares this peak value and controls it.

Shown it in figure 8, as for the power supply of the peak current control method, drain current waveform change by a period of integer double of the switching frequency. Such a phenomenon call a subharmonic oscillation. It is theoretically problem to occur. Therefore a suitable adjustment that is stable operating is necessary. In the case of continuous mode, even if the drain peak current is constant, the ON period change for the initial value of drain current. As a result, the suitable operation is not maintained in a period of switching. The IC has the slope compensation circuit built-in to control this phenomenon.

The slope compensation circuit operates so that fall drain peak current as ON duty

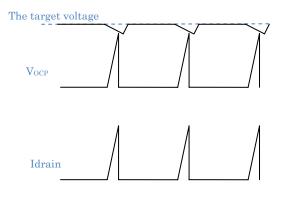


Figure 7 Constant Feedback Waveform


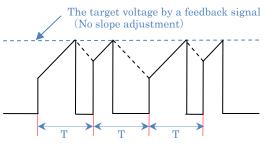


Figure 8 Drain Current Waveform by a Subharmonic Oscillation

become wide, and controls a subharmonic oscillation.

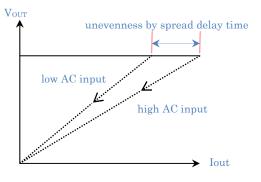8.4. Adjustable Over Current Protection Circuit

This circuit detects the peak value of drain current by every pulse and it is switched off the power MOSFET when D/ST(7pin,8pin) terminal voltage became over the OCP voltage. As this circuit has a input adjustable circuit built-in, it is realized overcurrent protection with a little AC input dependent.



The detection of drain current connects a current sense resistor between S/OCP(1pin) terminal to GND(3pin) terminal and carries it out. When

Figure9 output overload characteristics

the drop voltage by sense resistor reached the OCP threshold voltage, it is turned off the power MOSFET. The general PWM control IC tends to occur unevenness of drain peak current movement point for AC input voltage change.


Shown in figure 9 is output overload characteristics when the overcurrent protection circuit operated.


The IC has a input adjustable circuit built-in to adjust the unevenness. This circuit adjusts a difference of drain peak current movement point for AC input voltage.

This quantity of adjustment depend the value of drain peak current adjustment and on time. OCP threshold voltage after adjustment can demand it by next type.

 $\underline{VOCP[V]} = \underline{VOCP(L)[V]} + (\underline{DPC[V/\mu S]} \times ON Time[\mu S])$

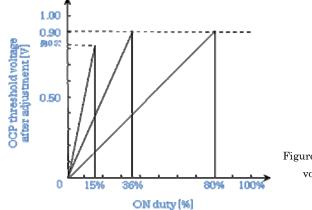But, OCP threshold voltage over ON duty 36% become VOCP(H)=0.9VTyp.



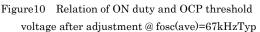

Shown in figure 10 is relation ON duty and OCP threshold voltage after adjustment. When you designed the transformer to become ON duty 36% in peak load and AC85V, the OCP movement point become to VOCP(H)=0.9VTyp.

The COMP pin is a terminal for phase compensation of the feedback control circuit. The condenser capacity to add, big one is stable, but it is necessary to adjust a fixed number after having confirmed a lead and delay of phase.

- (1) Stable operation, Abnormal oscillations or not
- (2) Start-up failure and Re-start failure or not

8.6. Latch Function

The latch circuit is stopped switching when OVP circuit and TSD circuit operated each and it protects the IC by keeping the stop state.

This circuit makes the delay time to prevent an irregular operation by noises and operates in the case of following to protect more than a constant time.

When the IC stops switching by this circuit, Vcc terminal voltage begins falling down. when Vcc terminal voltage falled down to 9.5V typical, it supplies start-up current in Vcc terminal. and it keeps the latch state to prevent falling down to 8.1V typical.

The latch cancellation turns off AC input once basically and it is canceled by falling Vcc terminal voltage to less than 8.1V typical.

8.7. Thermal Shut Down Circuit

When the junction temperature of IC reaches to 135° C by rising of the ambient temperature, the latch circuit operates.

The real temperature detection goes in a control element.

8.8. Over Voltage Protection Circuit

When the power supply IC became the no load state in constant current control, it become uncontrollable and occur to overvoltage in output. With it, the Vcc terminal voltage rises too. Shown in figure 11 is OVP circuit sequence.

The IC have the over voltage protection function built-in to protect output and load from overvoltage. The IC does not directly monitor, but it protects load by monitoring Vcc terminal voltage. In other words, the latch circuit operates and stops switching when Vcc terminal voltage exceed 29V typical.

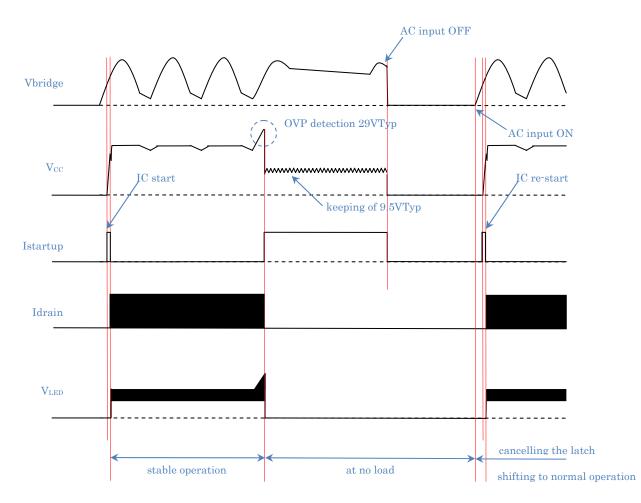



Figure11 OVP Circuit Sequence

9. Application Circuit Example for LED Driver


Shown below it is the application example for LED driver. The mention of parts name, parts placement, part fixed number are reference to the last.

For after considering attentions, the circuit fixed number and optimization of the transformer design, a heat design, EMC-prevention and so on are necessary for each load condition.

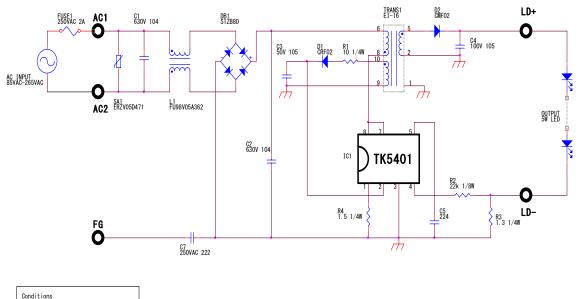9.1. Application Circuit Example 1(Application for non-isolated, universal AC line, 3W to 8W)




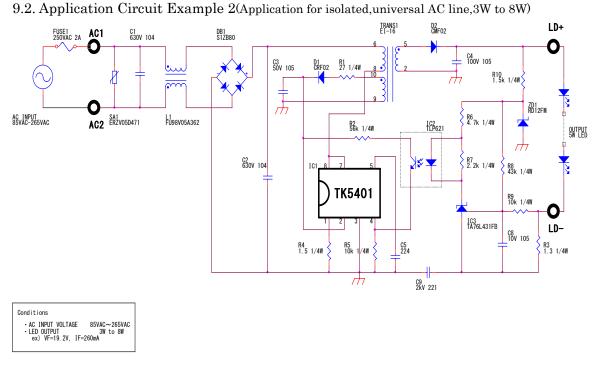- AC INPUT VOLTAGE 85VAC~265VAC - LED OUTPUT 3W to 8W ex) VF=19.2V, IF=260mA



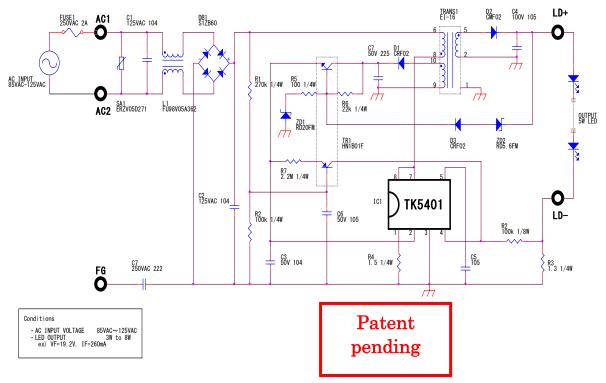9.3. Application Circuit Example 3

(Application for phase-controlled dimming, AC100V, 3W to 8W)




10. Typical Data's (The results of a 5W LED driver design)

10.1. Line regulation


Measurement condition : ambient temp, input freq 50Hz,

output voltage19.2V, output currnet260mA

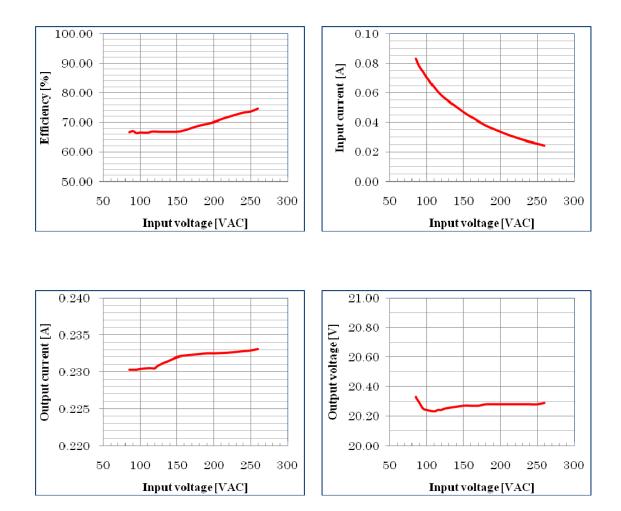

10.2. Ambient temperature characteristics

Aug,2009 Ver.1.3

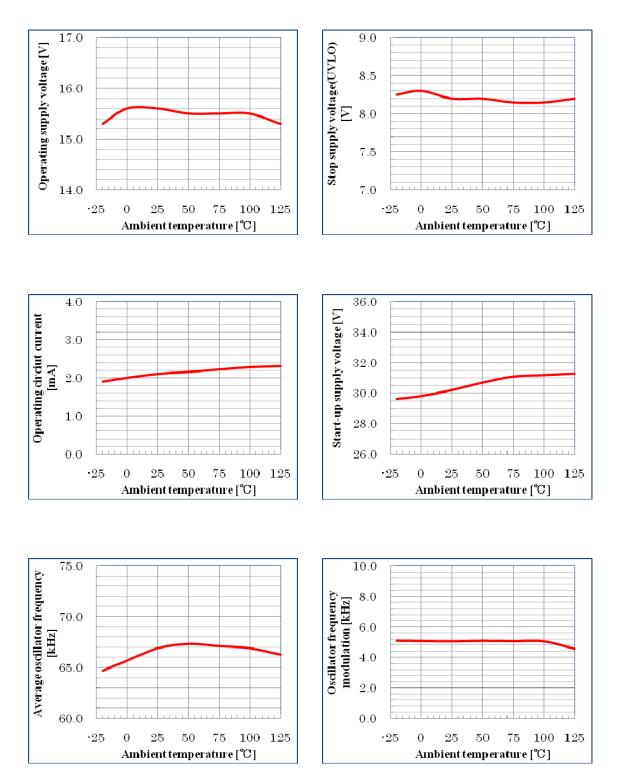

10.2. Ambient temperature dependence

11. Attentions

11.1. External Components

Each components of capacitance and inductance and power dissipation, please use it adapted in terms use. Transformer please suitably margin in each part for temperature rise by copper loss and iron loss. Please use a current sense resistor having small inside inductance and big serge tolerance because high frequency switching current flow.

Because a high frequency component is included for switching current, please find the transformer winding from a actual value of the operating current and select the current density of around 4 to 3A/mm2. In the case of temperature prevention,

For after considering the heating, it is necessary for transformer to adjust diameter and number of the winding that to lower the winding temperature by the increase of winding surface area by using Ritz lines.

- 11.2. Parts Placement and Pattern Design of Print Board
- (1) Shown it in figure 12, please wire it as possible thick and short for the loop patterns from S/OCP terminal to D/ST terminal of the IC so that switching current flow.
- (2) Please wire it as possible thick and short for the pattern of Vcc line. please insert a film condenser C (a level of $50V/0.1 \,\mu$ F) between Vcc terminal and GND terminal when the IC and distance with C2 are long by all means.
- (3) Drain terminal recommend so that make it as possible big pattern to be effective against the dissipation of heat.
- (4) Please wire it as possible short between S/OCP terminal and current sense resistor R1. In addition, please separate power GND and control GND by the other pattern well.

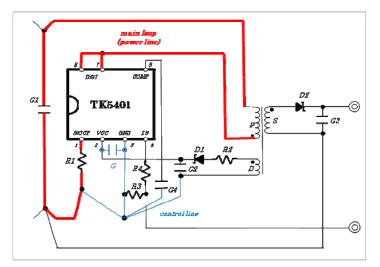


Figure12 Connect Pattern Example

11.3. Mounted Design of The Switching Power Supply

Please be careful wiring layout and parts placement enough because the irregular operation and noises and power loss show the great effect by patterning and mounting of conditions. Please consider it to lower the line impedance by making thick the pattern of high frequency current line and shortening the pattern of connection line between the parts.

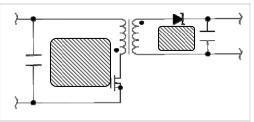


Figure13 Loop of High Frequency Current

Shown it in figure 13, please design pattern so that the loop area (section of diagonal) seem to become small as possible. Please shorten and thickly as possible ground line because it show the great effect for radiation noise.

The parts placement and the pattern distance that considered a safe standard are necessary because there are the route of high frequency and high voltage in general switching power supply.

Please be careful of designing the heat because the on-state resistance of Power MOSFET having a positive of temperature coefficient.

! Warning

• The contents in this document are subject to modify, for improvement and other purposes without notice. Please make sure that this document is the latest version before use.

• The operation and circuit examples in this document are provided for reference purposes only. Takion take on no responsibility for violation of industrial property, intellectual property, other rights of Takion or the third parties that be attributed to these examples.

• In the case of using that the product in this document, the user must take on responsibility for considering and determining.

•We will continue to improve quality and reliability of our products, but semiconductor products have certain fault and failure rates by nature.

The user must take on responsibility for designing and checking to secure equipment and system so that a part failure may not lead to injury accident, fire, social damages and others.

•Please don't use these products for devices that require high responsibility (such as transport machines and their control units, disaster prevention equipments, any kind of security equipment, aerospace instruments, nuclear power control units, medical instruments for life support and others).

•The contents in this document must not be transcribed or copied without our consent.