

Reference Design RD-269

PFC+PWM Combo Controller FAN6921 and Secondary-Side Synchronous Rectifier IC FSR510 - 90W Design

Featured Device	Application	Input Voltage Range	Output Voltage (Rated Current)	Rated Output Power	Topology
FAN6921 FSR510	Notebook Adaptor	90~264V _{AC}	19V (4.74A)	90W	BCM Boost PFC and Quasi-Resonant Flyback Converter

Key Features

FAN6921

BCM PFC Converter

- Zero-Current Detection
- Controlled On-Time Technique
- Cycle-by-Cycle Current Limiting
- Internal Leading-Edge Blanking for Current Sensing
- PFC Burst Mode Operation at Light-Load Condition (FAN6920)
- PFC Soft-Burst for Reducing Audible Noise
- Adjustable Burst Operation Voltage Range
- Minimum T_{OFF} for Frequency Limitation

Quasi-Resonant Converter

- Peak-Current-Mode Control
- Cycle-by-Cycle Current Limiting
- Internal Lead-Edge Blanking Time for Current Sensing
- Off-Modulation Technique
- Deep Extended Valley Switching
- Internal Minimum T_{OFF} for Frequency Limitation
- H/L Line Over-Power Compensation
- Internal 5ms Soft-Start

FSR510

- Highly Integrated Synchronous Rectification (SR) Combination Controller, Combining MOSFET and SR Controller
- Built-In Ultra-Low R_{DS-ON} MOSFET
- Internal Linear-Predict Timing Control Designed for Quasi-Resonant (QR) and Discontinuous Conduction Mode (DCM) Operation
- Internal Green-Mode Operation for Better No-Load Power Consumption
- PWM Frequency Tracking with Secondary-Side Winding Detection
- Ultra-Low V_{DD} Operating Voltage (5.3~25V) for Various Output Voltage Applications
- Ultra-Low Green-Mode Operating Current: 0.8mA (Typical)
- V_{DD} Over-Voltage Protection
- Gate Driver Clamp: 12V (Typical)
- TO220-6L Package



1. Schematic

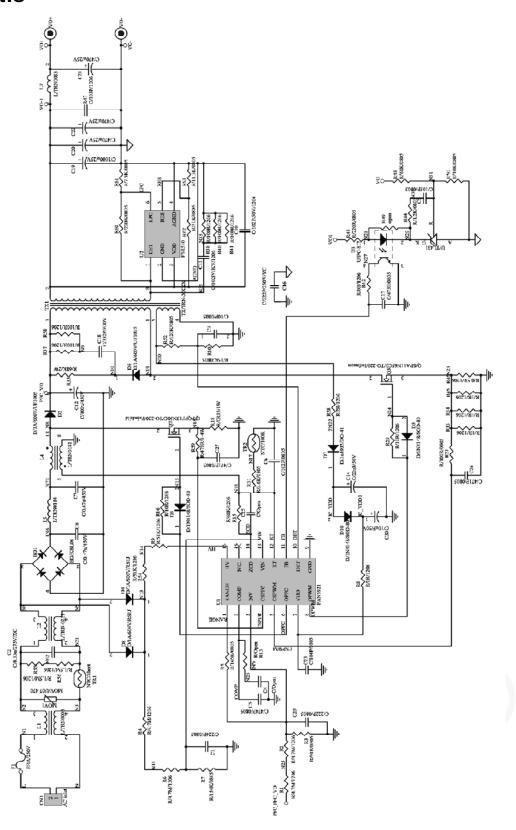


Figure 1. Schematic



2. Boost Inductor

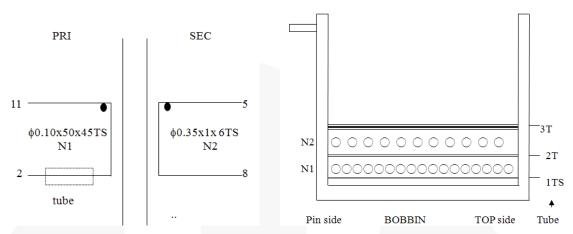


Figure 2. Inductor Schematic Diagram

2.1. Winding Specification

No	Pin (S - F)	Wire	Turns	Winding Method
N ₁	11→2	0.10Ф×50	45Ts	Solenoid Winding
Insulation: Mylar® Tape t = 0.03mm, 2 Layer				
N2	5→8	0.35Ф×1	6Ts	Solenoid Winding
Insulation: Mylar® Tape t = 0.03mm, 3 Layer				

Core: RM10 Bobbin: RM10

2.2. Electrical Characteristics

	Pin	Specification	Remark
Primary-Side Inductance	2-11	460µH ± 5%	100kHz, 1V

Mylar® is a registered trademark of Dupont Tejin Films



3. Flyback Converter Transformer

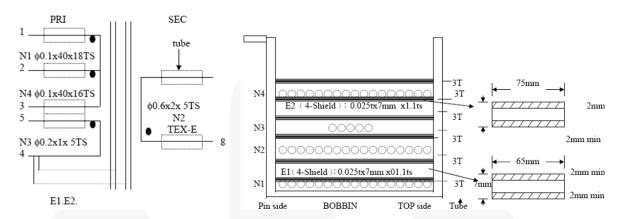


Figure 3. Transformer Schematic Diagram

3.1. Winding Specification

	Pin (S → F)	Wire	Turns	Winding Method	
N1	1 → 2	0.1φ×40	18	Solenoid Winding	
E1 Shie	Insulation: Polyester Tape t = 0.025mm, 3 Layer E1 Shield: 0.025mm x 7 mm, 1.1 turns, one end should be connected to pin 4 Insulation: Polyester Tape t = 0.025mm, 3 Layer				
N2	8 → Flying	0.60φ×2	5	Solenoid Winding	
Insulatio	Insulation: Polyester Tape t = 0.025mm, 3 Layer				
N3	5 → 4	0.20φ×1 5 Sole		Solenoid Winding	
E2 Shie	Insulation: Polyester Tape t = 0.025mm, 3 Layer E2 Shield : 0.025mm × 7mm, 1.1 turns, one end should be connected to pin 4 Insulation: Polyester Tape t = 0.025mm, 3 Layer				
N4	2 <i>→</i> 3	0.1φ×40 16 Solenoi		Solenoid Winding	
Insulatio	Insulation: Polyester Tape t = 0.025mm, 3 Layer				

Core: PQ3220 Bobbin: PQ3220

3.2. Electrical Characteristics

	Pin	Specification	Remark
Primary-Side Inductance	13	700µH ± 5%	100kHz, 1V
Primary-Side leakage Inductance	13	15µH ± 5%	Short One of the Secondary Windings



4. Typical Performance

Table 1. Standby Power Consumption

Operating Condition	Input Watts
When $V_{IN} = 90V_{AC}$, with No Load	0.225W
When $V_{IN} = 115V_{AC}$, with No Load	0.227W
When $V_{IN} = 240V_{AC}$, with No Load	0.263W
When $V_{IN} = 264V_{AC}$, with No Load	0.280W

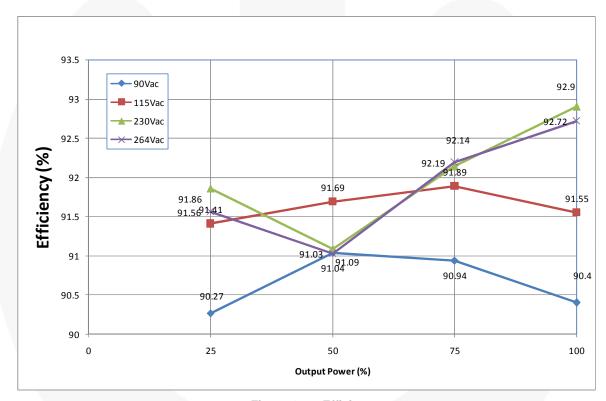


Figure 4. Efficiency



5. Related Resources

<u>FAN6921 — Integrated Critical Mode PFC and Quasi-Resonant Current Mode PWM Controller</u> Datasheet

FSR510 Highly Integrated Synchronous Rectification Combination Controller for Quasi-Resonant PWM Controller Datasheet

Reference Design Disclaimer

Fairchild Semiconductor Corporation ("Fairchild") provides these reference design services as a benefit to our customers. Fairchild has made a good faith attempt to build for the specifications provided or needed by the customer. Fairchild provides this product "as is" and without "recourse" and MAKES NO WARRANTY, EXPRESSED, IMPLIED OR OTHERWISE, INCLUDING ANY WARRANTY OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE.

Customer agrees to do its own testing of any Fairchild reference designs in order to ensure design meets the customer needs. Neither Fairchild nor Customer shall be liable for incidental or consequential damages, including but not limited to, the cost of labor, re-qualifications, rework charges, delay, lost profits, or loss of goodwill arising out of the sale, installation or use of any Fairchild product.

Subject to the limitations herein, Fairchild will defend any suit or proceeding brought against Customer if it is based on a claim that any product furnished hereunder constitutes an infringement of any intellectual property rights. Fairchild must be notified promptly in writing and given full and complete authority, information and assistance (at Fairchild's expense) for defense of the suit. Fairchild will pay damages and costs therein awarded against Customer but shall not be responsible for any compromise made without its consent. In no event shall Fairchild's liability for all damages and costs (including the costs of the defense by Fairchild) exceed the contractual value of the products or services that are the subject of the lawsuit. In providing such defense, or in the event that such product is held to constitute infringement and the use of the product is enjoined, Fairchild, in its discretion, shall procure the right to continue using such product, or modify it so that it becomes noninfringing, or remove it and grant Customer a credit for the depreciated value thereof. Fairchild's indemnity does not extend to claims of infringement arising from Fairchild's compliance with Customer's design, specifications and/or instructions, or the use of any product in combination with other products or in connection with a manufacturing or other process. The foregoing remedy is exclusive and constitutes Fairchild's sole obligation for any claim of intellectual property infringement and Fairchild makes no warranty that products sold hereunder will not infringe any intellectual property rights.



All solutions, designs, schematics, drawings, boards or other information provided by Fairchild to Customer are confidential and provided for Customer's own use. Customer may not share any Fairchild materials with other semiconductor suppliers.

