

FSDH321

(Application for DVB Power Supply)

Test Report

Featured Fairchild Products:

FSDH321, KA431A, FOD817



Disclaimer

Fairchild Semiconductor Limited ("Fairchild") provides these design services as a benefit to our customers. Fairchild has made a good faith attempt to build for the specifications provided or needed by the customer. Fairchild provides this product "as is" and without "recourse" and MAKES NO WARRANTY, EXPRESSED, IMPLIED OR OTHERWISE, INCLUDING ANY WARRANTY OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE.

Customer agrees to do its own testing of any Fairchild design in order to ensure design meets the customer needs. Neither Fairchild nor Customer shall be liable for incidental or consequential damages, including but not limited to, the cost of labor, re-qualifications, rework charges, delay, lost profits, or loss of goodwill arising out of the sale, installation or use of any Fairchild product.

Fairchild will defend any suit or proceeding brought against Customer if it is based on a claim that any of its products infringes any U.S., Canadian, Japanese, EU or EFTA member country intellectual property right. Fairchild must be notified promptly in writing and given full and complete authority, information and assistance (at Fairchild's expense) for defense of the suit. Fairchild will pay damages and costs therein awarded against Customer but shall not be responsible for any compromise made without its consent. In no event shall Fairchild's liability for such damages and costs (including legal costs) exceed the contractual value of the goods or services that are the subject of the lawsuit. In providing such defense, or in the event that such product is held to constitute infringement and the use of the product is enjoined, Fairchild, in its discretion, shall procure the right to continue using such product, or modify it so that it becomes non-infringing, or remove it and grant Customer a credit for the depreciated value thereof. Fairchild's indemnity does not extend to claims of infringement arising from Fairchild's compliance with Buyer's design, specifications and/or instructions, or use of any product in combination with other products or in connection with a manufacturing or other process. The foregoing remedy is exclusive and constitutes Fairchild's sole obligation for any claim of intellectual property infringement.

All solutions, designs, schematics, drawings, boards or other information provided by Fairchild to Customer are confidential and provided for Customer's own use. Customer may not share any Fairchild materials with other semiconductor suppliers.



Table of Content

1	1 General Introduction						
	1.1 Features of FSC Products1.2 Electrical Specification Requirement						
2	Circuit Description	5					
	 2.1 Demo Board Photo 2.2 Schematic 2.2.1 Circuit Description 2.2.2 Start Up 	5 6					
3	PCB Layout						
	3.1 Components Placement3.2 Bottom PCB Layout						
4	Bill of Material						
	4.1 Transformer Design4.2 Part List						
5	Test Result	10					
	 5.1 Start Up 5.2 Normal Operation 5.3 Power Off Waveform 5.4 Output Short Protection 5.5 Feed Back Circuit Open 5.6 Burst Operation 	11 11 12 14					
6	Efficiency and Output Voltage Test Result						
7 Reference and Resource							
	7.1 Application Notes	16					
8	Warning and Disclaimer						



1. General Introduction

FSDH321 Fairchild Power Switch (FPS) which is utilized in DVB power supply. FSDH321 is also used in adapter, charger applications. In order to minimize the power consumption in standby mode, the burst operation was applied. This demo board operates over an AC input range of 85VAC to 265VAC.

1.1 Features of Fairchild Products

FSDH321

http://www.fairchildsemi.com/pf/FS/FSDH321.html

Fairchild Power Switch (FPS)

- Internal avalanche rugged sense FET
- Consumes only 0.65W at 240VAC & 0.3W load with Advanced Burst-Mode Operation
- Frequency Modulation for EMI Reduction
- Precision Fixed Operating Frequency
- Internal Start-up Circuit
- Pulse-by-Pulse current limiting
- Abnormal over current protection (AOCP)
- Over voltage protection (OVP)
- Over load protection (OLP)
- Internal thermal shutdown function (TSD)
- Auto-restart mode
- Under voltage lockout (UVLO)
- Low operating current (max 3mA)
- Adjustable peak current limit
- Built-in soft start

KA431A

- Programmable output voltage to 36V
- 2.5V reference voltage, 50ppm/°C typical temperature coefficient
- Sink current capability of 1.0mA to 100mA

FOD817

- 4-DIP optotransistor output opto-coupler
- 5300 Vrms isolation

1.2 Electrical specification Requirement

Description	Min	Тур	Max	Units
Input Voltage (Vin)	85		265	Vac
Output Voltage (Vout1)	3.25	3.3	3.3 3.35	
Output Current (lout1)			1.0	Adc
Output Voltage (Vout2)	20.50	21	21.50	Vdc
Output Current (lout2)			0.15	Adc

Table 1. Power Supply Spec.



2. Circuit Description

2.1 Demo Board Photo


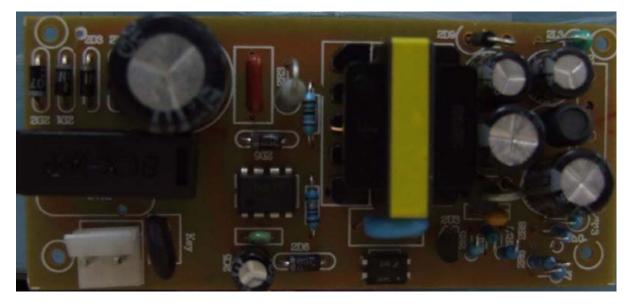


Figure 1. Photograph of Demo Board

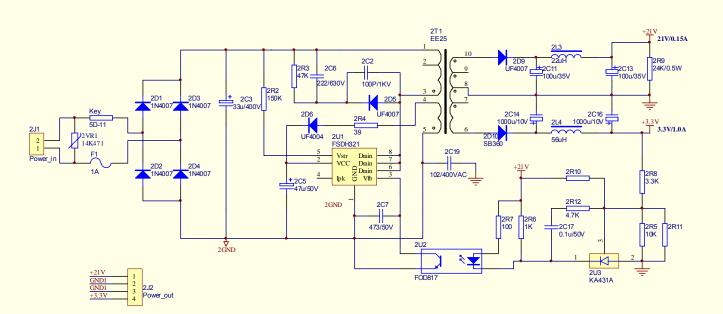

2.2 Schematic

Figure 2. Flyback Converter Schematic



2.2.1 Circuit Description

The demo board was based on flyback topology design. Flyback topology is poplar in power conversion because of the small relative components, the output power can be up to 100W. The detail design guides can be found in FSC application notes AN-4137 and AN-4140.

2.2.2 Start Up

The input of demo board is 85Vac to 265Vac.

When power on, the internal high voltage current source charge the Vcc capacitor C5 through 2R2. The internal switch will shut off when Vcc is above 12V and the operation voltage of Vcc will come from the source turn of transformer. The 2R2 is no use during FPS is normal operation until next start up process, so it can reduce the power consumption.

3. PCB Layout

3.1 Components Placement

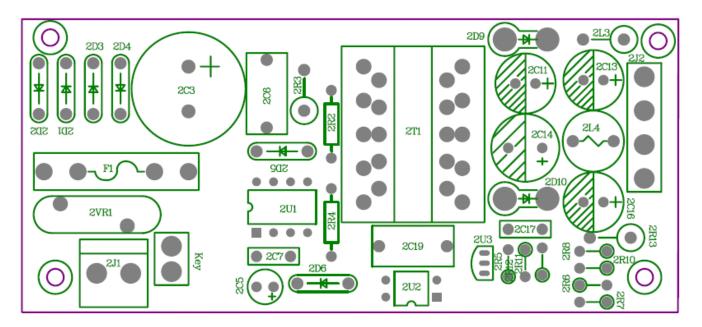


Figure 3. Top PCB Image



www.fairchildsemi.com

3.2 Bottom PCB layout

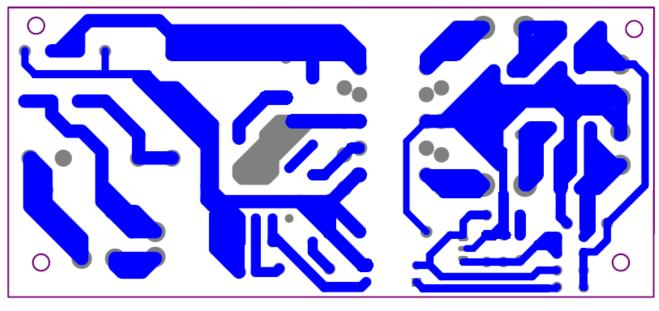


Figure 4. Bottom PCB Image

4. Bill of Material

4.1 Transformer Design

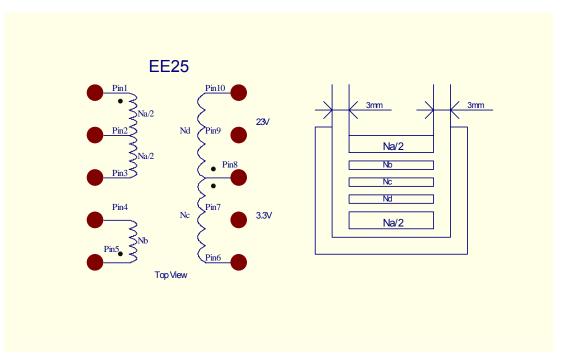


Figure 5. Transformer Specification



SEMICONDUCTOR

www.fairchildsemi.com

	Pin	Wire	Turn	Winding Method				
Na/2 1-2		ф0.35*1	30	Center Solenoid Winding				
	Insu	lation: Polyeste	r Tape t=0.050)mil, 2Layers				
Nb	5-4	ф0.23*1	12	Center Solenoid Winding				
	Insu	lation: Polyeste	r Tape t=0.050)mil, 2Layers				
Nc	8-6	ф0.35*3	3	Center Solenoid Winding				
Insulation: Polyester Tape t=0.050mil, 2Layers								
Nd	Nd 8-10 dp0.35*1 18 Center Solenoid Winding							
	Insulation: Polyester Tape t=0.050mil, 2Layers							
Na/2	2-3	ф0.35*1	38	Center Solenoid Winding				
	Insulation: Polyester Tape t=0.050mil, 2Layers							

Table 3. Winding Specification

Core: EE25 (Ae=44.3 mm²)

	Pin	Spec.	Remark
Inductance	1-3	1.0mH +/-10%	@100KHz
Leakage	1-3	10uH	Short all other pins

 Table 4. Electrical Characteristics

SEMICONDUCTOR

4.2 Part List

Part Value		Comment	Part	Value	Comment	
	Resistor		Capacitor			
2R2	150K	1/4W	2C2	100p/1KV	Open	
2R3	47K	1W	2C3	33u/400V	Electrolytic	
2R4	39	1/4W	2C5	47u/50V	Electrolytic	
2R5	10K	1/4W	2C6	222/630V	Polyester	
2R6	1K	1/4W	2C7	473/50V	Ceramic	
2R7	100	1/4W	2C11	100u/35V	Electrolytic	
2R8	3.3K	1/4W	2C13	100u/35V	Electrolytic	
2R9	24K	1/2W	2C14	1000u/10V	Electrolytic	
2R10		Open	2C16	1000u/10V	Electrolytic	
2R11		Open	2C17	0.1u/50V	Ceramic	
2R12	4.7K	1/4W	2C19	102/2KV	Ceramic	
2VR1	14K471	Open	Diode			
	Inductor		2D1	1N4007		
2L3	22uH	0.5A	2D2	1N4007		
2L4 56uH		1.5A	2D3	1N4007		
	IC		2D4	1N4007		
2U1	FSDH321	FPS	2D5	UF4007		
2U2	FOD817	Opto-Coupler	2D6	UF4004		
2U3 KA431A		Ref Voltage	2D9	UF4007		
Fuse			2D10	SB360		
F1	1.5A	250VAC		NTC		
	Transforme	r	Кеу	5D-11		
2T1	EE25					

Table 2. Part List




5. Test Result

5.1 Start Up

Vin (AC)	Time (S)		
85V	1.04		
265V	0.604		



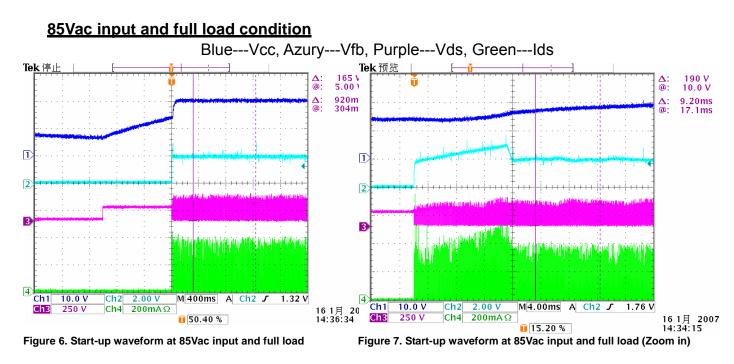

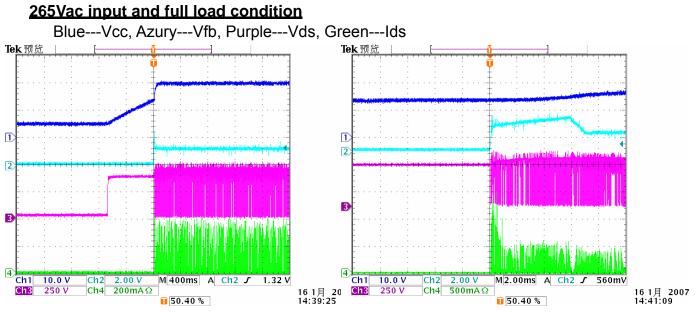


Figure 8. Start-up waveform at 265Vac input and full load

Figure 9. Start-up waveform at 265Vac input and full load (Zoom in)

⁻ Page 10 of 17

FAIRCHILD SEMICONDUCTOR

5.2 Normal Operation

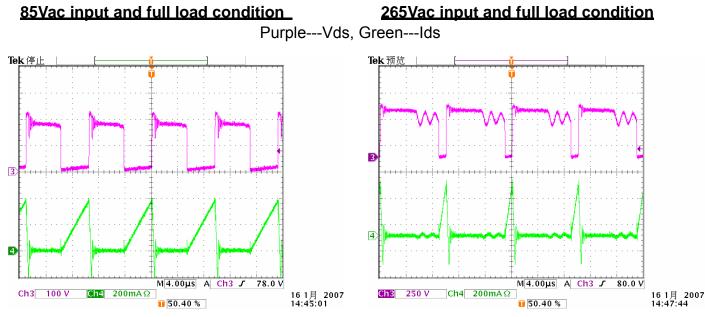



Figure 10. Normal operation waveform at 85Vac input and full load

Figure 11. Normal operation waveform at 265Vac input and full load

5.3 Power Off Waveform

85Vac input and full load condition

265Vac input and full load condition

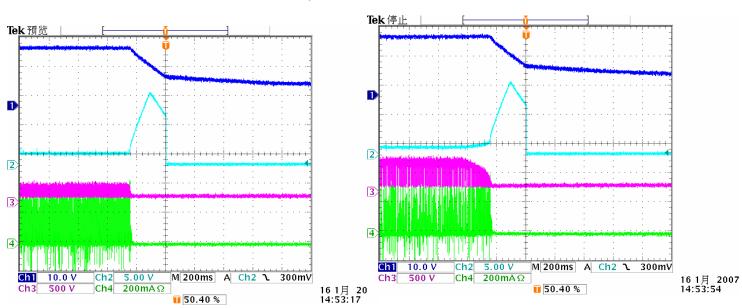

Purple---Vds, Green---Ids

Figure 12. Power off waveform at 85Vac input and full load

Figure 13. Power off waveform at 265Vac input and full load

5.4 Output Short Protection

Vin (AC)	3.3V/2A	21V/1A		
85V	Pass	Pass		
265V	Pass	Pass		

Table 6. Output Short Test

3.3V output short at 85Vac input voltage condition

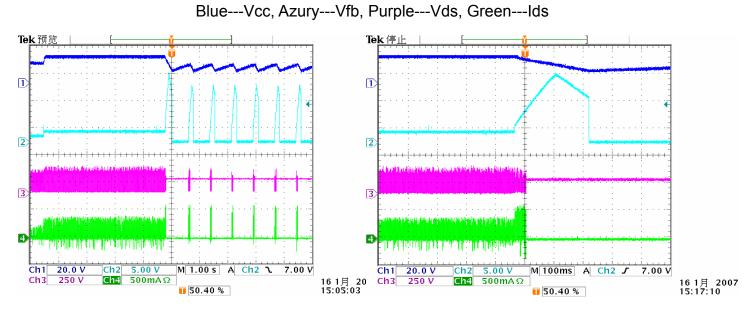


Figure 14. 3.3V output short at 85Vac input voltage condition

Figure 15. 3.3V output short at 85Vac input voltage condition (Zoom in)

21V output short at 85Vac input voltage condition Blue---Vcc, Azury---Vfb, Purple---Vds, Green---Ids Te<u>k</u>停」 Tek预》 Te<u>k</u>停止 1 1 2 2 3 3 4 4 7.00 V 7.00 V Ch1 Ch2 5.00 M 1.00 s Α Ch2 ٦ A Ch2 J Ch1 20.0 \ Ch2 5.00 V M 100ms Ch4 500mAΩ 16 1月 20 15:05:03 500mA Ω Ch3 250 V 250 V Ch4 16 1月 2007 15:17:10 Ch3 **1** 50.40 % 50.40 % Figure 16. 21V output short at 85Vac input voltage condition Figure 17. 21V output short at 85Vac input voltage condition (Zoom in)

- Page 12 of 17

FAIRCHILD

SEMICONDUCTOR

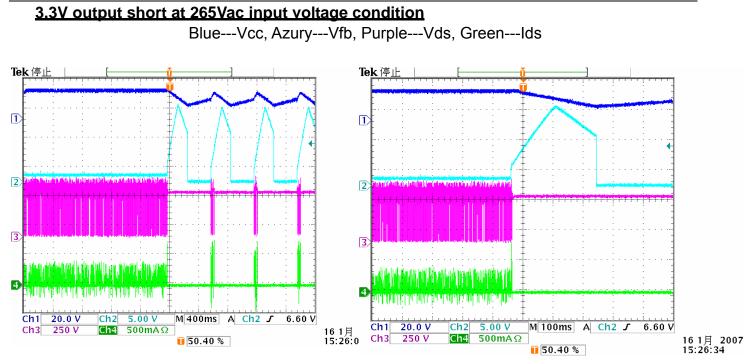


Figure 18. 3.3V output short at 265Vac input voltage condition Figure 19. 3.3V output short at 265Vac input voltage condition (Zoom in)

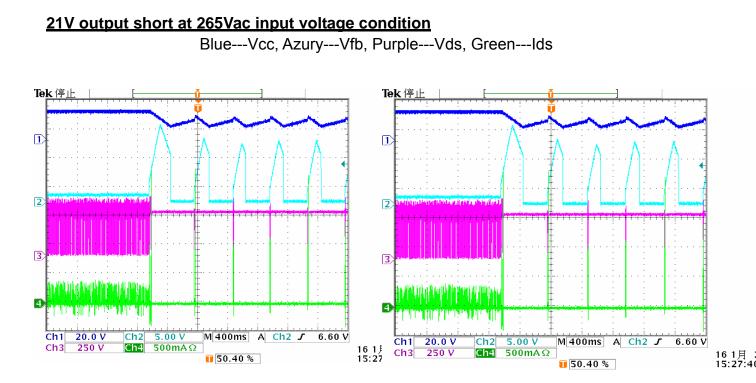


Figure 20. 21V output short at 265Vac input voltage condition


Figure 21. 21V output short at 265Vac input voltage condition (Zoom in)

5.5 Feed Back Circuit Open

FAIRCHILD SEMICONDUCTOR

Feed back open at 85Vac input voltage condition

Blue---Vcc, Azury---Vfb, Purple---Vds, Green---Ids

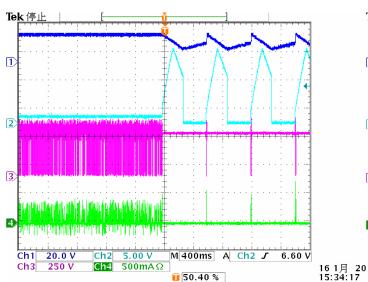

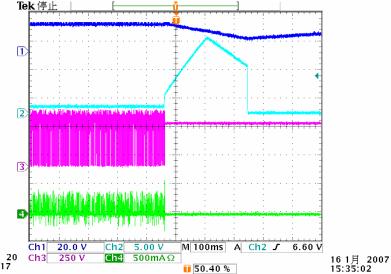


Figure 22. Feed back open at 85Vac input voltage condition

Figure 23. Feed back open at 85Vac input voltage condition (Zoom in)

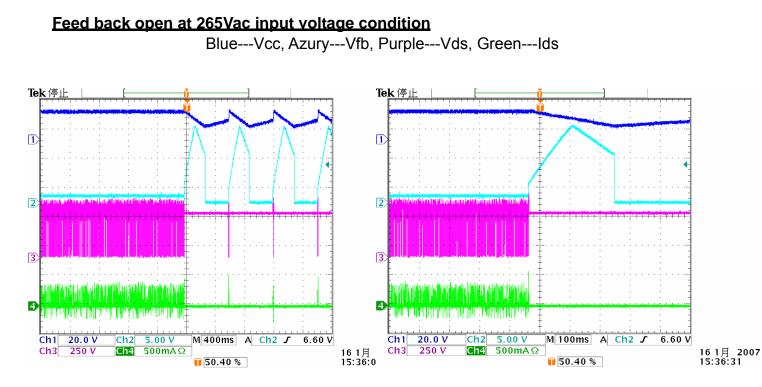


Figure 24. Feed back open at 265Vac input voltage condition

Figure 25. Feed back open at 265Vac input voltage condition (Zoom in)


5.6 Burst Operation

FAIRCHILD

SEMICONDUCTOR

Burst Operation at 85Vac Input Voltage condition

Blue---Vcc, Azury---Vfb, Purple---Vds, Green---Ids

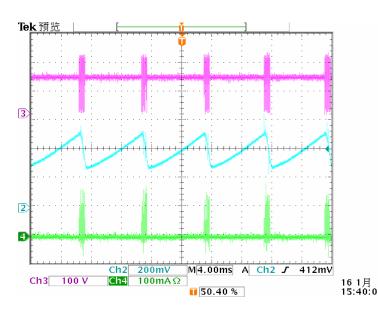

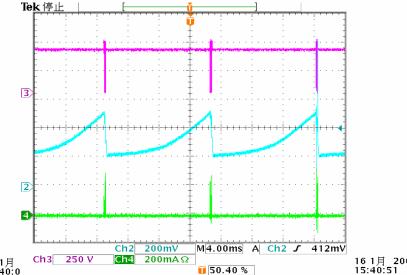


Figure 26. Burst Operation at 85Vac Input Voltage condition

Figure 27. Burst Operation at 265Vac Input Voltage condition



6. Efficiency and Output Voltage Test Result

	3.3V Output		21V Output			Davit	Dim		
Vin	Vout (V)	lout (A)	Tolerance	Vout (V)	lout (A)	Tolerance	Pout (W)	Pin (W)	Efficicency
	3.33	0.20	0.91%	20.65	0.10	-1.67%	2.73	3.70	73.81%
85Vac	3.30	0.60	0.00%	21.26	0.10	1.24%	4.11	5.50	74.65%
	3.27	1.00	-0.91%	21.46	0.15	2.19%	6.49	8.70	74.59%
						·			
	3.33	0.20	0.91%	20.62	0.10	-1.81%	2.73	3.80	71.79%
110Vac	3.30	0.60	0.00%	21.26	0.10	1.24%	4.11	5.60	73.32%
-	3.27	1.00	-0.91%	21.43	0.15	2.05%	6.48	8.70	74.53%
	3.33	0.20	0.91%	20.61	0.10	-1.86%	2.73	3.90	69.92%
150Vac	3.30	0.60	0.00%	21.27	0.10	1.29%	4.11	5.70	72.05%
	3.27	1.00	-0.91%	21.41	0.15	1.95%	6.48	8.70	74.50%
	3.33	0.20	0.91%	20.59	0.10	-1.95%	2.73	4.00	68.13%
180Vac	3.30	0.60	0.00%	21.27	0.10	1.29%	4.11	5.80	70.81%
-	3.27	1.00	-0.91%	21.41	0.15	1.95%	6.48	8.80	73.65%
	3.33	0.20	0.91%	20.59	0.10	-1.95%	2.73	4.10	66.46%
220Vac	3.30	0.60	0.00%	21.28	0.10	1.33%	4.11	6.00	68.47%
	3.27	1.00	-0.91%	21.40	0.15	1.90%	6.48	8.90	72.81%
	3.33	0.20	0.91%	20.59	0.10	-1.95%	2.73	4.20	64.88%
240Vac	3.30	0.60	0.00%	21.29	0.10	1.38%	4.11	6.10	67.36%
	3.27	1.00	-0.91%	21.39	0.15	1.86%	6.48	9.00	71.98%
	3.33	0.20	0.91%	20.67	0.10	-1.57%	2.73	4.30	63.56%
265Vac	3.30	0.60	0.00%	21.31	0.10	1.48%	4.11	6.30	65.25%
	3.27	1.00	-0.91%	21.39	0.15	1.86%	6.48	9.20	70.42%

Table 7. Output Voltage and Efficiency Test

7. Reference and Resource

7.1 Application Notes

Application note:

Flyback: <u>AN-4137</u>, <u>AN-4141</u>, <u>AN-4147</u>



8 Warning and Disclaimer

This Evaluation Board may employ high voltages so appropriate safety precautions should be used when operating this board. Replace components on the Evaluation Board only with those parts shown on the parts list in the User's Guide. Contact an authorized Fairchild representative with any questions.

The Evaluation Board is for demonstration purposes only and neither the Board nor this User's Guide constitute a sales contract or create any kind of warranty, whether express or implied, as to the applications or products involved. Fairchild warranties that its products will meet Fairchild's published specifications but does not guarantee that its products will work in any specific application. Fairchild reserves the right to make changes without notice to any products described herein to improve reliability, function or design. Either the applicable sales contract signed by Fairchild and Buyer, or if no contract exists Fairchild's Standard Terms and Conditions on the back of Fairchild invoices, govern the terms of sale of the products described herein.