

An Overview of Forward Converter with Various Reset Schemes

By

Gary Hua

9/20/07

Features of Forward Converter

- **One of fundamental topologies**
- **Most commonly used topology**
- **Applicable power level from a few Watts to a couple of Kilo-Watts**
- **Appears simple but difficult to optimize design**
- **Where are you on skill 1-10?**


Test

- 1. How does the B-H curve in the 3rd winding reset forward converter look?**
- 2. Which secondary diode is subject to higher switching loss?**
- 3. Can the resonant reset forward converter operate with ZVS?**
- 4. Can two-switch forward converter operate at greater than 50% duty cycle?**
- 5. Does the clamp diode in active-clamp forward converter suffer from reverse-recovery problem?**

Variations of Forward Topology


- **Third Winding Reset Forward**
- **Zener Clamp Forward**
- **R-C-D Clamp Forward**
- **Active Clamp Forward**
- **Resonant Reset Forward**
- **Two Switch Forward**
- **ZCS Quasi-Resonant Forward**
- **ZVS Quasi-Resonant Forward**
- **ZVS Multi-Resonant Forward**
- **ZVT Forward**
- **.....**

Third Winding Reset Forward

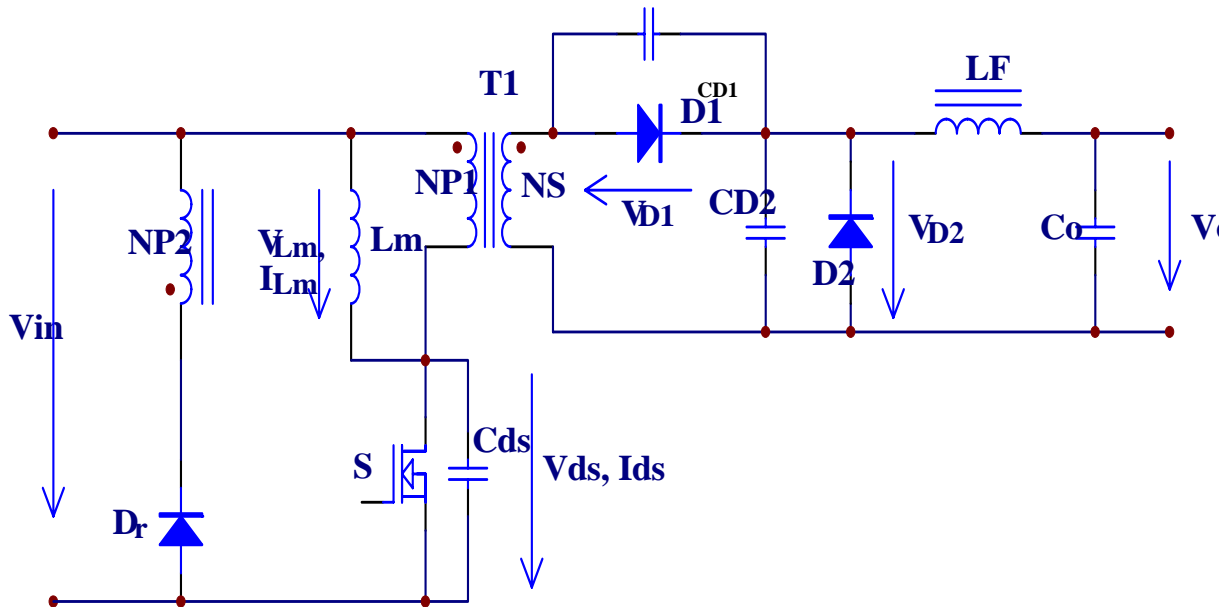


- How does B-H curve look?


Operating Stage A

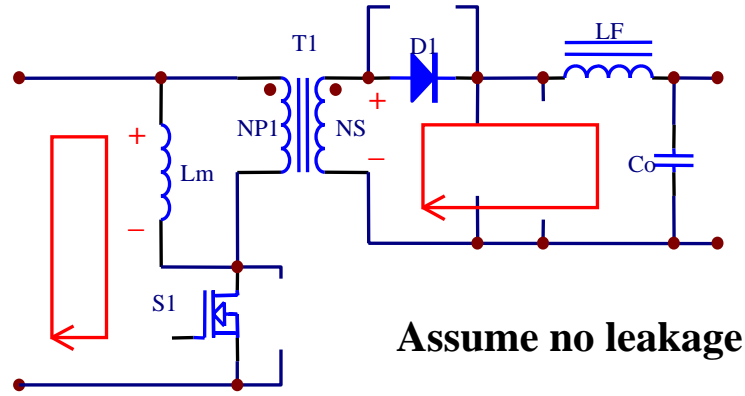

A

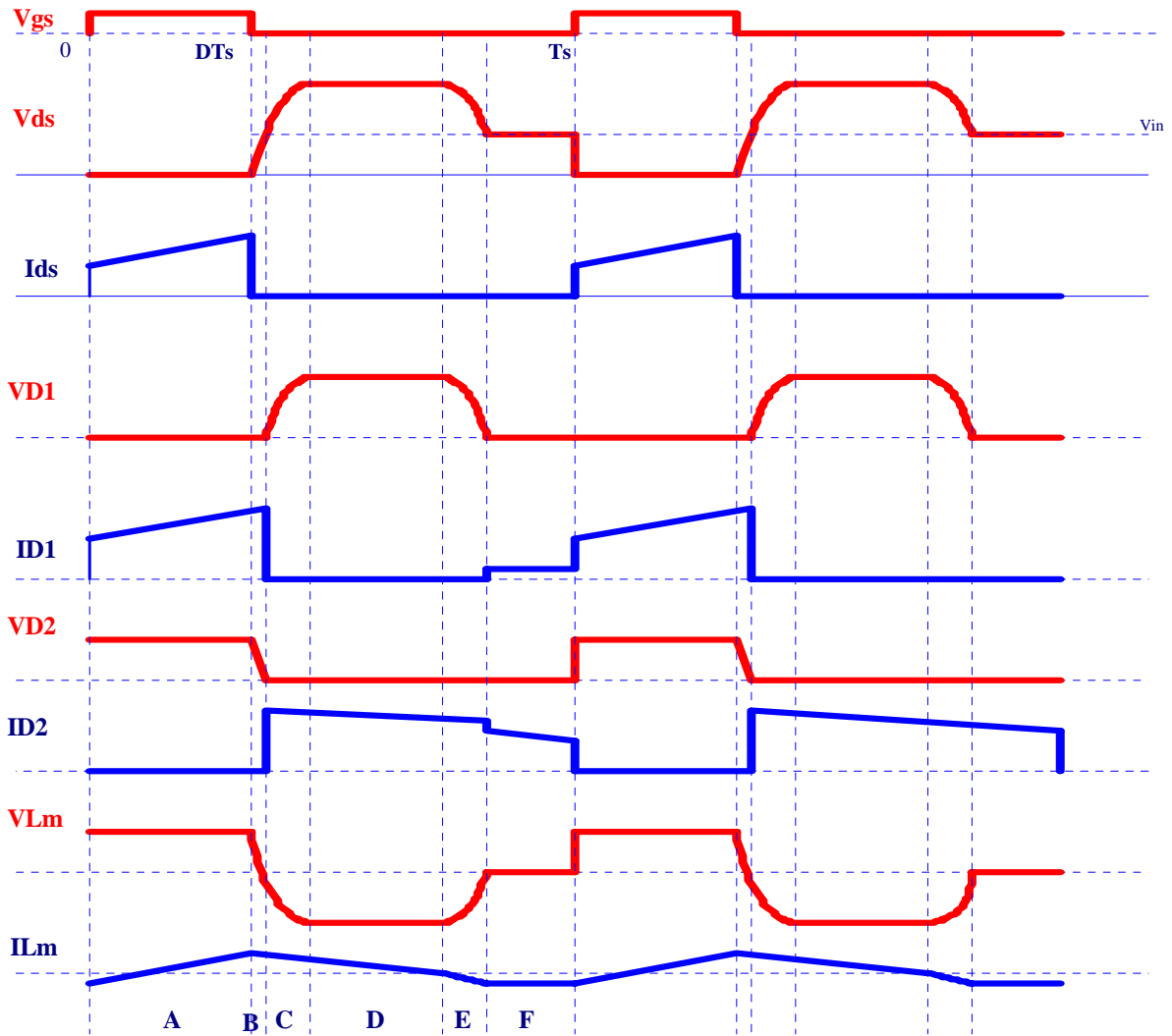


Operating Stage B


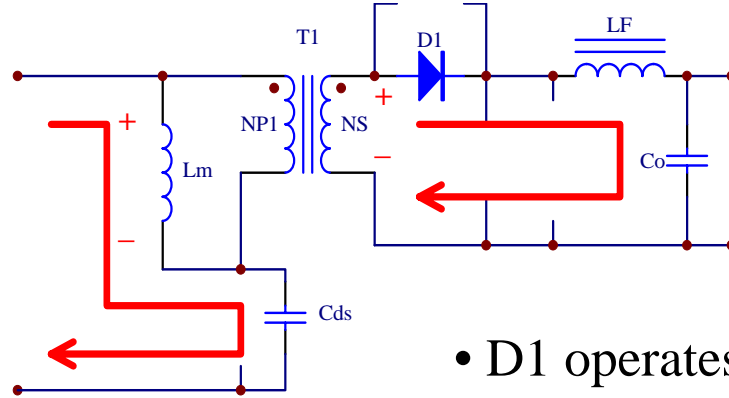


- D1 operates with ZVS



B

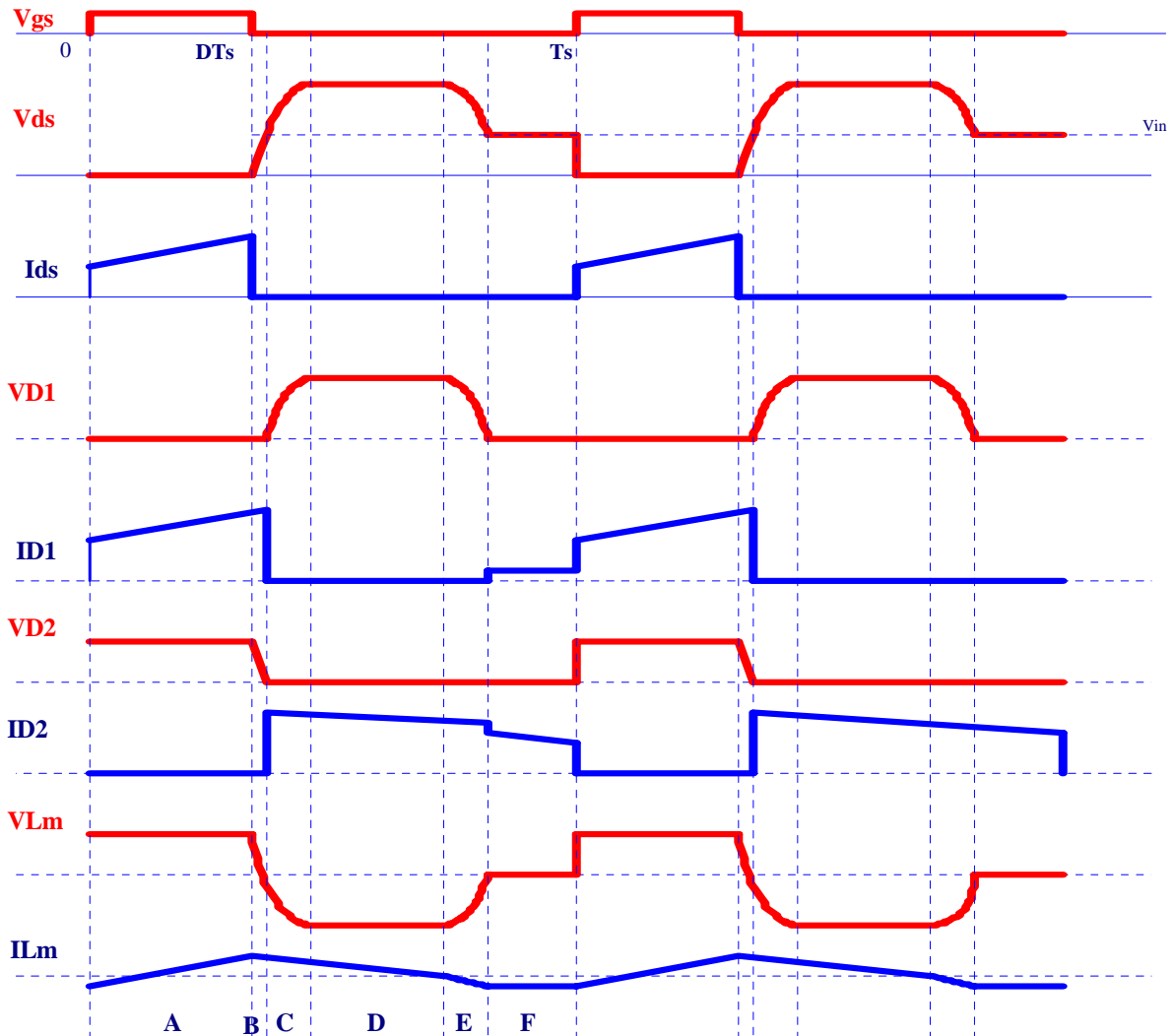



Operating Stage C

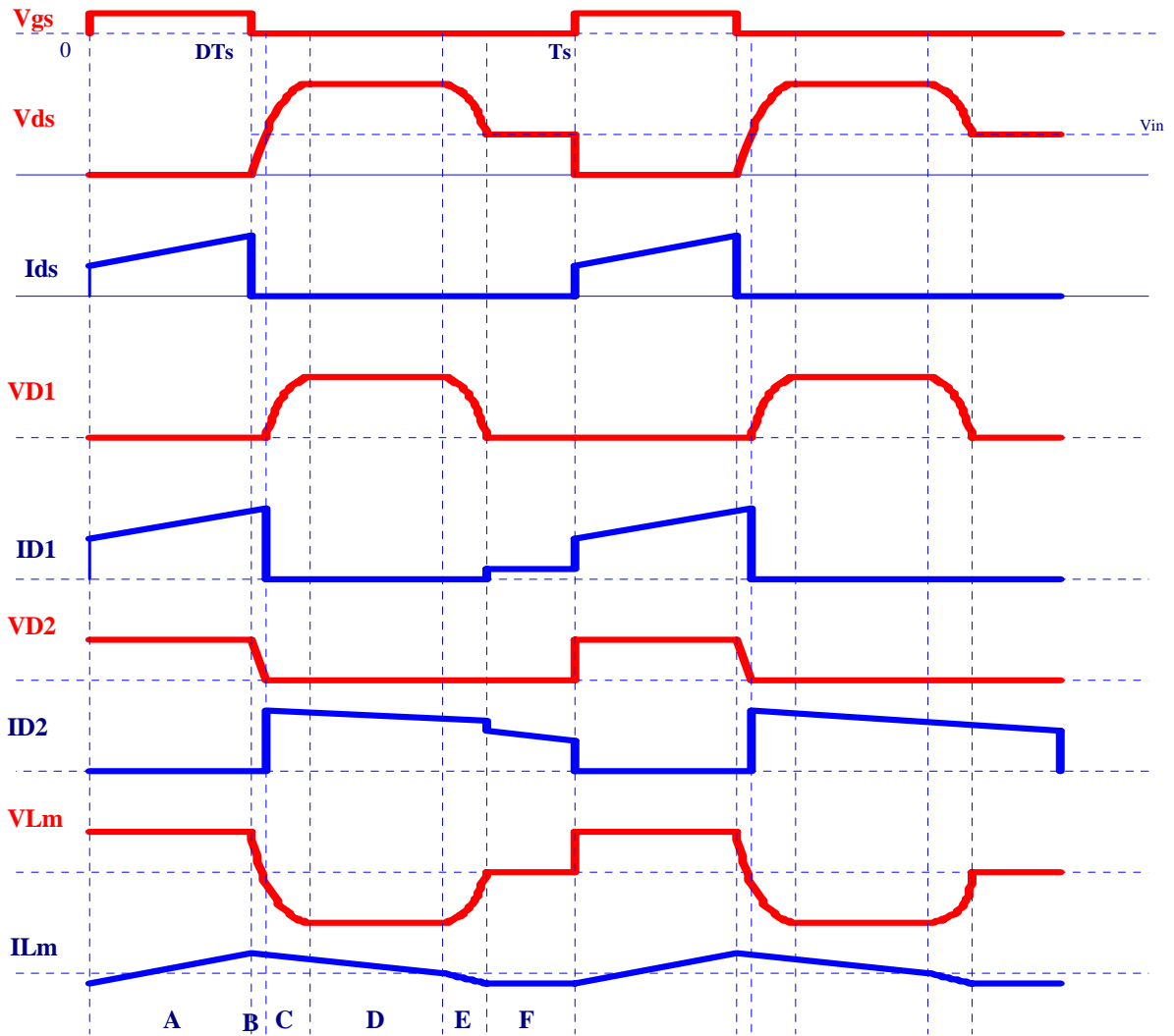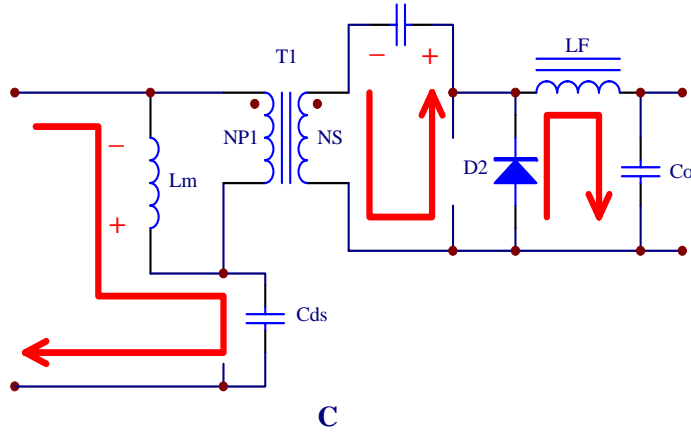



Operating Stage D

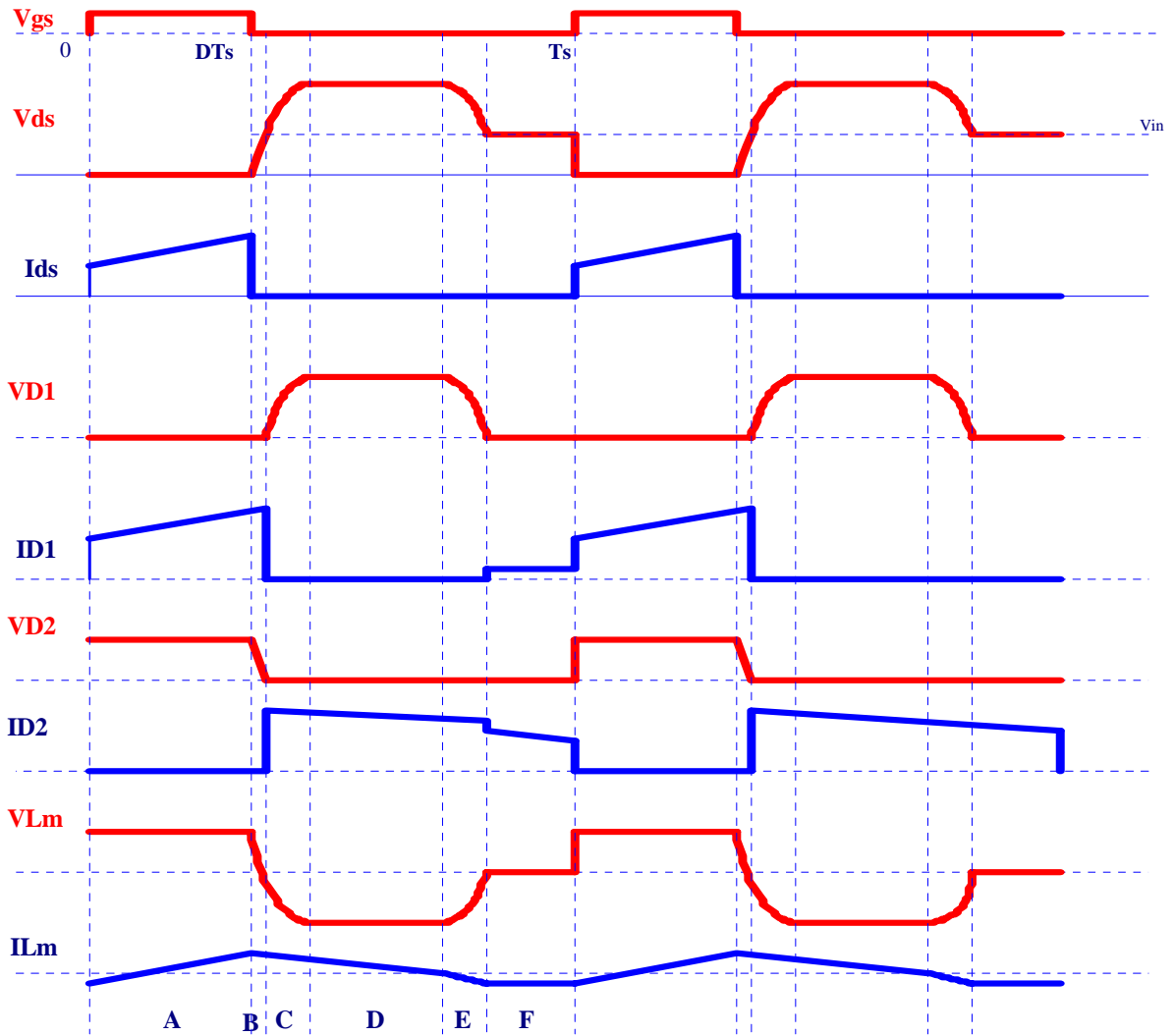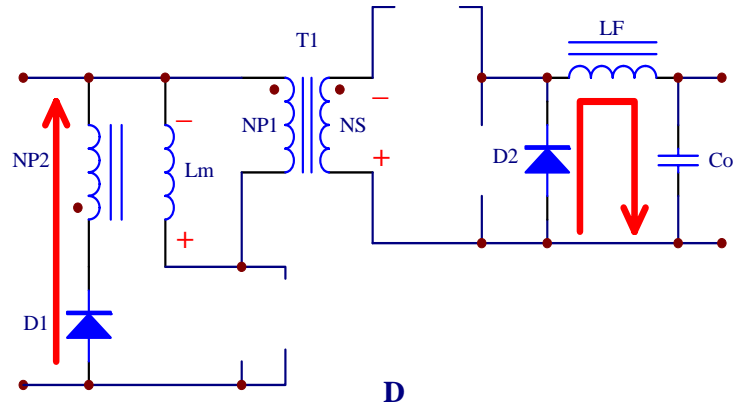

Operating Stage E

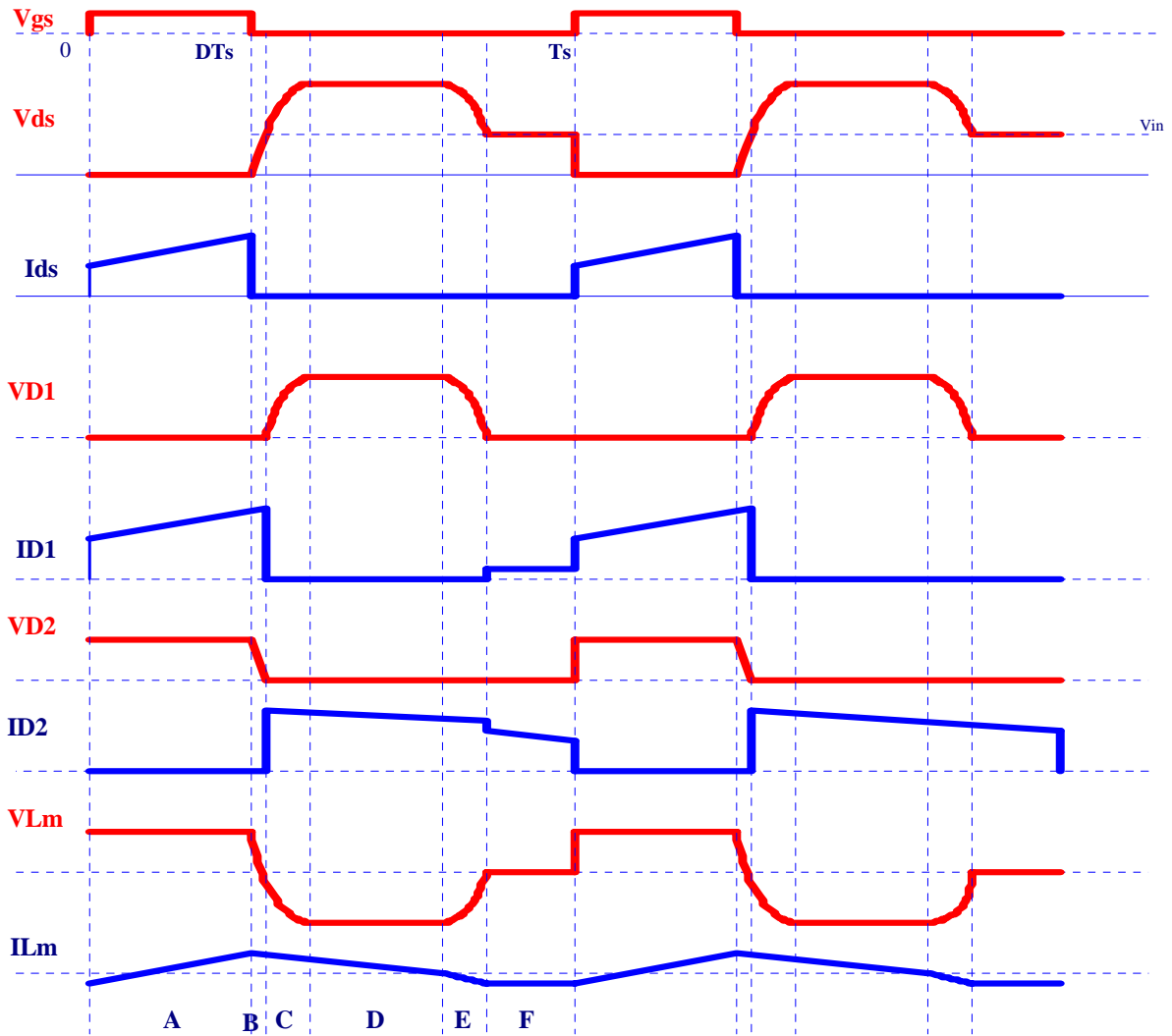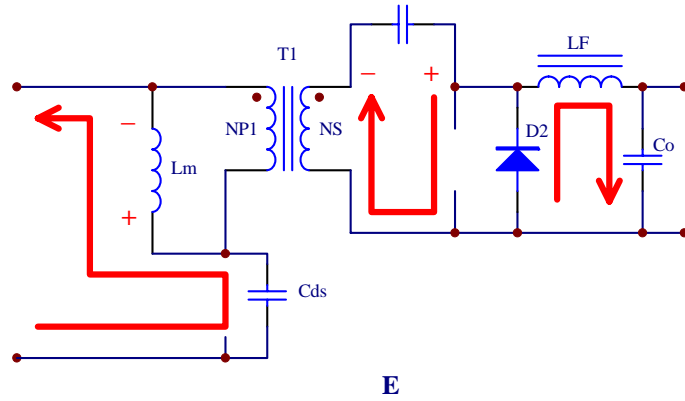

Operating Stage F

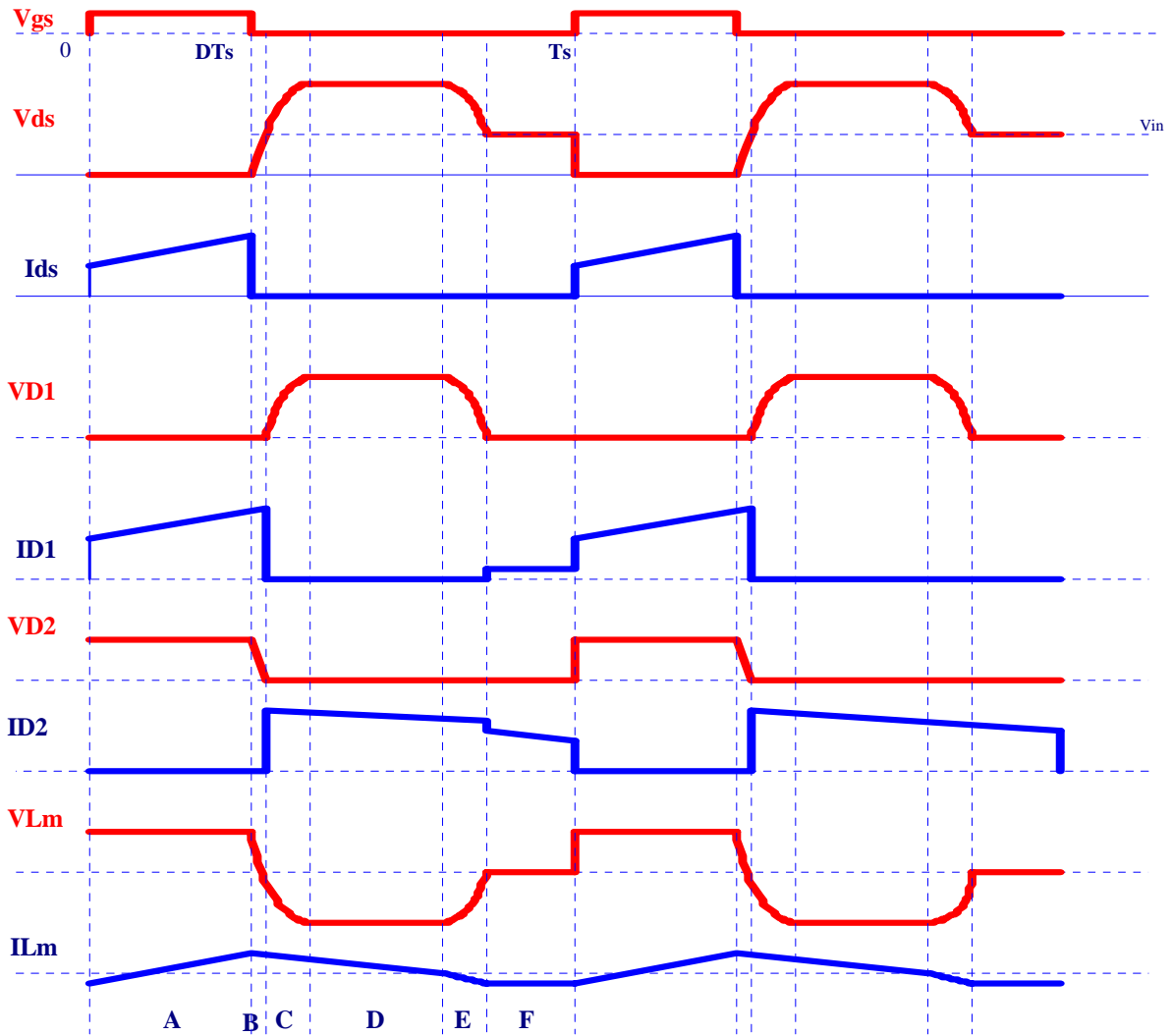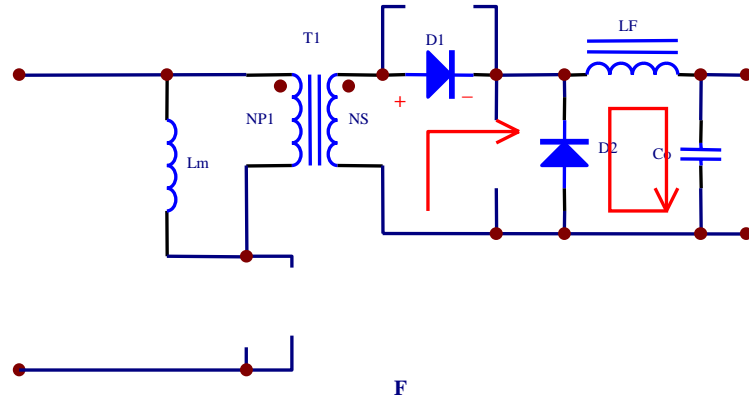

Third Winding Reset Forward

Advantages:

- Magnetizing energy recycled
- Part of TR leakage energy recycled
- Very reliable reset, no switch voltage overshoot during transient


Drawbacks:

- Third winding complicates TR design
- Max Duty cycle limited to about 40%
if $N_{p2}=N_{p1}$
- Clamp voltage proportional to V_{in}

Key Design Considerations

- **Extend maximum duty cycle to**
 - Reduce primary (S, TR) current stress
 - Reduce D2 voltage stress
 - Reduce output filter size
 - Reduce input filter size
 - Improve efficiency
- **Minimize leakage inductance between Np1 and Np2**
- **CD1 does not introduce switching loss**
- **How to extend max duty cycle and what are limitations?**

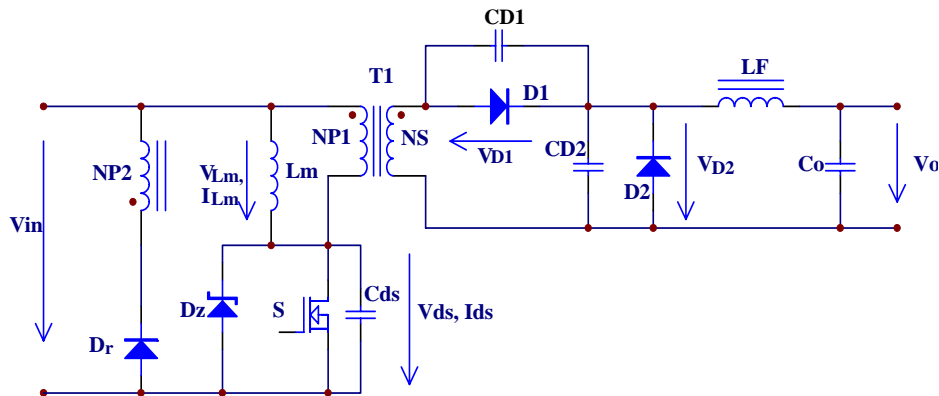Variation (2) of Third Winding Reset Forward




Advantages:

- Maximum switch voltage clamped by Zener diode
- Max duty cycle can be extended without increasing switch voltage stress

Drawbacks:

- Part of magnetizing energy dissipated in Dz at high line

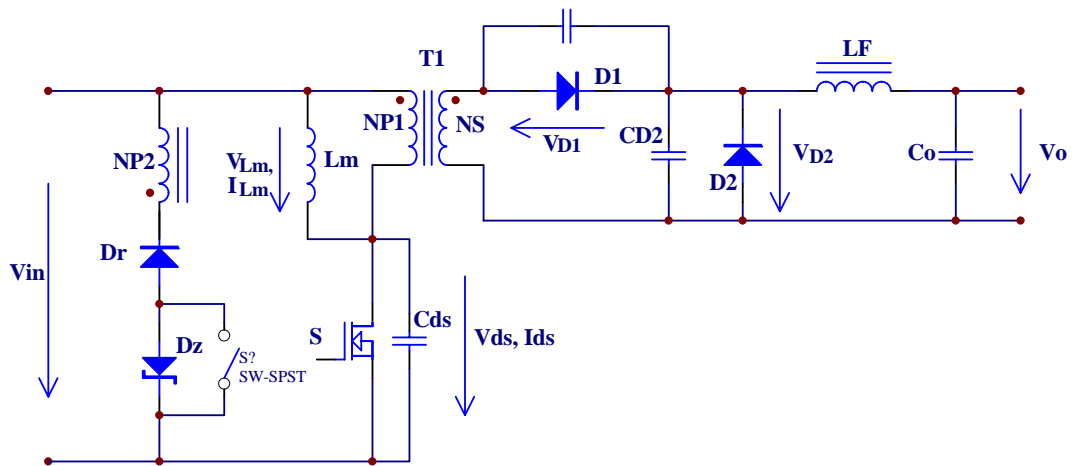Variation (3) of Third Winding Reset Forward





Advantages:

- Reset voltage increased at low line
- Max switch voltage remain unchanged

Drawbacks:

- Some magnetizing energy dissipated in D_z at low line

Zener Clamp Forward

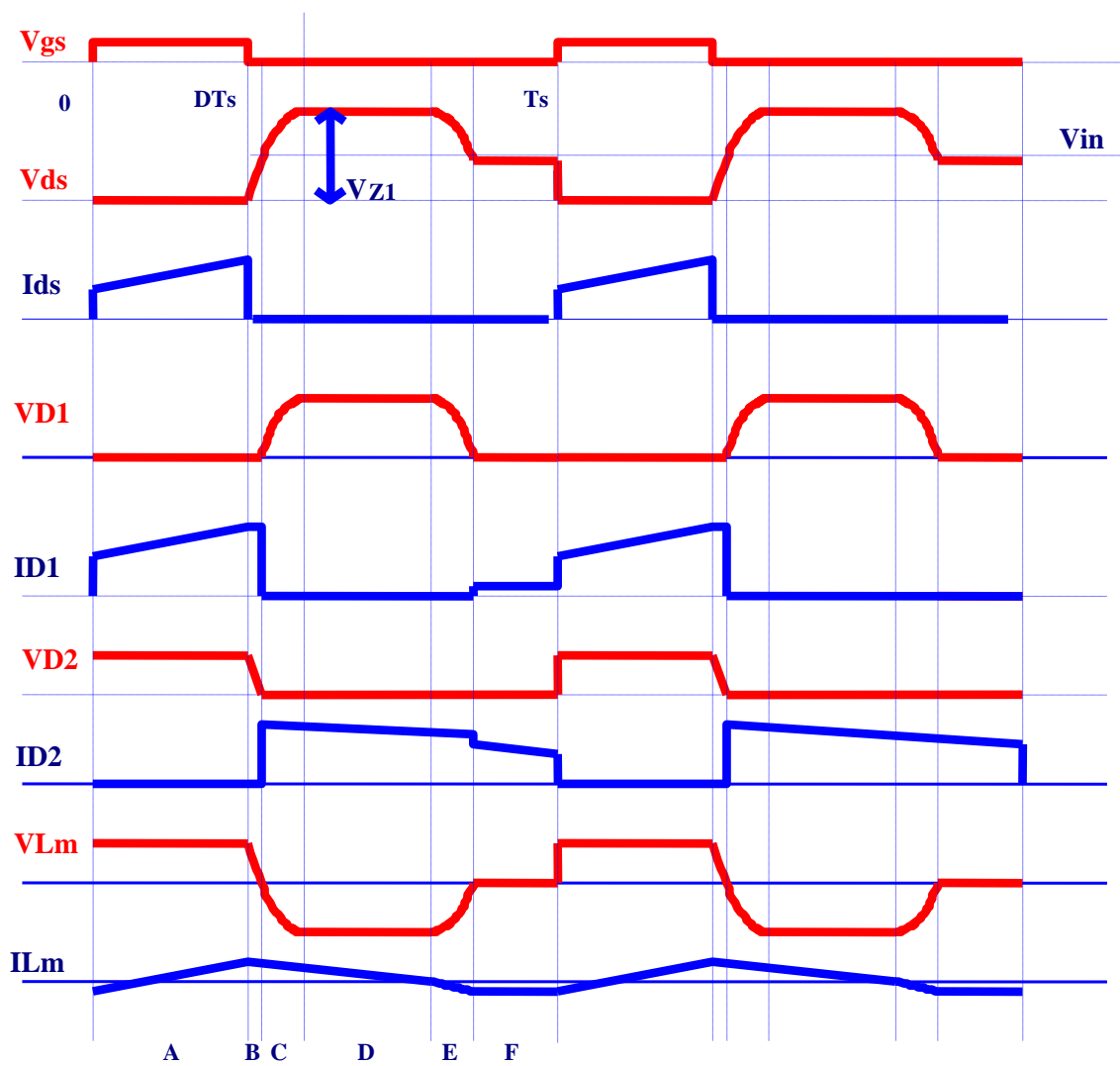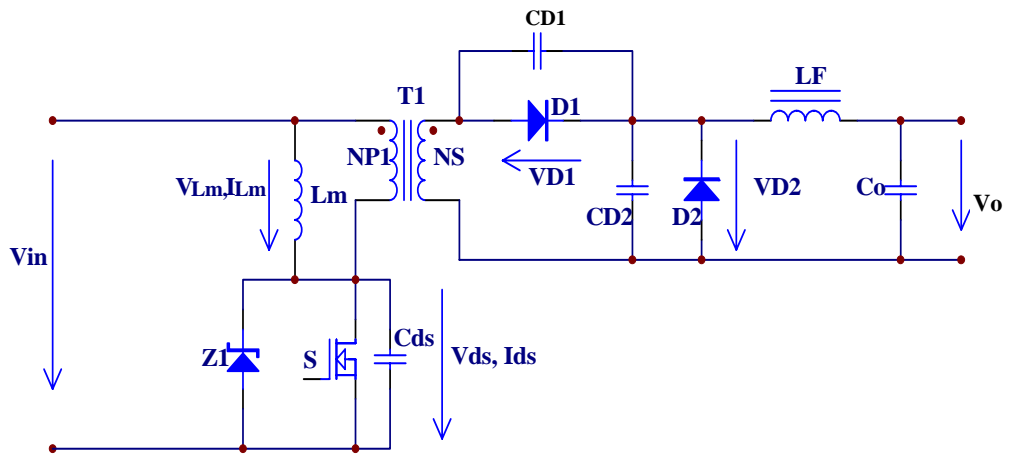

Zener Clamp Forward


Advantages:

- Simple
- Maximum switch voltage independent of line voltage
- Max duty cycle can exceed 50%
- Reliable

Drawbacks:

- Part of magnetizing and leakage energy dissipated
- High voltage Zener diode can be expensive

Variation (1) of Zener Clamp Forward

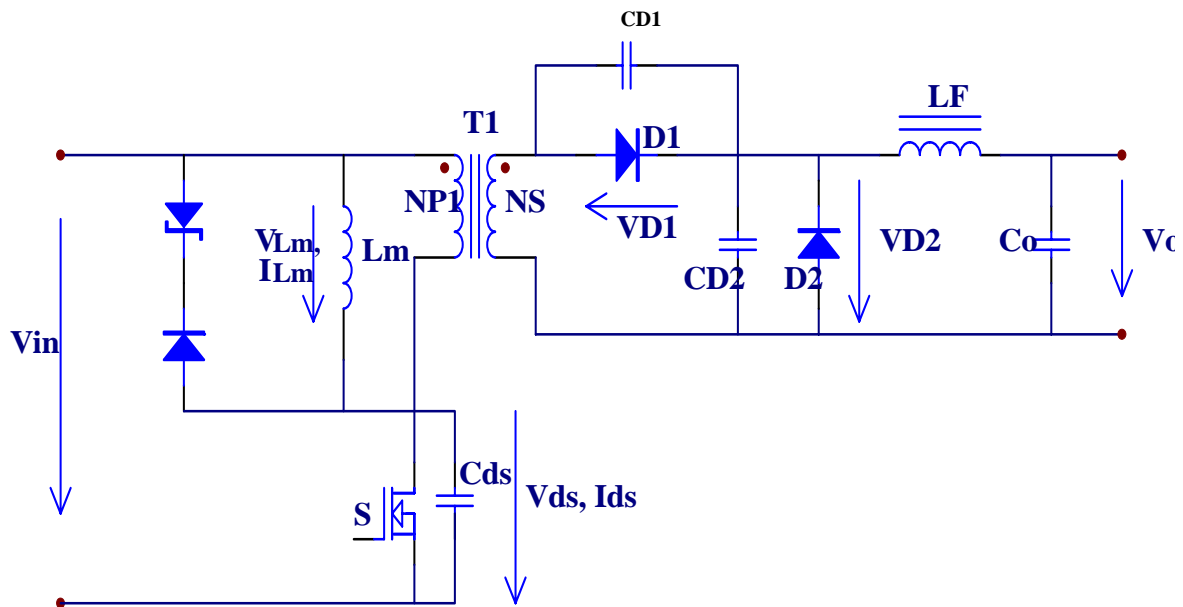

Advantages:

- Less power dissipated in Zener diode

Drawbacks:

- Switch voltage stress dependent on V_{in}

Variation (2) of Zener Clamp Forward

- Place the Zener diode on the secondary



Advantages:

- Can use low voltage Zener diode

Drawbacks:

- Does not clamp primary switch voltage spike induced by transformer leakage

R-C-D Clamp Forward

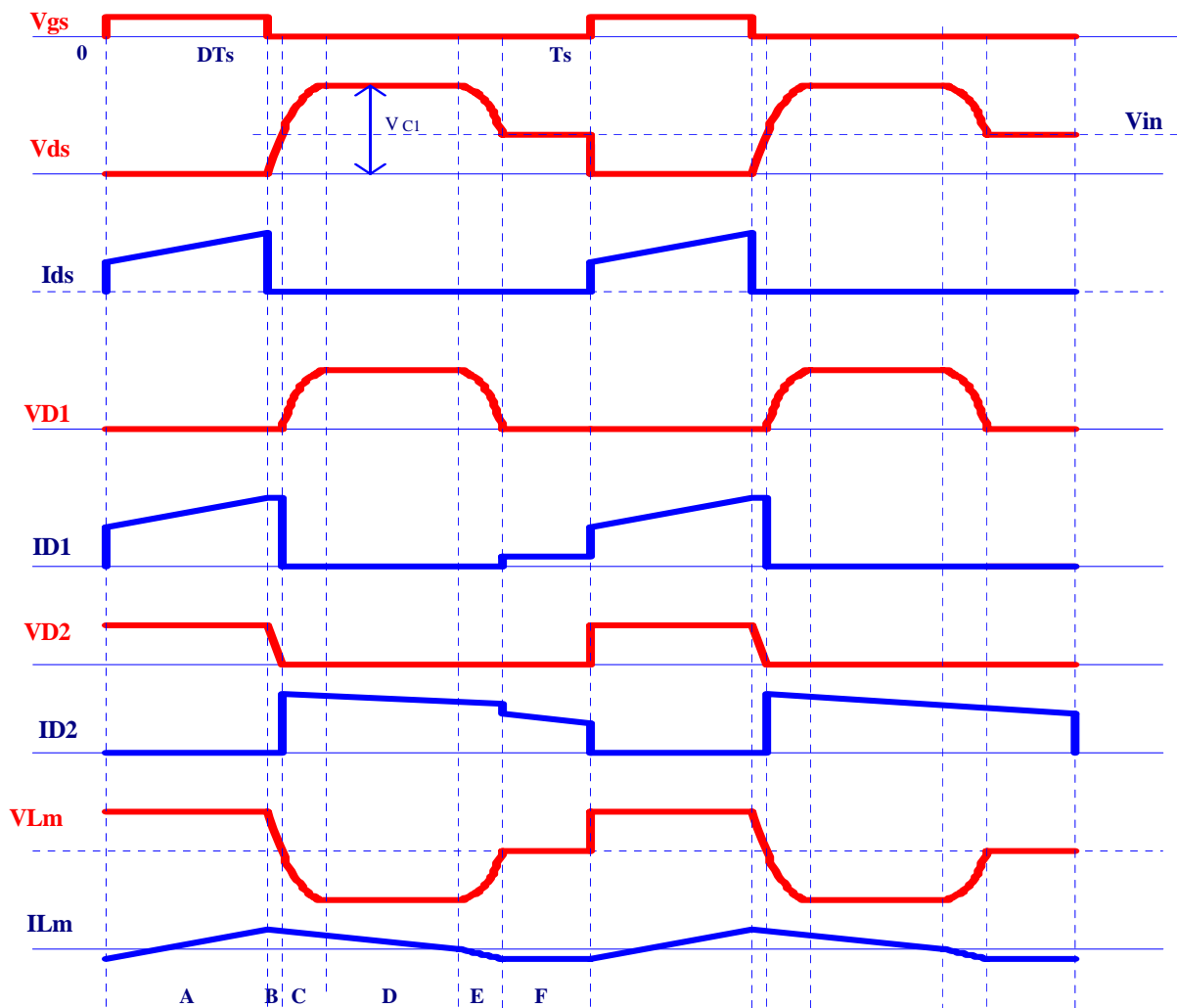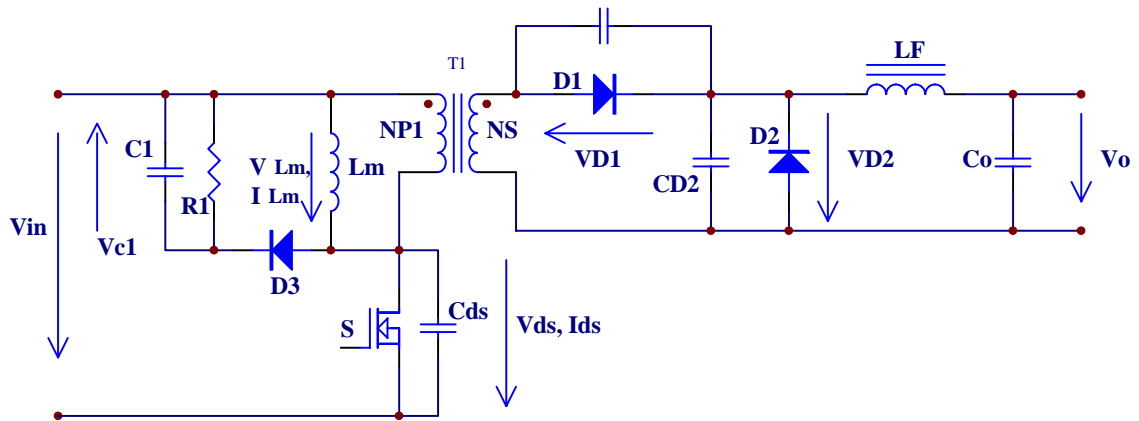

R-C-D Clamp Forward

Advantages:

- Low cost
- Flexible in selecting clamp voltage
- Clamp voltage almost independent of V_{in}



Drawbacks:

- Part of magnetizing and leakage energy dissipated

Key Design Notes

- R can be determined experimentally
- C can be connected to ground to eliminate switch voltage spike caused by parasitic inductance
- RC time constant 3-6 times bigger than switching period
- Use variable R to control switch voltage stress

Active Clamp Forward

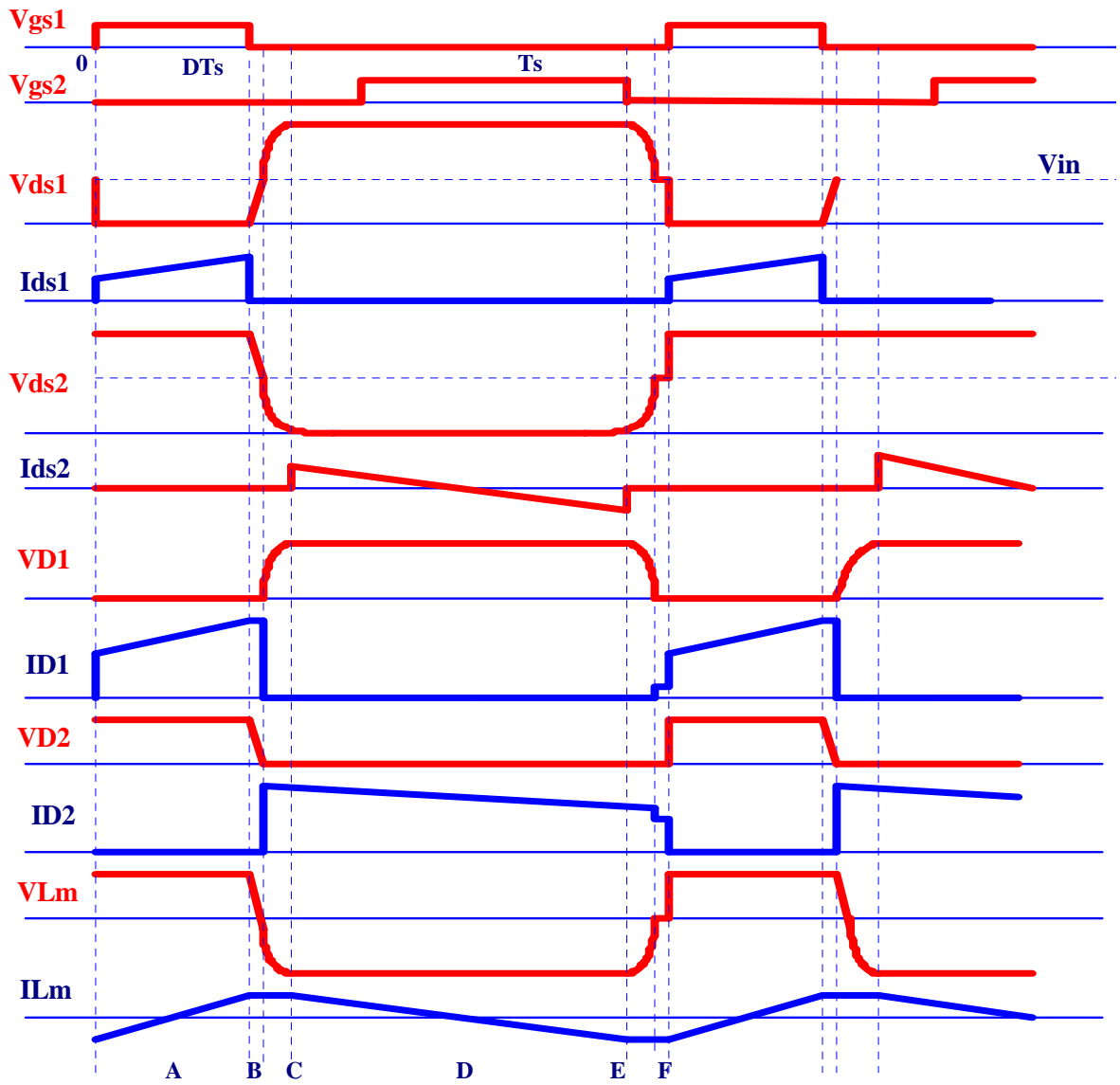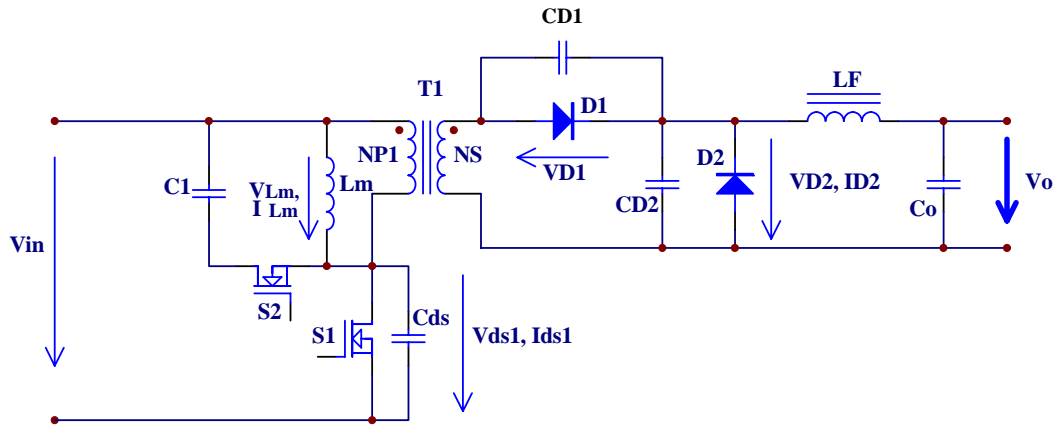

Active Clamp Forward

Advantages:

- Magnetizing and leakage energy recycled completely
- Optimum reset scheme
- Easy to self-drive SRs (major benefit!)
- Easy to implement ZVS

Drawbacks:

- Complicated and expensive
- High switch overshoot during dynamics (startup, line or load step changes, OCP and SCP)
- Patent issue?



Key Design Notes

- Magnetizing inductance is usually low
- C value needs to be selected carefully
- ZVS achieved at expense of increased conduction loss (about 30%)
- Need to watch dynamic behavior carefully
- Clamp switch slow body diode needs to be blocked for high input voltage applications

Variations of Active Clamp Forward

- 1. Use P-channel FET**
- 2. Clamp on secondary side**
- 3. Third winding reset**

Resonant Reset Forward

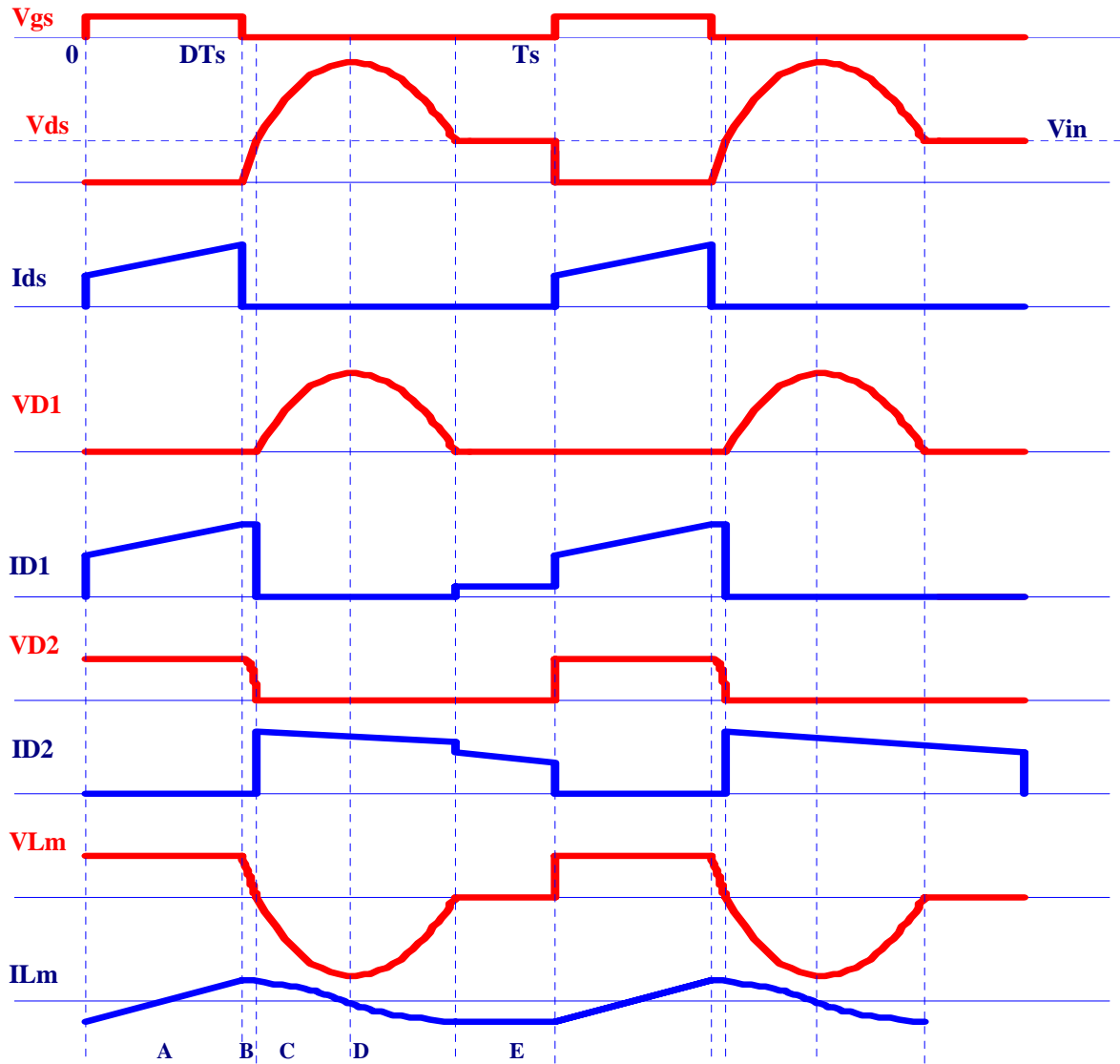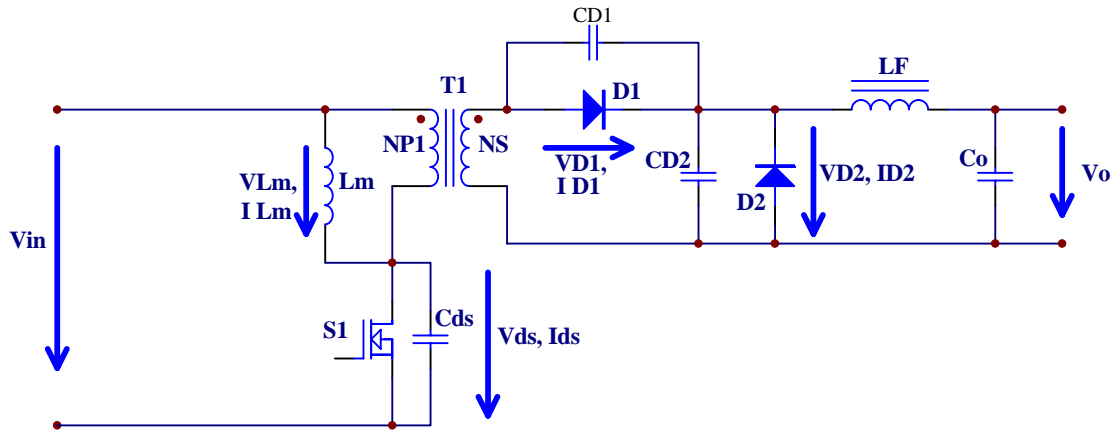

Resonant Reset Forward

Advantages:

- Simple and low cost
- Magnetizing and leakage energy fully recycled
- Easy to extend max duty cycle
- Widely used in wide input range (such as military) applications

Drawbacks:

- Sinusoidal reset waveform has higher peak than square like waveform

Key Design Notes


- **External resonant cap is often needed to reduce peak switch voltage**
- **C can be placed across D1 to avoid excessive capacitive turn on loss**
- **Power switch can be turned on before completion of resonance**
- **How to reduce max switch voltage stress?**

Reducing Switch Voltage Stress (1)



- **Add a zener across power switch (not the transformer)**

Reducing Switch Voltage Stress (2)

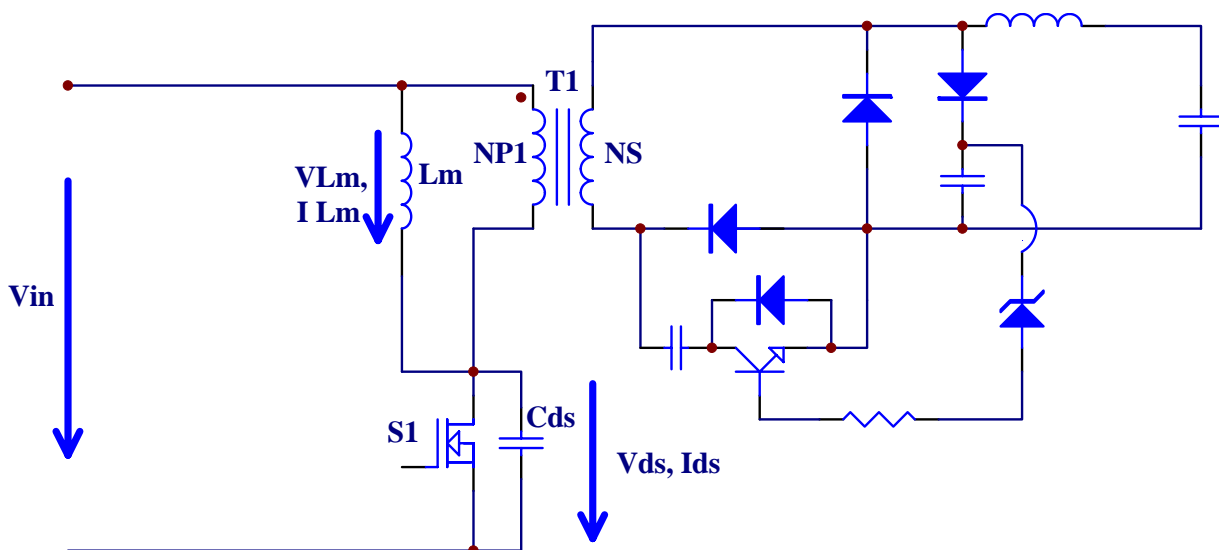- Add an external cap and a switch on secondary



Two Switch Forward

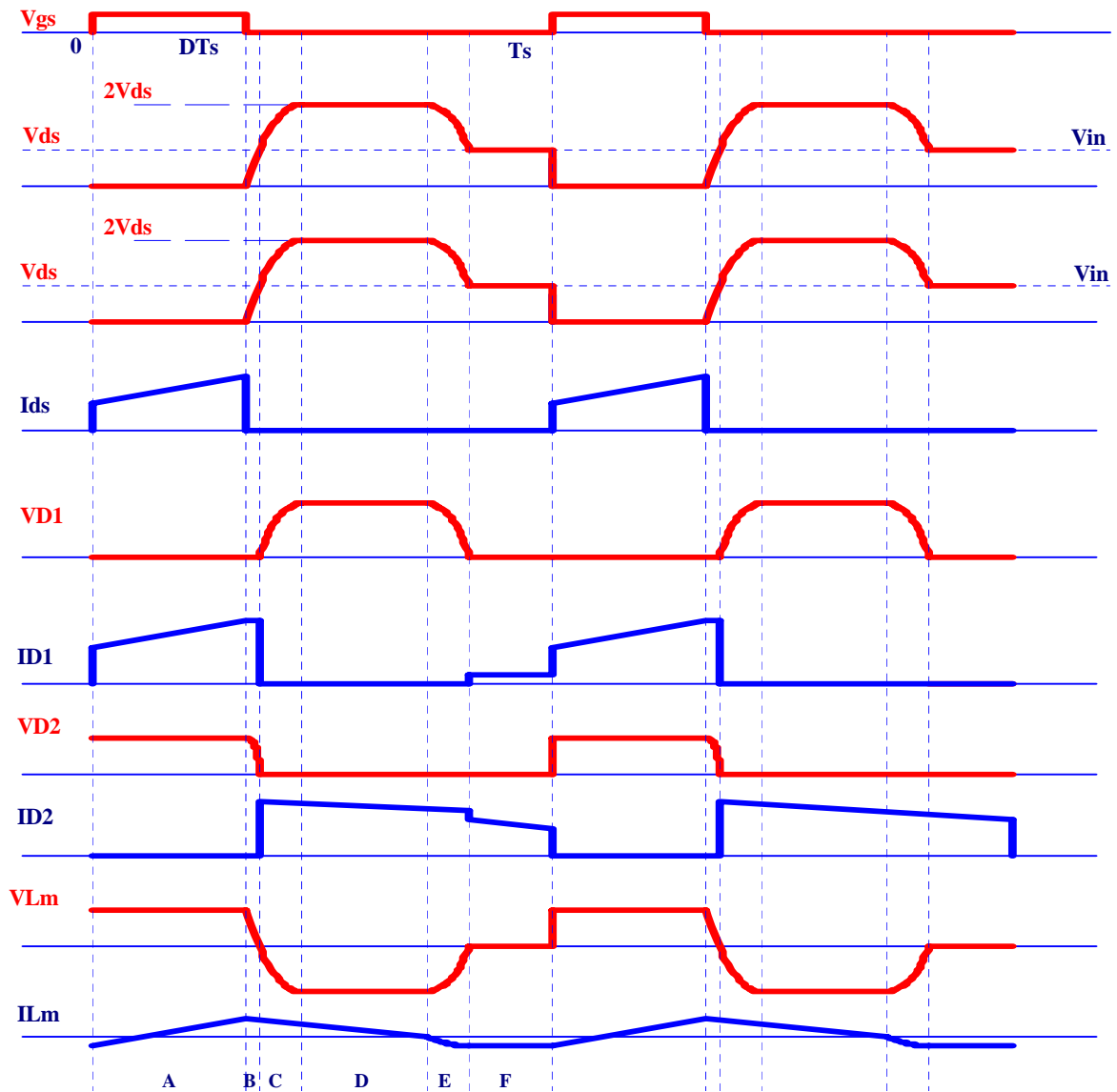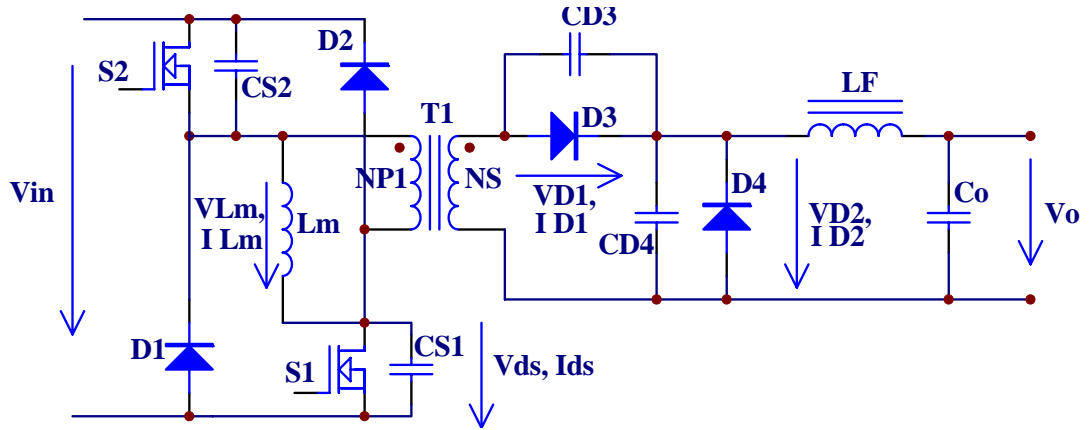

Two Switch Forward


Advantages:

- Low switch voltage stress
- Suited for high power applications
- Very reliable reset
- Magnetizing and leakage energy recycled completely

Drawbacks:

- Needs a second switch with float driving
- Duty cycle limited to about 40%
- How to extend duty cycle?

Variation (1) of 2-Switch Forward

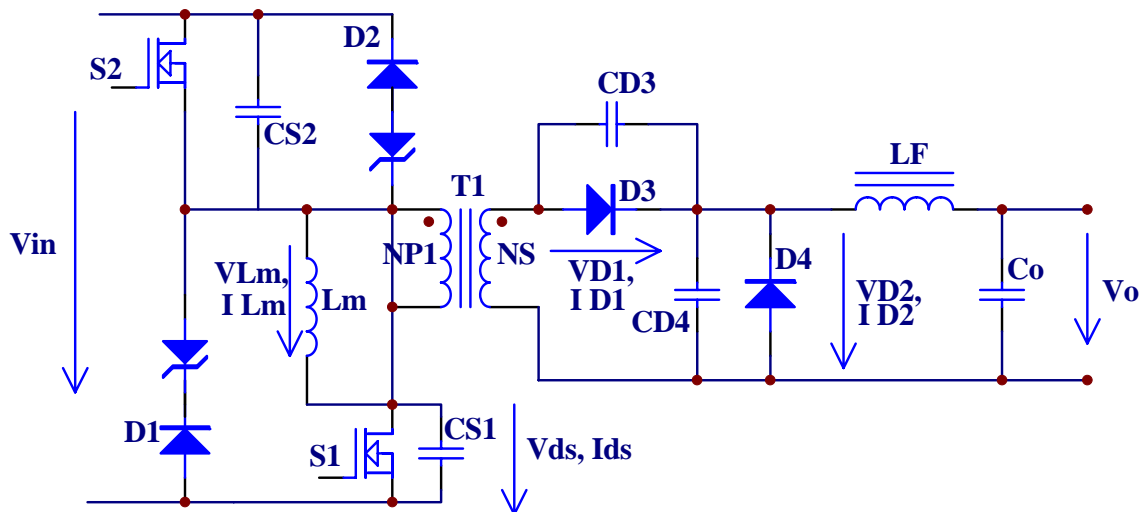

Advantages:

- Duty cycle can exceed 50%
- Simple and low cost

Drawbacks:

- Increases max. switch voltage stress
(which may not be a problem)

