

Application Note – iW3620 Design considerations to select PFC inductor

This application note provides the design considerations for selecting PFC inductor in the LED driver design with iW3620.

Figure 1 shows a universal AC input line LED driver design with power factor correction.

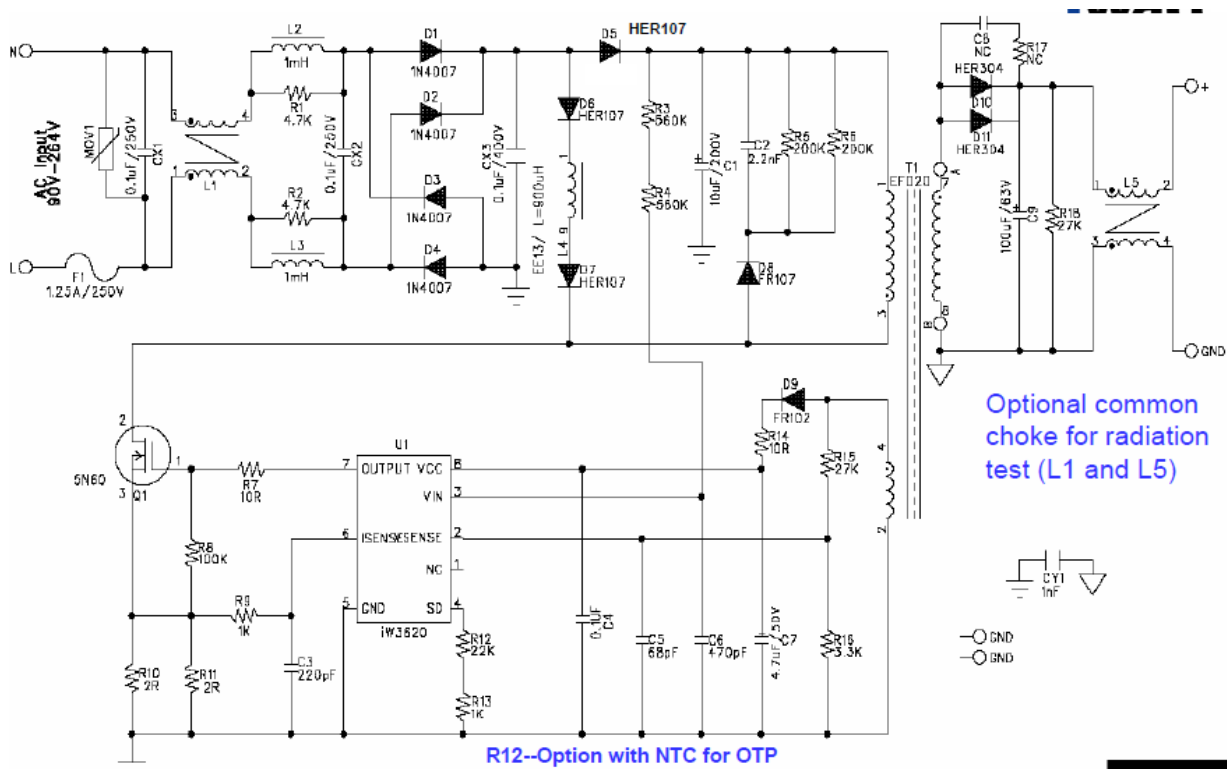


Figure 1 An iW3620 design – 28V/0.5A for universal AC input

1 Considerations for selecting PFC inductor

The PFC inductor is selected based on the following considerations.

1. Support the output loading. The PFC inductor stores energy when MOSFET turns on and releases partial energy to the output loading when MOSFET turns off.
2. Boost the bulk capacitor voltage level V_{bulk} . V_{bulk} has to be limited at the highest input voltage.
3. Meet the power factor requirement. The lower the inductance, the higher the power factor.

4. Meet the efficiency requirement. Higher PFC inductance often leads to higher efficiency because less power is processed through the boost circuit..

Figure 2 shows a simplified schematic.

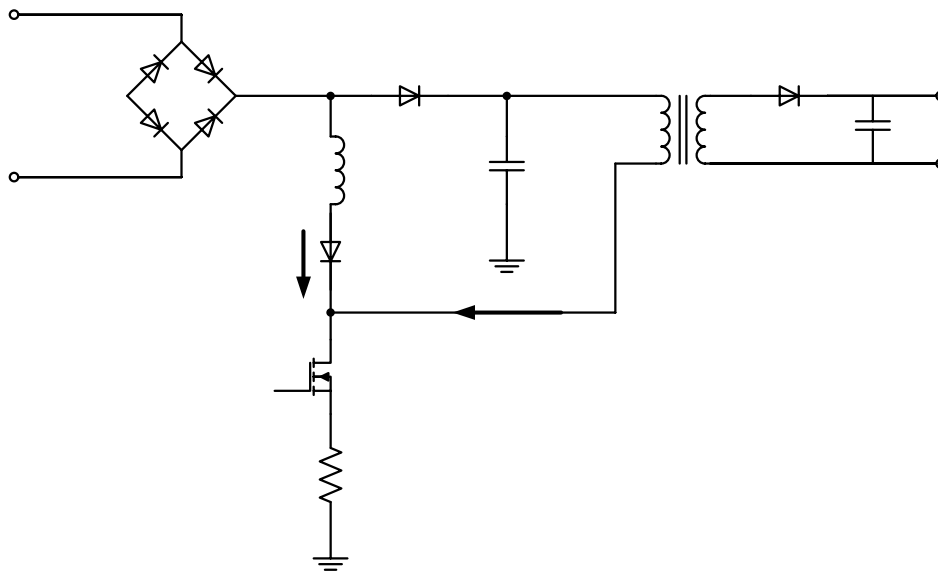


Figure 2 A simplified schematic

V_{in}

$D1$ V_b

V_{ac}

2 PFC inductor operating modes

Figure 3 shows the active operating modes for inductor L_{pfc} .

When MOSFET Q1 turns on, input voltage is applied on L_{pfc} . The inductor current rises with slope V_{in}/L_{pfc} . The transformer T1 primary winding current rises with slope V_{bulk}/L_m .

I_{pfc}

$D2$

When MOSFET Q1 turns off, the inductor current continues flowing through the transformer primary winding N_p . Partial energy is transferred to the secondary side loading. Partial energy is transferred into the bulk capacitor C_{bulk} . The energy in the transformer is transferred to the output loading.

It is noted that Figure 3 does not include the state when both L_{pfc} and L_m having zero current. Figure 3 also assume the V_{bulk} is always higher than V_{in} such that D1 does not conduct in steady state operation. This is usually true when V_{in} is at high line. When V_{in} is at low line, D1 also helps to charge the bulk capacitor.

$Q1$

R_{ss}

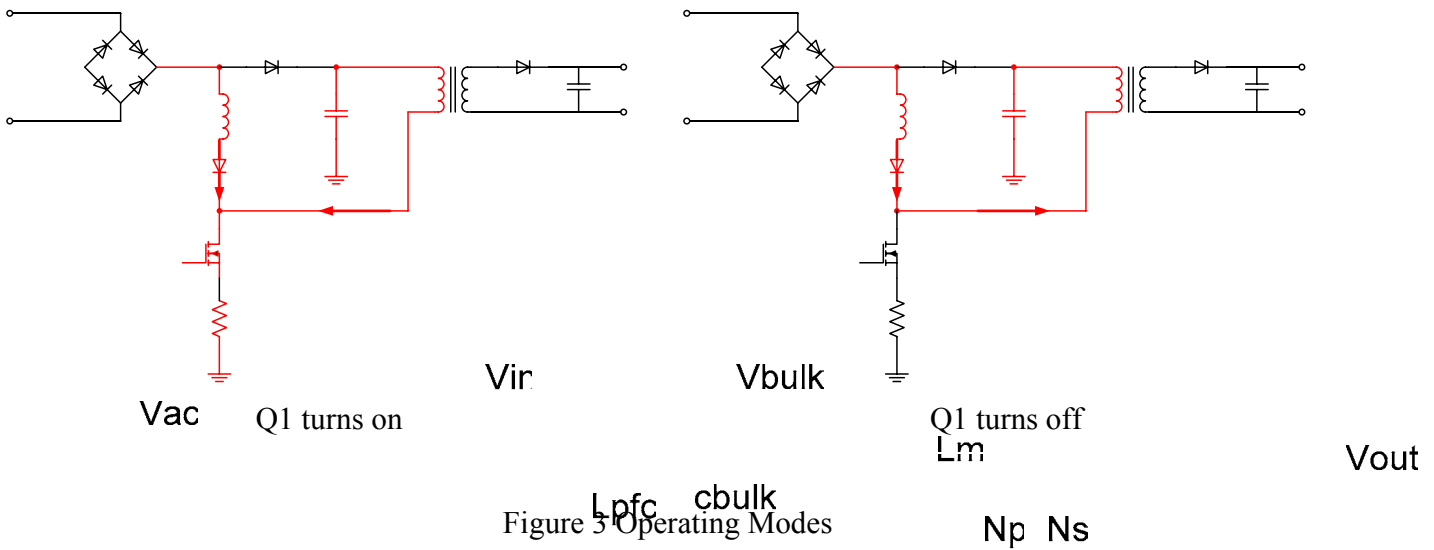


Figure 3 Operating Modes

D2

3 Determine bulk capacitor voltage

Assumption:

- V_{bulk} is always higher than V_{in} voltage. Diode D1 does not conduct in steady state operation. If $V_{in} = V_{amp} \sin(\omega t)$, then $V_{bulk} > V_{amp}$.
- V_{bulk} ripple is negligible, i.e. V_{bulk} is a constant DC voltage.
- Both PFC inductor and transformer are in DCM operating mode.

When Q1 turns on, the bulk capacitor releases energy to the transformer T1. The energy is then transferred to the output load when Q1 turns off. When Q1 turns off, the bulk capacitor is charged by the PFC inductor.

The power release from C_{bulk} in one cycle can be expressed as $P_{o2} = \frac{(V_{bk} T_{on})^2}{2L_m T_p}$

The power input from PFC inductor to the bulk capacitor is $P_i = \frac{V_{in} T_{on} T_{rst} V_{bk}}{2L_{pfc} T_p}$

Since $V_{in} = V_{amp} \sin(\omega t)$, by power balance during half AC cycle

$$\frac{1}{\pi} \int_0^{\pi} \frac{V_{amp} \sin(\omega t) T_{on} T_{rst} V_{bk}}{2L_{pfc} T_p} d\omega t = \frac{(V_{bk} T_{on})^2}{2L_m T_p}$$

By $V_{in} T_{on}$ balance on PFC inductor $T_{rst} = \frac{V_{in} T_{on}}{V_{bk} + N_{ps}(V_{out} + V_d) - V_{in}}$

The ratio between the PFC inductance and the magnetizing inductance vs. Vbulk is calculated to be

$$K_r = \frac{L_{pfc}}{L_m} = \frac{1}{\pi V_{bk}} \int_0^\pi \frac{[V_{amp} \sin(\omega t)]^2}{V_{bk} + N_{ps}(V_{out} + V_d) - V_{amp} \sin(\omega t)} d\omega t$$

Where

Vamp = AC input voltage amplitude

Vbulk = bulk capacitor voltage

Lm = magnetizing inductance

Nps = primary to secondary turn ratio

Vout = output voltage

Vd = output rectifier forward voltage drop

Assume the input voltage is 264Vac; the number of primary winding is 78; the number of secondary winding is 28, the output voltage is 28V, the output diode forward voltage drop is 0.5V.

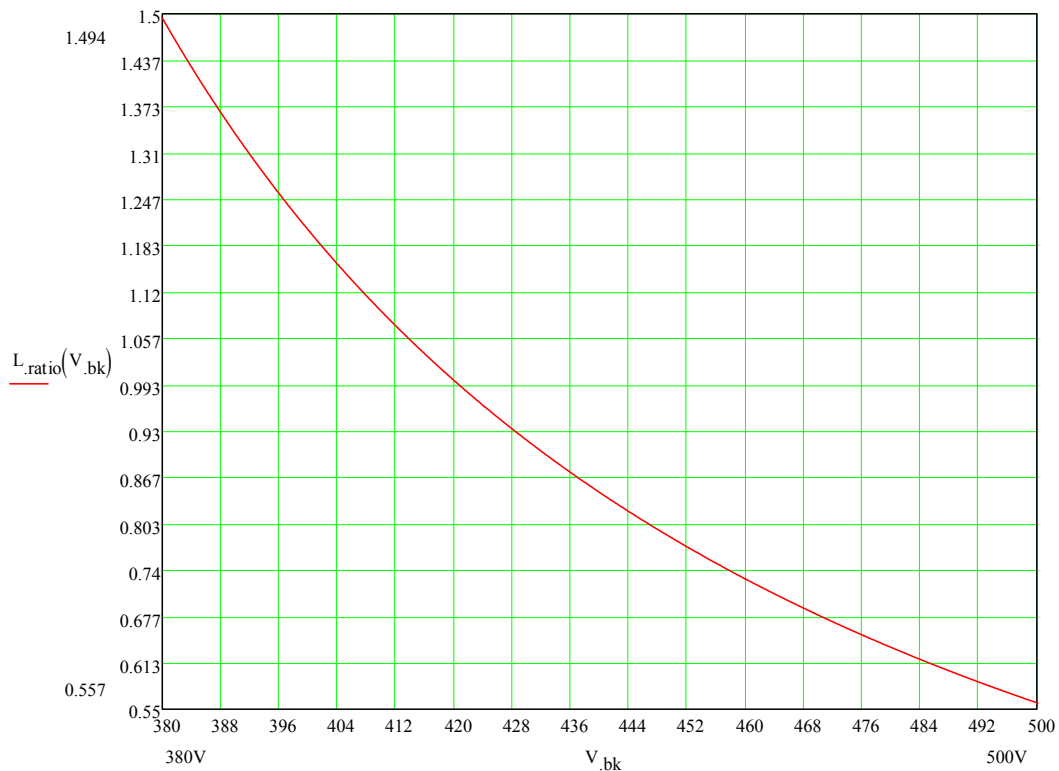


Figure 4 Kr ratio vs. Vbulk when AC input is 264V.

For example, if limit the average bulk voltage to 460V, from Figure 4, the ratio of PFC inductance vs. the magnetizing inductance is about $K_r = 0.72$.

4 PFC inductance and Flyback transformer magnetizing inductance

Assume V_{bulk} is always higher than V_{in} , then the power transferred from PFC inductor to the output loading can be expressed as $P_{o1} = \frac{V_{in} T_{on} T_{rst} N_{ps} (V_{out} + V_d)}{2L_{pfc} T_p} \eta_x$. The power delivered to the output

loading from the bulk capacitor is $P_{o2} = \frac{(V_{bk} T_{on})^2}{2L_m T_p} \eta_x$.

The total output power can be derived that $P_{out} = \frac{(V_{bk} T_{on})^2}{2T_p} \eta_x \left(\frac{1}{K_L L_{pfc}} + \frac{1}{L_m} \right)$

Where
$$K_L = \frac{1}{\frac{1}{\pi} \int_0^\pi \left(\frac{V_{amp} \sin(\omega t)}{V_{bk}} \right)^2 \frac{N_{ps} (V_{out} + V_d)}{V_{bk} + N_{ps} (V_{out} + V_d) - V_{amp} \sin(\omega t)} d\omega t}$$

Pout can also be rewritten as $P_{out} = \frac{(V_{bk} T_{on})^2}{2L_{eq} T_p} \eta_x$

Where
$$\frac{1}{L_{eq}} = \frac{1}{K_L L_{pfc}} + \frac{1}{L_m}$$

L_{eq} can represent the equivalent magnetizing inductance in a normal Flyback circuit design without considering the PFC inductor.

So the design process is, if V_{bulk} is known by estimation or measurement, L_{eq} can be calculated by following iW3620 design spreadsheet. Once L_{eq} is obtained, the PFC inductance and the L_m can be calculated by

$$L_{pfc} = K_r L_m, \quad L_m = \left(\frac{1}{K_L K_r} + 1 \right) L_{eq}$$

L_{eq} is usually designed at the lowest AC input where enough output power is needed to support the loading. So L_{pfc} and L_m are also calculated considering lowest V_{bulk} voltage.

For example, for a universal AC input line, 28V/0.5A output design, the desired L_{eq} is calculated to be 0.62mH. At AC input voltage 90Vac, average V_{bulk} is estimated to be 114V. Then calculate $K_L = 1.666$. We have $L_m = 1.13\text{mH}$; $L_{pfc} = 0.82\text{mH}$.

It is noted that if the AC input voltage drops, less power is transferred to the bulk capacitor from the PFC inductor. The diode D1 starts to forward bias when the PFC inductor is not enough to charge up the bulk capacitor.

The bulk capacitor voltage is also determined by the bulk capacitance. High bulk capacitance leads to lower voltage ripple on the bulk capacitor.