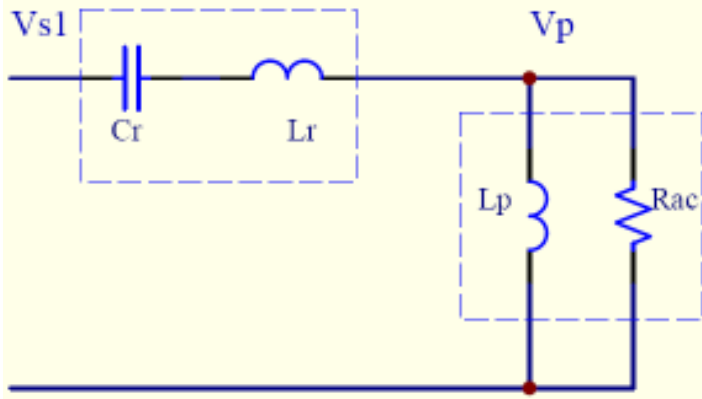


## LLC(SRC)G 值推導



$$k = \frac{L_p}{L_r}, \quad \omega_r = \frac{1}{\sqrt{L_r C_r}} \circ$$

$$f_1 = \frac{1}{2\pi\sqrt{L_r C_r}} = f_r,$$

$$f_2 = \frac{1}{2\pi\sqrt{(L_r + L_p)C_r}} \circ$$

$$Z_o = \sqrt{\frac{L_r}{C_r}} = 2\pi f_1 L_r = \frac{1}{2\pi f_1 C_r}, \quad Q = \frac{Z_o}{R_{ac}}, \quad s = j2\pi f = j\omega, \quad j^2 = -1, \quad x = \frac{\omega}{\omega_r}$$

$$|G| = \frac{V_p}{V_{s1}} = \frac{sL_p // R_{ac}}{\frac{1}{sC_r} + sL_r + (sL_p // R_{ac})} = \frac{k * (x)^2}{\sqrt{\{(1+k) * (x)^2 - 1\}^2 + \{Q * k * (x) * [(x)^2 - 1]\}^2}} = |M|$$

$$= \frac{k * (x)^2}{[(1+k)(x)^2 - 1] + jQ * k * (x) * [(x)^2 - 1]} \Rightarrow \frac{k * (x)^2}{\sqrt{[(1+k)(x)^2 - 1]^2 + \{Q * k * (x) * [(x)^2 - 1]\}^2}}$$

當  $x = \frac{\omega}{\omega_r} = 1, \quad \omega = \omega_r$

$$|M| = \frac{k * (1)^2}{[(1+k)(1)^2 - 1] + jQ * k * (1) * [(1)^2 - 1]} \Rightarrow \frac{k * (1)^2}{\sqrt{[(1+k)(1)^2 - 1]^2 + \{Q * k * (1) * [(1)^2 - 1]\}^2}} = 1$$

代表在諧振頻率時不管負載如何變動增益都是固定為 1。