



# Applications Note: SY5800A

## Single Stage Flyback And PFC Controller


### With Primary Side Control For LED Lighting

*Preliminary Specification*

### General Description

The SY5800A is a single stage Flyback and PFC controller targeting at LED lighting applications. It is a primary side controller without applying any secondary feedback circuit for low cost, and drives the Flyback converter in the quasi-resonant mode to achieve higher efficiency. It keeps the Flyback converter in constant on time operation to achieve high power factor.

### Ordering Information

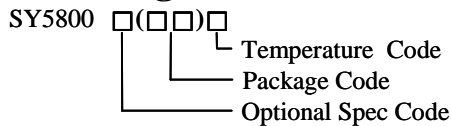

Temperature Range: -40°C to 125°C

Ordering Number	Package type	Note
SY5800AFBC	MSOP10	----
SY5800AFAC	SO8	----

### Features

- Primary side control eliminates the opto-coupler.
- Valley turn-on of the primary MOSFET to achieve low switching losses
- 0.3V primary current sense reference voltage leads to a lower sense resistance thus a lower conduction loss.
- Internal high current MOSFET driver: 1A sourcing and 2A sinking
- Low start up current: 15uA typical
- Reliable short LED and Open LED protection
- Power factor >0.90 with single-stage conversion.
- Compact package: MSOP10 and SO8

### Applications

- LED lighting
- Down light
- Tube lamp
- PAR lamp
- Bulb

### Typical Applications

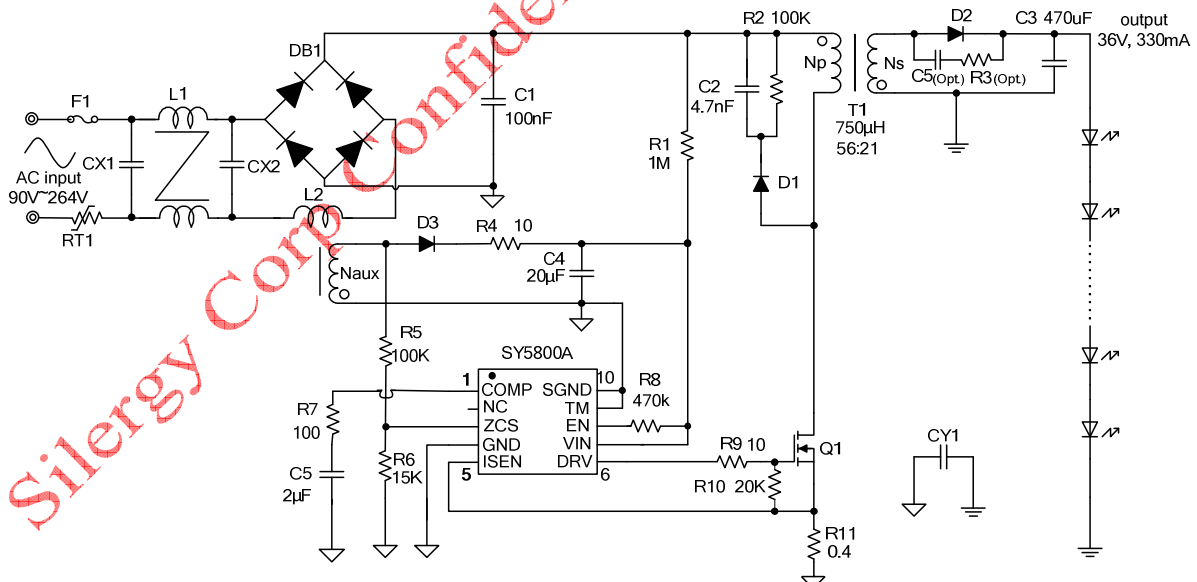


Figure 1. Schematic Diagram MSOP10


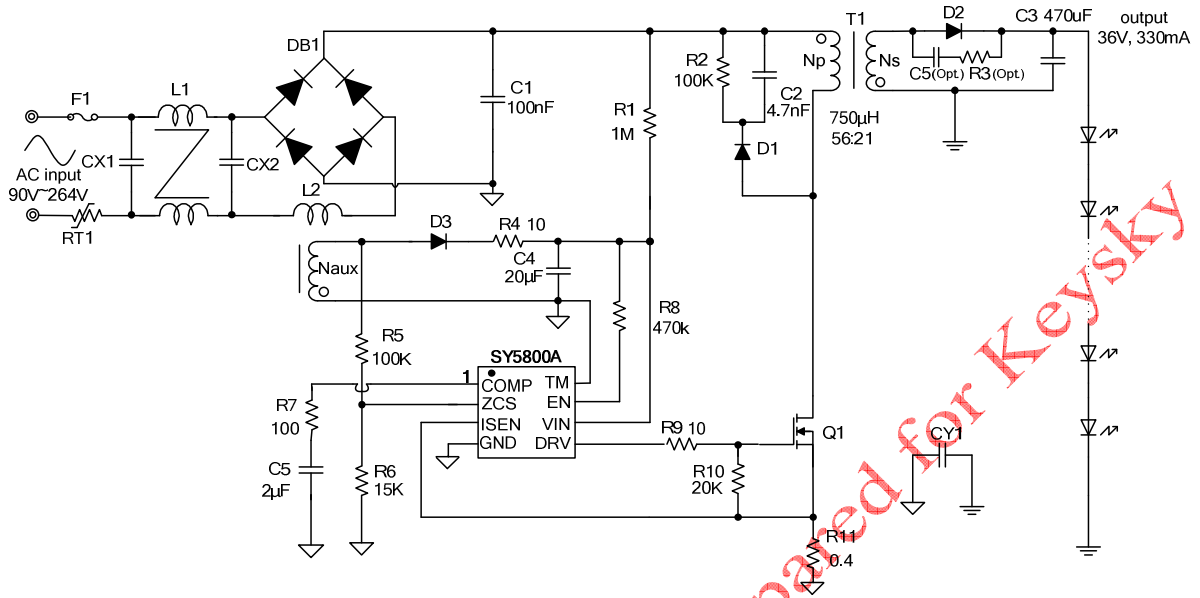


Figure 2. Schematic Diagram SO8

Silergy Corp Confidential Prepared for Keysky

## Pinout (top view)

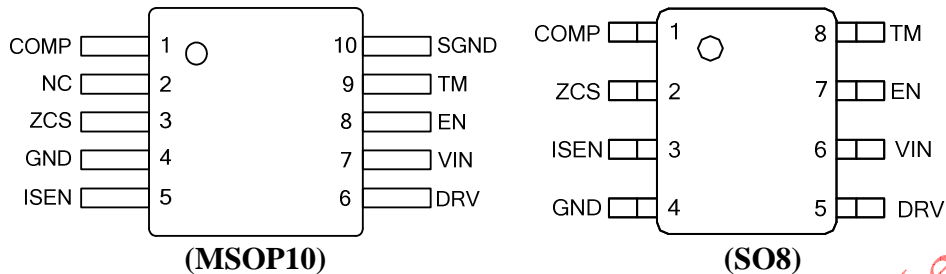

**Top Mark:** AFDxyz for SY5800AFBC (device code: AFD, x=year code, y=week code, z=lot number code)  
 AFBxyz for SY5800AFAC (device code: AFB, x=year code, y=week code, z=lot number code)

Pin Name	Pin number SO8	Pin number MSOP10	Pin Description
COMP	1	1	Loop compensation pin. Connect a RC network across this pin and ground to stabilize the control loop.
NC	----	2	No connection.
ZCS	2	3	Inductor current zero-crossing detection pin. This pin receives the auxiliary winding voltage by a resistor divider and detects the inductor current zero crossing point. This pin also provides over voltage protection and line regulation modification function simultaneously. If the voltage on this pin is above 1.42V, the IC would enter over voltage protection mode. Good line regulation can be achieved by adjusting the upper resistor of the divider.
ISEN	3	5	Current sense pin. Connect this pin to the source of the primary switch. Connect the sense resistor across the source of the primary switch and the GND pin. $(current\ sense\ resistor\ R_s: R_s = k \frac{V_{REF} \times N_{PS}}{I_{OUT}}, k = 0.16)$
GND	4	4	Ground pin
DRV	5	6	Gate driver pin. Connect this pin to the gate of primary MOSFET.
VIN	6	7	Power supply pin. This pin also provides output over voltage protection along with ZCS pin.
EN	7	8	Enable pin. Enable the IC by pulling the voltage on this pin above 1.5V and Shut down the IC by pulling the voltage on this pin below 0.2V. If not used, connect this pin to VIN pin with a resistor (470kΩ is recommended).
TM	8	9	Connected to ground.
SGND	----	10	Signal ground.

## Absolute Maximum Ratings (Note 1)

VIN, DRV	-----	-0.3V to 17V
EN, ZCS	-----	-0.3V to VIN+0.3V
ISEN, COMP, TM	-----	3.6V
Power Dissipation, @ TA = 25°C MSOP10/SO8	-----	0.8W/1.1W
Package Thermal Resistance (Note 2)		
MSOP10/SO8, $\theta_{JA}$	-----	125°C/W / 88°C/W
MSOP10/SO8, $\theta_{JC}$	-----	60°C/W / 45°C/W
Temperature Range	-----	-40°C to 150°C
Lead Temperature (Soldering, 10 sec.)	-----	260°C
Storage Temperature Range	-----	-65°C to 150°C

## Recommended Operating Conditions (Note 3)

VIN, DRV	-----	8V~15.4V
Junction Temperature Range	-----	-40°C to 125°C
Ambient Temperature Range	-----	-40°C to 85°C

## Block Diagram

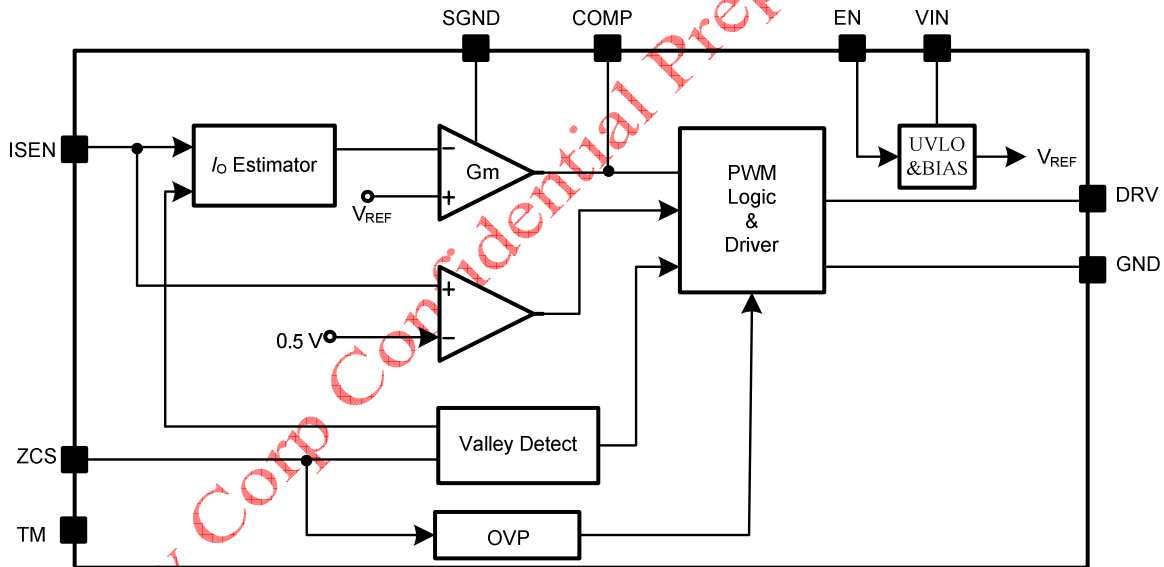


Figure3. Block Diagram

## Electrical Characteristics

( $V_{IN} = 12V$  (Note 3),  $T_A = 25^\circ C$  unless otherwise specified)

Parameter	Symbol	Test Conditions	Min	Typ	Max	Unit
<b>Power Supply Section</b>						
Input voltage range	$V_{VIN}$		8		15.4	V
VIN turn-on threshold	$V_{VIN,ON}$				17.6	V
VIN turn-off threshold	$V_{VIN,OFF}$		6.0		7.9	V
VIN OVP voltage	$V_{VIN,OVP}$			$V_{VIN,ON}+0.85$		V
Start up Current	$I_{ST}$	$V_{VIN} < V_{VIN,OFF}$		15		$\mu A$
Operating Current	$I_{VIN}$	$C_L=100pF, f=15kHz$		1		mA
Shunt current in OVP mode	$I_{VIN,OVP}$	$V_{VIN} > V_{VIN,OVP}$	1.6	2	2.5	mA
<b>Error Amplifier Section</b>						
Internal reference voltage	$V_{REF}$		0.294	0.3	0.306	V
<b>Current Sense Section</b>						
Current limit reference voltage	$V_{ISEN,MAX}$			0.5		V
<b>ZCS pin Section</b>						
ZCS pin OVP voltage threshold	$V_{ZCS,OVP}$			1.42		V
<b>Gate Driver Section</b>						
Gate driver voltage	$V_{Gate}$			$V_{VIN}$		V
Maximum source current	$I_{SOURCE}$			1		A
Minimum sink current	$I_{SINK}$			2		A
Max ON Time	$T_{ON,MAX}$	$V_{COMP}=1.5V$		24		$\mu s$
Min ON Time	$T_{ON,MIN}$			400		ns
Max OFF Time	$T_{OFF,MAX}$			39		$\mu s$
Min OFF Time	$T_{OFF,MIN}$			2		$\mu s$
Maximum switching frequency	$f_{MAX}$			120		kHz
<b>Enable function Section</b>						
Enable ON	$V_{EN,ON}$			1.5		V
Enable OFF	$V_{EN,OFF}$			0.2		V
<b>Thermal Section</b>						
Thermal Shutdown Temperature	$T_{SD}$			150		$^\circ C$

**Note 1:** Stresses beyond the “Absolute Maximum Ratings” may cause permanent damage to the device. These are stress ratings only. Functional operation of the device at these or any other conditions beyond those indicated in the operational sections of the specification is not implied. Exposure to absolute maximum rating conditions for extended periods may affect device reliability.

**Note 2:**  $\theta_{JA}$  is measured in the natural convection at  $T_A = 25^\circ C$  on a low effective single layer thermal conductivity test board of JEDEC 51-3 thermal measurement standard. Test condition: Device mounted on 2” x 2” FR-4 substrate PCB, 2oz copper, with minimum recommended pad on top layer and thermal vias to bottom layer ground plane.

**Note 3:** Increase VIN pin voltage gradually higher than  $V_{VIN,ON}$  voltage then turn down to 12V.

## Operation

SY5800A is a constant current Flyback controller with primary side control and PFC function that targets at LED lighting applications.

The Device provides primary side control to eliminate the opto-couplers or the secondary feedback circuits, which would cut down the cost of the system.

High power factor is achieved by constant on operation mode, with which the control scheme and the circuit structure are both simple.

In order to reduce the switching losses and improve EMI performance, Quasi-Resonant switching mode is applied, which means to turn on the power MOSFET at voltage valley; the start up current of SY5800A is rather small (15uA typically) to reduce the standby power loss further; the maximum switching frequency is clamped to 120kHz to reduce switching losses and improve EMI performance when the converter is operated at light load condition.

SY5800A provides reliable protections such as Short Circuit Protection (SCP), Open LED Protection (OLP), Over Temperature Protection (OTP), etc.

SY5800A is available with SO8 and MSOP10 package.

## Applications Information

### Start up

After AC supply or DC BUS is powered on, the capacitor  $C_{VIN}$  across VIN and GND pin is charged up by BUS voltage through a start up resistor  $R_{ST}$ . Once  $V_{VIN}$  rises up to  $V_{VIN\_ON}$ , the internal blocks start to work.  $V_{VIN}$  will be pulled down by internal consumption of IC until the auxiliary winding of Flyback transformer could supply enough energy to maintain  $V_{VIN}$  above  $V_{VIN\_OFF}$ .

The whole start up procedure is divided into two sections shown in Fig.4.  $t_{STC}$  is the  $C_{VIN}$  charged up section, and  $t_{STO}$  is the output voltage built-up section. The start up time  $t_{ST}$  composes of  $t_{STC}$  and  $t_{STO}$ , and usually  $t_{STO}$  is much smaller than  $t_{STC}$ .

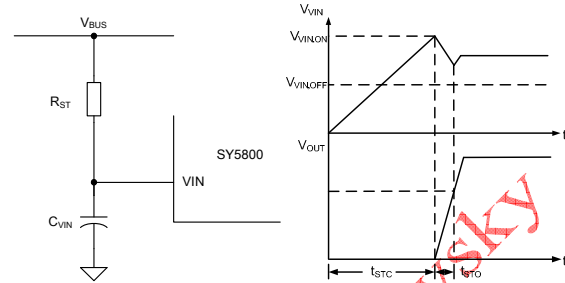


Fig.4 Start up

The start up resistor  $R_{ST}$  and  $C_{VIN}$  are designed by rules below:

(a) Preset start-up resistor  $R_{ST}$ , make sure that the current through  $R_{ST}$  is larger than  $I_{ST}$  and smaller than  $I_{VIN\_OVP}$

$$\frac{V_{BUS}}{I_{VIN\_OVP}} < R_{ST} < \frac{V_{BUS}}{I_{ST}} \quad (1)$$

Where  $V_{BUS}$  is the BUS line voltage.

(b) Select  $C_{VIN}$  to obtain an ideal start up time  $t_{ST}$ , and ensure the output voltage is built up at one time.

$$C_{VIN} = \frac{\left(\frac{V_{BUS}}{R_{ST}} - I_{ST}\right) \times t_{ST}}{V_{VIN\_ON}} \quad (2)$$


(d) If the  $C_{VIN}$  is not big enough to build up the output voltage at one time. Increase  $C_{VIN}$  and decrease  $R_{ST}$ , go back to step (a) and redo such design flow until the ideal start up procedure is obtained.

### Internal pre-charge design for quick start up

After  $V_{VIN}$  exceeds  $V_{VIN\_ON}$ ,  $V_{COMP}$  is pre-charged by an internal current source. The PWM block won't start to output PWM signals until  $V_{COMP}$  is over the initial voltage  $V_{COMP\_IC}$ , which can be programmed by  $R_{COMP}$ . Such design is meant to reduce the start up time shown in Fig.5.

The voltage pre-charged  $V_{COMP\_IC}$  in start-up procedure can be programmed by  $R_{COMP}$

$$V_{COMP\_IC} = 600mV - 300\mu A \times R_{COMP} \quad (3)$$

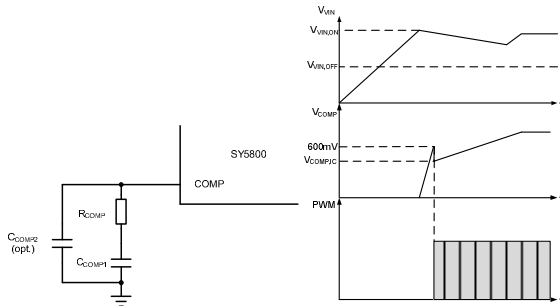
**Fig.5 pre-charge scheme in start up**

Where  $V_{COMP-IC}$  is the pre-charged voltage of COMP pin.

Generally, a big capacitance of  $C_{COMP}$  is necessary to achieve high power factor and stabilize the system loop ( $1\mu F \sim 2\mu F$  recommended); The voltage pre-charged in start-up procedure can be programmed by  $R_{COMP}$ ; On the other hand, larger  $R_{COMP}$  can provide larger phase margin for the control loop; A small ceramic capacitor is added to suppress high frequency interruption ( $10pF \sim 100pF$  is recommended if necessary)

### Shut down

After AC supply or DC BUS is powered off, the energy stored in the BUS capacitor will be discharged. When the auxiliary winding of Flyback transformer can not supply enough energy to VIN pin,  $V_{VIN}$  will drop down. Once  $V_{VIN}$  is below  $V_{VIN-OFF}$ , the IC will stop working and  $V_{COMP}$  will be discharged to zero.

### Primary-side constant-current control


Primary side control is applied to eliminate secondary feedback circuit or opto-coupler, which reduces the circuit cost. The switching waveforms are shown in Fig.6.

The output current  $I_{OUT}$  can be represented by,

$$I_{OUT} = \frac{I_{SP}}{2} \times \frac{t_{DIS}}{t_s} \quad (4)$$

Where  $I_{SP}$  is the peak current of the secondary side;  $t_{DIS}$  is the discharge time of Flyback transformer;  $t_s$  is the switching period.

The secondary peak current is related with primary peak current, if the effect of the leakage inductor is neglected.

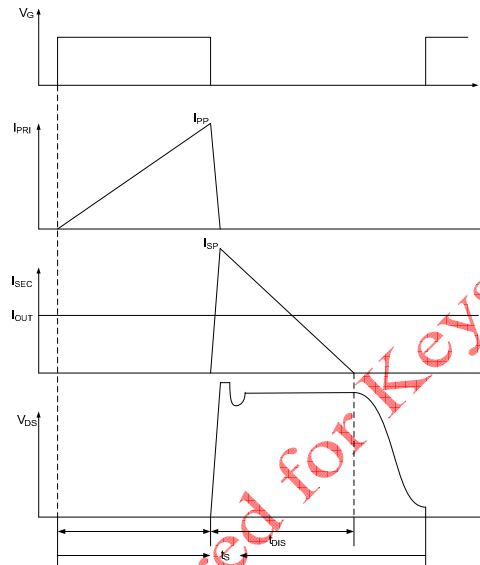
**Fig.6 switching waveforms**

$$I_{SP} = N_{PS} \times I_{PP} \quad (5)$$

Where  $N_{PS}$  is the turns ratio of primary to secondary of the Flyback transformer.

Thus,  $I_{OUT}$  can be represented by

$$I_{OUT} = \frac{N_{PS} \times I_{PP}}{2} \times \frac{t_{DIS}}{t_s} \quad (6)$$

The primary peak current  $I_{PP}$  and inductor current discharge time  $t_{DIS}$  can be detected by the IC, and the effect of the leakage inductor can be compensated by internal control scheme.  $I_{OUT}$  can be induced finally by

$$I_{OUT} = \frac{k_1 \times k_2 \times V_{REF} \times N_{PS}}{R_s} \quad (7)$$

Where  $k_1$  is the output current weight coefficient;  $k_2$  is the output modification coefficient;  $V_{REF}$  is the internal reference voltage;  $R_s$  is the current sense resistor.

$k_1, k_2$  and  $V_{REF}$  are all internal constant parameters,  $I_{OUT}$  can be programmed by  $N_{PS}$  and  $R_s$ .

$$R_s = \frac{k_1 \times k_2 \times V_{REF} \times N_{PS}}{I_{OUT}} \quad (8)$$

### Quasi-Resonant Operation

QR mode operation provides low turn-on switching losses for Flyback converter.

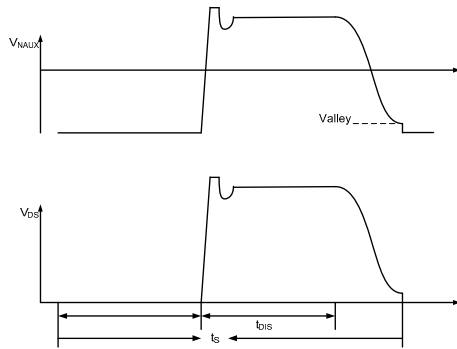


Fig.7 QR mode operation

The voltage across drain and source of the primary MOSFET is reflected by the auxiliary winding of the Flyback transformer. ZCS pin detects the voltage across the auxiliary winding by a resistor divider. When the voltage across drain and source of the primary MOSFET is at voltage valley, the MOSFET would be turned on.

### Over Voltage Protection (OVP) & Open LED Protection (OLP)

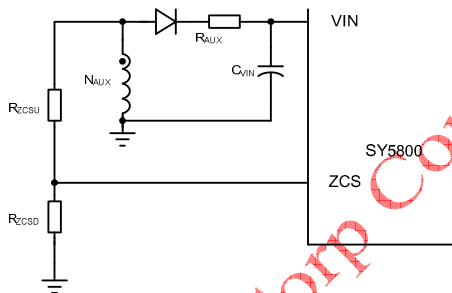


Fig.8 OVP&OLP

The output voltage is reflected by the auxiliary winding voltage of the Flyback transformer, and both ZCS pin and VIN pin provide over voltage protection function. When the load is null or large transient happens, the output voltage will exceed the rated value. When  $V_{VIN}$  exceeds  $V_{VIN,OVP}$  or  $V_{ZCS}$  exceeds  $V_{ZCS,OVP}$ , the over voltage protection is triggered and the IC will discharge  $V_{VIN}$  by an internal current source  $I_{VIN,OVP}$ . Once  $V_{VIN}$  is below  $V_{VIN,OFF}$ , the IC will shut down and be charged again by BUS voltage through start up resistor. If the over voltage condition still exists, the system will operate in hiccup mode.

Thus, the turns of the auxiliary winding  $N_{AUX}$  and the resistor divider is related with the OVP function.

$$\frac{V_{ZCS,OVP}}{V_{OVP}} = \frac{N_{AUX}}{N_s} \times \frac{R_{ZCSD}}{R_{ZCSU} + R_{ZCSD}} \quad (9)$$

$$\frac{V_{VIN,OVP}}{V_{OVP}} \geq \frac{N_{AUX}}{N_s} \quad (10)$$

Where  $V_{OVP}$  is the output over voltage specification;  $R_{ZCSU}$  and  $R_{ZCSD}$  compose the resistor divider. The turns ratio of  $N_s$  to  $N_{AUX}$  and the ratio of  $R_{ZCSU}$  to  $R_{ZCSD}$  could be induced from equation (9) and (10).

### Short Circuit Protection (SCP)

When the output is shorted to ground, the output voltage is clamped to zero. The voltage of the auxiliary winding is proportional to the output winding, so  $V_{VIN}$  will drop down without auxiliary winding supply. Once  $V_{VIN}$  is below  $V_{VIN,OFF}$ , the IC will shut down and be charged again by the BUS voltage through the start up resistor. If the short circuit condition still exists, the system will operate in hiccup mode.

In order to guarantee SCP function not effected by voltage spike of auxiliary winding, a filter resistor  $R_{AUX}$  is needed ( $10\Omega$  typically) shown in Fig.8.

### Line regulation modification

The IC provides line regulation modification function to improve line regulation performance.

Due to the sample delay of ISEN pin and other internal delay, the output current increases with increasing input BUS line voltage. A small compensation voltage  $\Delta V_{ISEN-C}$  is added to ISEN pin during ON time to improve such performance. This  $\Delta V_{ISEN-C}$  is adjusted by the upper resistor of the divider connected to ZCS pin.

$$\Delta V_{ISEN,C} = V_{BUS} \times \frac{N_{AUX}}{N_p} \times \frac{1}{R_{ZCSU}} \times k_3 \quad (11)$$

Where  $R_{ZCSU}$  is the upper resistor of the divider;  $k_3$  is an internal constant as the modification coefficient.



The compensation is mainly related with  $R_{ZCSU}$ , larger compensation is achieved with smaller  $R_{ZCSU}$ . Normally,  $R_{ZCS}$  ranges from 100kΩ~1MΩ.

Then  $R_{ZCSD}$  can be selected by,

$$\frac{\frac{V_{ZCS\_OVP}}{V_{OUT}} \times \frac{N_s}{N_{AUX}}}{1 - \frac{V_{ZCS\_OVP}}{V_{OUT}} \times \frac{N_s}{N_{AUX}}} \times R_{ZCSU} > R_{ZCSD} \quad (12),$$

And,

$$R_{ZCSD} \geq \frac{\frac{V_{ZCS\_OVP}}{V_{OVP}} \times \frac{N_s}{N_{AUX}}}{1 - \frac{V_{ZCS\_OVP}}{V_{OVP}} \times \frac{N_s}{N_{AUX}}} \times R_{ZCSU} \quad (13)$$

Where  $V_{OVP}$  is the output over voltage protection specification;  $V_{OUT}$  is the rated output voltage;  $R_{ZCSU}$  is the upper resistor of the divider;  $N_s$  and  $N_{AUX}$  are the turns of secondary winding and auxiliary winding separately.

## Power Device Design

### MOSFET and Diode

When the operation condition is with maximum input voltage and full load, the voltage stress of MOSFET and secondary power diode is maximized;

$$V_{MOS\_DS\_MAX} = \sqrt{2}V_{AC\_MAX} + N_{PS} \times (V_{OUT} + V_{D\_F}) + \Delta V_s \quad (14)$$

$$V_{D\_R\_MAX} = \frac{\sqrt{2}V_{AC\_MAX}}{N_{PS}} + V_{OUT} \quad (15)$$

Where  $V_{AC\_MAX}$  is maximum input AC RMS voltage;  $N_{PS}$  is the turns ratio of the Flyback transformer;  $V_{OUT}$  is the rated output voltage;  $V_{D\_F}$  is the forward voltage of secondary power diode;  $\Delta V_s$  is the overshoot voltage clamped by RCD snubber during OFF time.

When the operation condition is with minimum input voltage and full load, the current stress of MOSFET and power diode is maximized.

$$I_{MOS\_PK\_MAX} = I_{P\_PK\_MAX} \quad (16)$$

$$I_{MOS\_RMS\_MAX} = I_{P\_RMS\_MAX} \quad (17)$$

$$I_{D\_PK\_MAX} = N_{PS} \times I_{P\_PK\_MAX} \quad (18)$$

$$I_{D\_AVG} = I_{OUT} \quad (19)$$

Where  $I_{P\_PK\_MAX}$  and  $I_{P\_RMS\_MAX}$  are maximum primary peak current and RMS current, which will be introduced later.

### Transformer ( $N_{PS}$ and $L_M$ )

$N_{PS}$  is limited by the electrical stress of the power MOSFET:

$$N_{PS} \leq \frac{V_{MOS\_BR/DS} \times 90\% - \sqrt{2}V_{AC\_MAX} - \Delta V_s}{V_{OUT} + V_{D\_F}} \quad (20)$$

Where  $V_{MOS\_BR/DS}$  is the breakdown voltage of the power MOSFET.

In Quasi-Resonant mode, each switching period cycle  $t_s$  consists of three parts: current rising time  $t_1$ , current falling time  $t_2$  and quasi-resonant time  $t_3$  shown in Fig.9.

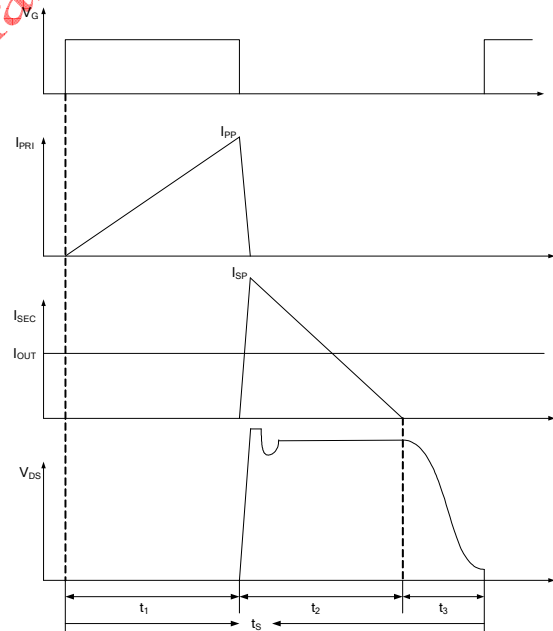


Fig.9 switching waveforms

The system operates in the constant on time mode to achieve high power factor. The ON time increases with the input AC RMS voltage decreasing and the load

increasing. When the operation condition is with minimum input AC RMS voltage and full load, the ON time is maximized. On the other hand, when the input voltage is at the peak value, the OFF time is maximized. Thus, the minimum switching frequency  $f_{S-MIN}$  happens at the peak value of input voltage with minimum input AC RMS voltage and maximum load condition; Meanwhile, the maximum peak current through MOSFET and the transformer happens.

Once the minimum frequency  $f_{S-MIN}$  is set, the inductance of the transformer could be induced. The design flow is shown as below:

(a) Select  $N_{PS}$

$$N_{PS} \leq \frac{V_{MOS(BR)DS} \times 90\% - \sqrt{2}V_{AC\_MAX} - \Delta V_S}{V_{OUT} + V_{D,F}} \quad (21)$$

(b) Preset minimum frequency  $f_{S-MIN}$

(c) Compute relative  $t_s$ ,  $t_1$  ( $t_3$  is omitted to simplify the design here)

$$t_s = \frac{1}{f_{S-MIN}} \quad (22)$$

$$t_1 = \frac{t_s \times N_{PS} \times (V_{OUT} + V_{D,F})}{\sqrt{2}V_{AC\_MIN} + N_{PS} \times (V_{OUT} + V_{D,F})} \quad (23)$$

(d) Design inductance  $L_M$

$$L_M = \frac{V_{AC\_MIN}^2 \times t_1^2 \times \eta}{2P_{OUT} \times t_s} \quad (24)$$

(e) Compute  $t_3$

$$t_3 = \pi \times \sqrt{L_M \times C_{Drain}} \quad (25)$$

Where  $C_{Drain}$  is the parasitic capacitance at drain of MOSFET.

(f) Compute primary maximum peak current  $I_{P-PK-MAX}$  and RMS current  $I_{P-RMS-MAX}$  for the transformer fabrication.

$$I_{P-PK-MAX} = \frac{2P_{OUT} \times \left[ \frac{L_M}{\sqrt{2}V_{AC\_MIN}} + \frac{L_M}{N_{PS} \times (V_{OUT} + V_{D,F})} \right]}{L_M \times \eta} + \sqrt{\frac{4P_{OUT}^2 \times \left[ \frac{L_M}{\sqrt{2}V_{AC\_MIN}} + \frac{L_M}{N_{PS} \times (V_{OUT} + V_{D,F})} \right]^2 + 4L_M \times \eta \times P_{OUT} \times t_3}{L_M \times \eta}} \quad (26)$$

Where  $\eta$  is the efficiency;  $P_{OUT}$  is rated full load power

Adjust  $t_1$  and  $t_3$  to  $t_1'$  and  $t_3'$  considering the effect of  $t_3$

$$t_3' = \frac{\eta \times L_M \times I_{P-PK-MAX}^2}{4P_{OUT}} \quad (27)$$

$$t_1' = \frac{L_M \times I_{P-PK-MAX}}{\sqrt{2}V_{AC\_MIN}} \quad (28)$$

$$I_{P-RMS-MAX} \approx \sqrt{\frac{t_1'}{6t_3'}} \times I_{P-PK-MAX} \quad (29)$$

(g) Compute secondary maximum peak current  $I_{S-PK-MAX}$  and RMS current  $I_{S-RMS-MAX}$  for the transformer fabrication.

$$I_{S-PK-MAX} = N_{PS} \times I_{P-PK-MAX} \quad (30)$$

$$t_2 = t_3' - t_1' - t_3 \quad (31)$$

$$I_{S-RMS-MAX} \approx \sqrt{\frac{t_2'}{6t_3'}} \times I_{S-PK-MAX} \quad (32)$$

### Transformer design ( $N_P, N_S, N_{AUX}$ )

The design of the transformer is similar with ordinary Flyback transformer. the parameters below are necessary:

Necessary parameters	
Turns ratio	$N_{PS}$
Inductance	$L_M$
Primary maximum current	$I_{P-PK-MAX}$
Primary maximum RMS current	$I_{P-RMS-MAX}$
Secondary maximum RMS current	$I_{S-RMS-MAX}$

The design rules are as followed:

(a) Select the magnetic core style, identify the effective area  $A_e$ .

(b) Preset the maximum magnetic flux  $\Delta B$

$$\Delta B = 0.22 \sim 0.26 T$$

(c) Compute primary turn  $N_P$

$$N_P = \frac{L_M \times I_{P-PK-MAX}}{\Delta B \times A_e} \quad (33)$$

(d) Compute secondary turn  $N_S$

$$N_S = \frac{N_P}{N_{PS}} \quad (34)$$

(e) compute auxiliary turn  $N_{AUX}$

$$N_{AUX} = N_S \times \frac{V_{VIN}}{V_{OUT}} \quad (35)$$

Where  $V_{VIN}$  is the working voltage of VIN pin (10V~11V is recommended).

(f) Select an appropriate wire diameter

With  $I_{P-RMS-MAX}$  and  $I_{S-RMS-MAX}$ , select appropriate wire to make sure the current density ranges from 4A/mm<sup>2</sup> to 10A/mm<sup>2</sup>.

(g) If the winding area of the core and bobbin is not enough, reselect the core style, go to (a) and redesign the transformer until the ideal transformer is achieved.

### Output capacitor $C_{OUT}$

Preset the output current ripple  $\Delta I_{OUT}$ ,  $C_{OUT}$  is induced by

$$C_{OUT} = \frac{\sqrt{\left(\frac{2I_{OUT}}{\Delta I_{OUT}}\right)^2 - 1}}{4\pi f_{AC} R_{LED}} \quad (36)$$

Where  $I_{OUT}$  is the rated output current;  $\Delta I_{OUT}$  is the demanded current ripple;  $f_{AC}$  is the input AC supply frequency;  $R_{LED}$  is the equivalent series resistor of the LED load.

### RCD snubber for MOSFET

The power loss of the snubber  $P_{RCD}$  is evaluated first

$$P_{RCD} = \frac{N_{PS} \times (V_{OUT} + V_{D,F}) + \Delta V_S}{\Delta V_S} \times \frac{L_K}{L_M} \times P_{OUT} \quad (37)$$

Where  $N_{PS}$  is the turns ratio of the Flyback transformer;  $V_{OUT}$  is the output voltage;  $V_{D,F}$  is the forward voltage of the power diode;  $\Delta V_S$  is the overshoot voltage clamped by RCD snubber;  $L_K$  is the leakage inductor;  $L_M$  is the inductance of the Flyback transformer;  $P_{OUT}$  is the output power.

The  $R_{RCD}$  is related with the power loss:

$$R_{RCD} = \frac{(N_{PS} \times (V_{OUT} + V_{D,F}) + \Delta V_S)^2}{P_{RCD}} \quad (38)$$

The  $C_{RCD}$  is related with the voltage ripple of the snubber  $\Delta V_{C-RCD}$ :

$$C_{RCD} = \frac{N_{PS} \times (V_{OUT} + V_{D,F}) + \Delta V_S}{R_{RCD} f_s \Delta V_{C-RCD}} \quad (39)$$

## Layout

(a) To achieve better EMI performance and reduce line frequency ripples, the output of the bridge rectifier should be connected to the BUS line capacitor first, then to the switching circuit.

(b) The ground of the BUS line capacitor, the ground of the current sample resistor and the signal ground of the IC should be connected in a star connection.

(c) The circuit loop of all switching circuit should be kept small: primary power loop, secondary loop and auxiliary power loop.

(d) The wire connected to ISEN and DRV should be as thick as possible.

(e) The resistor divider is recommended to be put beside the IC.

## Design Example

A design example of typical application is shown below step by step.

### #1. Identify design specification

Design Specification			
$V_{AC(RMS)}$	90V~264V	$V_{OUT}$	38V
$I_{OUT}$	320mA	$\eta$	87%

### #2. Transformer design ( $N_{PS}$ , $L_M$ )

Refer to Power Device Design

Conditions			
$V_{AC\_MIN}$	90V	$V_{AC\_MAX}$	264V
$\Delta V_S$	50V	$V_{MOS\_ (BR)DS}$	600V
$P_{OUT}$	12W	$V_{D,F}$	1V
$C_{Drain}$	100pF	$f_{S\_MIN}$	75kHz

#### (a) Compute turns ratio $N_{PS}$ first

$$N_{PS} \leq \frac{V_{MOS\_ (BR)DS} \times 90\% - \sqrt{2} V_{AC\_MAX} - \Delta V_S}{V_{OUT} + V_{D,F}}$$

$$= \frac{600V \times 0.9 - \sqrt{2} \times 264V - 50V}{38V + 1V}$$

$$= 2.99$$

$N_{PS}$  is set to

$$N_{PS} = 2.67$$

#### (b) $f_{S\_MIN}$ is preset

$$f_{S\_MIN} = 75kHz$$

#### (c) Compute the switching period $t_s$ and ON time $t_1$ at the peak of input voltage.

$$t_s = \frac{1}{f_{S\_MIN}} = 13.3\mu s$$

$$t_1 = \frac{t_s \times N_{PS} \times (V_{OUT} + V_{D,F})}{\sqrt{2} V_{AC\_MIN} + N_{PS} \times (V_{OUT} + V_{D,F})}$$

$$= \frac{13.3\mu s \times 2.67 \times (38V + 1V)}{\sqrt{2} \times 90V + (38V + 1V)}$$

$$= 6\mu s$$

(d) Compute the inductance  $L_M$

$$\begin{aligned} L_M &= \frac{V_{AC\_MIN}^2 \times t_1^2 \times \eta}{2P_{OUT} \times t_s} \\ &= \frac{90V^2 \times 6\mu s^2 \times 0.87}{2 \times 12W \times 13.3\mu s} \\ &= 780\mu H \end{aligned}$$

Set

$$L_M = 750\mu H$$

(e) Compute the quasi-resonant time  $t_3$

$$\begin{aligned} t_3 &= \pi \times \sqrt{L_M \times C_{Drain}} \\ &= \pi \times \sqrt{750\mu H \times 100pF} \\ &= 860ns \end{aligned}$$

(f) Compute primary maximum peak current  $I_{P\_PK\_MAX}$

$$\begin{aligned} I_{P\_PK\_MAX} &= \frac{2P_{OUT} \times \left[ \frac{L_M}{\sqrt{2}V_{AC\_MIN}} + \frac{L_M}{N_{PS} \times (V_{OUT} + V_{D,F})} \right]}{L_M \times \eta} \\ &+ \frac{\sqrt{4P_{OUT}^2 \times \left[ \frac{L_M}{\sqrt{2}V_{AC\_MIN}} + \frac{L_M}{N_{PS} \times (V_{OUT} + V_{D,F})} \right]^2 + 4L_M \times \eta \times P_{OUT} \times t_3}}{L_M \times \eta} \\ &= 1.038A \end{aligned}$$

Adjust switching period  $t_s$  and ON time  $t_1$  to  $t'_s$  and  $t'_1$ .

$$\begin{aligned} t'_s &= \frac{\eta \times L_M \times I_{P\_PK\_MAX}^2}{4P_{OUT}} \\ &= \frac{0.87 \times 750\mu H \times 1.038A^2}{4 \times 12W} \\ &= 14.45\mu s \end{aligned}$$

$$\begin{aligned} t'_1 &= \frac{L_M \times I_{P\_PK\_MAX}}{\sqrt{2}V_{AC\_MIN}} \\ &= \frac{750\mu H \times 1.038A}{\sqrt{2} \times 90V} \\ &= 6.12\mu s \end{aligned}$$

Compute primary maximum RMS current  $I_{P\_RMS\_MAX}$

$$I_{P\_RMS\_MAX} \approx \sqrt{\frac{t'_1}{6t'_s}} \times I_{P\_PK\_MAX} = \sqrt{\frac{6.12\mu s}{6 \times 14.45\mu s}} \times 1.038A = 0.289A$$

(g) Compute secondary maximum peak current and the maximum RMS current.

$$I_{S\_PK\_MAX} = N_{PS} \times I_{P\_PK\_MAX} = 2.67 \times 1.038A = 2.77A$$

$$t'_2 = t'_s - t_1 - t_3 = 14.45\mu s - 6.12\mu s - 0.86\mu s = 7.47\mu s$$

$$I_{S\_RMS\_MAX} \approx \sqrt{\frac{t'_2}{6t'_s}} \times I_{S\_PK\_MAX} = \sqrt{\frac{7.47\mu s}{6 \times 14.45\mu s}} \times 2.77A = 0.81A$$

#3. Select power MOSFET and secondary power diode

Refer to Power Device Design

Known conditions at this step			
$V_{AC\_MAX}$	264V	$N_{PS}$	2.67
$V_{OUT}$	36V	$V_{D\_F}$	1V
$\Delta V_S$	50V	$\eta$	87%

(a) Compute the voltage and the current stress of MOSFET:

$$\begin{aligned} V_{MOS\_DS\_MAX} &= \sqrt{2}V_{AC\_MAX} + N_{PS} \times (V_{OUT} + V_{D\_F}) + \Delta V_S \\ &= \sqrt{2} \times 264V + 2.67 \times (38V + 1V) + 50V \\ &= 527V \end{aligned}$$

$$I_{MOS\_PK\_MAX} = I_{P\_PK\_MAX} = 1.038A$$

$$I_{MOS\_RMS\_MAX} = I_{P\_RMS\_MAX} = 0.289A$$

(b) Compute the voltage and the current stress of secondary power diode

$$\begin{aligned} V_{D\_R\_MAX} &= \frac{\sqrt{2}V_{AC\_MAX}}{N_{PS}} + V_{OUT} \\ &= \frac{\sqrt{2} \times 264V}{2.67} + 38V \\ &= 178V \end{aligned}$$

$$I_{D\_PK\_MAX} = N_{PS} \times I_{P\_PK\_MAX} = 2.67 \times 1.038A = 2.77A$$

$$I_{D\_AVG} = I_{OUT} = 0.32A$$

#4. Select the output capacitor  $C_{OUT}$

Refer to Power Device Design

Conditions			
$I_{OUT}$	320mA	$\Delta I_{OUT}$	$0.3I_{OUT}$
$f_{AC}$	50Hz	$R_{LED}$	$12 \times 1.6\Omega$

The output capacitor is

$$C_{OUT} = \frac{\sqrt{\left(\frac{2I_{OUT}}{\Delta I_{OUT}}\right)^2 - 1}}{4\pi f_{AC} R_{LED}}$$

$$= \frac{\sqrt{\left(\frac{2 \times 0.32A}{0.3 \times 0.32A}\right)^2 - 1}}{4\pi \times 50Hz \times 12 \times 1.6\Omega}$$

$$= 546\mu F$$

#5. Design RCD snubber

Refer to Power Device Design

Conditions			
$V_{OUT}$	38V	$\Delta V_S$	50V
$N_{PS}$	2.67	$L_K/L_M$	1%
$P_{OUT}$	12W		

The power loss of the snubber is

$$P_{RCD} = \frac{N_{PS} \times (V_{OUT} + V_{D.F}) + \Delta V_S}{\Delta V_S} \times \frac{L_K}{L_M} \times P_{OUT}$$

$$= \frac{2.67 \times (38V + 1V) + 50V}{50V} \times 0.01 \times 12W$$

$$= 0.37W$$

The resistor of the snubber is

$$R_{RCD} = \frac{(N_{PS} \times (V_{OUT} + V_{D.F}) + \Delta V_S)^2}{P_{RCD}}$$

$$= \frac{(2.67 \times (38V + 1V) + 50V)^2}{0.37W}$$

$$= 64k\Omega$$

The capacitor of the snubber is

$$C_{RCD} = \frac{N_{PS} \times (V_{OUT} + V_{D,F}) + \Delta V_S}{R_{RCD} f_s \Delta V_{C,RCD}}$$

$$= \frac{2.67 \times (38V + 1V) + 50V}{64k\Omega \times 100kHz \times 25V}$$

$$= 1nF$$

#6. Set VIN pin

Refer to Start up

Conditions			
V <sub>BUS-MIN</sub>	90V × 1.414	V <sub>BUS-MAX</sub>	264V × 1.414
I <sub>ST</sub>	15μA (typical)	V <sub>IN-ON</sub>	16V (typical)
I <sub>VIN-OVP</sub>	2mA (typical)	t <sub>ST</sub>	500ms (designed by user)

(a) R<sub>ST</sub> is preset

$$R_{ST} < \frac{V_{BUS}}{I_{ST}} = \frac{90V \times 1.414}{15\mu A} = 8.48M\Omega,$$

$$R_{ST} > \frac{V_{BUS}}{I_{VIN\_OVP}} = \frac{264V \times 1.414}{2mA} = 186k\Omega$$

Set R<sub>ST</sub>

$$R_{ST} = 250k\Omega \times 3 = 750k\Omega$$

(b) Design C<sub>VIN</sub>

$$C_{VIN} = \frac{\left(\frac{V_{BUS}}{R_{ST}} - I_{ST}\right) \times t_{ST}}{V_{VIN\_ON}}$$

$$= \frac{\left(\frac{90V \times 1.414}{750k\Omega} - 15\mu A\right) \times 500ms}{16V}$$

$$= 4.83\mu F$$

Set C<sub>VIN</sub>

$$C_{VIN} = 20\mu F$$

#7 Set COMP pin

Refer to **Internal pre-charge design for quick start up**

Parameters designed			
R <sub>COMP</sub>	500Ω	V <sub>COMP,IC</sub>	450mV





# SY5800A

---

C <sub>COMP1</sub>	2 $\mu$ F	C <sub>COMP2</sub>	100pF
--------------------	-----------	--------------------	-------

*Silergy Corp Confidential Prepared for Keysky*

#8 Set current sense resistor to achieve ideal output current

Refer to **Primary-side constant-current control**

Known conditions at this step			
$k_1 \times k_2$	0.16	$N_{PS}$	2.67
$V_{REF}$	0.3V	$I_{OUT}$	0.32A

The current sense resistor is

$$R_S = \frac{k_1 \times k_2 \times V_{REF} \times N_{PS}}{I_{OUT}}$$

$$= \frac{0.16 \times 0.3V \times 2.67}{0.32A}$$

$$= 0.4\Omega$$

#9 set ZCS pin

Refer to **Line regulation modification** and **Over Voltage Protection (OVP) & Open Loop Protection (OLP)**

First identify  $R_{ZCSU}$  need for line regulation.

Known conditions at this step			
$k_3$	68		
Parameters Designed			
$R_{ZCSU}$	100k $\Omega$		

Then compute  $R_{ZCSD}$

Conditions			
$V_{ZCS\_OVP}$	1.42V	$V_{OVP}$	48V
$V_{OUT}$	38V		
Parameters designed			
$R_{ZCSU}$	100k $\Omega$		
$N_S$	21	$N_{AUX}$	5

$$R_{ZCSD} < \frac{\frac{V_{ZCS\_OVP}}{V_{OUT}} \times \frac{N_S}{N_{AUX}}}{1 - \frac{V_{ZCS\_OVP}}{V_{OUT}} \times \frac{N_S}{N_{AUX}}} \times R_{ZCSU}$$

$$= \frac{\frac{1.42V}{38V} \times \frac{21}{6}}{1 - \frac{1.42V}{38V} \times \frac{21}{6}} \times 100k\Omega$$

$$= 18.62k\Omega$$

$$R_{ZCSD} \geq \frac{\frac{V_{ZCS\_OVP}}{V_{OVP}} \times \frac{N_s}{N_{AUX}}}{1 - \frac{V_{ZCS\_OVP}}{V_{OVP}} \times \frac{N_s}{N_{AUX}}} \times R_{ZCSU}$$


$$= \frac{1.42V}{48V} \times \frac{21}{5} \times 100k\Omega$$

$$= 14.19k\Omega$$


$R_{ZCSD}$  is set to

$$R_{ZCSD} = 15k\Omega$$


#10 final result

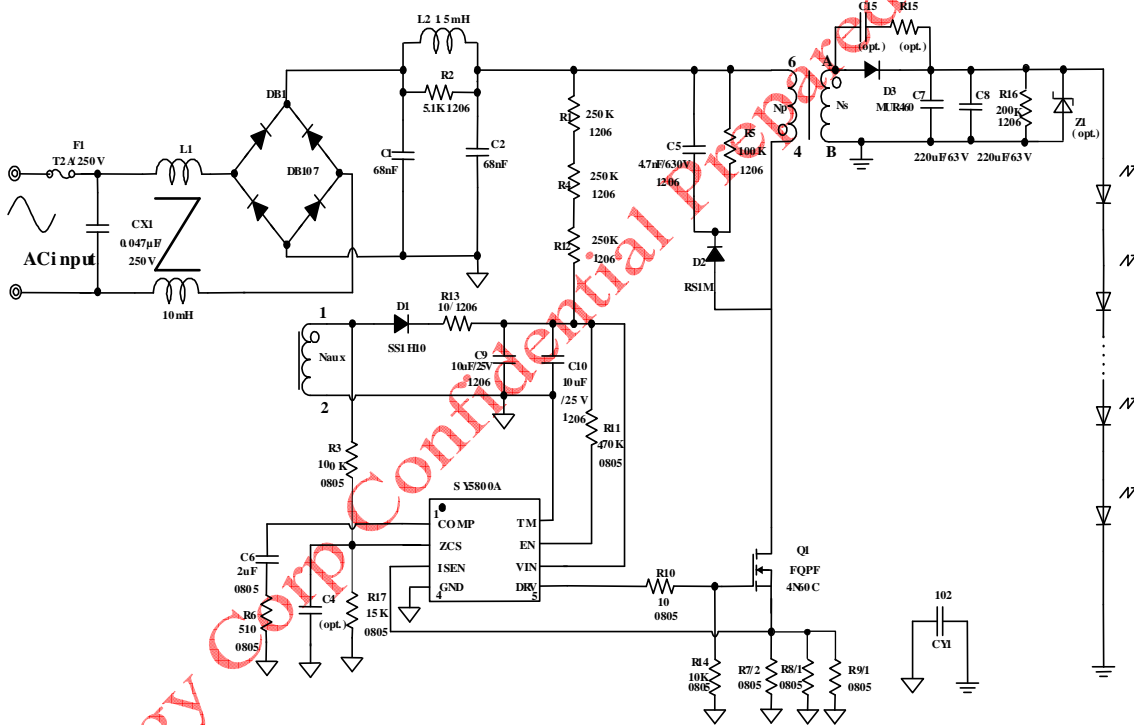

**MSOP10 Package outline & PCB layout**

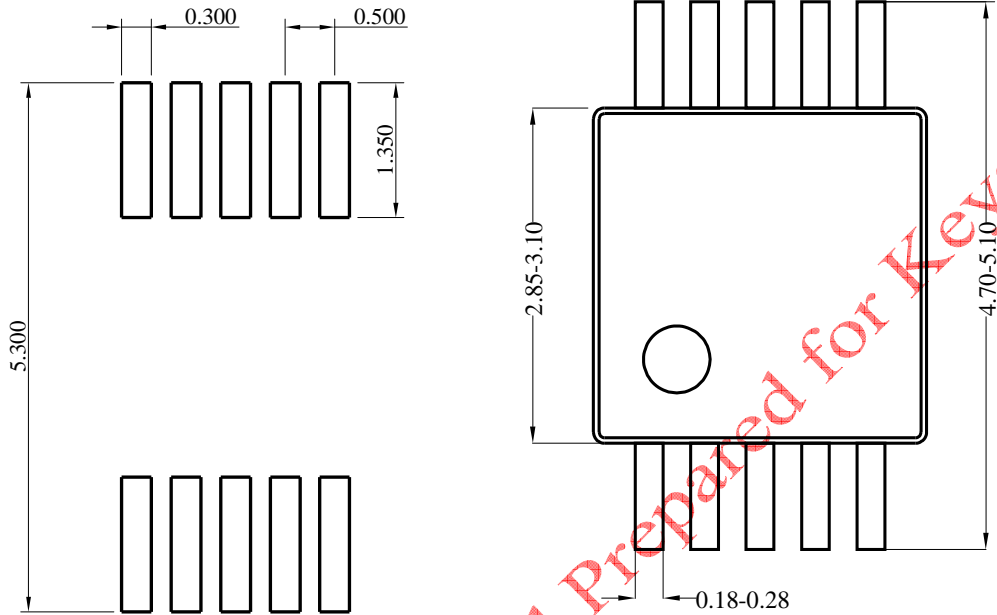


**Recommended Pad Layout**

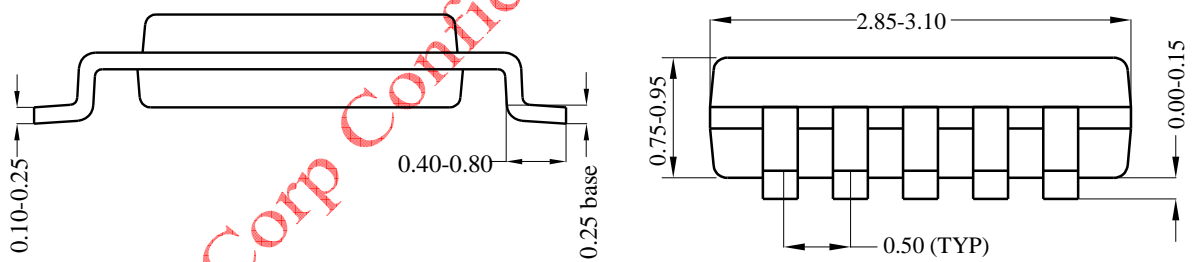


**Notes: All dimension in MM**  
**All dimension do not include mold flash & metal burr**

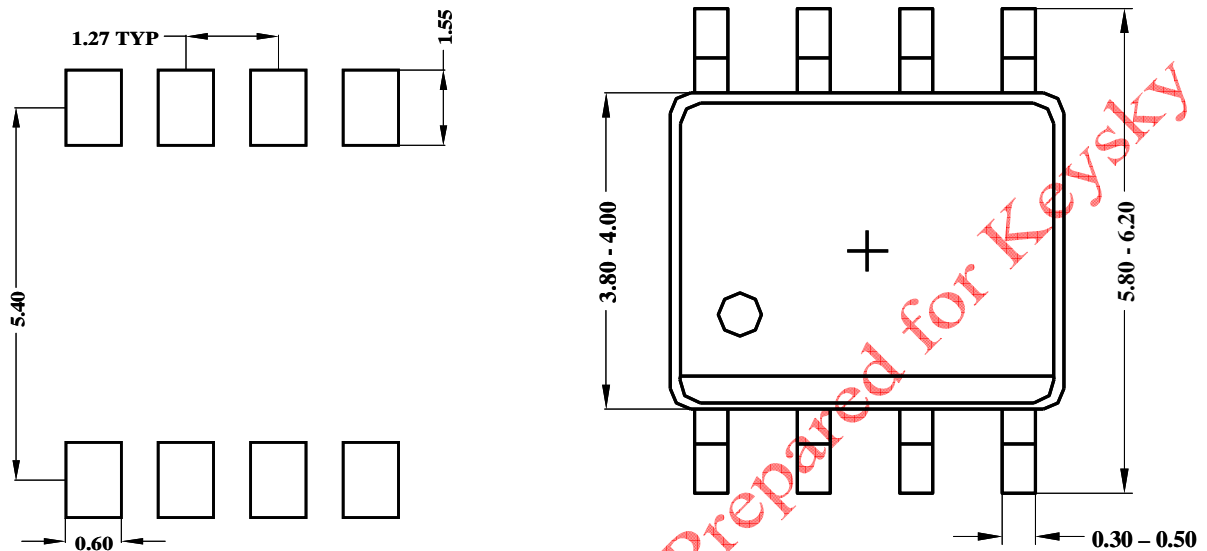**SO8 Package Outline & PCB Layout Design**



**Recommended Pad Layout**

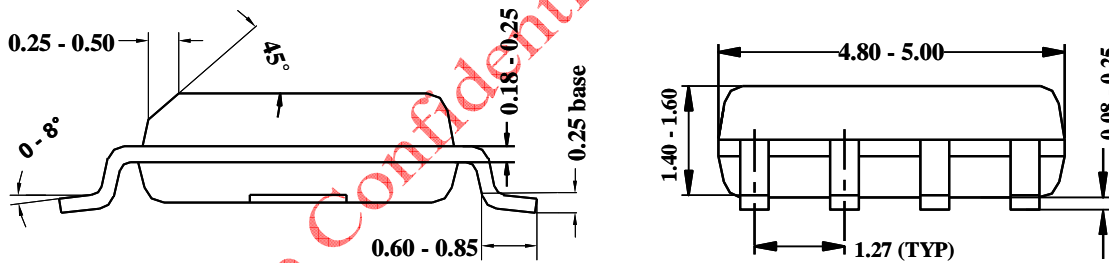

**Notes: All dimensions are in millimeters.  
All dimensions don't include mold flash & metal burr.**