

PRACTICAL SWITCHING POWER SUPPLY DESIGN

Marty Brown




MOTOROLA

Series in Solid State Electronics

Practical Switching Power Supply Design

Marty Brown
Motorola Semiconductor

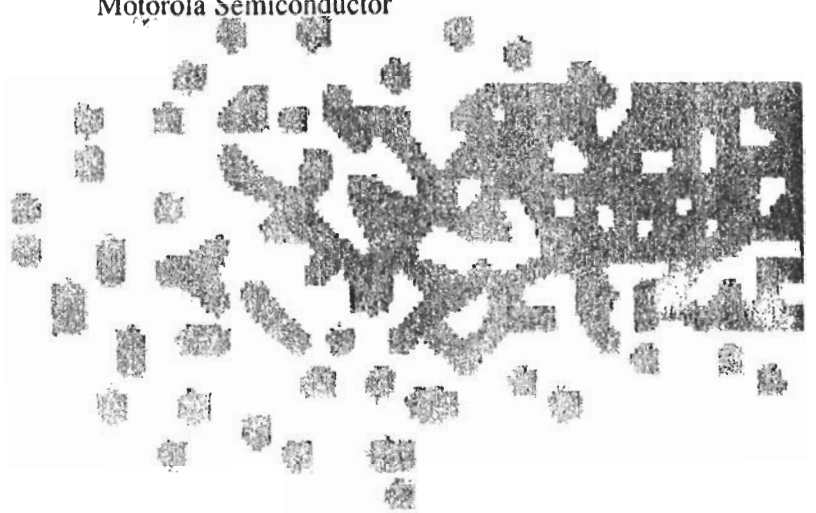

MOTOROLA
Series in Solid State Electronics

Practical Switching Power Supply Design



ACADEMIC PRESS, INC.

A Division of Harcourt Brace & Company

San Diego New York Boston London Sydney Tokyo Toronto

Motorola reserves the right to make changes without further notice to any products herein to improve reliability, function or design. Motorola does not assume any liability arising out of the application or use of any product or circuit described herein; neither does it convey any license under its patent rights nor the rights of others. Motorola products are not authorized for use as components in life support devices or systems intended for surgical implant into the body or intended to support or sustain life. Buyer agrees to notify Motorola of any such intended end use whereupon Motorola shall determine availability and suitability of its product or products for the use intended. Motorola and [™] are registered trademarks of Motorola, Inc. Motorola, Inc. is an Equal Employment Opportunity/Affirmative Action Employer.

This book is printed on acid-free paper. (∞)

Copyright © 1990 by Academic Press

All Rights Reserved.

No part of this publication may be reproduced or transmitted in any form or by any means, electronic or mechanical, including photocopy, recording, or any information storage and retrieval system, without permission in writing from the publisher.

Academic Press

A Harcourt Science and Technology Company
525 B Street, Suite 1900, San Diego, California 92101-4495, USA
<http://www.apnet.com>

Academic Press

Harcourt Place, 32 Jamestown Road, London NW1 7BY, UK
<http://www.hbuk.co.uk/ap/>

Library of Congress Cataloging-in-Publication Data

Brown, Marty.

Practical switching power supply design / Marty Brown.

p. cm.

ISBN 0-12-137030-5 (alk. paper)

1. Switching circuits--Design and construction. 2. Power semiconductors--Design and construction. 3. Semiconductor switches--

-Design and construction. I. Title.

TK7868.S9B66 1990

621.381'5--dc20

89-17518
CIP

Printed In The United States Of America

01 02 03 IBT 11 10 9 8 7

Contents

Preface ix

CHAPTER 1

Why Use Switching Power Supplies? 1

CHAPTER 2

How a Switching Power Supply Works 5

2.1 Forward-Mode Switching Regulators 5

2.2 Flyback-Mode Switching Regulators 7

CHAPTER 3

A Walk through a Representative Switching Power Supply 9

3.1 The EMI Filter 9

3.2 Bulk Input Filter (Storage) Capacitor 9

3.3 Transformer 11

3.4 Power Switches 12

3.5 Output Rectifiers 12

3.6 The Output Filter Section 12

3.7 Current Sense Elements 13

3.8 Voltage Feedback Elements 13

3.9 The Control Section 14

CHAPTER 4

Switching Power Supply Topologies 17

4.1 Factors Affecting the Choice of an Appropriate Topology 17

4.2 Non-Transformer-Isolated Switching Power Supply Topologies 20

4.2.1	The Buck Regulator Topology	20
4.2.2	The Boost Regulator Topology	24
4.2.3	The Buck–Boost Regulator Topology	26
4.3	Transformer-Isolated Switching Power Supply Topologies	29
4.3.1	The Flyback Regulator Topology	29
4.3.2	The Push–Pull Regulator Topology	34
4.3.3	The Half-Bridge Regulator Topology	38
4.3.4	The Full-Bridge Regulator Configuration	40

CHAPTER 5

Semiconductors Used in a Switching Power Supply 43

5.1	Bipolar Power Transistors	43
5.2	Power MOSFETs	50
5.3	Rectifiers	56
5.4	Switching Power Supply Control Integrated Circuits	58
5.4.1	Voltage-Mode Control	60
5.4.2	Current-Mode Control	61
5.4.3	Quasi-Resonant-Mode Control	63

CHAPTER 6

The Magnetic Components within a Switching Power Supply 67

6.1	Basic Magnetism and Ferromagnetism	68
6.2	The Forward-Mode Transformer	76
6.3	The Flyback Transformer	83
6.4	The Forward-Mode Filter Choke	90
6.5	Mutually Coupled Forward-Mode Filter Inductors	94

CHAPTER 7

Cross-Regulation of the Outputs 97

7.1	Transformer Techniques	99
7.2	The Voltage-Sensing Network	99
7.3	Mutually Coupled Output Filter Chokes	100

CHAPTER 8

Protection 103

8.1	Protecting the Supply and the Load from the Input Line	103
8.1.1	AC Line Input Adverse Operating Conditions	104
8.1.2	DC Line Input Adverse Operating Conditions	105

8.2	Protecting the Load from the Supply and Itself	107
8.2.1	Hardware Implementations to Address Overvoltage	109
8.2.2	Hardware Implementations to Address Overcurrent	111

CHAPTER 9

Miscellaneous Topics 115

9.1	Power Supply and System Grounds	115
9.2	The Use and Design of Clamps and Snubbers	119
9.3	RFI and EMI Design Considerations	125
9.4	Power Supply and Product Safety Considerations	128
9.5	Testing Power Supply Units	132
9.5.1	Line Regulation	132
9.5.2	Load Regulation	133
9.5.3	Dynamic Load Response Time	133
9.5.4	Dielectric Withstanding Voltage	135
9.5.5	Holdup Time	137
9.5.6	Overcurrent Limit Test	138

CHAPTER 10

Closing the Loop—Feedback and Stability 141

10.1	The Bode Plot as a Basic Tool	141
10.2	Closing the Loop	145
10.3	The Stability Criteria Applied to Power Supplies	146
10.4	The Control-to-Output Transfer Functions of Common Switching Power Supply Topologies	148
10.4.1	Forward-Mode Control-to-Output Transfer Functions (Voltage-Mode Control)	149
10.4.2	Flyback-Mode and Current-Mode Controlled Forward Converters	151
10.5	Common Error Amplifier Compensation Techniques	154
10.5.1	Single-Pole Compensation	155
10.5.2	Zero-Pole Pair Compensation	158
10.5.3	Two-Pole–Two-Zero Compensation	162
10.6	Attempting to Compensate for a Right-Half-Plane Zero	167

CHAPTER 11

Resonant Converters—An Introduction 169

11.1	Why Resonant Switching Power Supplies?	170
11.2	Basic Quasi-Resonant Converter Operation	172
11.3	The Resonant Switch—A Method of Creating a Quasi-Resonant Family	178

11.4	The Zero-Voltage Quasi-Resonant Converter Family	181
11.5	Second-Side Resonance	186
11.6	Effects of Parasitic Elements within High-Frequency Supplies	189
11.6.1	Transformer- and Inductor-Centered Parasitic Effects	190
11.6.2	Layout- and Component-Dependent Parasitic Losses	193
CHAPTER 12		
	Switching Power Supply Design Examples	199
12.1	A Low-Cost, Low-Power Flyback Converter	199
12.2	A 100-kHz, 50-W, Off-Line, Half-Bridge Switching Power Supply	209
12.3	A 50-W, Parallel Resonant, Half-Bridge, Quasi-Resonant Converter	220
12.4	A 60-W, Off-Line Flyback Converter with Battery Backup	227
	Bibliography	235
	Index	237